

Homework 7

ECE 5/411 – CMOS Analog IC Design (Spring 2014)

Due on Thursday, April 10, 2014.

Note:

1. Use Cadence schematic capture, layout and Spectre simulation tools, available on the AMS servers for the homework problems.
2. Use the $1\mu\text{m}$ CMOS parameters from Table 1 posted on the site, along with the corresponding Spectre models.

Problem 1: Understand Examples 21.6-21.10 in the CMOS Textbook. Fig. 1 shows amplifier circuits with wide-swing cascoded bias voltages (V_{bias1} to V_{bias4}) generated for the current and overdrive parameters from Table 1. For each of these amplifiers

(a) Determine the frequency response (perform symbolic as well as numerical calculations for DC gain and pole-zero locations, and provide hand-sketched Bode magnitude and phase responses)

(b) Estimate the unity-gain frequency (f_{un}), gain and phase margins for the amplifiers.

(c) Create circuit schematics and verify your calculations with Spectre simulations.

Extra: Use/modify the provided MATLAB scripts (e.g. *CommonSourceFreqResp1.m* or *TwoStageFreqResp1.m*) to generate frequency response and pole-zero plots to augment your understanding.

Problem 2: Read Section 6.3 in the Analog CMOS IC Textbook. Figure 2 shows a source follower (SF) designed using parameters from Table 1.

(a) Determine the frequency response for Fig. 2 (a). Create circuit schematics and verify your calculations with Spectre simulations.

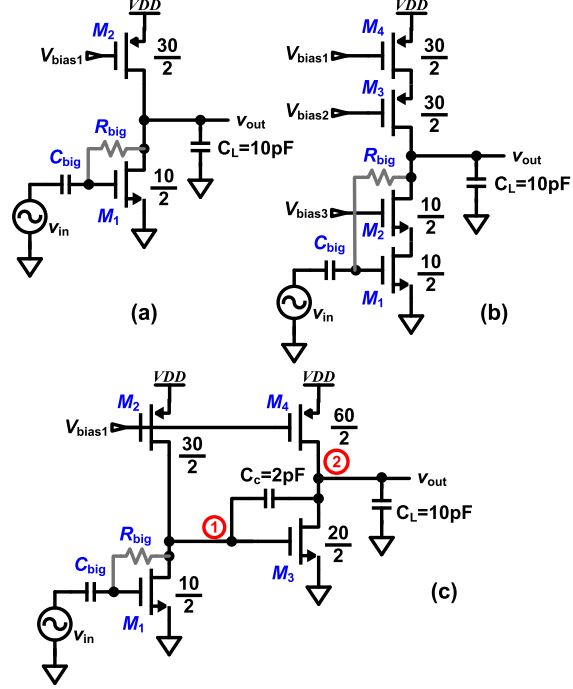


Figure 1

(b) Assuming $R_s = 0$, derive the input AC impedance Z_{in} of the SF. Show that the overall input capacitance contributed by M_1 is the sum of C_{gd1} and a fraction of C_{gs1} . Plot $|Z_{in}(f)|$ using Spectre and verify your results.

(c) Figure 2 (b) shows the SF driving a large load with a pulsed source. It can be shown that the equivalent output impedance of the SF can be expressed as an inductive combination $Z_{out} = (sL || R_1) + R_2$. Here, $R_2 = \frac{1}{g_{m1}}$, $R_1 = R_s - \frac{1}{g_{m1}}$ and $L = \frac{C_{gs1}}{g_{m1}} \left(R_s - \frac{1}{g_{m1}} \right)$. This property is commonly used to realize active inductors on chip. Using Spectre, plot $|Z_{out}(f)|$ for the cases including $R_s \gg \frac{1}{g_{m1}}$ and $R_s \ll \frac{1}{g_{m1}}$ to demonstrate this behavior.

(d) In Figure 2 (b), use a 10 MHz clock source as the input to the SF, and plot output response for $R_s = 0, 50, 1k, \text{ and } 10k$.

Explain your observations.

 


Figure 2

Problem 3: Figure 3 (a) shows the canonical model discussed in class for a two-stage amplifier with Miller compensation (i.e. pole-splitting). Use values: $g_{m1} = 20 \frac{\mu A}{V}$, $R_1 = 4M\Omega$, $g_{m2} = 80 \frac{\mu A}{V}$, $R_2 = 0.5M\Omega$, $C_{in} = 10fF$, $C_1 = 40fF$, $C_C = 250fF$, $C_L = 1pF$, $R_z = 12.5k\Omega$. Suitably modify the MATLAB file *TwoStage-FreqResp1.m* for the individual parts of this problem.

(a) Determine the poles and zeros of the open-loop transfer function $\frac{v_{out}}{v_{in}}(s)$ -calculate the transfer function symbolically and then numerically. Show the pole-zero plot, Bode magnitude and phase response and determine A_v , f_{un} and ϕ_M .

(b) Using the method used in class, show that the zero location in the amplifier without zero-nulling resistor R_z is given by $\omega_z = \frac{g_{m2}}{C_C}$. Similarly, derive the expression for the zero location when a zero-nulling resistor R_z is added in series with C_C . Using the MATLAB script demonstrate pole-splitting (root locus for varying C_C) with zero-nulling with this script.

(c) The circuits in Fig. 3 (b, c) are modified versions of the two-stage Miller compensated amplifier. Calculate their transfer functions and compare them with that of the conventional structure. Explain the difference with results.

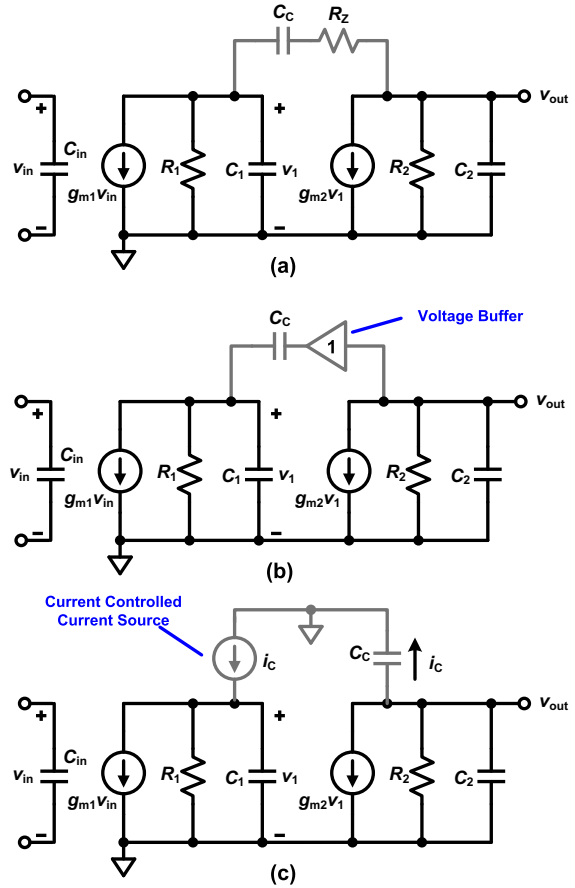


Figure 3