



# Opamp Design Project

## Help Session

Boise, 19/Apr/2014

 
Vishal Saxena



Table 1: Opamp design specifications.


Parameter	Specified Value
Technology	TSMC 180n CMOS
Supply voltage, $V_{DD}$	1.8 V
Typical load	$100k\Omega    2pF$
Unit gain frequency ( $f_{un}$ )	$> 50 MHz$ for ECE 411
	$> 200 MHz$ for ECE 511
Open-loop gain ( $A_{OL}$ )	$> 75 dB$
Slew-rate ( $SR$ )	$> 500 \frac{V}{\mu s}$
Phase margin ( $\phi_M$ )	$\gtrsim 63^\circ$
Power consumption	Minimum possible
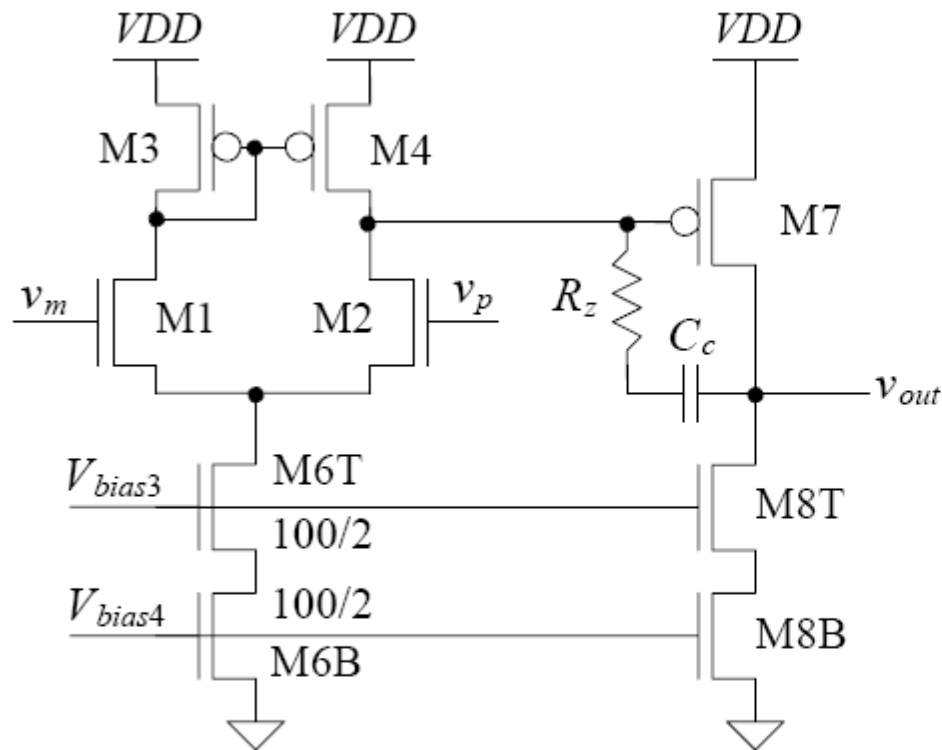
# Two-Stage Opamp

 


**Figure 24.1** Block diagram of two-stage op-amp with output buffer.

# Two-Stage Opamp




Parameters from Table 9.2  
with biasing circuit from  
Fig. 20.47. Unlabeled NMOS  
are 50/2 and PMOS are 100/2.  
Scale factor is 50 nm.



Op-amp schematic symbol

**Figure 24.2** Basic two-stage op-amp.

# Design Equations

 

$$A_v = g_{m1}R_1g_{m2}R_2$$


$$\omega_{p1} \approx \frac{1}{g_{m2}R_2R_1C_c}$$

$$\omega_{p2} \approx \frac{g_{m2}C_c}{C_2(C_1+C_c)+C_cC_1} = f\left(\frac{g_{m2}}{C_2}\right)$$


$$\omega_z \approx \frac{g_{m2}}{C_c}$$

$$\omega_{un} \approx \frac{g_{m1}}{C_c}$$
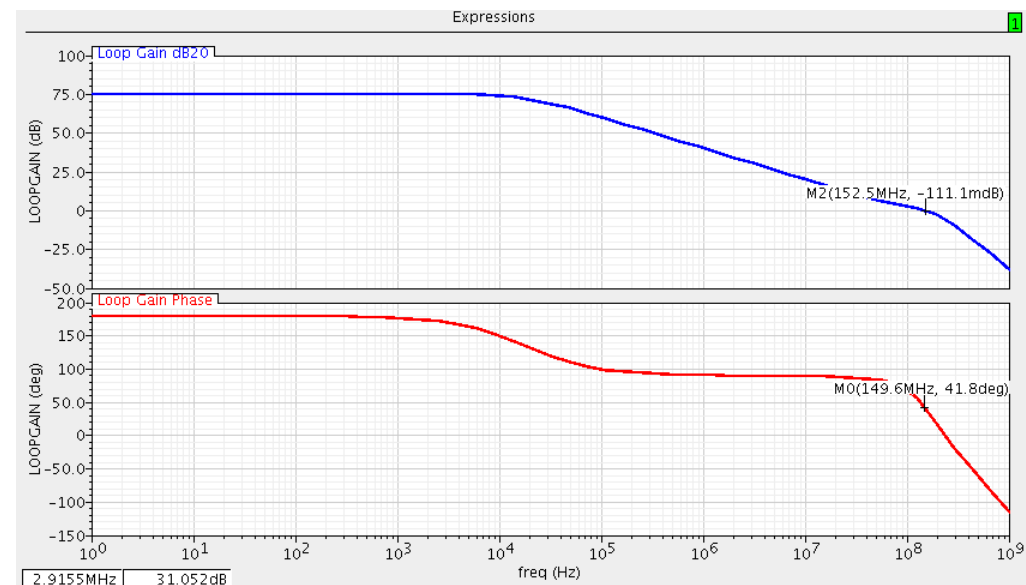
$$\omega_{z,nulling-R} \approx \frac{1}{\left(\frac{1}{g_{m2}-R_z}\right)C_c}$$




# Two-Stage Opamp –Zero-Nulling R

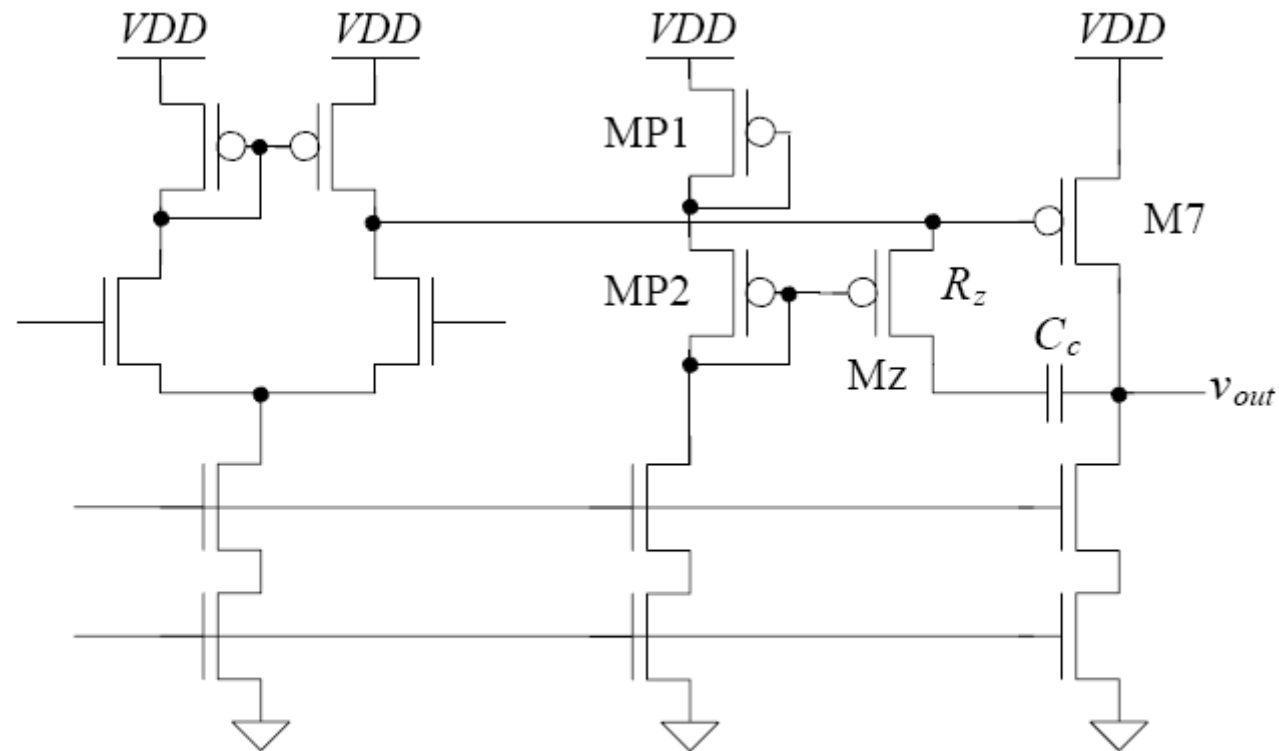


**Figure 24.15** Making the zero-nulling resistor process independent.

# Two-Stage Opamp –Voltage Buffer Compensation

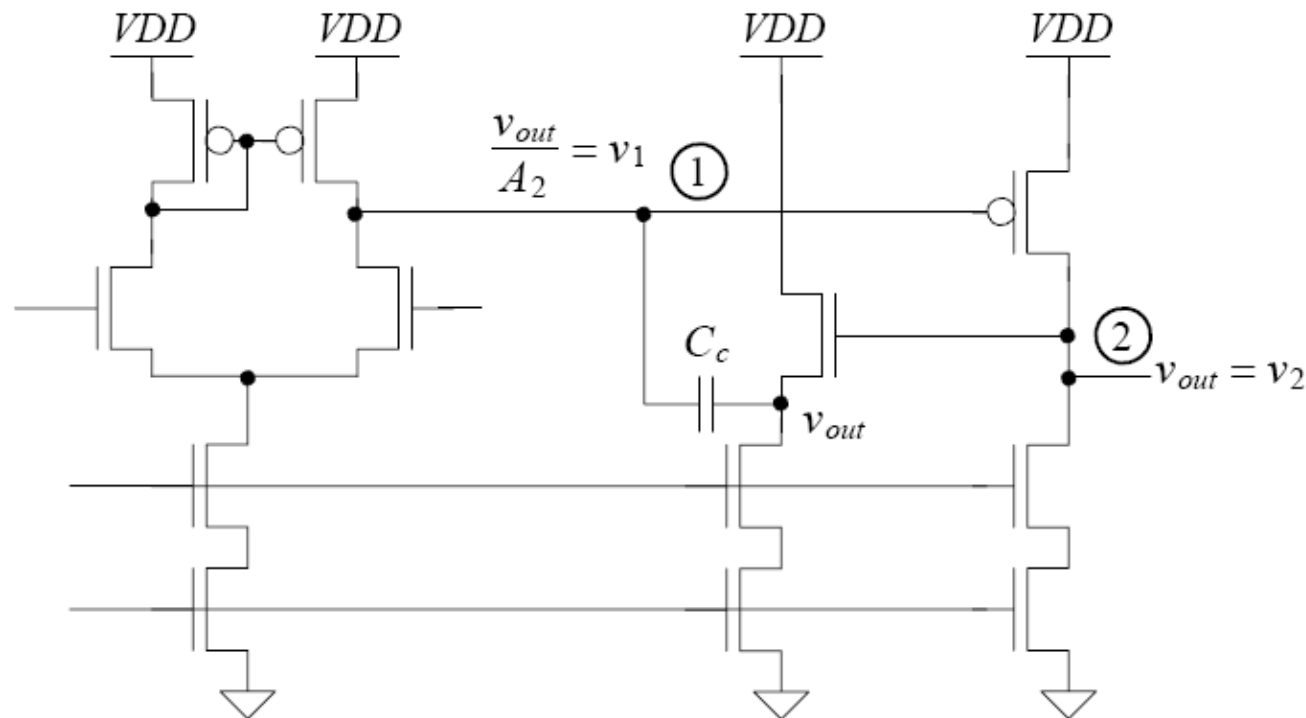

**Figure 24.16** Using an amplifier to eliminate forward signal feedthrough via the compensation capacitor.


# Two-Stage Opamp –Common Gate Compensation

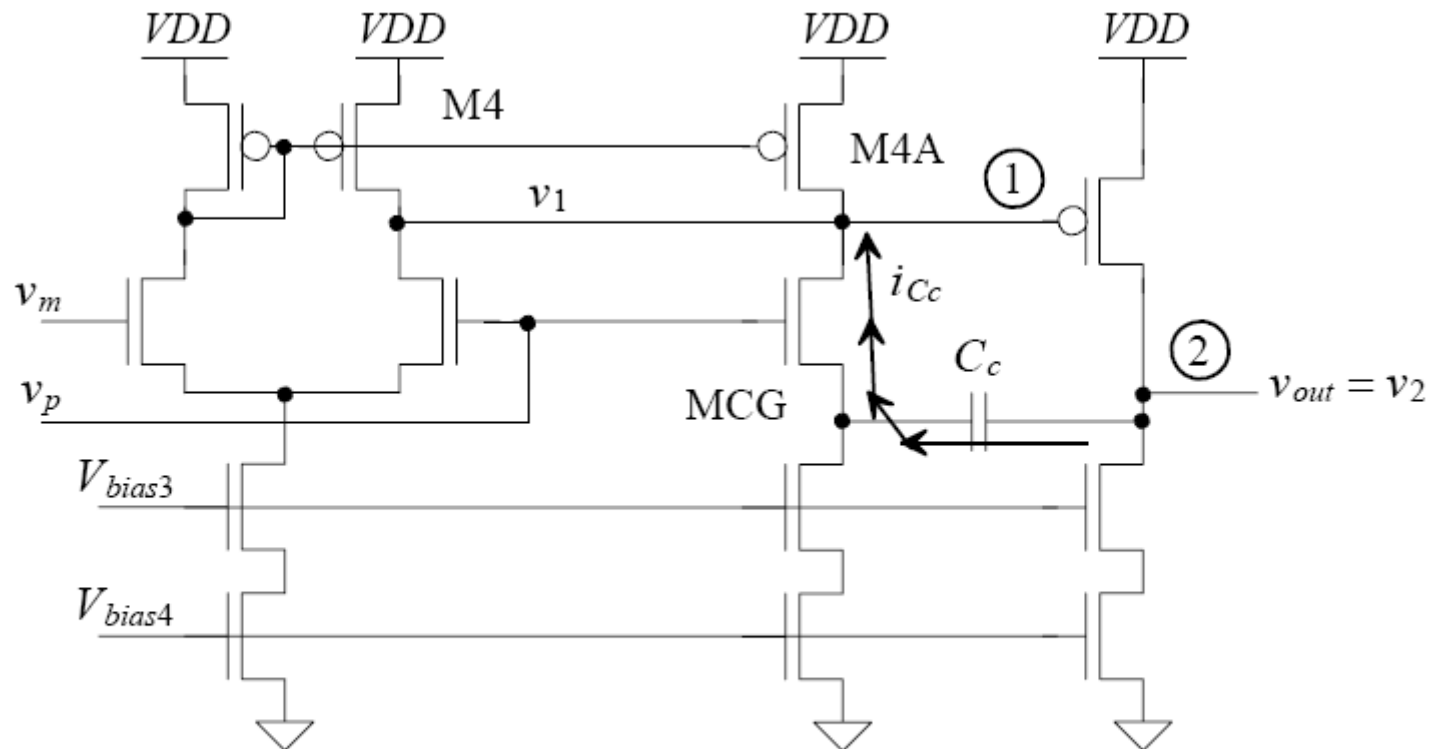


**Figure 24.17** Feeding back a current indirectly to avoid the RHP zero.



# Class-A Stage: Slewing

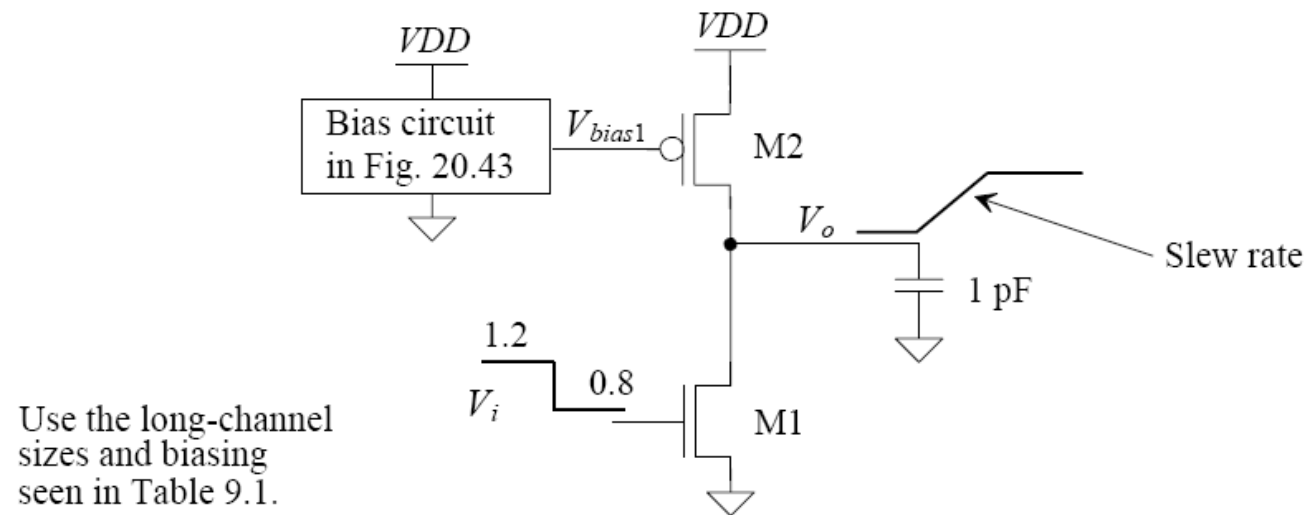


**Figure 21.18** Slew rate limitations in a class A amplifier.

 

**Figure 21.19** Verifying the results in Ex. 21.5
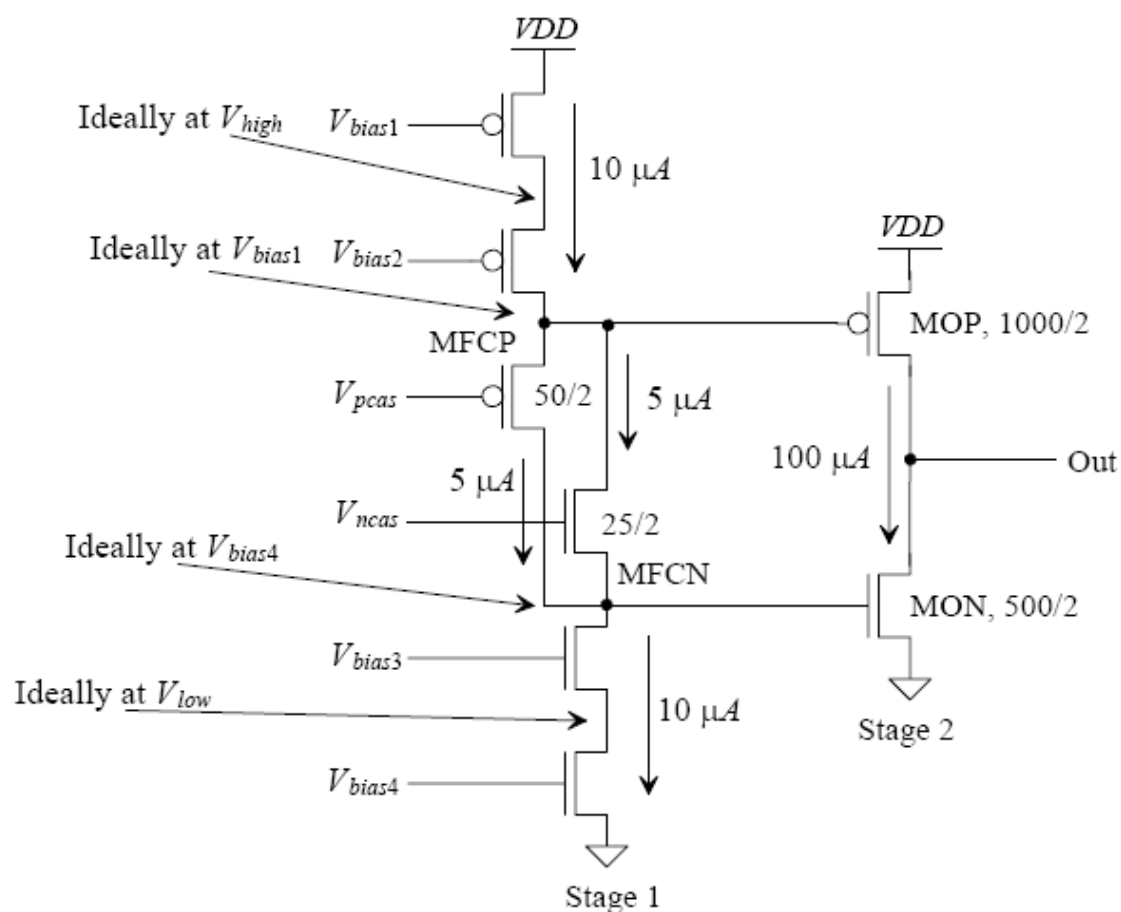
# Class-AB Stage: Floating Current Mirror



Bias voltages come from Fig. 20.47 (short-channel parameters in Table 9.2).  
Unlabeled NMOS are 50/2, while unlabeled PMOS are 100/2.

**Figure 20.49** Biasing with a floating current source.

# Two-Stage Opamp –Telescopic with Class-AB Stage


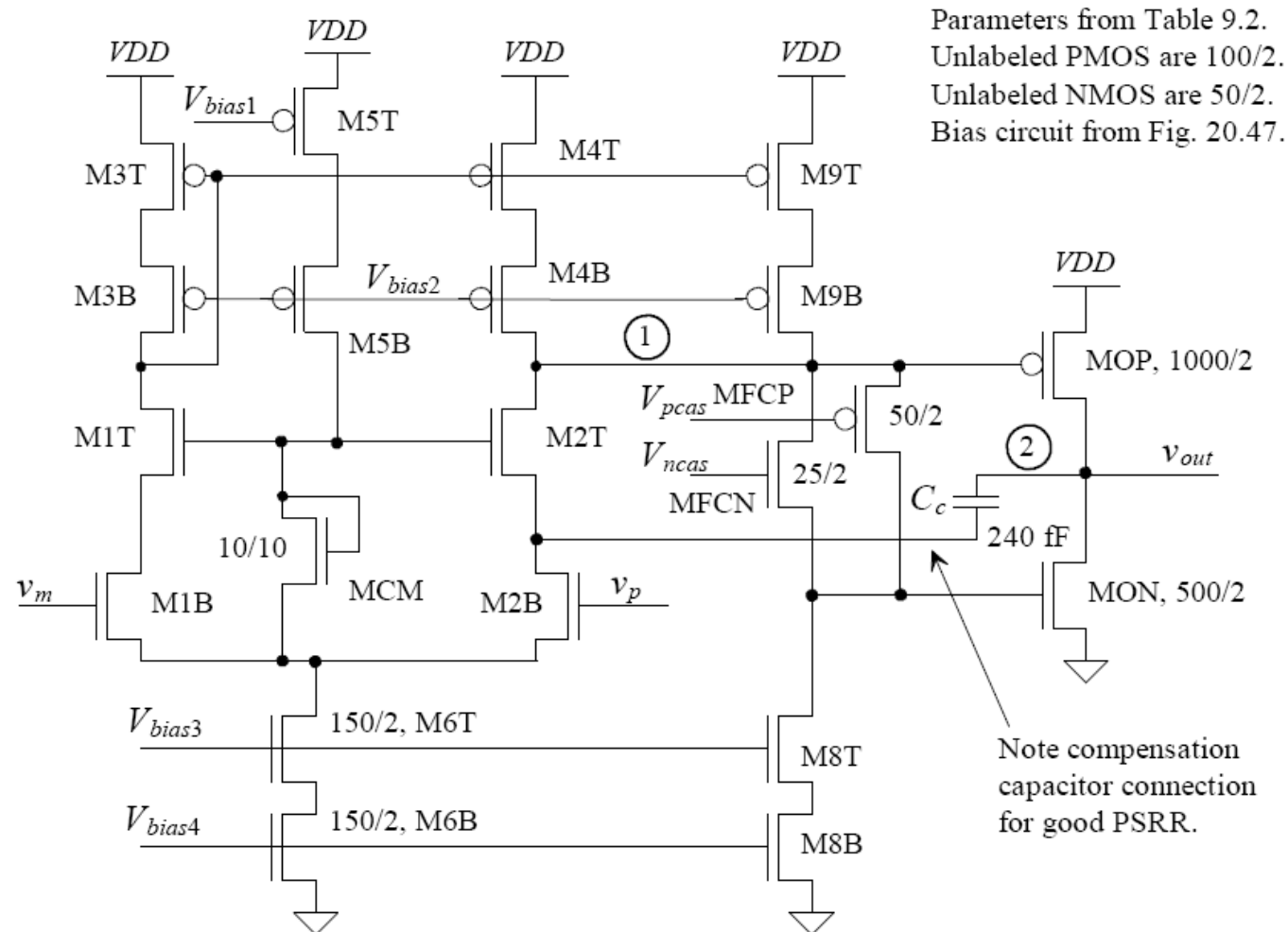



Figure 24.29 A CMOS op-amp with output buffer.

# Folded Cascode OTA

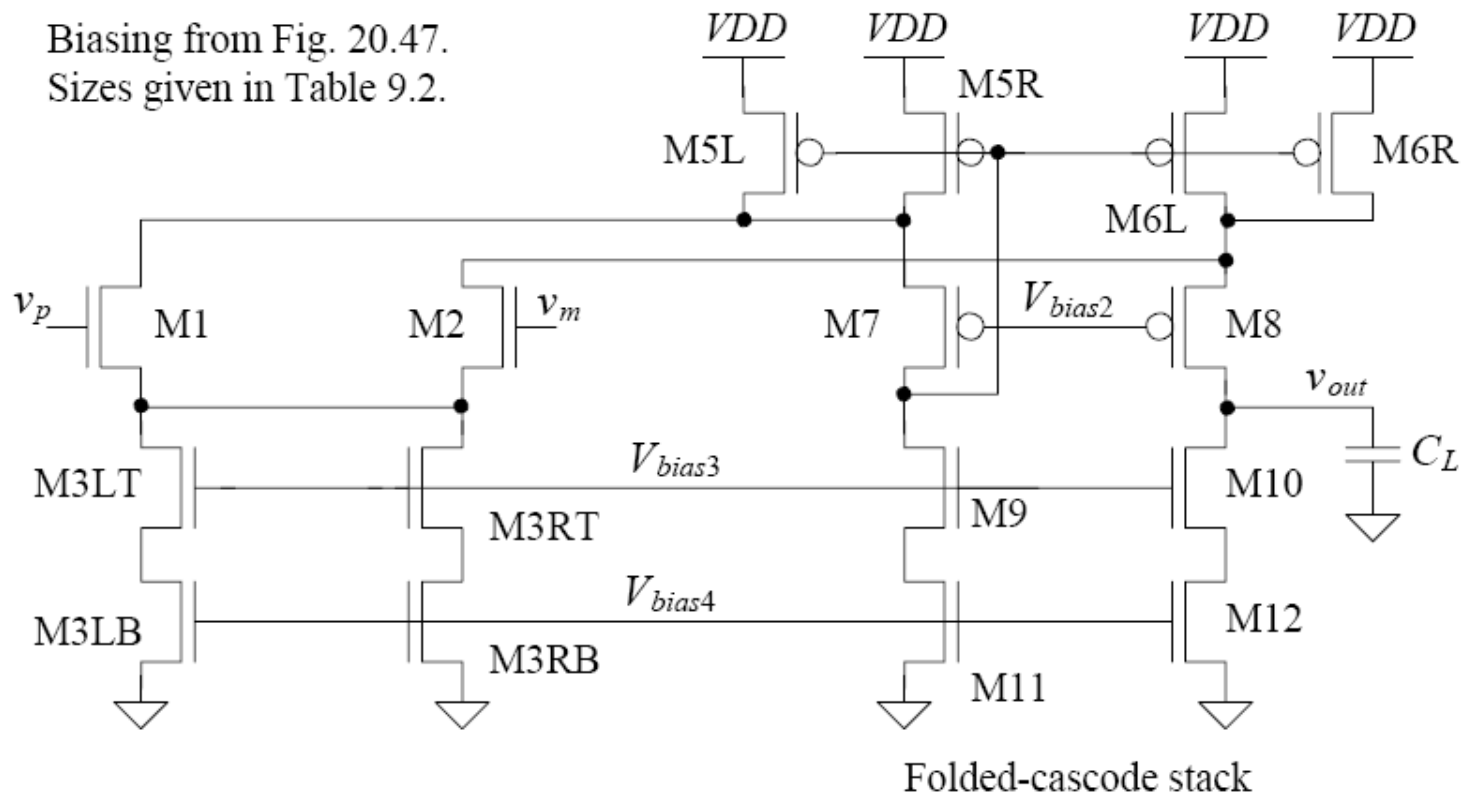


**Figure 24.42** A folded-cascode OTA.

# Two-Stage Opamp –Folded-Cascode with Class-AB Stage

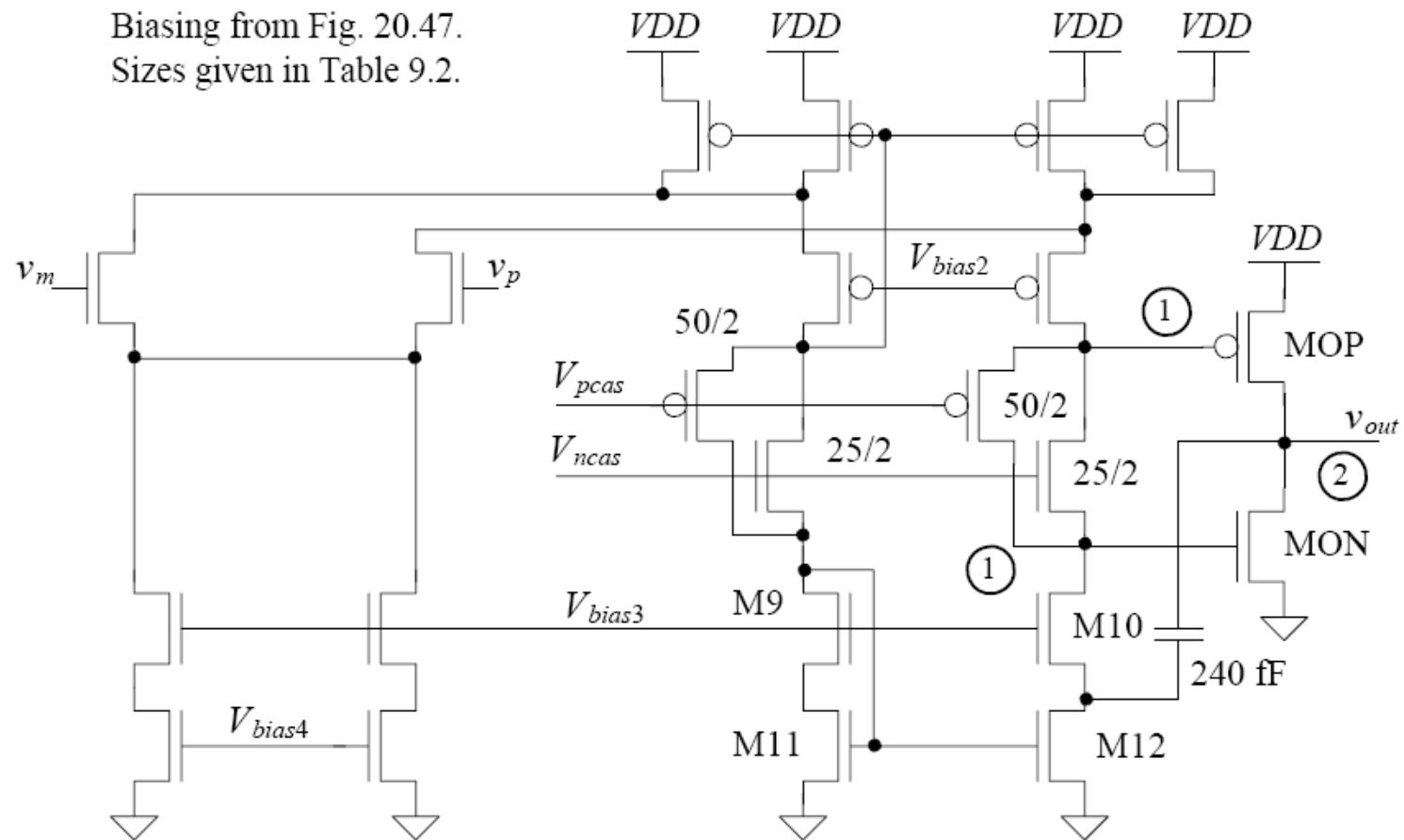

**Figure 24.44** Folded-cascode op-amp with class AB output buffer.
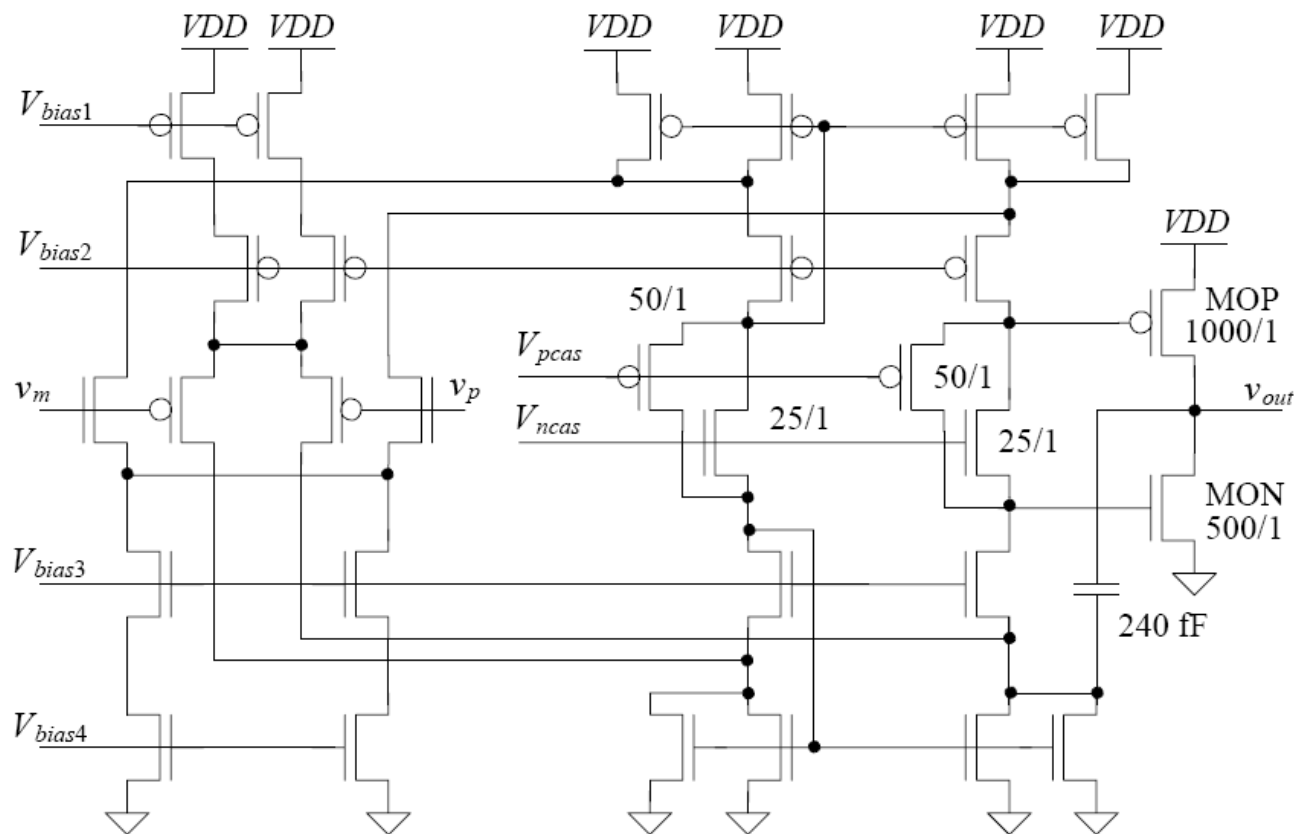
# Two-Stage Opamp –Folded-Cascode + Class-AB Stage, Full-rail input CMR




Biasing from Fig. 20.47.  
Unlabeled NMOS are 50/1.  
Unlabeled PMOS are 100/1.

**Figure 24.48** An op-amp with an input common-mode range that extends beyond the power supply rails and that can drive heavy loads.

# Two-Stage Opamp –Gain Enhancement

Biassing using Fig. 20.47.  
Unlabeled NMOS are 50/1.  
Unlabeled PMOS are 100/1.

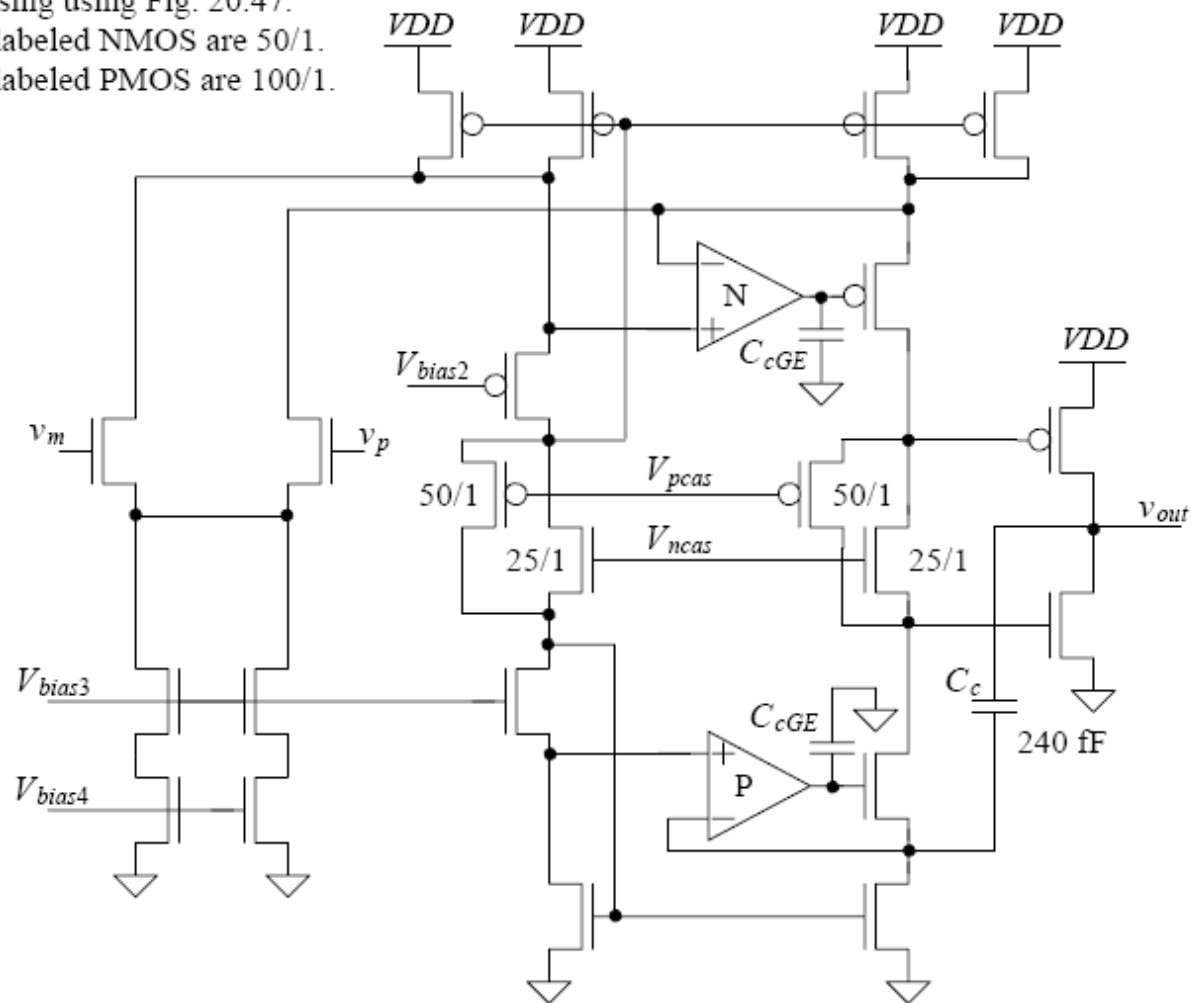

**Figure 24.51** Folded-cascode op-amp with class AB output buffer and gain-enhancement.

# Two-Stage Opamp –AC Response

 


Figure 24.9 Circuit configuration used to simulate open-loop frequency response.

## Caveat:

- Don't use this method.
- Use STB analysis with *iprobe* instead.


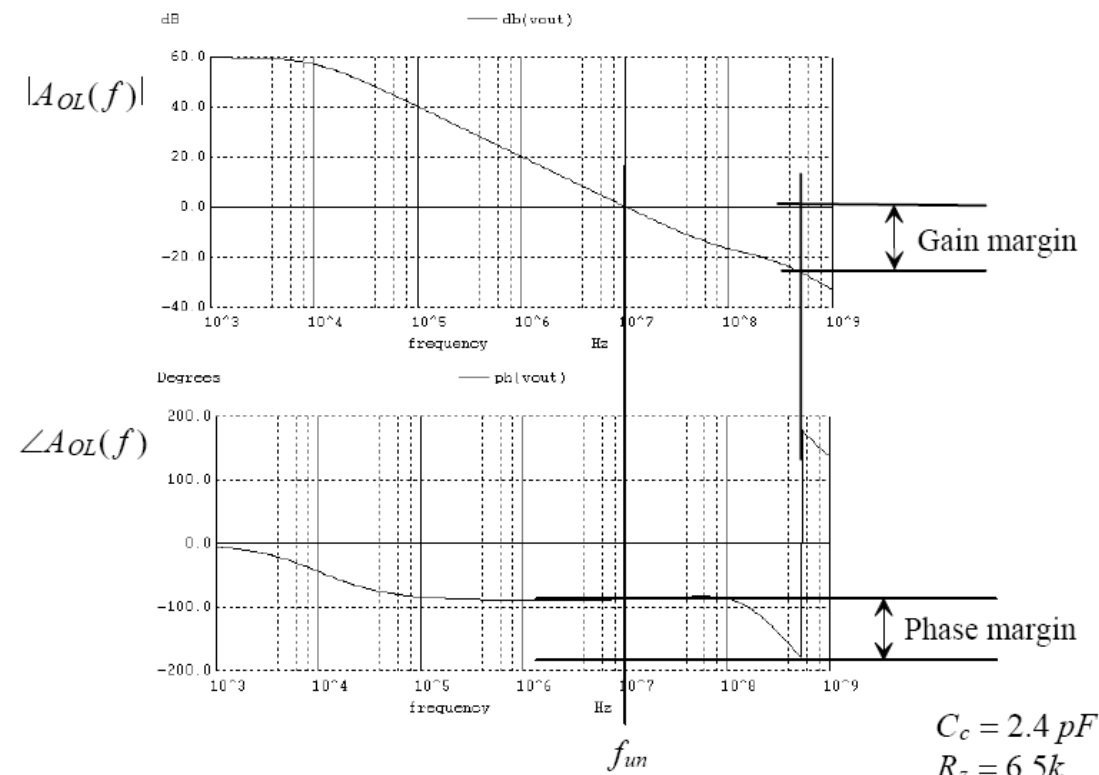


Figure 24.13 Adding a zero nulling resistor to the op-amp in Fig. 24.8.

 

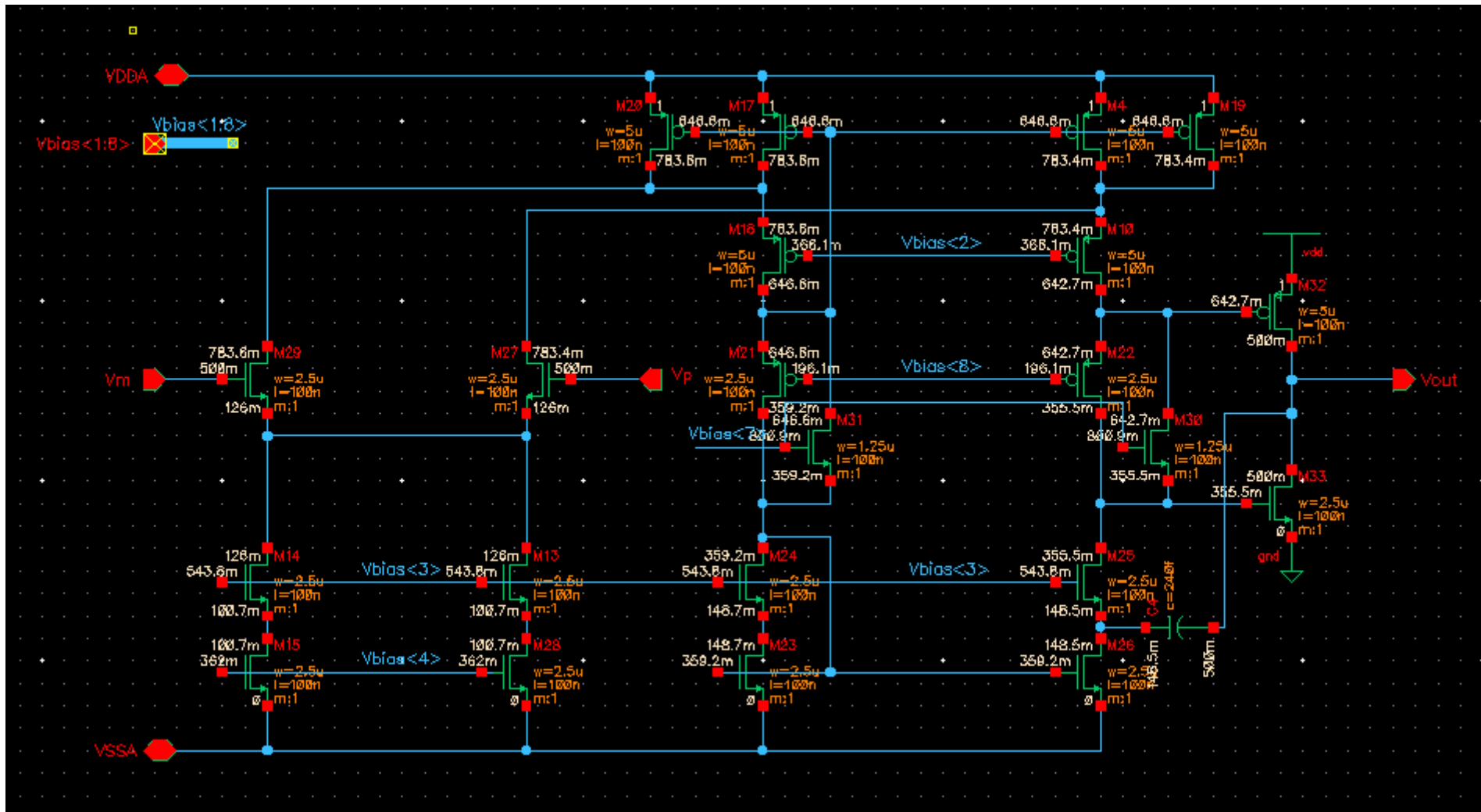
# Two-Stage Opamp –Step Response

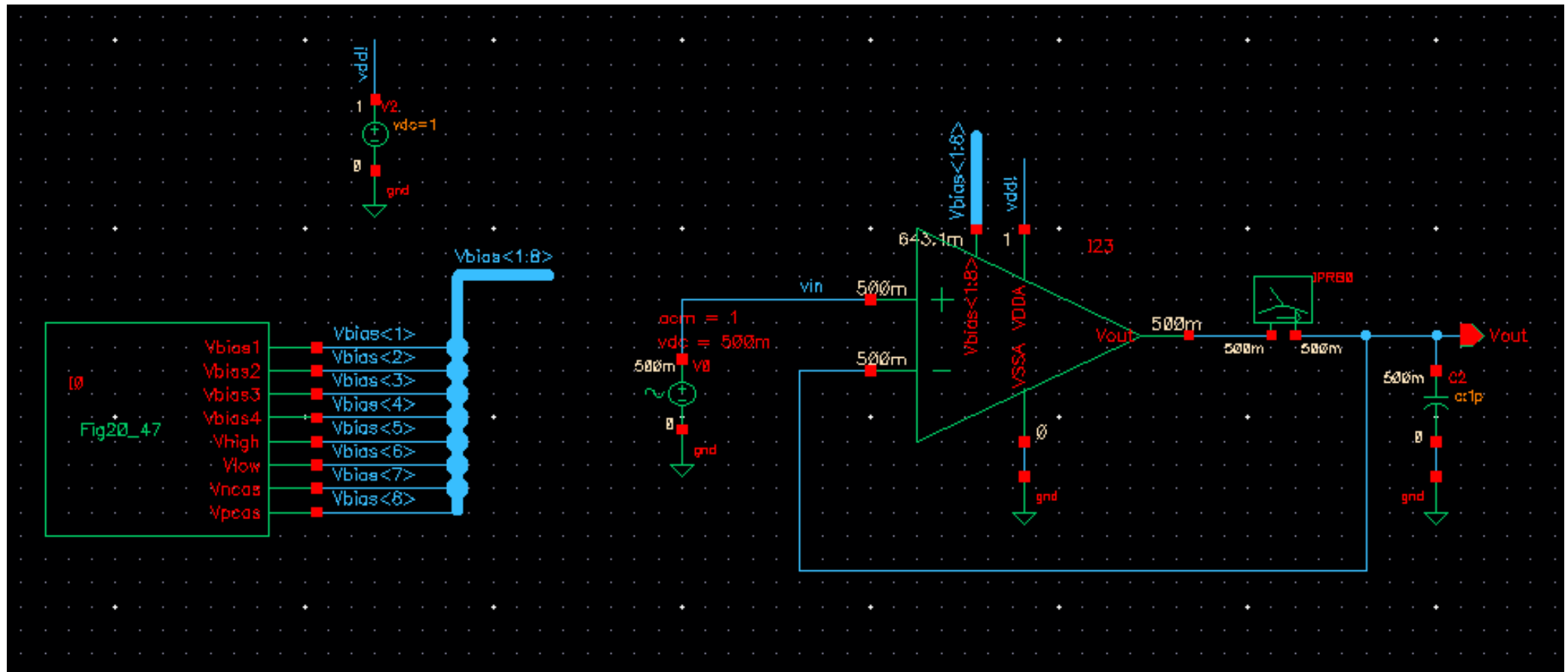


**Figure 24.14** Good step response of the op-amp with the zero absent.




- The STB analysis linearizes the circuit about the DC operating point and computes the loop-gain, gain and phase margins (if the sweep variable is frequency), for a feedback loop or a gain device [1].
- Refer to the Spectre Simulation Reference [1] and [2] for details.






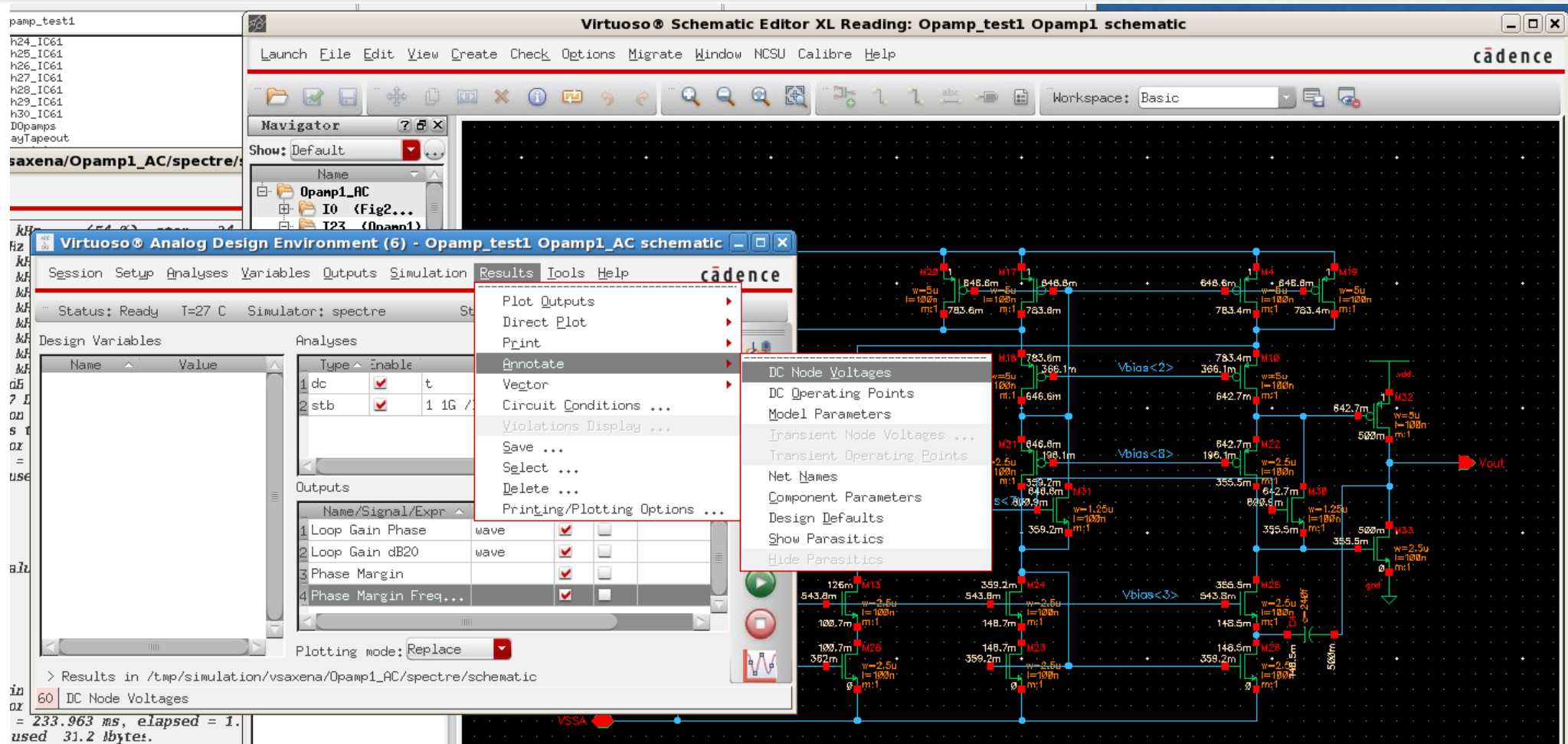- Pay attention to the **iprobe** component (from analogLib)
  - Acts as a short for DC, but breaks the loop in stb analysis
- Place the probe at a point where it completely breaks (all) the loop(s).



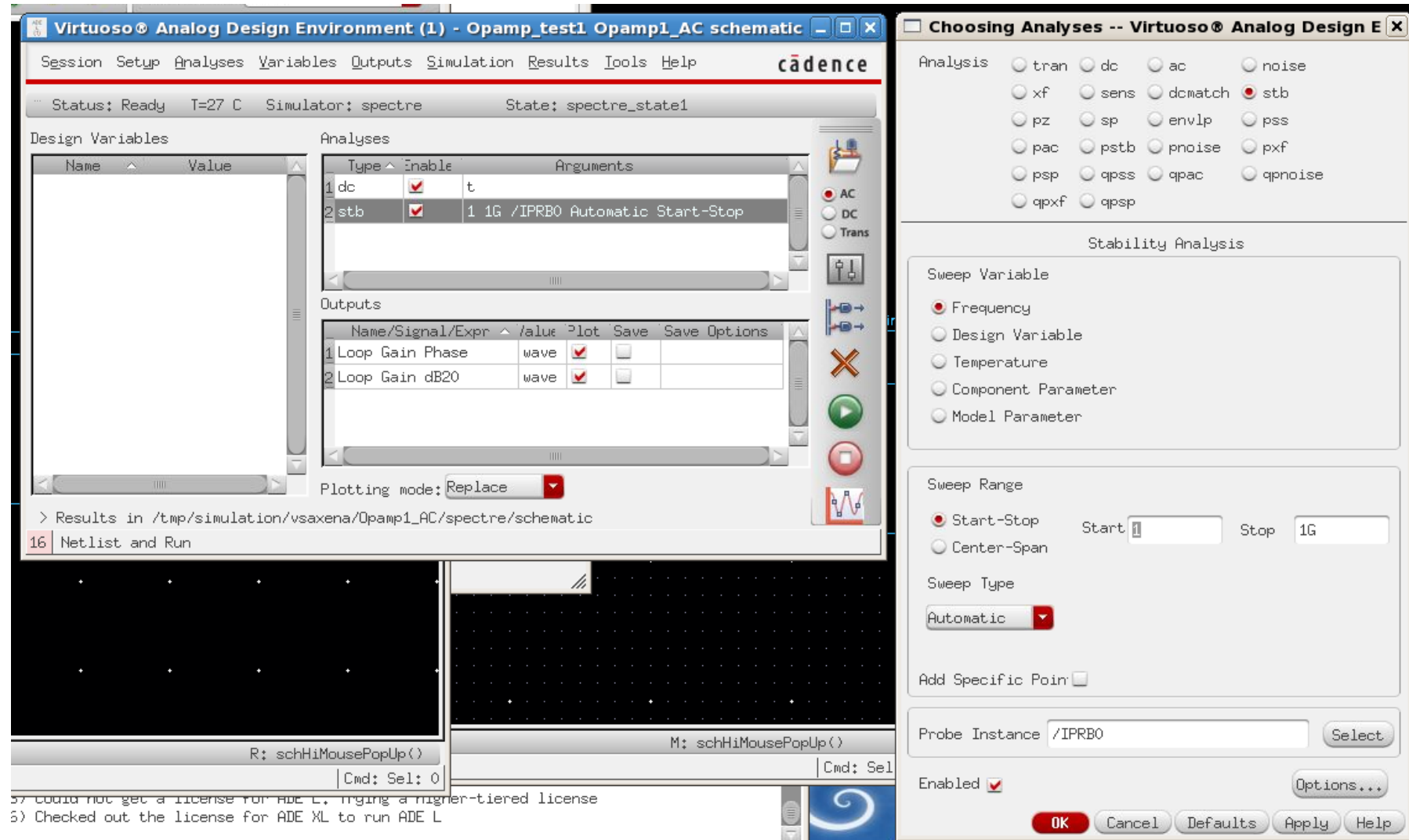- Annotating the node voltages and DC operating points of the devices helps debug the design
- Check device gds to see if its in triode or saturation regions



The screenshot displays the Cadence Virtuoso Analog Design Environment (ADE) interface for the 'Opamp1\_AC' schematic. The main window shows the 'Analyses' tab with a table of analysis types and arguments.

Type	Enable	Arguments
1 dc	<input checked="" type="checkbox"/>	t
2 stb	<input checked="" type="checkbox"/>	1 1G /IPRB0 Automatic Start-Stop

Below the analyses table, the 'Outputs' section shows a table of output signals and their plotting options.

Name/Signal/Expr	/alu	Plot	Save	Save Options
1 Loop Gain Phase	wave	<input checked="" type="checkbox"/>	<input type="checkbox"/>	
2 Loop Gain dB20	wave	<input checked="" type="checkbox"/>	<input type="checkbox"/>	

The 'Plotting mode' is set to 'Replace'. The command window at the bottom shows the following commands:


```

> Results in /tmp/simulation/vsaxena/Opamp1_AC/spectre/schematic
16 Netlist and Run
R: schHiMousePopUp()
M: schHiMousePopUp()
Cmd: Sel: 0

```


On the right, the 'Choosing Analyses' dialog box is open, showing the 'Analysis' section with radio buttons for various analysis types. The 'Stability Analysis' section is also visible, with 'Frequency' selected as the sweep variable and 'Start-Stop' as the sweep range.

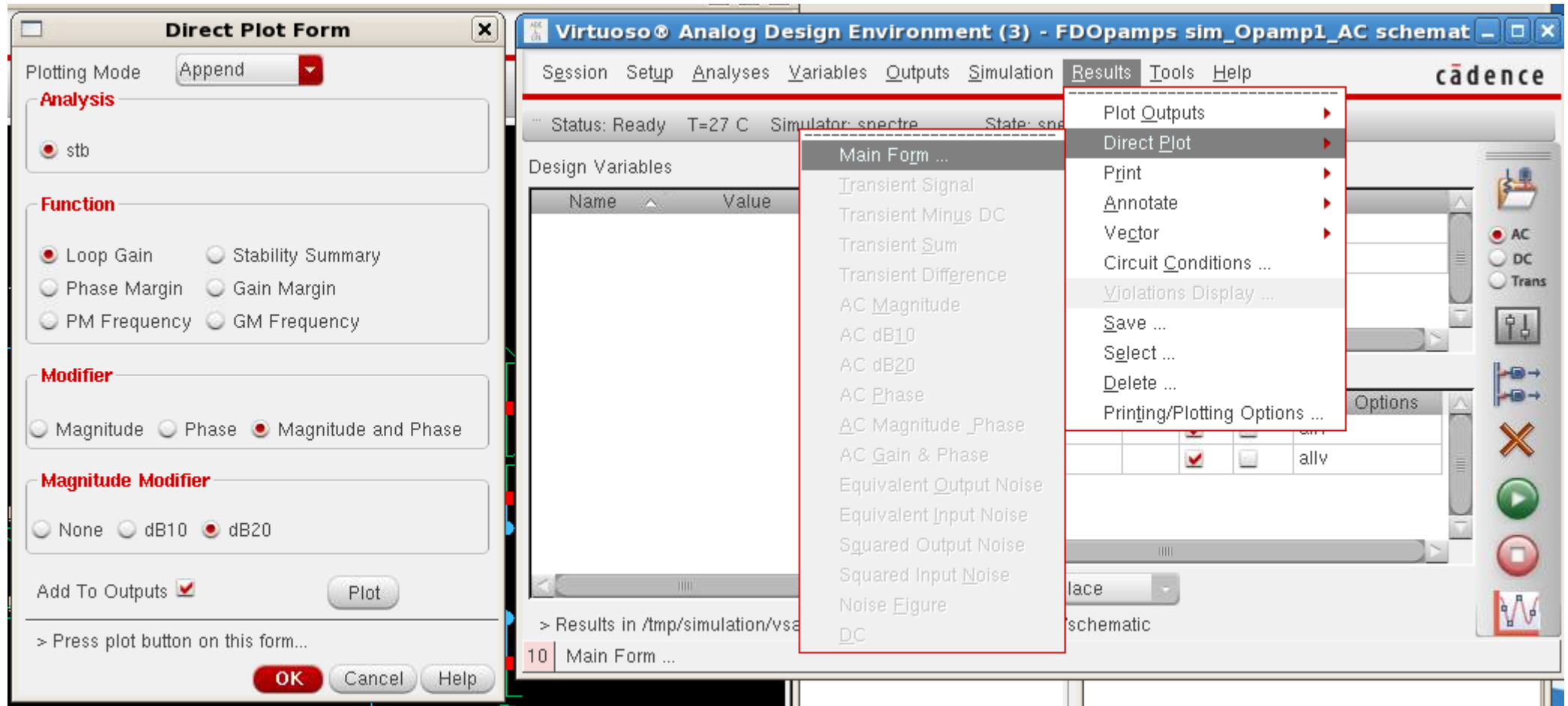- Always have dc analysis on for debugging purpose



- Results->Direct Plot-> Main Form


# Open Loop Response Bode Plots

 


- Here,  $f_{un}=152.5$  MHz,  $PM=41.8^\circ$
- Try to use the stb analysis while the circuit is in the desired feedback configuration
  - Break the loop with realistic DC operation points



# Transient Step Response Test Bench

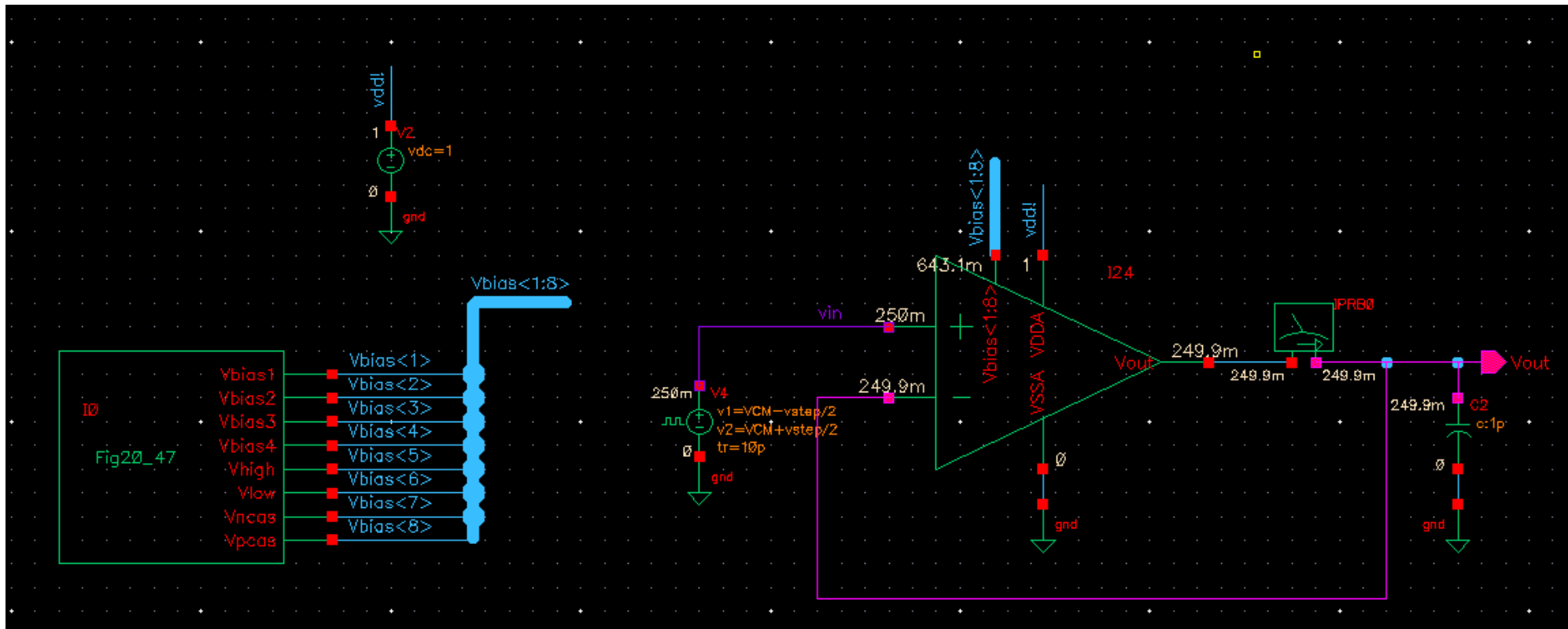


 - Transient step-response verifies the closed-loop stability
- Use small as well as large steps for characterization
- iprobe acts as a short (can remove it)




- Observe the ringing (PM was  $41^\circ$ )
  - Compensate more

# Large Step Response

 


- Note the slewing in the output

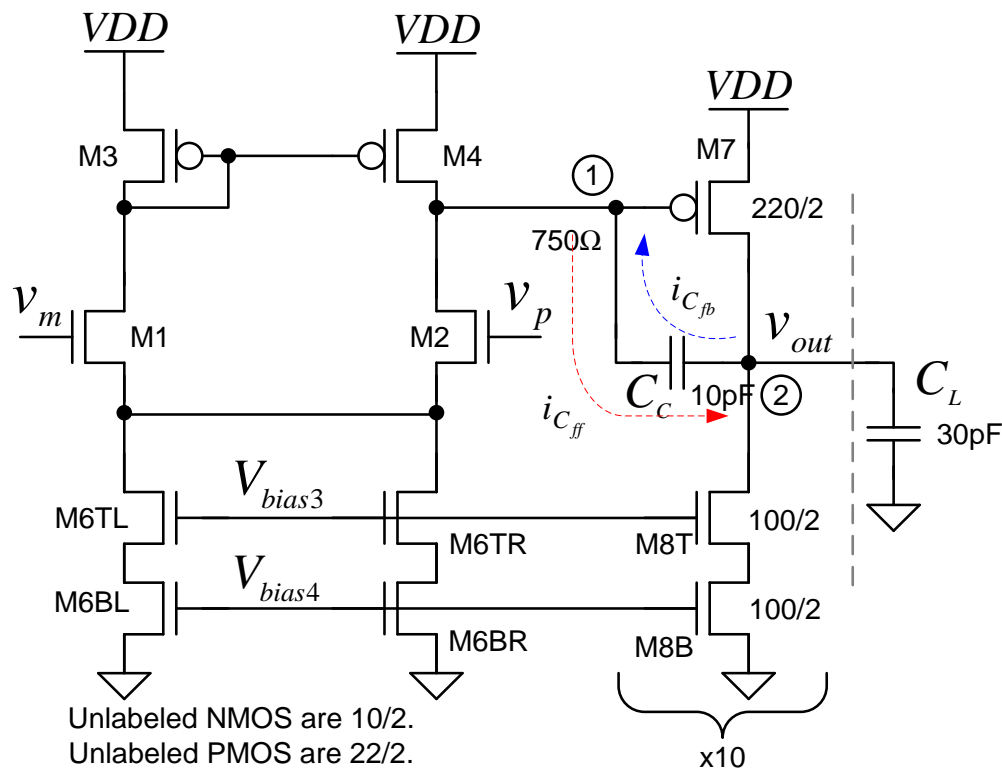

- Compensation capacitor ( $C_c$ ) between the output of the gain stages causes pole-splitting and achieves dominant pole compensation.
- An RHP zero exists at  $z_1 = \frac{g_{m2}}{C_c}$ 
  - Due to feed-forward component of the compensation current ( $i_c$ ).
- The second pole is located at  $-\frac{g_{m2}}{C_1 + C_2}$
- The unity-gain frequency is  $f_{un} = \frac{g_{m1}}{2\pi C_c}$
- A benign undershoot in step-response due to the RHP zero


❖ All the op-amps presented have been designed in AMI C5N 0.5 $\mu$ m CMOS process with scale=0.3  $\mu$ m and  $L_{min}=2$ . The op-amps drive a 30pF off-chip load offered by the test-setup.
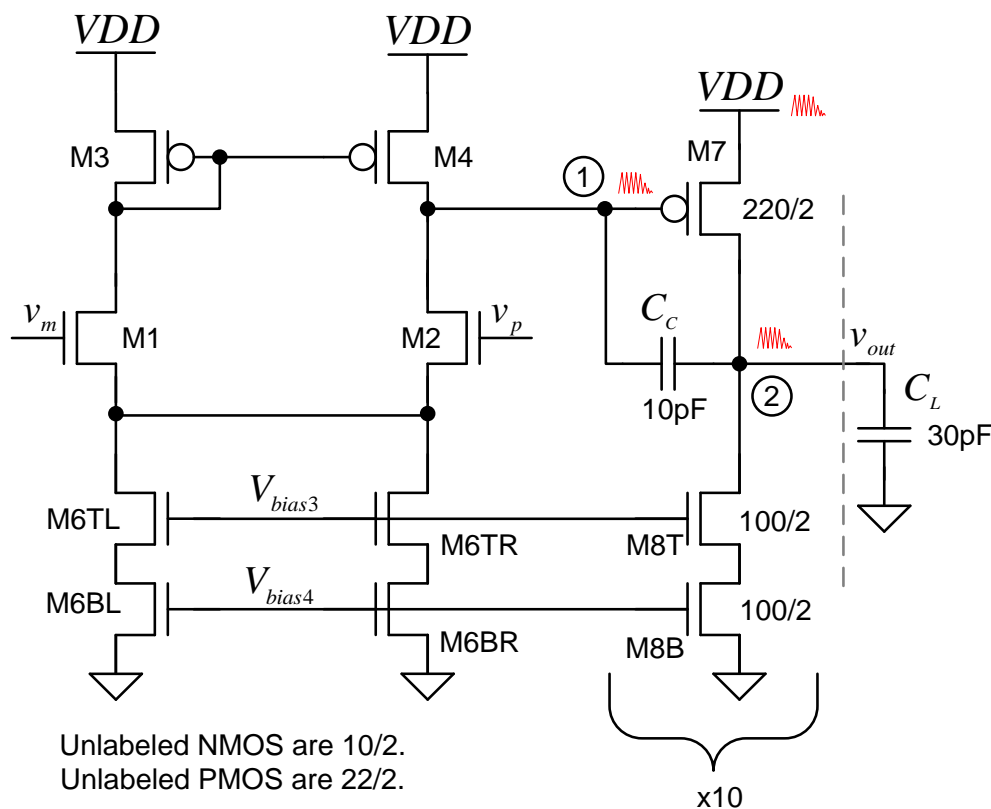
# Drawbacks of Direct (Miller) Compensation



- The RHP zero decreases phase margin
  - Requires large  $C_c$  for compensation (10pF here for a 30pF load!).
- Slow-speed for a given load,  $C_L$ .
- Poor PSRR
  - Supply noise feeds to the output through  $C_c$ .
- Large layout size.


# Indirect (or Ahuja) Compensation

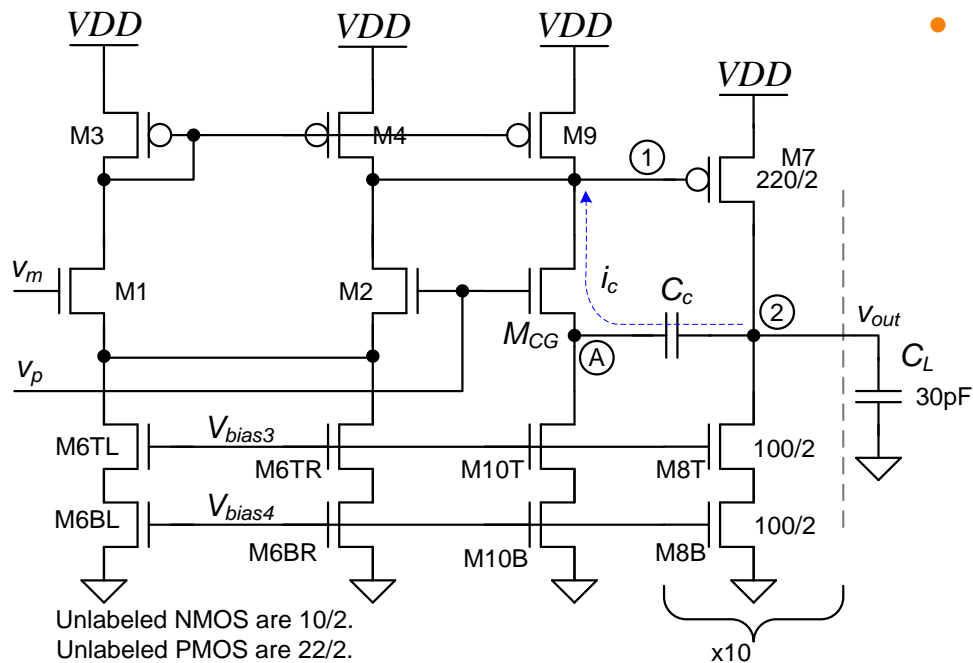

An indirect-compensated op-amp using a common-gate stage.


- The RHP zero can be eliminated by blocking the feed-forward compensation current component by using
  - A common gate stage,
  - A voltage buffer,
  - Common gate “embedded” in the cascode diff-amp, or
  - A current mirror buffer.
- Now, the compensation current is fed-back from the output to node-1 indirectly through a low-Z node-A.
- Since node-1 is not loaded by  $C_c$ , this results in higher unity-gain frequency ( $f_{un}$ ).
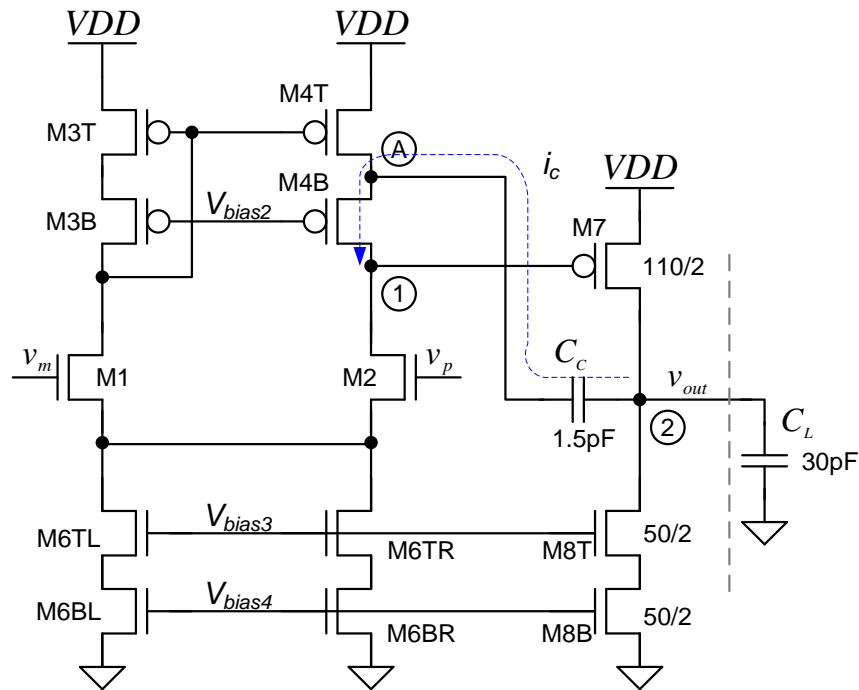
# Indirect Compensation in a Cascoded Op-amp



Unlabeled NMOS are 10/2.  
Unlabeled PMOS are 44/2.

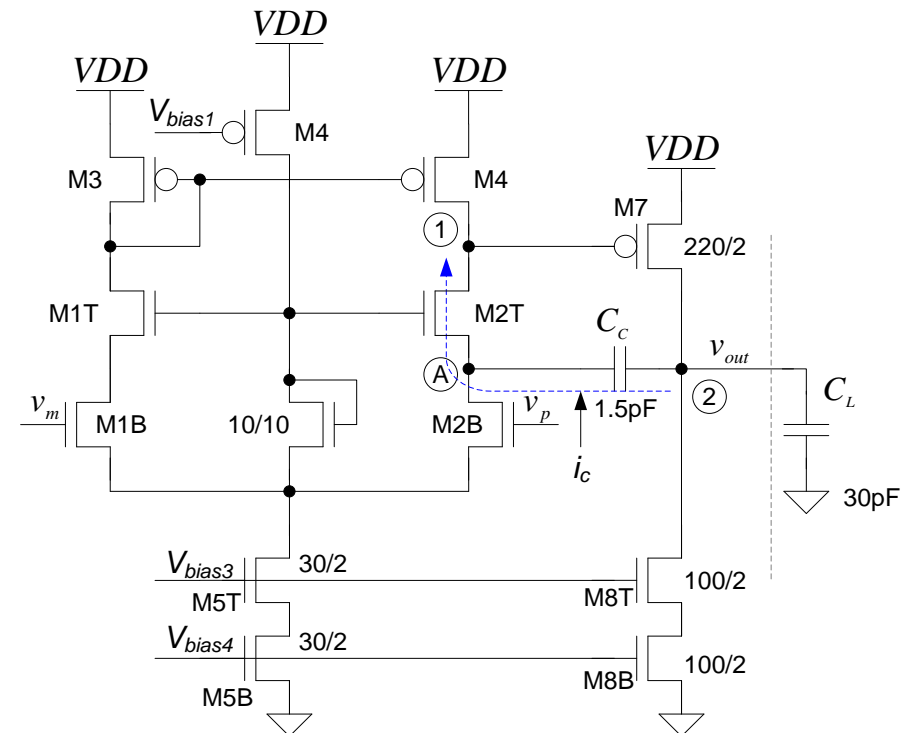Indirect-compensation using  
cascoded current mirror load.



Unlabeled NMOS are 10/2.  
Unlabeled PMOS are 22/2.

Indirect-compensation using  
cascoded diff-pair.


- Employing the common gate device “embedded” in the cascode structure for indirect compensation avoids a separate buffer stage.

✓ Lower power consumption.

✓ Also voltage buffer reduces the swing which is avoided here.


Saxena
 
# Analytical Modeling of Indirect Compensation



The compensation current ( $i_c$ ) is indirectly fed-back to node-1.


Block Diagram

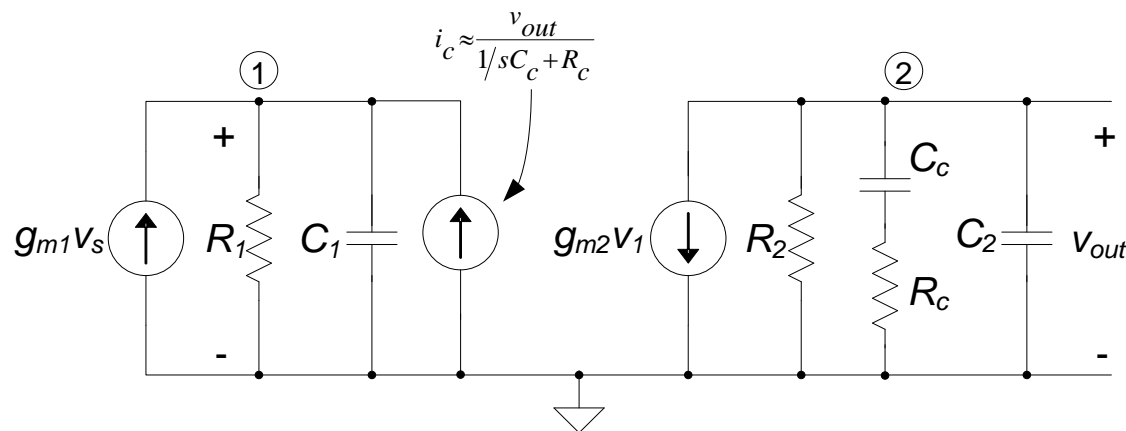

$R_C$  is the resistance attached to node-A.

Small signal analytical model



 

- ❑ Pole  $p_2$  is much farther away from  $f_{un}$ .  
✓ Can use smaller  $g_{m2} \Rightarrow$  less power!
- ❑ LHP zero improves phase margin.
- ❑ Much faster op-amp with lower power and smaller  $C_c$ .
- ❑ Better slew rate as  $C_c$  is smaller.

$$\frac{v_{out}}{v_s} = -A_v \left( \frac{1 + b_1 s}{1 + a_1 s + a_2 s^2 + a_3 s^3} \right)$$

$$z_1 \approx -\frac{1}{R_c C_c} \quad \text{LHP zero}$$

$$p_1 \approx -\frac{1}{a_1} = -\frac{1}{g_{m2} R_2 R_1 C_c}$$


$$p_2 \approx -\frac{a_1}{a_2} = -\frac{g_{m2} R_1 C_c}{C_2 (R_c C_c + R_1 C_1)} \approx -\frac{g_{m2} C_c}{C_L C_1}$$

$$p_3 \approx -\frac{a_2}{a_3} = -\left[ \frac{1}{R_c C_c} + \frac{1}{R_1 C_1} \right]$$


$$f_{un} = \frac{|p_1| A_v}{2\pi} \approx \frac{g_{m1}}{2\pi C_c}$$
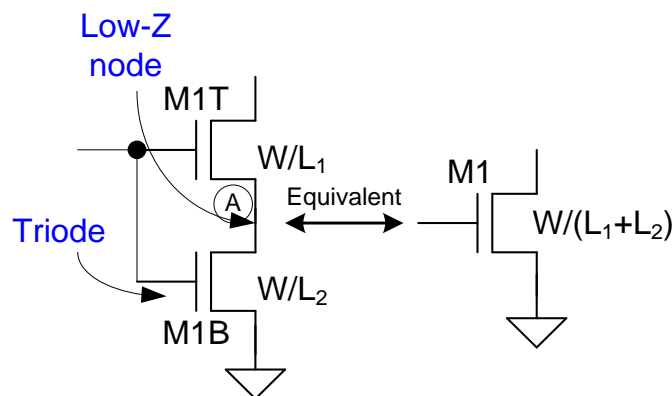
# Indirect Compensation Using Split-Length Devices


- As  $V_{DD}$  scales down, cascoding is becoming tough. Then how to realize indirect compensation as we have no low-Z node available?
- Solution: Employ split-length devices to create a low-Z node.**
  - Creates a pseudo-cascode stack but its really a single device.
- In the NMOS case, the lower device is always in triode hence node-A is a low-Z node. Similarly for the PMOS, node-A is low-Z.



NMOS

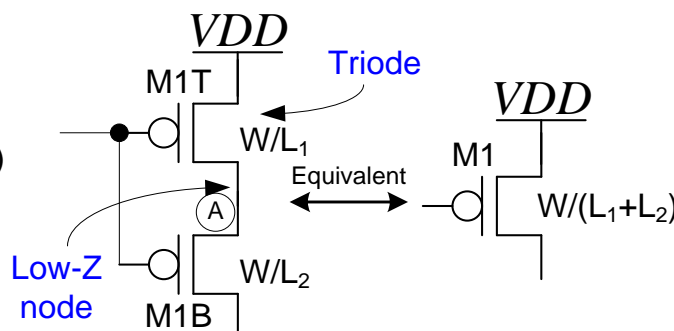


PMOS

 


Split-length 44/4(=22/2)  
PMOS layout

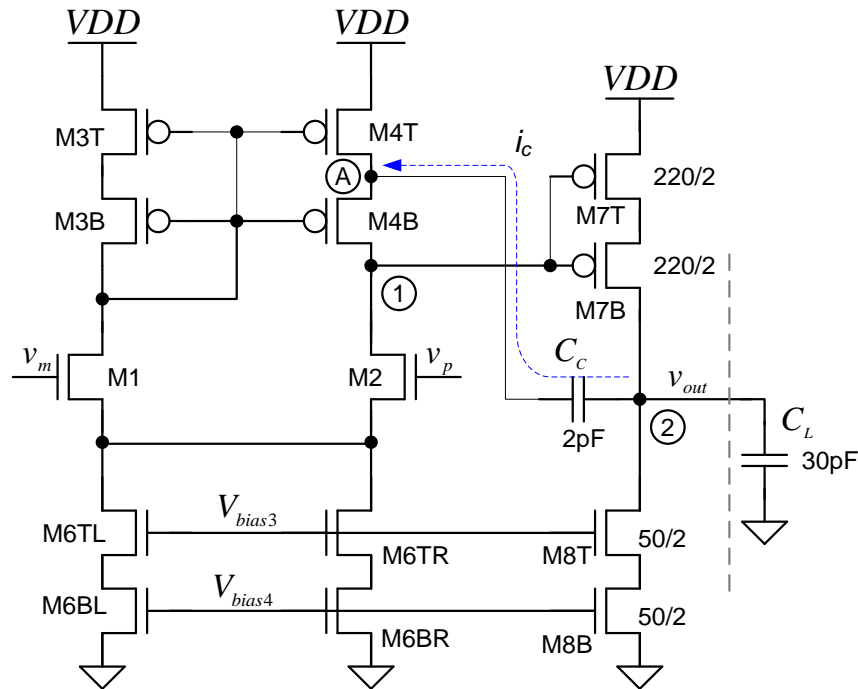
# Split-Length Current Mirror Load (SLCL) Op-amp



 Unlabeled NMOS are 10/2.  
Unlabeled PMOS are 22/2.





Frequency Response

 

Small step-input settling in follower configuration

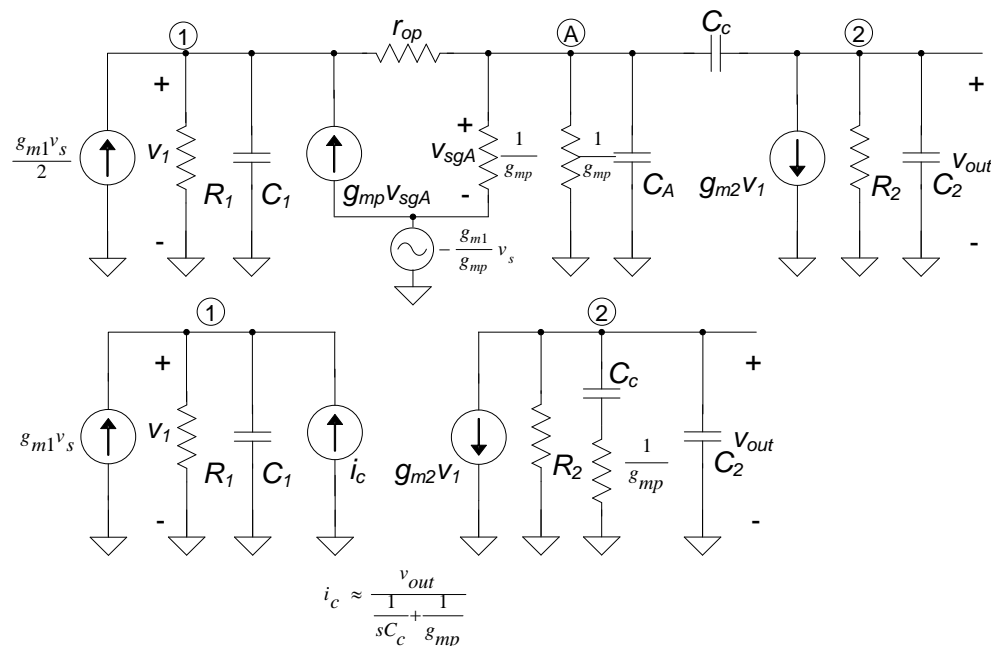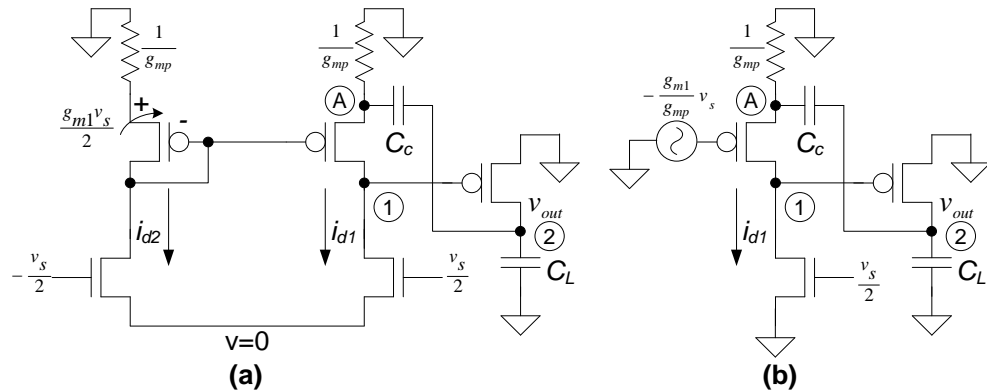- The current mirror load devices are split-length to create low-Z node-A.
- Here,  $f_{un}=20\text{MHz}$ ,  $PM=75^\circ$  and  $t_s=60\text{ns}$ .



$$f_{un} = \frac{g_{m1}}{2\pi(2C_c)}$$

$$p_1 \approx -\frac{1}{2g_{m2}R_2R_1C_c}$$


$$|Re(p_{2,3})| = \frac{g_{m2}}{C_L} \sqrt{\frac{g_{mp}C_L}{g_{m2}C_1}}$$

$$z_1 \approx -\frac{4g_{mp}}{3(C_c + C_A)} = -\frac{4\sqrt{2}g_{m1}}{3(C_c + C_A)} \approx \frac{8\sqrt{2}}{3}\omega_{un}$$

Here  $f_{z1} = 3.77f_{un}$

✓ LHP zero appears at a higher frequency than  $f_{un}$ .


# Split-Length Diff-Pair (SLDP) Op-amp

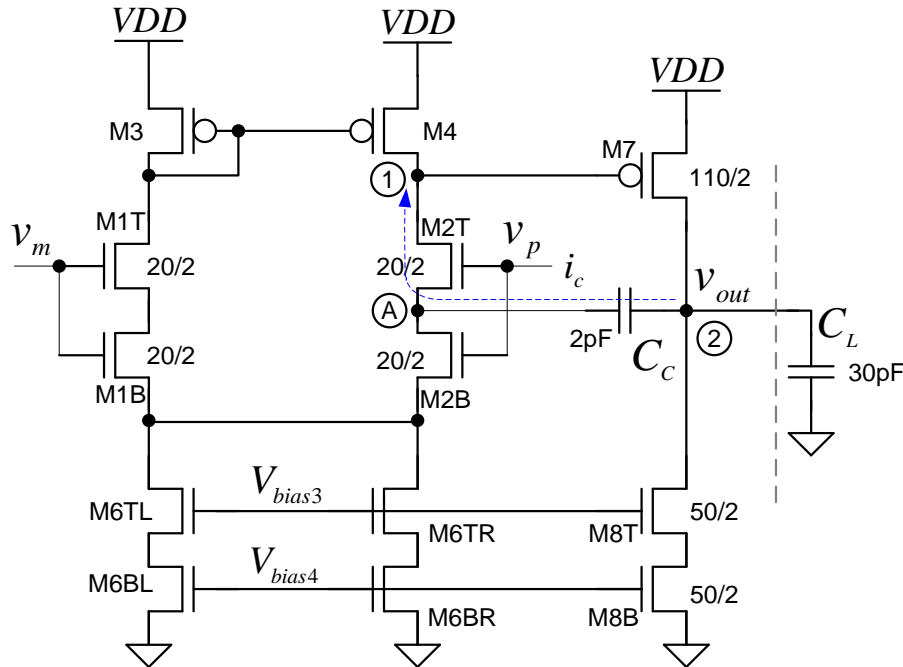


Unlabeled NMOS are 10/2.  
Unlabeled PMOS are 22/2.

- ❑ The diff-pair devices are split-length to create low-Z node-A.
- ❑ Here,  $f_{un}=35\text{MHz}$ ,  $\text{PM}=62^\circ$ ,  $t_s=75\text{ns}$ .
- ❑ Better PSRR due to isolation of node-A from the supply rails.



Saxena

 

Frequency Response

 

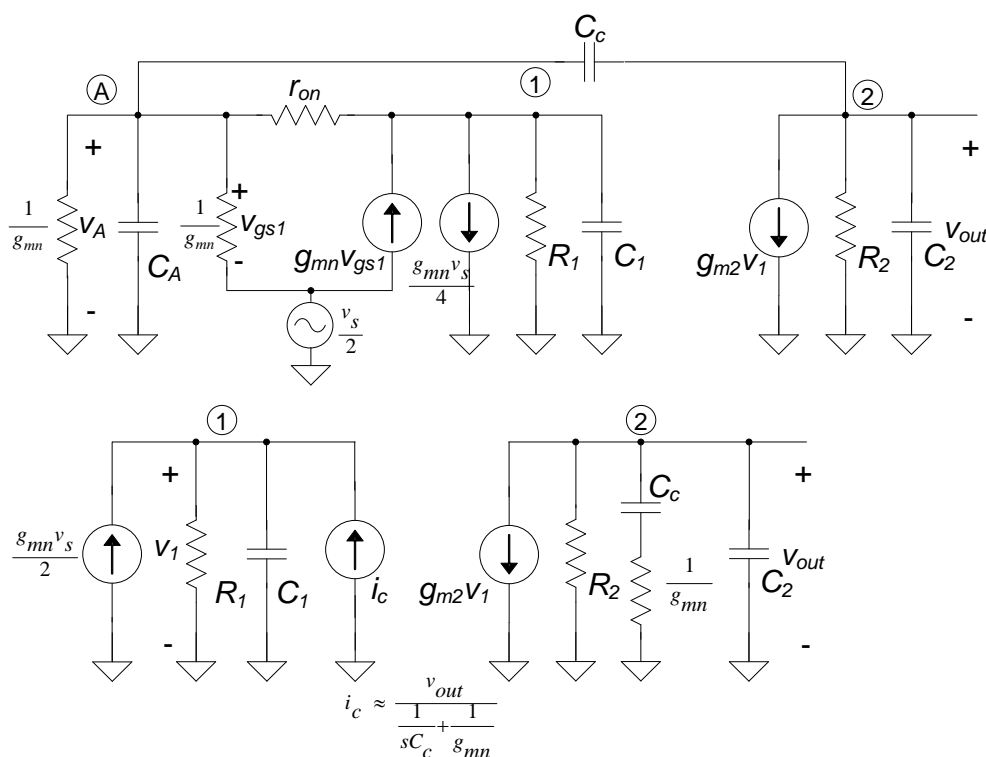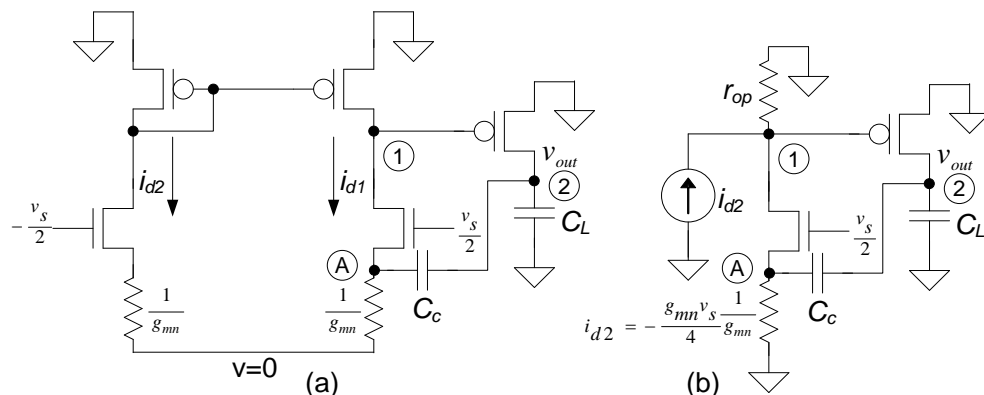Small step-input settling in follower configuration



$$f_{un} = \frac{2g_{m1}}{2\pi C_c}$$

$$p_1 \approx -\frac{2}{g_{m2}R_2R_1C_c}$$

$$|Re(p_{2,3})| = \frac{g_{m2}}{C_L} \sqrt{\frac{g_{mp}C_L}{g_{m2}C_1}}$$

$$z_1 \approx -\frac{4g_{mn}}{3(C_c + C_A)} = -\frac{4\sqrt{2}g_{m1}}{3(C_c + C_A)} \approx \frac{2\sqrt{2}}{3}\omega_{un}$$


Here  $f_{z1} = 0.94f_{un}$ ,

✓ LHP zero appears slightly before  $f_{un}$  and flattens the magnitude response.

✓ This may degrade the phase margin.

Not as good as SLCL, but is of great utility in multi-stage op-amp design due to higher PSRR.


# Test Chip 1: Two-stage Op-amps

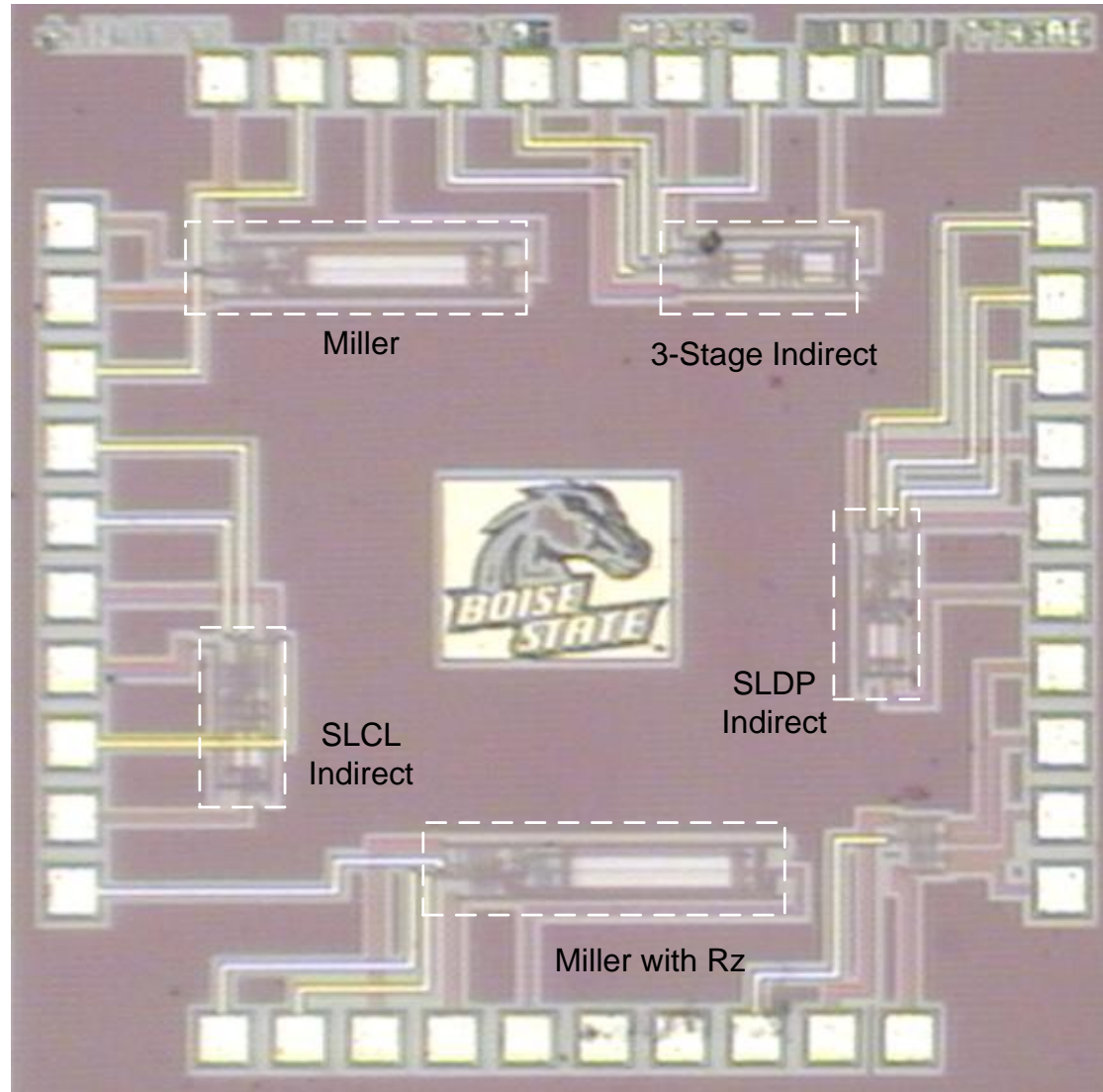


- AMI C5N 0.5 $\mu$ m CMOS, 1.5mmX1.5mm die size.



 
# Test Results and Performance Comparison



 Miller with  $R_z$  ( $t_s=250\text{ns}$ )



SLCL Indirect ( $t_s=60\text{ns}$ )

 

SLDP Indirect ( $t_s=75\text{ns}$ )

Performance comparison of the op-amps for  $C_L=30\text{pF}$ .

Op-amp Topology	$A_{DC}$ (dB)	$f_{un}$ (MHz)	$C_C$ (pF)	PM	$t_s$ (ns)	Power (mW)	Layout area ( $\text{mm}^2$ )
Miller	57	2.5	10	$74^\circ$	270	1.2	0.031
Miller with $R_z$	57	2.7	10	$85^\circ$	250	1.2	0.034
SLCL (this work)	66	20	2	$75^\circ$	60	0.7	0.015
SLDP (this work)	60	35	2	$62^\circ$	75	0.7	0.015

- ☐ 10X gain bandwidth ( $f_{un}$ ).
- ☐ 4X faster settling time.
- ☐ 55% smaller layout area.
- ☐ 40% less power consumption.





# Effect of LHP-zero on Settling

- ❑ In certain cases with indirect compensation, the LHP-zero ( $\omega_{z,LHP}$ ) shows up near  $f_{un}$ .
  - ✓ Causes gain flattening and degrades PM
  - ✓ Hard to push out due to topology restrictions
- ❑ Ringing in closed-loop step response
  - ✓ This ringing is uncharacteristic of the 2<sup>nd</sup> order system.
  - ✓ Used to be a benign undershoot with the RHP zero, here it can be pesky
  - ✓ Is this settling behavior acceptable?
- ❑ Watch out for the  $\omega_{z,LHP}$  for clean settling behavior!
  
## Caveat:

- **When using indirect compensation be aware of the LHP-zero induced transient settling issues**



Small step-input settling in follower configuration



[1] Spectre User Simulation Guide, pages 160-165

<http://www.designers-guide.org/Forum/YaBB.pl?num=1170321868>

[2] M. Tian, V. Viswanathan, J. Hangtan, K. Kundert, "Striving for Small-Signal Stability: Loop-based and Device-based Algorithms for Stability Analysis of Linear Analog Circuits in the Frequency Domain," Circuits and Devices, Jan 2001.

<http://www.kenkundert.com/docs/cd2001-01.pdf>

[3] <https://secure.engr.oregonstate.edu/wiki/ams/index.php/Spectre/STB>