



Project Help Session

Note Title

4/19/2014

Table 1: Opamp design specifications.



Parameter	Specified Value
Technology	TSMC 180n CMOS ✓
Supply voltage, V_{DD}	1.8 V ✓
Typical load	$100k\Omega 2pF$
Unit gain frequency (f_{un})	$> 50 MHz$ for ECE 411 $> 200 MHz$ for ECE 511
Open-loop gain (A_{OL})	$> 75 dB$
Slew-rate (SR)	$> 500 \frac{V}{\mu s}$
Phase margin (ϕ_M)	$\approx 63^\circ$
Power consumption	Minimum possible

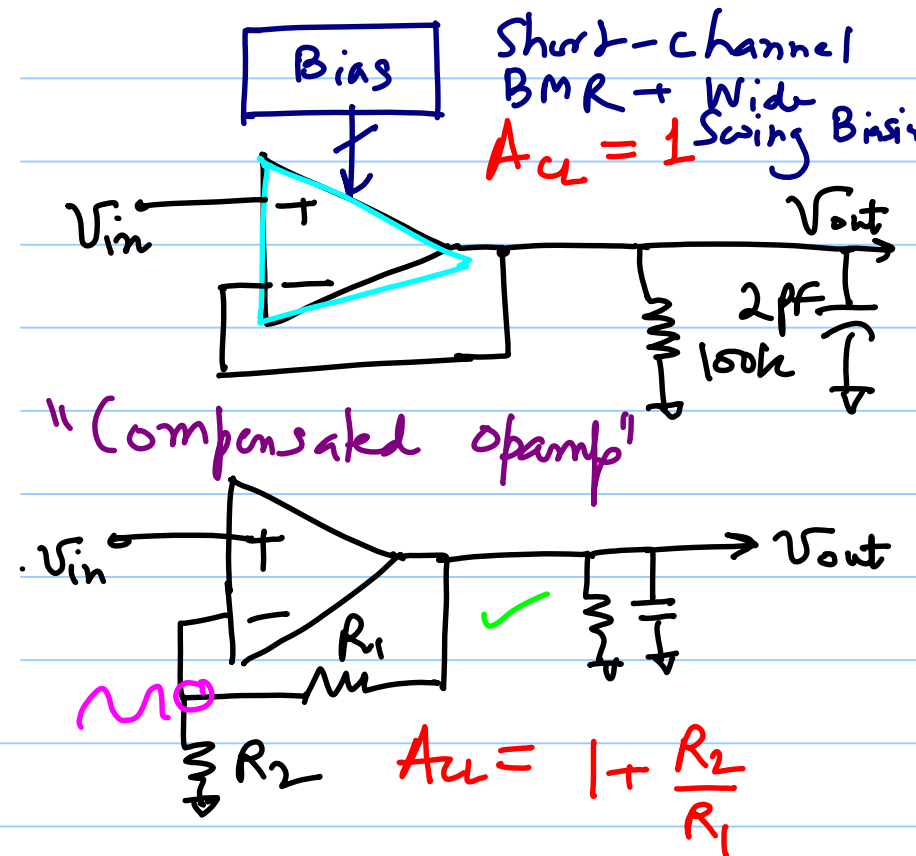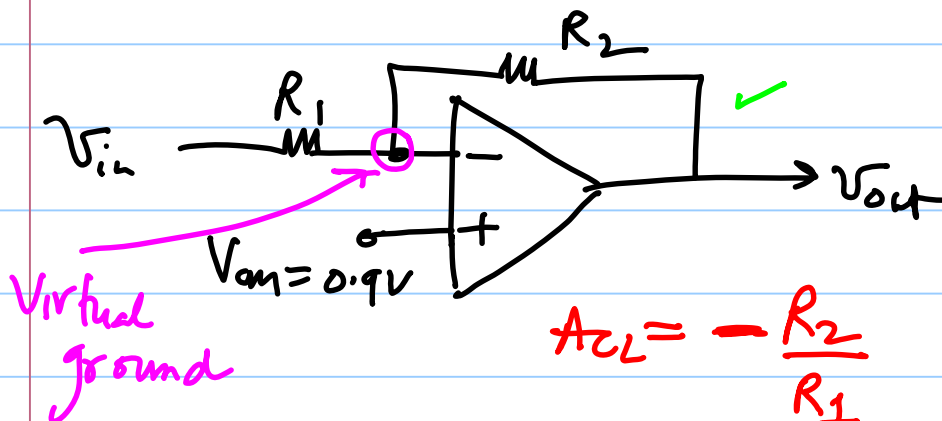


$$f_{un} = \frac{\omega_{un}}{2\pi} = 200 MHz$$


Slewing in opamps

UAB
follower

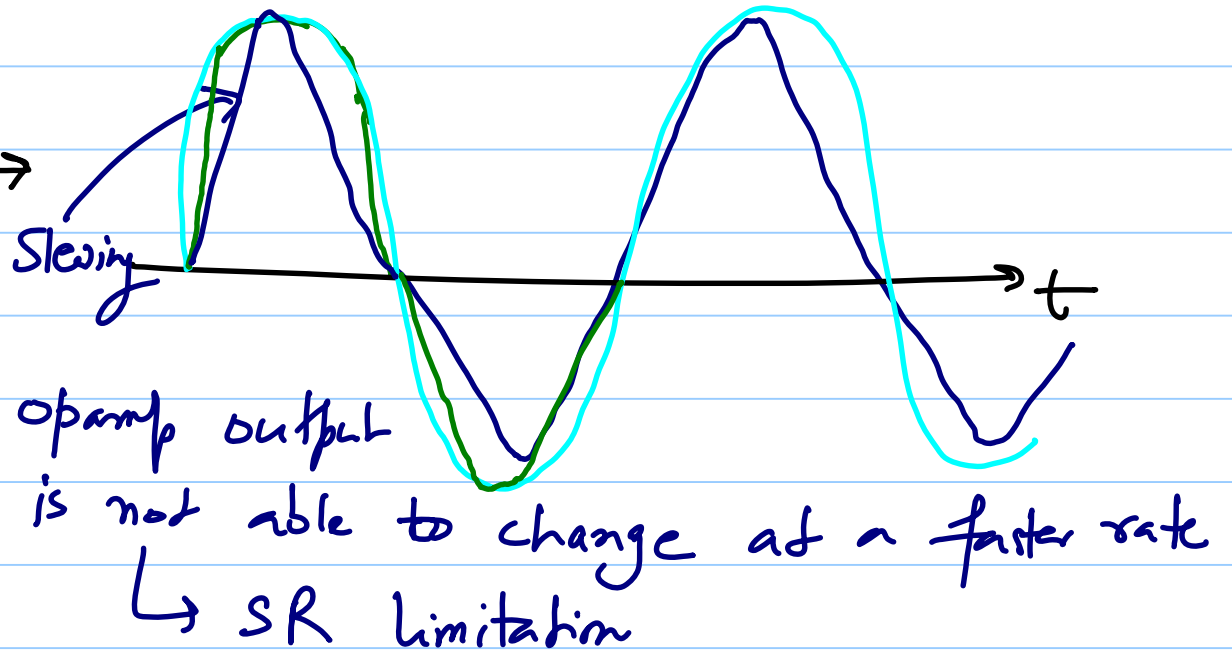
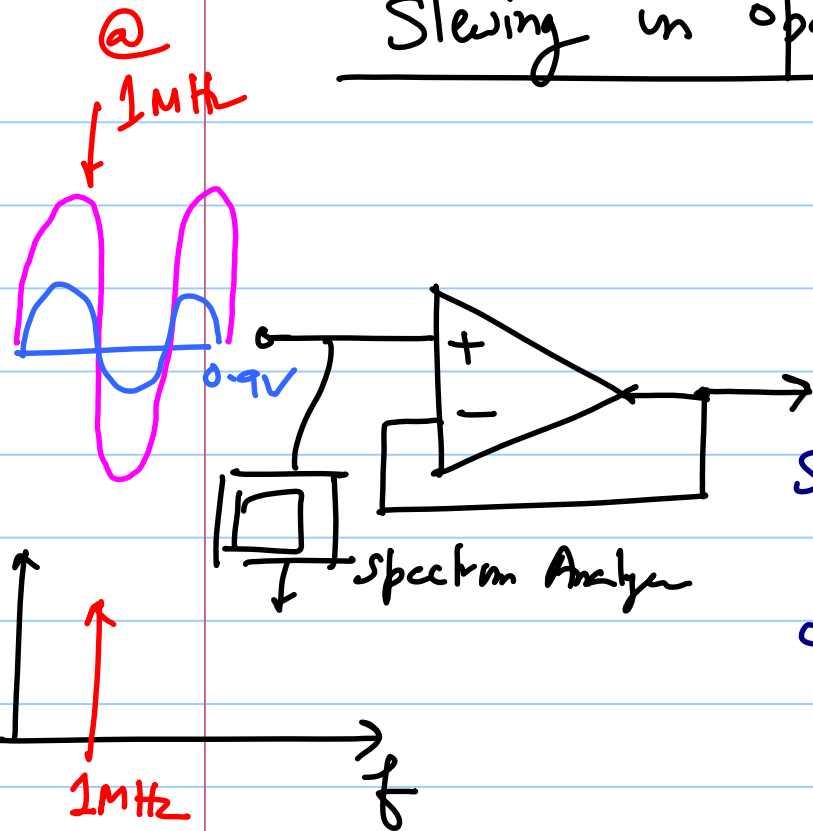


Slewing is a non linear behavior


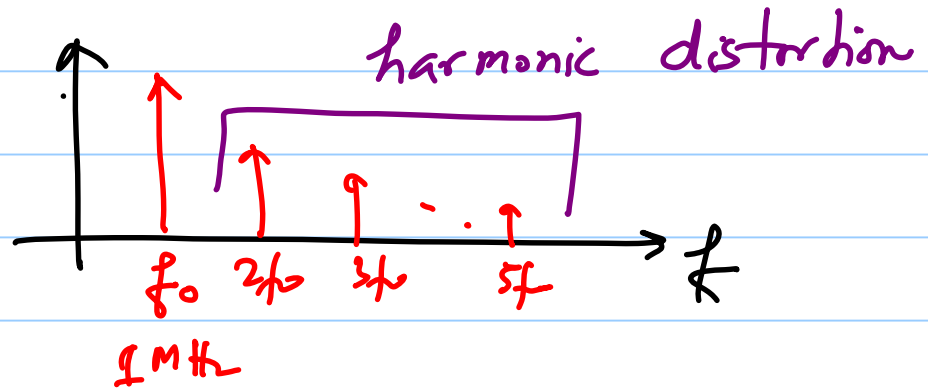


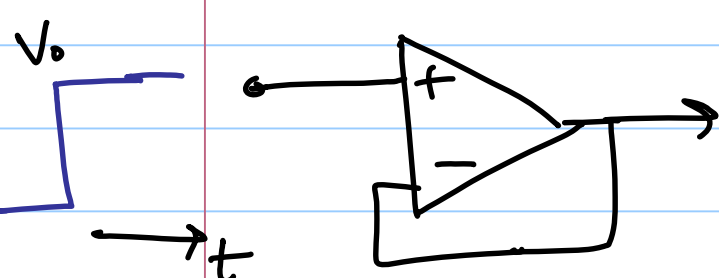



Non-linear settling behavior

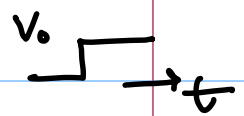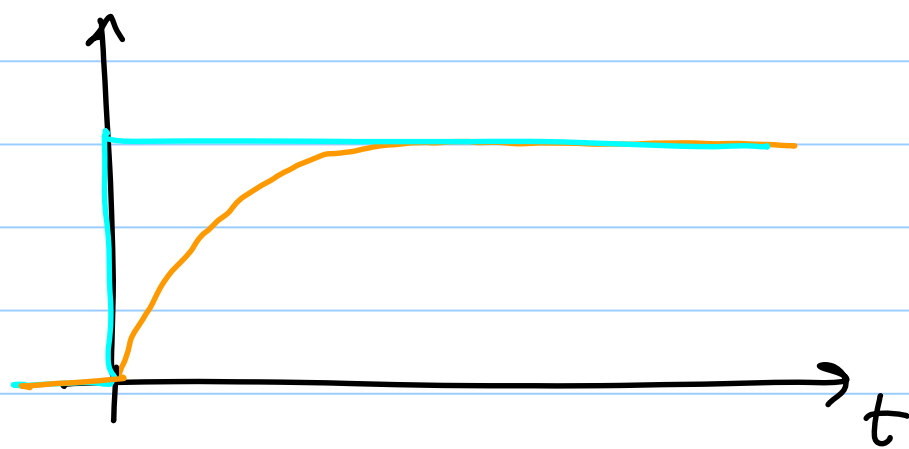


with slewing

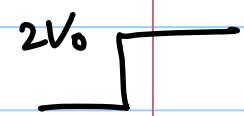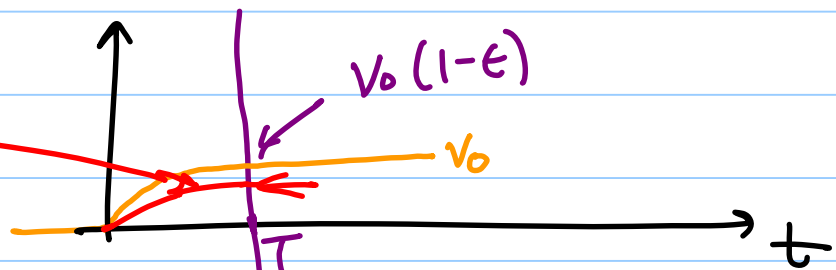


Linear settling

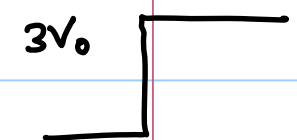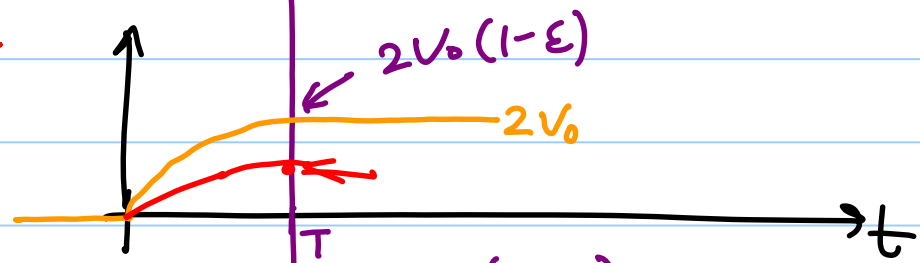

slewing

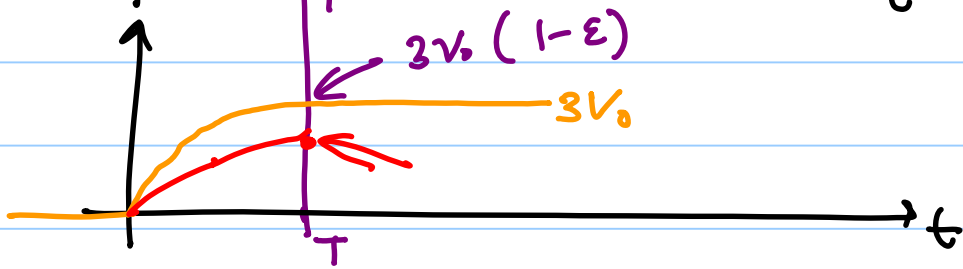

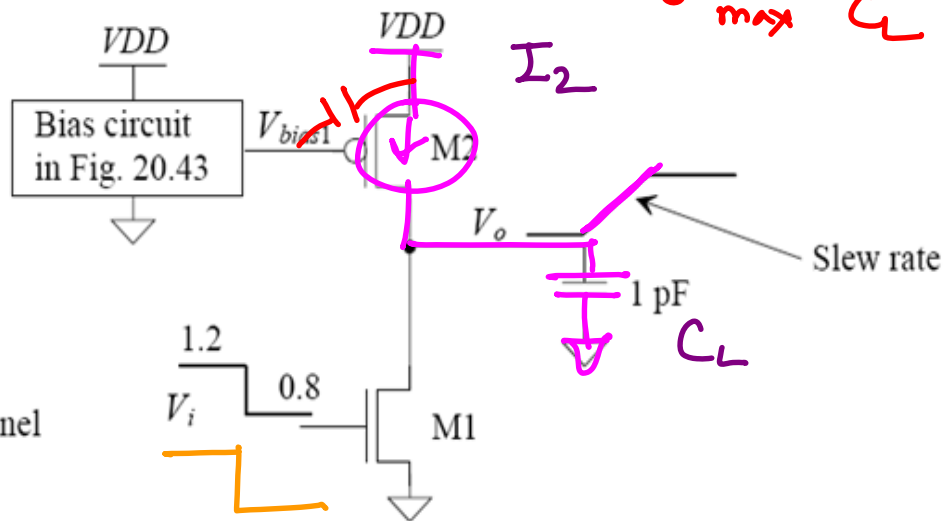Use the long-channel sizes and biasing seen in Table 9.1.



$$SR_{max} = \frac{I_2}{C_L}$$

Slewing (non-linear settling)

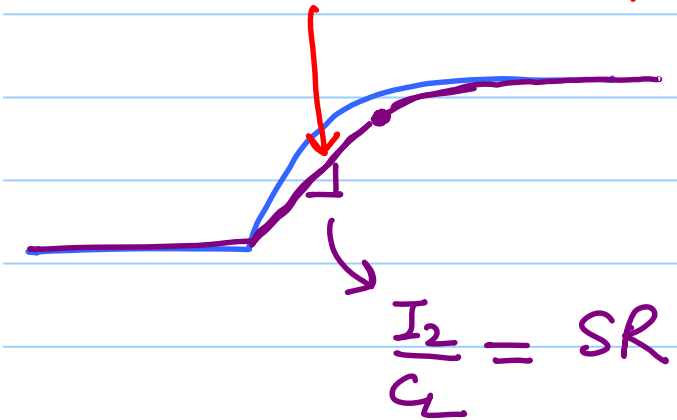


Figure 21.18 Slew rate limitations in a class A amplifier.

$$\frac{dV_{out}}{dt} \leq SR$$

Slew rate limitations because of
"current source charging sizable amount
of capacitance"




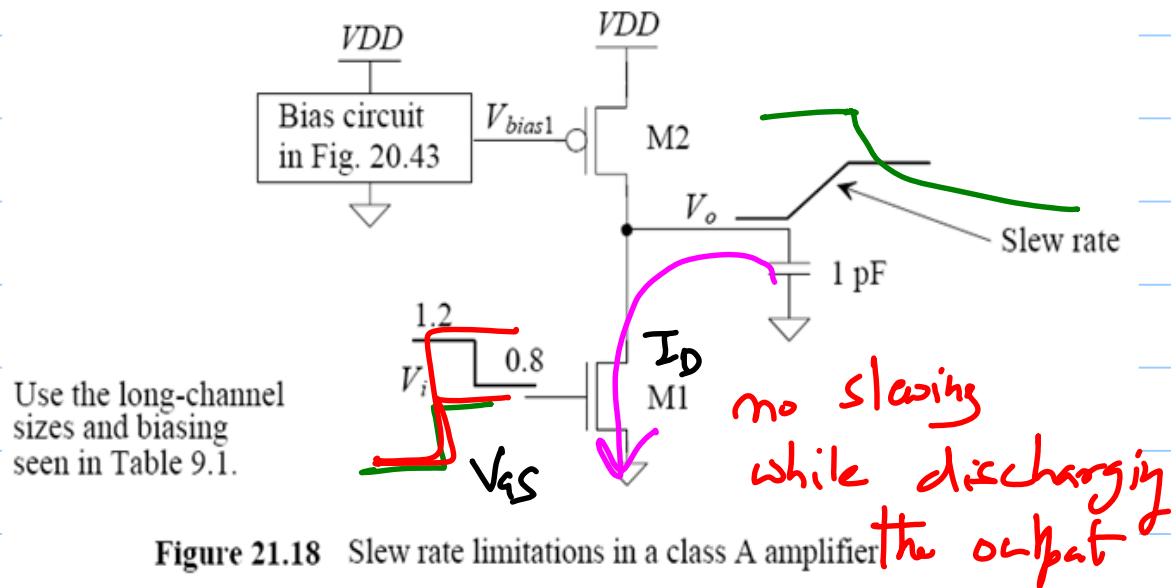



Figure 21.18 Slew rate limitations in a class A amplifier

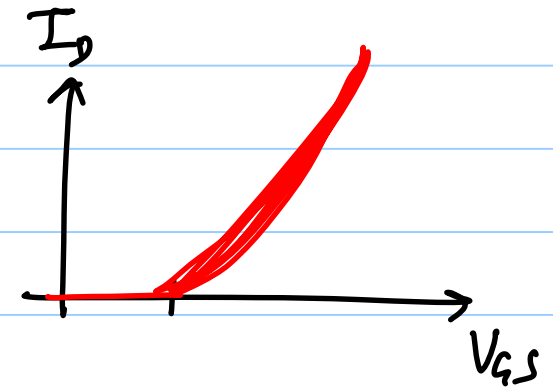

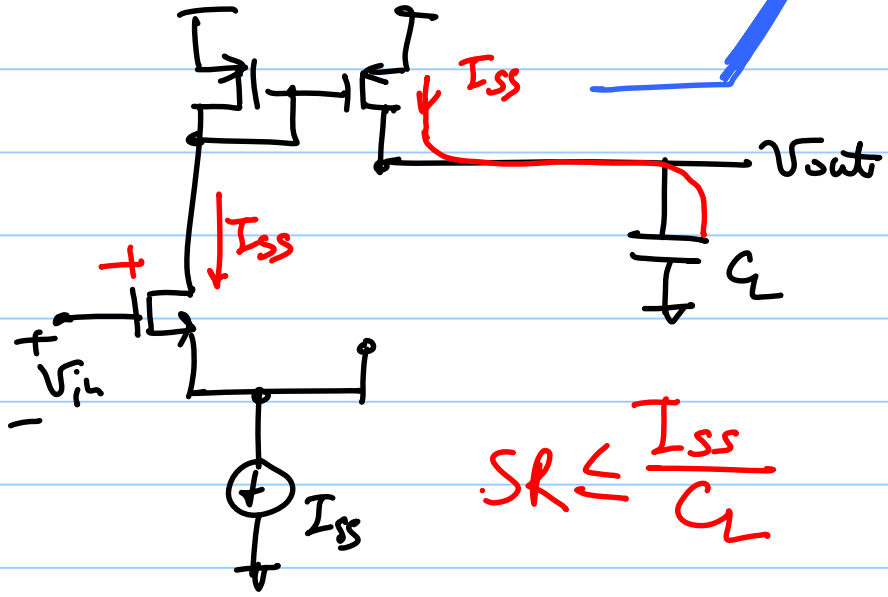

$$SR \leq \frac{I_{SS}}{C_L}$$

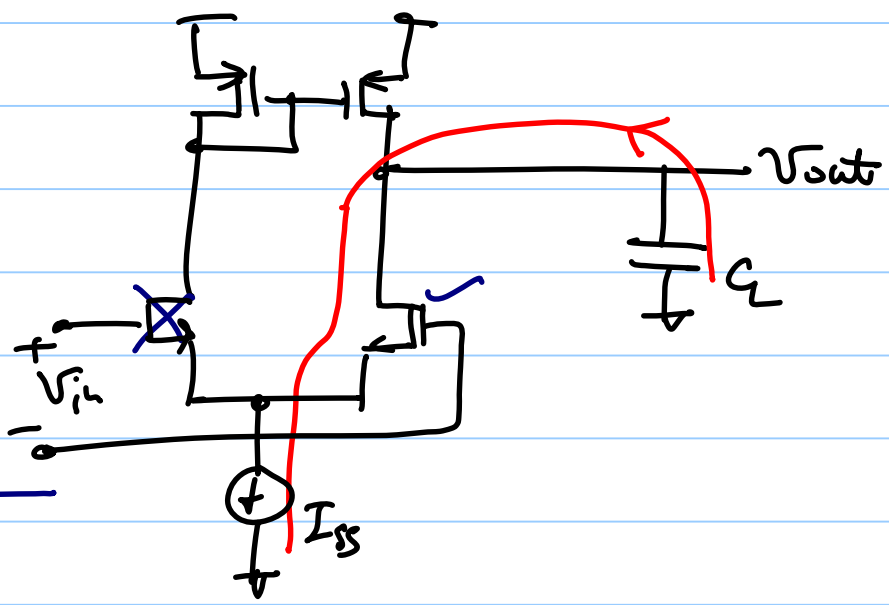

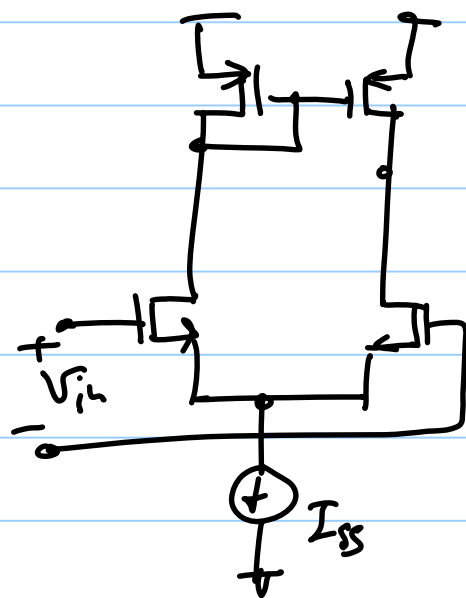

$$\approx \frac{g_m r_o}{2}$$

Telescopic

$$g_m \left(\frac{g_m r_o^2}{2} \right)$$

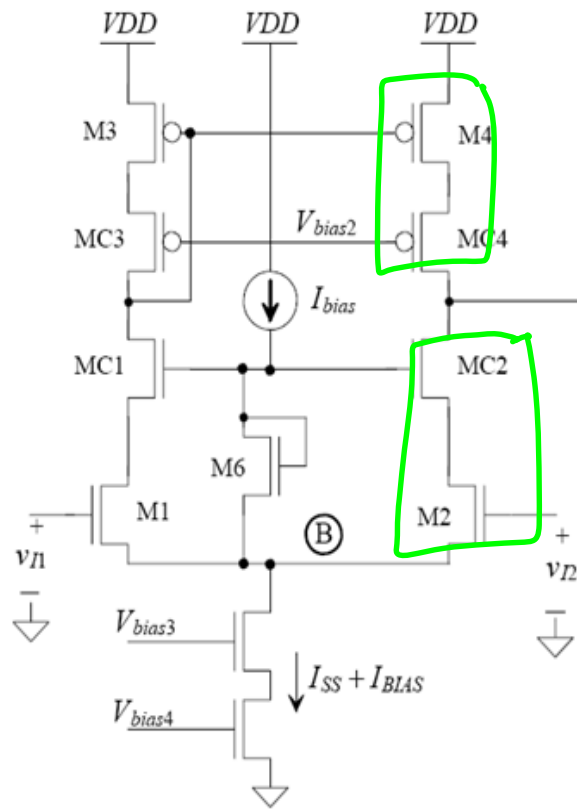


Figure 22.30 Cascode differential amplifier.

$$R_{out} = (g_{m1} r_{o1})_p \parallel (g_{m2} r_{o2})_n \parallel R_L$$

$\downarrow$
 $100k$
 $\downarrow$
 $100k$