
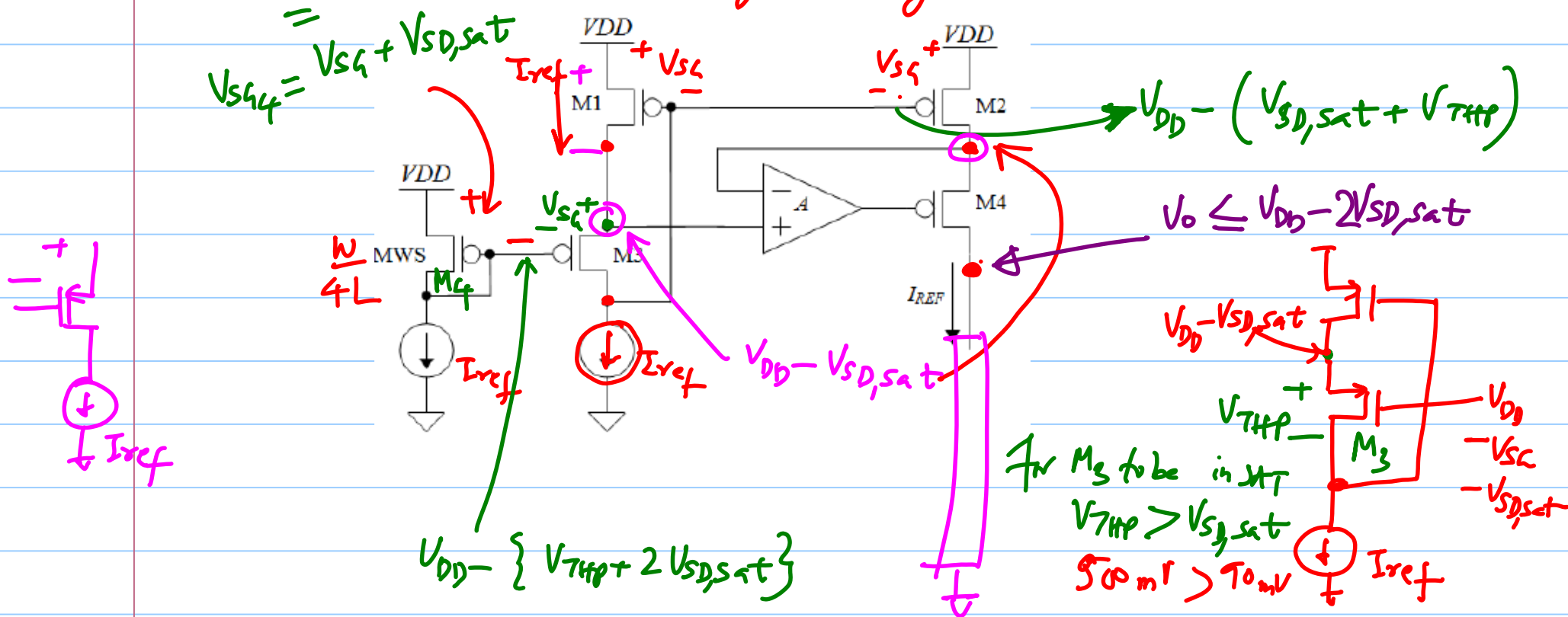


Note Title


3/4/2014

$$R_0 \subseteq g_{mp} \gamma_p^2 \cdot A$$

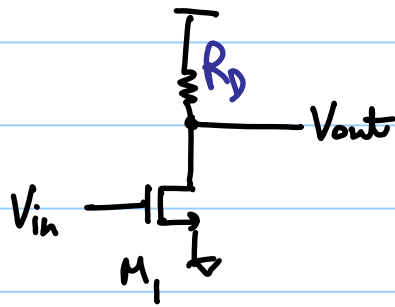
$$I_{\text{reg}} \neq \frac{2}{\beta R^2} \left(1 - \frac{1}{\sqrt{R}}\right)^2$$



Ac

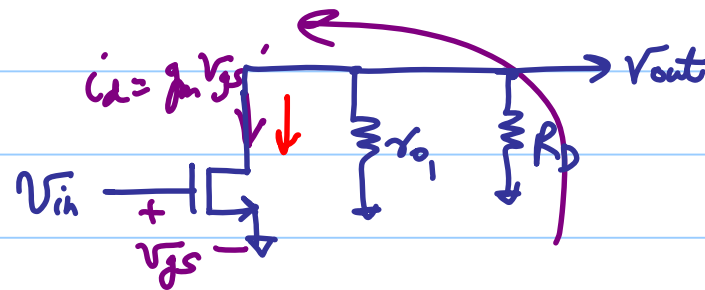


$$V_{out} = - i_d (r_o \parallel R_D)$$

$\downarrow$
 $g_m V_{in}$

$$\Rightarrow A_v = \frac{V_{out}}{V_{in}} = - g_m (r_o \parallel R_D)$$

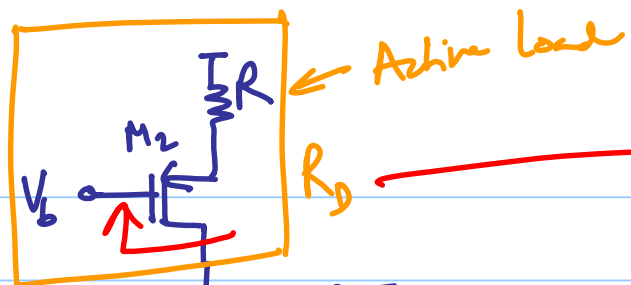
$$\approx - g_m R_D \quad \text{for } r_o \gg R_D$$




$R_D = g_{m2} r_{o2} R$

$$A_v = -g_{m1} (r_{o1} \parallel g_{m2} r_{o2} R)$$

$$\gamma = 0$$

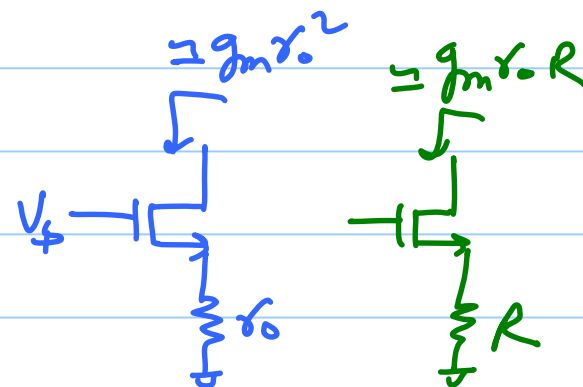

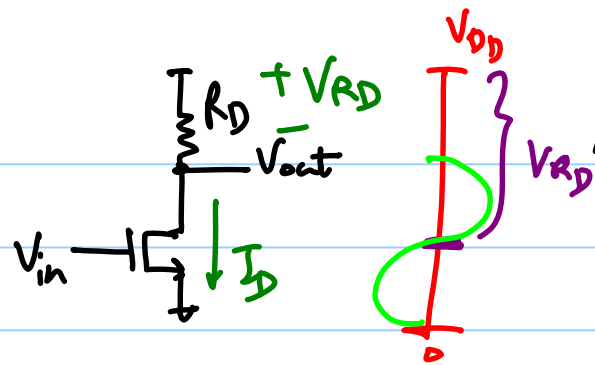

$$A_v = -g_{m1} R_D$$

$$= -\sqrt{2K_p \frac{W}{L} \cdot I_D} \cdot R_D$$

$$= -\sqrt{2k_n \frac{W}{L} I_D} \cdot \frac{V_{RD}}{I_D}$$

$$= -\sqrt{2K_p \frac{W}{L}} \cdot \frac{V_{RD}}{\sqrt{I_D}}$$

$$\underline{r_o \gg R_D}$$

How to increase $|A_v|$?




* $\frac{W}{L} \uparrow \rightarrow$ large device cap



* $V_{RD} \uparrow \rightarrow$ less swing

* $I_D \downarrow \Rightarrow$ lower speed

decouple R_D from V_{RD}

Diode Connected Load

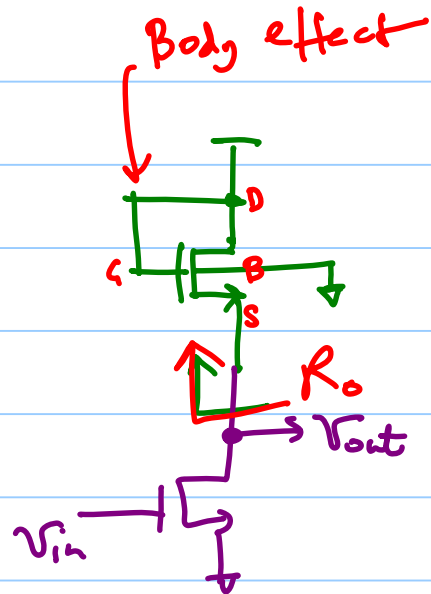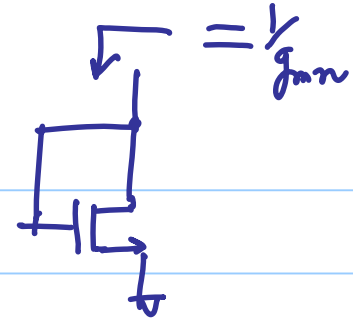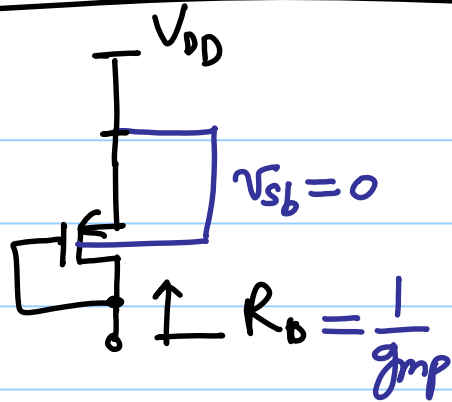

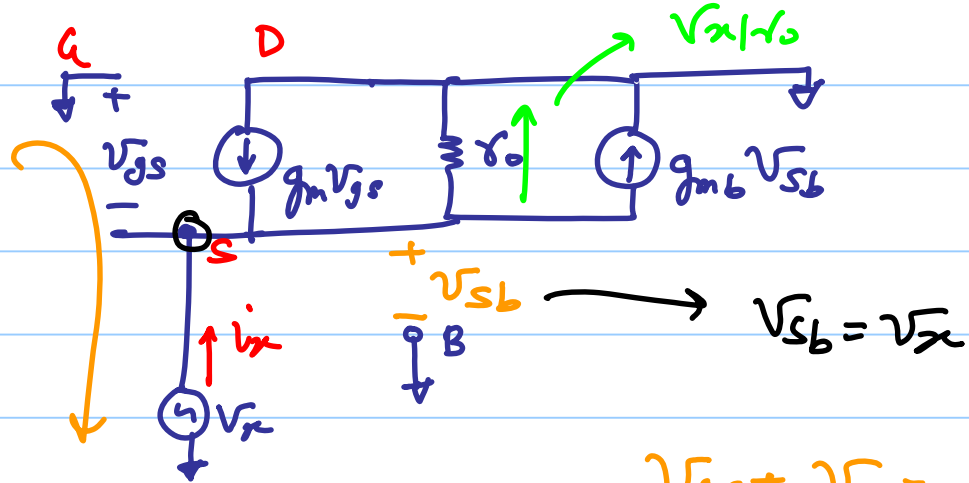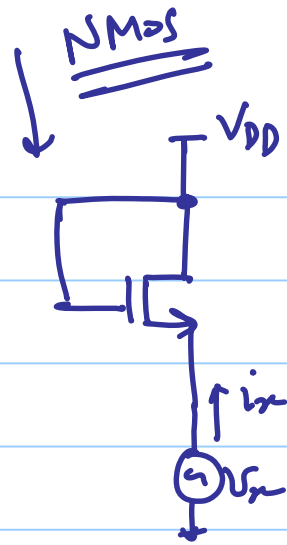

$$V_{gs} + V_x = 0$$

$$\Rightarrow V_{gs} = -V_x$$

①

KCL:

$$i_x + g_m V_{gs} - g_{mb} V_{sb} - \frac{V_x}{r_o} = 0$$

$$i_x - g_m V_x - g_{mb} V_x - \frac{V_x}{r_o} = 0$$

$$i_x = V_x \left[(g_m + g_{mb}) + \frac{1}{r_o} \right]$$


$$\Rightarrow R_x = \frac{V_x}{i_x} = \frac{1}{(g_m + g_{mb}) + \frac{1}{r_o}}$$

if $g_m \gg \frac{1}{r_o}$

$$\approx \frac{1}{(g_m + g_{m6})}$$

$$g_{m6} = \eta g_m$$

$$= \frac{1}{g_m (\eta + 1)}$$

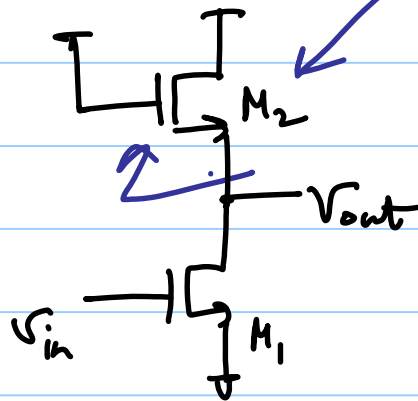

$$A_v = -g_{m1} \left(r_{o1} \parallel \left(\frac{1}{g_{m2}(\eta + 1)} \right) \right)$$

$$\approx -\frac{g_{m1}}{g_{m2}} \cdot \frac{1}{(\eta + 1)}$$

$$r_{o1} \gg \frac{1}{g_{m2}}$$





$$\Rightarrow A_v = -\sqrt{\frac{(W/L)_1}{(W/L)_2}} \cdot \frac{1}{(\eta + 1)}$$


$$\because g_m = \sqrt{2\beta I_D}$$

* Low small-signal gain

* Input/output characteristics is relatively linear

Razavi

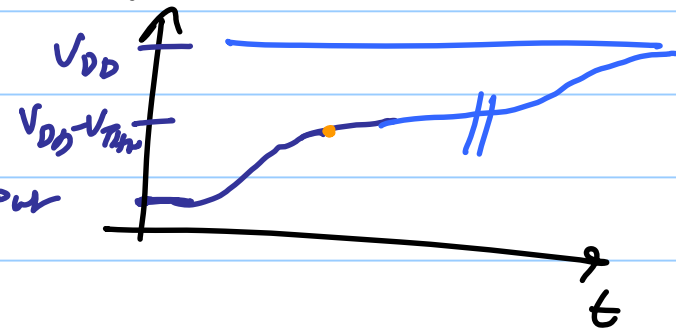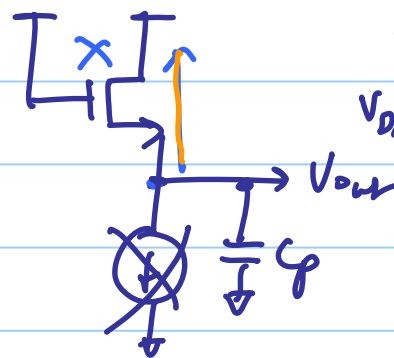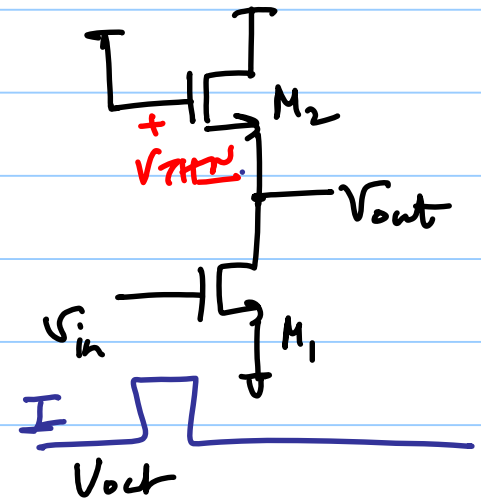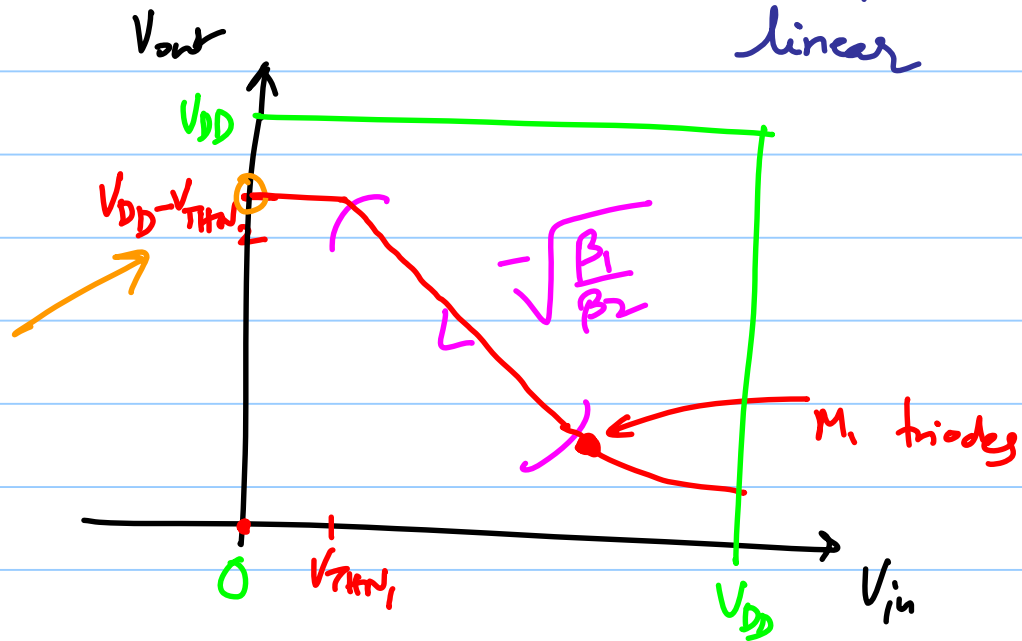

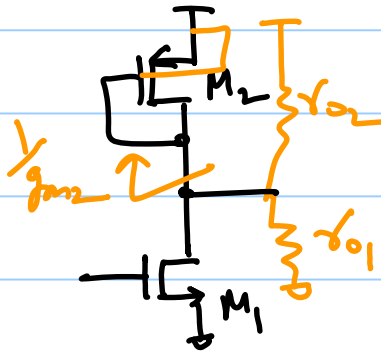


$$A_v \approx -g_{m1} (r_{o1} \parallel r_{o2} \parallel \frac{1}{g_{m2}})$$


$$\approx -\frac{g_{m1}}{g_{m2}}$$

if r_o 's are large

CS stage with current-source load

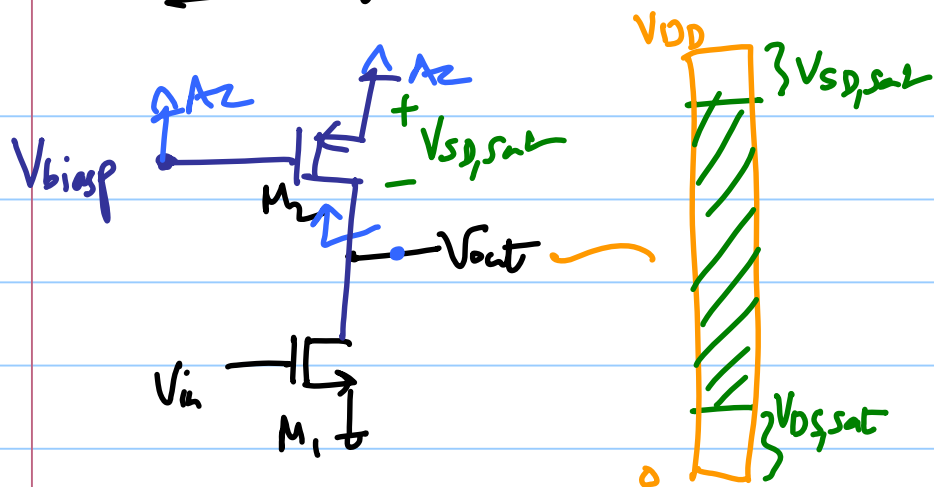

Az picture

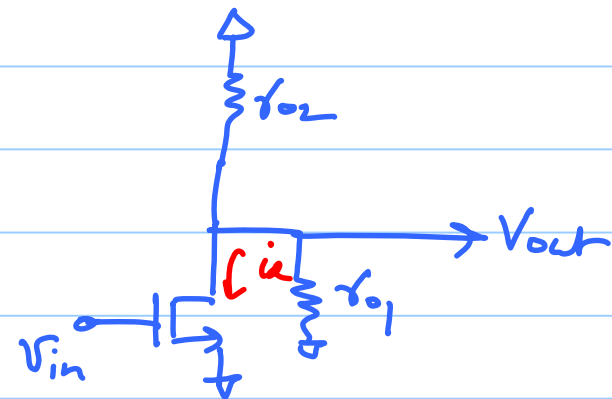


- * Large o/p swing
- * Large gain


$$V_{out} = -(g_m v_{in})(r_{o1} || r_{o2})$$

$$\Rightarrow \boxed{A_v = -g_m(r_{o1} || r_{o2})}$$

$$\approx -g_m \frac{r_o}{2}$$

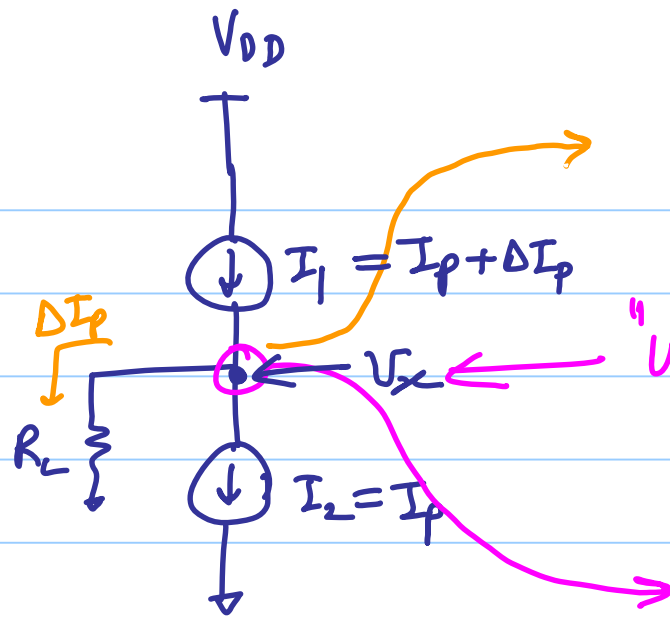

"Undefined in a practical circuit"

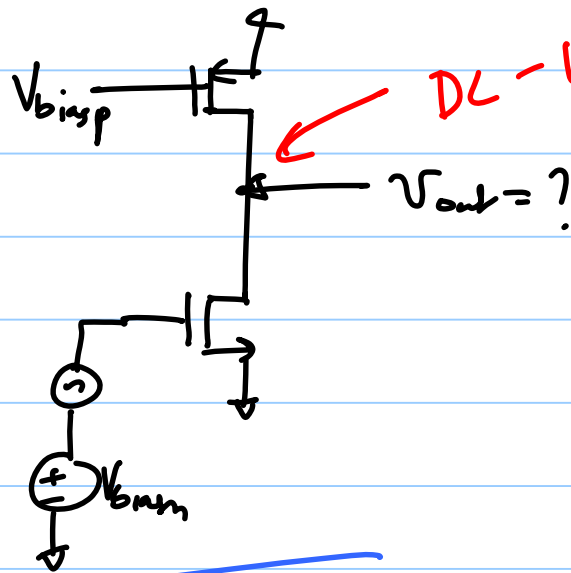

DC-level is underlined

