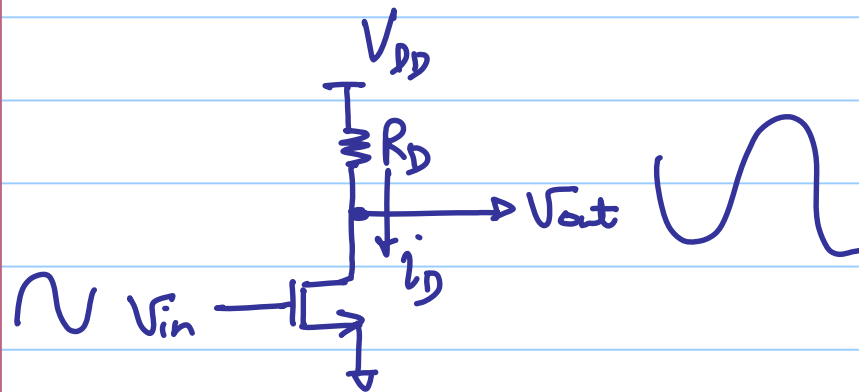


ECE 511 - Lecture 14

Note Title


3/6/2014



VCCS

$g_m R_D > 1$ voltage
small signal gain
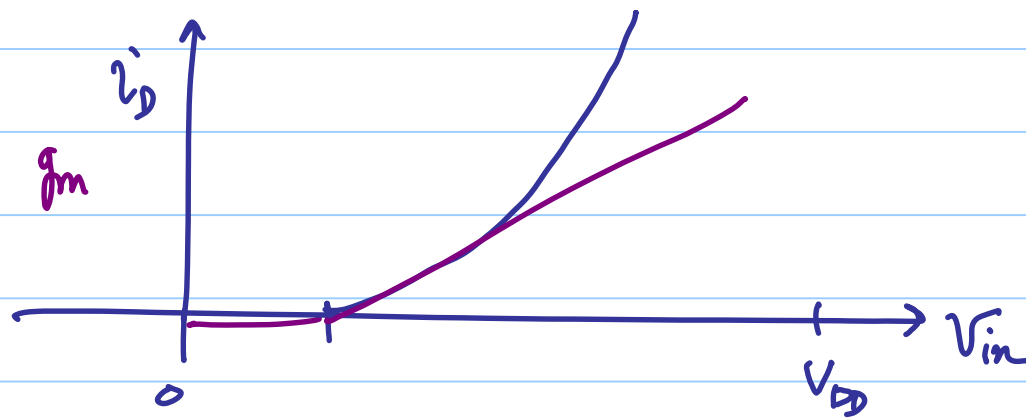
$$P_{avg} = \langle V_{DD} \cdot I_D \rangle$$




Large signal behavior

$$g_m = f(V_{in})$$

$$\Rightarrow A_v = g_m R_D$$

↳ non-linearity



C8 : Source Degeneration

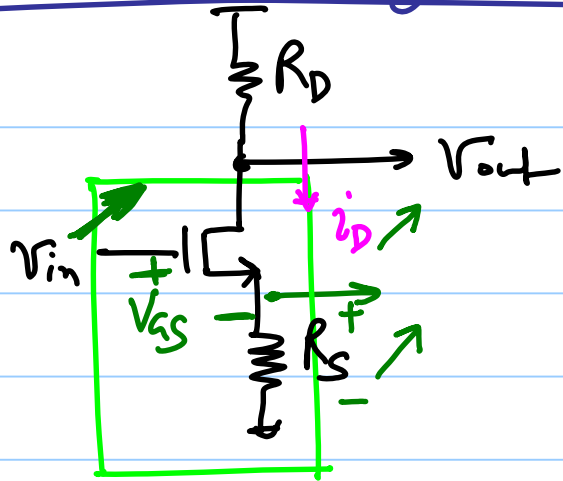

due to the -ve feedback
 V_{gs} is "almost" constant

$$i_D \approx \frac{V_{in} - V_{gs}}{R_S}$$

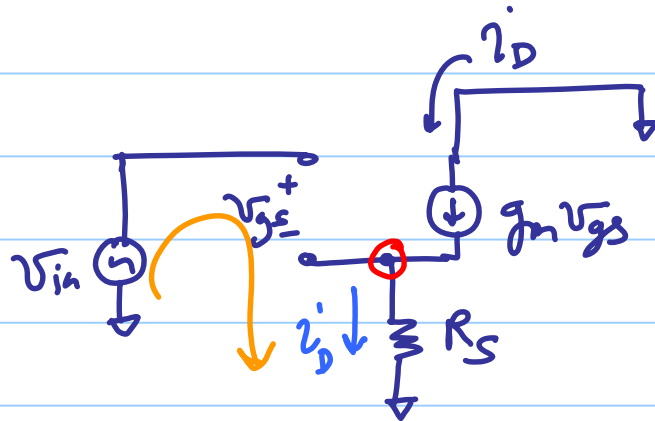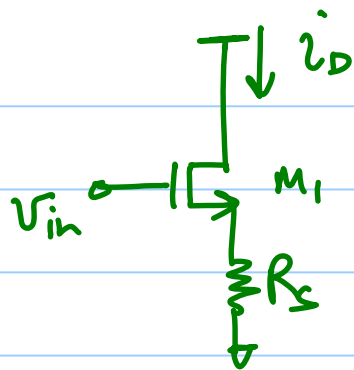large portion of V_{in} is dropped across the resistor
 $R_S \Rightarrow$ change in i_D is almost linear



$\lambda = 0, \gamma = 0$
Simplifying
assumption


KVL: $v_{gs} = V_{in} - i_D R_S \rightarrow \textcircled{1}$

KCL: $i_D = g_m v_{gs} \rightarrow \textcircled{2}$

$i_D = g_m (V_{in} - i_D R_S)$


$\Rightarrow i_D (1 + g_m R_S) = g_m V_{in}$
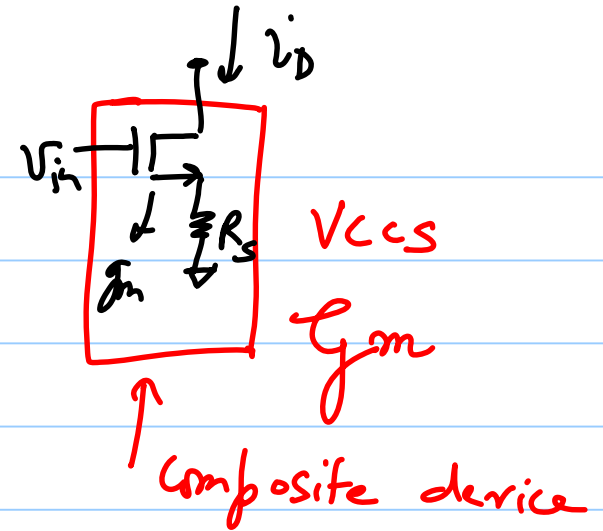
$$\boxed{\frac{i_D}{v_{in}} = \frac{g_m}{1 + g_m R_S} = g_m}$$



$$\boxed{g_m = \frac{g_m}{1 + g_m R_S}} = \frac{1}{R_S + \frac{1}{g_m}}$$

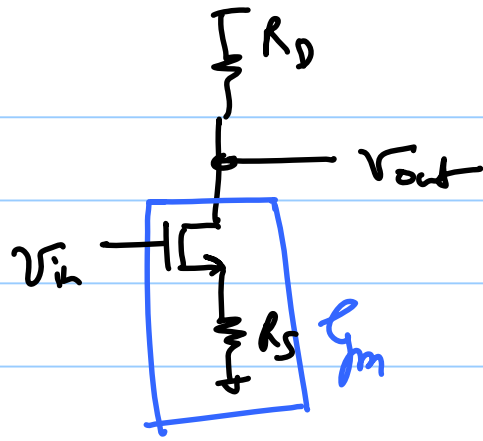for $R_S \gg \frac{1}{g_m} \Rightarrow g_m \approx \frac{1}{R_S}$ $\leftarrow$ g_m becomes a weak function of g_m
 $\Rightarrow$ drain current is a "linearized" function of v_{in} .
 $g_m \gg \frac{1}{R_S}$




$$A_v = -g_m R_D$$

$$= - \frac{g_m R_D}{1 + g_m R_S} \approx - \frac{R_D}{R_S} \quad \text{for } g_m \gg \frac{1}{R_S}$$

$\Rightarrow$ gain A_v is reduced by a factor of $(1 + g_m R_S)$

$\Rightarrow$ lower gain

Trading off linearity with gain.




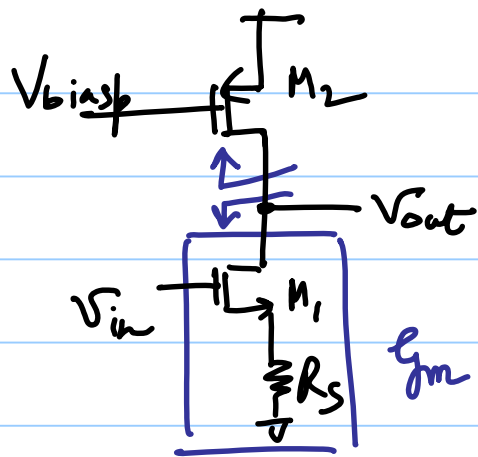




$$A = -g_m \cdot R_{out}$$


$$\frac{g_m}{1 + g_m R_S}$$

$$\rightarrow r_{o2} \parallel (r_{o1}, R_S)$$

from cascoding

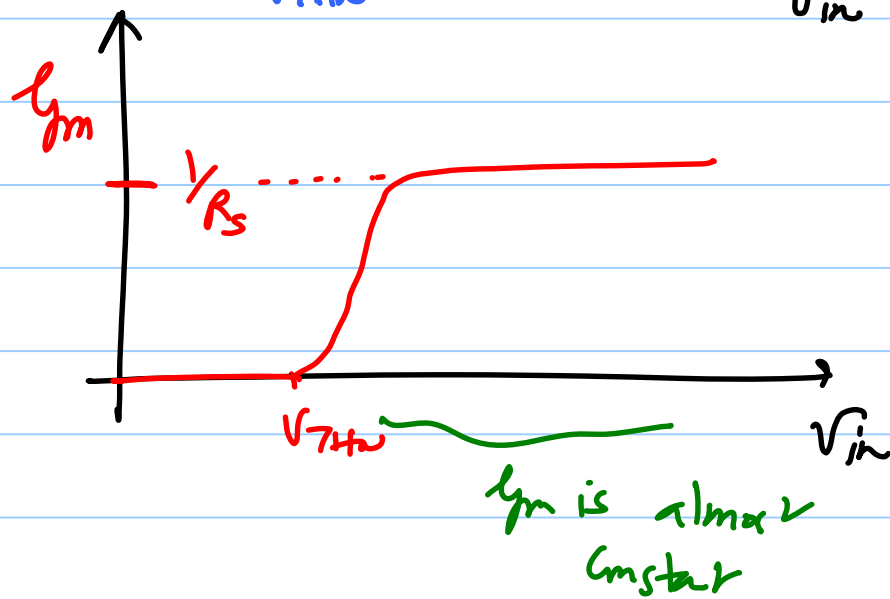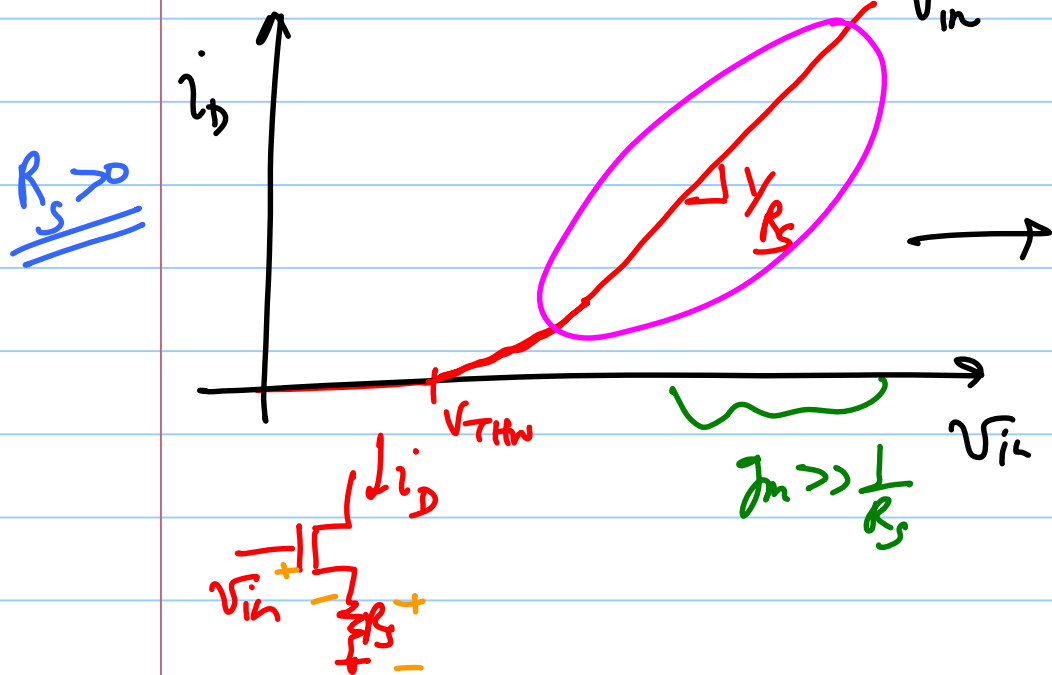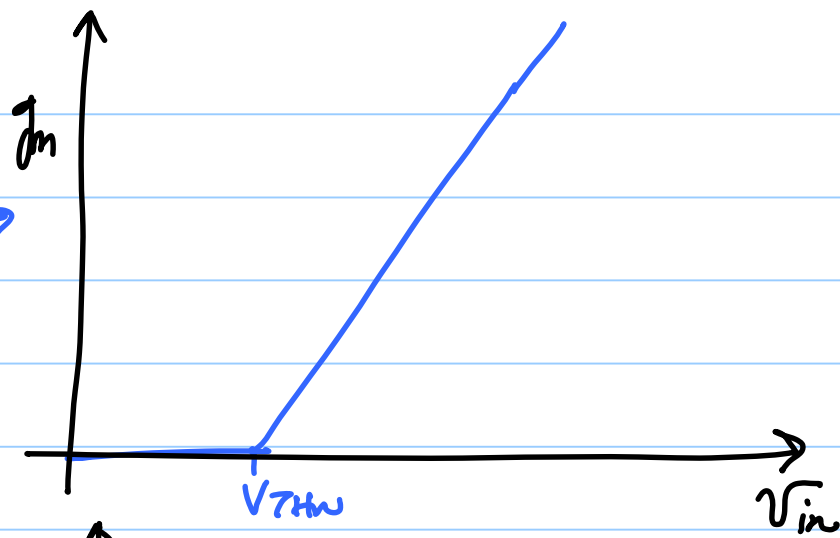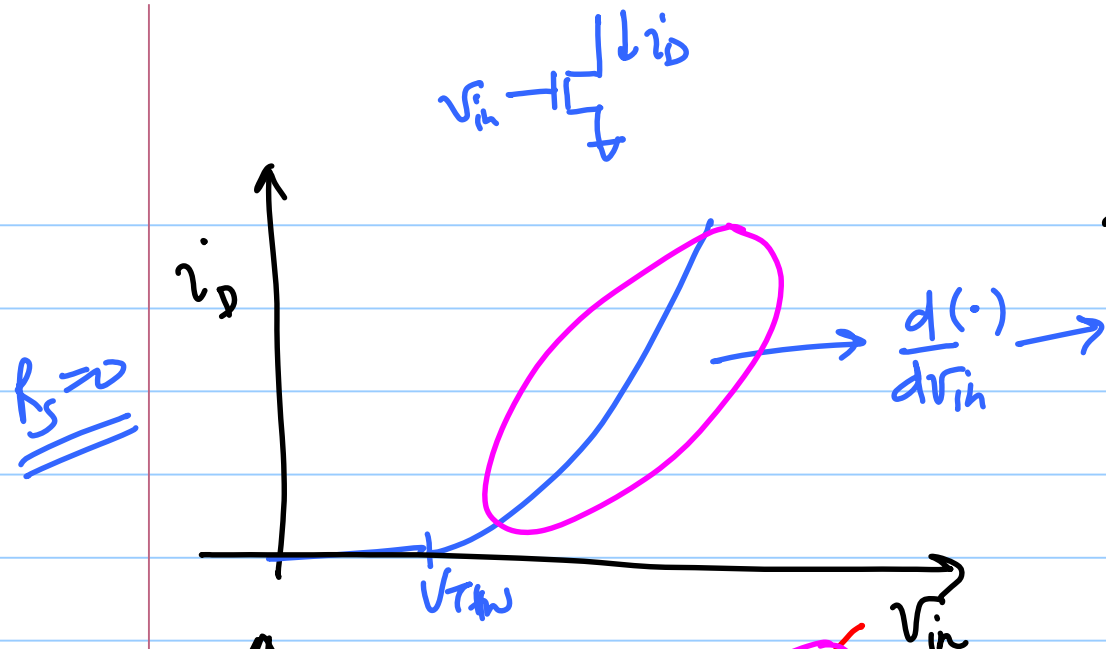

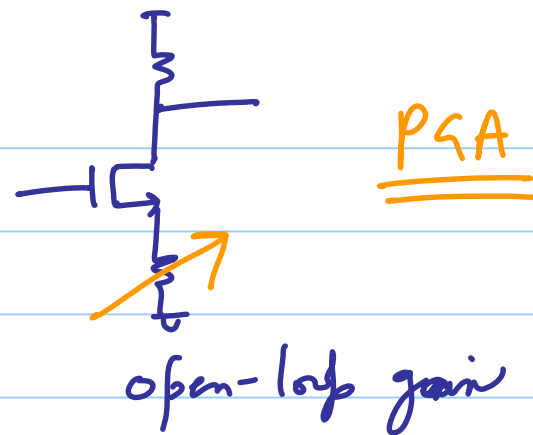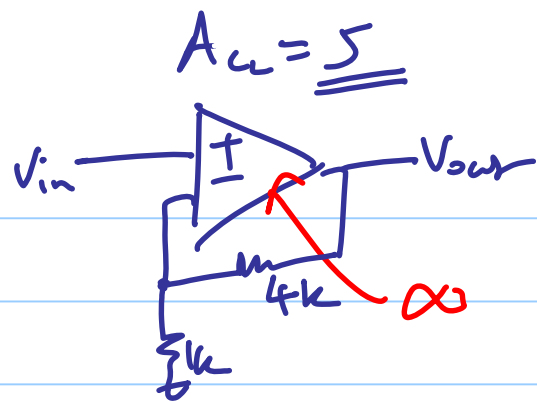



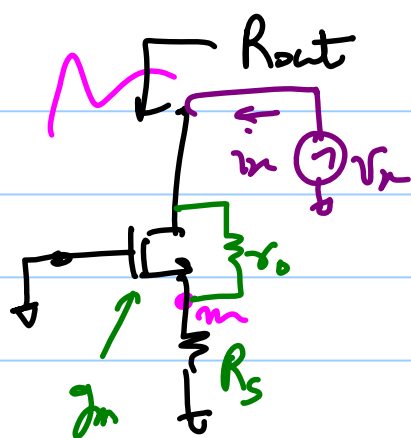



$$R_{out} = [1 + (g_m + \underline{g_{mb}}) R_s] r_o$$

$$\approx g_m R_s r_o$$

Razavi

Source follower (CD)

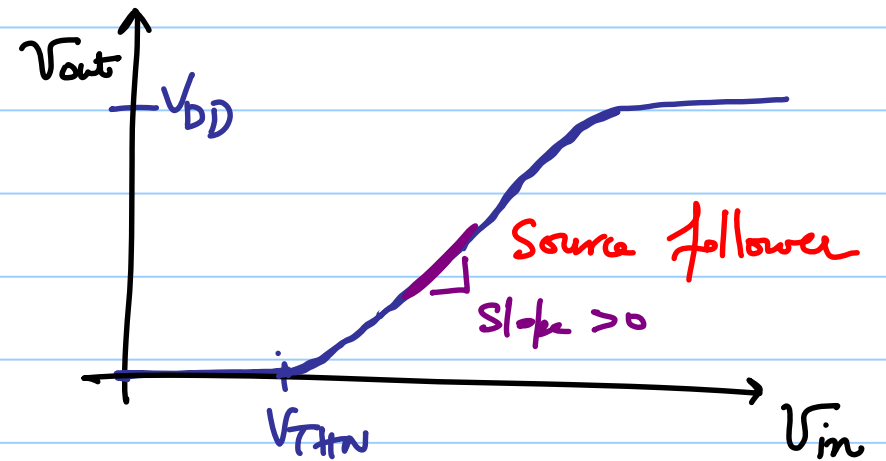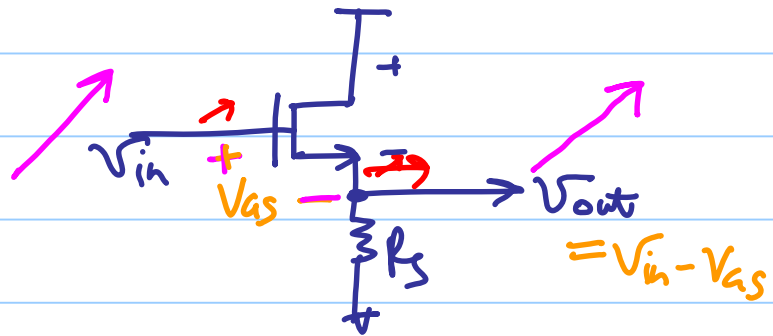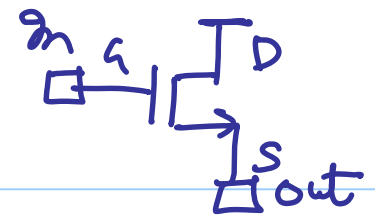

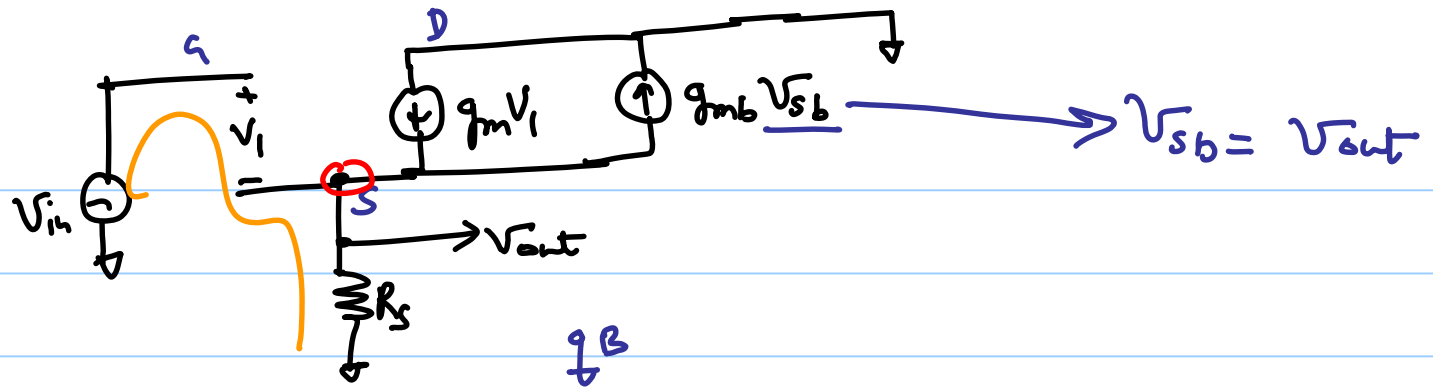

KVL: $V_{out} = V_{in} - V_1 \longrightarrow \textcircled{1}$

KCL: $g_m V_1 - g_{mb} V_{out} = \frac{V_{out}}{R_S} \longrightarrow \textcircled{2}$

$$g_m (V_{in} - V_{out}) - g_{mb} V_{out} = \frac{V_{out}}{R_S}$$

$$\Rightarrow V_{out} [g_m + g_{mb} + \frac{1}{R_S}] = g_m V_{in}$$

$$\Rightarrow A_v = \frac{V_{out}}{V_{in}} = \frac{g_m R_S}{1 + (g_m + g_{mb}) R_S}$$

non-inverting "gain"


$$g_{m6} = \eta g_m \quad \nearrow 0.7$$



$$\frac{g_m R_s}{1 + (\eta + 1) g_m R_s}$$

$$\approx \frac{1}{(\eta + 1) + \frac{1}{g_m R_s}}$$


$$\approx \boxed{\frac{1}{\eta + 1}} \text{ for } g_m R_s \gg 1$$

$$\boxed{A_v < 1}$$

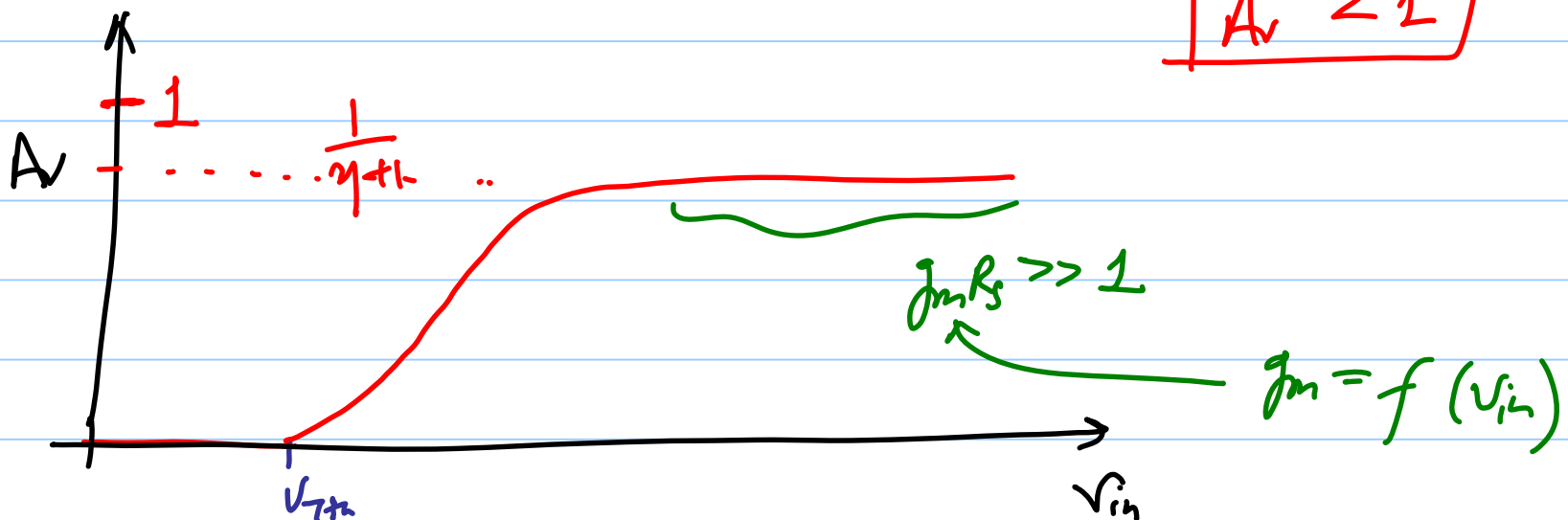

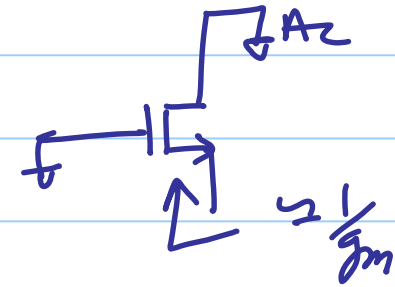
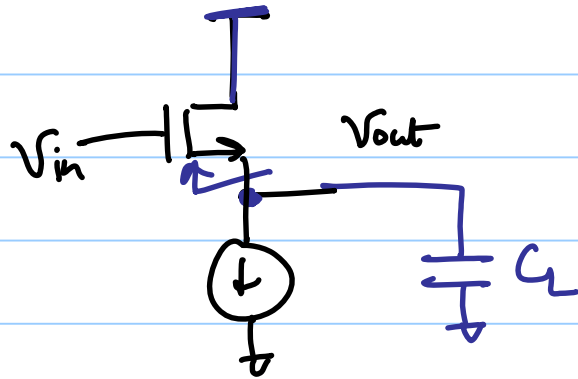


"Voltage Buffer"

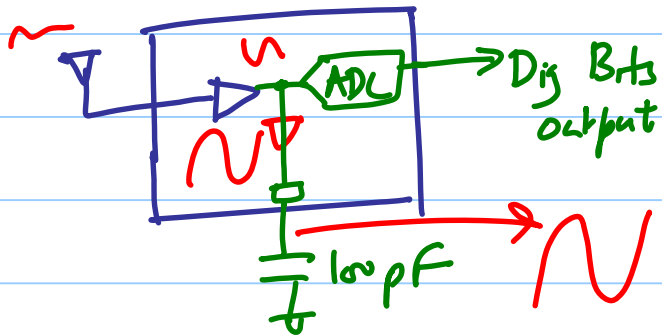


Analog Buffer
"Test Circuit"



"DC level shifting"

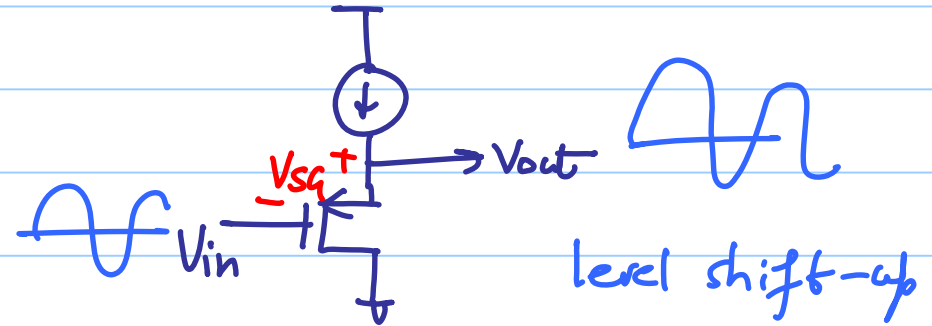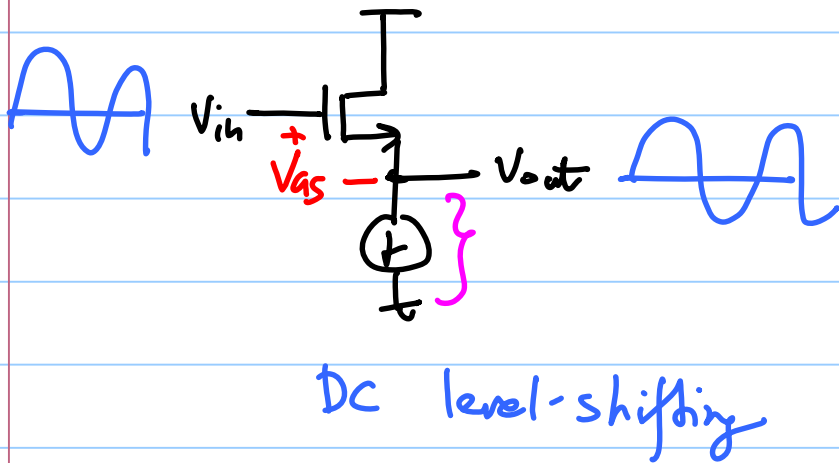

Voltage
limited headroom

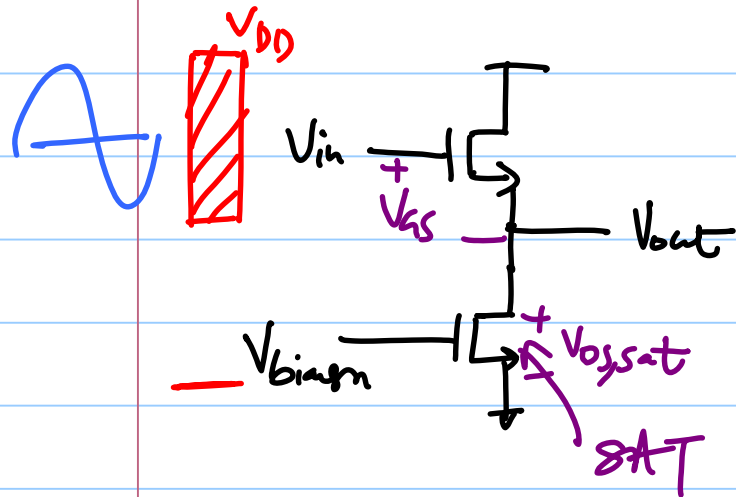

$$V_{in} \geq V_{gs} + V_{ds,sat}$$

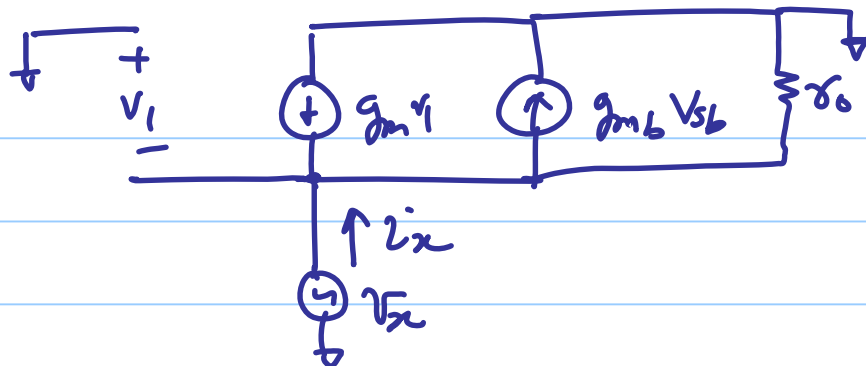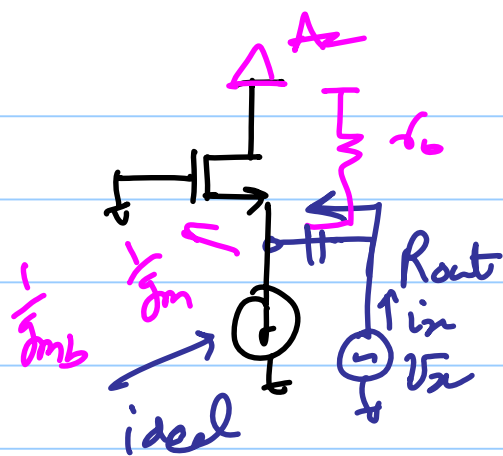

$$i_x - g_m v_x - g_{mb} v_x + \frac{v_x}{R_S} = 0$$


$$R_{out} = \frac{v_x}{i_x} = \frac{1}{g_m + g_{mb} + \frac{1}{R_S}}$$

$$R_{out} = \frac{1}{\frac{1}{g_m} \parallel \frac{1}{g_{mb}} \parallel R_S} \approx \frac{1}{\frac{1}{g_m} \parallel \frac{1}{g_{mb}}}$$

"Low 'output impedance'"

Voltage Buffer

VCVS, $gain = 1$

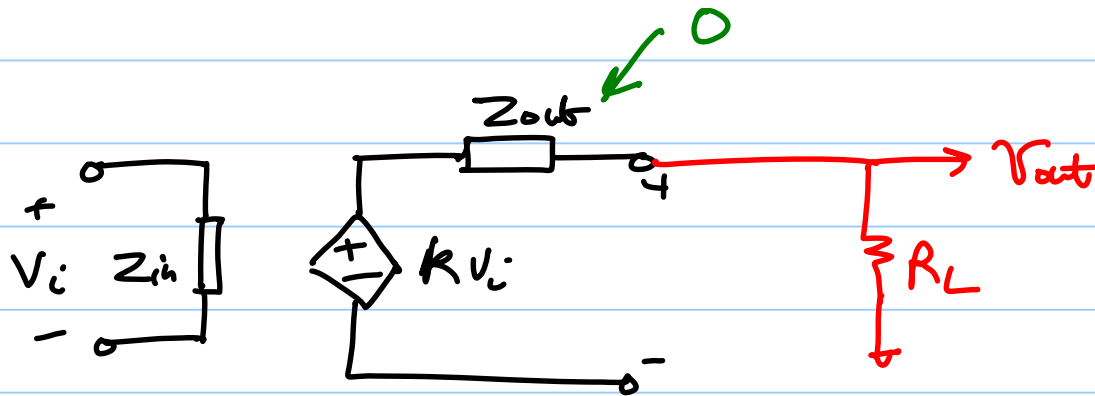

$$V_{out} = \left(\frac{R_L}{R_L + Z_{out}} \right) kV_i$$

$\Rightarrow$ ideally want $Z_{out} = 0$

$\Rightarrow$ sf $Z_{out} = \frac{1}{\infty} \Rightarrow$ Voltage Buffer

