
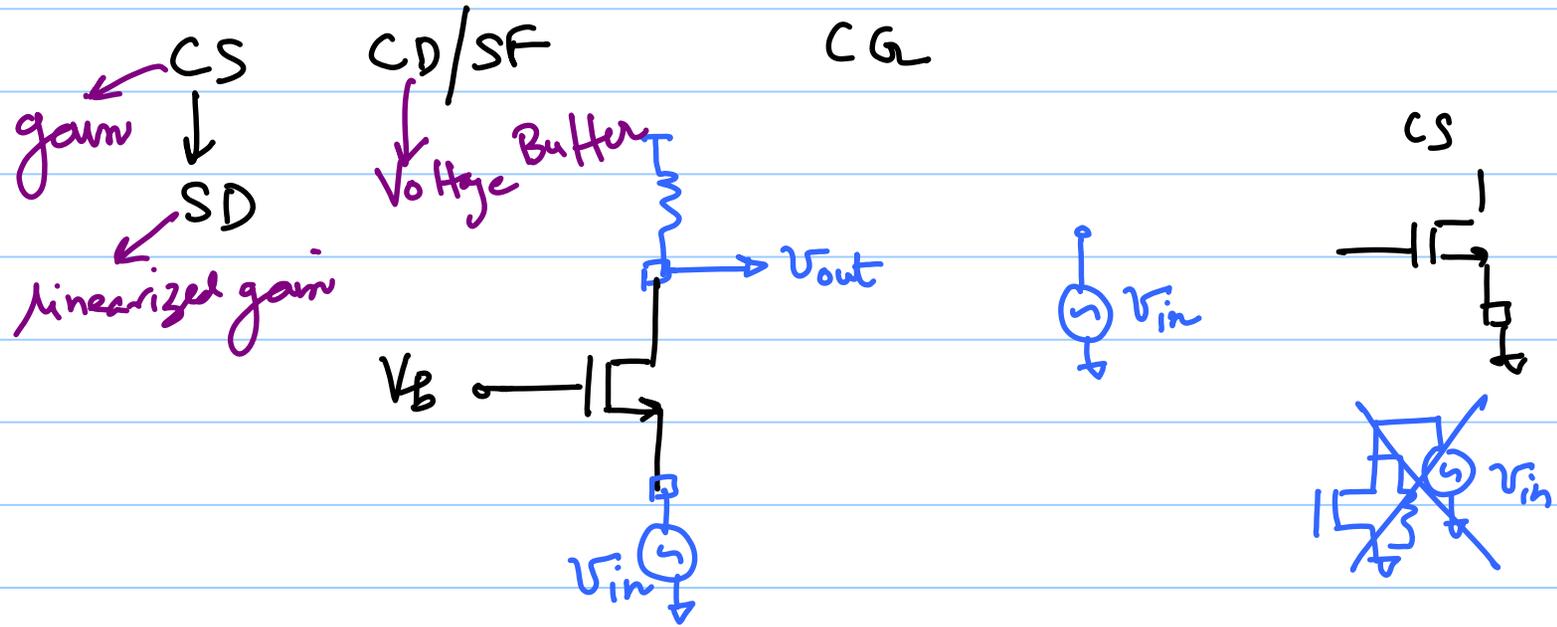


Lecture 15 - ECE 511


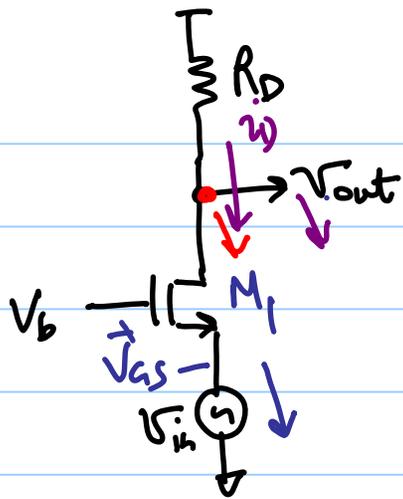




\Rightarrow the small signal gain

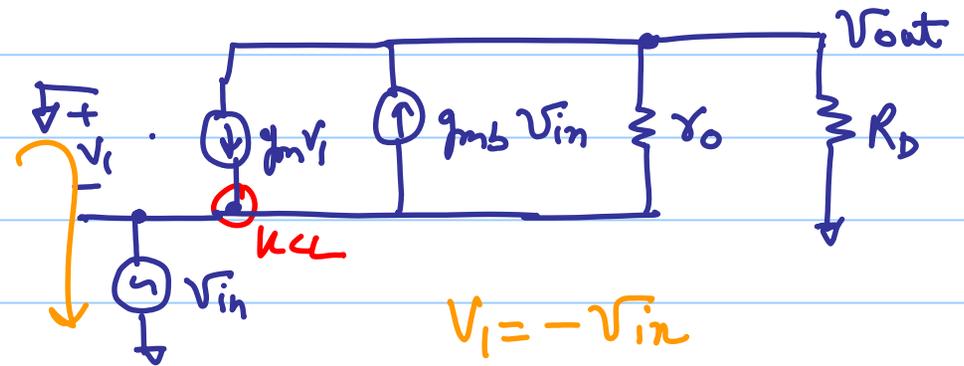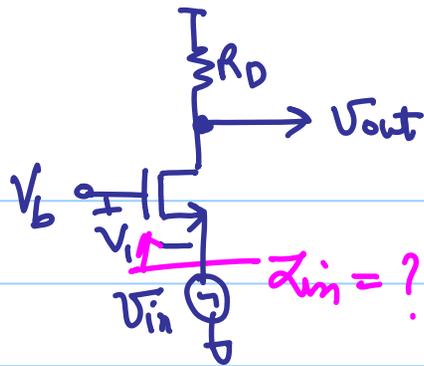M_1 triodes
 M_1 is in SAT
 $V_b - V_{THTN}$
 M_1 is cutoff





$$-g_m V_i + g_m b V_{in} - \frac{(V_{out} - V_{in})}{r_o} - \frac{V_{out}}{R_D} = 0$$

$$\Rightarrow (g_m + g_m b) V_{in} + \frac{V_{in}}{r_o} = \frac{V_{out}}{r_o} + \frac{V_{out}}{R_D}$$

$$\Rightarrow V_{in} \left(\frac{1}{r_o} + (g_m + g_m b) \right) = \frac{V_{out}}{r_o \parallel R_D}$$

$$\Rightarrow A_v = \frac{V_{out}}{V_{in}} = \left[(g_m + g_m b) + \frac{1}{r_o} \right] \cdot (R_D \parallel r_o)$$

$$A_v = \frac{(g_m + g_{m_b}) r_o + 1}{r_o} \cdot \frac{R_D r_o}{R_D + r_o}$$

$$= \frac{(g_m + g_{m_b}) r_o + 1}{R_D + r_o} \cdot R_D$$

for $r_o \gg R_D$




$$(g_m + g_{m_b}) r_o \gg 1$$



$$A_v \approx (g_m + g_{m_b}) R_D$$

CG $A_v = + (1 + \eta) g_m R_D$ ← Low Z_{in}

$$g_{m_b} = \eta g_m$$

CS $A_v = - g_m R_D$ ← High Z_{in}

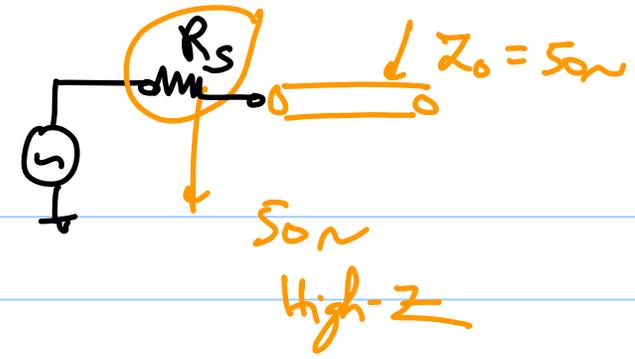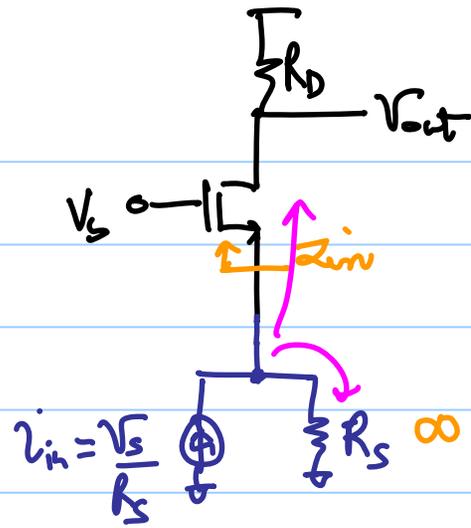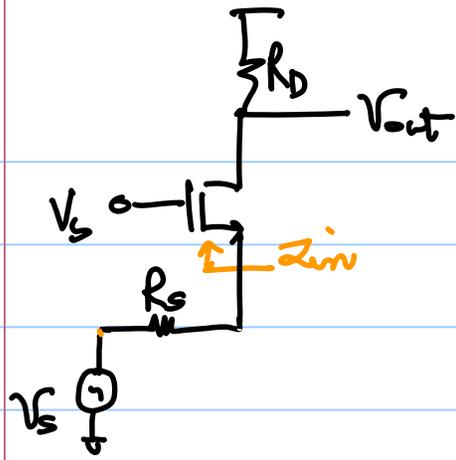

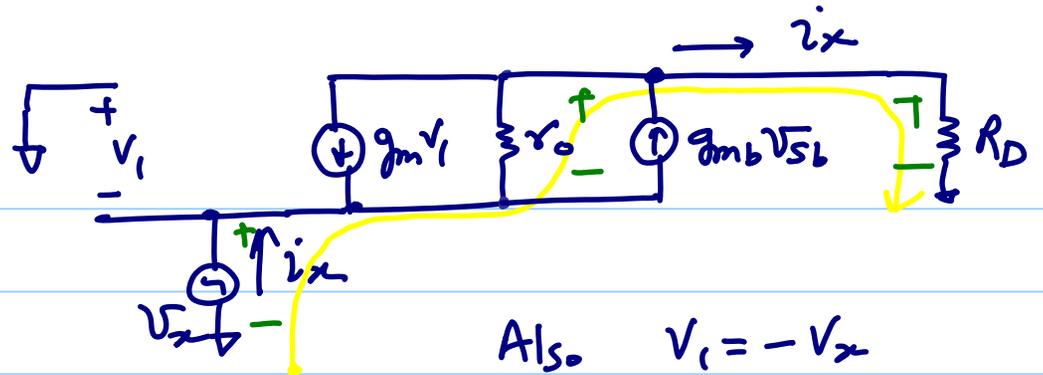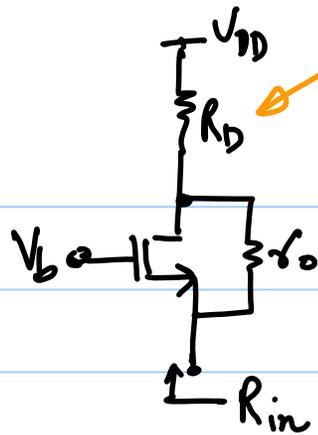

$$\begin{aligned} \neq \text{Current thru } r_o &\Rightarrow i_x + g_m V_i + g_{mb} V_i \\ &= i_x - (g_m + g_{mb}) V_x \longrightarrow \textcircled{1} \end{aligned}$$

Add up all the voltages across r_o & R_D

$$R_D i_x + r_o [i_x - (g_m + g_{mb}) V_x] = V_x$$



$$\Rightarrow R_{in} = \frac{V_x}{i_x} = \frac{R_D + r_o}{1 + (g_m + g_{mb}) r_o}$$

$$(g_m + g_{mb}) r_o \gg 1$$

$$R_{in} \approx \frac{R_D}{(g_m + g_{mb}) r_o} + \frac{1}{(g_m + g_{mb})}$$

Special cases:

Ⓐ $R_D = 0$

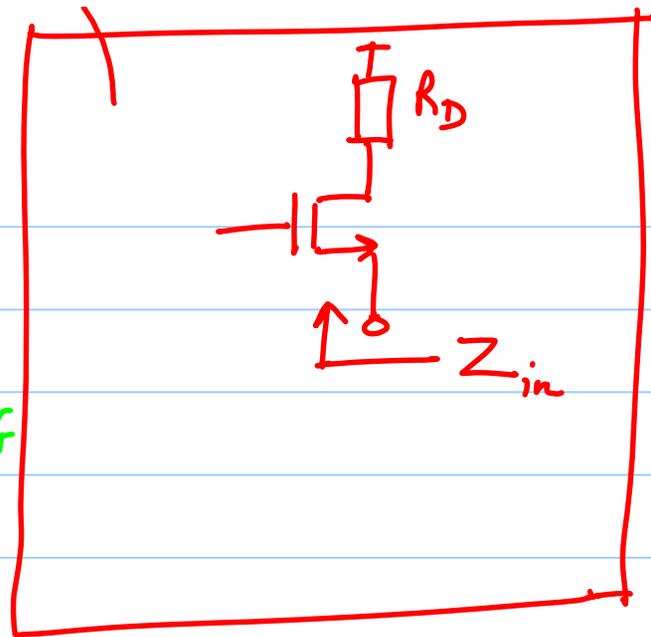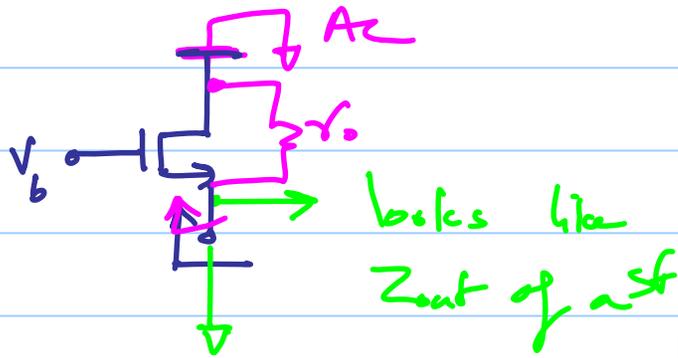

$$R_{in} = \frac{r_o}{1 + (g_m + g_{mb})r_o}$$

$$= \frac{1}{\frac{1}{r_o} + (g_m + g_{mb})} \approx r_o \parallel \frac{1}{(g_m + g_{mb})} \approx \frac{1}{(g_m + g_{mb})}$$



$$r_o \gg \frac{1}{g_m}$$

$$\Rightarrow g_m r_o \gg 1$$

② $R_D \ll r_o$

$$R_{in} \approx \frac{R_D \rightarrow r_o}{(g_m + g_{mb})r_o} + \frac{1}{(g_m + g_{mb})}$$

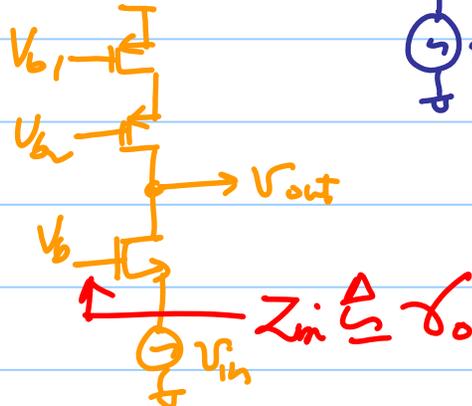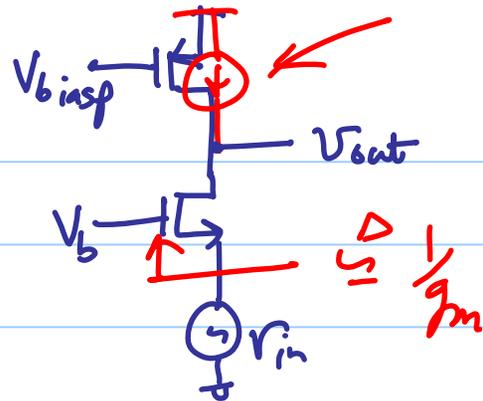
$$\approx \frac{2}{(g_m + g_{mb})} \triangleq \frac{1}{g_m}$$



③ $R_D \triangleq g_m r_o^2$

$$R_{in} = \frac{g_m r_o^2}{(g_m + g_{mb})r_o} + \frac{1}{(g_m + g_{mb})} = \frac{r_o}{(\eta + 1)} + \frac{1}{(\eta + 1)g_m} \triangleq r_o$$


Razavi

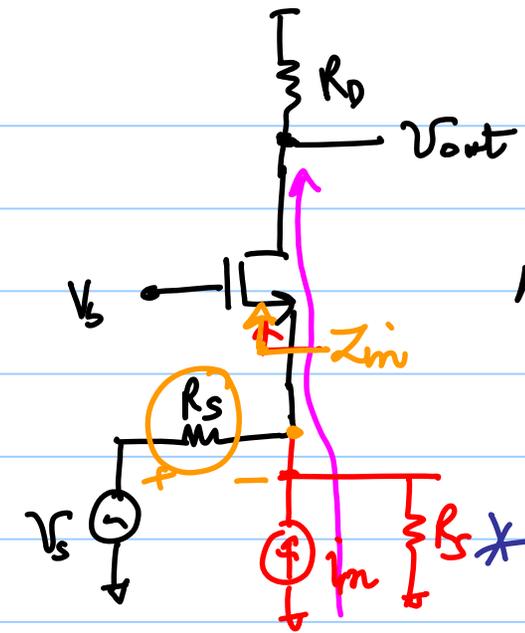

$$A_v = \frac{(g_m + g_{m_b})r_o + 1}{r_o + (g_m + g_{m_b})r_o R_S + R_S + R_D} \cdot R_D$$

* Not a great voltage amplifier

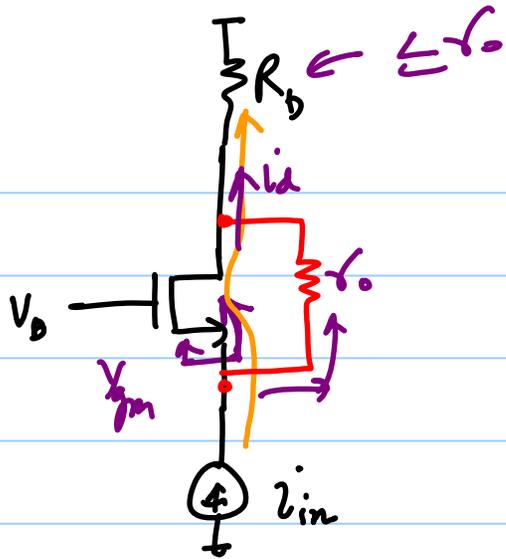$Z_{in} \rightarrow \text{low}$ (we want high Z_{in})



$$\frac{1}{g_m} \leftarrow r_o$$




$$\Rightarrow r_d \approx r_{in}$$

"acts like a current conveyor"
 "current buffer"

Red from Razavi
 on CB

Amplifier Type	Gain	Z_{in}	Z_{out}	Application
CS	Large ($\gg 1$)	∞	Moderate	Amplifier stage
CS+SD	Moderate	∞	High/moderate	Linear Amplifier
CD/SF	low (< 1)	∞	Low (≈ 1)	Voltage Buffer
CA	Medium/high	Low	moderate/high	Current Buffer

Cascode stage

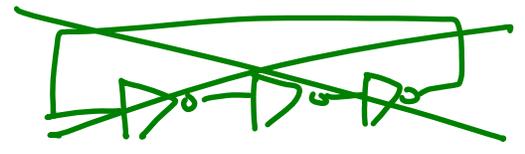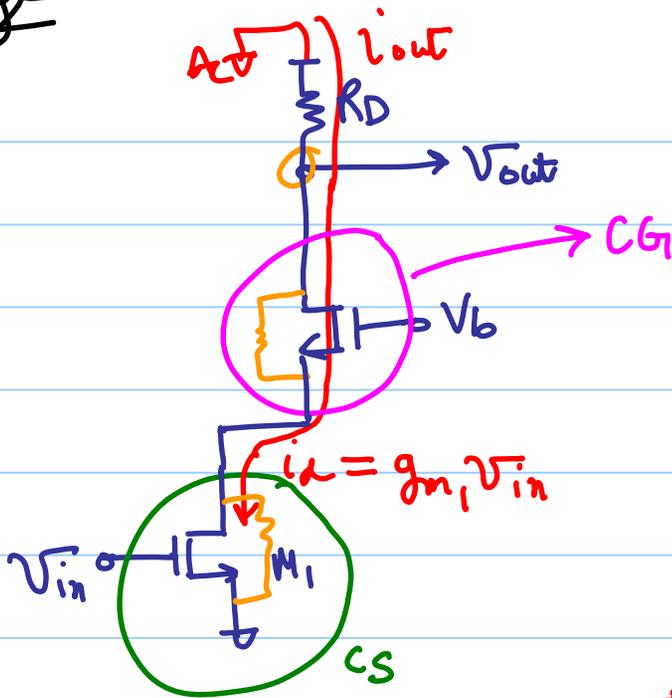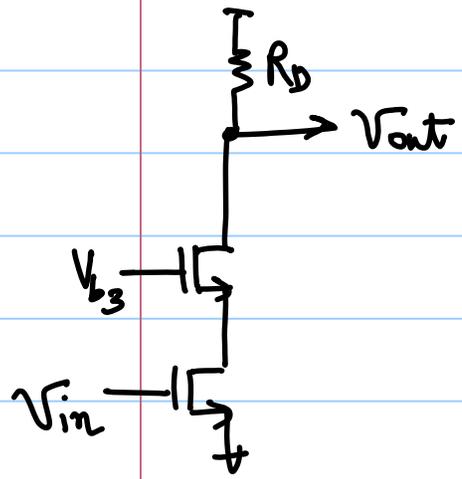



$r_o = \infty$
 $\lambda = 0$

$$V_{out} \approx -i_{out} \cdot R_D$$

$$= -g_{m1} V_{in} R_D$$

$$\Rightarrow |A_v| \approx -g_{m1} R_D$$
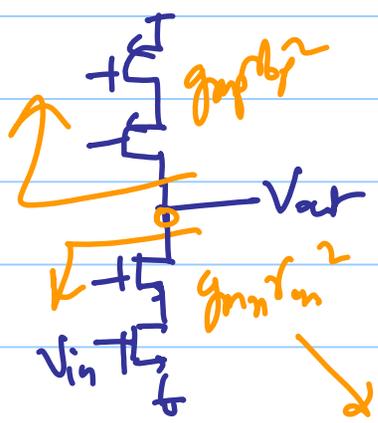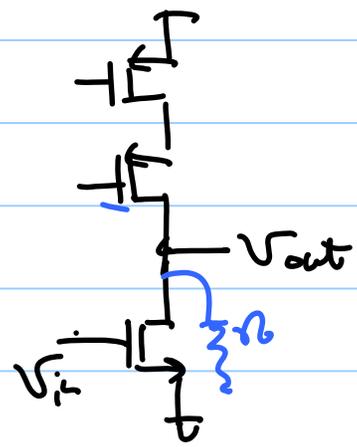
$$(g_{mp} r_{op}^2) \parallel (g_{mn} r_{on}^2)$$



$$A_v = -g_{m1} (r_{o1} \parallel g_{m1} r_{o1}^2) \approx -g_{m1} r_{o1}$$

$$A_v = -g_{m1} (g_{m1} r_{op}^2) \parallel (g_{m1} r_{on}^2)$$

Lemma

In a linear circuit voltage gain $= -g_m R_{out}$

where $g_m \Rightarrow$ transconductance when the o/p is shorted to ground.

and $R_{out} \Rightarrow$ o/p resistance of the circuit when the i/p is set to zero.

