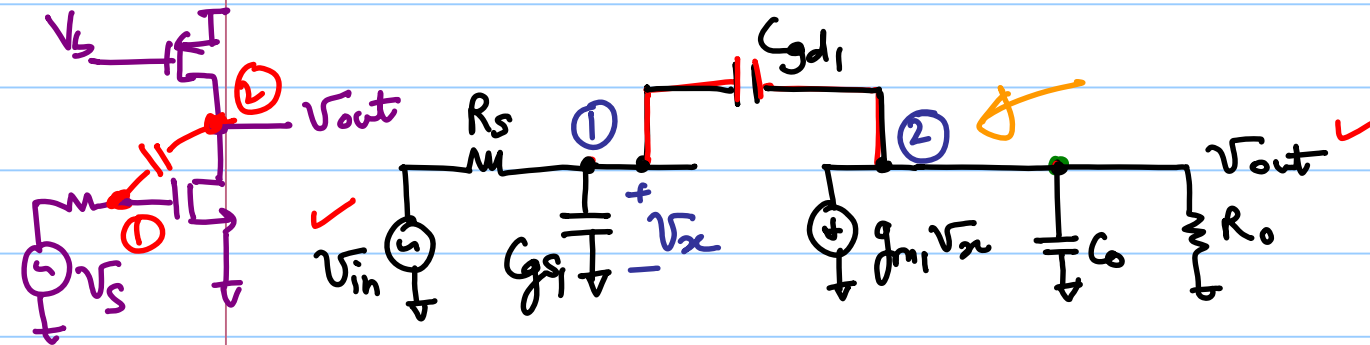


ECE 511 - Lecture 17

Note Title

3/20/2014



$$R_o = r_{o1} || r_{o2}$$

$$C_o = C_{db} + C_{gd} + \dots$$

Solve for V_x and substitute in ②

$$V_x = - \frac{V_{out} (C_{gd}s + \frac{1}{R_o} + C_o s)}{g_{m1} - sC_{gd}}$$

$$\frac{V_{out}}{V_{in}}(s) = \frac{\boxed{(C_{gd}s - g_{m1})R_o} \leftarrow N}{\underbrace{\left\{ R_s \xi s^2 + [R_s(1 + g_{m1}R_o)C_{gd} + R_sC_{gs} + R_o(C_{gd} + C_o)]s + 1 \right\}}_{D \Rightarrow}}$$

2nd-order Transfer Function

where $\xi = C_{gs}C_{gd} + C_{gs}C_o + C_{gd}C_o$

$N^r \Rightarrow$

$$(s C_{gd1} - g_{m1}) R_o = \underbrace{-g_{m1} R_o}_{\text{DC gain} \rightarrow A_v} \left(1 - \frac{s}{\omega_z} \right)$$

zero at $s = \omega_z = + \frac{g_{m1}}{C_{gd1}}$

$\boxed{\omega_z = + \frac{g_{m1}}{C_{gd1}}}$ RHP zero

RHP zero

$$\omega_z = \frac{g_{m1}}{C_{gd1}}$$

zero

"In Bode phase plot an RHP zero pulls the phase down by 90° "

$D^s \Rightarrow 2^{nd}$ -order system $\Rightarrow$ two-poles $\rightarrow$ real or complex - conjugate


If we assume $|\omega_{p1}| \ll |\omega_{p2}|$

then

$$D(s) = \left(1 + \frac{s}{\omega_{p1}}\right) \left(1 + \frac{s}{\omega_{p2}}\right)$$

Assumption
 $\Rightarrow$ poles are real
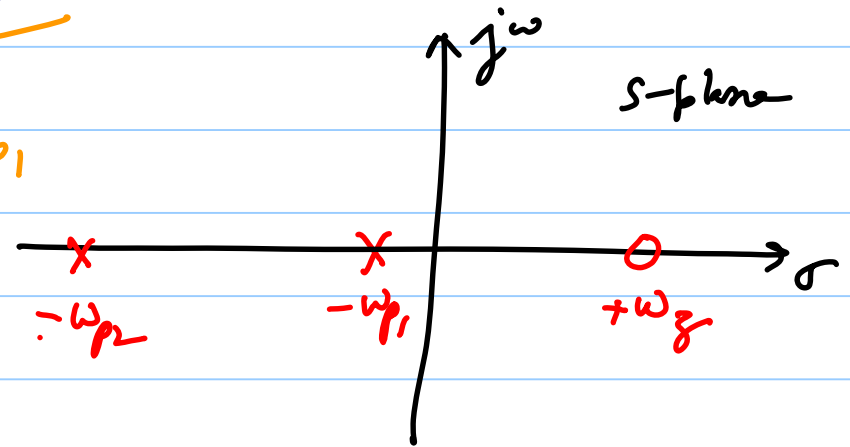
$$\Rightarrow D(s) = \underbrace{\frac{s^2}{\omega_{p1}\omega_{p2}}}_{\approx \frac{s}{\omega_{p1}}} + \left(\frac{1}{\omega_{p1}} + \frac{1}{\omega_{p2}}\right)s + 1$$



Since $\omega_{p1} \ll \omega_{p2}$

$$\Rightarrow \frac{1}{\omega_{p1}} \gg \frac{1}{\omega_{p2}}$$

$$\Rightarrow \text{coeff}^n \text{ of 's'} \approx \frac{1}{\omega_{p1}}$$

$$\omega_{p2} = \frac{1}{R_S(1 + \underbrace{g_{m1}R_o}_{|A_v|})C_{gd1} + R_S C_{gs1} + \boxed{R_o(C_{gd1} + C_o)}} \quad \leftarrow$$

$\uparrow$ C_{in} from Miller

Extra term
 $\hookrightarrow$ Contribution from mode (2)

①

2nd pole

Effⁿ for s^2 was $(\omega_{p1} \cdot \omega_{p2})^{-1}$

$$\Rightarrow \omega_{p2} = \frac{1}{\omega_{p1}} \times \frac{1}{R_S R_o \xi}$$

$$= \frac{1}{\omega_{p1}} \times \frac{1}{R_S R_o [C_{gs1} C_{gd1} + C_{gs1} C_o + C_{gd1} C_o]}$$

$$\Rightarrow \omega_{p2} = \frac{R_s (1 + g_m R_o) C_{gd1} + R_s C_{gs1} + R_o (C_{gd1} + C_o)}{R_s R_o [C_{gs1} C_{gd1} + C_{gs1} C_o + C_{gd1} C_o]} \quad \text{--- (2)}$$

if $C_{gs1} \gg (1 + g_m R_o) C_{gd1} + \frac{R_o}{R_s} (C_{gd1} + C_o)$

$$\omega_{p2} \approx \frac{1}{R_o (C_{gd1} + C_o)} \quad \Leftarrow \text{Same as } \omega_{out}$$

Valid only when C_{gs1} dominates
the response

↳ otherwise not


$$\frac{V_{out}}{V_{in}}(s) = \frac{A_v \left(1 - \frac{s}{\omega_z}\right)}{\left(1 + \frac{s}{\omega_{p1}}\right) \left(1 + \frac{s}{\omega_{p2}}\right)},$$

$$A_v = -g_{m1} R_o$$

Zero

$$\omega_z = + \frac{g_{m1}}{C_{gd1}} \Rightarrow \text{RHP zero}$$

Az picture

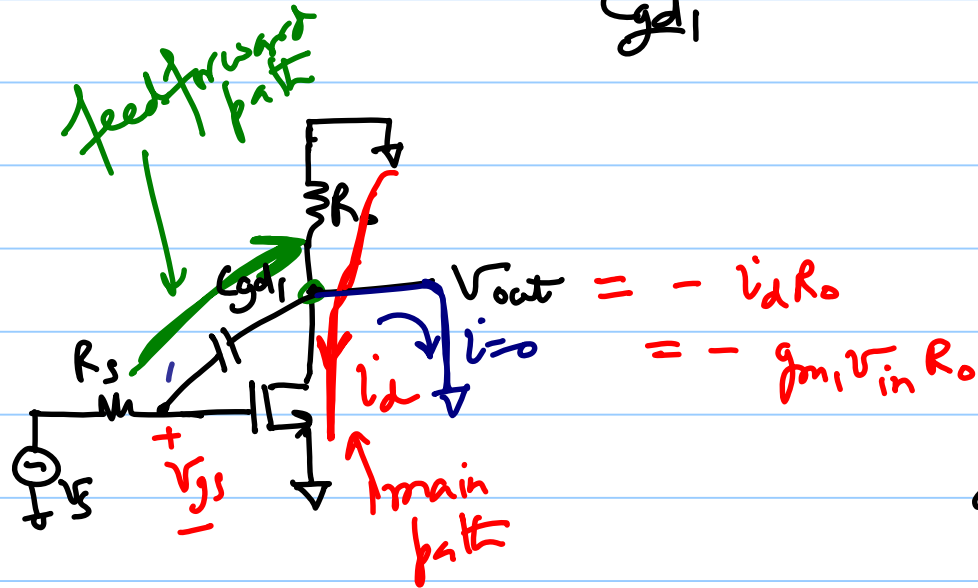

at $\omega = \omega_z \Rightarrow$ net Az current = 0

$$\text{at } s = s_z \Rightarrow \frac{V_{out}}{V_{in}}(s) = 0$$

$$\Rightarrow A_v \approx \text{finite } V_{in} \Rightarrow \underline{\underline{V_{out}(s_z) = 0}}$$

$$\cancel{g_{m1} v_{gs}} = \frac{v_{gs}}{1/s_z C_{gd1}} = s_z C_{gd1} \cancel{v_{gs}}$$

$$S_z = + \frac{g_{m1}}{C_{gd1}}$$

* RHP zero reduces phase

⇒ @ high frequencies the signal thru C_{gd1} adds to the main path in the opposite phase

* also $\omega = \omega_z \Rightarrow$ net AC current to $V_{out} \Rightarrow 0$

"Pole Splitting"

$$\omega_z = \frac{g_{m1}}{C_{gd1}}$$

$$\omega_{p1} = \frac{1}{R_s [(1 + |A_v|) C_c + C_{gs1}] + R_o (C_c + C_o)}$$



$$\omega_{p2} = \frac{R_s (1 + g_m R_o) C_c + R_s C_{gs1} + R_o (C_c + C_o)}{R_s R_o [C_{gs1} C_c + C_{gs1} C_o + C_c C_o]}$$

① $C_c = 0$ & large C_o

$$\omega_{p1} \approx \frac{1}{R_s C_{gs1} + R_o C_o}$$

$$\omega_{p2} \approx \frac{R_s C_{gs1} + R_o C_o}{R_s R_o C_{gs1} C_o} \approx \frac{1}{R_o C_o}$$

$$\omega_z \rightarrow \infty$$

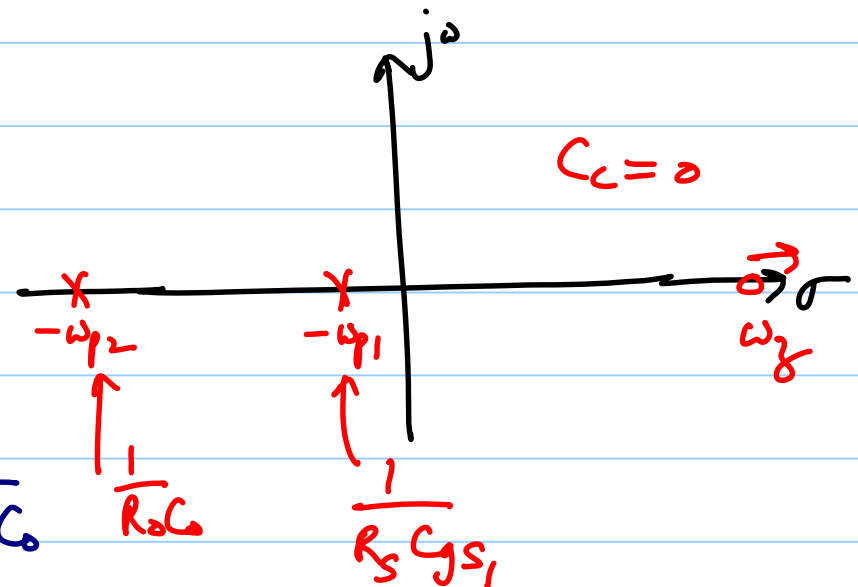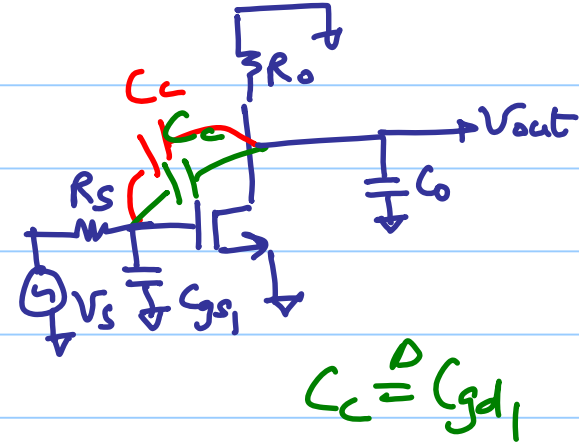

Now increase C_c

Consider when $C_c \gg C_{gs1}$

$$\omega_{p1} \approx \frac{1}{R_S(1+A_v)C_c + R_o(C_c + C_o)}$$


$$\omega_{p2} \approx \frac{R_S(1+g_{m1}R_o)C_c + \cancel{R_o(C_c + C_o)}}{R_S R_o C_c [C_o + C_{gs1}]}$$

$$\approx \frac{\cancel{R_S}(1+g_{m1}\cancel{R_o})\cancel{C_c}}{\cancel{R_S} \cancel{R_o} \cancel{C_c} (C_o + C_{gs1})} \approx \frac{g_{m1}}{C_o + C_{gs1}}$$


$$\omega_z = \frac{+g_{m1}}{C_c}$$

	$C_c = 0$	$C_c \gg C_{gs1}, \quad C_c \approx C_o$
ω_{p1}	$\approx \frac{1}{R_S C_{gs1} + R_o C_o}$	$\approx \frac{1}{R_S (1+ A_v) \underline{C_c} + R_o [\underline{C_c} + C_o]}$ ω_{p1} is smaller
ω_{p2}	$\approx \frac{1}{R_o C_o}$	$\approx \frac{g_{m1}}{C_o + C_{gs1}} \stackrel{\Delta}{\approx} \frac{g_{m1}}{C_o} = g_{m1} R_o \left(\frac{1}{\underline{R_o C_o}} \right)$ $\Rightarrow \omega_{p2}$ is increased by a large value
ω_z	$\frac{g_{m1}}{C_{gs1}}$	$\frac{g_{m1}}{C_c} \leftarrow$ RHP zero is at lower frequency


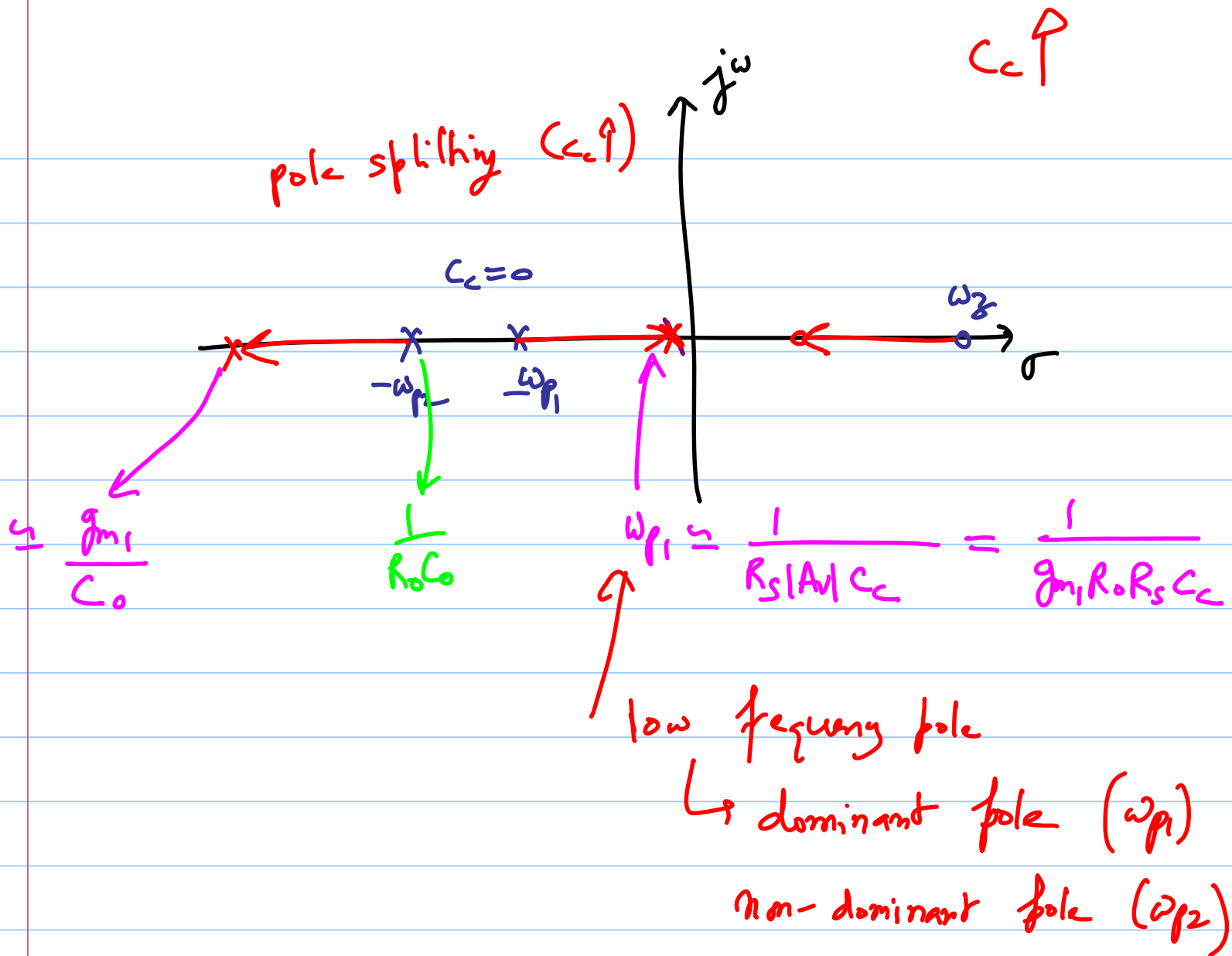
Miller Compensation $\Rightarrow$ pole splitting $\Rightarrow C_c \uparrow$



for a large C_c
at high frequencies.


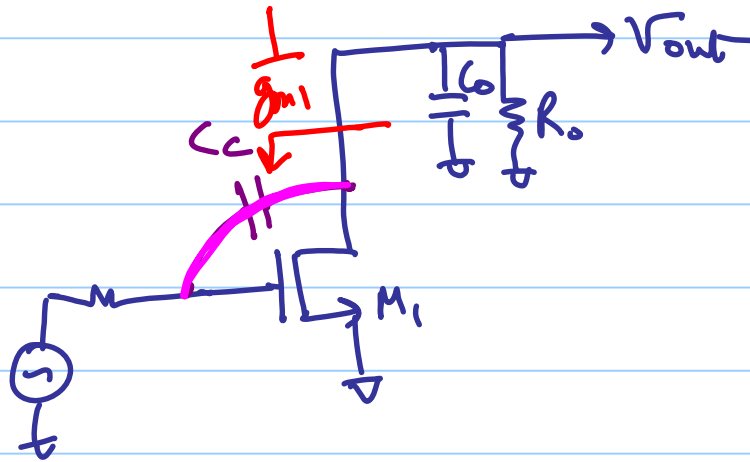

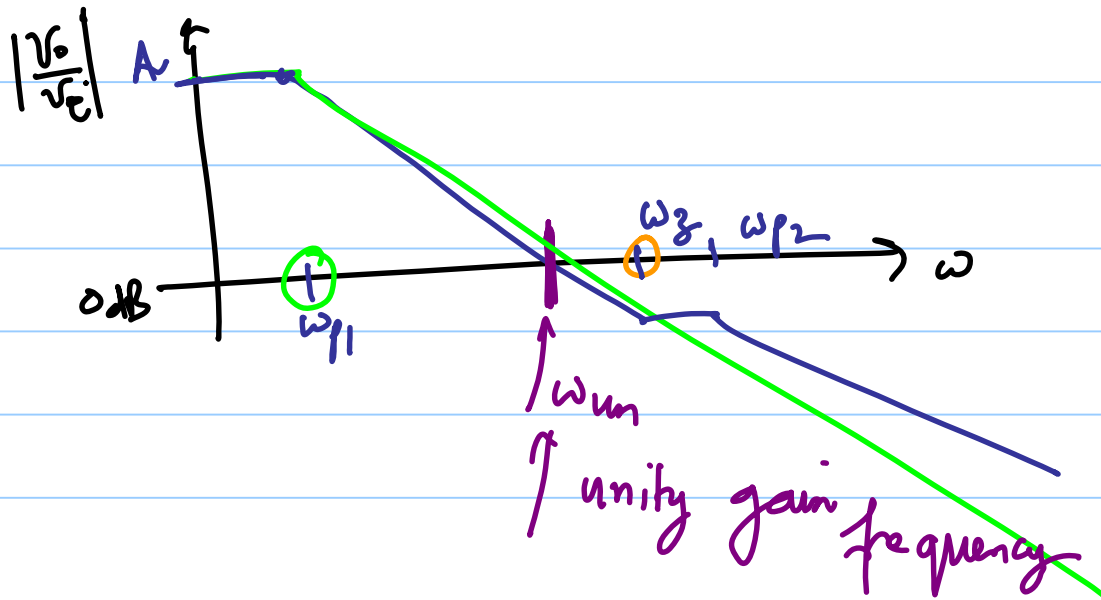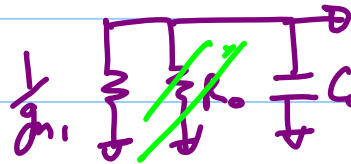
$$\omega_{p2} \approx \frac{g_{m1}}{C_o}$$



Cancel the RHP zero


$$\omega_z = + \frac{g_{m1}}{C_c}$$

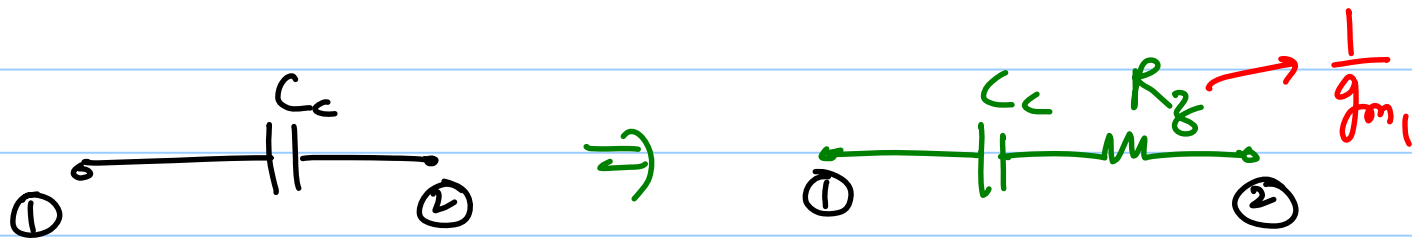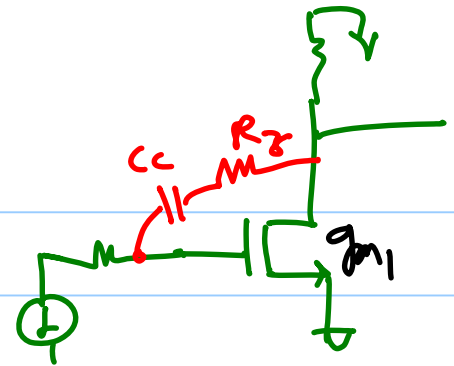


$$\omega_z = \frac{1}{C_c \left(\frac{1}{g_{m1}} - R_z \right)}$$

If $R_z = \frac{1}{g_{m1}} \Rightarrow \omega_z \rightarrow \infty$ zero disappears

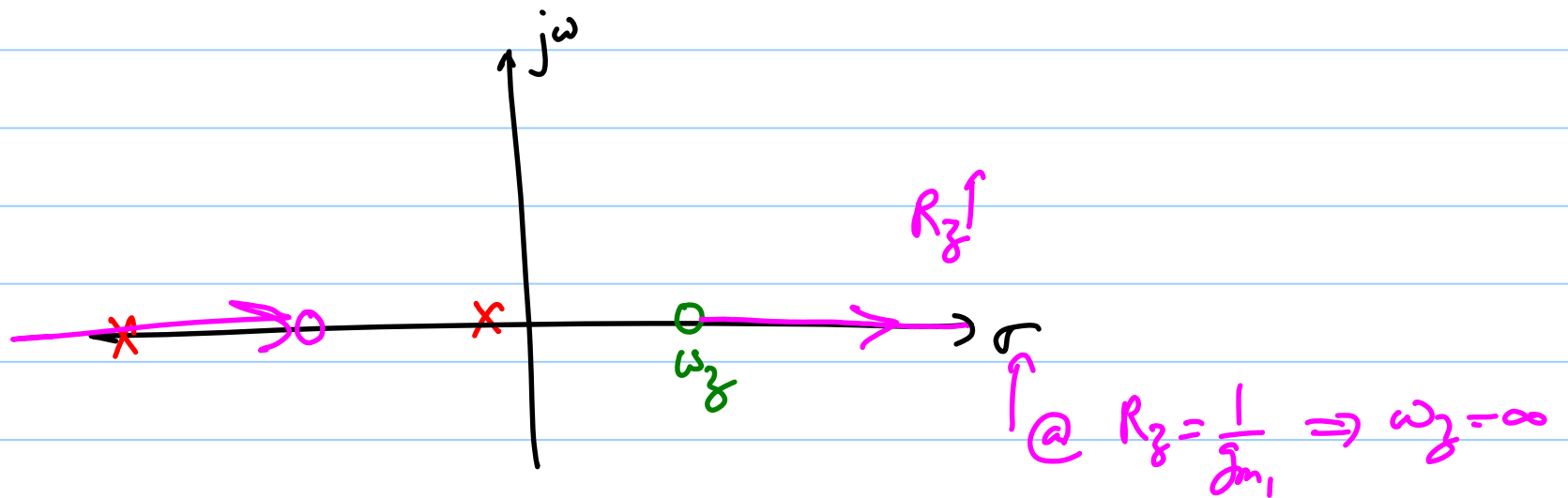$R_z > \frac{1}{g_{m1}} \Rightarrow$ zero appears in the LHP



Pole splitting Summary

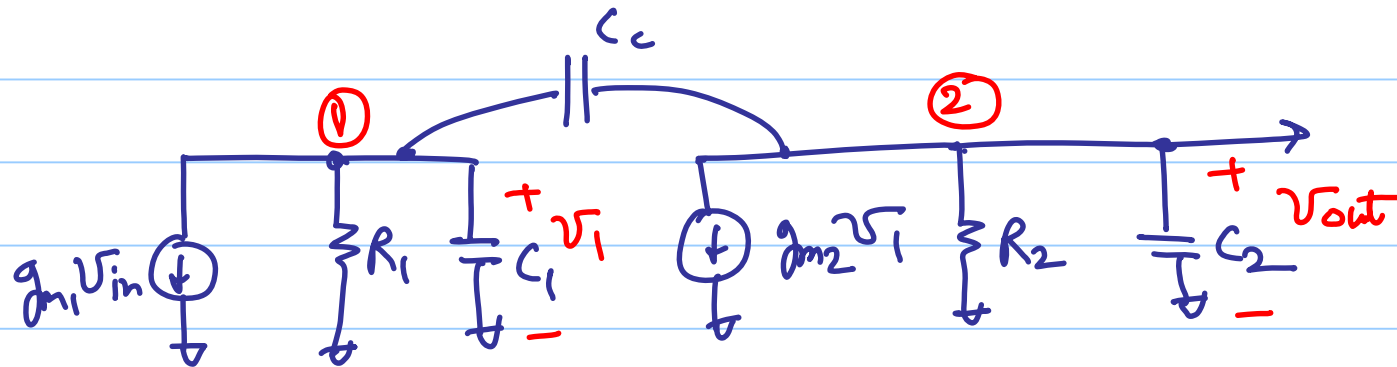

$$A_v = g_{m1}R_1 g_{m2}R_2$$

$$\omega_{p1} = \frac{1}{R_2(C_2 + C_c) + R_1(C_1 + C_c(1 + g_{m2}R_2))} \Rightarrow \frac{1}{g_{m2}R_2 R_1 C_c}$$

$$\omega_{p2} \approx \frac{g_{m2}C_c}{C_c C_1 + C_1 C_2 + C_c C_2} \approx \frac{g_{m2}}{C_2} \quad \text{for } C_c \approx C_2 \gg C_1$$

$$\omega_z = \frac{g_{m2}}{C_c}$$

$$\frac{V_{out}(s)}{V_{in}} = A_v(s) = \frac{A_v (1 - s/\omega_z)}{(1 + s/\omega_{p1})(1 + s/\omega_{p2})}$$