

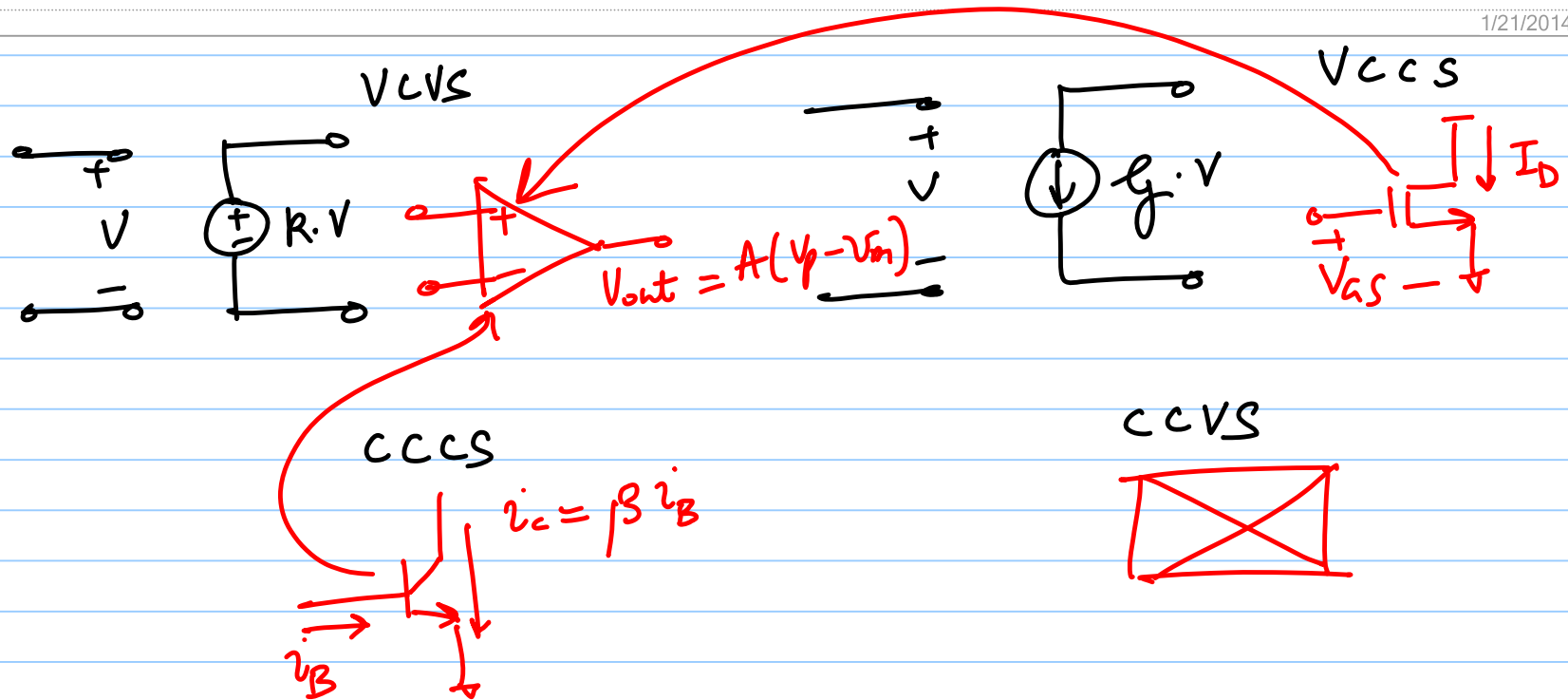
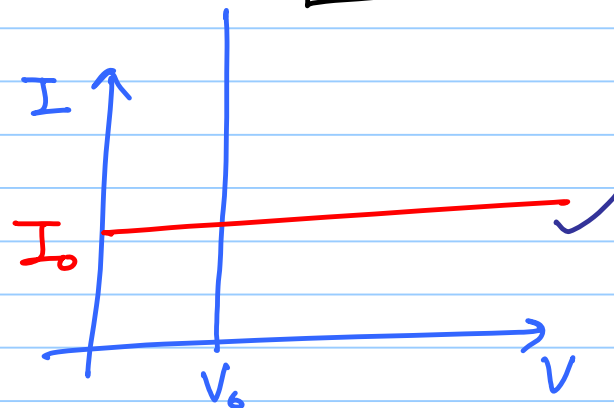


ECE 511 - Lecture 1


Note Title

1/21/2014

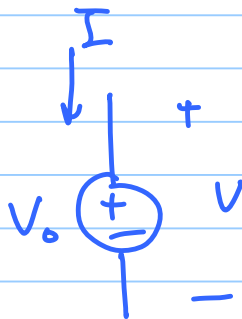


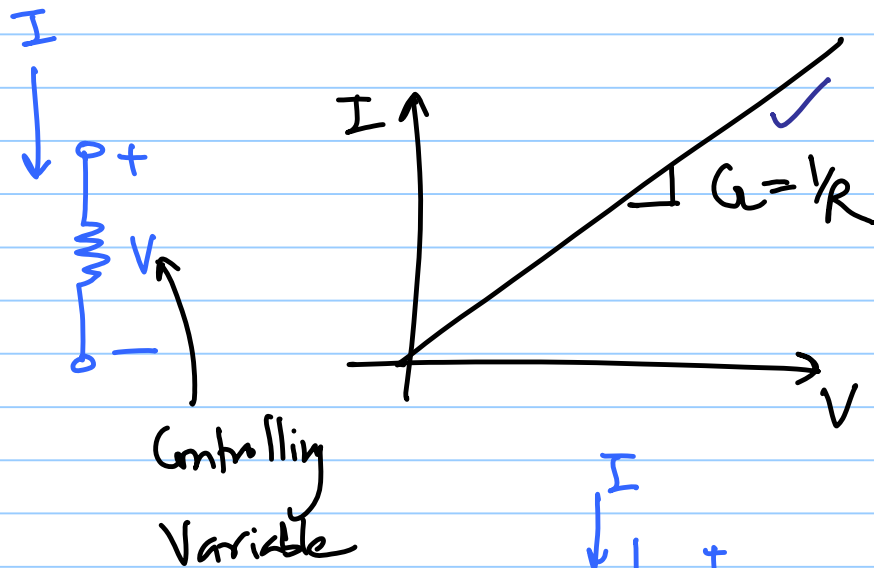

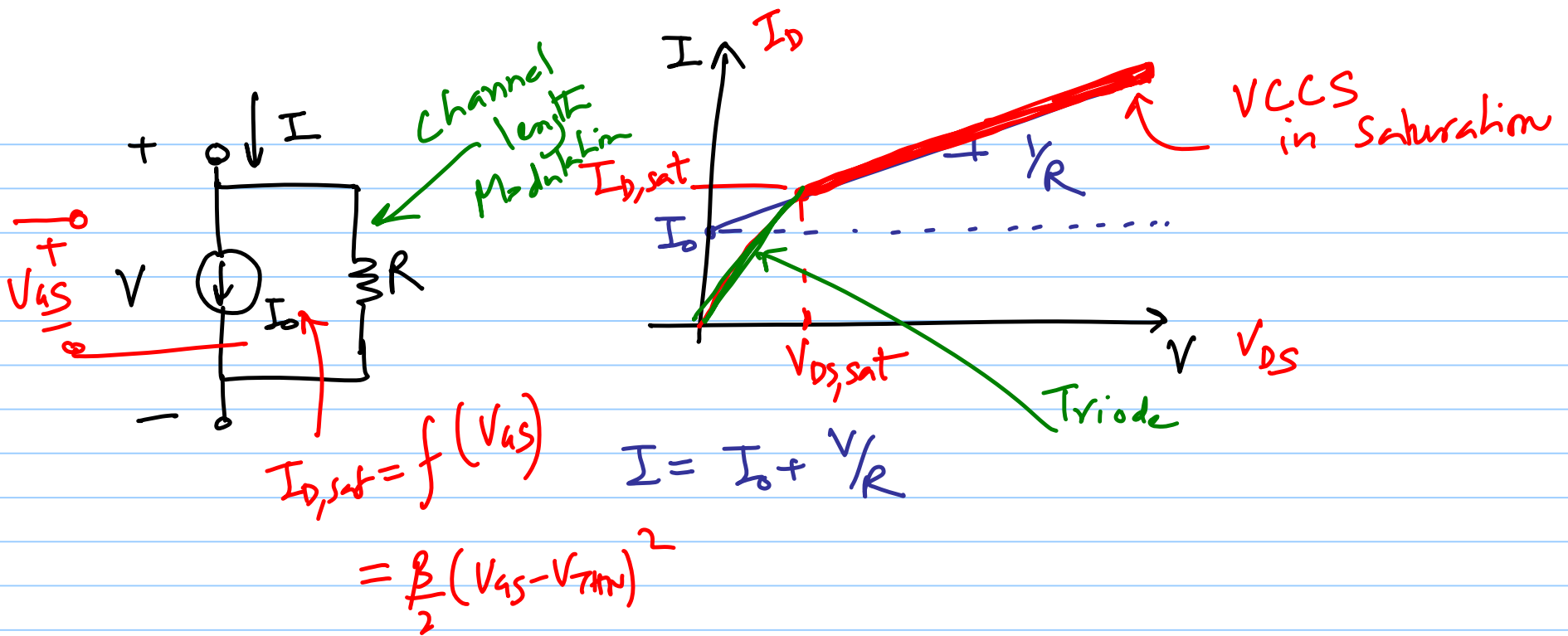Triode
Saturation (pinch-off)
CLM (λ)
short-channel effects
Body effect



I-V curves of a MOSFET

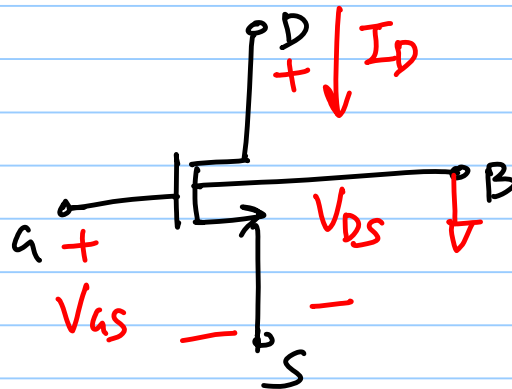

independent variable


dependent variable





$$I_D = f(V_{gs}, V_{ds}, V_{sb})$$

$$I_D = f(V_{GS}, V_{DS})$$

I_D vs V_{GS}

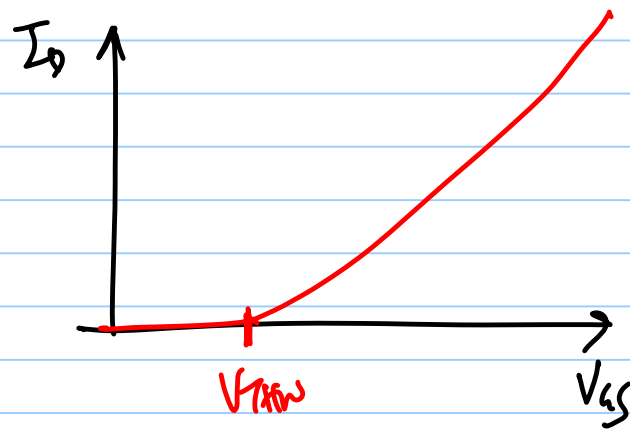
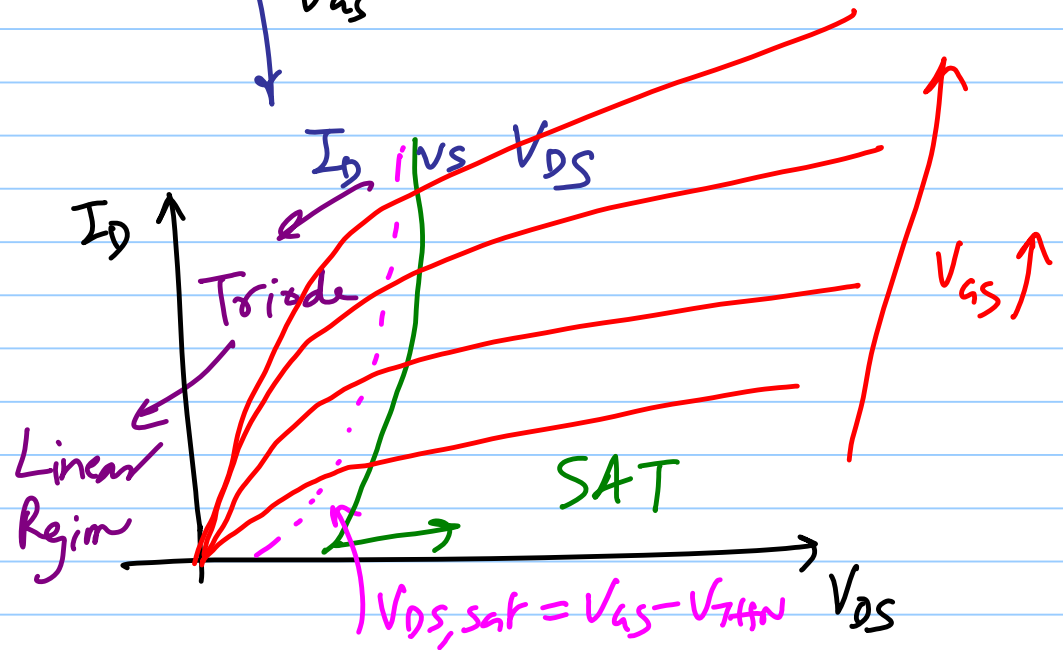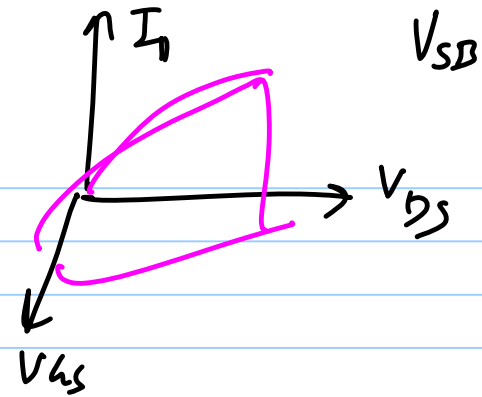
$$I_D = \frac{k_p W}{2 L} (V_{GS} - V_{THN})^2$$




Triode

$$I_D = K'_n \frac{W}{L} \left[\underbrace{(V_{GS} - V_{THN})}_{V_{OV}} V_{DS} - \frac{V_{DS}^2}{2} \right]$$

$$V_{DS, \text{sat}} = V_{GS} - V_{THN}$$

V_{OV}
"Overdrive Voltage"

overdrive

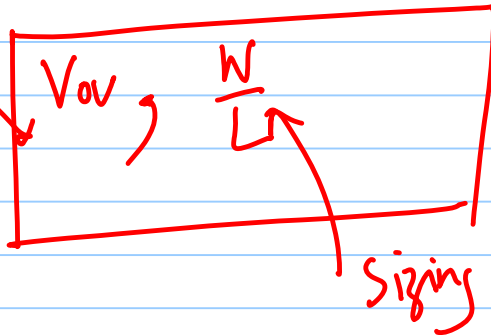

Sizing


$$V_{OV} = V_{GS} - V_{THN}$$

↑ voltage above threshold by which the MOSFET is driven

for long channel CMOS

$$V_{DS, \text{sat}} \triangleq V_{OV}$$

In Saturation

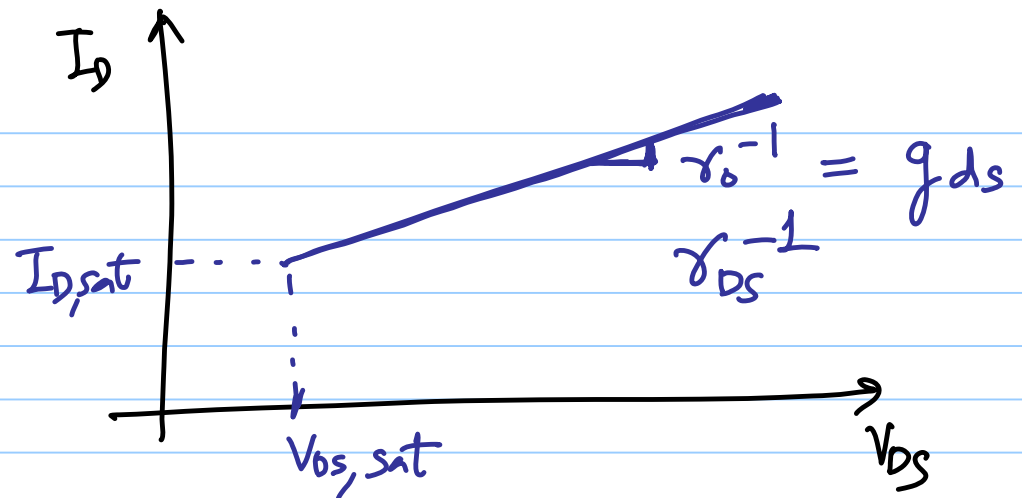



$$I_D = I_{D,sat} + I_{D,sat} \lambda (V_{DS} - V_{DS,sat})$$

$$\gamma_o = \left(\frac{\partial I_D}{\partial V_{DS}} \right)^{-1} = (\lambda I_{D,sat})^{-1}$$


$$\gamma_o = \frac{1}{\lambda I_{D,sat}}$$

$\lambda \Rightarrow$ CLM parameter
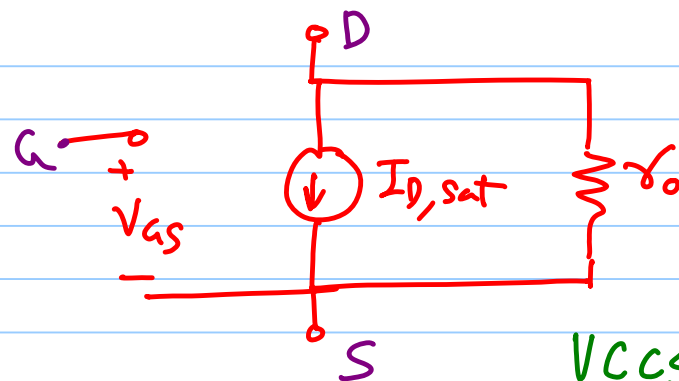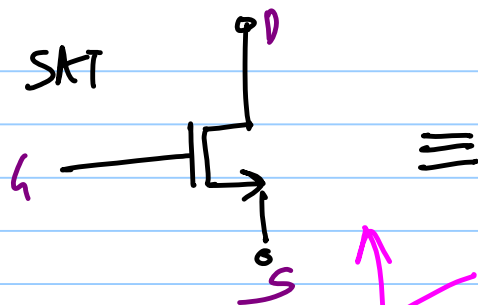
$$I_{D,sat} = \frac{K p_n}{2} \frac{W}{L} V_{ov}^2$$



V_{CCS} with r_o

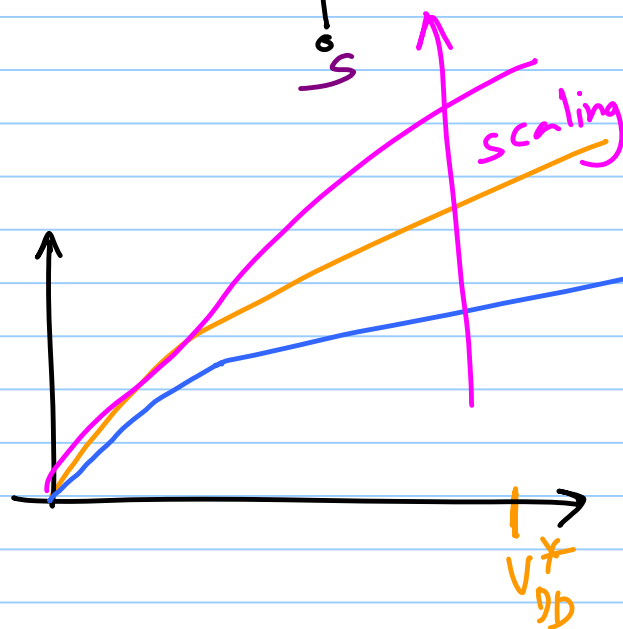


with CMOS scaling


$L \downarrow$

$r_o \downarrow$

$A_v = g_m r_o \downarrow$

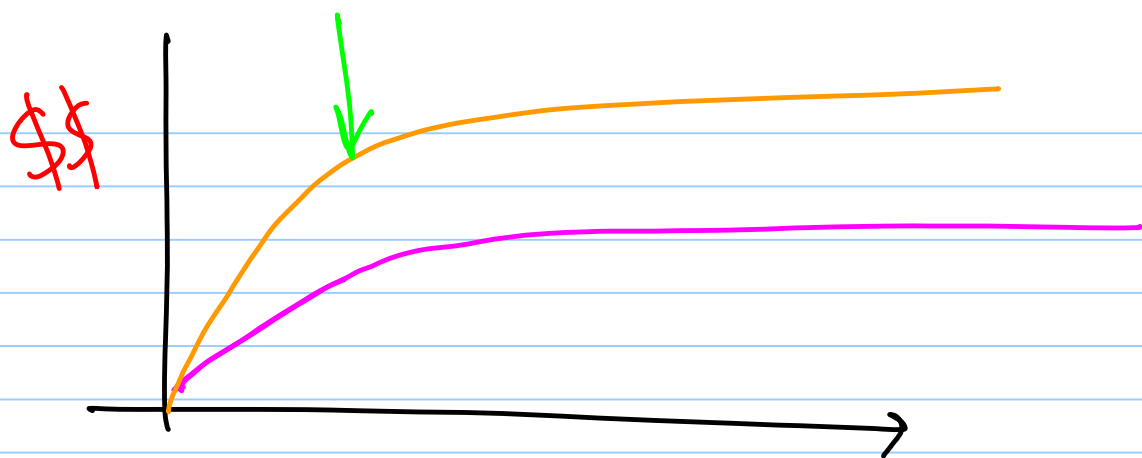

In Triode :

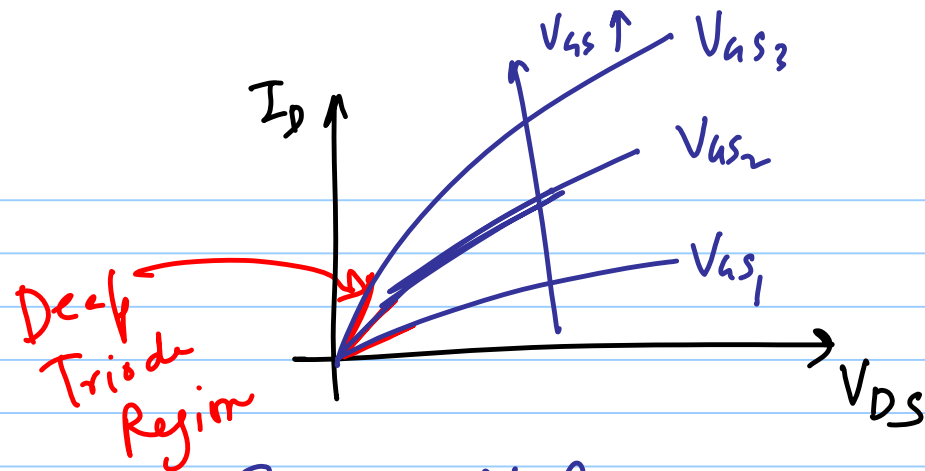



$$I_D = k_p n \frac{W}{L} \left[(V_{GS} - V_{THN}) V_{DS} - \frac{V_{DS}^2}{2} \right]$$

$$\frac{\partial I_D}{\partial V_{DS}} = \underbrace{k_p n \frac{W}{L}}_{\beta} [V_{GS} - V_{THN} - V_{DS}]$$

$$R_{ch} = \left(\frac{\partial I_D}{\partial V_{DS}} \right)^{-1} = \frac{1}{\beta (V_{GS} - V_{THN} - V_{DS})}$$

VCR

Voltage Controlled resistor

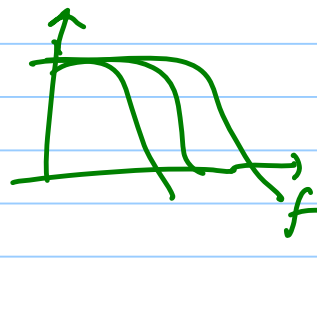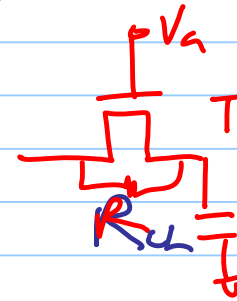


$$R_{ch} = \frac{1}{\beta(V_{GS} - V_{THN} - V_{DS})}$$

Let's say the M_1 is in deep Triode

$$V_{DS} \ll V_{GS} - V_{THN}$$


$$R_{ch} \approx \frac{1}{\beta(V_{GS} - V_{THN})}$$

Trend: $R_{ch} \propto \frac{1}{V_{ov}}$

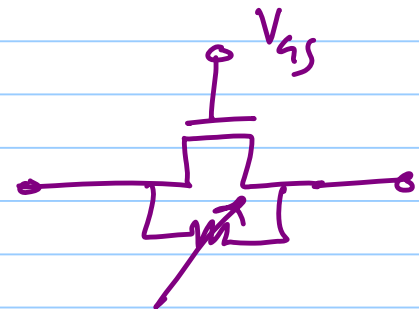


Saturation

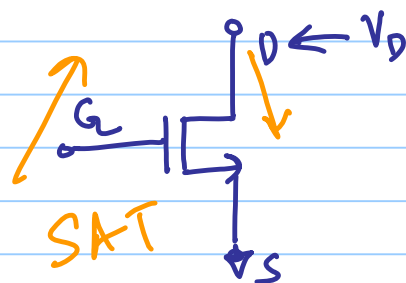(Chap 9 $\rightarrow$ CMOS)
(Chap 2 $\leftarrow$ Razavi)


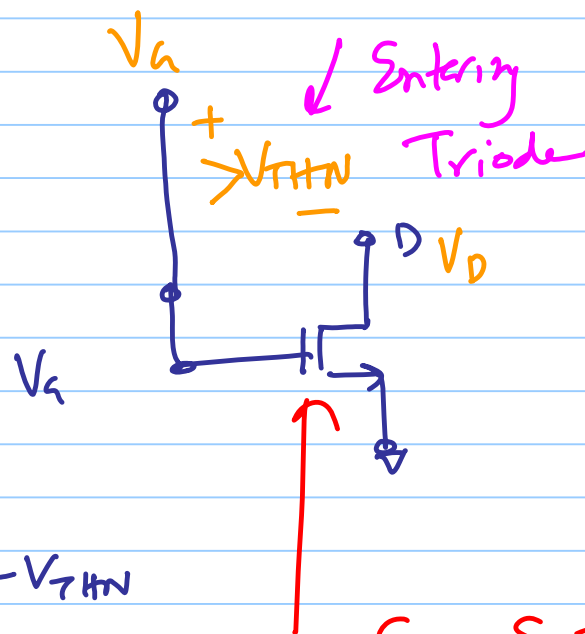
$$V_{DS, \text{sat}} = V_{GS} - V_{THN}$$



$$V_{DS} \leq V_{GS} - V_{THN}$$

$$V_{DS} \leq V_{DS, \text{sat}}$$

for Saturation

$$V_D > V_G - V_{THN}$$

$$\checkmark \quad V_G < V_D + V_{THN}$$

