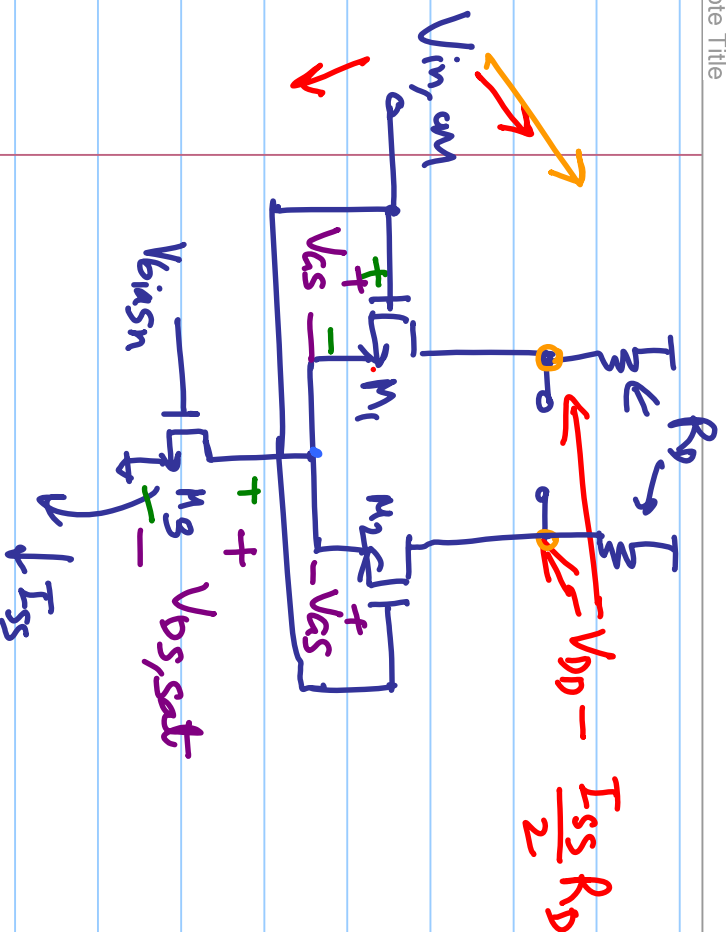


EECE 511 - Lecture 20


Input Common-Mode Range
Input CMR





$$V_{in,cm} \geq V_{GS1,2} + V_{DS,sat3}$$

$$V_{in,cm} \leq \left(V_{DD} - \frac{I_{SS}}{2} R_D \right) + V_{THN}$$

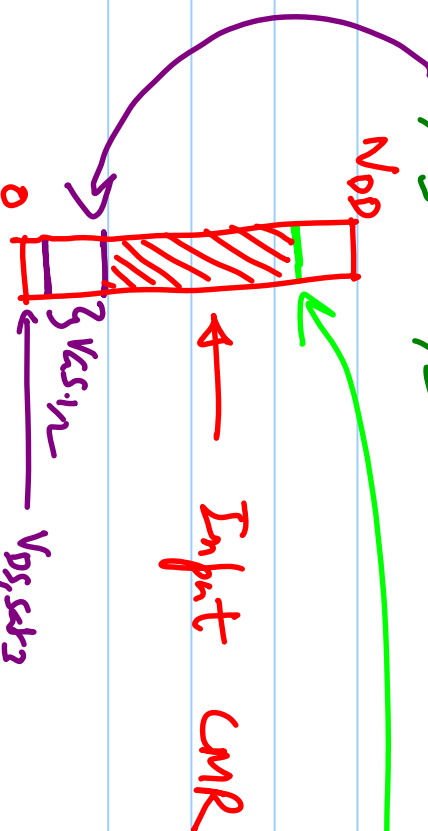
$$V_{DS,sat3} + V_{GS1,2} \leq V_{in,cm} \leq \left(V_{DD} - \frac{I_{SS}}{2} R_D \right) + V_{THN}$$



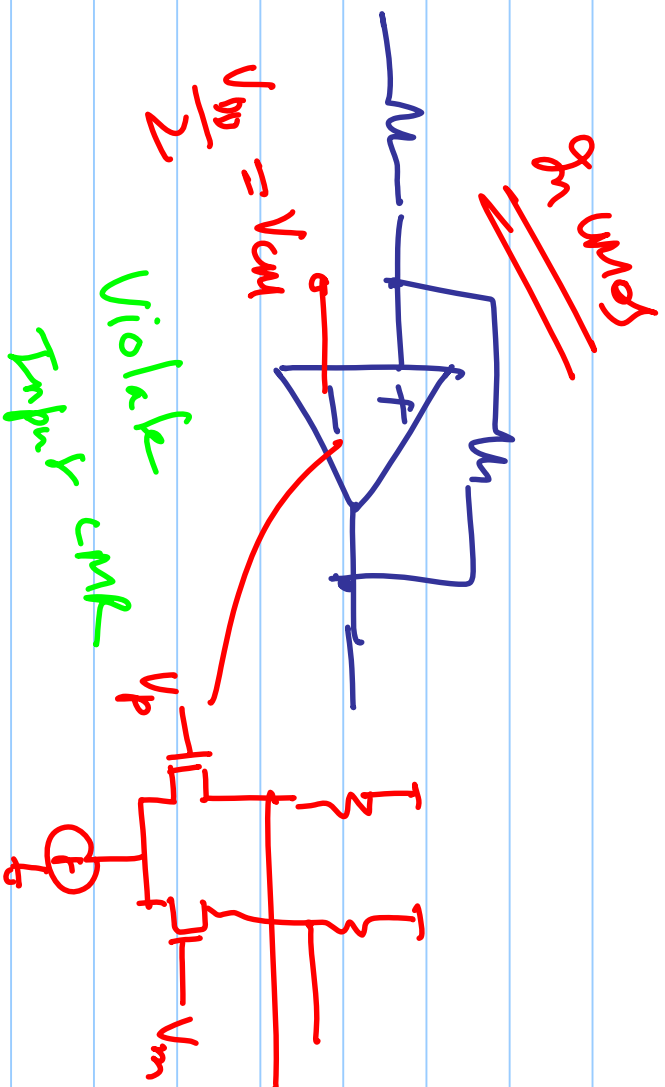

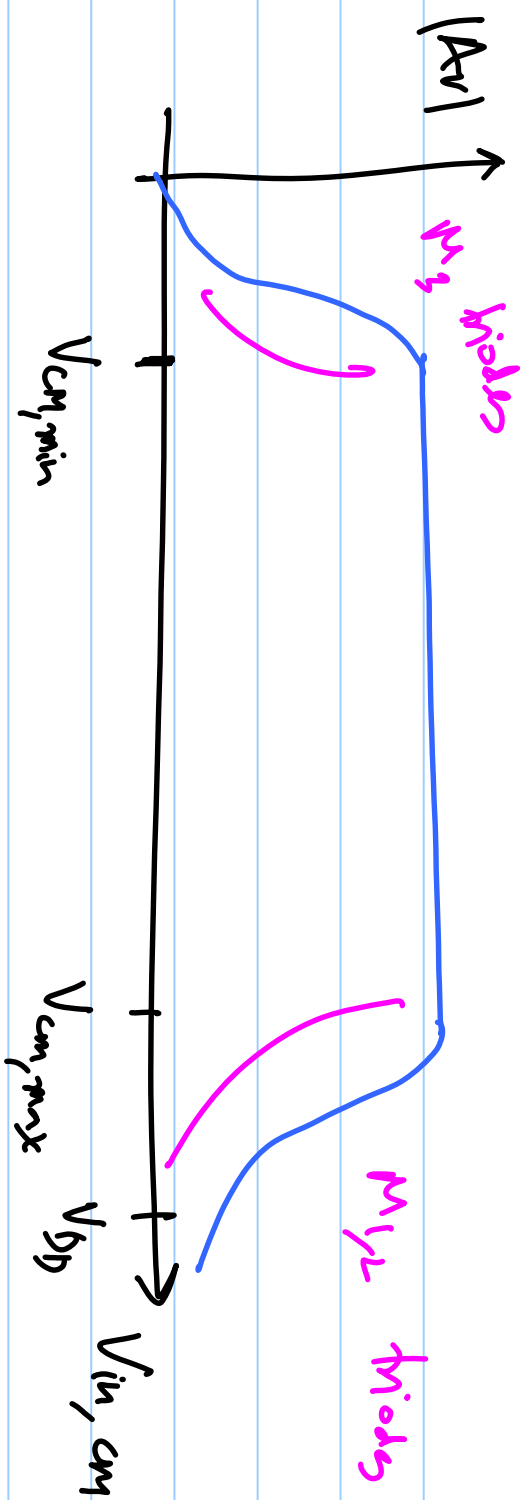


Small-Signal Analysis:

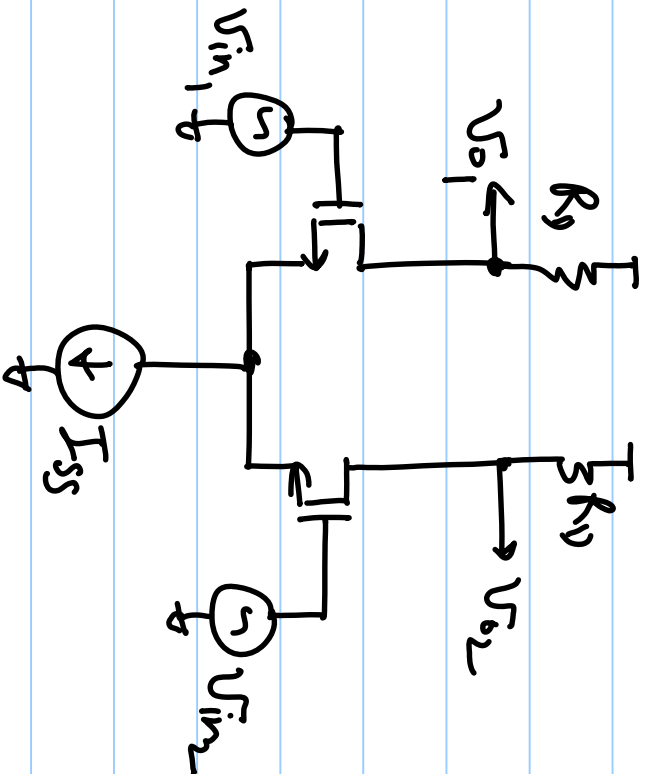


Lemma:

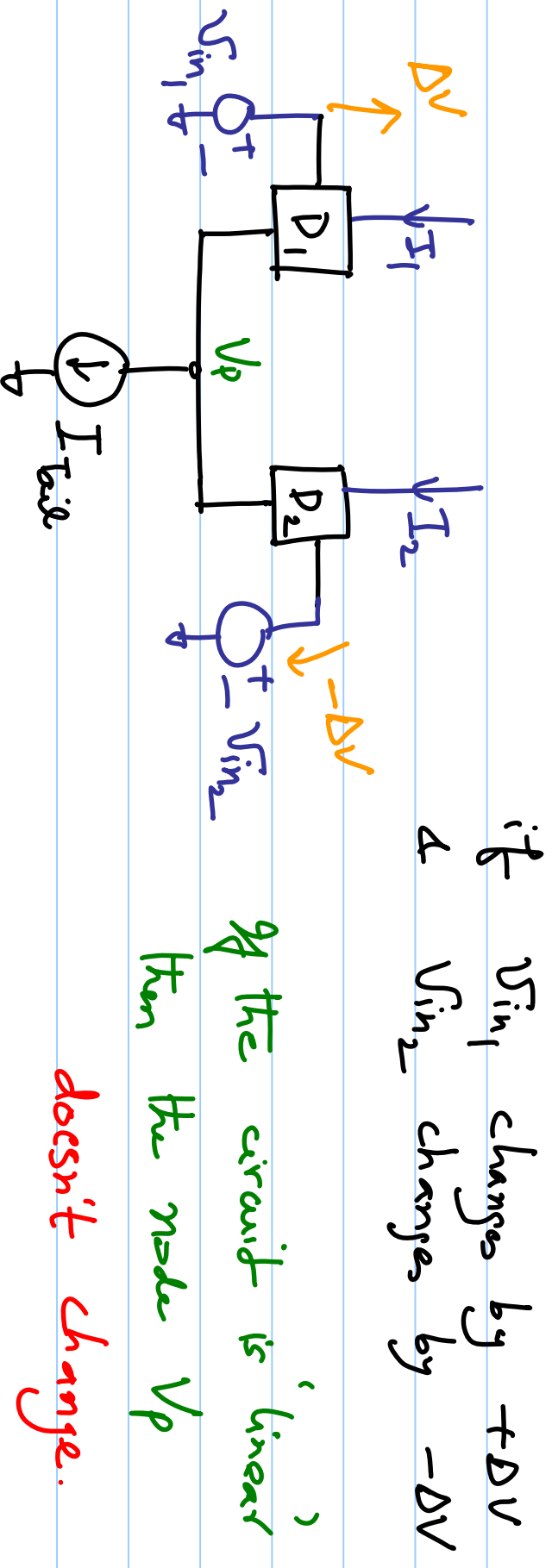
In the symmetric circuit shown below
when D_1 & D_2 are any 3-terminal
devices (i.e. MOSFET)




input is f_u -differentia

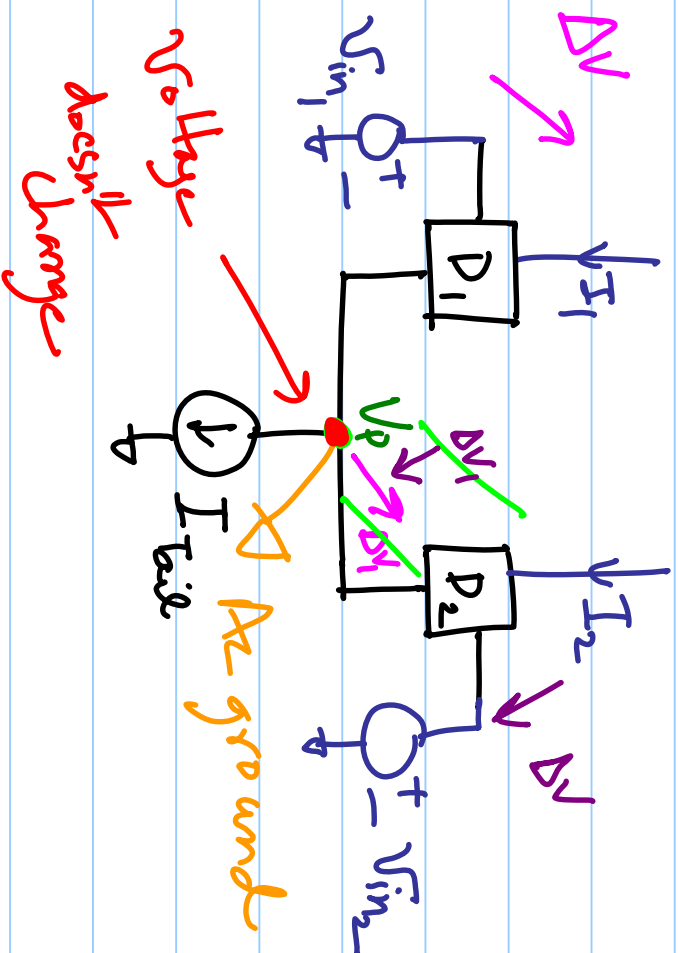

2 Half Circuits

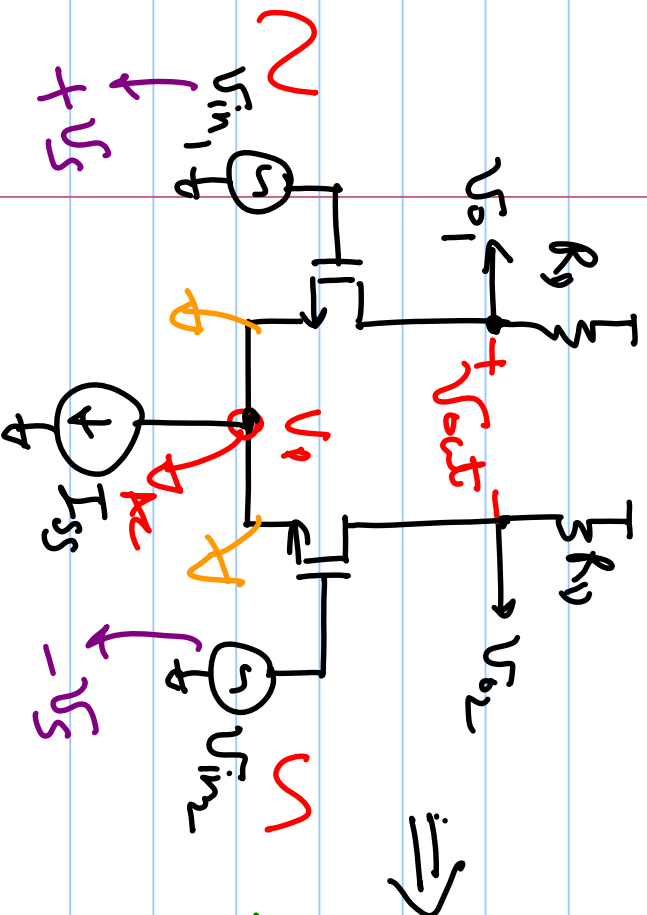

$\Rightarrow$

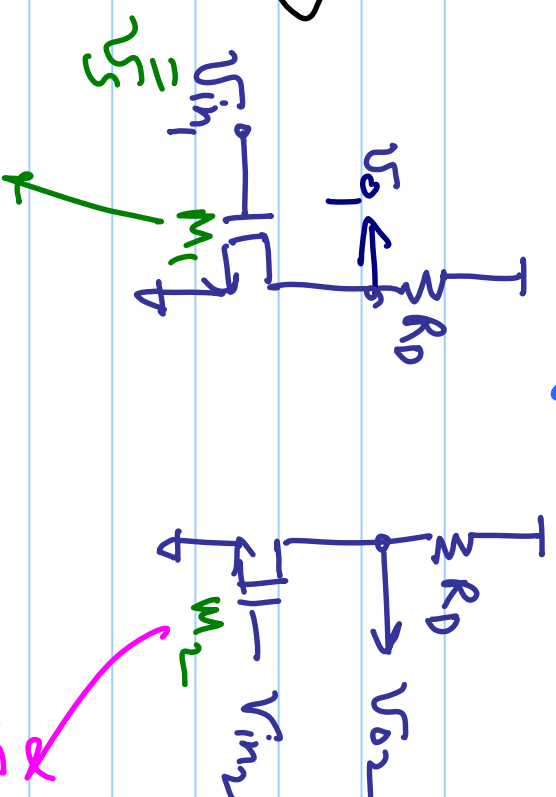

$$\frac{v_{o1}}{v_{in1}} = -g_{m1}(r_{o1} \parallel R_D)$$



$$\frac{v_{o2}}{v_{in2}} = -g_{m2}(r_{o2} \parallel R_D)$$

$$A_v = \frac{v_{out}}{v_s} = \left(\frac{v_{o1}}{v_s} \right) - \left(\frac{v_{o2}}{-v_s} \right)$$

$$= \left[-g_m(r_{o1} \parallel R_D) \right] - \left[+g_m(r_{o2} \parallel R_D) \right]$$



$$= -2g_m(g_m(r_{o1} \parallel R_D))$$

Half Circuit Analysis

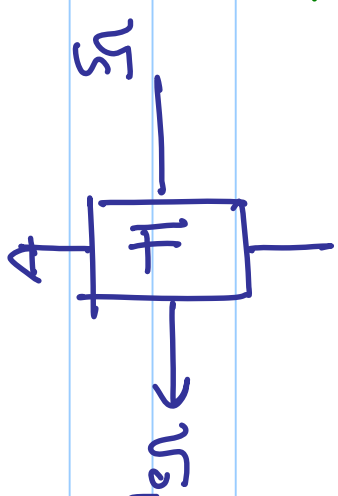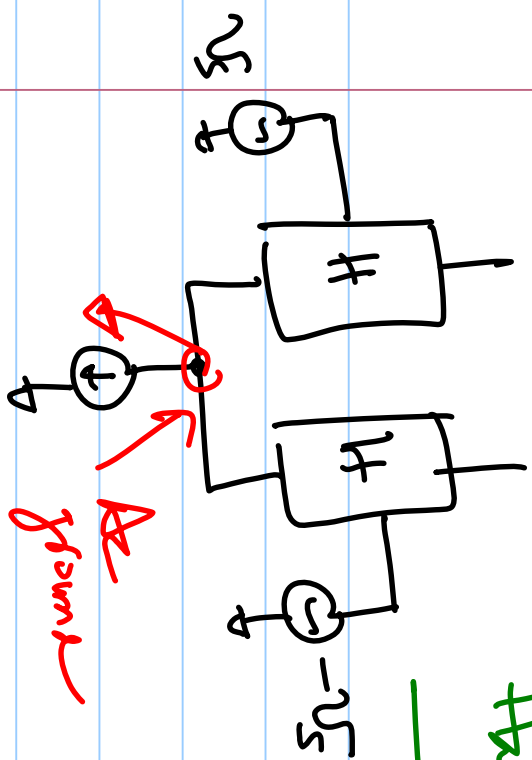

$2 \times ()$

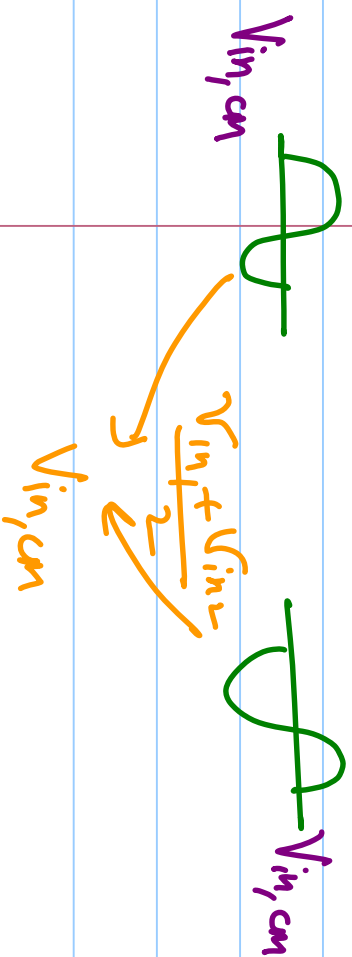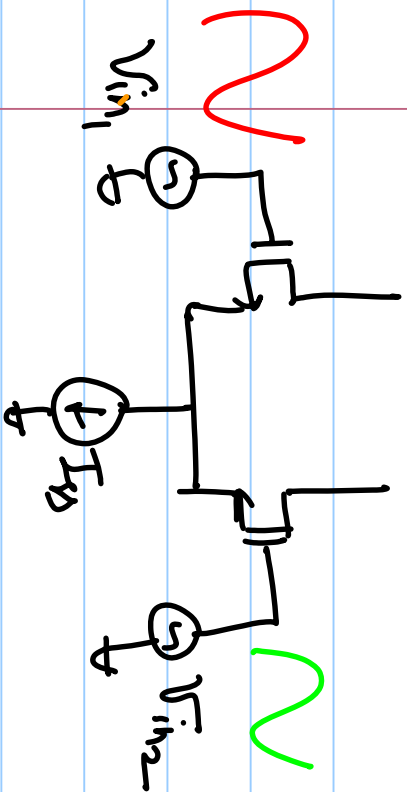Q: What if the inputs are not fully-differential, but different



$$V_{in1} = \left(\frac{V_{in1} - V_{in2}}{2} \right) + \left(\frac{V_{in1} + V_{in2}}{2} \right)$$

$$V_{in2} = \left(\frac{V_{in2} - V_{in1}}{2} \right) + \left(\frac{V_{in1} + V_{in2}}{2} \right)$$



Differential mode signal

(Equal & opposite sign)

CM-signal


(Not a DC-level)

(any more)

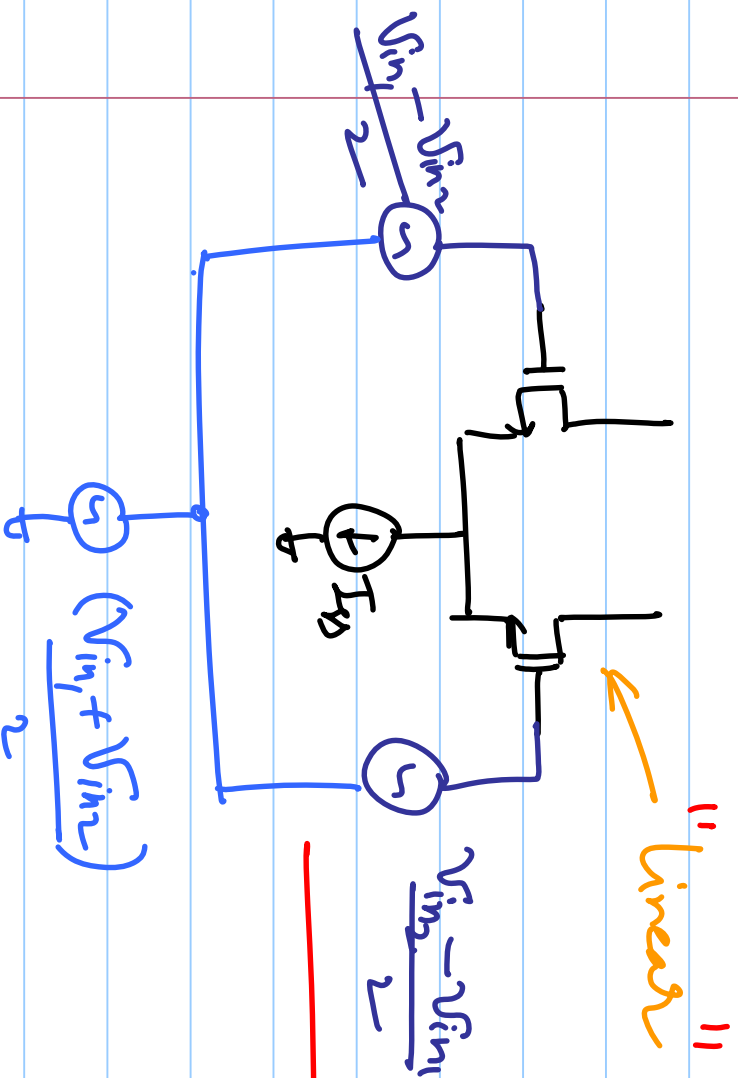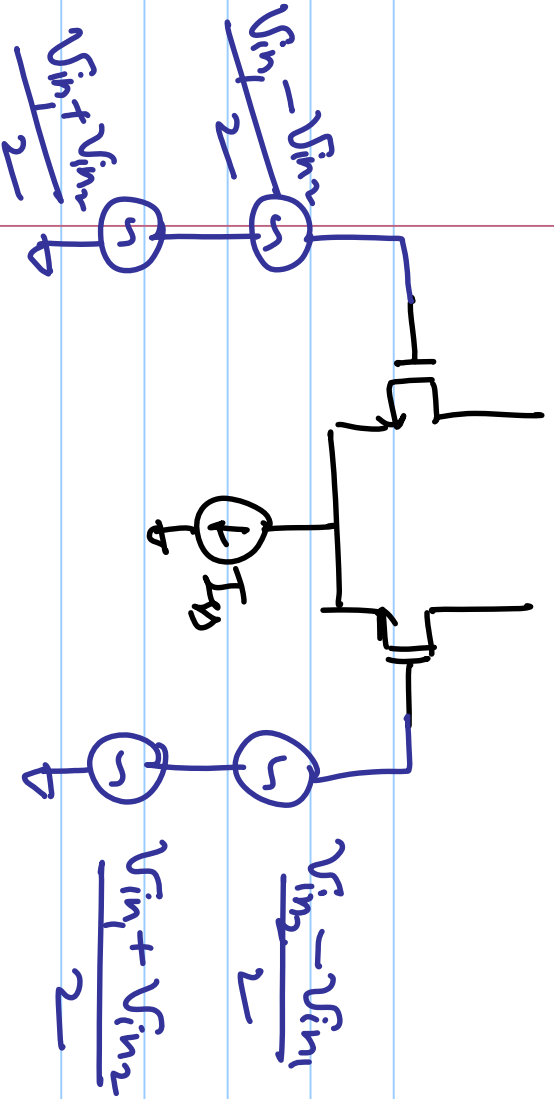


→ Break using
superposition

✓
Analyze this

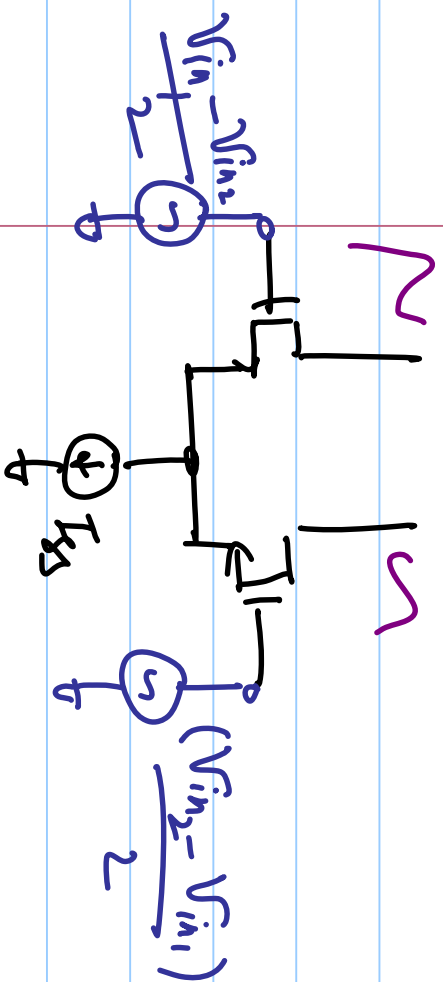

✓
Analyze that

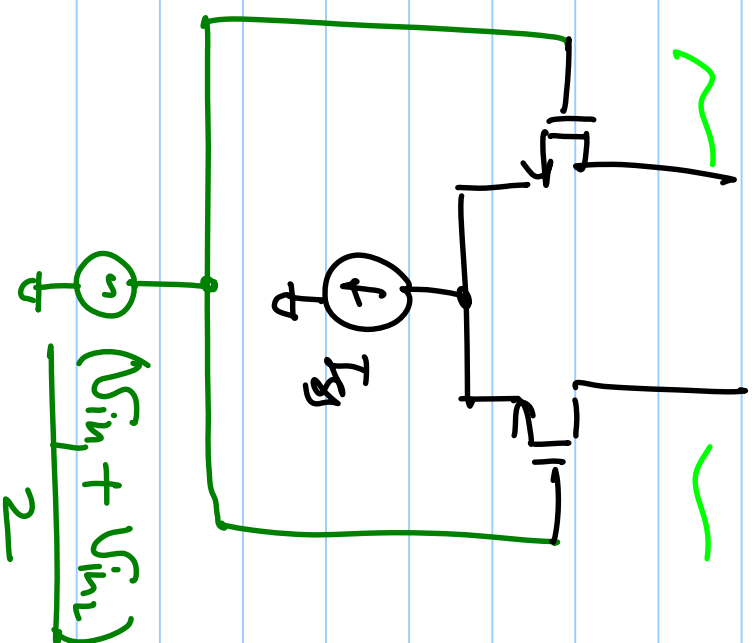


Differential Equivalent

Circuit


↓ 2 x Half Circuits

Apply Lemma


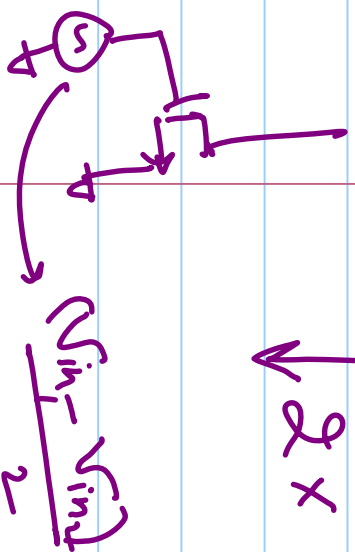


Common-mode Equiv
Circuit


Common-Mode Response / Analysis

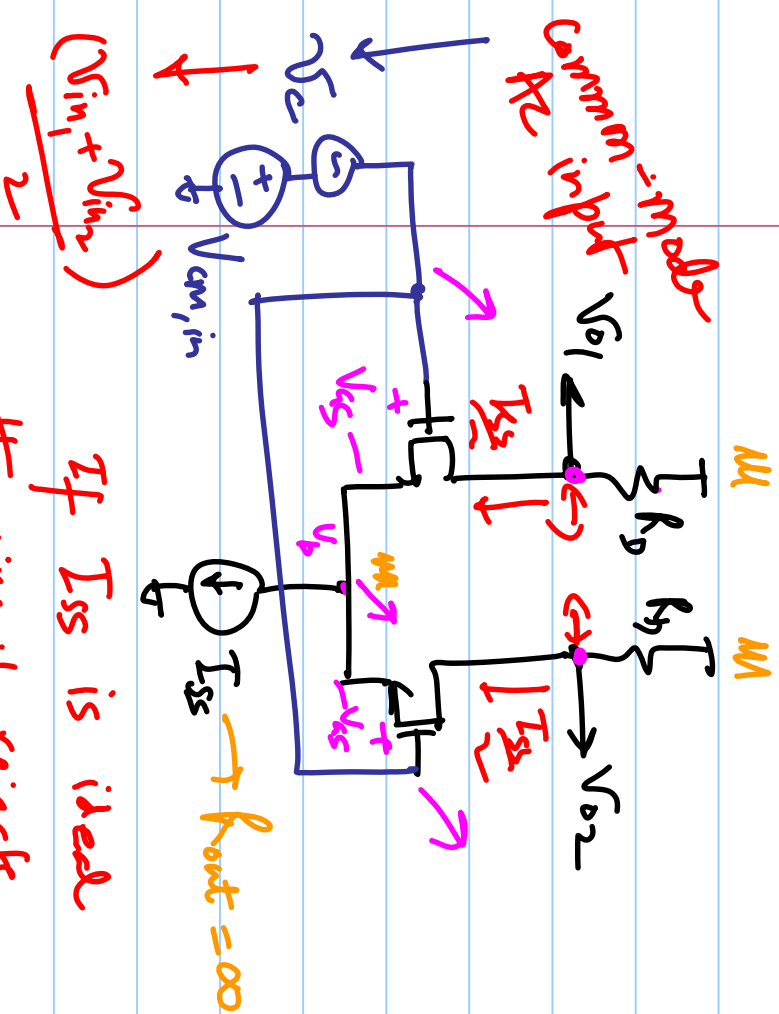

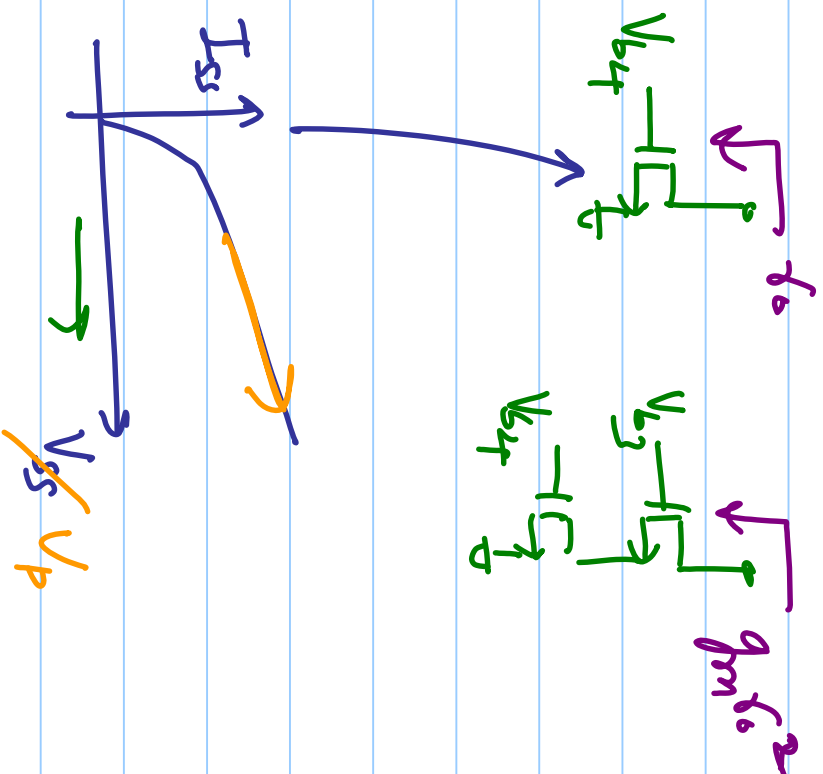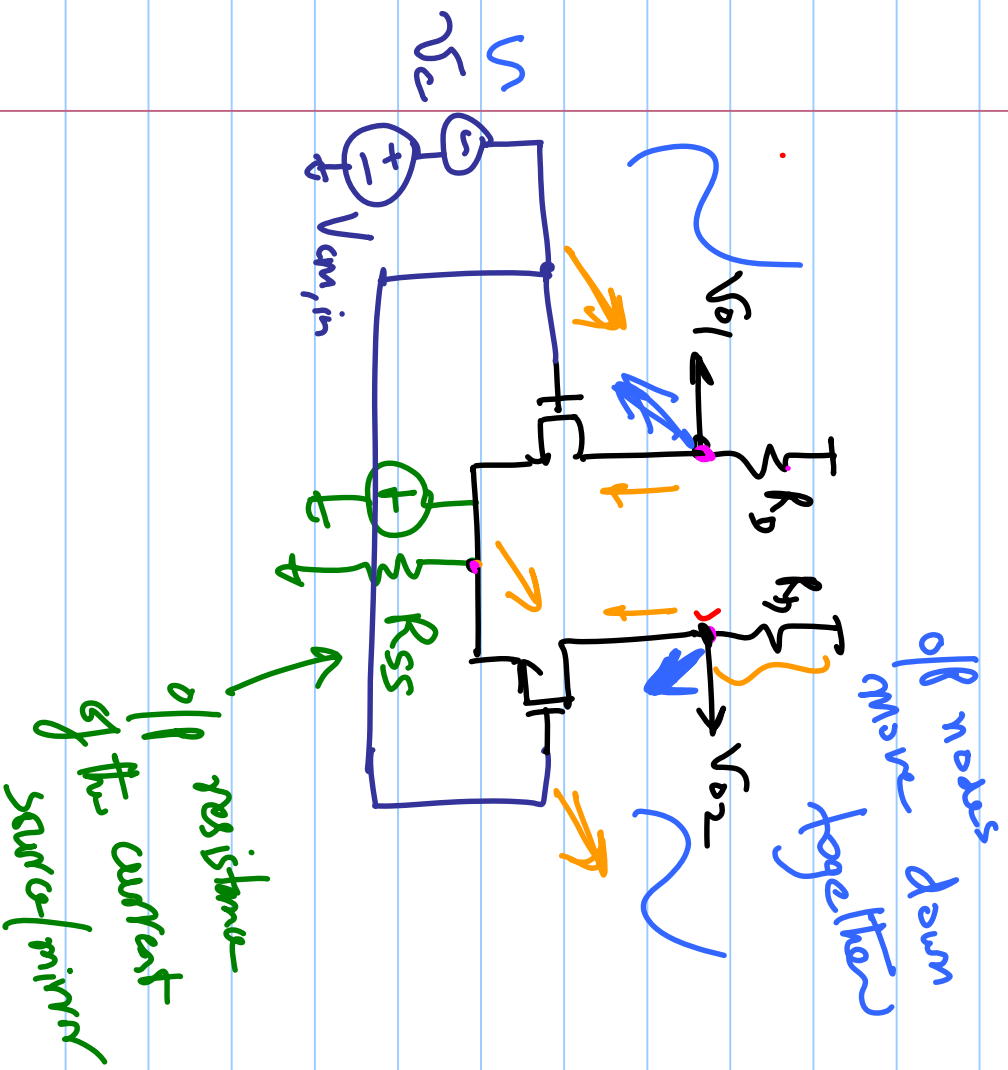
If I_{SS} is ideal
the circuit rejects
input CM disturbance



Common-Mode
AC picture

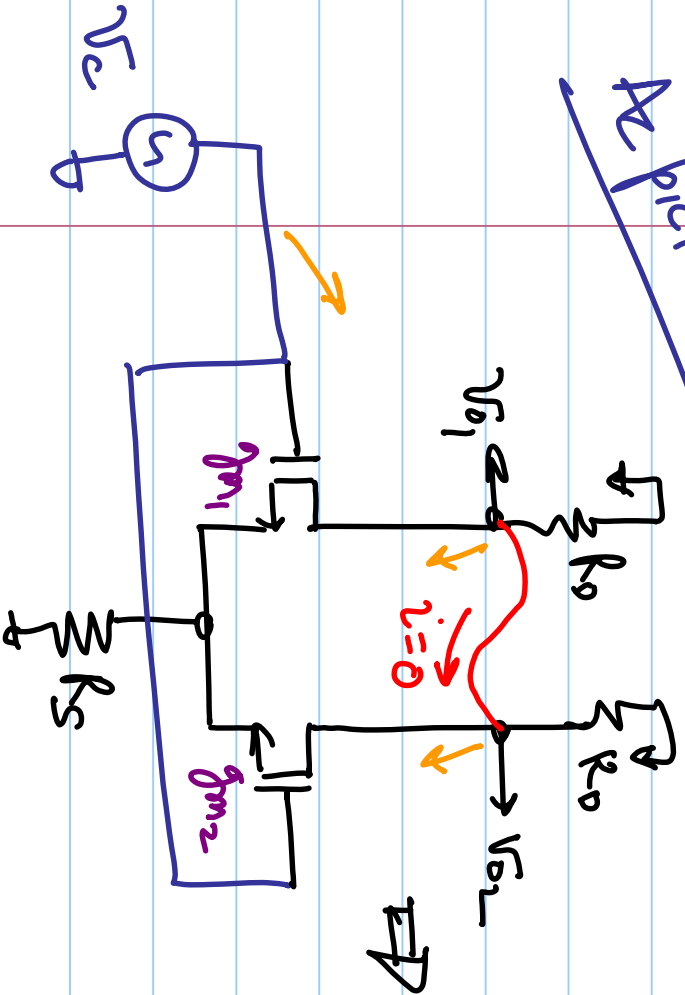

CM Equivalent
Circuit

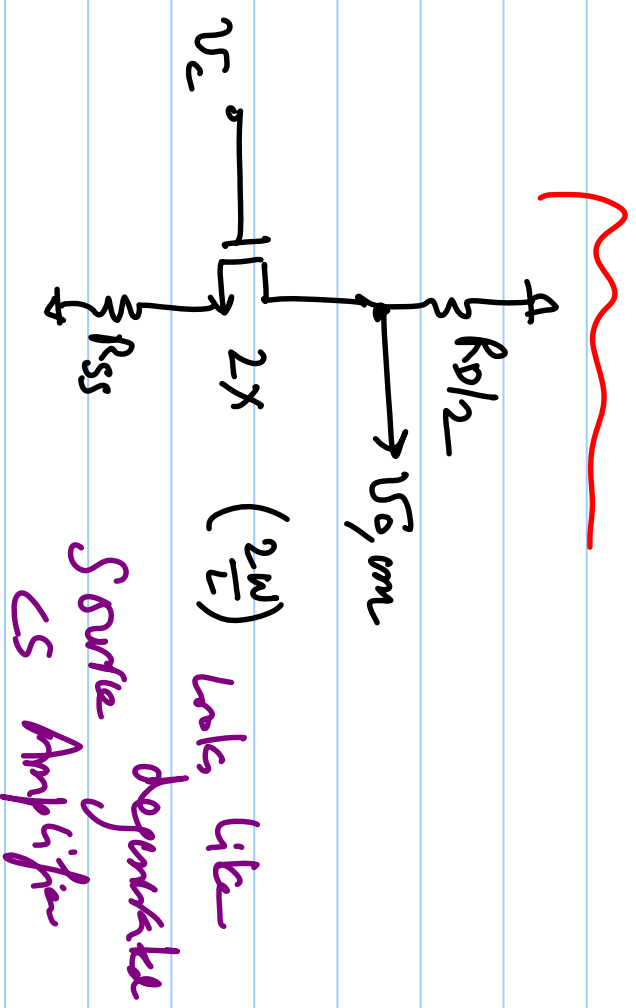

Common mode AC gain

$$A_{v,cm} = \frac{v_{o,cm}}{v_c} = -g_m \times \frac{R_D}{2}$$



$$= - \left(\frac{g_{m1,2}}{1 + 2g_{m1,2}R_{SS}} \right) \cdot \frac{R_D}{2}$$

$$= \frac{-R_D/2}{(1/2g_{m1,2}) + R_{SS}}$$

$$\sqrt{f_r \quad R_{ss} \rightarrow \infty, \quad A_{r, \infty} = 0}$$


$$q_s \quad R_{ss} \gg \frac{1}{2g_{m1/2}}$$

Single-ended Diff-amp

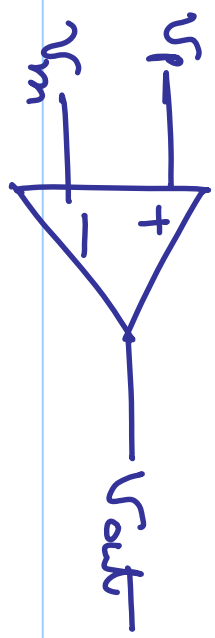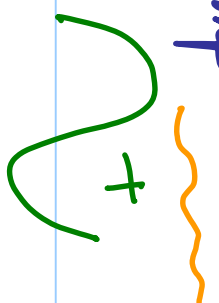

DM + CM

Common-mode Rejection Ratio

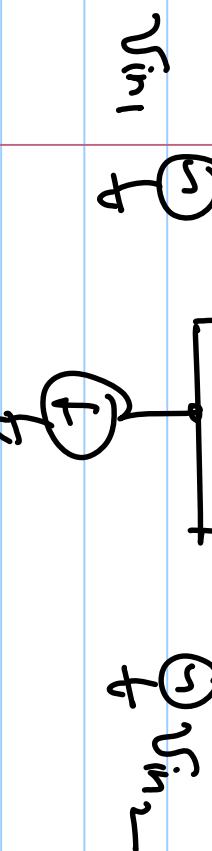

$v_d =$

v_c

CMRR =

$$\left| \frac{A_{v,DM}}{A_{v,CM}} \right|$$

We want a large CMRR

Differential Amplifier

