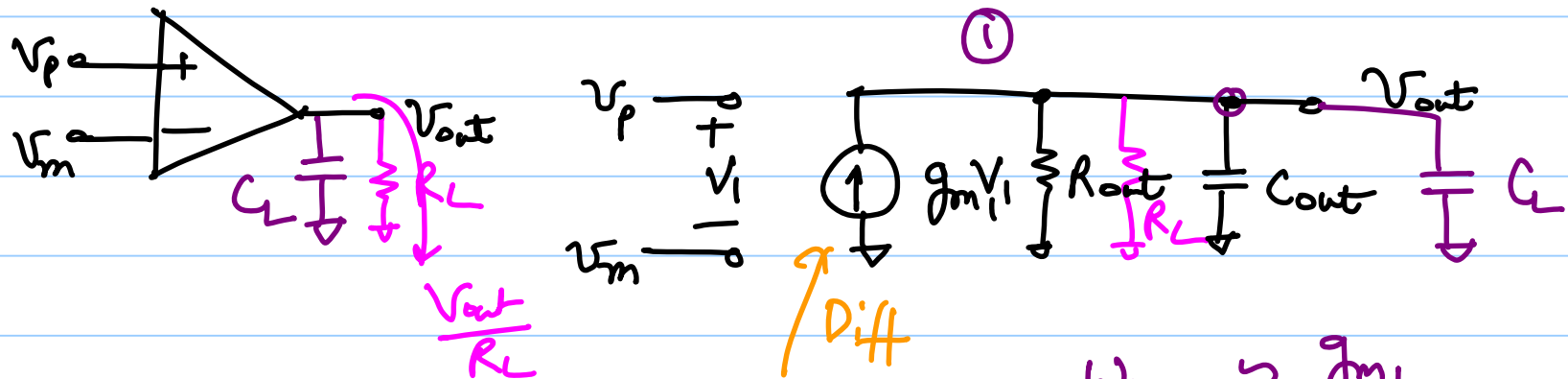


ECE 511 - Lecture 24

Note Title

4/24/2014


Single stage Diff Amplifier





$$\omega_{un} \approx \frac{g_{m1}}{C_L}$$

$$A_v = \cancel{g_{m1} R_{out}} \\ g_{m1} (R_{out} || R_L)$$

slowing

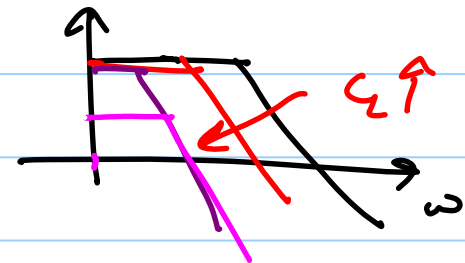

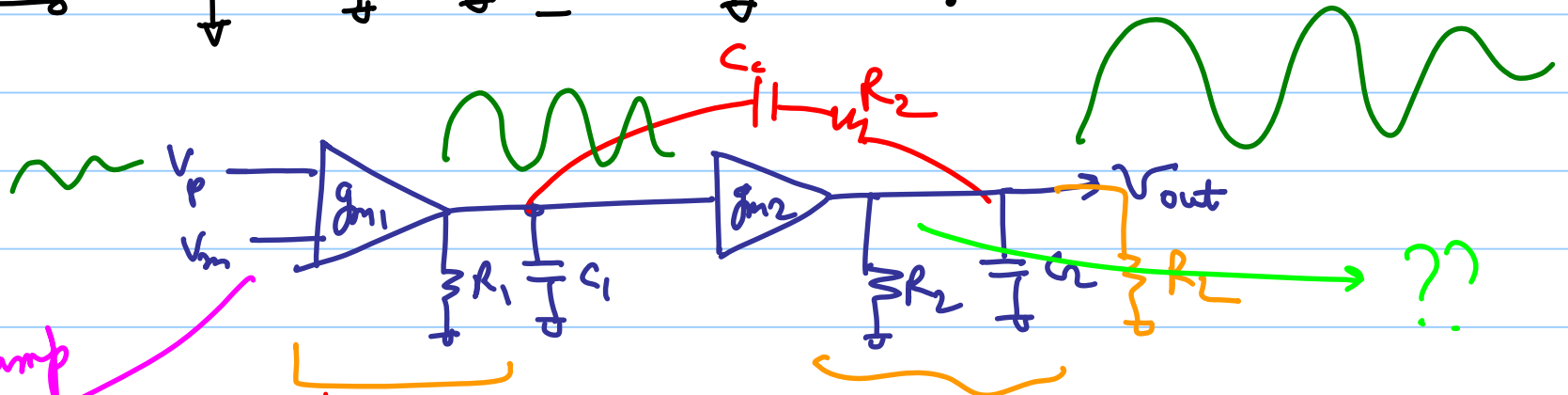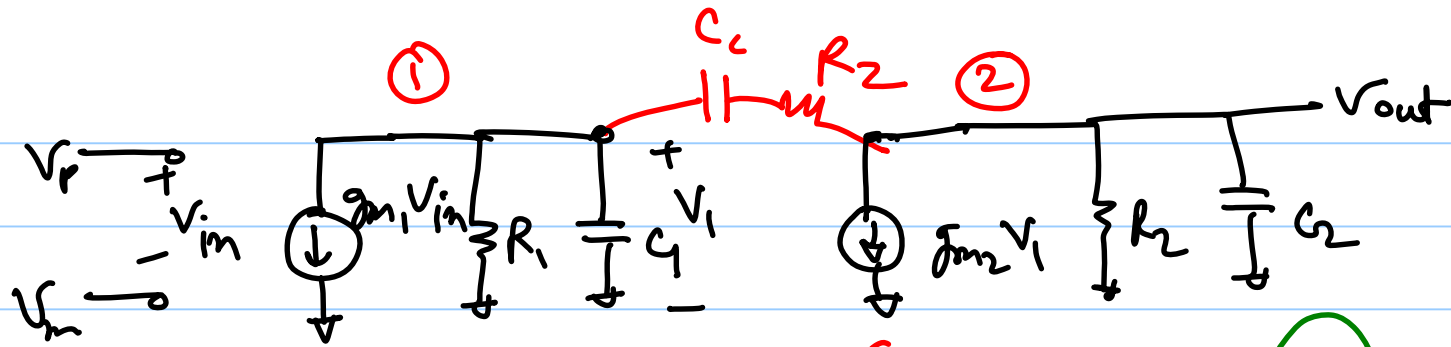

CM Load Diffamp
Telescopic
Folded Cascode




$g_{m1} R_1$
High-Stage

$g_{m2} (R_2 || R_L)$

High swing
large load drive
capacity

isolate gain from swing/drive
requirements

* Diffamp has a limited o/p swing

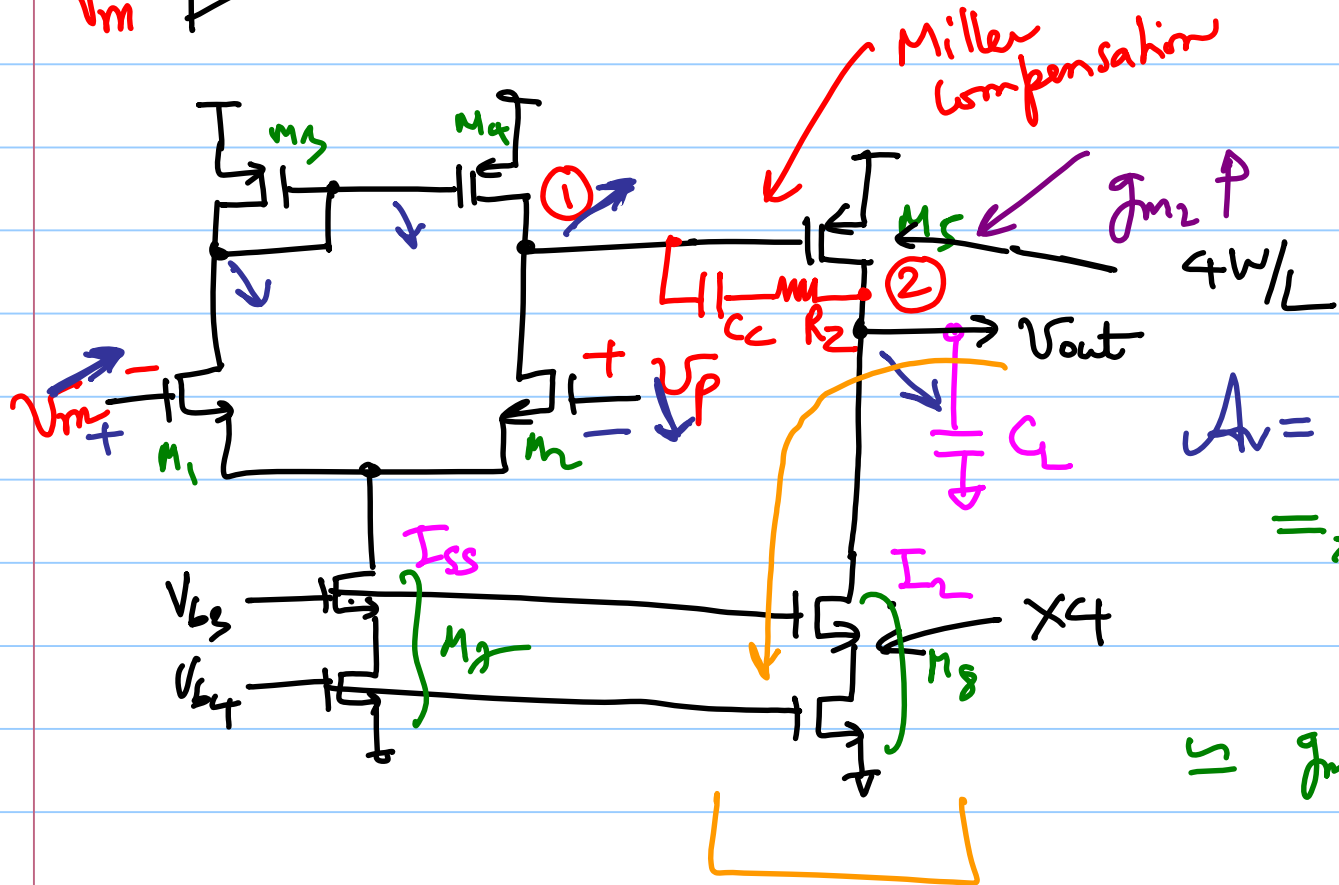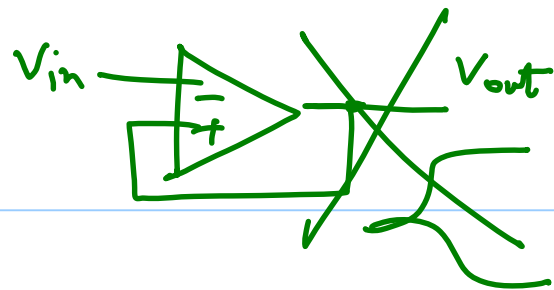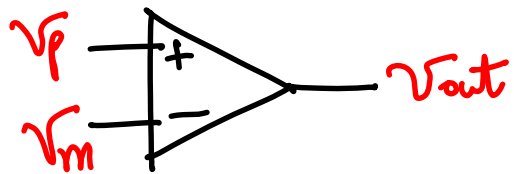


$$A_v = A_{v1} \cdot A_{v2}$$

$$= g_{m1,2} (\tau_{o2} \parallel \tau_{o4}) \times$$

$$\times g_{m5} (\tau_{o5} \parallel g_{m8} \tau_{o8}^2)$$

$$\approx g_{m1,2} (\tau_{o2} \parallel \tau_{o4}) \times g_{m5} \tau_{o5}$$

Class A ← Slew rate

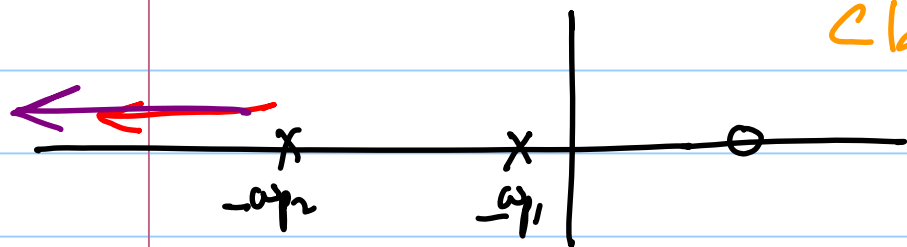

Second stage have higher $M \times (W/L)$ for g_{m2}

$$\downarrow \omega_{\text{om}} = \frac{g_{m1}}{C_{cc}}$$






$$\omega_{p2} \nearrow f \left(\frac{g_{m2}}{C_L} \right) \nearrow$$

$$C_c \uparrow$$

$$\boxed{f_T \propto \frac{V_{ov}}{L}}$$




$$\left\{ \begin{array}{l} g_{m1} \\ C_c \\ g_{m2} \end{array} \right.$$

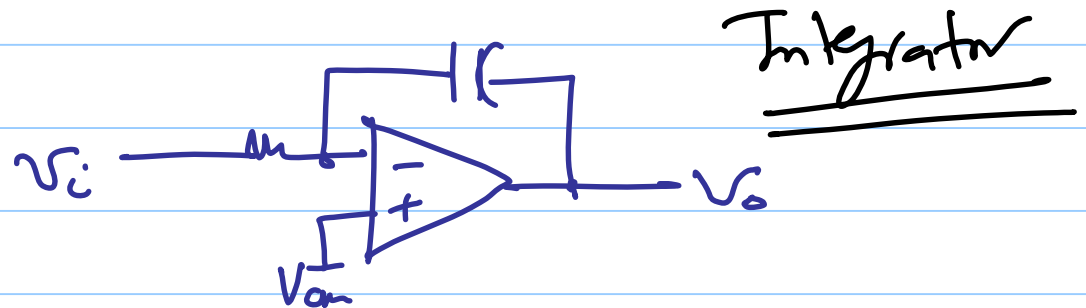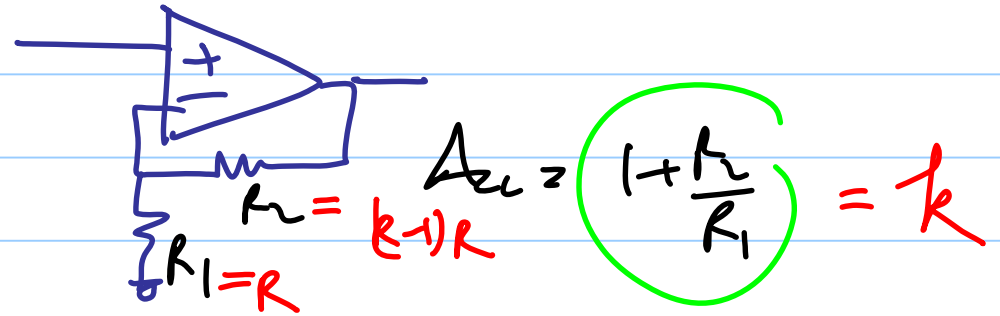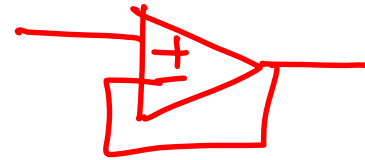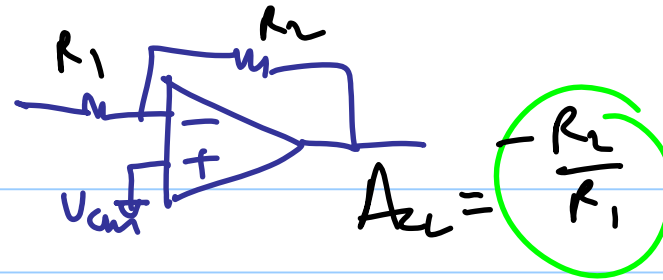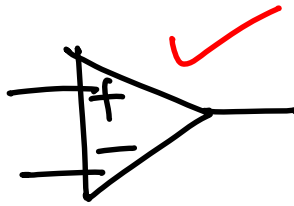
$$\boxed{V_{ov} = 2-5\% \text{ of } V_{DD}}$$




"Negative feedback Loop"

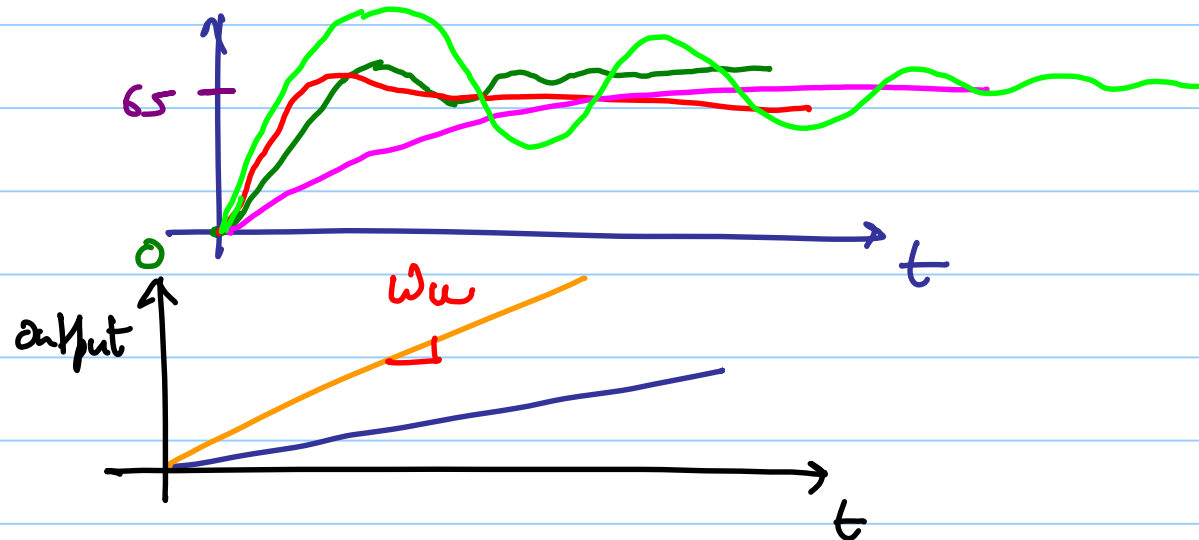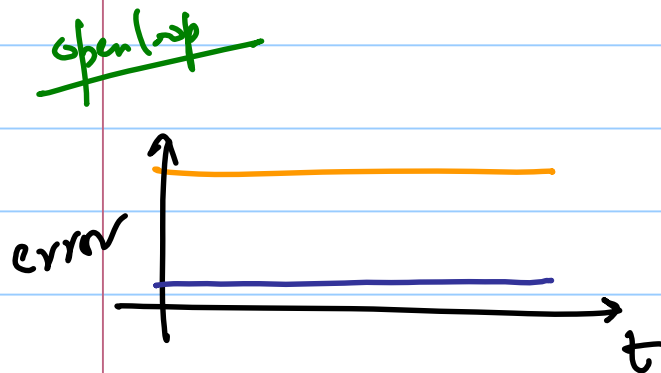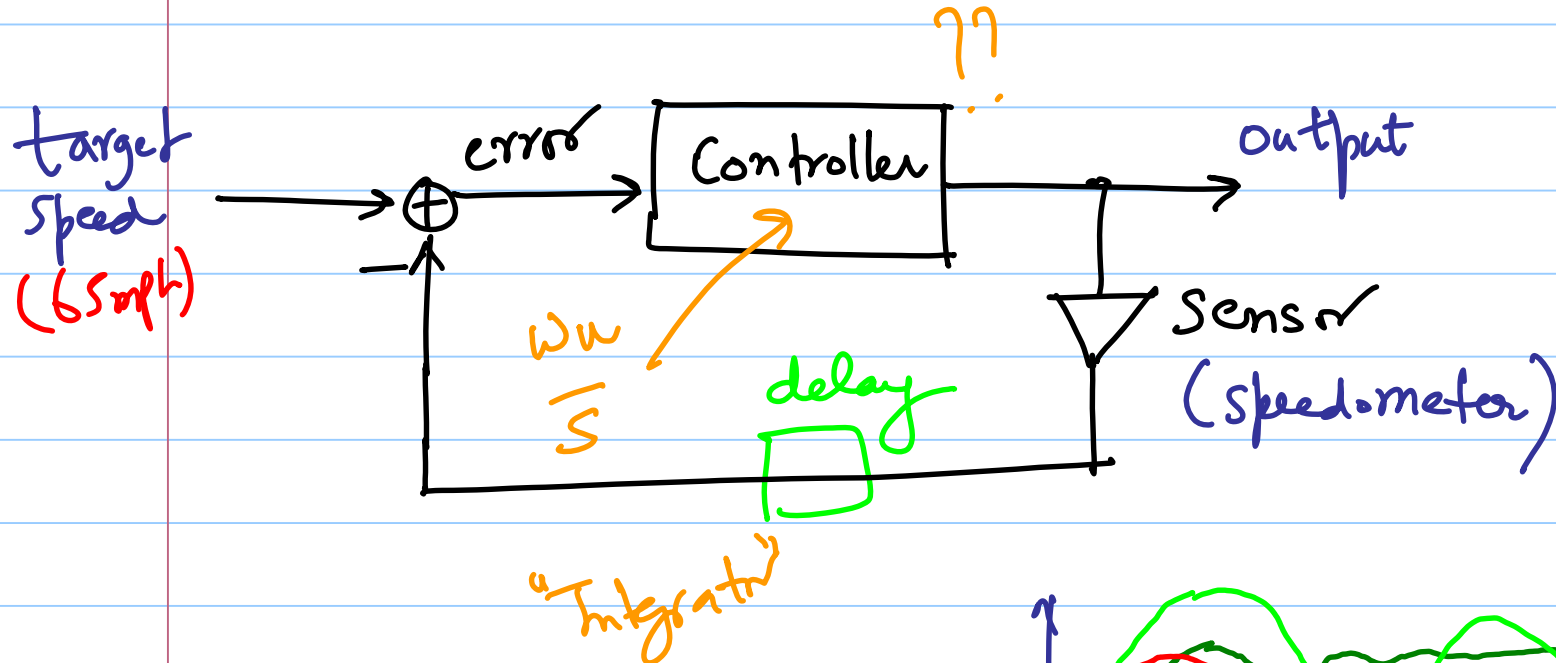Controller: change the o/r until error goes to zero



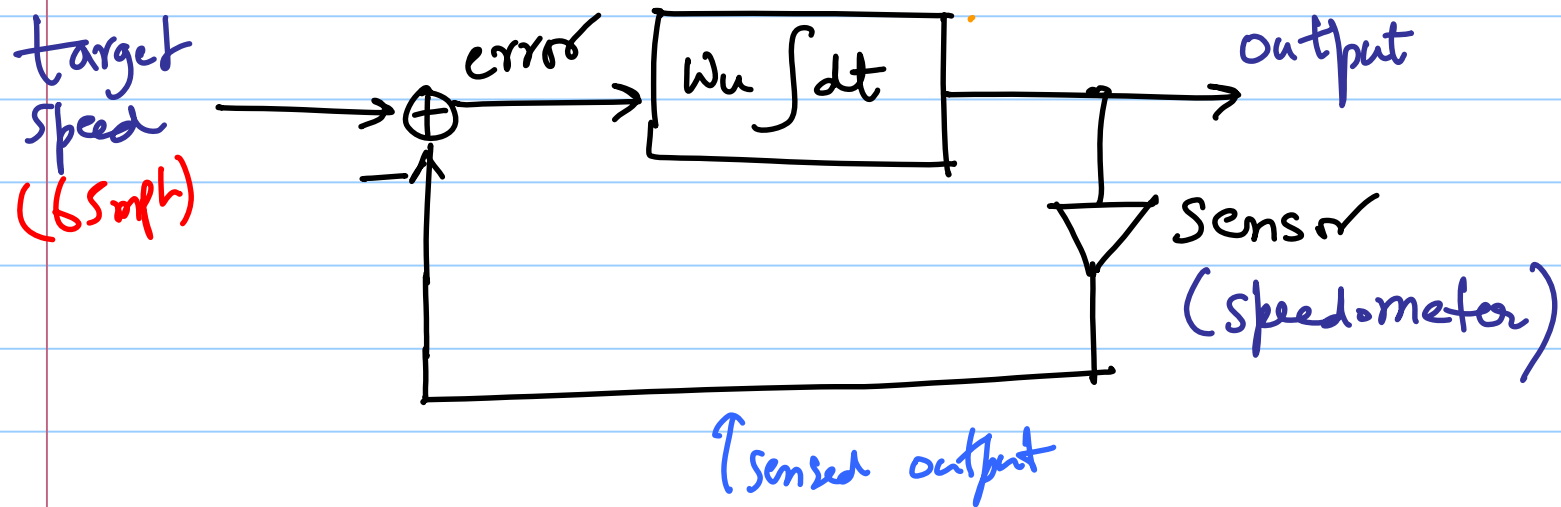


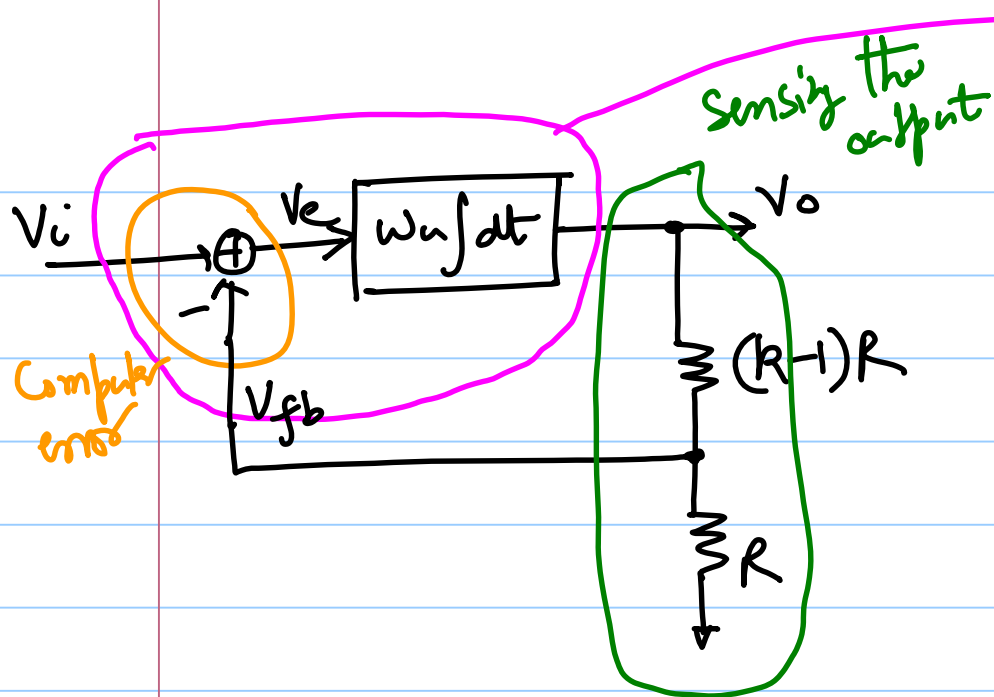

we require $V_o = kV_i$

In steady-state error $\rightarrow 0$
 $\Rightarrow V_o \rightarrow kV_i$



precise gain set by
resistive ratio


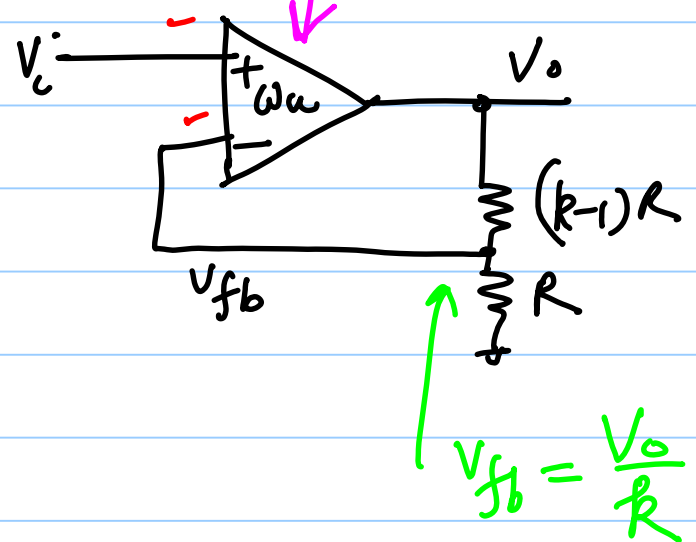



$$V_e = V_i - \frac{V_o}{k} \rightarrow 0$$

$$\Rightarrow V_o \rightarrow kV_i$$

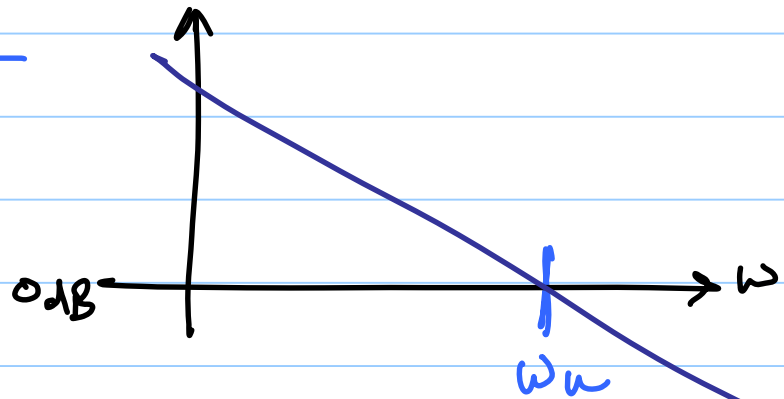
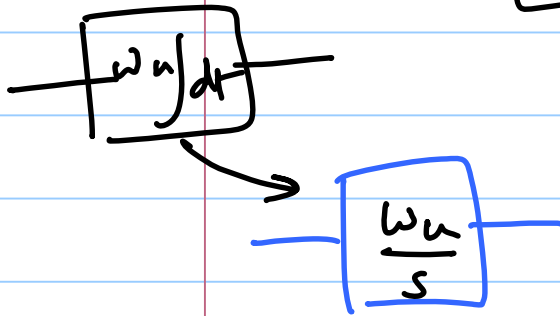
$\omega_u \rightarrow$ is the slope of the ^{open-loop} output for a unit step input
 $\hookrightarrow$ also the unity gain frequency of the comp. (controller)



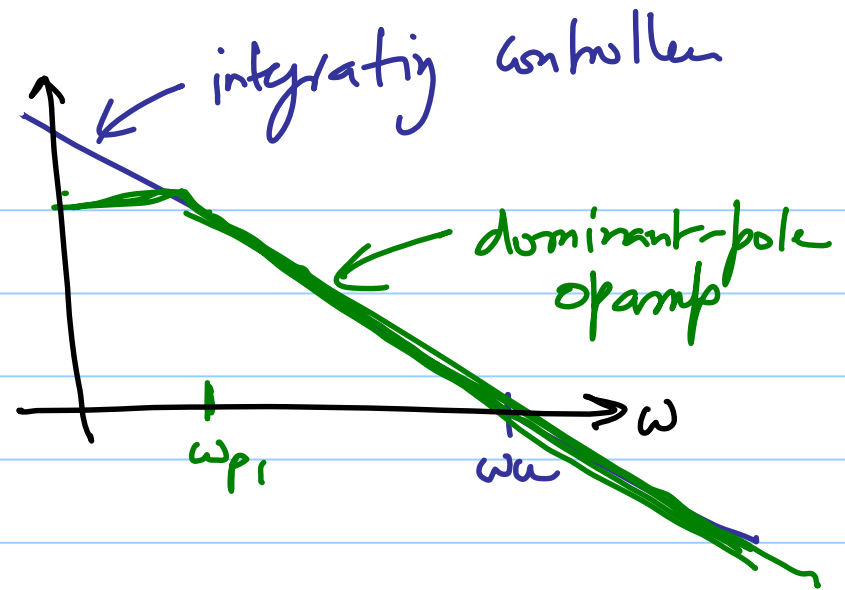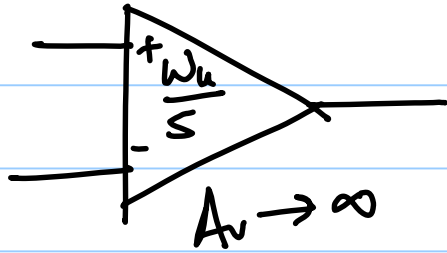

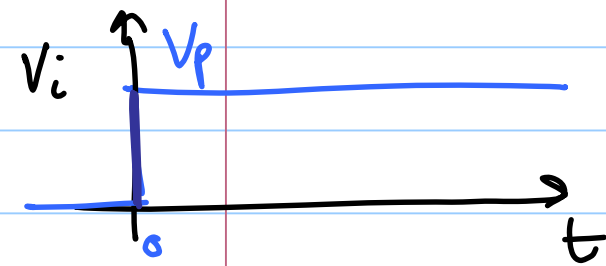

Assume $V_o(t=0) = 0$

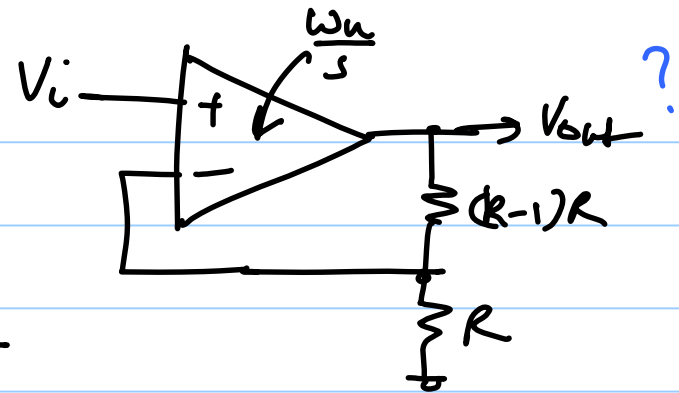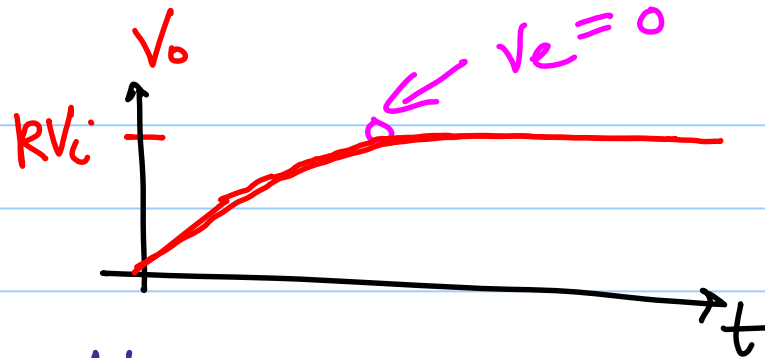


at $t=0$, $V_e = V_p \Rightarrow$ output start ramping at a rate $W_u V_p$

$\Rightarrow$ feedback signal $V_{fb} = \frac{W_u V_p}{R}$

as $V_{fb} \uparrow \Rightarrow V_e \downarrow$
 $\Rightarrow$ rate of increase in $V_o \downarrow$
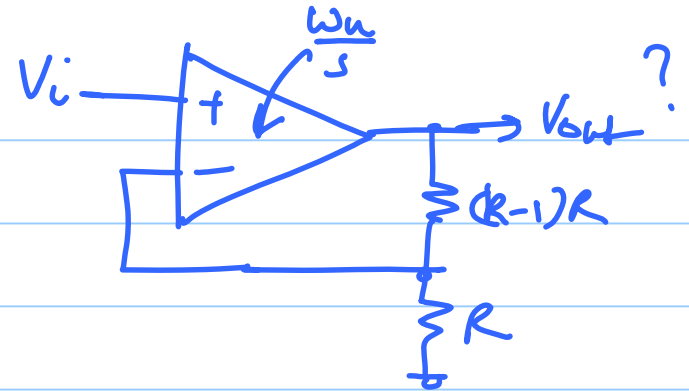
$$V_o(s) = \frac{\omega_u}{s} \left[V_i(s) - \frac{V_o(s)}{R} \right]$$



$$\frac{V_o(s)}{V_i(s)} = \frac{k}{1 + \frac{ks}{\omega_u}}$$

for $V_i(s) = \frac{V_p}{s}$


$$\Rightarrow V_o(s) = \frac{kV_p}{s \left(1 + \frac{ks}{\omega_u} \right)}$$

→ partial fraction
& apply inverse Laplace Transform

$$V_{out}(t) = kV_p \left[1 - e^{-\left(\frac{\omega_u t}{R} \right)} \right]$$

closed loop gain $\rightarrow k$

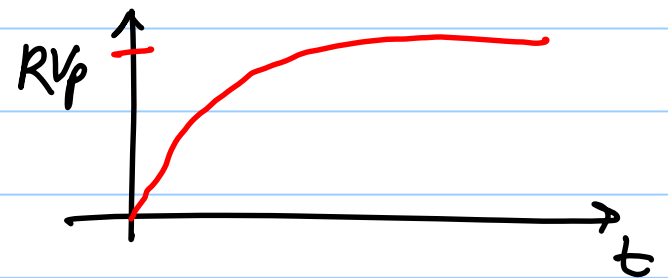closed-loop bandwidth $\rightarrow \omega_{uf}/R$




$$\frac{V_o}{V_i}(s) = \frac{k}{1 + \frac{s k}{\omega_u}} = \frac{A_{CL}}{1 + s/\omega_{3dB}}$$

$$\omega_{3dB} = \frac{\omega_u}{k}$$


$$A_{CL} \times \omega_{3dB} = k + \frac{\omega_u}{k}$$

$$= \omega_u$$

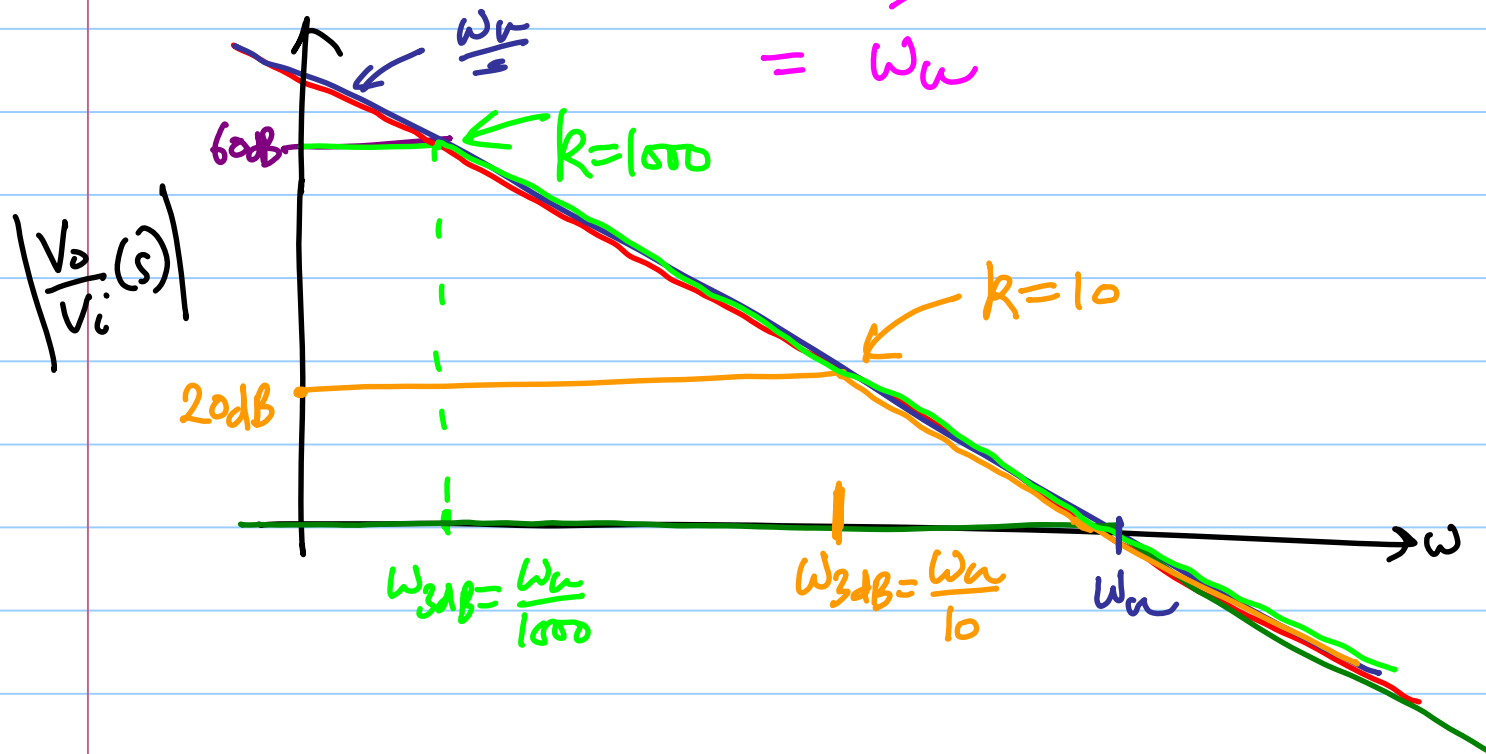

$k=1$

Microelectronics
by
Razavi

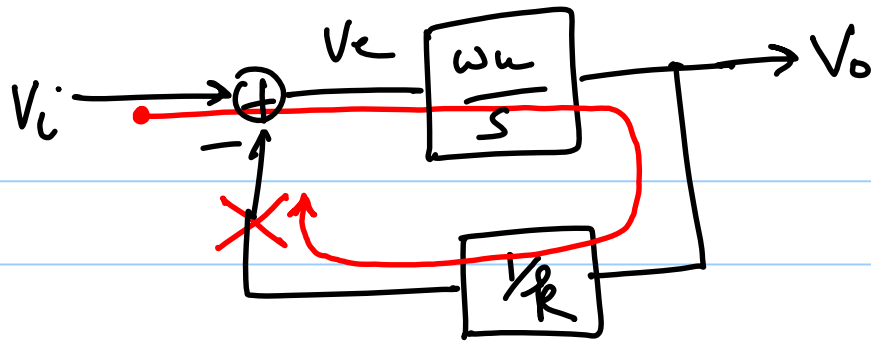


ω_u = unity gain frequency
of the integrator
controller

Loop-response

$$L(s) = \frac{\omega_u}{k \cdot s}$$

← loop-gain ⇒ implies
open-loop
behavior
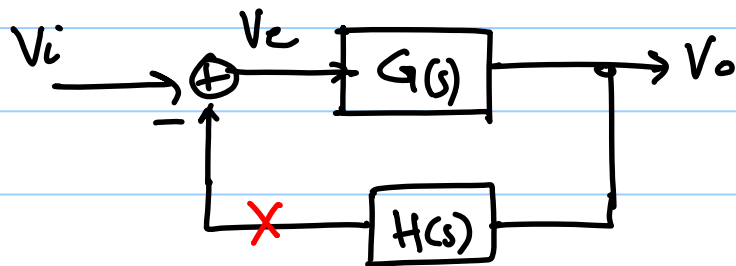
$$\omega_{u, \text{loop}} = \frac{\omega_u}{k} \leftarrow \text{unity gain loop frequency}$$



$$L(s) = G(s) \cdot H(s)$$

closed-loop response

$$\frac{V_o(s)}{V_i(s)} = \frac{G(s)}{1 + G \cdot H(s)}$$

$$\frac{V_o}{V_i}(s) = \frac{G}{1+GH} = \frac{1}{H(s)} \cdot \frac{1}{1 + \frac{1}{G(s) \cdot H(s)}}$$

$$\approx \begin{cases} \frac{1}{H(s)} \\ G(s) \end{cases}$$

$$|GH| \gg 1 \leftarrow |L| \gg 1$$

$$|GH| \ll 1$$

for large $|L| \gg 1$ (loop gain)

$$\text{closed-loop gain} \approx \frac{1}{|H|}$$