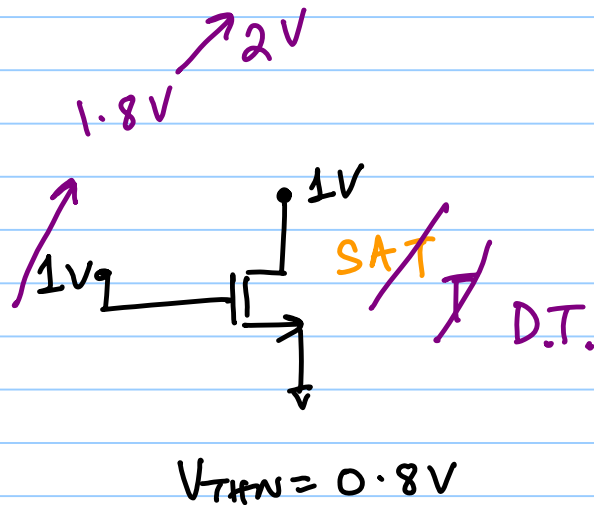



ECE 511- Lecture 2

Note Title

1/23/2014




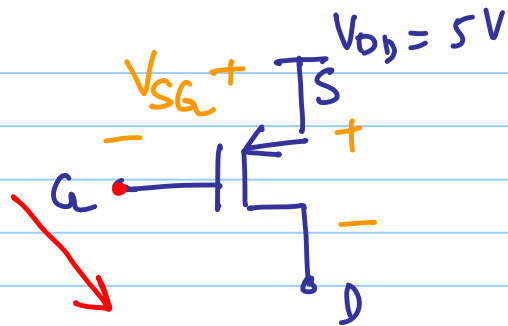The NMOS can have the gate at max V_{THN} higher than the draining before the NMOS triodes.



for SAT,
 $V_{SD} > V_{SD, sat}$


$$V_{THP} = 0.9V$$

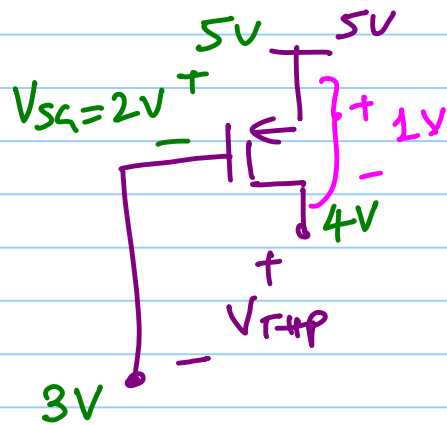

$$V_{SD, sat} = V_{SG} - V_{THP} = 1.1V$$

The gate at min, $|V_{THP}|$ lower than the drain, before PM triode


for saturation: $V_G > V_D - |V_{THP}|$

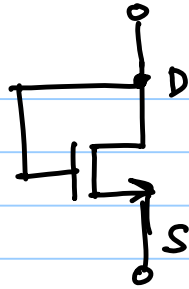

Diode connected MOSFET
 $\rightarrow$ gate - Drain are shorted

$$I_D = f(V_{GS}, V_{DS})$$


$$\Rightarrow I_D = f(V_{GS})$$

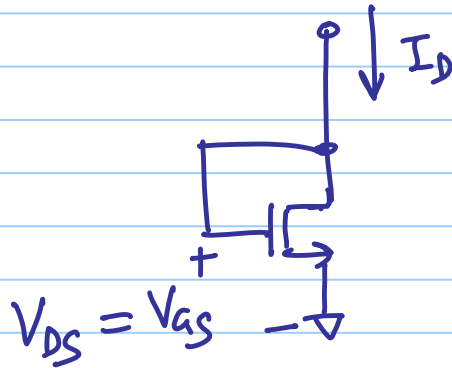

$$\text{for } V_{GS} > V_{THN} \Rightarrow I_D > 0$$


$$\text{For Saturation} \Rightarrow V_{DS} \geq V_{GS} - V_{THN}$$

$\Rightarrow$ Always in Saturation!

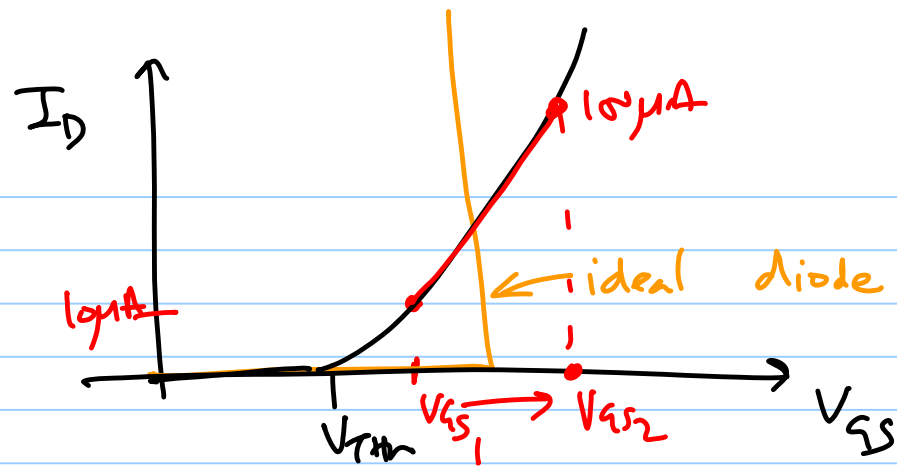

removed 1 independent variable $\Rightarrow V_{DS}$

$$\lambda = 0$$

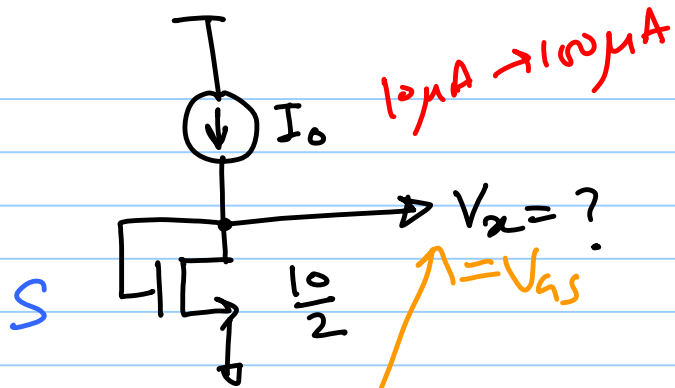

$$K'_n = 120 \frac{\mu\text{A}}{\text{V}^2}$$




$$V_{THN} = 0.8$$


$$I_o = 10 \mu\text{A}$$

$$I_D = \frac{K'_n}{2} \frac{W}{L} (V_{GS} - V_{THN})^2 \quad \text{---} (1 + \lambda(V_{DS}))$$

$$V_{GS} = \sqrt{\frac{2I_D}{\beta}} + V_{THN}$$


for hand-calc
assume $\lambda = 0$

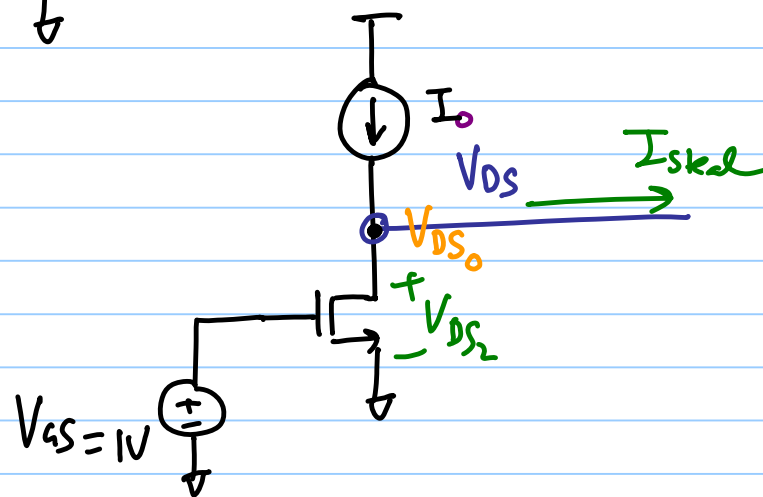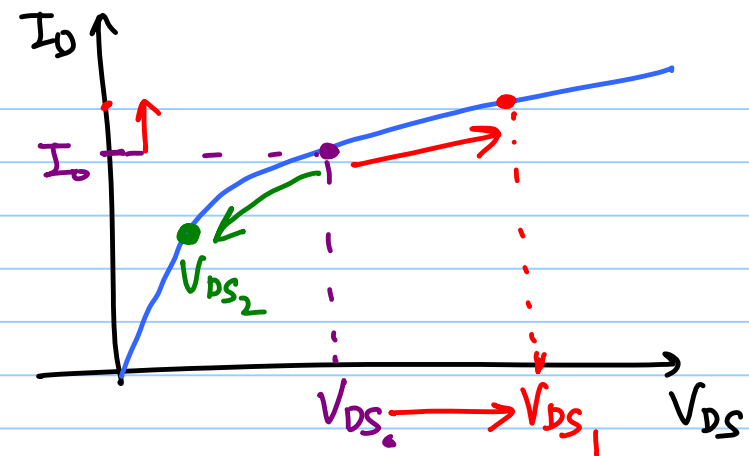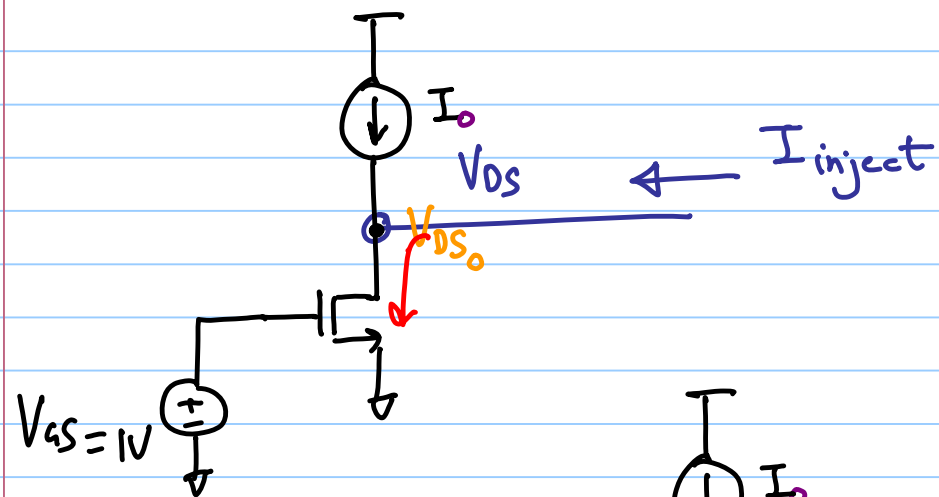

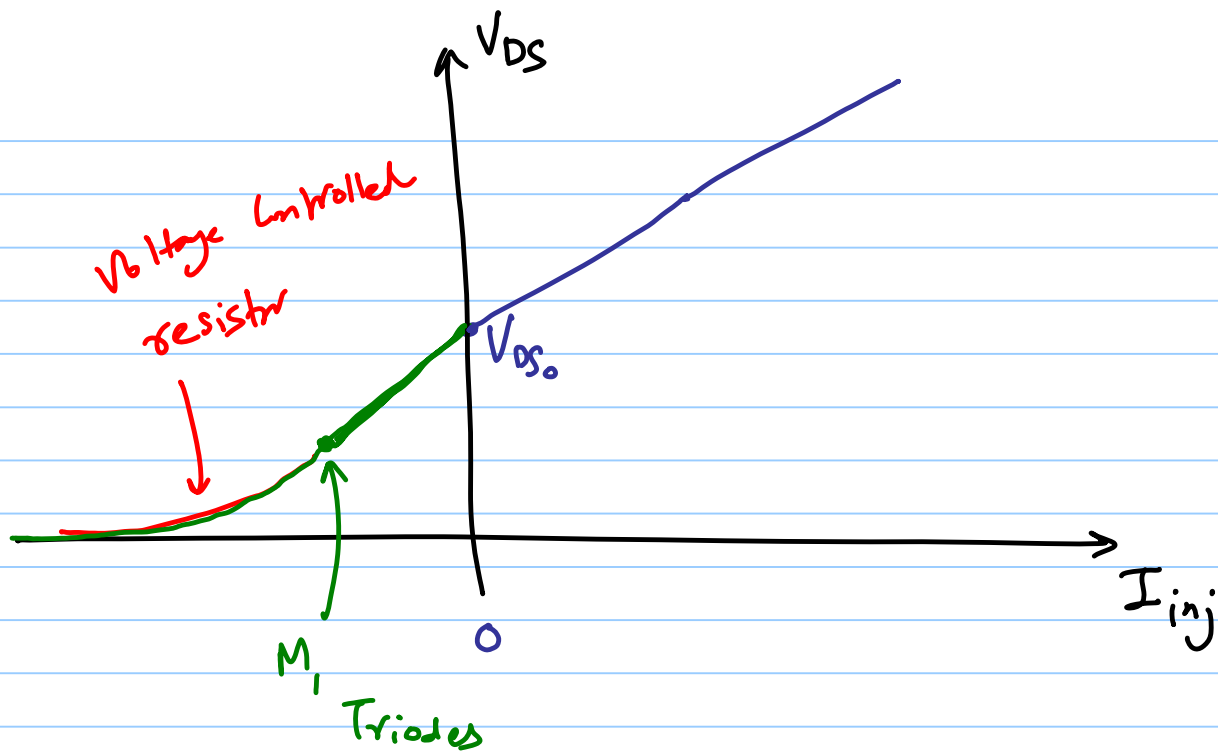



HW

PMOS

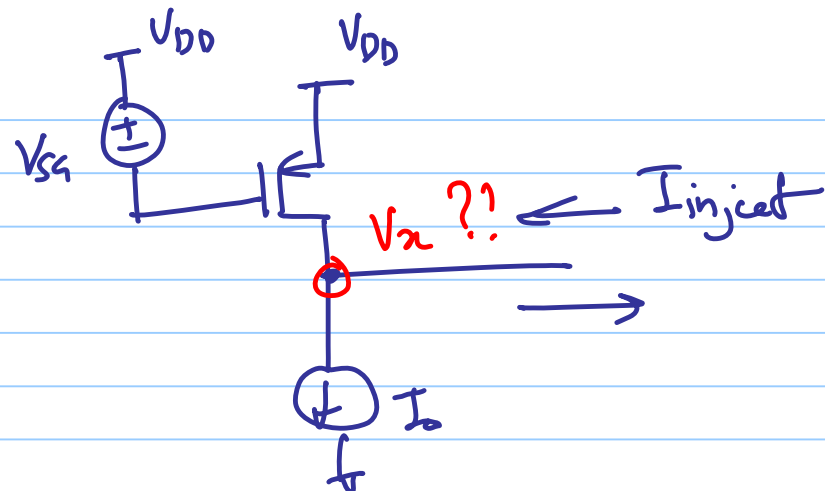

"Small-Signal Analysis"

"Bias"

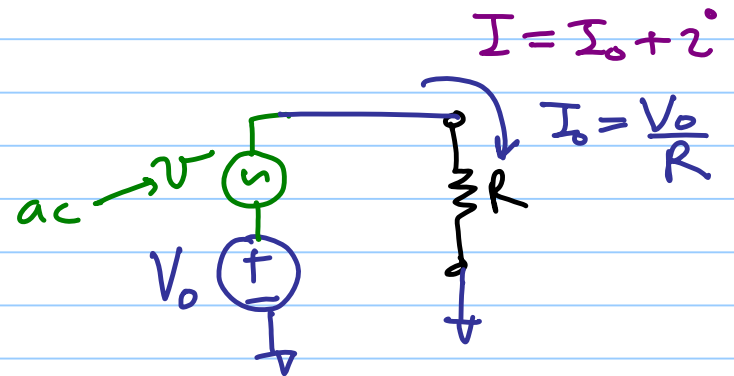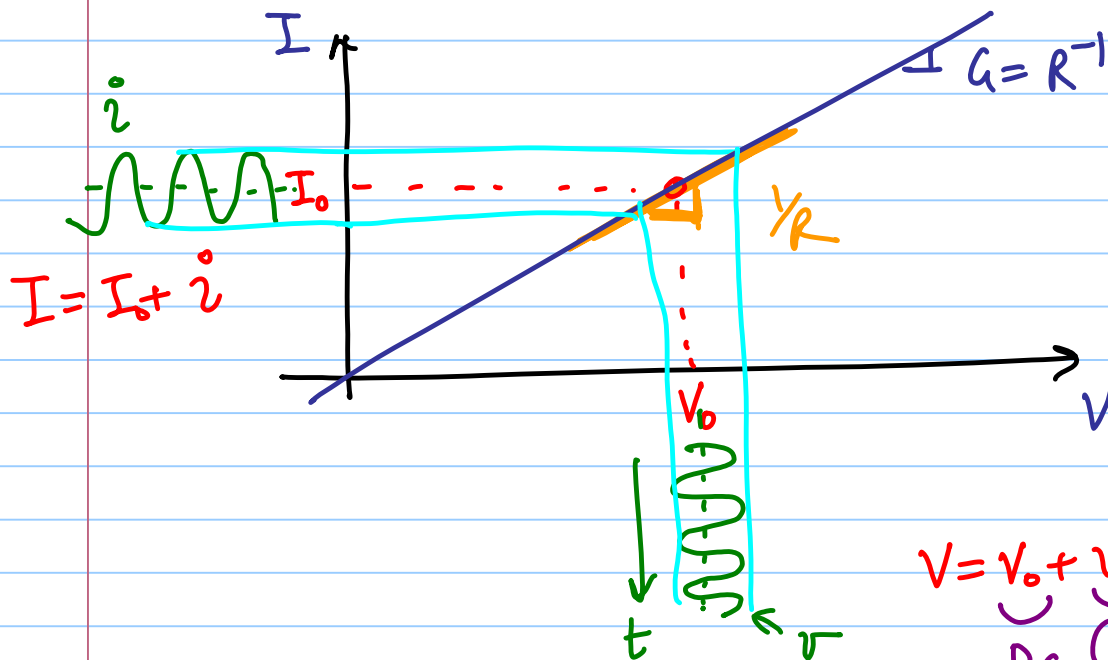

$$V = \underbrace{V_0}_{\text{DC}} + \underbrace{v}_{\text{AC}}$$

Small-signal incremental

$$I = \frac{V}{R}$$


$$(I_0 + i) = \frac{(V_0 + v)}{R}$$

$$I_0 + i = \frac{V_0}{R} + \frac{v}{R}$$

$\downarrow$
 $\frac{V_0}{R}$
 (bias point)

$$i = \frac{v}{R}$$

small signal
behavior

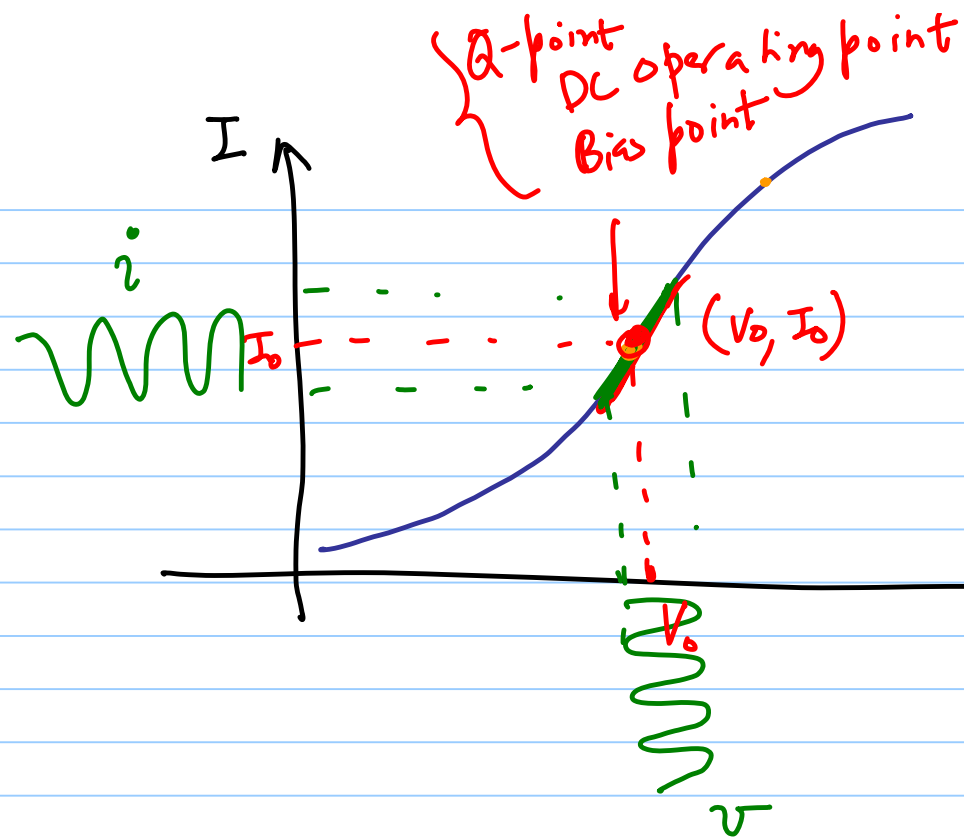

$$i \leftrightarrow v$$

$$I = f(V) = \tanh\left(\frac{V}{V_A}\right)$$

$$\text{slope} = \frac{\partial I}{\partial V} = \frac{i}{v}$$

small
signal

$$\text{Resistance} = \frac{1}{\text{slope}} = \frac{v}{i}$$

$$I = f(V)$$

Taylor Series Expansion
 $V = V_0$

DC operating point

$$I_0 = f(V_0)$$

$$(V = V_0 + v)$$

Ac signal

$$I = \underbrace{f(V_0)}_{I_0} + f'(V_0) \cdot \underbrace{(V - V_0)}_v + \frac{f''(V_0)}{2} \underbrace{(V - V_0)^2}_{v^2} + \frac{f'''(V_0)}{6} \underbrace{(V - V_0)^3}_{v^3} + \dots$$

higher order terms

$$I - I_0 = f'(V_0) \cdot v + \frac{f''(V_0)}{2} v^2 + \frac{f'''(V_0)}{6} v^3 + \dots$$

$$i = a_1 v + a_2 v^2 + a_3 v^3 + \dots$$

$a_1 = f'(V_0)$


If v is sufficiently small, we can neglect higher-order terms

$$i = g_1 v$$

Small-signal parameter

Small-signal
conductance

$$g_1 = \left. \frac{\partial i}{\partial v} \right|_{v=v_0}$$

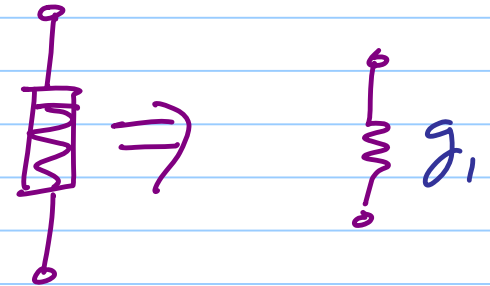

$\Rightarrow$ We can linearize a non-linear circuit about the DC Bias point, by taking the first term in the Taylor Series Expansion.


$$i = g_1 v + \underbrace{g_2 v^2 + g_3 v^3 + \dots}_{\text{distortion}}$$


$$\begin{cases} \cos 2\theta = 1 - 2\sin^2\theta \\ \sin^2\theta = \frac{1 - \cos 2\theta}{2} \end{cases}$$

$$v = A \sin(\omega_1 t)$$


$$i = \underline{\underline{g_1(A \sin \omega_1 t)}} + \underline{\underline{g_2(A^2 \sin^2 \omega_1 t)}} + \underline{\underline{g_3(A^3 \sin^3 \omega_1 t)}}$$

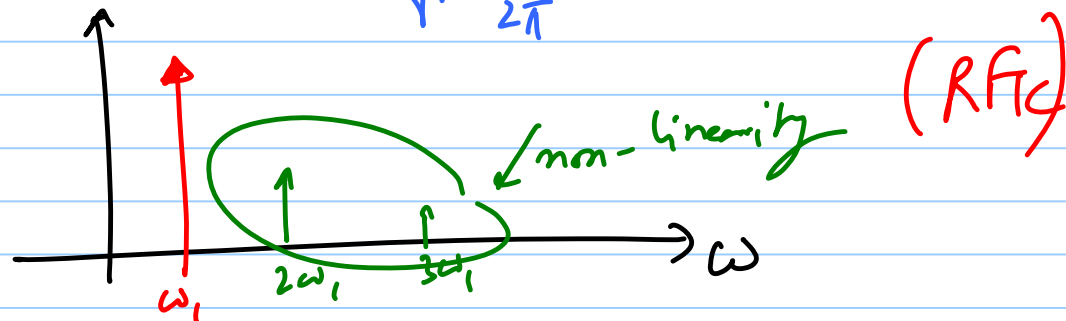$f_1 = \frac{\omega_1}{2\pi}$
 $\omega_1, 2\omega_1$
 $\omega_1, 3\omega_1$




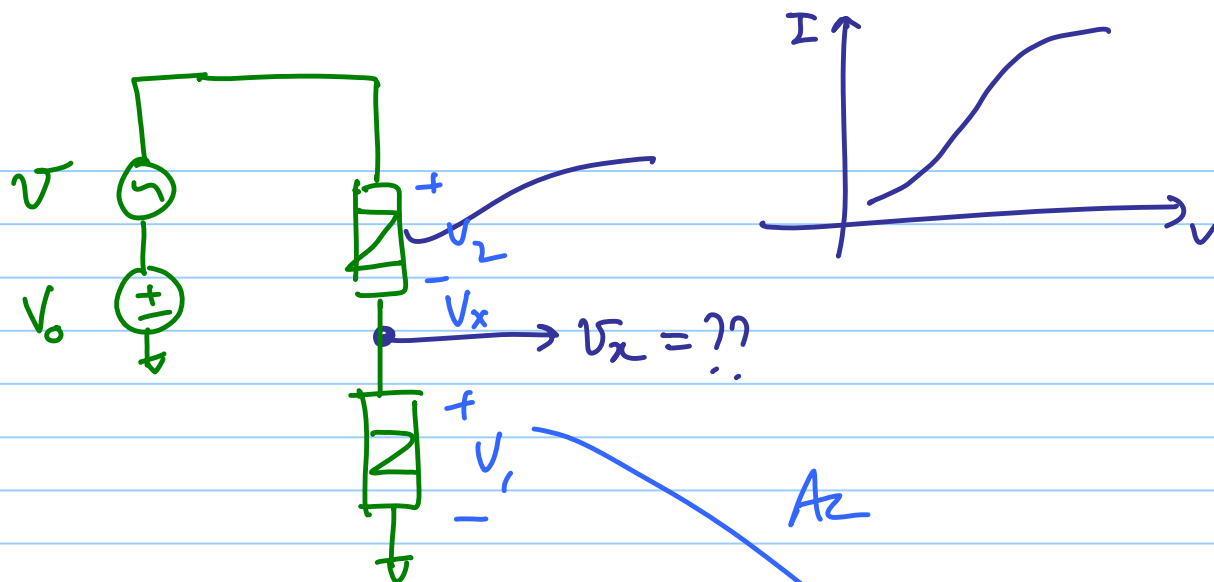

A_2

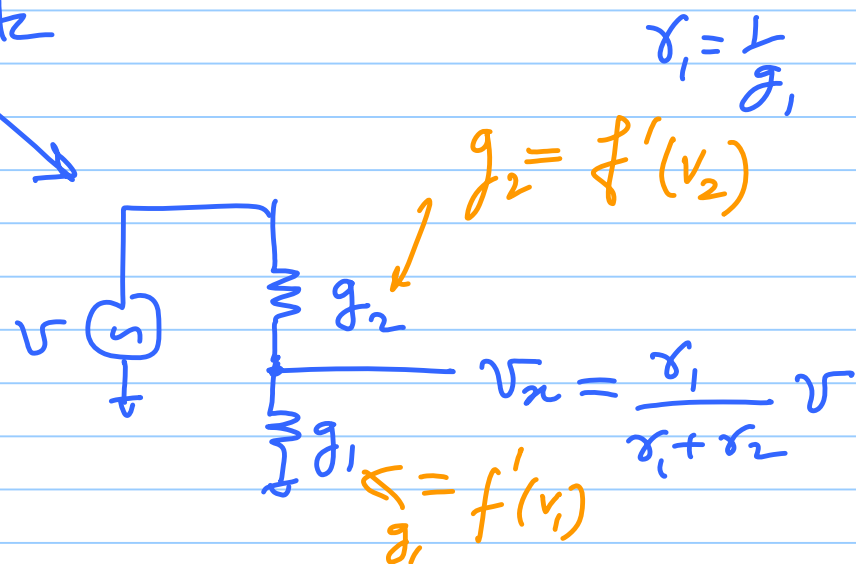

NMOS in Saturation

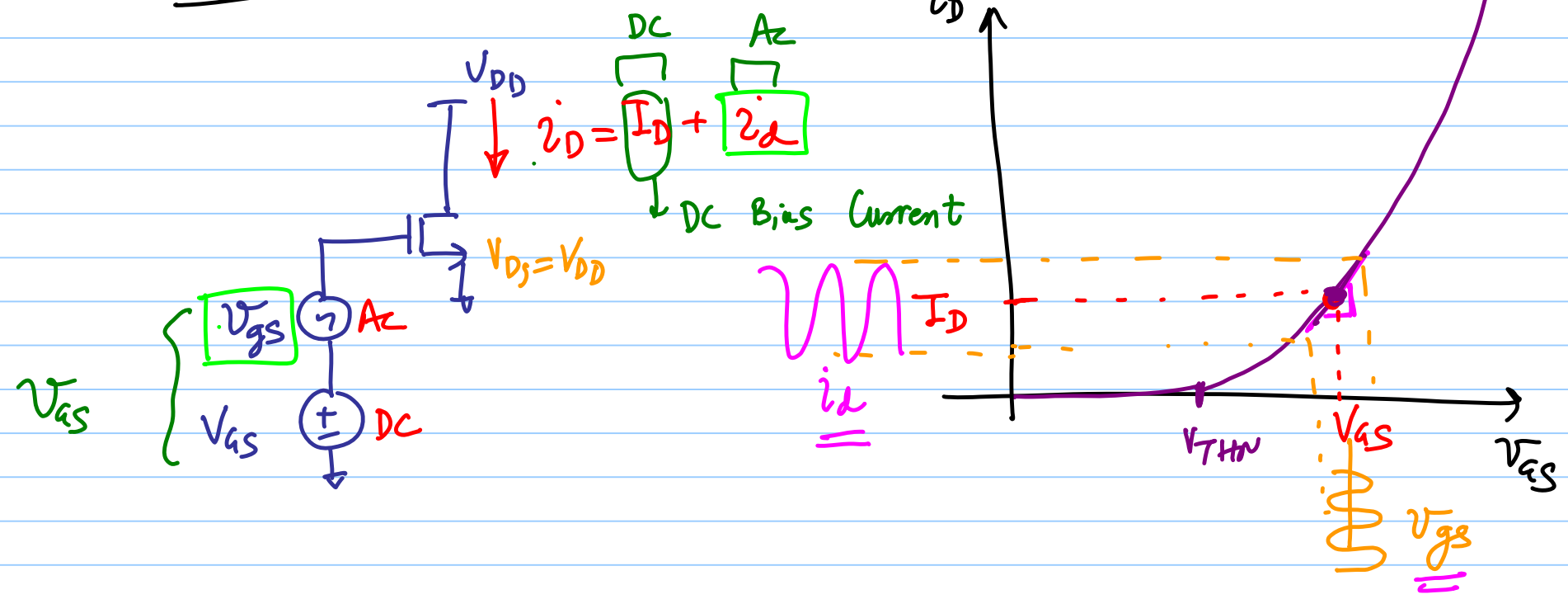

$$i_D = \frac{K_P n}{2} \frac{W}{L} (V_{GS} - V_{THN})^2$$

$I_D + i_d$ (pointing to i_D)
 $V_{GS} + v_{gs}$ (pointing to V_{GS})

$$i_d = () v_{gs}$$

$$g_m = \left. \frac{\partial i_D}{\partial V_{GS}} \right|_{V_{GS}=V_{GS}} = \frac{K_P n}{2} \frac{W}{L} (V_{GS} - V_{THN}) \Big|_{V_{GS}=V_{GS}} = \underbrace{K_P n \cdot \frac{W}{L}}_{\beta} \underbrace{(V_{GS} - V_{THN})}_{V_{OV}}$$

Transconductance

$$i_d = g_m v_{gs}$$

$$g_m = \beta_n (V_{GS} - V_{THN}) = \beta_n V_{OV} \longrightarrow \textcircled{1}$$

$$g_m = \beta_n \cdot \sqrt{\frac{2I_D}{\beta_n}} = \sqrt{2\beta_n I_D} \longrightarrow \textcircled{2}$$

$$V_{GS} - V_{THN} = \sqrt{\frac{2I_D}{\beta_n}}$$


$$g_m = \beta_n (V_{GS} - V_{THN})$$

$$= \frac{2I_D}{(V_{GS} - V_{THN})^2} \times \cancel{(V_{GS} - V_{THN})} = \frac{2I_D}{V_{GS} - V_{THN}} = \frac{2I_D}{V_{OV}} \longrightarrow \textcircled{3}$$

$$g_m = \left\{ \begin{array}{l} \beta_n V_{ov} \\ \sqrt{2\beta_n I_D} \\ \frac{2I_D}{V_{ov}} \end{array} \right.$$


(W/L) Sizing
 β_n, V_{ov}, I_D

$$g_m = \beta V_{ov}$$

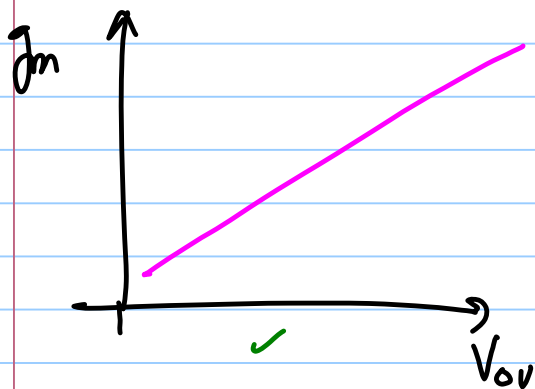


$$\left(\frac{W}{L}\right) = \text{constant}$$

$$g_m = \sqrt{2\beta_n I_D}$$

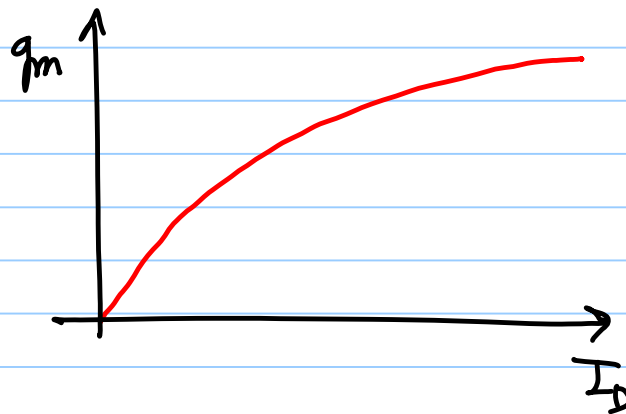

$$\left(\frac{W}{L}\right) = \text{constant}$$

$$g_m = \frac{2I_D}{V_{ov}}$$

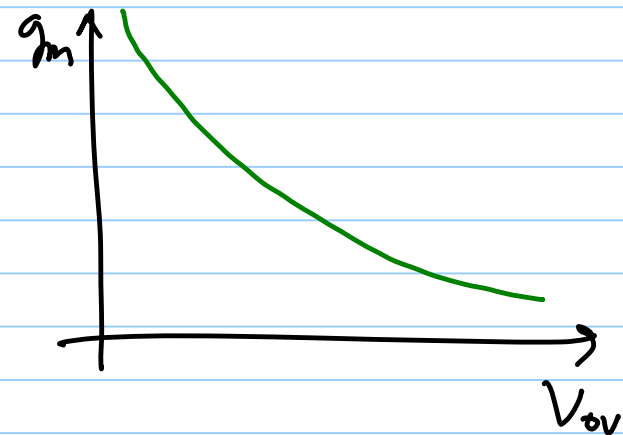

$$I_D = \text{constant}$$

Small-signal model (so far)

