


ECE 511- Lecture 3



Note Title

1/28/2014

"Try Open NX
client"

$$g_m = \left. \frac{\partial i_D}{\partial V_{GS}} \right|_{V_{GS}}$$

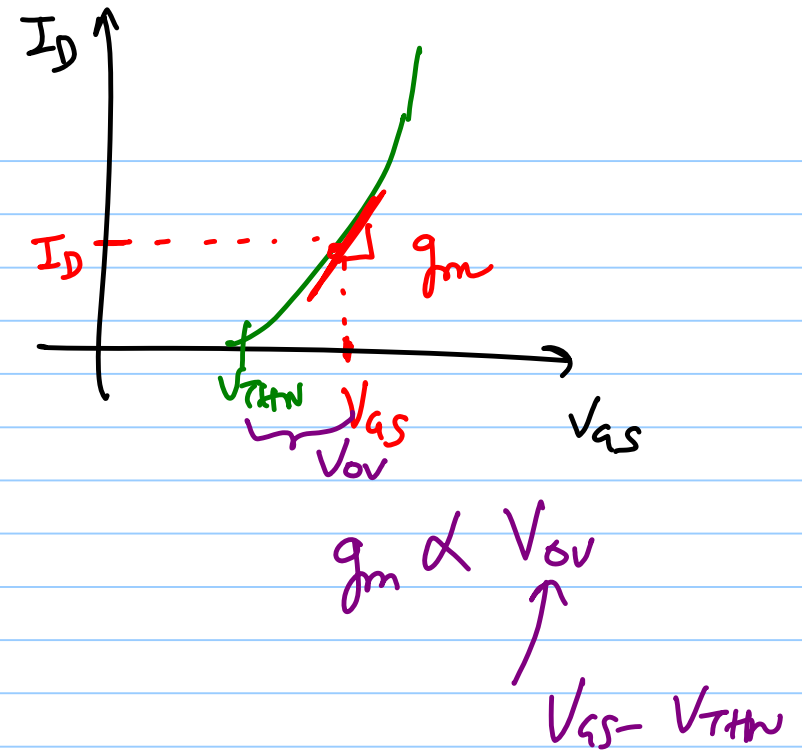

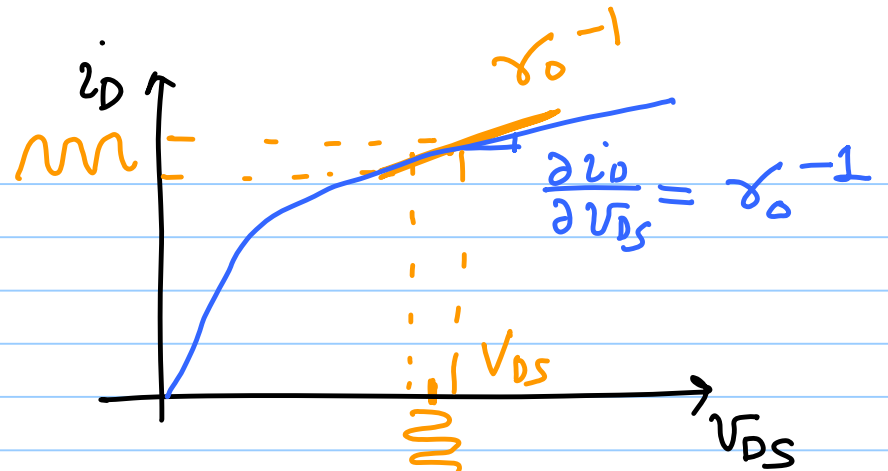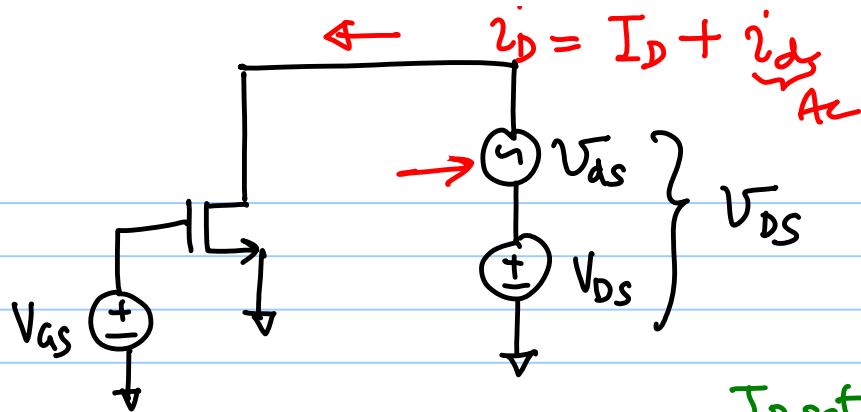


$$i_D = \frac{k \mu_n}{2} \frac{W}{L} (V_{GS} - V_{THN})^2 [1 + \lambda (V_{DS} - V_{DS,sat})]$$

$I_{D,sat}$

$$g_0 = g_{ds} = \gamma_0^{-1} = \frac{\partial i_D}{\partial V_{DS}} = I_{D,sat} \cdot \lambda$$



$$\gamma_0 = \frac{1}{\lambda I_{D,sat}}$$

Small-signal Model
"So-far"

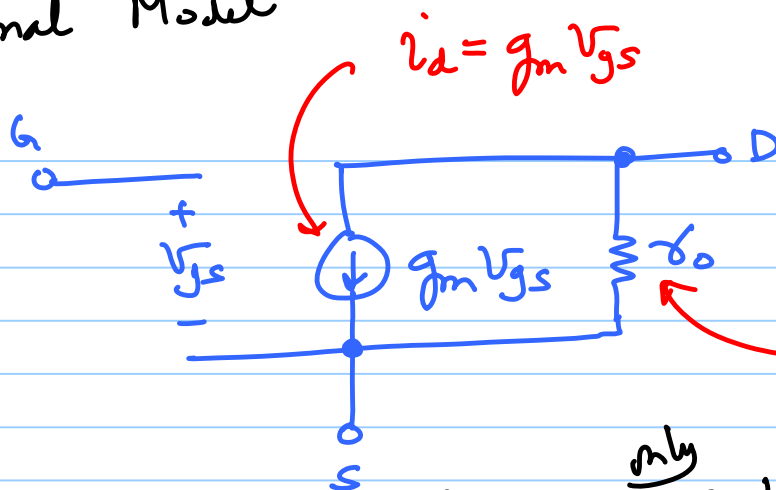

Not ^{only} 3 terminals

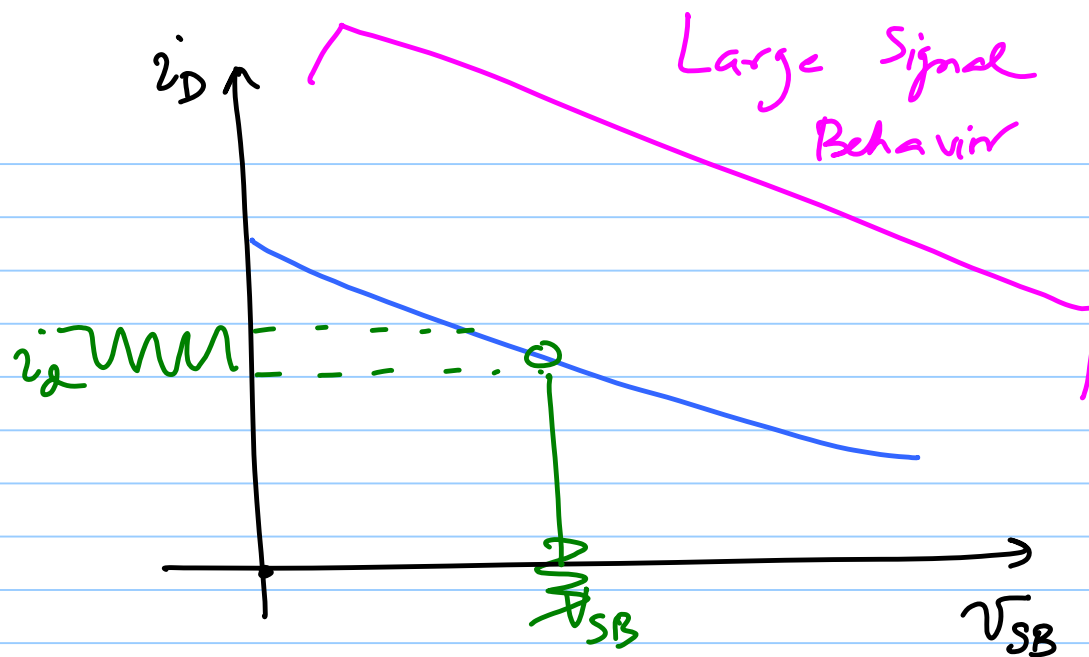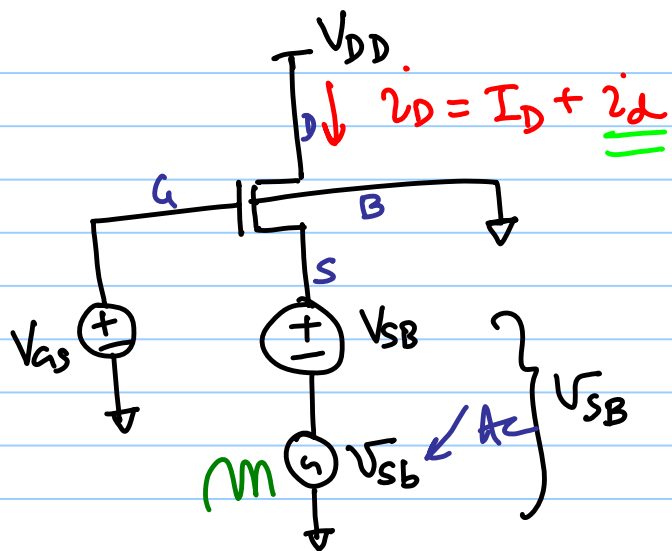accounts for $\lambda > 0$
Channel length Modulation



Body transconductance

$$g_{mb} = \left. \frac{\partial i_D}{\partial V_{SB}} \right|_{V_{SB}}$$

$$i_D = \frac{\mu_n C_{ox}}{2} \frac{W}{L} (V_{GS} - V_{THN})^2 \quad \text{f}(V_{SB})$$

$$g_{m_b} = \left. \frac{\partial i_D}{\partial V_{SB}} \right|_{V_{SB}} = \underbrace{\frac{\mu_n C_{ox}}{2} \frac{W}{L} (V_{GS} - V_{THN})}_{g_m} \times \left(- \frac{\partial V_{THN}}{\partial V_{SB}} \right) \bigg|_{V_{SB}}$$

$$= g_m \cdot \left(- \frac{\partial V_{THN}}{\partial V_{SB}} \right) \bigg|_{V_{SB}} \quad ?$$

$$V_{THN} = V_{THN0} + \gamma \left(\frac{\sqrt{V_{SB} + |2V_{fp}|}}{\sqrt{2V_{fp}}} \right)$$

$$= g_m \cdot \underbrace{\left(- \frac{\gamma}{2} (|2V_{fp}| + V_{SB})^{-1/2} \right)}_{\eta}$$


$$g_{mb} = g_m \cdot \eta$$

describes the
dependence of
 i_d on V_{SB}


$$\eta = \frac{-\gamma}{2\sqrt{|2V_{FB}| + V_{SB}}}$$


Since $\eta < 0 \Rightarrow$ effect of g_{mb} opposes g_m

* Small signal model of 4-terminal NMOS

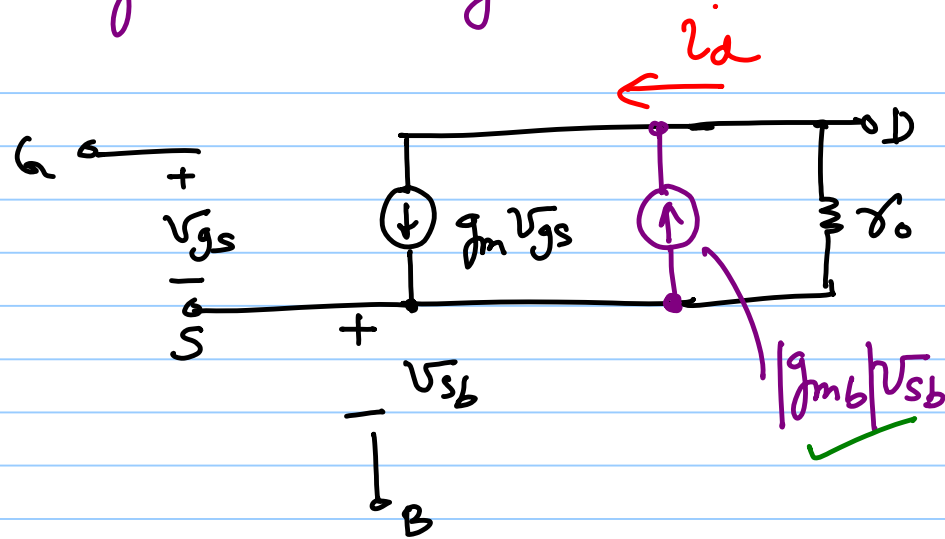


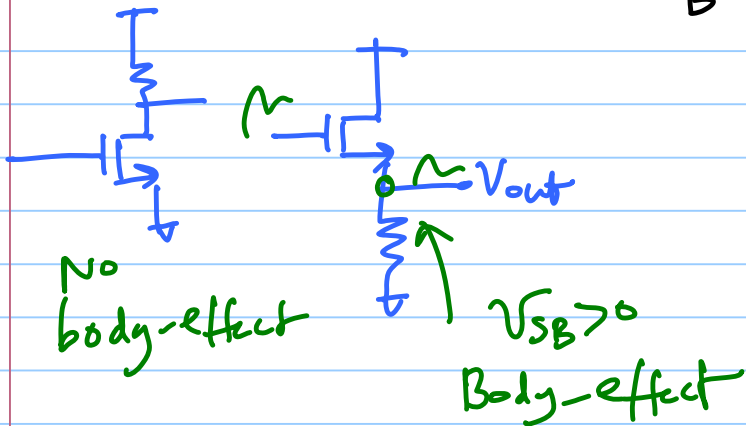If source is "wiggling"
 $\Rightarrow g_{mb}$ comes into picture.




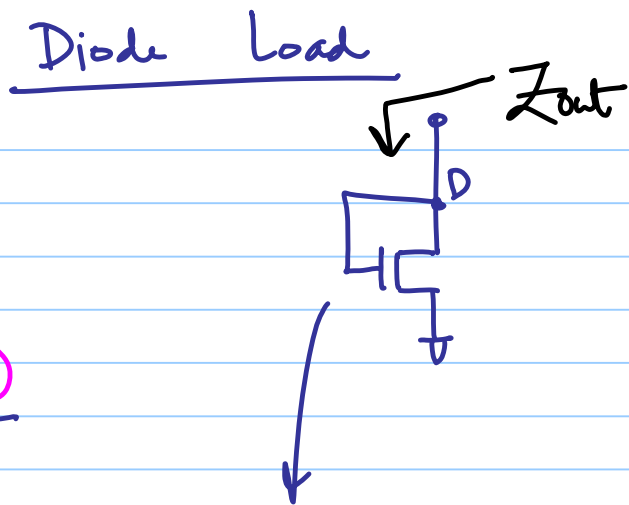

Small signal

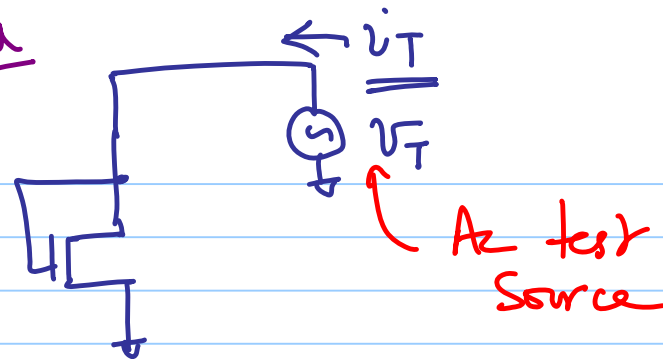

$$Z_{out} = \frac{V_T}{i_T}$$

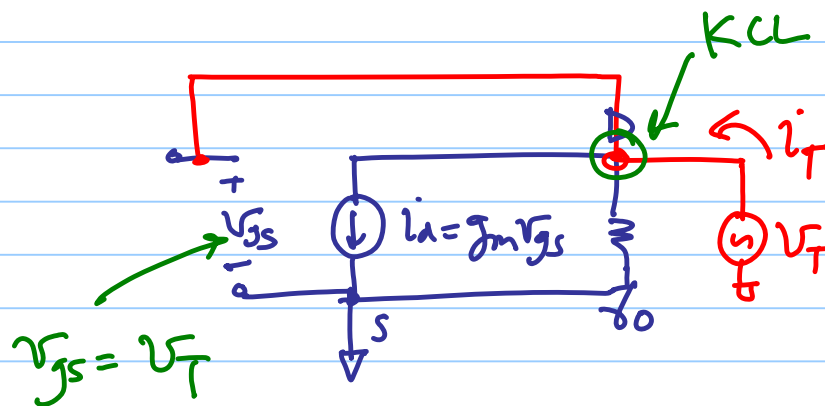

Find an expression
for i_T

KCL:

$$i_T - \overset{i_d}{g_m v_T} - \frac{v_T}{r_o} = 0$$

$$i_T = (g_m + \frac{1}{r_o}) v_T$$


$$\rightarrow Z_{out} = \frac{v_T}{i_T} = \frac{1}{g_m + \frac{1}{r_o}} = \frac{r_o}{1 + g_m r_o} = \frac{\frac{1}{g_m} \cdot r_o}{\frac{1}{g_m} + r_o}$$

$$= \frac{1}{g_m} \parallel r_o$$

$$\approx \frac{1}{g_m}$$

if $r_o \gg \frac{1}{g_m}$
Long channel MOSFET



Again
 $\lambda = 0$

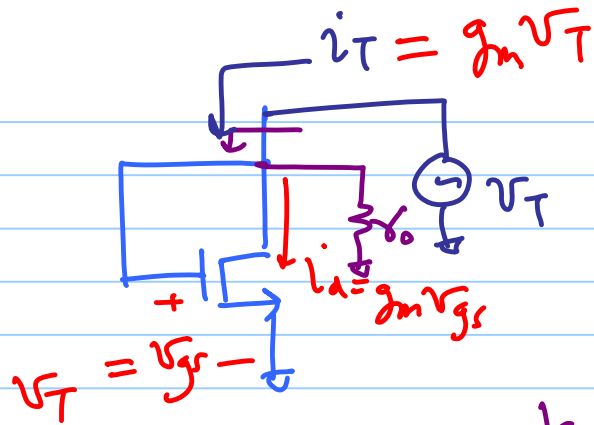

$$\frac{1}{g_m} \parallel r_o$$

$$i_T = g_m v_T$$
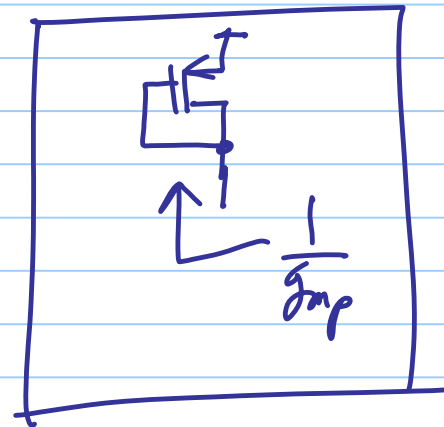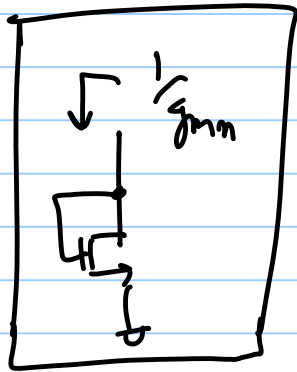
$$\Rightarrow Z_{out} = \frac{v_T}{i_T} = \frac{1}{g_m}$$



$$Z_{out} \rightarrow \frac{1}{g_m} \approx \boxed{\frac{1}{\beta V_{ov}}} \quad 5k\Omega$$

Deep Triode $\Rightarrow R_{ch} \approx \boxed{\frac{1}{\beta (V_{GS} - V_{THN})}} \quad \text{for } V_{DS} \ll V_{DS,sat}$

$\uparrow$
500 Ω

Table 9.1



low-Impedance


$$\frac{1}{g_m}$$







$$6.67k\Omega$$

r_o

$$5M\Omega$$

High-Impedance

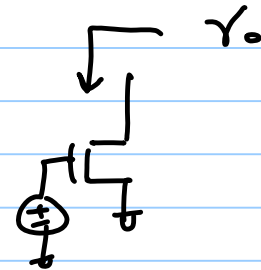

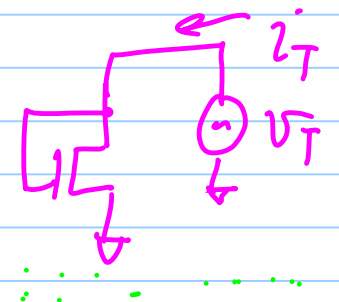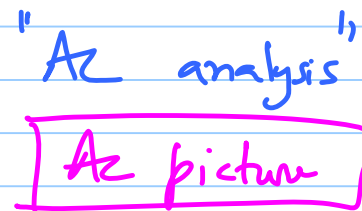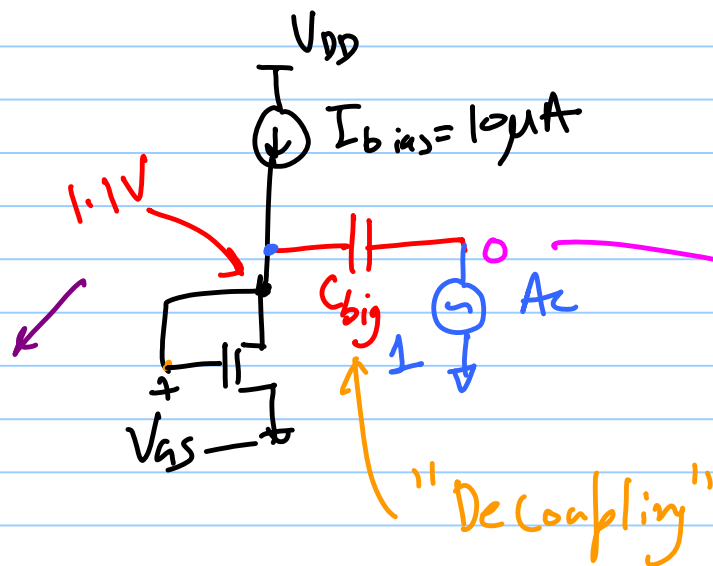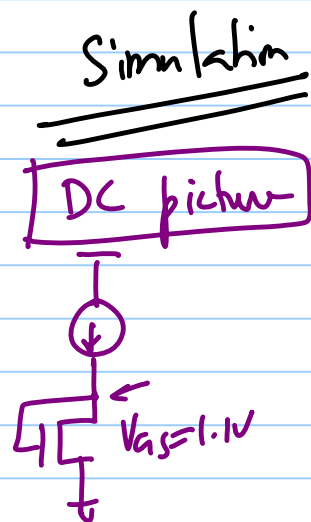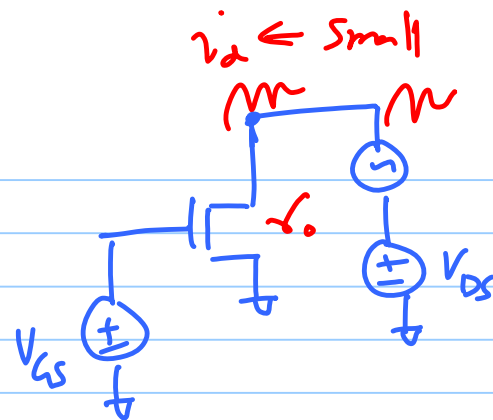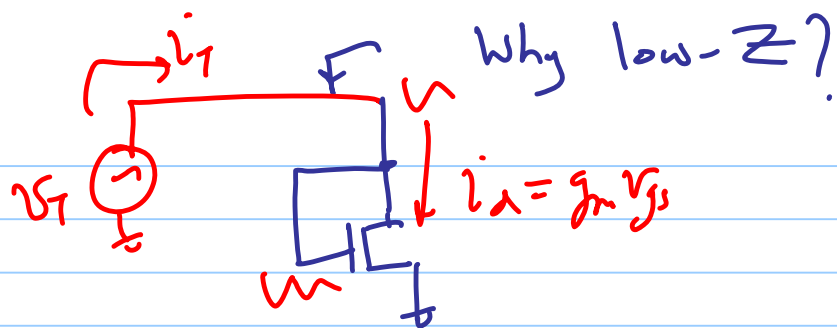

Small-Signal Analysis

"equivalent"
Circuit

① Given a circuit, draw the DC picture

→ short AC voltage sources
→ open AC current sources

Solve for DC operating point for all the devices.

② Use DC operating points from step ①, find
small-signal parameters (g_m , r_o , g_{m_b} , ...)

"Linearization Step"

③ Draw AC picture

↳ replace devices by small-signal models

↳ short all DC voltage sources

↳ open all DC current sources

Solve for AC values in the circuit

Final result $\Rightarrow$ Superposition of ② & ③

Ex 9.5 of CMOS book