

ECE 511 - Lecture 6

Note Title

2/6/2014



Current Mirrors:

Current sources

* are used widely in circuit design



* How to design stable current sources.

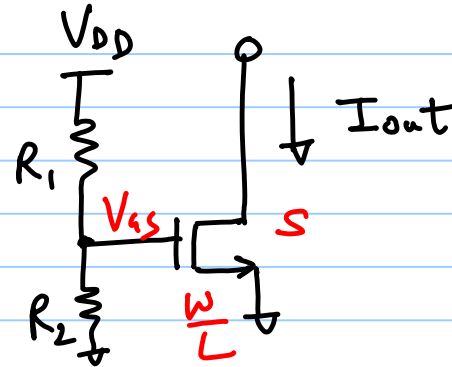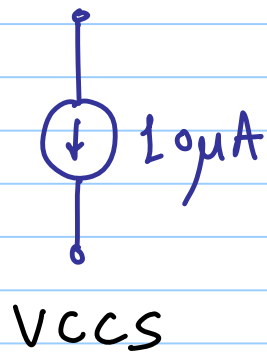

$$\lambda = 0$$

$$I_{out} = \frac{K_p n}{2} \frac{W}{L} \left(\underbrace{\frac{R_2}{R_1 + R_2} V_{DD}}_{V_{ov}} - \underbrace{V_{THN}}_{\checkmark} \right)^2$$

→ depends V_{DD} , process (V_{THN}), Temp

Temperature
Dependence

$$I_D = \frac{K_p}{2} \frac{W}{L} (V_{GS} - V_{THN})^2$$

$$\frac{\partial V_{THN}}{\partial T} \approx -\frac{k}{q} \ln\left(\frac{N_{D, poly}}{N_A}\right) \approx -1 \text{ mV}^\circ\text{C}$$


$$K_p(T) = K_p(T_0) \left(\frac{T}{T_0}\right)^{-3/2}$$

$$T \uparrow \Rightarrow V_{THN} \downarrow \quad \boxed{K_p \downarrow}$$

CMOS


Fig 9.29

9.30

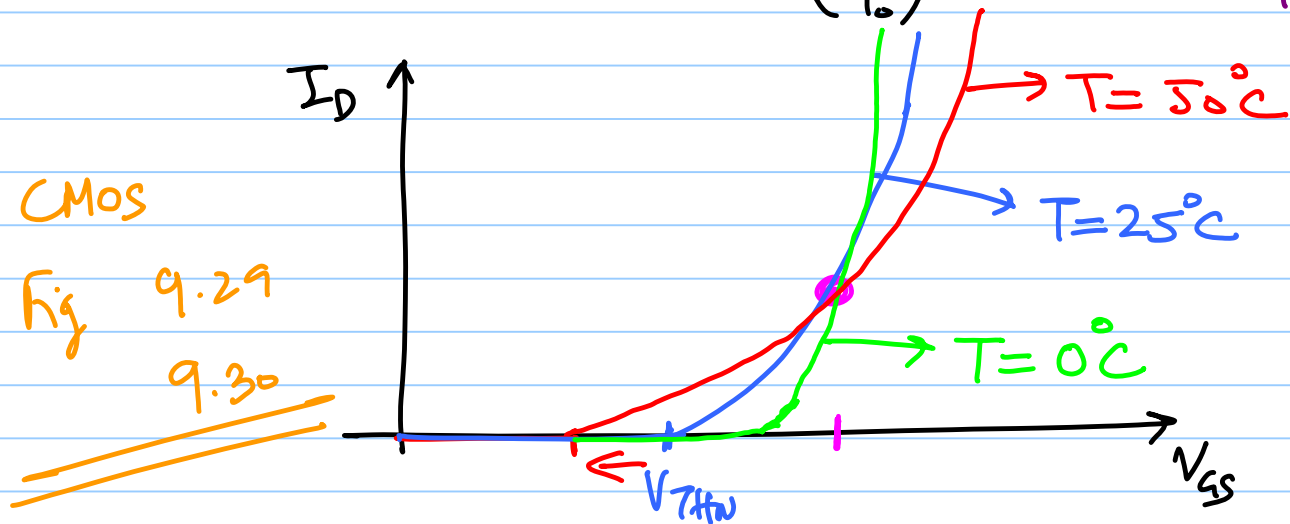


DC sweep over V_{GS}
parametric sweep
Temperature

Solⁿ

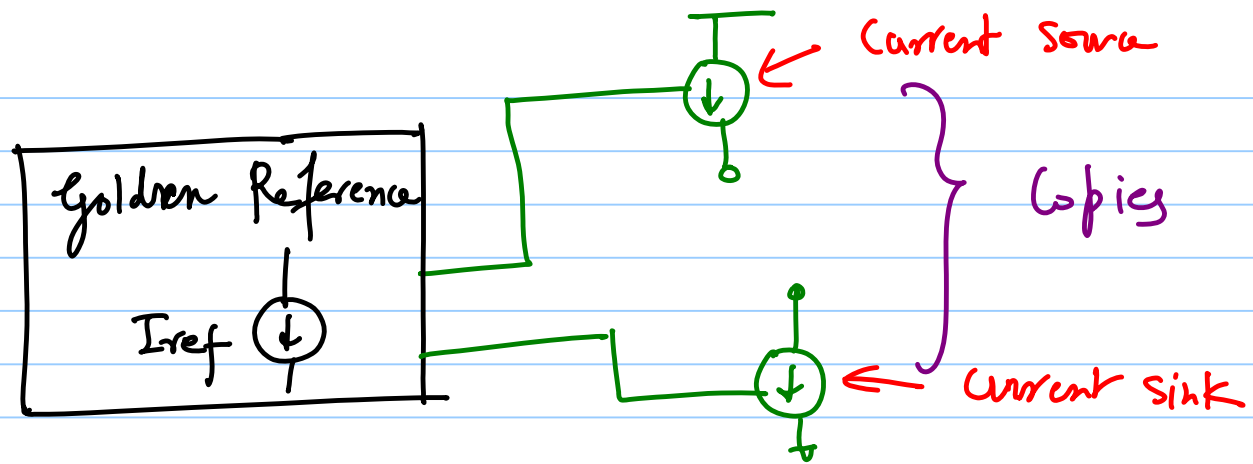

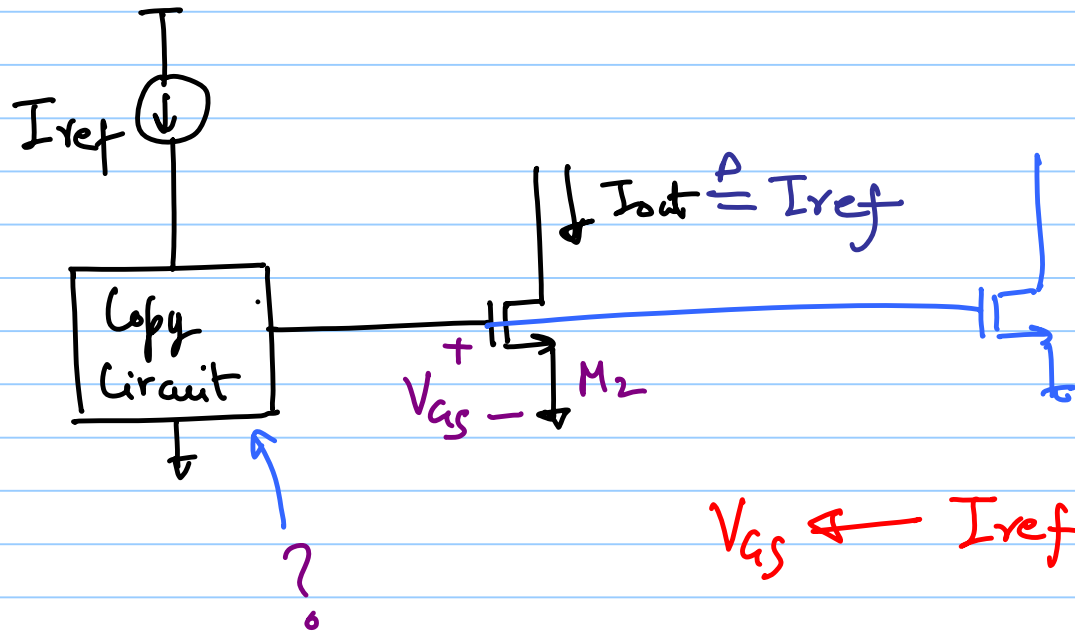
* How to generate copies of a reference current?



How to assure that
 $I_{out} = I_{ref}$?

$V_{GS} \leftarrow I_{ref}$

$\lambda = 0$

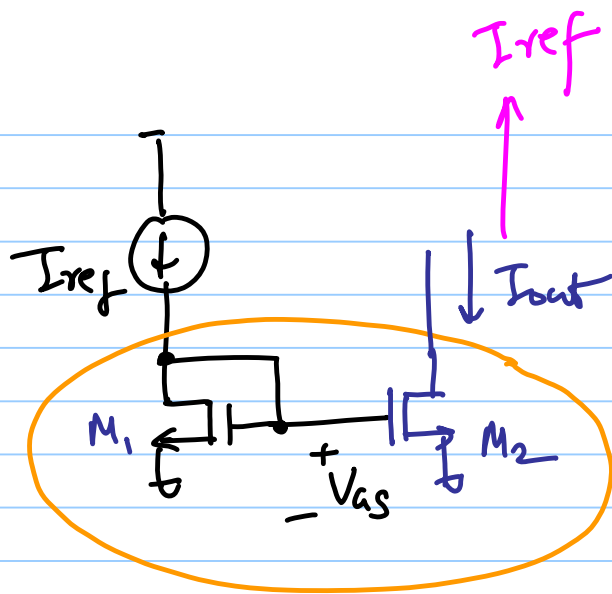

Current Mirror

$$I_{ref} = \frac{k_p}{2} \frac{W}{L} (V_{GS} - V_{THN})^2$$

$$I_{ref} = f(V_{GS})$$


$$\Rightarrow V_{GS} = f^{-1}(I_{ref}) \leftarrow \text{independent of } V_{DS}$$

$$I_{out} = f(V_{GS})$$

$$= f(f^{-1}(I_{ref}))$$

$$= I_{ref}, \text{ assuming } \lambda = 0$$



$$\boxed{\lambda = 0}$$

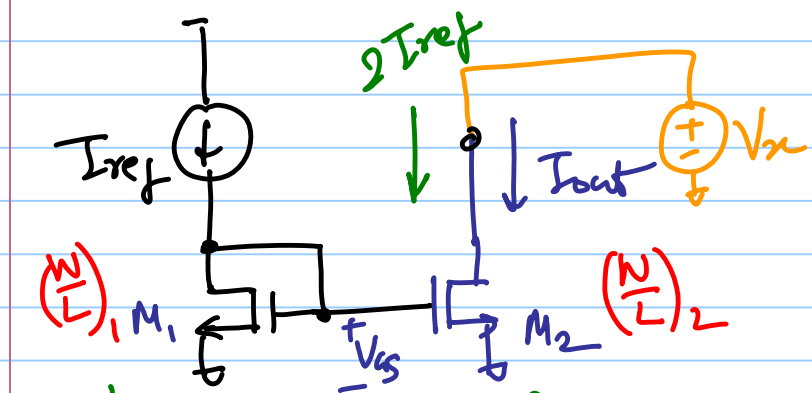

$$I_{ref} = \frac{1}{2} k p_n \left(\frac{W}{L} \right)_1 (V_{gs} - V_{thn})^2$$

$$I_{out} = \frac{1}{2} k p_n \left(\frac{W}{L} \right)_2 (V_{gs} - V_{thn})^2$$

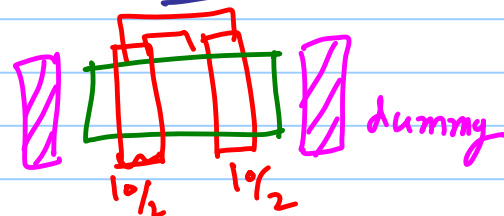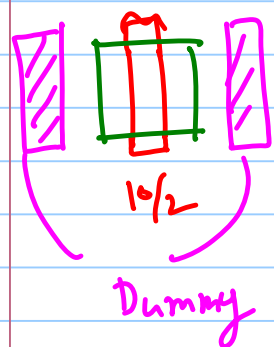
$$\frac{I_{out}}{I_{ref}} = \frac{(W/L)_2}{(W/L)_1} = \frac{W_2}{W_1}$$





$$\text{Let } L_1 = L_2$$



* precisely copy and scale currents by W ratio

$$\lambda = 0$$

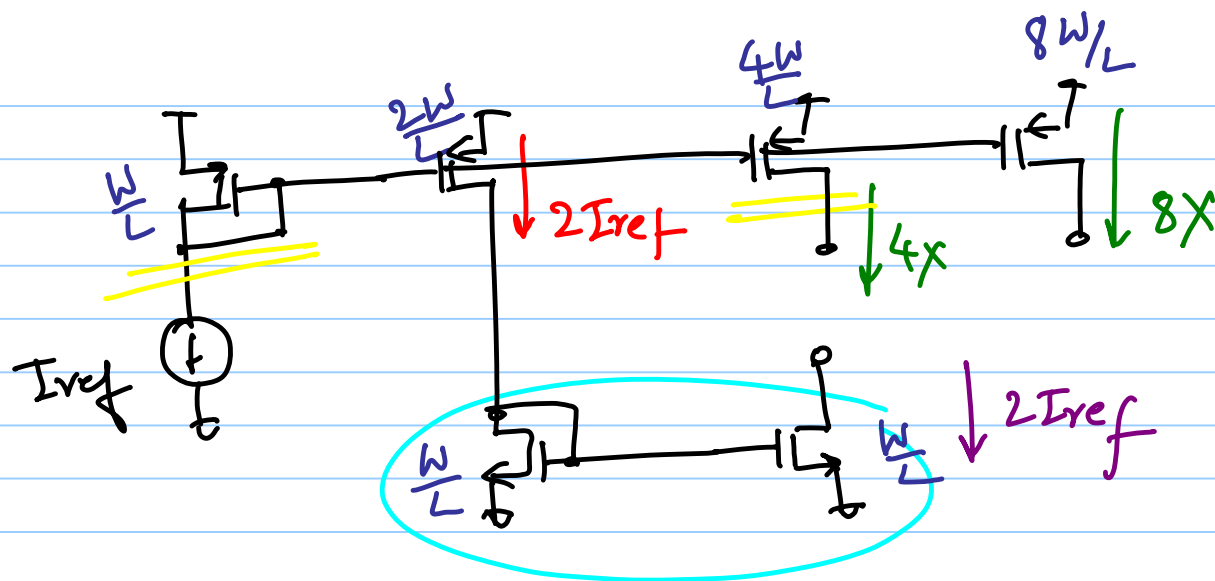


* Now, what happens with $\lambda > 0$

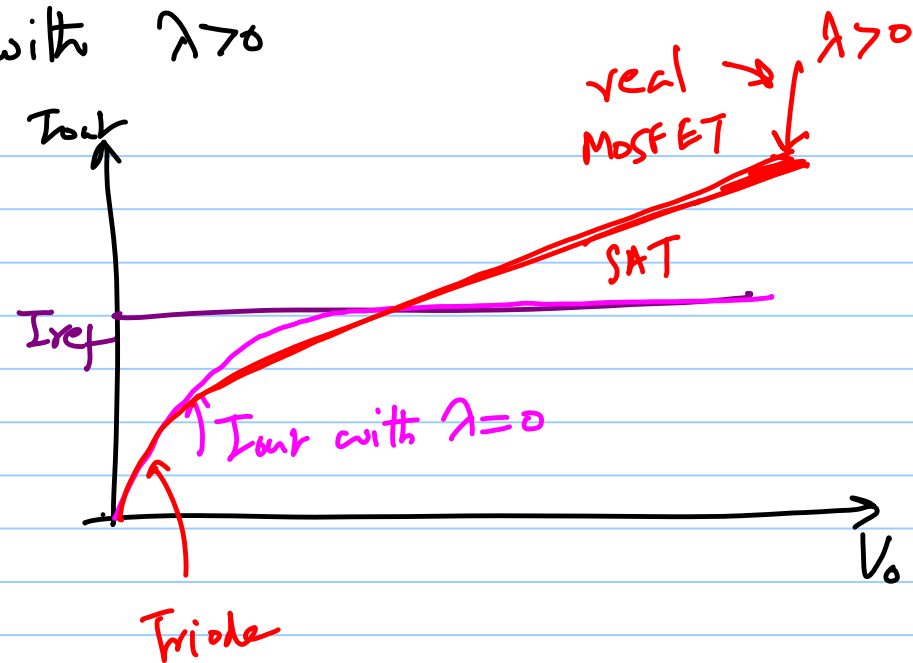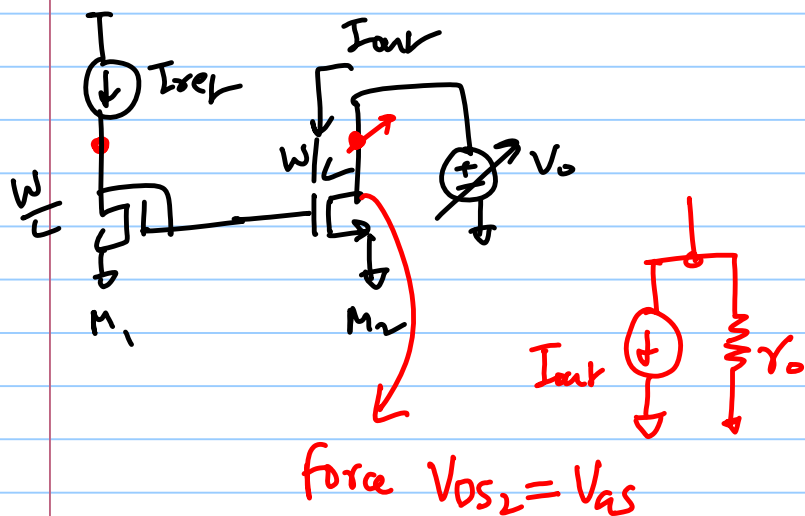

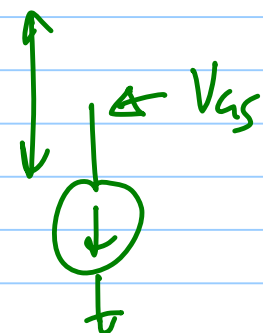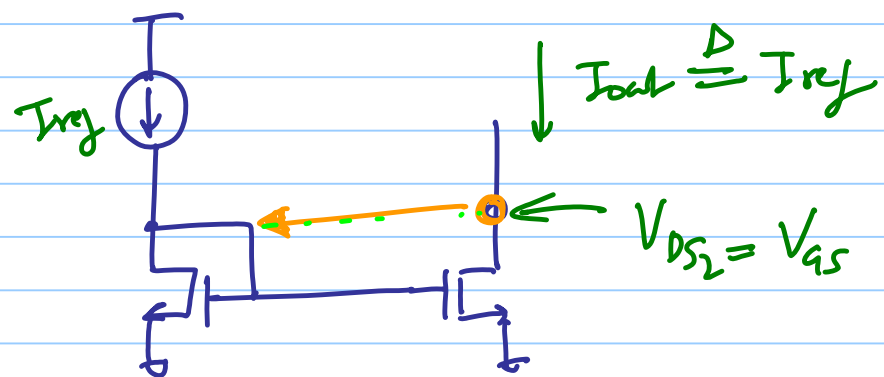

$$\lambda = 0$$

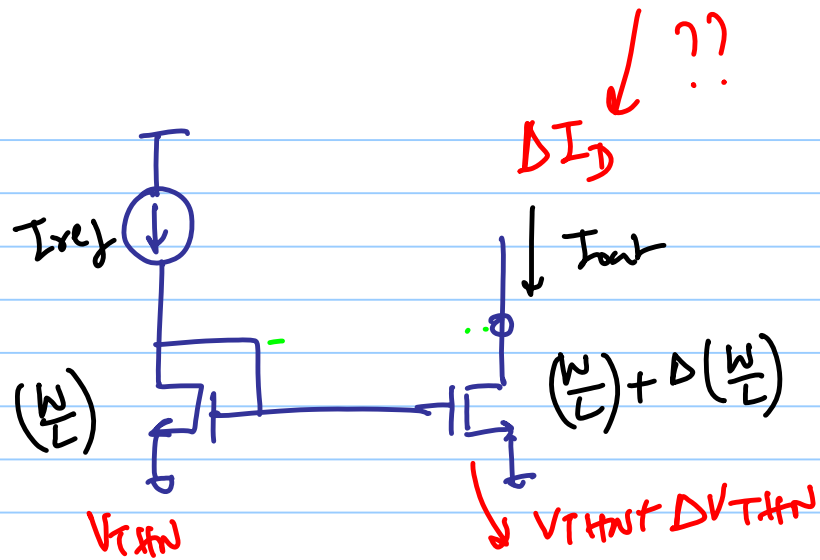

$$y = f(x_1, x_2, \dots)$$

$$\Delta y = \underbrace{\frac{\partial f}{\partial x_1}}_{\text{Sensitivity}} \Delta x_1 + \underbrace{\frac{\partial f}{\partial x_2}}_{\text{Sensitivity}} \Delta x_2 + \dots$$

$$I_D = \frac{k_p n}{2} \left(\frac{W}{L}\right) (V_{GS} - V_{THN})^2$$

$$\Delta I_D = \frac{\partial I_D}{\partial (W/L)} \cdot \Delta \left(\frac{W}{L} \right) + \frac{\partial I_D}{\partial (V_{GS} - V_{THN})} \cdot \Delta (V_{GS} - V_{THN})$$

$$\Delta I_D = \frac{K_p n}{2} (V_{GS} - V_{THN})^2 \cdot \Delta \left(\frac{W}{L} \right) - K_p n \frac{W}{L} (V_{GS} - V_{THN}) \Delta V_{THN}$$

% mismatch

$$\frac{\Delta I_D}{I_D} = \frac{\Delta (W/L)}{W/L} - 2 \frac{\Delta V_{THN}}{(V_{GS} - V_{THN})}$$

To minimize $\left(\frac{\Delta I_D}{I_D} \right)$

① Large V_{ov}

② Large W/L

gaussian


$$Y = X_1 \pm X_2$$




$$\sigma_Y = \sqrt{\sigma_{X_1}^2 + \sigma_{X_2}^2}$$

Monte-Carlo
Analysis

$$\sigma_{\Delta V_{THN}} = \frac{A_{V_{THN}}}{\sqrt{WL}}$$

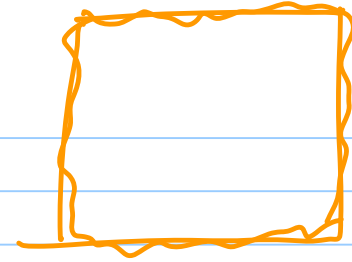
$$\sigma_{(DW/L)} \neq \frac{A_{WL}}{\sqrt{WL}}$$




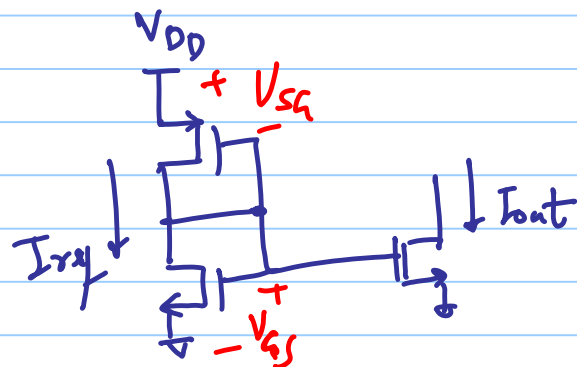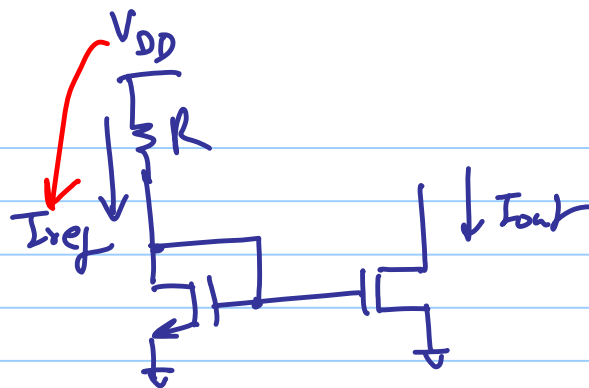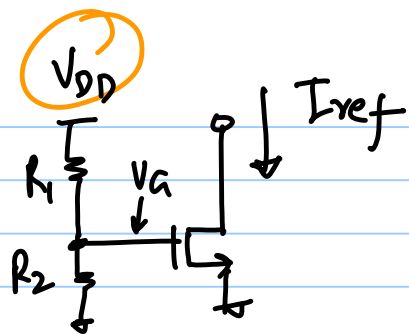

Supply Independent Biasing

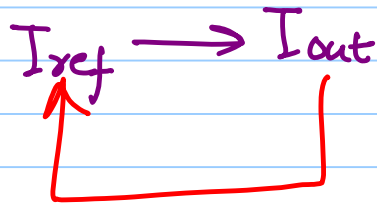
* In order to get rid of V_{DD} sensitivity, the circuit must bias itself!



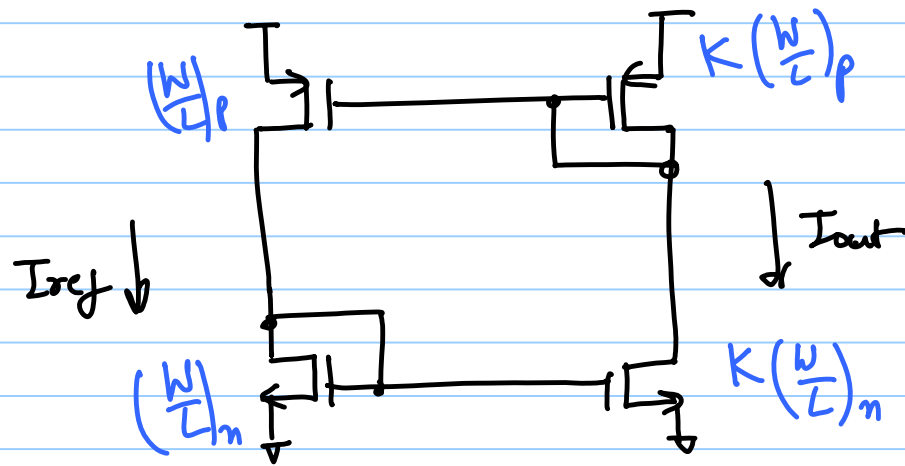

$$I_{out} = K \cdot I_{ref} \quad (\lambda = 0)$$

↓
both are indep of V_{DD} .

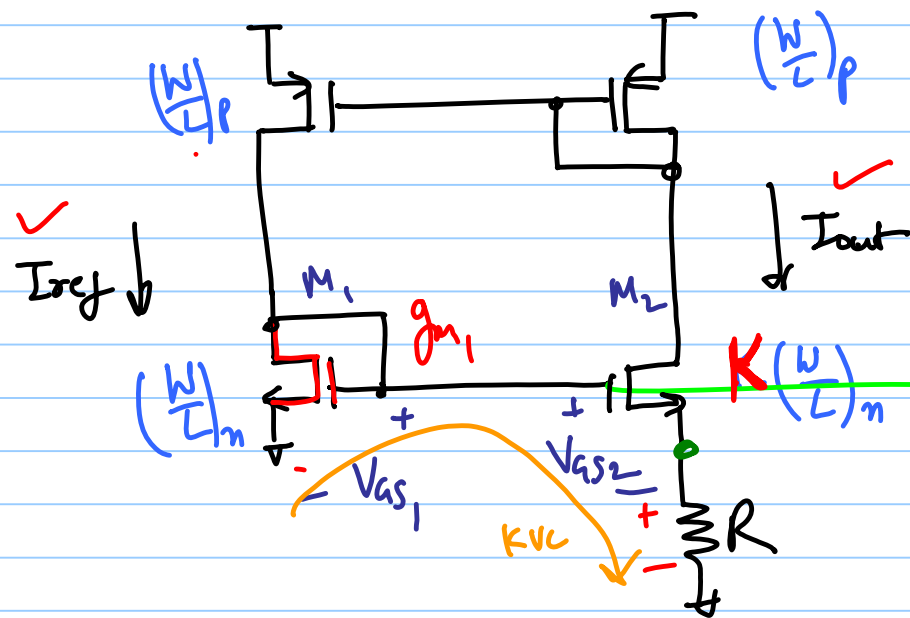

* Add a 'constant' to the circuit

* PMOS devices set

$$I_{out} = I_{ref} \quad (\lambda=0)$$

$$V_{GS1} = V_{GS2} + I_{out} \cdot R$$

$$\underline{I_{ref} = I_{out}}$$

$$\sqrt{\frac{2 I_{out}}{K \mu_n \left(\frac{W}{L}\right)_1}} + \cancel{V_{TH1}} = \sqrt{\frac{2 I_{out}}{K \mu_n \left(\frac{W}{L}\right)_1 K}} + \cancel{V_{TH2}} + I_{out} \cdot R$$

$\underbrace{\left(\frac{W}{L}\right)_1}_2$

* neglect body effect

$$\sqrt{\frac{2 I_{out}}{K \mu_n \left(\frac{W}{L}\right)}} \left(1 - \frac{1}{\sqrt{K}}\right) = I_{out} \cdot R$$

$$I_{out} = 0, \frac{2}{K\beta_n(\frac{W}{L})} \cdot \frac{1}{R_2} \left(1 - \frac{1}{\sqrt{K}}\right)^2$$

$$I_{out} = 0, \frac{2}{\beta_n R_2} \left(1 - \frac{1}{\sqrt{K}}\right)^2$$

* Beta Multiplier Circuit (BMR)

* Constant "g_m" bias Circuit

$$g_{m1} = \sqrt{2\beta I_{out}} = \frac{2}{R} \left(1 - \frac{1}{\sqrt{K}}\right) \leftarrow \text{independent of } V_{DD}$$

↑
Varies Temp