
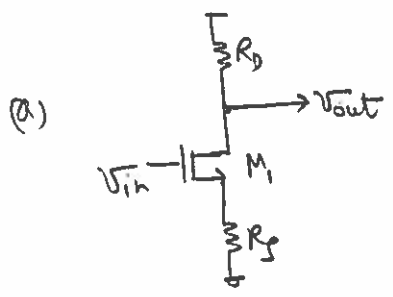


HW # 6


Problem 1:

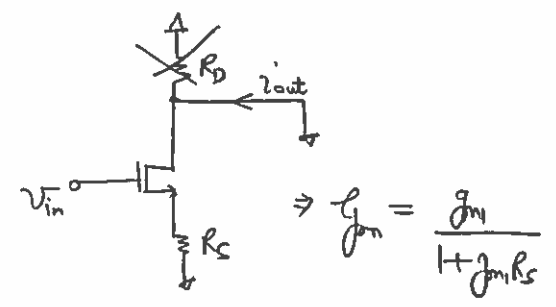

Find g_m




R_{out}

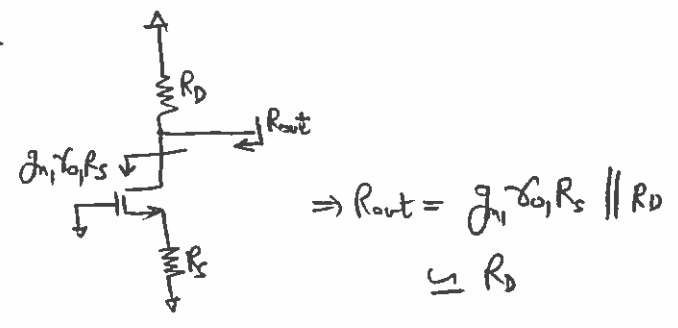


$$\Rightarrow A_v = -g_m R_{out} = \frac{-g_m R_D}{1 + g_m R_S}$$


(b)

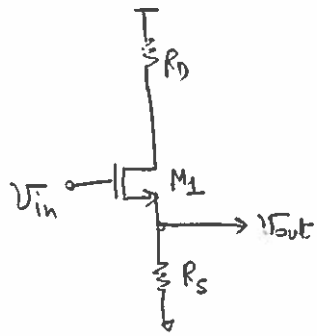

(i) Using $A_v = g_m R_{out}$ Method:

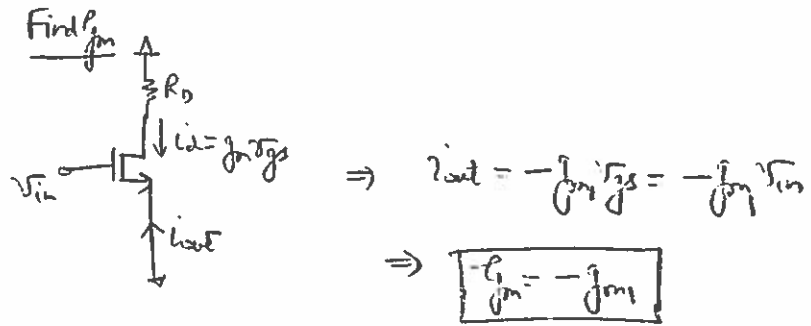

Find R_{out}

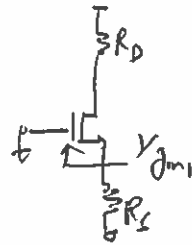


Assuming $R_D \ll r_o$, impedance looking up the source $\approx \frac{1}{g_m}$

$$\Rightarrow R_{out} = \frac{1}{g_m} \parallel R_S$$




$$\begin{aligned} \Rightarrow A_v &= -g_m R_{out} = +g_m \times \frac{1}{g_m} \parallel R_S \\ &= \frac{g_m \cdot \frac{1}{g_m} \cdot R_S}{\frac{1}{g_m} + R_S} = +\frac{R_S}{\frac{1}{g_m} + R_S} \end{aligned}$$

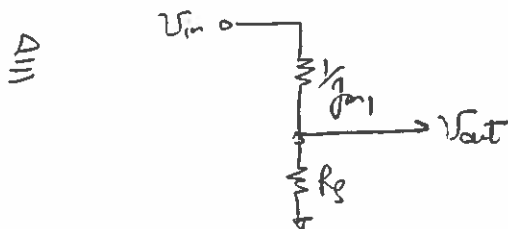* Also, it can be observed that V_{out} is resulting due to a voltage divider formed using $\frac{1}{g_m}$ & R_S



(c)

(3)

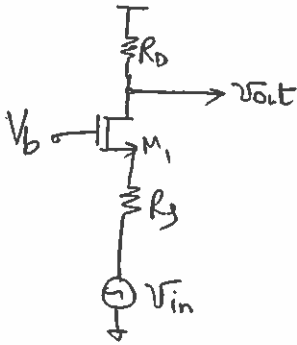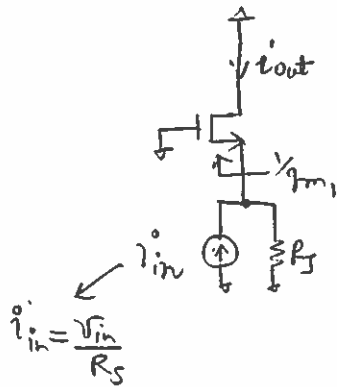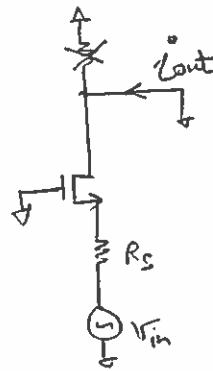
Find g_m :
 $\Rightarrow$ i_{in} divides between $\frac{1}{g_m}$ & R_S

$$\Rightarrow i_{out} = -i_{in} \times \frac{R_S}{\frac{1}{g_m} + R_S}$$

$$= - \frac{V_{in}}{R_S} \times \frac{R_S}{\frac{1}{g_m} + R_S}$$

$$= - V_{in} \times \frac{1}{\frac{1}{g_m} + R_S}$$

$$\Rightarrow \boxed{g_m = - \frac{1}{\frac{1}{g_m} + R_S}}$$

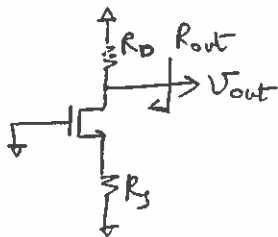Find R_{out} :



$$R_{out} = R_D \parallel (g_m v_{gs} \parallel R_S)$$

$$\approx R_D$$


$$\Rightarrow A_v = -g_m R_{out} = + \frac{R_D}{\frac{1}{g_m} + R_S} = + \frac{g_m R_D}{1 + g_m R_S}$$

cross check: for $R_S = 0$, $A_v = + g_m R_D$ ✓

(d)

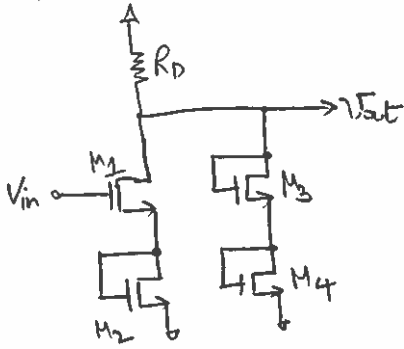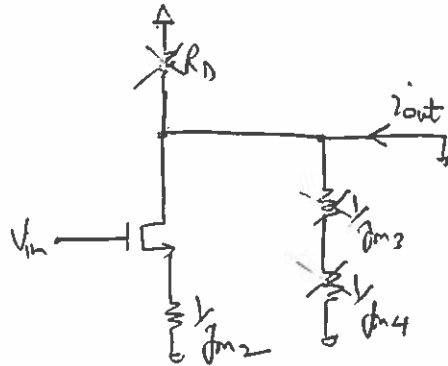Find τ_{gm} :

$$\Rightarrow \tau_{gm} = \frac{g_{m1}}{1 + g_{m1} \times \frac{1}{g_{m2}}} = \boxed{\frac{g_{m1} g_{m2}}{g_{m1} + g_{m2}}}$$

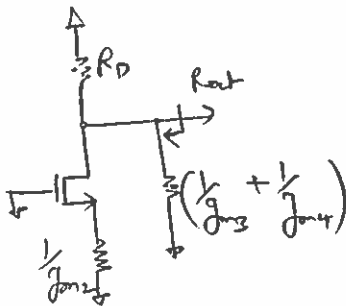Find R_{out} :


$$R_{out} = R_D \parallel \underbrace{\left(g_{m1} \times \frac{1}{g_{m2}} \right)}_{\text{large term}} \parallel \left(\frac{1}{g_{m3}} + \frac{1}{g_{m4}} \right)$$

$$\approx R_D \parallel \left(\frac{1}{g_{m3}} + \frac{1}{g_{m4}} \right) \approx \frac{1}{g_{m3}} + \frac{1}{g_{m4}}$$


$$\Rightarrow A_1 = -g_{m1} R_{out} \approx -\frac{g_{m1} g_{m2}}{(g_{m1} + g_{m2})} \times \left(\frac{1}{g_{m3}} + \frac{1}{g_{m4}} \right)$$

(e)

5

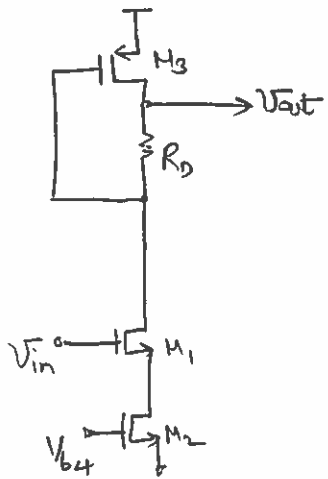

→

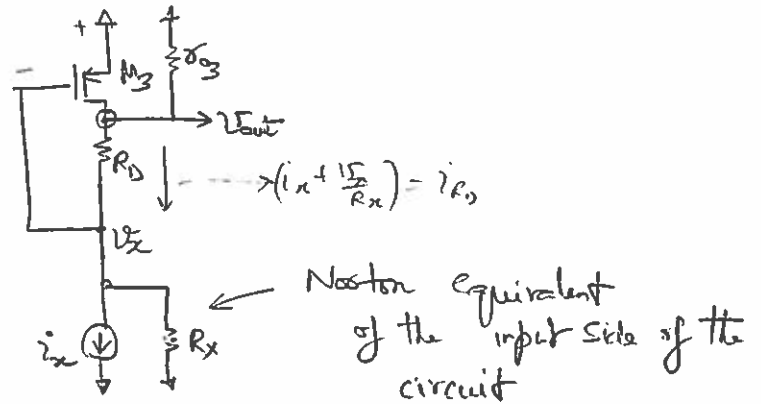

$$i_x = \frac{g_{m1} V_{in}}{1 + g_{m1} r_{o2}}, \quad R_x = g_{m1} r_{o1} r_{o2}$$

KCL @ V_x

$$V_x + \left(i_x + \frac{V_x}{R_x} \right) R_D = V_{out} \longrightarrow (1)$$

KCL @ V_{out}

$$\underbrace{\left(-g_{m3} V_x + \frac{V_{out}}{r_{o3}} \right)}_{\text{current due to } M_3} + \underbrace{\left(i_x + \frac{V_x}{R_x} \right)}_{i_{R_D}} = 0 \longrightarrow (2)$$

$$\text{Solve (2) for } V_x \Rightarrow V_x = - \frac{i_x + \frac{V_{out}}{r_{o3}}}{g_{m3} + \frac{1}{R_x}}$$



Substitute V_x in (1), and solve

$$\frac{V_{out}}{V_{in}} = \frac{\frac{g_{m1}}{1 + g_{m1} r_{o2}} (g_{m3} R_D - 1)}{\frac{1}{R_x} + g_{m3} + \frac{1}{r_{o3}} \left(1 + \frac{R_D}{R_x} \right)}$$

$$\approx \frac{g_{m1}}{1 + g_{m1} r_{o2}} \times \frac{(g_{m3} R_D - 1)}{g_{m3} + \frac{1}{r_{o3}}} \approx \underbrace{\frac{g_{m1}}{1 + g_{m1} r_{o2}} \times \frac{(g_{m3} R_D - 1)}{g_{m3}}}_{\text{Ans.}}$$

(f)

⑤

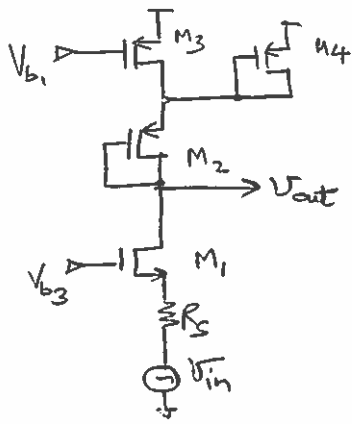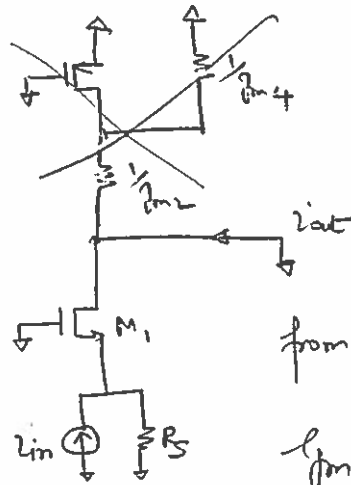Find g_m :

from part (c)

$$g_m = \frac{-1}{\frac{1}{g_{m1}} + R_S}$$

Find R_{out} :

$$R_{out} = g_{m1} r_{o1} R_S$$

$$R_{up} = (r_{o3} \parallel \frac{1}{g_{m4}}) + \frac{1}{g_{m2}}$$

$$\approx \frac{1}{g_{m2}} + \frac{1}{g_{m4}}$$

$$\Rightarrow R_{out} = (g_{m1} r_{o1}) R_S \parallel \left(\frac{1}{g_{m2}} + \frac{1}{g_{m4}} \right)$$

$$= \frac{1}{g_{m2}} + \frac{1}{g_{m4}}$$

$$\Rightarrow A_v = -g_{m1} R_{out}$$



$$= + \frac{g_{m1}}{1 + g_{m1} R_S} \times \left(\frac{1}{g_{m2}} + \frac{1}{g_{m4}} \right)$$

Ans.

Common-Gate Topology

Find g_m


(g)

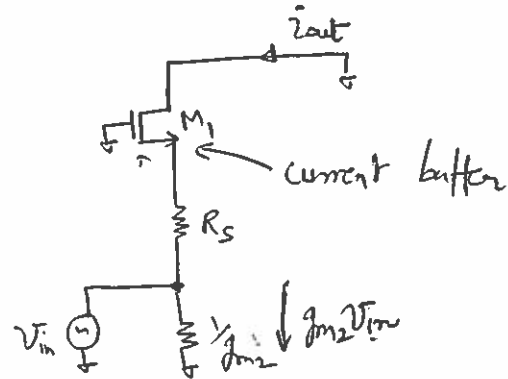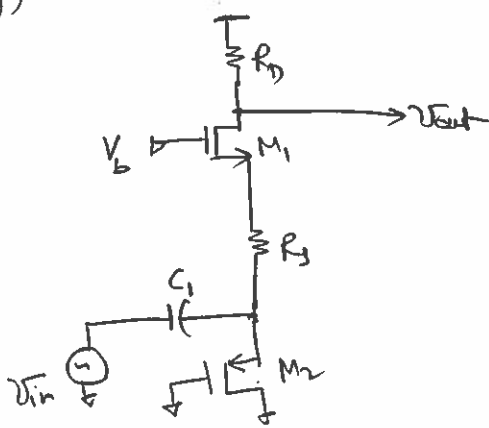

$$\Rightarrow i_{out} = g_{m2} V_{in}$$

$$\Rightarrow g_m = g_{m2}$$

Find R_{out} :

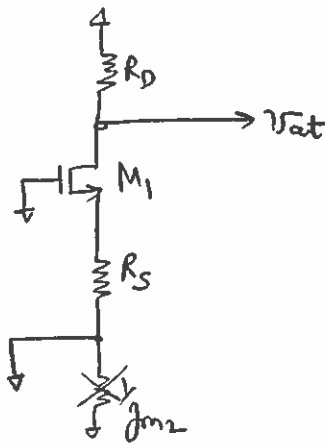


$$\Rightarrow R_{out} = R_D \parallel (g_{m1} r_{o1} R_S)$$

$$\approx R_D$$

$$\Rightarrow A_v = -g_m R_{out} \approx -g_{m2} R_D$$

(h) find $\underline{g_m}$:

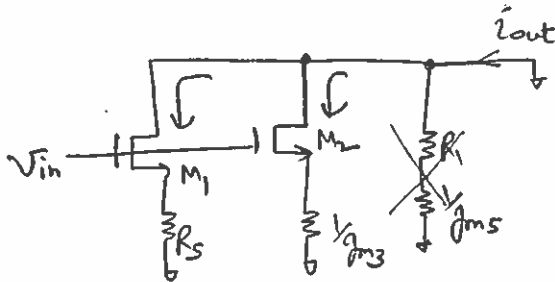

$$\Rightarrow i_{out} = \left(\frac{g_{m1}}{1 + g_{m1}R_S} + \frac{g_{m2}}{1 + \frac{g_{m2}}{g_{m3}}} \right) V_{in}$$

$$\Rightarrow \underline{g_m} = \frac{g_{m1}}{1 + g_{m1}R_S} + \frac{g_{m2}g_{m3}}{g_{m2} + g_{m3}}$$

find R_{out} :

$$R_{up} = g_{m4} v_{o4} R_D$$

$$R_{down} = \underbrace{(g_{m1} v_{o1} R_S)}_{\text{Large}} \parallel \underbrace{(g_{m2} v_{o2} \cdot \frac{1}{g_{m3}})}_{\text{Large}} \parallel (R_1 + \frac{1}{g_{m5}})$$

$$\approx R_1 + \frac{1}{g_{m5}}$$

$\Rightarrow$

$$A_v = -\underline{g_m} R_{out} \approx - \left[\frac{g_{m1}}{1 + g_{m1}R_S} + \frac{g_{m2}g_{m3}}{g_{m2} + g_{m3}} \right] \left(R_1 + \frac{1}{g_{m5}} \right)$$


Ans.

Problem 2

9

$$kP_n = 50 \frac{\mu A}{V^2}$$

$$V_{thn} = 0.7V$$

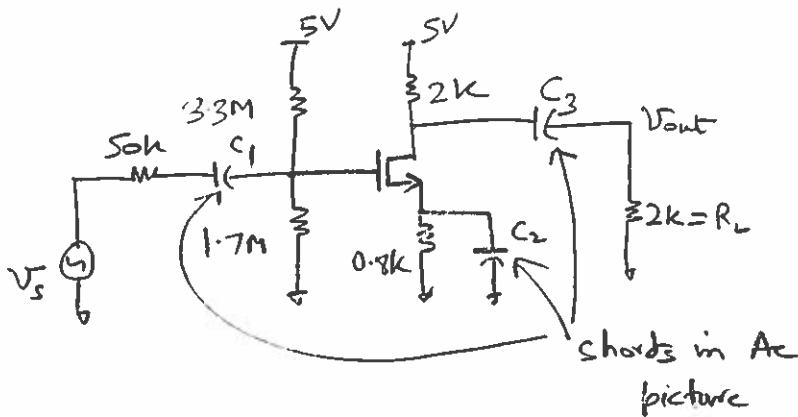


(a) DC picture

Given $I_D = 1mA$

$$\Rightarrow V_{GS} = 1.7 - 1mA \times 0.8k$$

$$\boxed{V_{GS} = 0.9V}$$

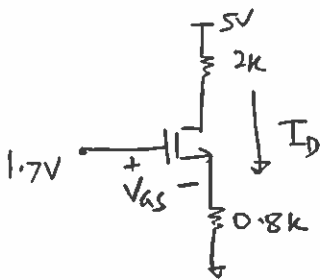

$$\Rightarrow I_D = 1mA = \frac{kP_n}{2} \left(\frac{W}{L}\right) (V_{GS} - 0.7)^2$$

$$\Rightarrow \left(\frac{W}{L}\right) = \frac{1mA \times 2}{50 \frac{\mu A}{V^2}} \times \frac{1}{(0.2)^2}$$

$$= \frac{4}{(0.4)^2} = 100$$

$$\Rightarrow \boxed{\frac{W}{L} = 100}$$


$$V_{DS} = 5 - (2k + 0.8k) 1mA$$

$$= 5 - 2.8$$

$$\Rightarrow \boxed{V_{DS} = 2.2V}$$

Az picture

(10)

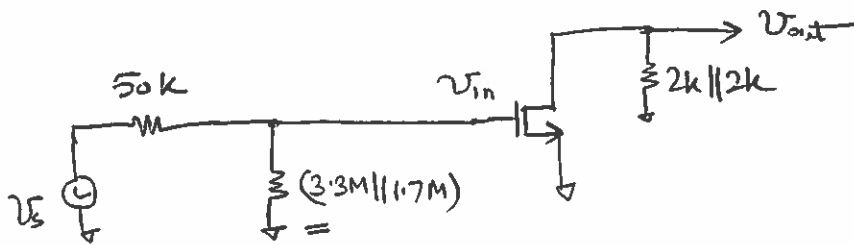

$$g_m = \sqrt{2\beta I_D} = \frac{2I_D}{V_{ov}}$$

$$= \frac{2 \times 1\text{mA}}{0.2\text{V}}$$

$$g_m = 10 \frac{\text{mA}}{\text{V}}$$

(b)

$$\frac{V_{out}}{V_{in}} = -g_m (r_o || R_D || R_L) = -g_m \times 1\text{k}$$


$$= -10 \frac{\text{mA}}{\text{V}} \times 1\text{k}\Omega$$

$$= -10$$

$$\Rightarrow \frac{V_{out}}{V_s} = -\frac{1 \cdot 122\text{M}}{50\text{k} + 1.122\text{M}} \times 10$$

$$A_v = -9.573$$


(c)

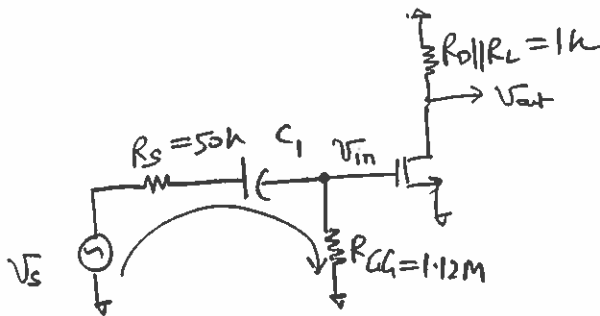

Make suitable
Approximations Here


$$\omega_{PL} = \frac{1}{(R_s + R_{G1}) C_1} \leq \frac{\omega_{in}}{10} = 10$$
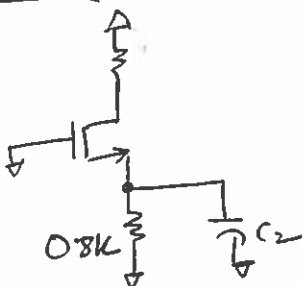
$$\Rightarrow C_1 \geq \frac{1}{10 \times (50\text{k} + 1.122\text{M})} = 8.53 \times 10^{-8} \text{F} = 85.3 \text{nF}$$



$$\frac{1}{0.8\text{k} C_2} \leq 10$$

$$\Rightarrow C_2 \geq 125 \mu\text{F}$$

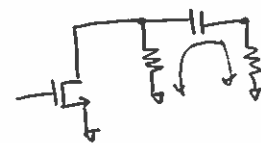


$$\frac{1}{(2\text{k} + 2\text{k}) C_3} \leq 10$$

$$\Rightarrow C_3 \geq 25 \mu\text{F}$$

Problem 3

(a) DC picture:
5V

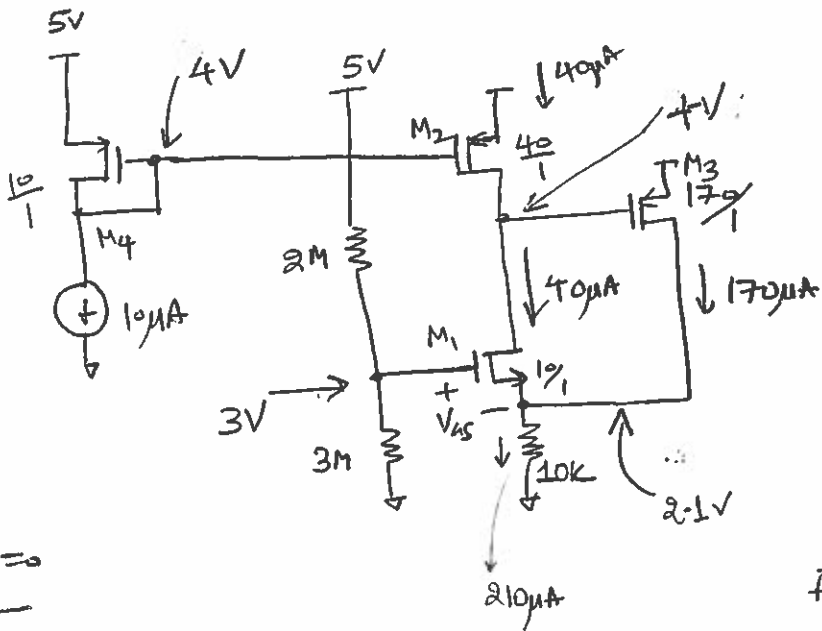

Here $\lambda = 0$


$$\Rightarrow V_{AS} = 3 - 2.1V = \boxed{0.9V}$$

$$\Rightarrow V_{DS} = 4.0V - 2.1V$$

$$K_{P_n} = 2.150 \frac{\mu A}{V_2}, V_{TN} = 0.7$$
$$k_{rp} = 50 \frac{\mu A}{V^2}, \quad V_{T+P} = 0.8$$

$$\begin{aligned} \text{for } M_1: I_D &= 40 \mu A, \left(\frac{W}{L}\right) = 10 \\ \Rightarrow V_{GS1} &= \sqrt{\frac{2I_D}{\beta}} + V_{THn} \\ &= 0.9V \end{aligned}$$

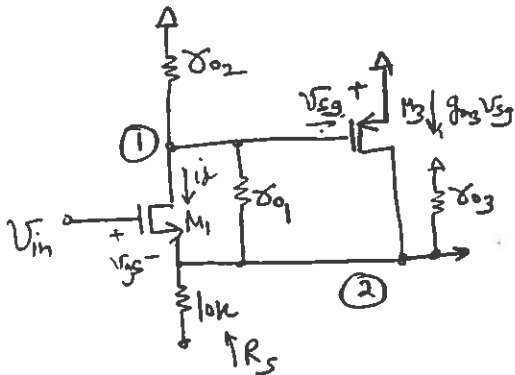Feedback stabilizes gate of M_3 at 4V such that it sinks $170\mu A$ to set $40\mu A$ in M_1



$$\frac{v_1}{\gamma_{01}} + \frac{(v_1 - v_2)}{\gamma_{01}} + g_{m1}(v_{in} - v_2) = 0$$

$$\frac{V_1}{\gamma_{o1} \parallel \gamma_{o2}} - V_2 \left(g_{m1} + \frac{1}{\gamma_{o1}} \right) = -g_{m1} V_{in} \rightarrow (1)$$

$$\frac{V_2}{R_2} + \frac{V_2}{R_3} + \frac{(V_2 - V_1)}{R_1} - g_{m3} V_2 - g_{m1} (V_{in} - V_2) = 0$$

$$\Rightarrow \frac{v_2}{\tau_{02} || R_5 || r_{o1}} - g_{m1} v_2 + \left(g_{m3} - \frac{1}{r_{o1}} \right) v_1 = g_{m1} v_{in} \rightarrow (2)$$

$$v_1 = v_2 \left(g_{m1} + \frac{1}{r_{o1}} \right) r_{o1} \parallel r_{o2} - g_{m1} r_{o1} \parallel r_{o2} \cdot v_{in}$$

plug into ②

$$v_2 \left[\frac{1}{r_{o1} \parallel r_{o3} \parallel R_S} - g_{m2} \right] + (g_{m3} - \frac{1}{r_{o1}}) \left[\left(g_{m1} + \frac{1}{r_{o1}} \right) r_{o1} \parallel r_{o2} - g_{m1} r_{o1} \parallel r_{o2} \right] v_{in} = g_{m1} v_{in}$$

$$\Rightarrow v_2 \left[\frac{1}{r_{o1} \parallel r_{o3} \parallel R_S} - g_{m2} + (g_{m3} - \frac{1}{r_{o1}}) \left(g_{m1} + \frac{1}{r_{o1}} \right) r_{o1} \parallel r_{o2} \right] = \left[g_{m1} + g_{m1} r_{o1} \parallel r_{o2} \left(g_{m3} - \frac{1}{r_{o1}} \right) \right] v_{in}$$

$$\Rightarrow \frac{v_{out}}{v_{in}} = \frac{v_2}{v_{in}} = \frac{g_{m1} \left[1 + (g_{m3} - \frac{1}{r_{o1}}) r_{o1} \parallel r_{o2} \right]}{\left(\frac{1}{r_{o1} \parallel r_{o3} \parallel R_S} - g_{m2} \right) + (g_{m3} - \frac{1}{r_{o1}}) \left(g_{m1} + \frac{1}{r_{o1}} \right) r_{o1} \parallel r_{o2}} \longrightarrow \textcircled{3}$$

Calculations:

$$\left. \begin{array}{l} M_1: \quad g_{m1} = 0.4 \frac{\text{mA}}{\text{V}} \Rightarrow r_{o1} = 250 \text{ k}\Omega \\ M_2: \quad g_{m2} = 0.4 \frac{\text{mA}}{\text{V}} \Rightarrow r_{o2} = 250 \text{ k}\Omega \\ M_3: \quad g_{m3} = 1.7 \frac{\text{mA}}{\text{V}} \Rightarrow r_{o3} = 58.82 \text{ k}\Omega \end{array} \right\}$$

plug these values into ③