Homework 6

ECE 5/411 - CMOS Analog IC Design

Note:

1. Use Cadence schematic capture, layout and Spectre simulation tools, available on the AMS servers for the homework problems.

Problem 1: Assuming all transistors are in saturation, find expressions for small-signal voltage gain $(A_v = G_m R_{out})$, R_{in} and R_{out} for each of the circuits shown below. Use variables g_{m1} , r_{o1} , g_{m2} , r_{o2} , etc. Assume that $r_o = \infty$, unless you must have a finite value.



Figure 1

Problem 2: The NMOS in the figure below has $V_{THN} = 0.7V$, and $KP_n = 500\mu A/V^2$. The drain current in the device is 1mA.



- a) Determine the small signal gain from v_s to v_{out} .
- b) Determine the W/L for the device and the DC operating points V_{GS} and V_{DS} .
- c) The lowest frequency in v_s is $\omega_{in} = 100$ rad/s. Determine the minimum values of C_1 , C_2 and C_3 required so that the frequencies associated with their charging/discharging is at least 10 times smaller than ω_{in} .
- d) The supply voltage is changed to 5.5. Determine the small signal gain of the amplifier.

Problem 3: For the amplifier shown in the figure below:



Figure 3

 $V_{THN} = 0.7V$, and $KP_n = 200 \frac{\mu A}{V^2}$

 $V_{THP} = 0.8V$, and $KP_p = 50 \frac{\mu A}{V^2}$

$$\gamma = 0$$

- a) Determine the operating points of all the devices in the circuit. For this part, neglect channel length modulation $(\lambda = 0)$.
- b) All transistors in the circuit have finite r_o , such that for any transistor $g_m r_o = 100$. Draw the small signal equivalent circuit of the amplifier, and determine the small signal gain $\left(\frac{v_{out}}{v_{in}}\right)$. Also determine the input and output resistances of the amplifier (Perform low-frequency analysis only).