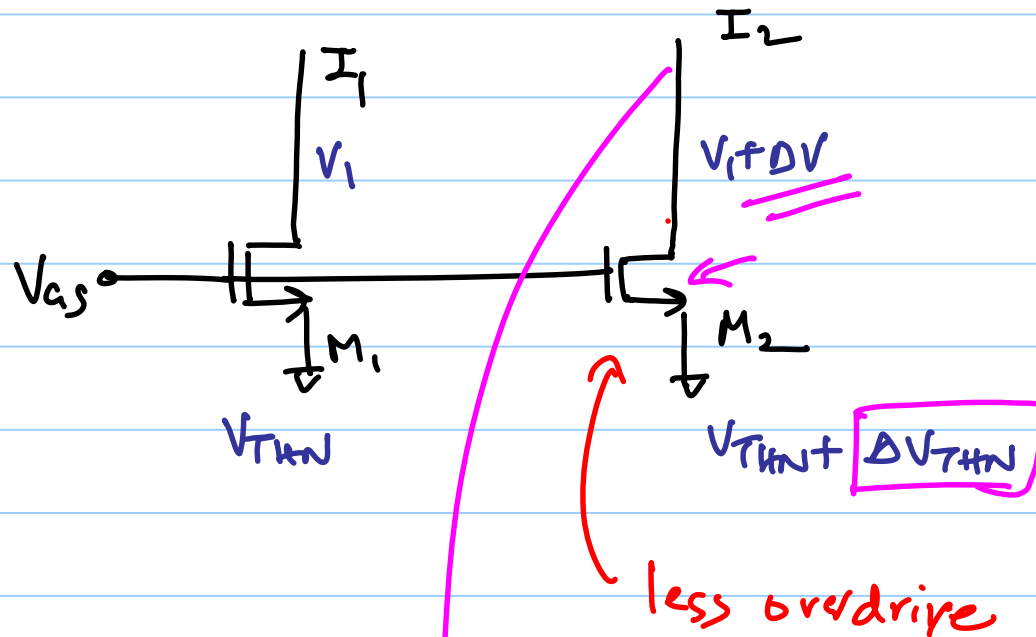


ECE 511 - Lecture 10

Note Title


2/17/2015



$$I_2 = I_1 + i_2$$


$$I_2 = I_1 - g_{m2} \Delta V_{thn} + \frac{\Delta V}{\gamma_{o2}}$$
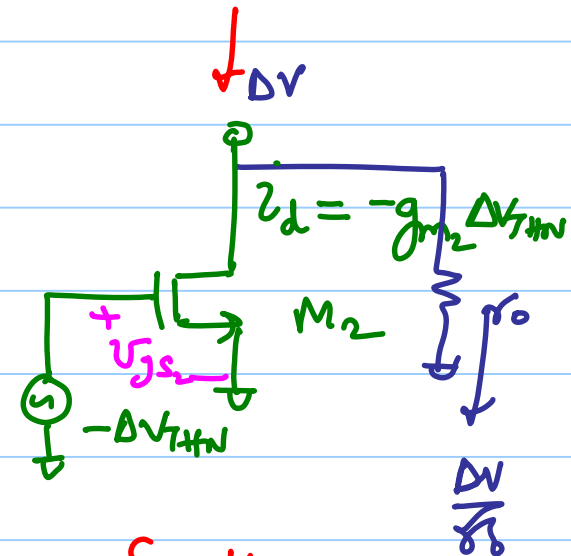
$$i_2 = g_{m2} \Delta V_{thn} + \frac{\Delta V}{\gamma_{o2}}$$



Small-signal picture for M_2

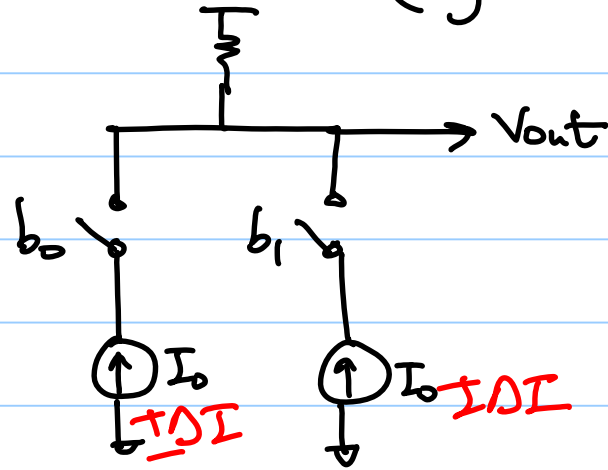2-level DAC (Digital to analog converter)



$$b_1, b_0 = 00 \Rightarrow I_{out} = 0$$

$$b_1, b_0 \Rightarrow 01 \Rightarrow I_0$$

$$b_1, b_0 \Rightarrow 11 \Rightarrow 2I_0$$


① Use large V_{ov}
to reduce mismatch




$$\Delta V_{THW}$$

② Use large Area


$$\Delta V_{DS}$$

$$\Delta \left(\frac{W}{L} \right)$$

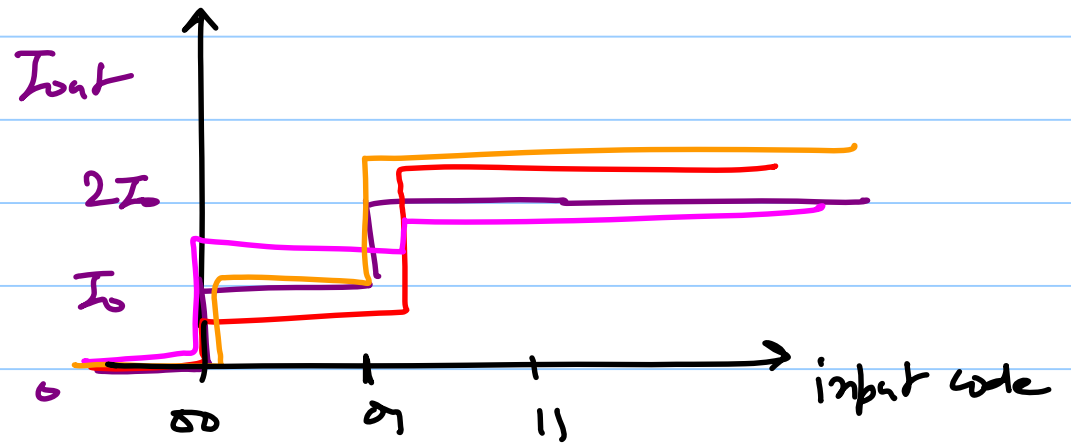

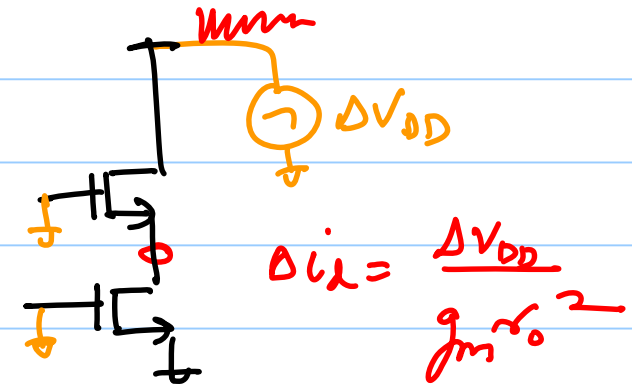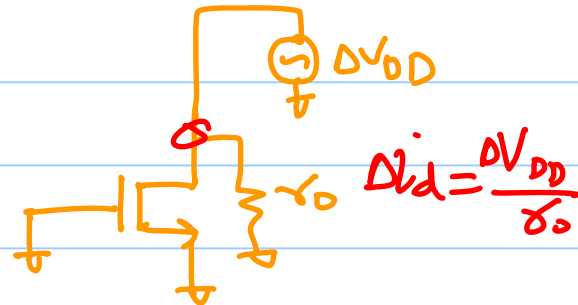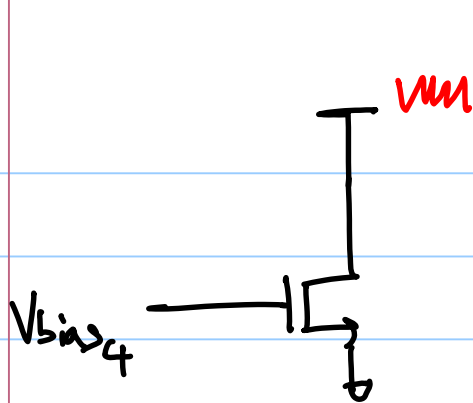

power supply insensitivity

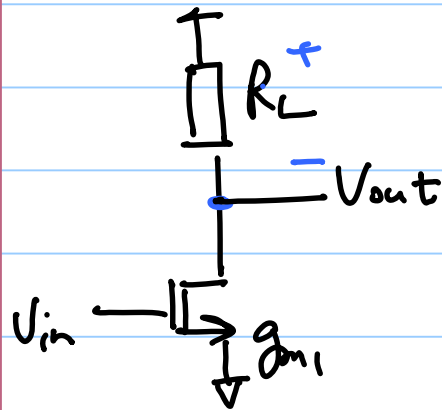


$$A_v = -g_{m1}(R_{o1} \parallel R_L)$$

$$A_v = -g_m R_D$$

$R_D \uparrow$

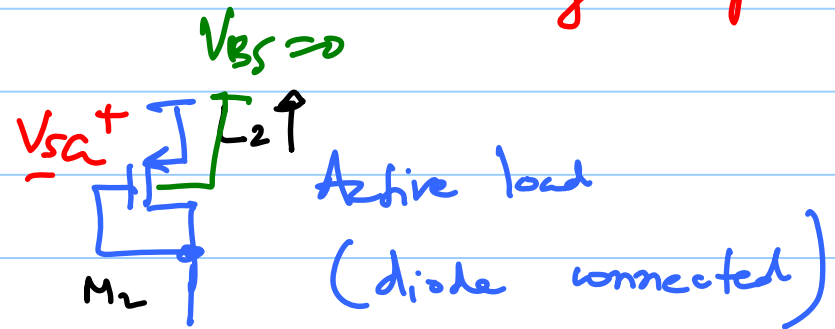We want to decouple the load resistance from the voltage drop across it.






(-) gain was less

$$A_v = -\sqrt{\frac{(W/L)_1}{(W/L)_2}}$$

need large devices to increase gain
 $\rightarrow$ more cap

* $L \uparrow \Rightarrow V_{GS} \uparrow \Rightarrow$ headroom issues.

Ex NMOS load
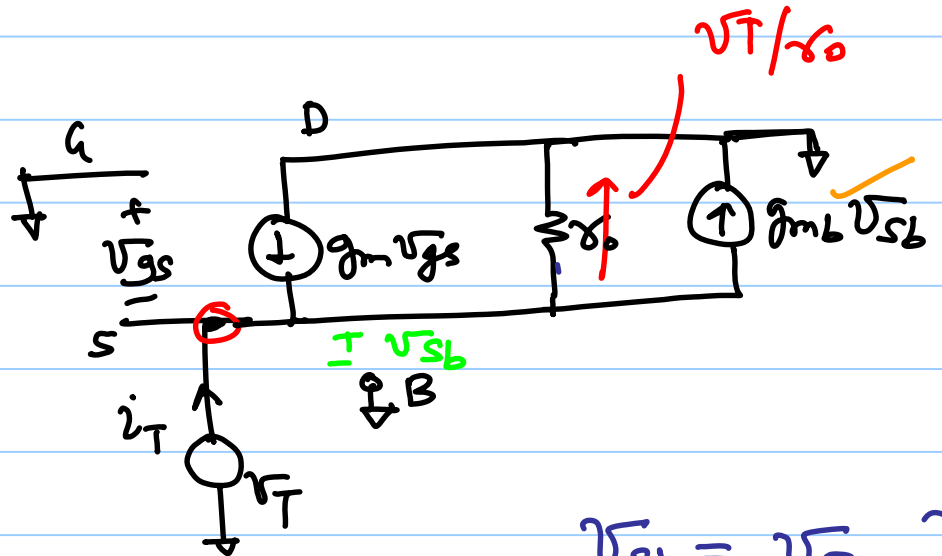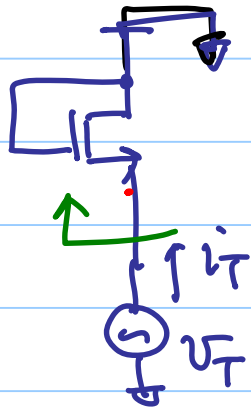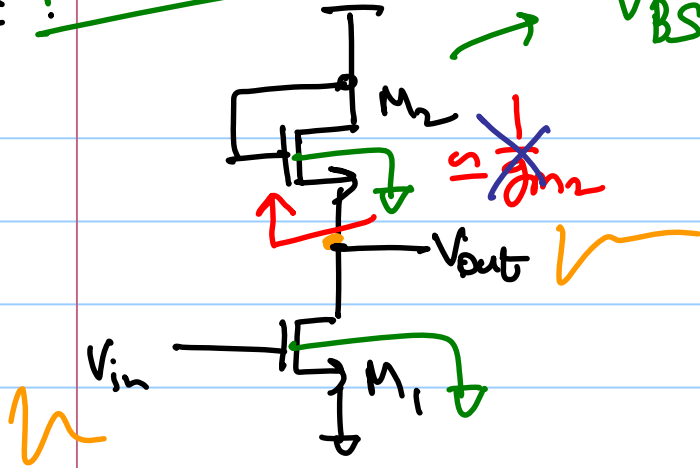
$$V_{BS} \neq 0$$


$$\left. \begin{aligned} v_{sb} &= v_T \\ v_{gs} &= -v_T \end{aligned} \right\}$$

$$g_{m_s} v_{gs} - g_{m_b} v_{sb} + i_T - \frac{v_T}{r_o} = 0$$

$$-(g_m + g_{mb})v_T + i_T - \frac{v_T}{r_o} = 0$$

$$v_T \left[(g_m + g_{m_b}) + \frac{1}{r_o} \right] = i_T$$

$$R_T = \frac{1}{g_m + g_{m_b} + r_o^{-1}}$$

Assume


$$g_m \gg \frac{1}{r_o}$$

$$\approx \frac{1}{g_m + g_{m_b}}$$

$$= \frac{1}{g_m(\eta + 1)}$$

$$g_{m_b} = \eta g_m$$

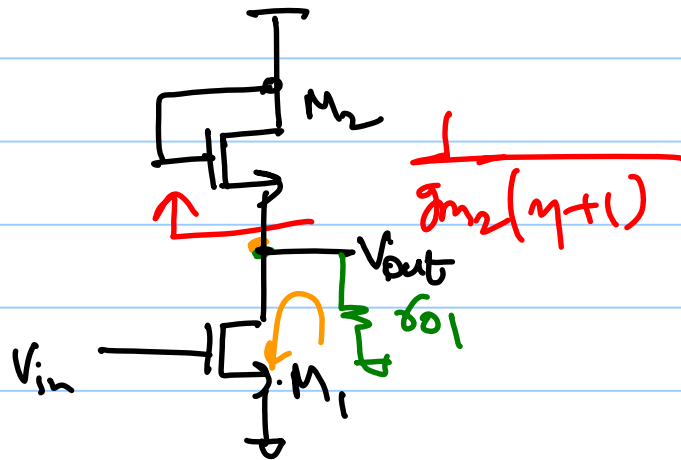impedance is actually lower
by $\frac{1}{(\eta + 1)}$





$$A_v = -g_{m1} \left[r_{o1} \parallel \frac{1}{g_{m2}(\eta+1)} \right]$$

$$\approx -\frac{g_{m1}}{g_{m2}(\eta+1)}$$

$$= \left(-\sqrt{\frac{(W/L)_1}{(W/L)_2}} \right) \frac{1}{\eta+1}$$



low gain

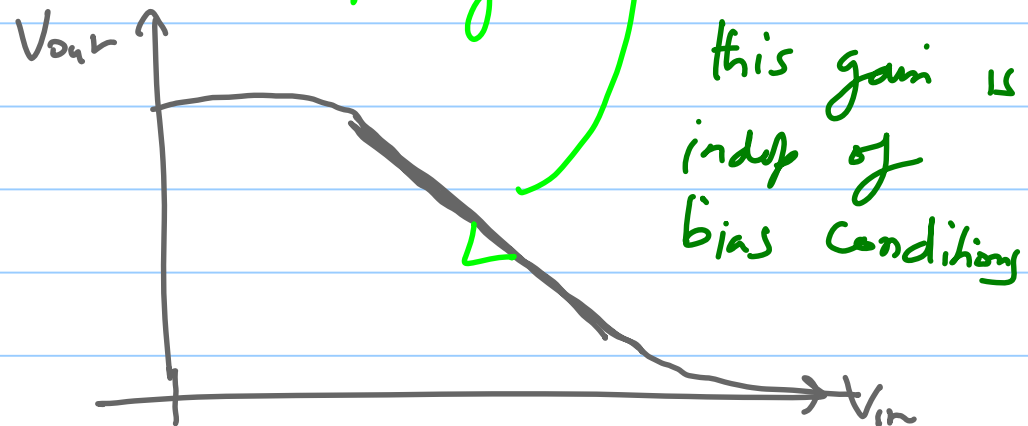

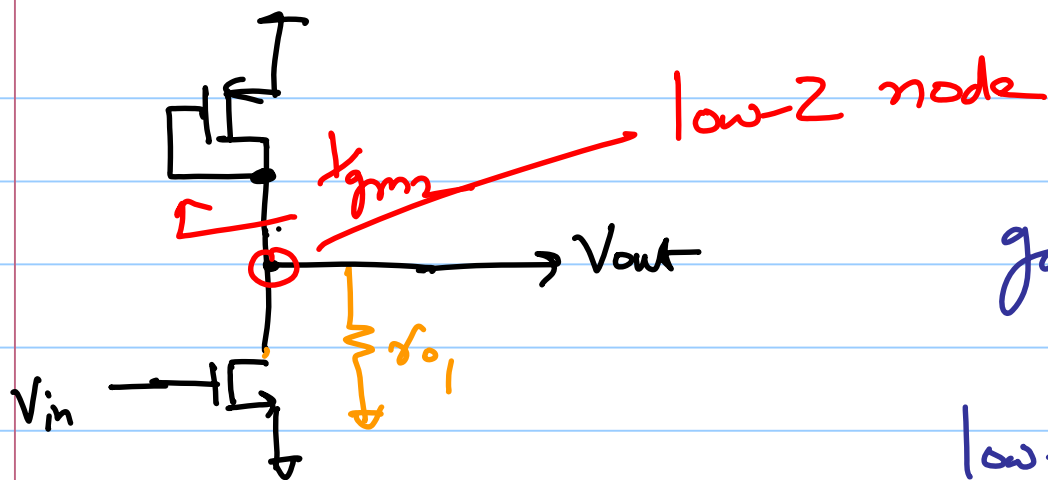


$$\text{gain} \approx g_m \cdot Z_{out}$$

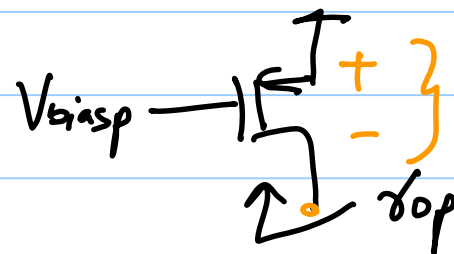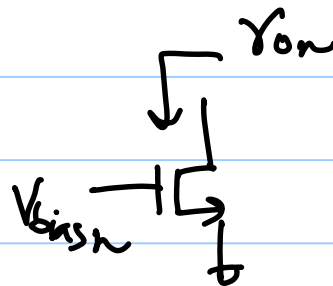low-impedance at the output
kills the gain







CS stage with current-source load

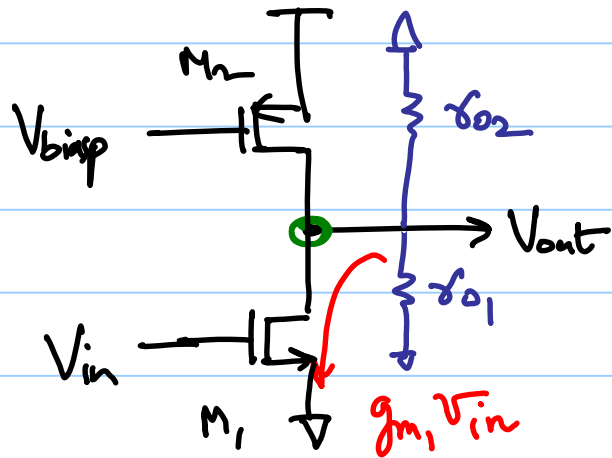


$$A_v = -g_{m1} (r_{o1} \parallel r_{o2})$$



$$\approx \frac{g_{m1} r_{o2}}{2}$$

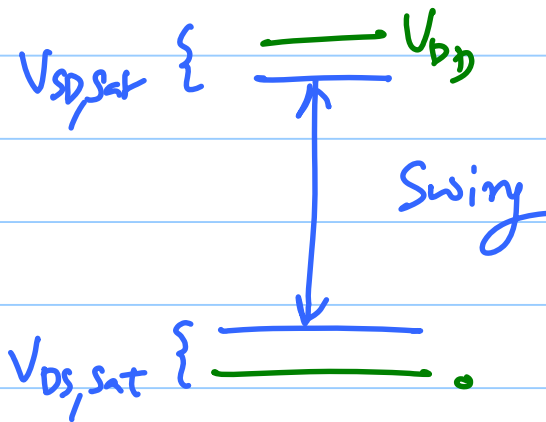

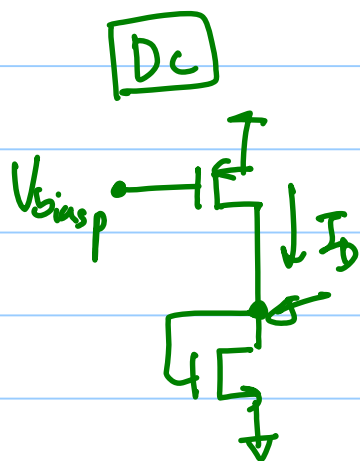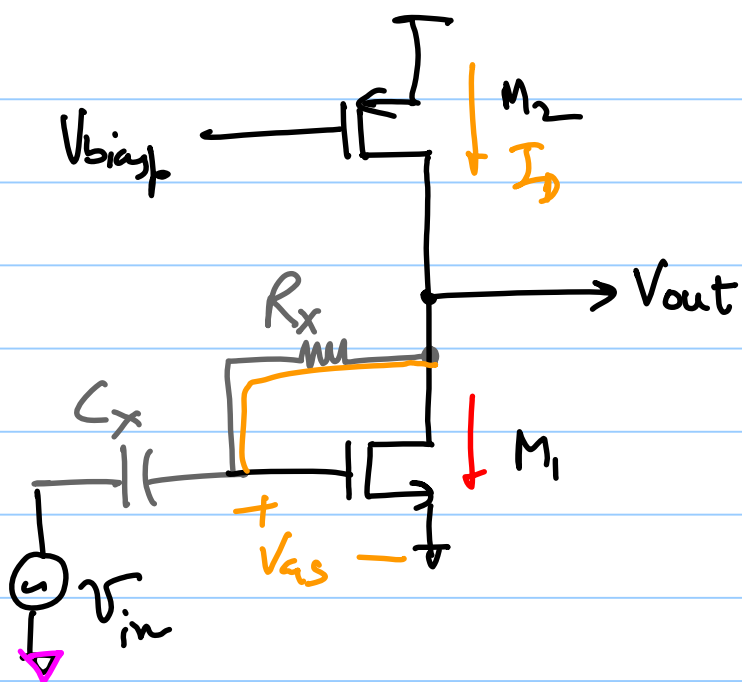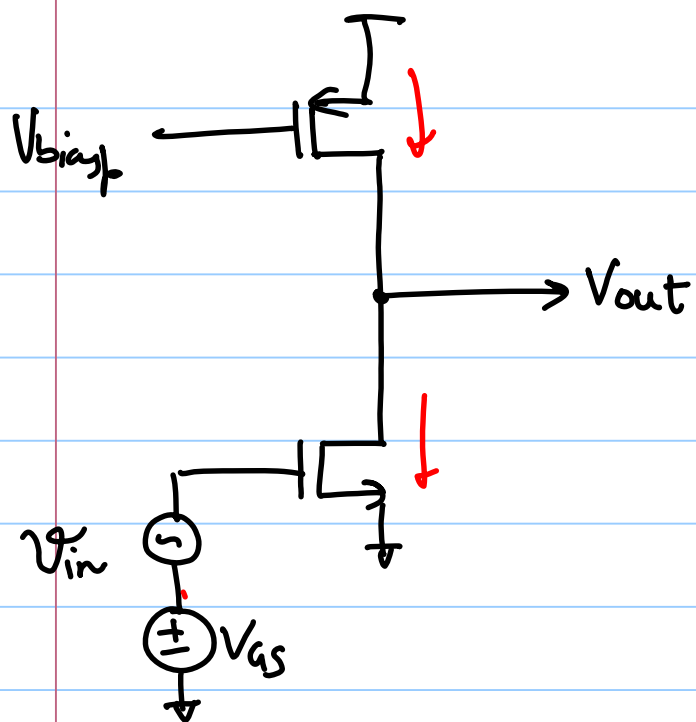

Ac

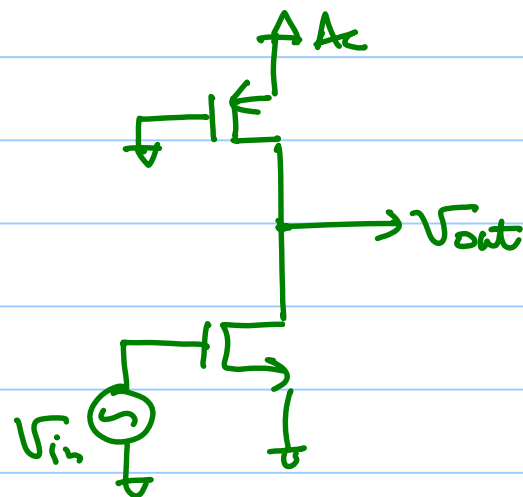

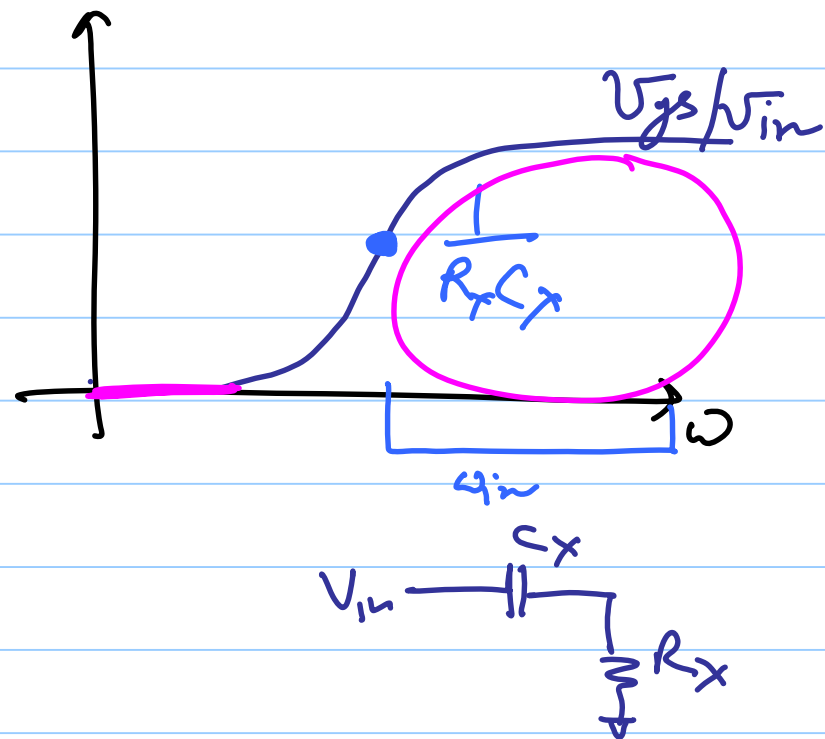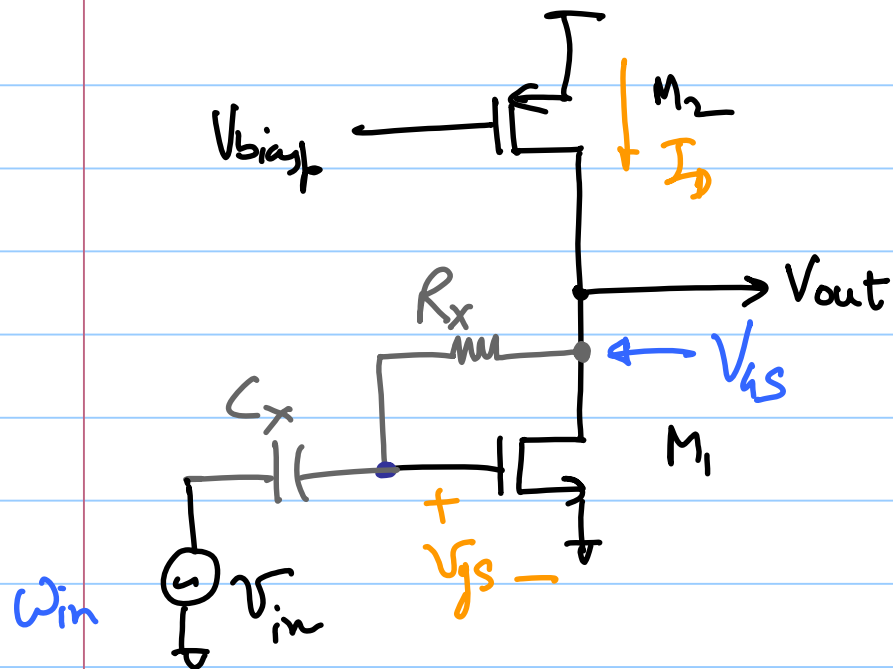

$$\omega_x \ll \omega_{in}$$

$$\frac{1}{R_x C_x} \ll \omega_{in}$$


$$R_x C_x \gg \frac{1}{\omega_{in}} = \frac{10}{\omega_{in}}$$


$$\omega_{in} = 2\pi \times 1\text{kHz}$$

$$R_x C_x \geq \frac{10}{6.28 \times 10^3} = 1.6 \text{ ms}$$

$$R_x = 100\text{k}\Omega$$
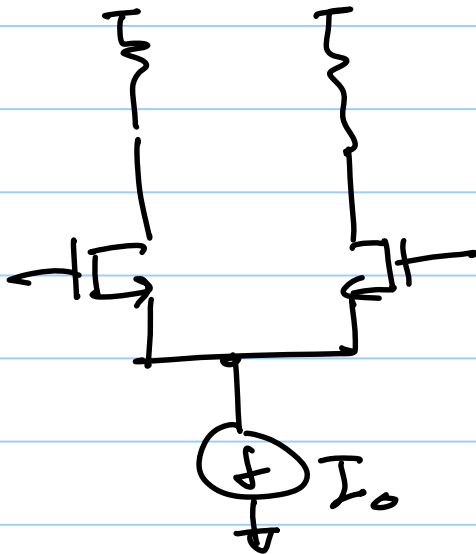
$$C_x = \frac{1.6 \times 10^{-3}}{10^5} = 1.6 \times 10^{-8} \\ = 16 \text{ nF}$$







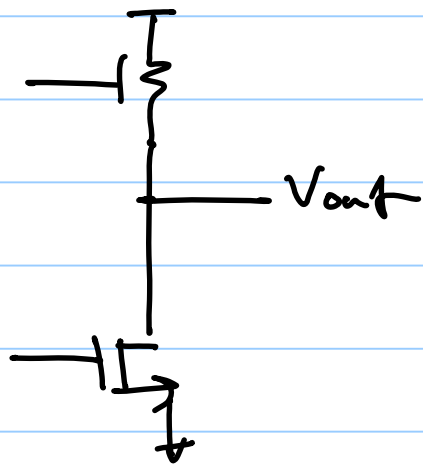



Triode load

↳ poor gain

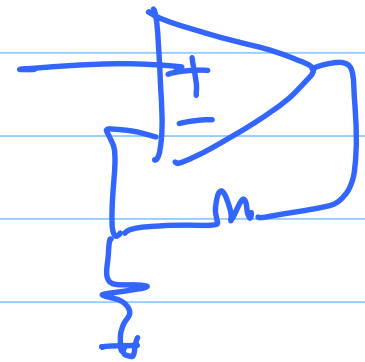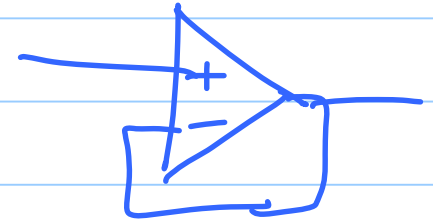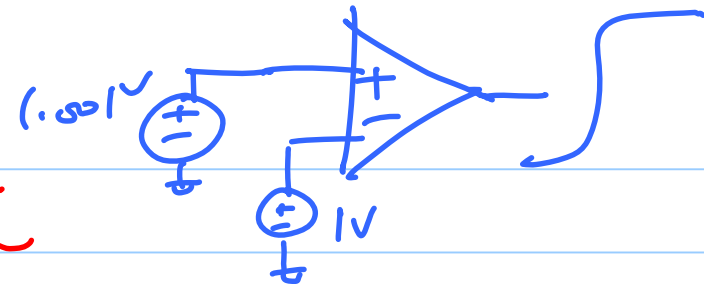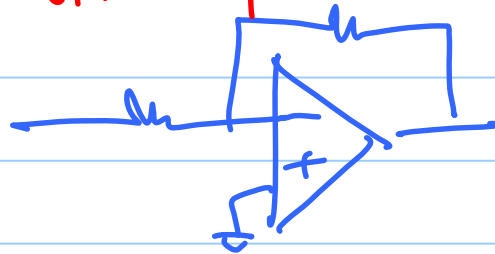Always use large gain
stays with feedback



Source Degeneration

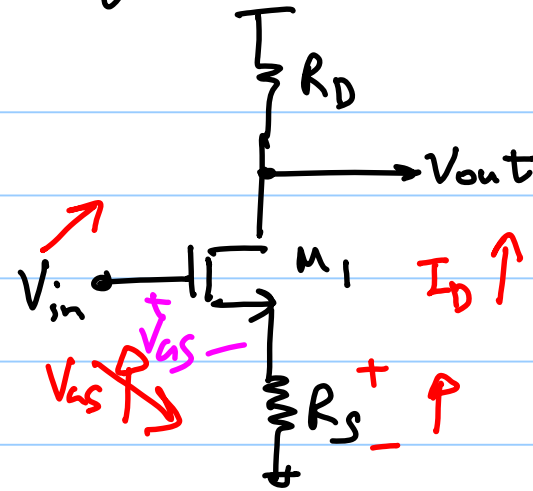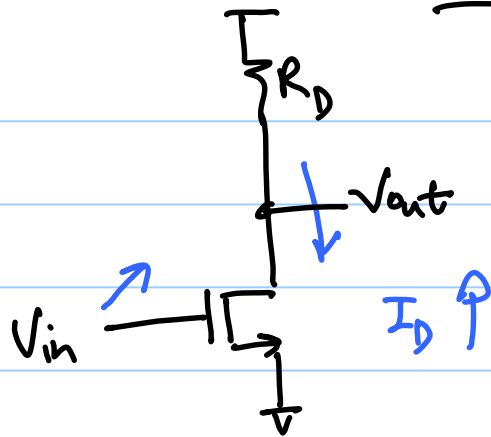



$$I_D = \frac{V_{in} - V_{as}}{R_S}$$

$M_1 \Rightarrow$ non linear IV characteristics

$R_S \Rightarrow$ linear resistance

$\Rightarrow$ a large portion of V_{in} is dropped across R_S
 $\hookrightarrow I_D$ shows linear dependence on V_{in}

$$\lambda = 0, \quad \gamma = 0$$

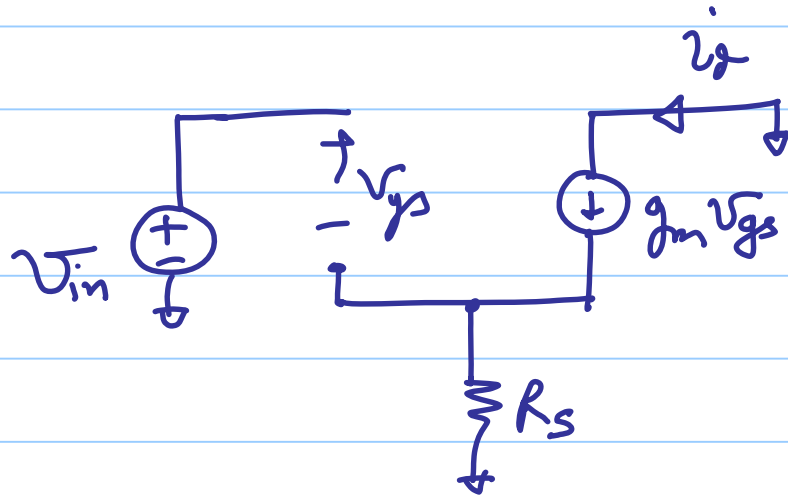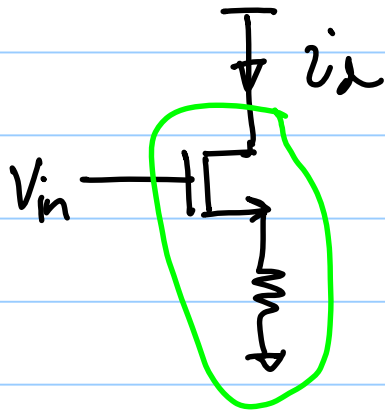

$$G_m = \frac{g_m}{1 + g_m R_s}$$

$$\approx \frac{1}{R_s} \quad \text{for } g_m R_s \gg 1$$