



ECE 511 - Lecture 11

Note Title


2/19/2015

Voltage gain at DC


$$A_v = -g_{m1}(R_L \parallel r_{o1})$$

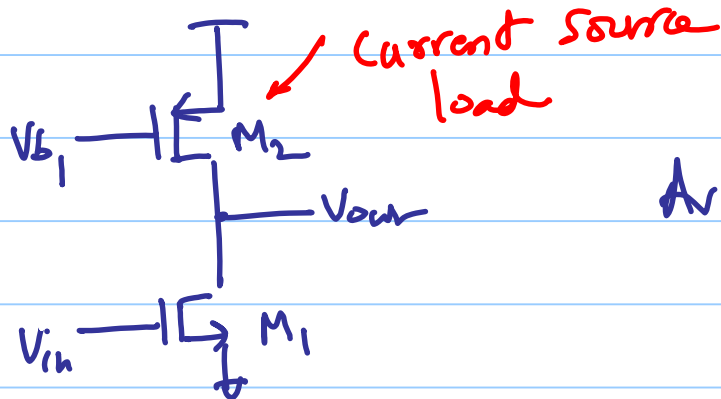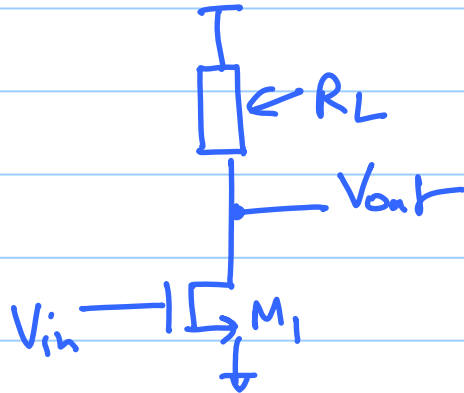
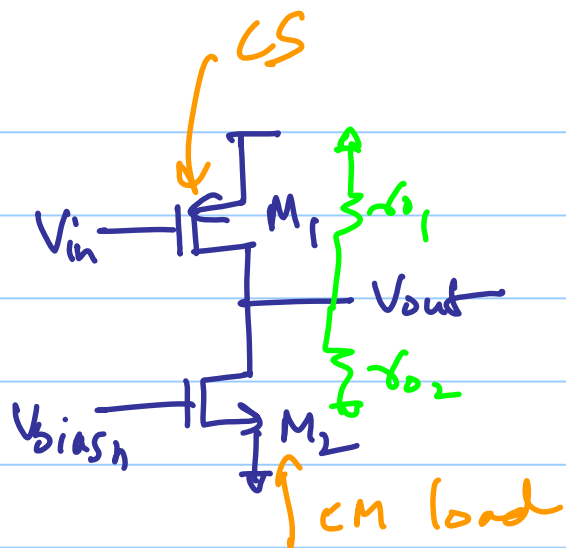
$$A_v = -g_{m1} r_{o1} \parallel r_{o2}$$



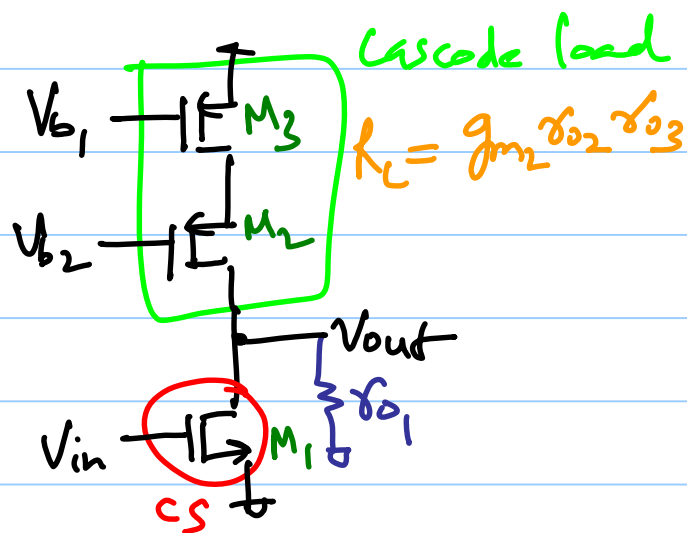
$$A_v = -g_{m1} \cdot (r_{O1} \parallel r_{O2})$$



$$A_v = -g_{m1} \cdot [r_{O1} \parallel (g_{m2} r_{O2} r_{O3})]$$


$$\approx -g_{m1} r_{O1}$$

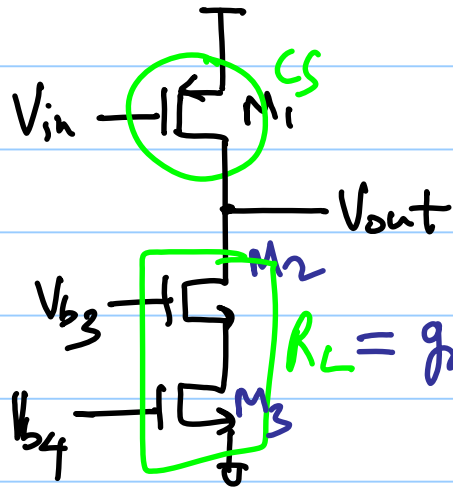

$$A_v = -g_{m1} \cdot r_{o1} \parallel R_L$$

$$R_L = g_{m2} r_{o2} r_{o3}$$

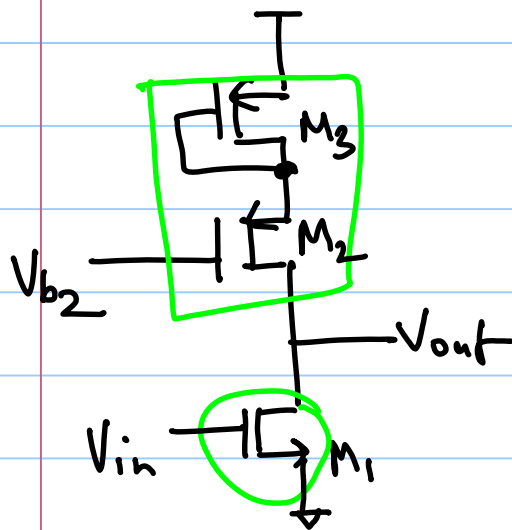
$$R_L = \boxed{g_{m2} r_{o2} r_{o3}} + \underbrace{r_{o2} + r_{o3}}$$




$$A_v = -g_{m1} \cdot r_{o1} \parallel R_L$$

$$\downarrow$$

$$g_{m2} r_{o2} \cdot \frac{1}{g_{m3}}$$

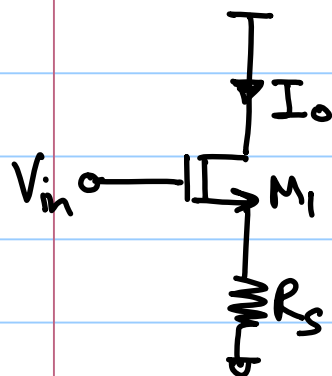

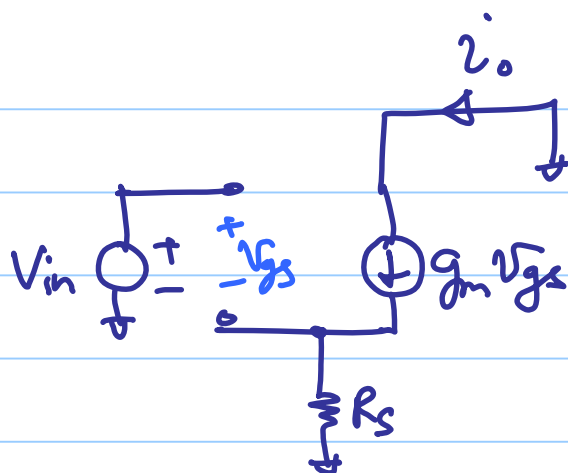$\lambda=0, \gamma=0$
 $\hookrightarrow$ Exact analysis in Razavi Book





$$v_{gs} = V_{in} - i_o R_s$$

$$i_o \approx g_m v_{gs} = g_m (V_{in} - i_o R_s)$$

$$i_o (1 + g_m R_s) = g_m V_{in}$$

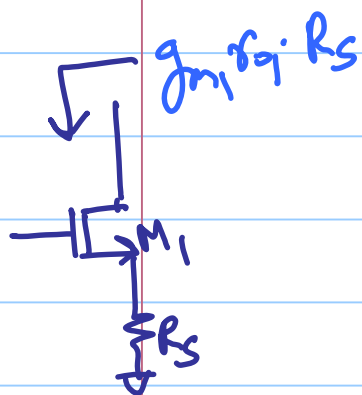
$$\Rightarrow \frac{i_o}{V_{in}} = \boxed{\frac{g_m}{1 + g_m R_s}} = \underline{g_m}$$



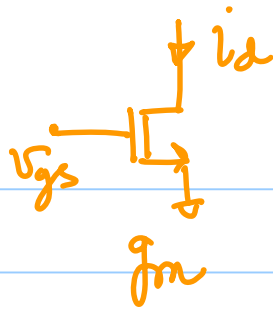

A small-signal model of a MOSFET with a source resistor R_s . The transconductance is labeled g_m . The formula for the effective transconductance is given as:

$$g_{m'} = \frac{g_m}{1 + g_m R_s}$$

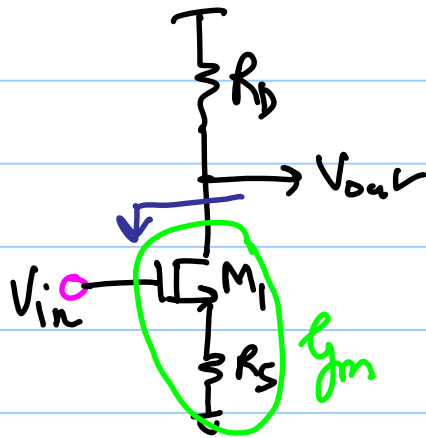




$$A_v = -g_m \cdot R_D \parallel (g_{m'} R_s)$$

$$\approx -g_m \cdot R_D$$

$$= -\frac{g_{m_1}}{1 + g_{m_1} R_s} \cdot R_D$$

$$= -\frac{g_{m_1} R_D}{1 + g_{m_1} R_s}$$

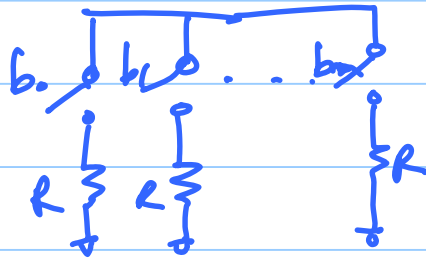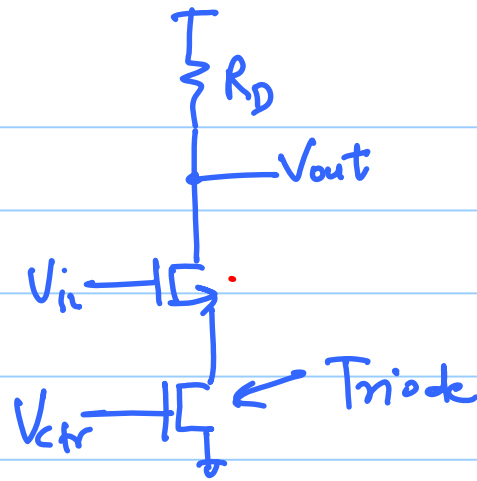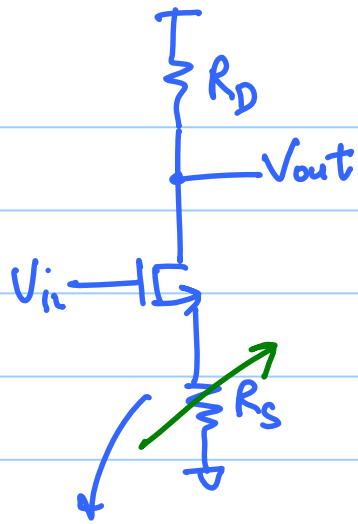As gain is reduced by a factor of
 $(1 + g_{m_1} R_s)$



$$A_v = - \frac{g_{m1} R_D}{1 + g_{m1} R_S}$$

Let's say $g_{m1} R_S \gg 1$

$$\Rightarrow \boxed{g_{m1} R_S \gg 1}$$

$$\Rightarrow \frac{1}{g_{m1}} \ll R_S \checkmark$$

$$\Rightarrow g_{m1} \gg \frac{1}{R_S}$$

$$= - \frac{\cancel{g_{m1}} R_D}{\cancel{g_{m1}} R_S} = \boxed{- \frac{R_D}{R_S}}$$

"Linear" gain

as $g_{m1} r_s \gg 1$

$$g_m = \frac{g_{m1}}{1 + g_{m1} r_s} \approx \frac{1}{r_s}$$

$\Rightarrow g_m$ becomes a weak function of g_m








$\Rightarrow$ drain current is linearized function of the input voltage

Tradeoff b/w
gain Δ linearity


Exact analysis:

$$g_m = \frac{I_{out}}{v_{in}} = \frac{g_{m1} r_o}{R_s + [1 + (g_{m1} + g_{mb1}) R_s] \cdot r_o}$$

$\leftarrow$ Exercise

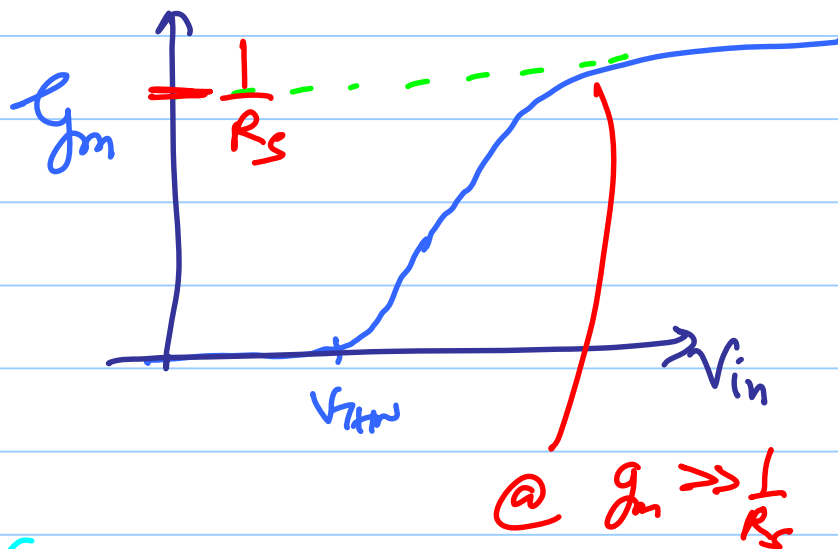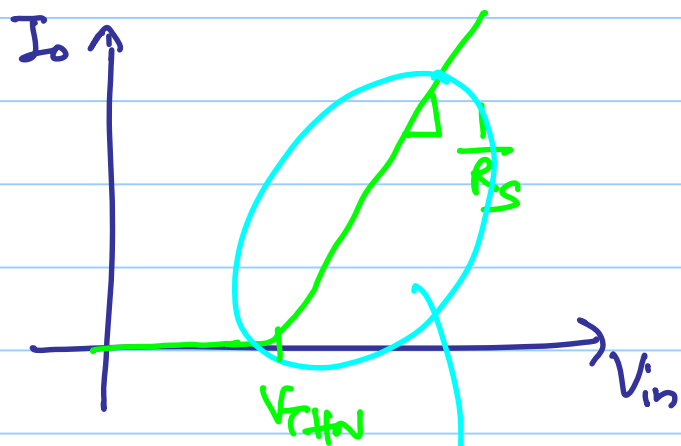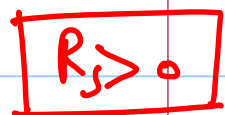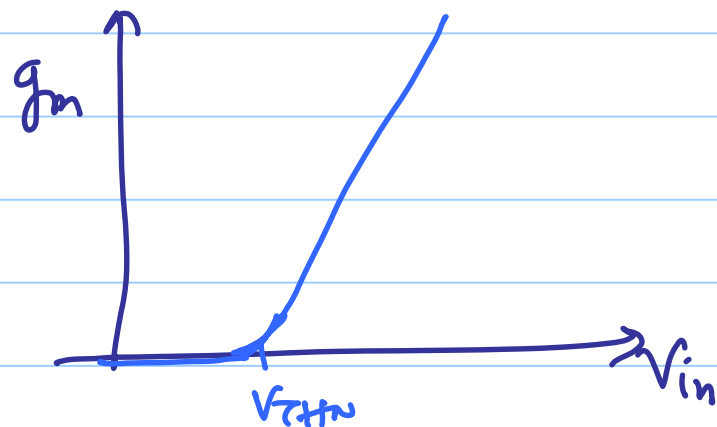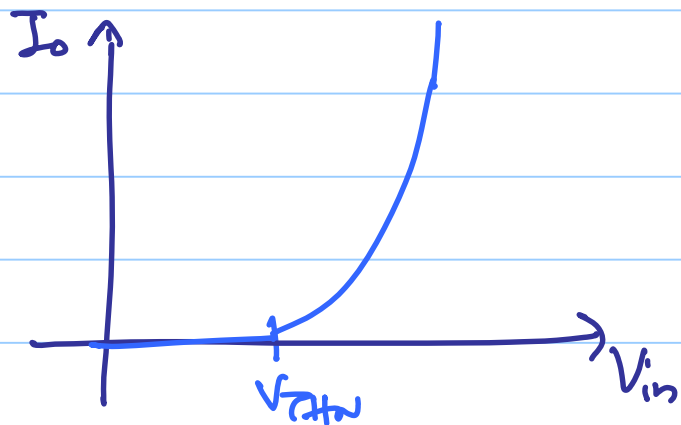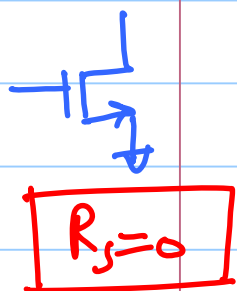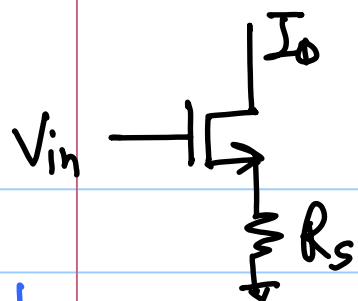


jump

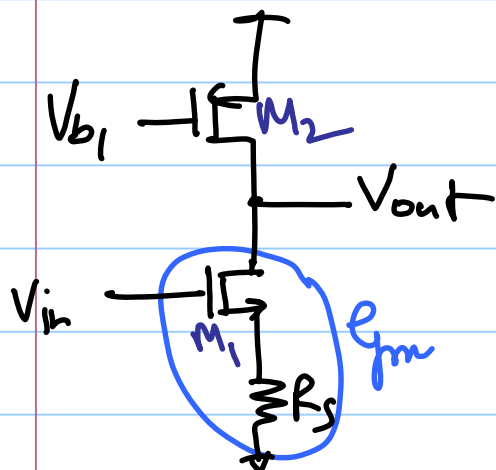

$$A_v = -g_{m1} \left[r_{o2} \parallel (g_{m1} r_{o1} R_S) \right]$$



$$= -\frac{g_{m1}}{1 + g_{m1} R_S} \cdot r_{o2} \parallel R_x$$

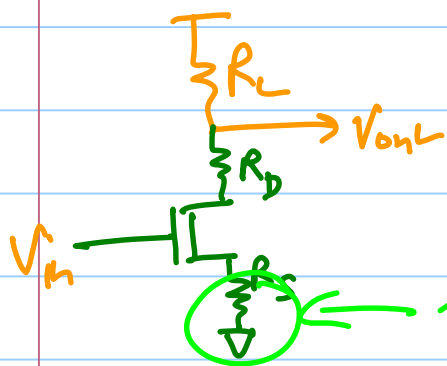
$$\approx -\frac{g_{m1} r_{o2}}{1 + g_{m1} R_S}$$




parasitics can also
cause degeneration

Common Drain (Source follower)

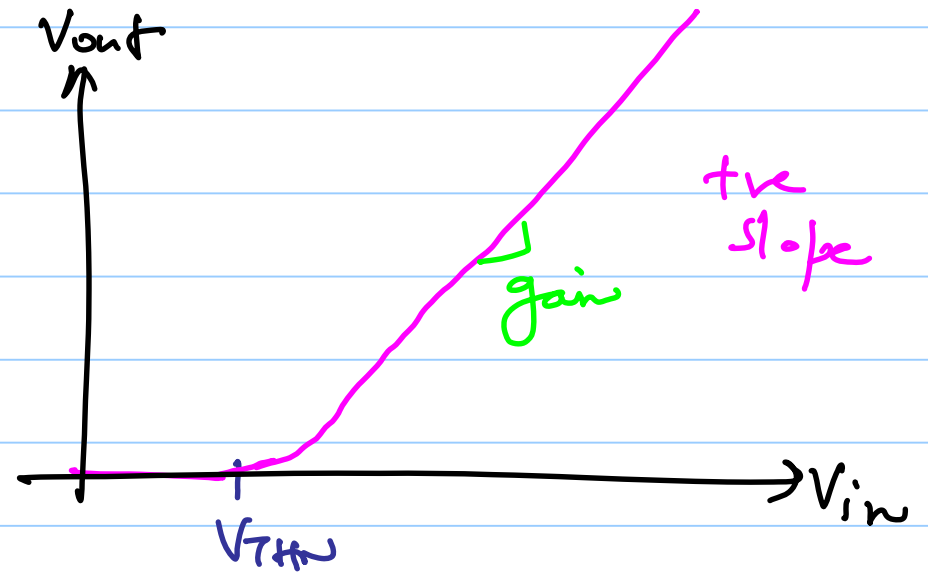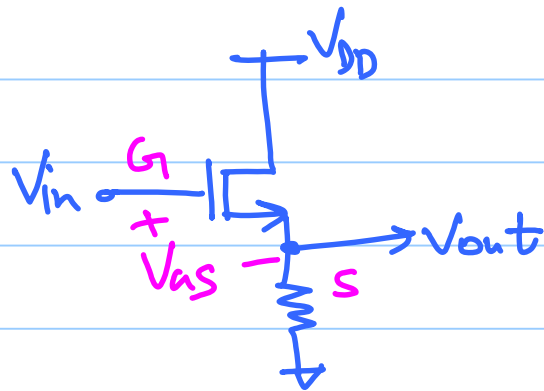

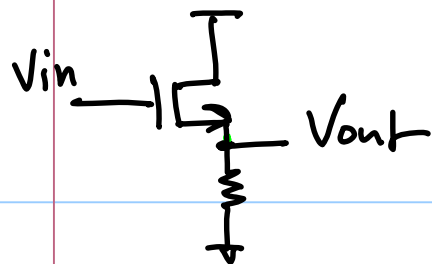

$\lambda = 0$
for simpler
analysis

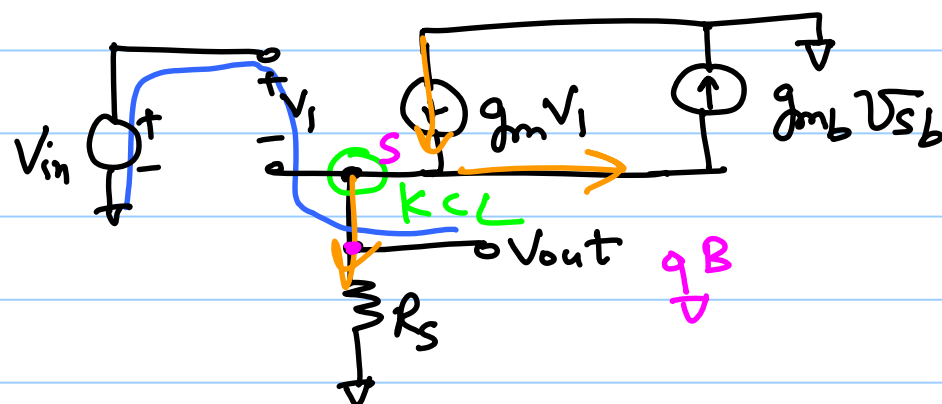

$$V_{in} - V_1 = V_{out} \rightarrow \textcircled{1}$$

$$V_{S_b} = V_{out} \rightarrow \textcircled{2}$$

$$g_m V_1 - g_{m_b} V_{out} = \frac{V_{out}}{R_s} \rightarrow \textcircled{3}$$

$$\Rightarrow g_m (V_{in} - V_{out}) - g_{m_b} V_{out} = \frac{V_{out}}{R_s}$$


$$\Rightarrow V_{out} \left[(g_m + g_{m_b}) + \frac{1}{R_s} \right] = g_m V_{in}$$

$$\Rightarrow \frac{V_{out}}{V_{in}} = \frac{g_m R_s}{1 + (g_m + g_{mb}) R_s} < 1$$


non-inverting "gain"

$$= \frac{g_m R_s}{1 + (\eta + 1) g_m R_s}$$
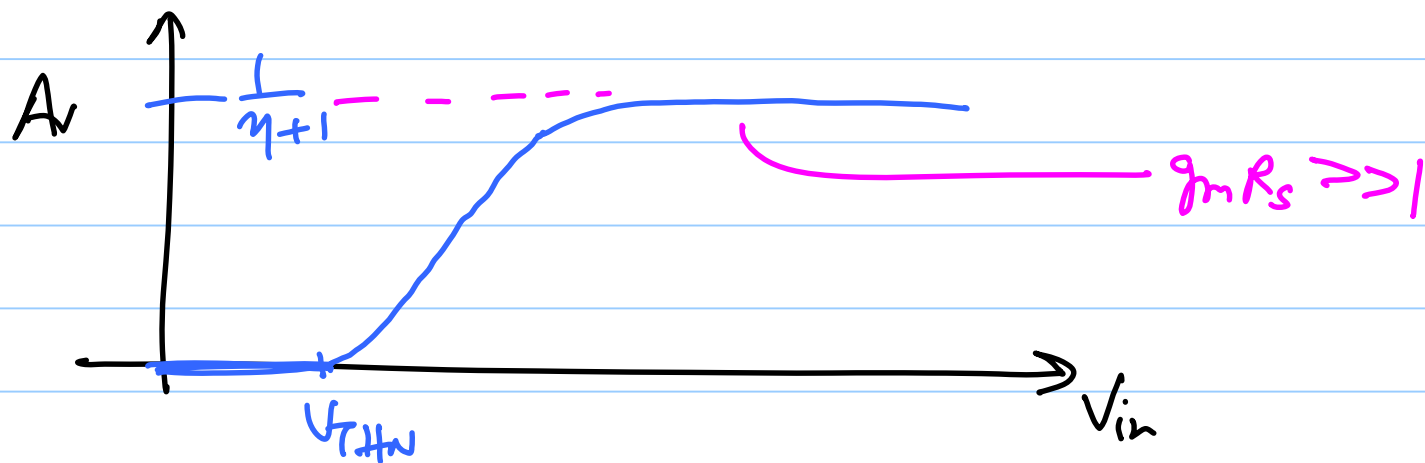
$$= \frac{1}{(\eta + 1) + \frac{1}{g_m R_s}} < 1$$



*

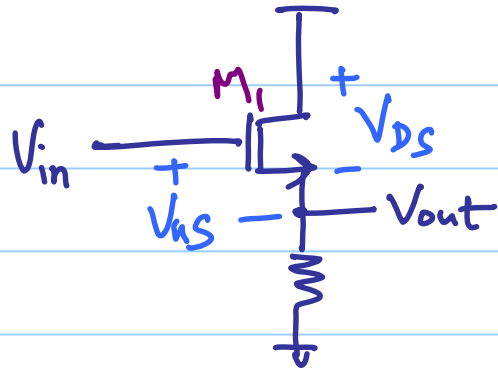

$$\begin{aligned} V_{DS} &= V_{DD} - V_{out} \\ &= V_{DD} - (V_{in} - V_{gs}) \\ &= V_{DD} - V_{in} + V_{gs} \end{aligned}$$


for M_1 to be in saturation

$$V_{DS} \geq V_{DS, sat}$$

$$\Rightarrow V_{DD} - V_{in} + V_{gs} \geq V_{gs} - V_{THN}$$

$$V_{in} \leq V_{DD} + V_{THN} \quad \text{Always satisfied}$$



M_1 never triodes

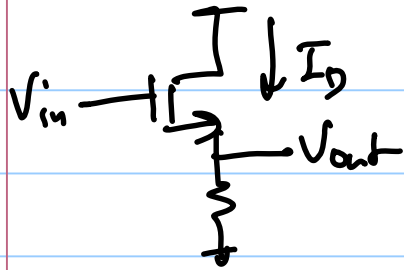

$$V_{in} \uparrow \Rightarrow I_D \uparrow \Rightarrow g_m \uparrow$$




$\Rightarrow$ non-linearity with larger input amplitude

$\Rightarrow$ fix the bias current

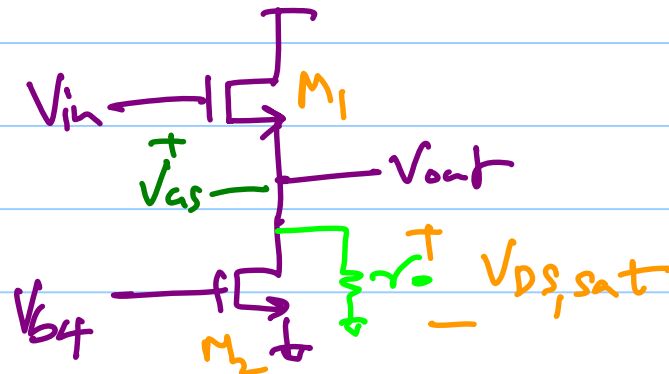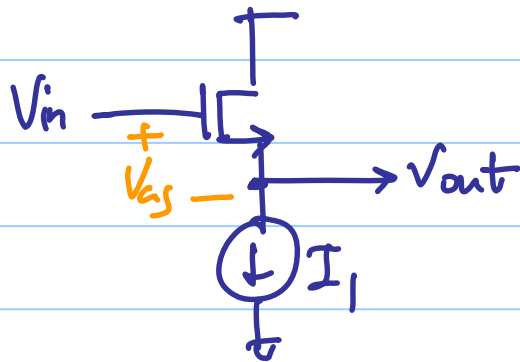


M_2 must be in SAT
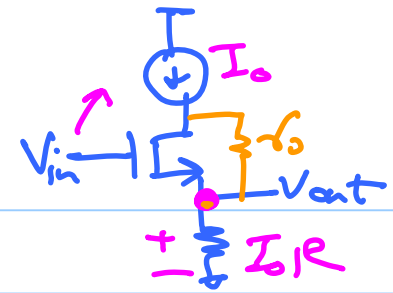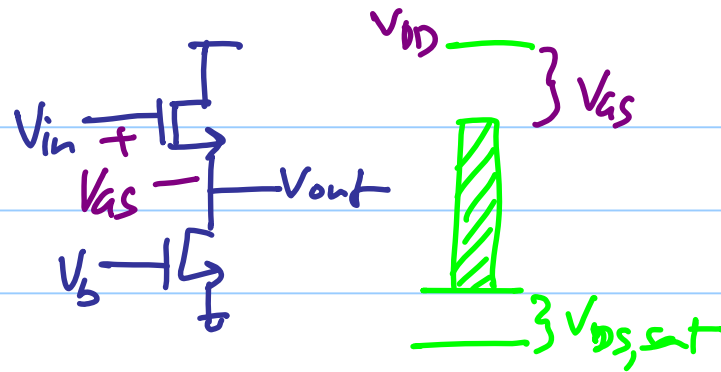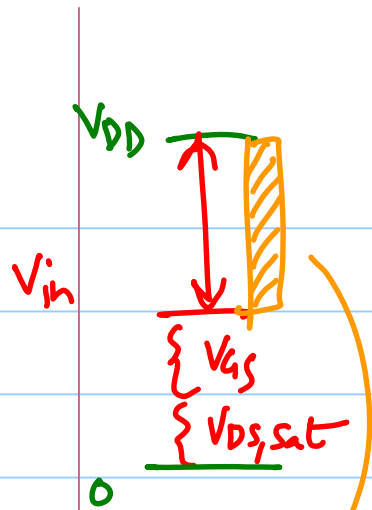
$$\Rightarrow V_{in} > V_{GS} + V_{DS,sat}$$



input headroom
is reduced

level shifting by V_{GS}

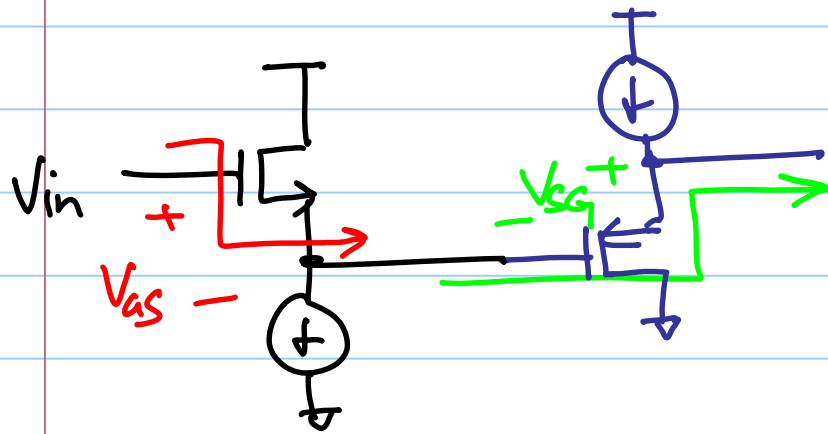

$\Rightarrow$ Can use for DC level shifter