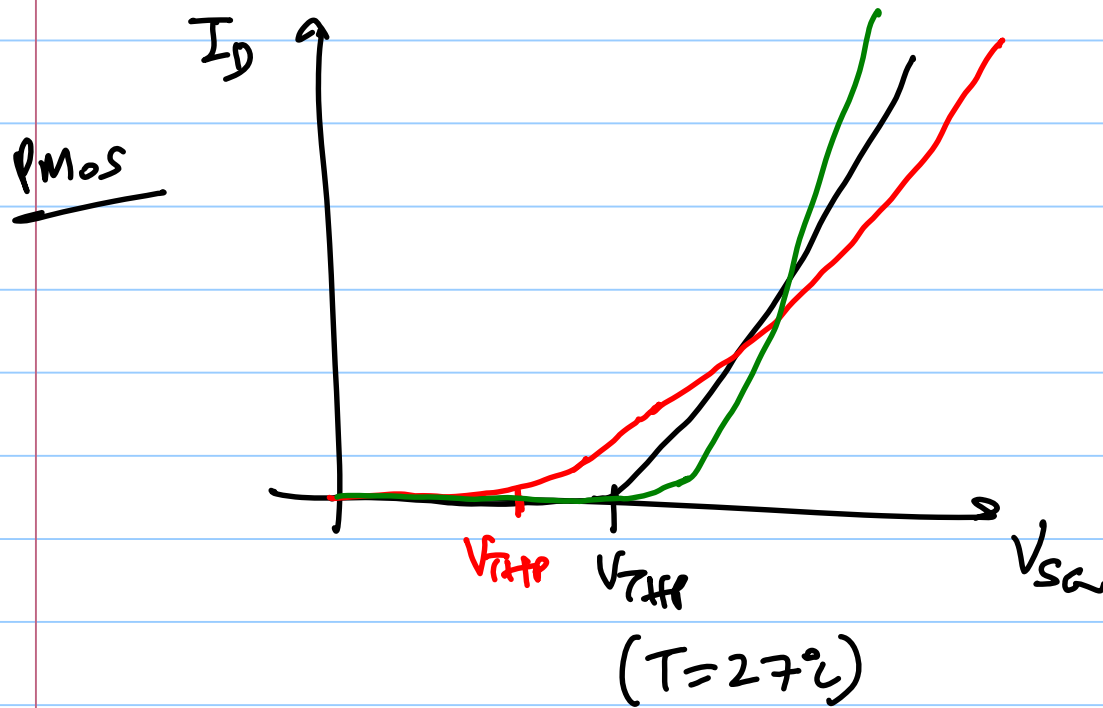


ECE 511 - Lecture

Note Title


2/26/2015



$$T = 50^{\circ}\text{C}$$
$$V_{THTP} \downarrow \quad K_P \downarrow$$

$$I_D = \frac{1}{2} \underline{K_P} \frac{W}{L} (V_{SG} - V_{THTP})^2$$


$$T = 0^{\circ}\text{C}$$


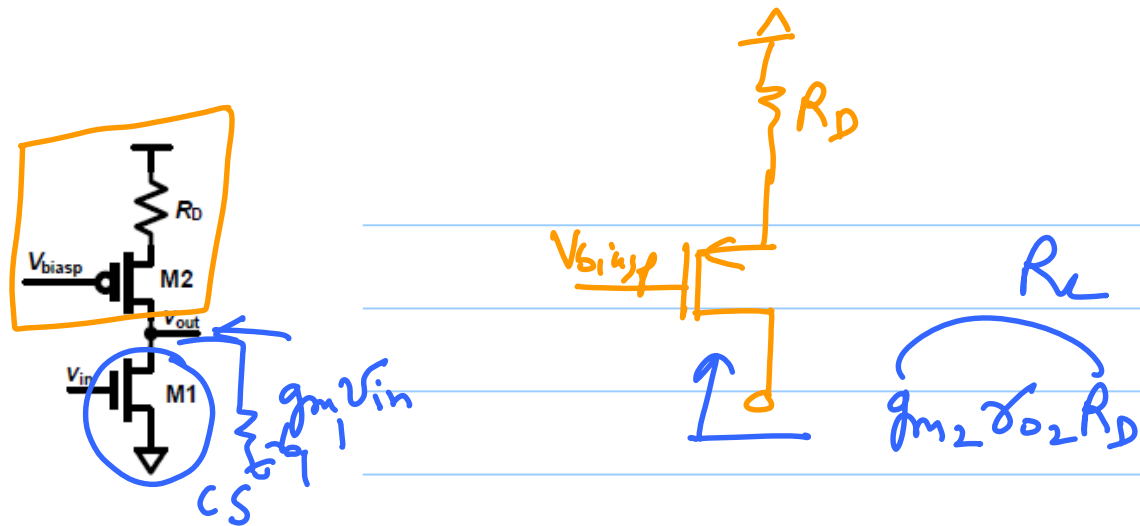


$$V_{out} = -i_d (r_{o1} \parallel R_L)$$

$$= -g_{m1} V_{in} (r_{o1} \parallel R_L)$$
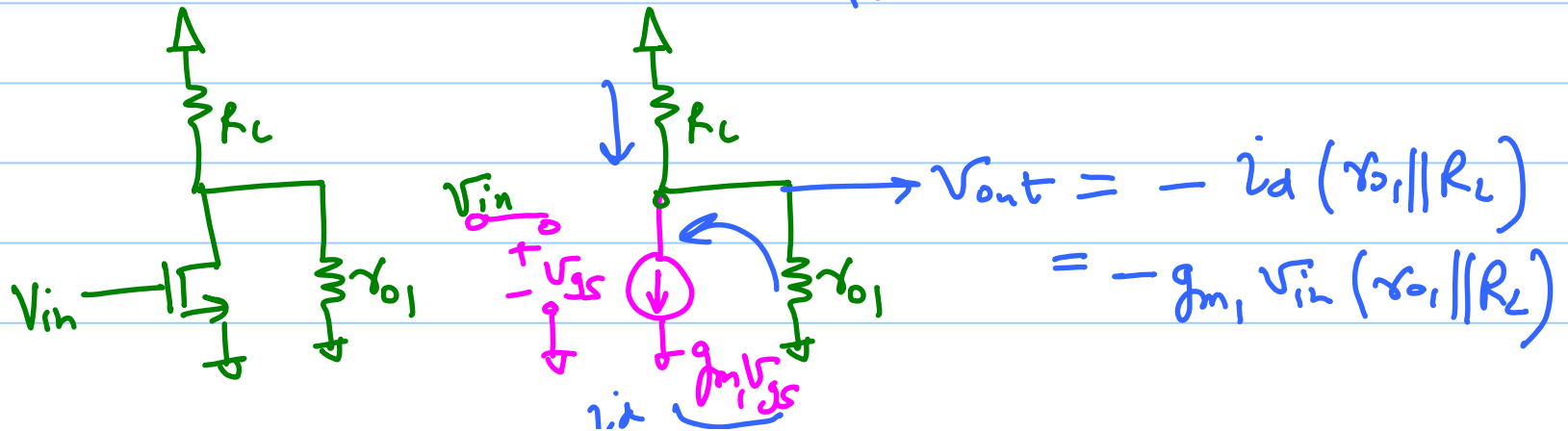
$$\Rightarrow A_v = \frac{V_{out}}{V_{in}} = -g_{m1} (r_{o1} \parallel R_L)$$



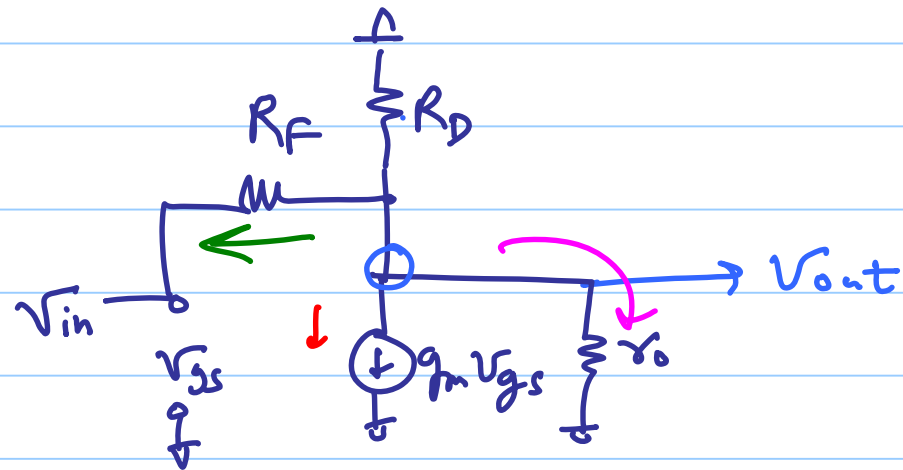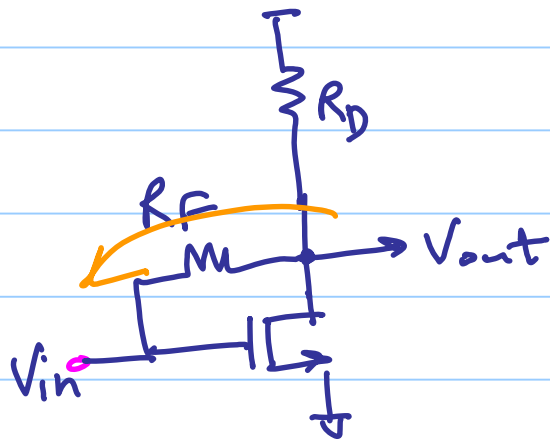

KCL

$$-\frac{V_{out}}{R_o \parallel R_D} - \frac{(V_{out} - V_{in})}{R_F} - g_m V_{in} = 0$$


$$-V_{out} \left[\frac{1}{R_o \parallel R_D} + \frac{1}{R_F} \right] = g_m V_{in} - \frac{V_{in}}{R_F}$$




$$\Rightarrow \frac{-V_{out}}{r_o \parallel R_D \parallel R_F} = (g_m - \frac{1}{R_F}) V_{in}$$

$$A_v = \frac{V_{out}}{V_{in}} = - (g_m - \frac{1}{R_F}) (r_o \parallel R_D \parallel R_F)$$


g_m & r_o dimensions

$$g_m \ll \frac{1}{R_F}$$

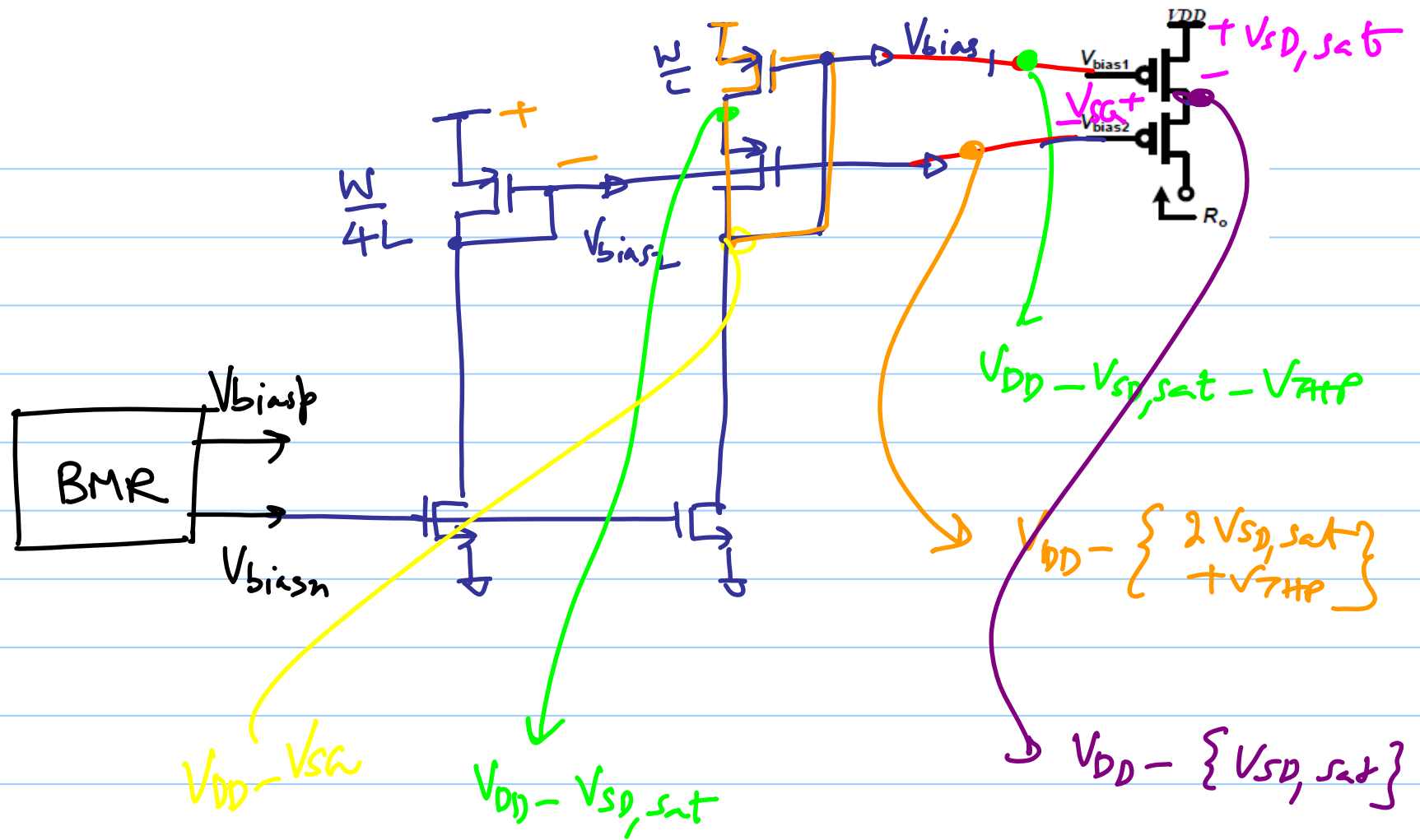


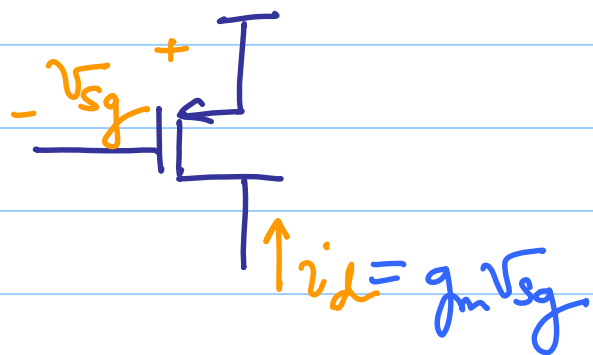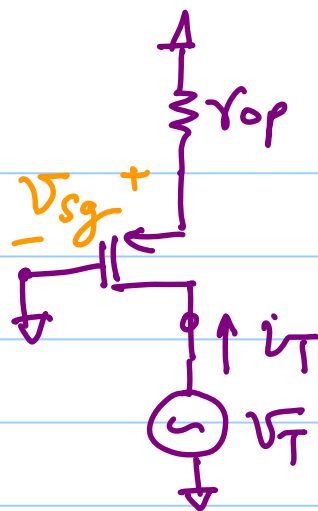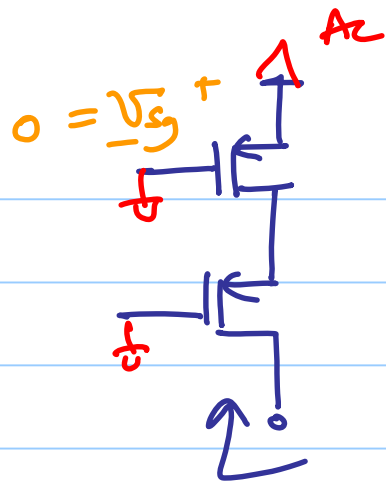

①

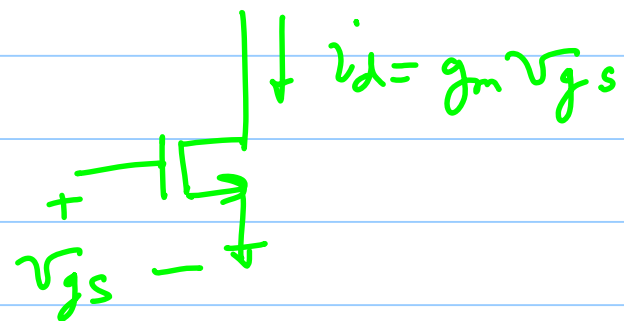


$$-V_{SG1} +$$

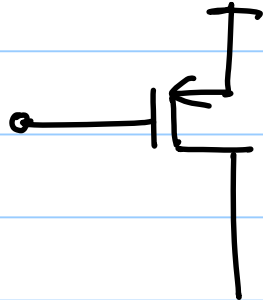


$$\downarrow I_D$$

$$i_D = I_D + i_d$$



OR

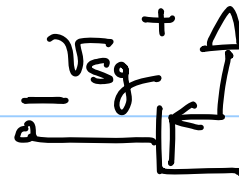


$$\downarrow i_d = g_m v_{sg}$$

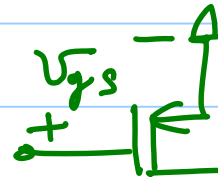

$$\uparrow i_d = g_m v_{gs}$$

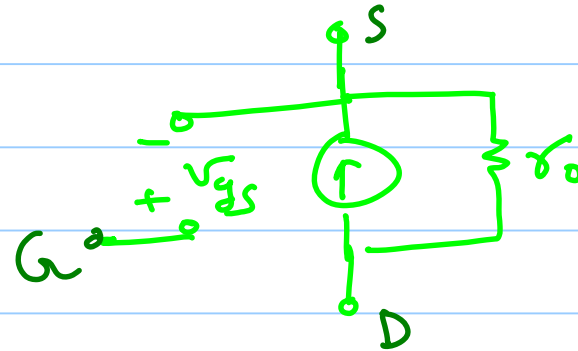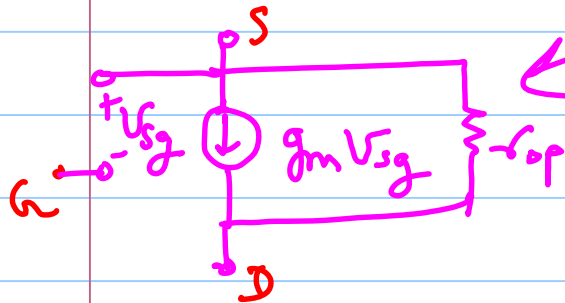

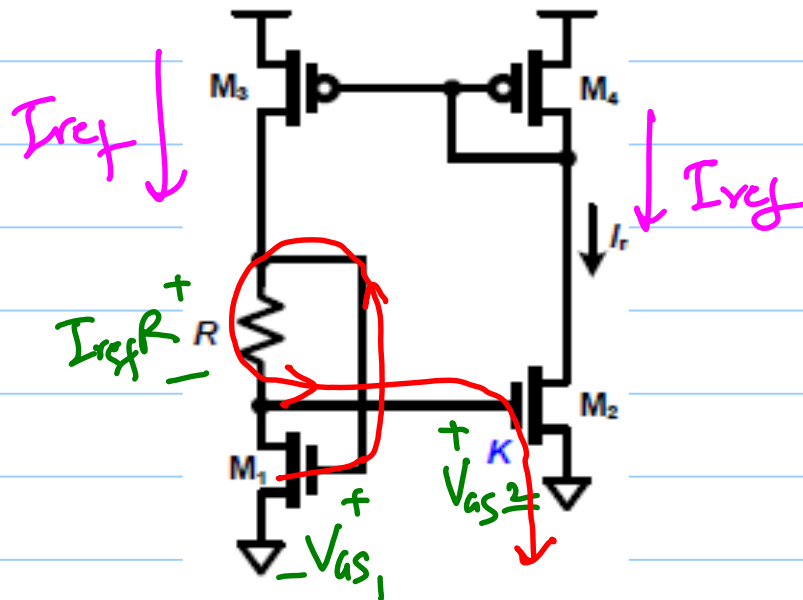

$$V_{GS1} - I_{ref}R = V_{GS2}$$

$$V_{GS1} = V_{GS2} + I_{ref}R$$

$$V_{THN1} = V_{THN2}$$

as V_{SB} are same

no body-effect

$$I_{ref} = \frac{2}{\beta R^2} \left(1 - \frac{1}{\sqrt{K}} \right)^2$$

$$V_{biasn} \Leftarrow V_{GS} = \sqrt{\frac{2I_{ref}}{\beta}} + V_{THN}$$



$$= \sqrt{\frac{2}{\beta} \cdot \frac{2}{\beta R^2} \left(1 - \frac{1}{\sqrt{k}}\right)^2} + V_{THN}$$

$$= \frac{2}{\beta R} \left(1 - \frac{1}{\sqrt{k}}\right) + V_{THN}$$



Indep of supply term

$$g_m = \beta(V_{GS} - V_{THN}) = \frac{2}{R} \left(1 - \frac{1}{\sqrt{k}}\right)$$
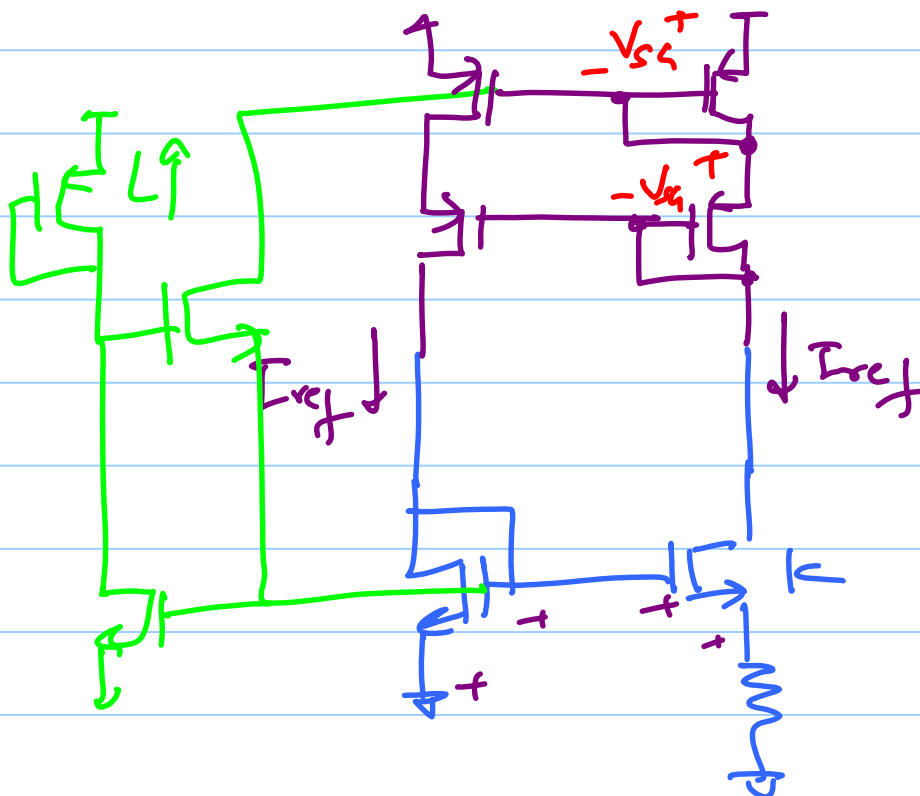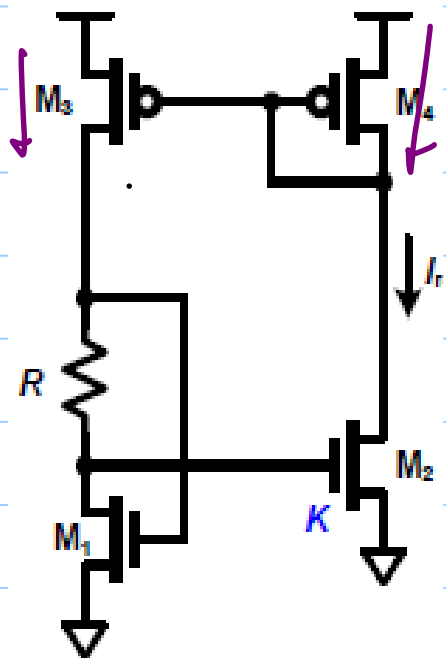
$$\text{for } k=4 \quad g_m = \frac{1}{R}$$



THE FOLLOWING CIRCUIT DIAGRAMS SHOW THE

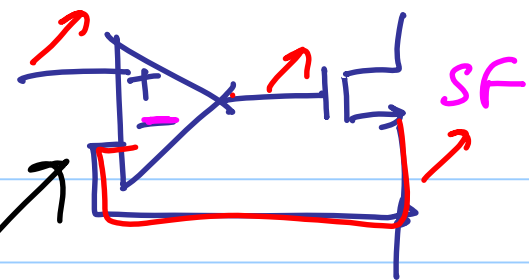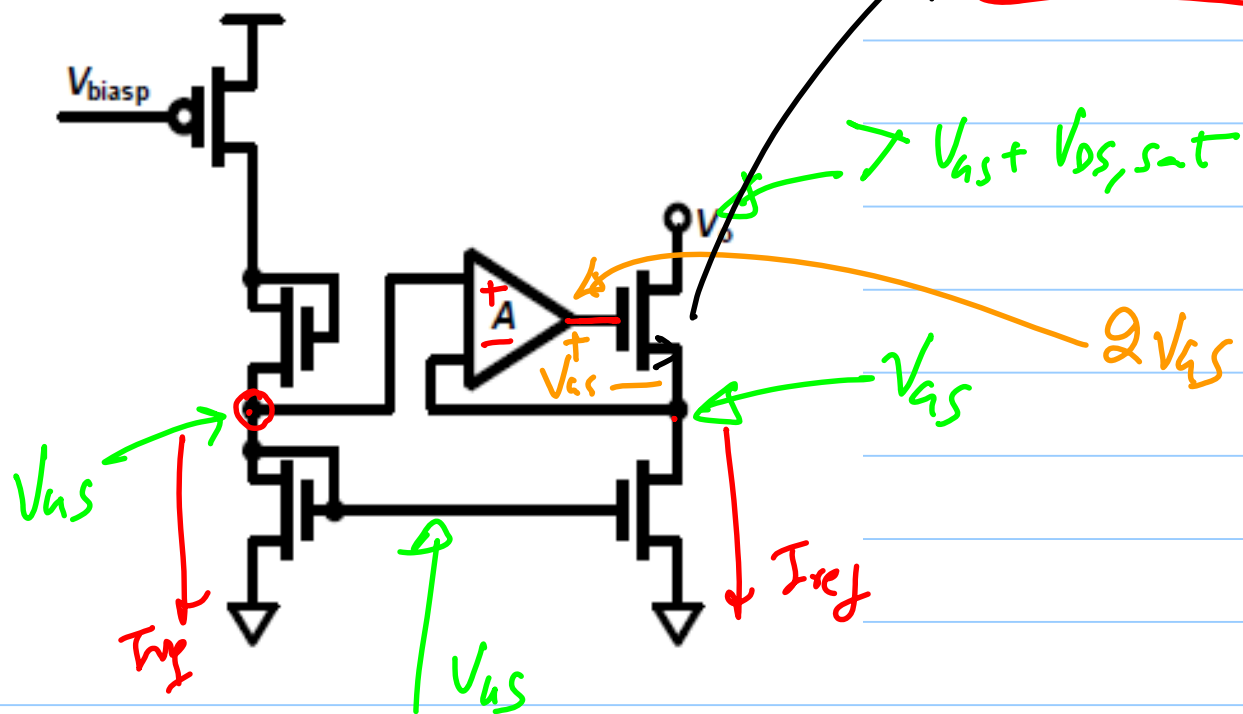

Aside

