
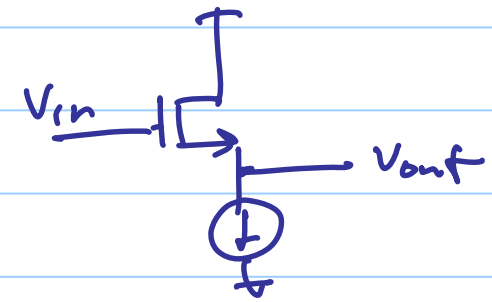




ECE 511 - Lecture 14

Note Title

3/5/2015

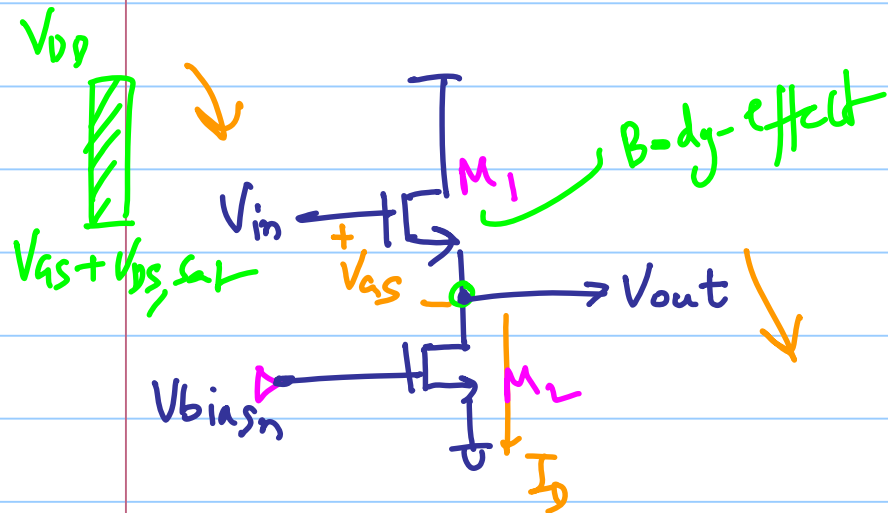

Voltage Buffer with DC level-shift

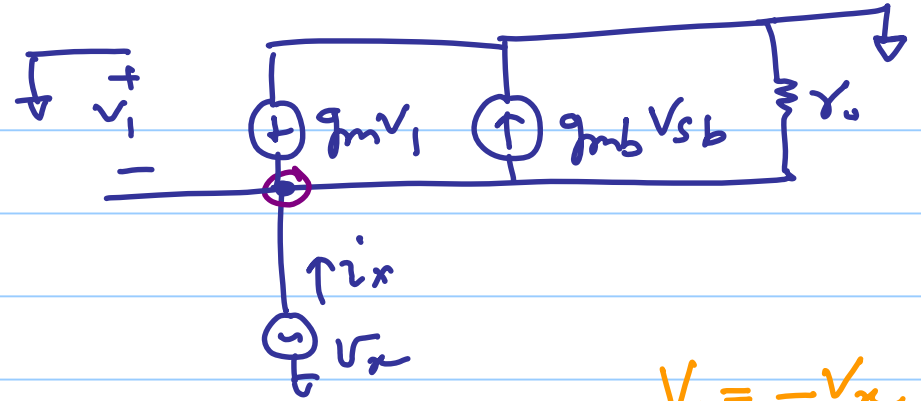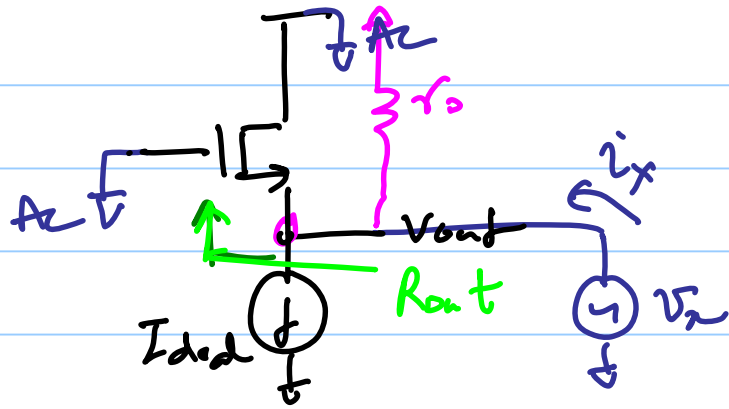

$$V_1 = -V_x$$

$$V_{sb} = V_x$$

$$i_x - g_m V_x - g_{mb} V_x - \frac{V_x}{r_o} = 0$$




$$R_{out} = \frac{V_x}{i_x} = \frac{1}{(g_m + g_{mb}) + \frac{1}{r_o}}$$

low- Z
output


$$= \left(\frac{1}{g_m} \right) \parallel \left(\frac{1}{g_{mb}} \right) \parallel r_o \stackrel{\text{body-effect}}{\approx} \frac{1}{g_m} \text{ for } \gamma = 0$$

resistance looking into the source
 $\rightarrow$ drain is at AC ground

$\Rightarrow$

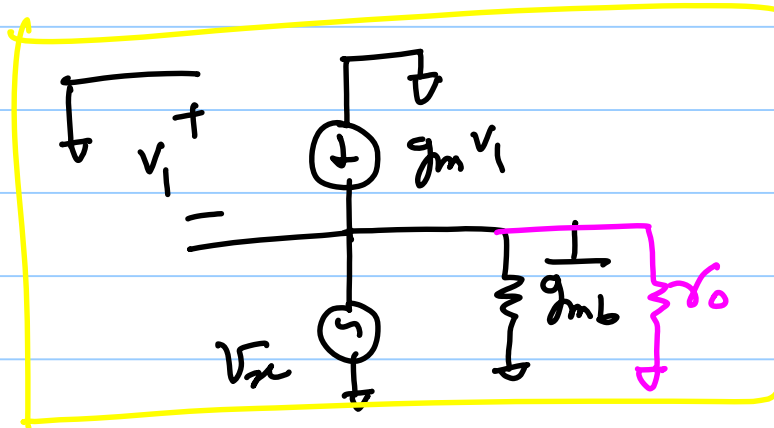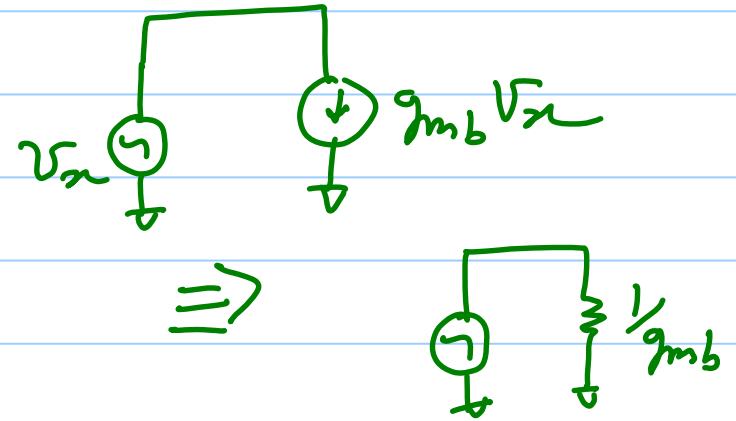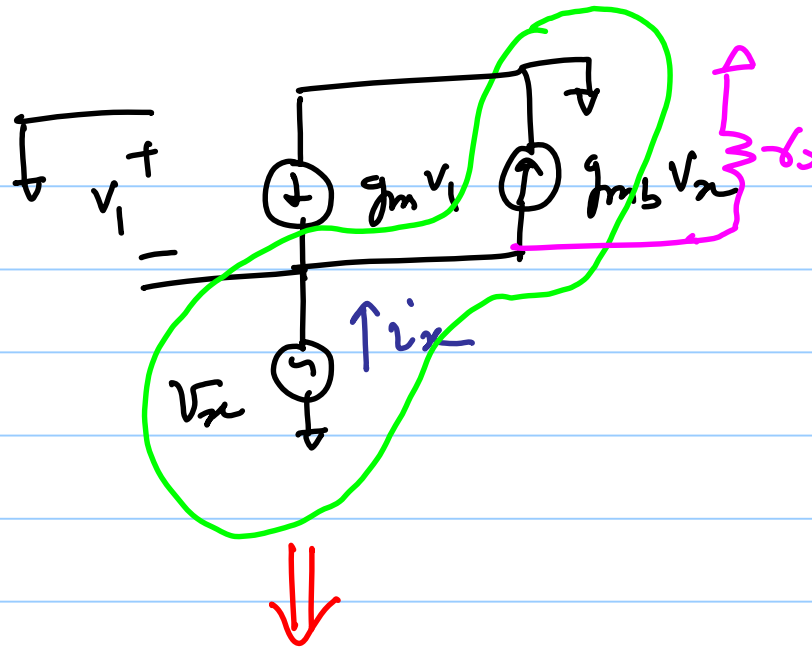

Model for SF device M_1 .

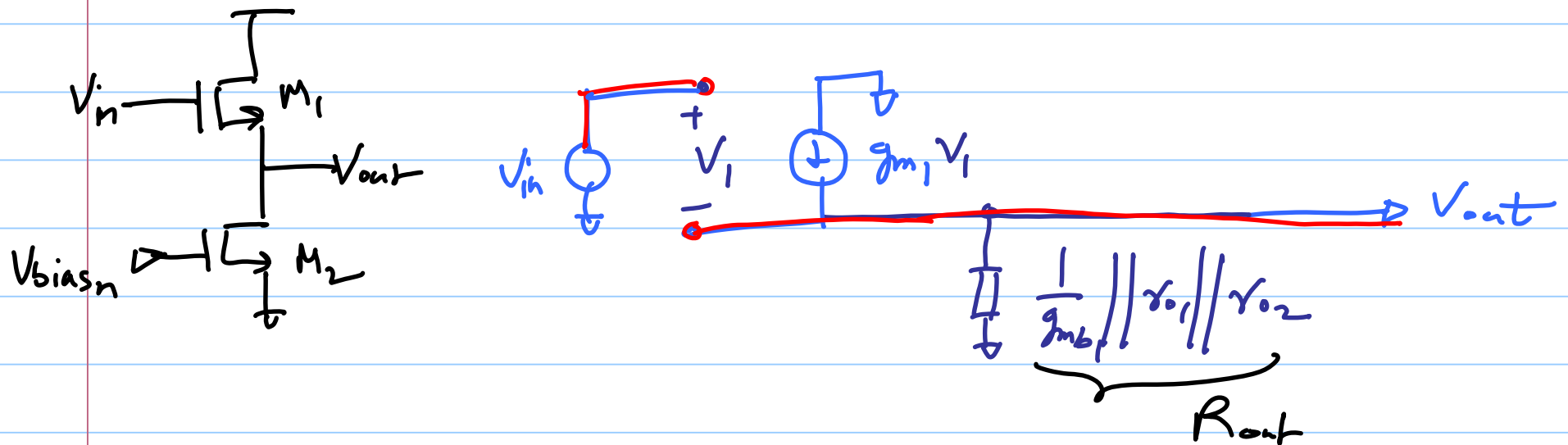


$$V_{out} = g_{m1} V_1 \cdot R_{out}$$

$$\Rightarrow V_{out} = g_{m1} R_{out} (V_{in} - V_{out})$$

$$\Rightarrow V_{out} [1 + g_{m1} R_{out}] = g_{m1} R_{out} \cdot V_{in}$$
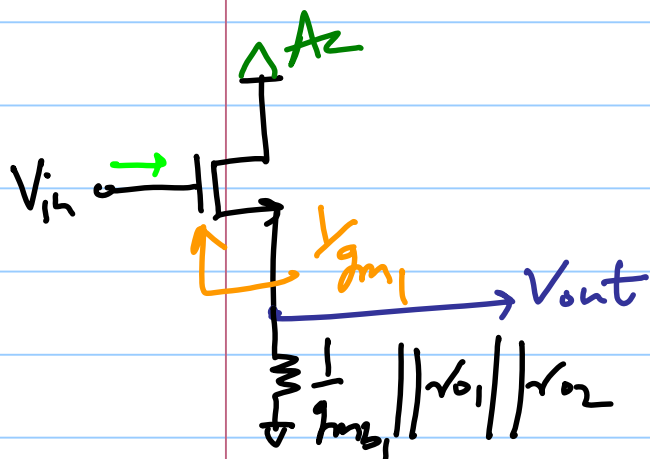
$$\Rightarrow A_v = \frac{V_{out}}{V_{in}} = \frac{g_{m1} R_{out}}{1 + g_{m1} R_{out}}$$



$$= \frac{R_{out}}{\frac{1}{g_m} + R_{out}}$$

$$= \frac{\frac{1}{g_{m_b}} \parallel r_{o_1} \parallel r_{o_2}}{\left(\frac{1}{g_{m_1}} \right) + \frac{1}{g_{m_b}} \parallel r_{o_1} \parallel r_{o_2}}$$


can visualize as a voltage divider

between $\frac{1}{g_{m_1}}$ & $\frac{1}{g_{m_b}} \parallel r_{o_1} \parallel r_{o_2}$

Resistance looking
into the source

Resistance
connected to the
source

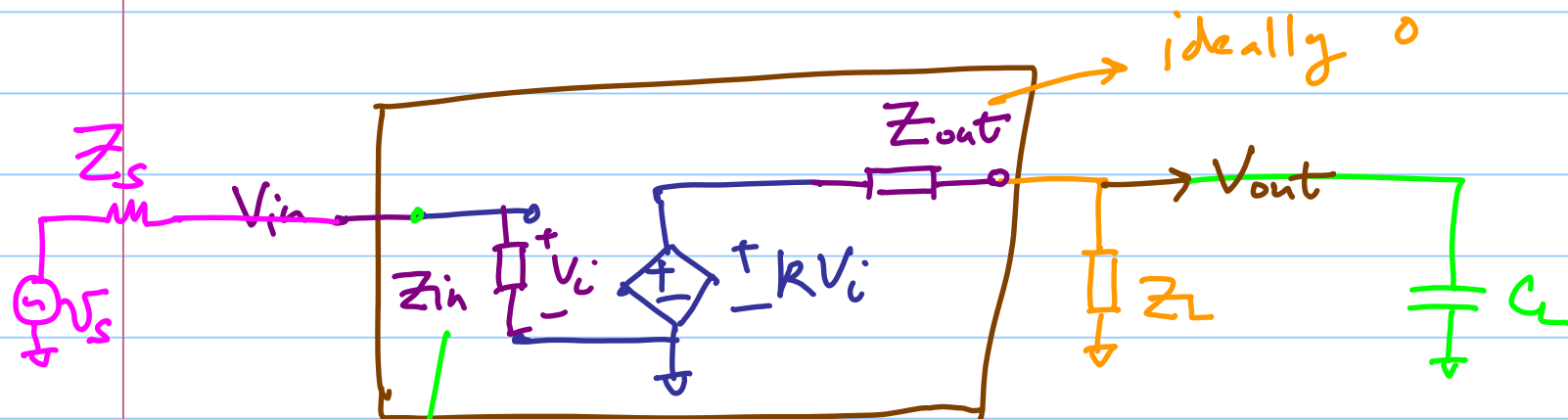
Voltage Buffer ($VCVS, \overset{k}{\text{gain}}=1$)





$Z_{in} \rightarrow \infty$

$$\omega_{3dB} = \frac{1}{R_{out} C_L}$$



$$\approx \frac{g_m}{C_L}$$

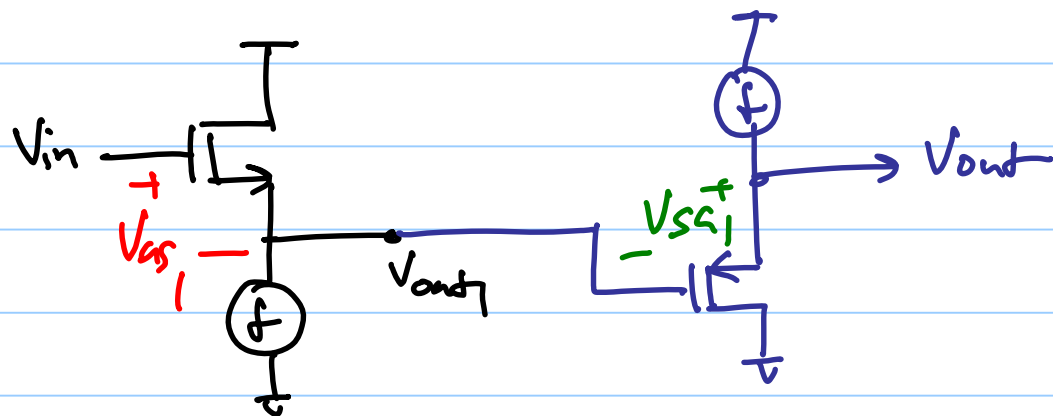

Common-Gate Stage

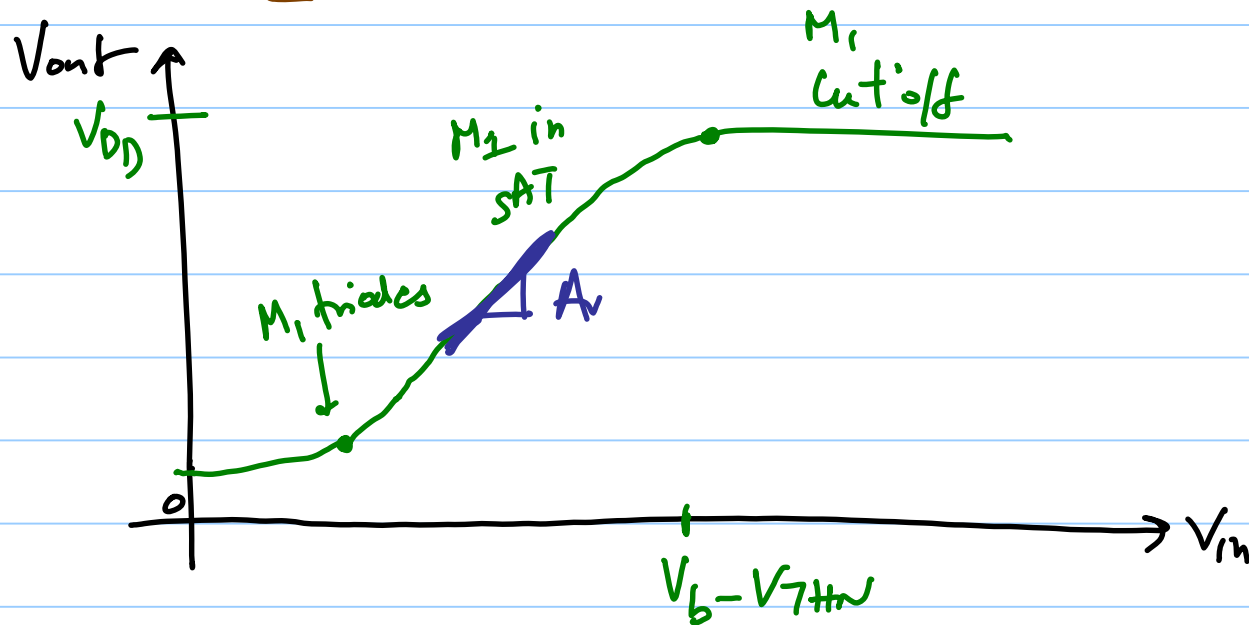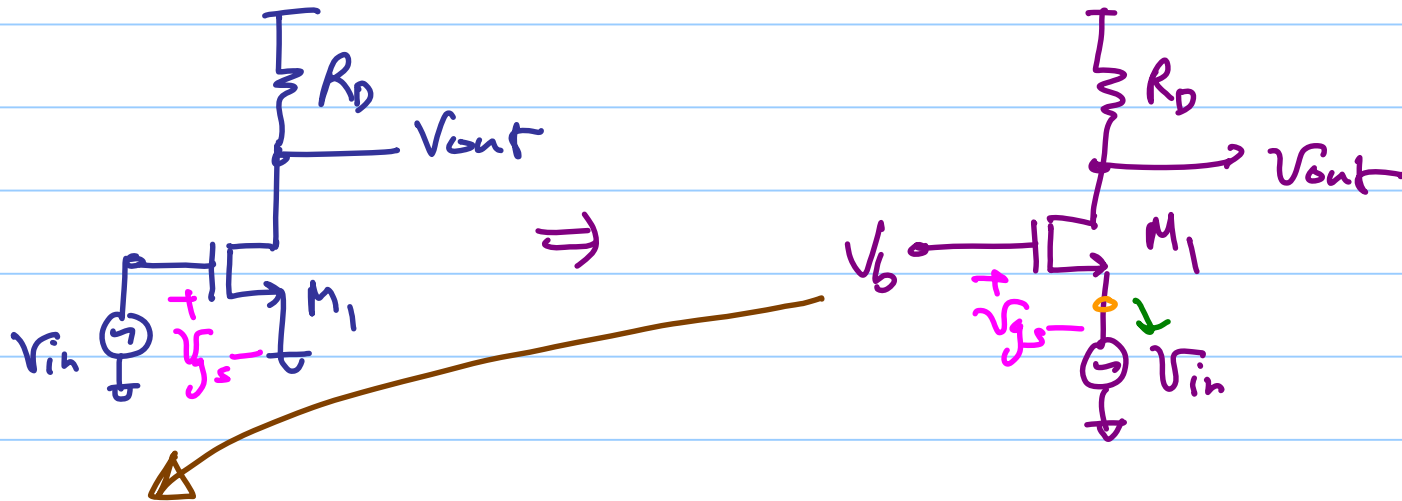

MMIC

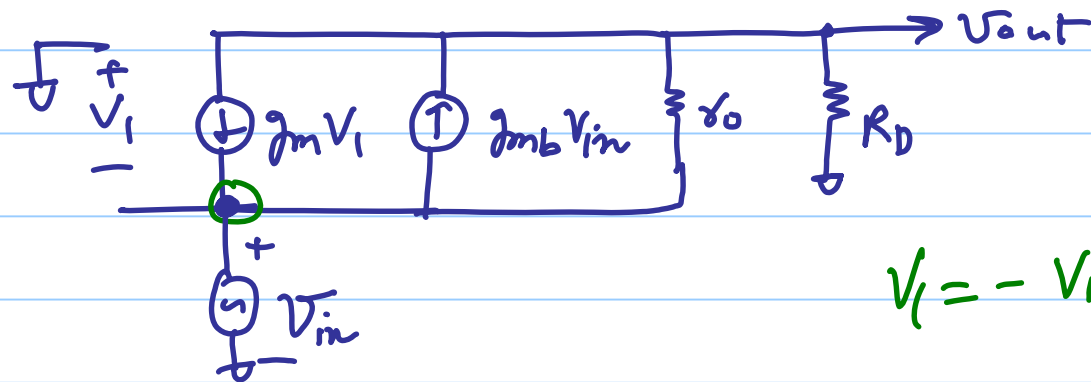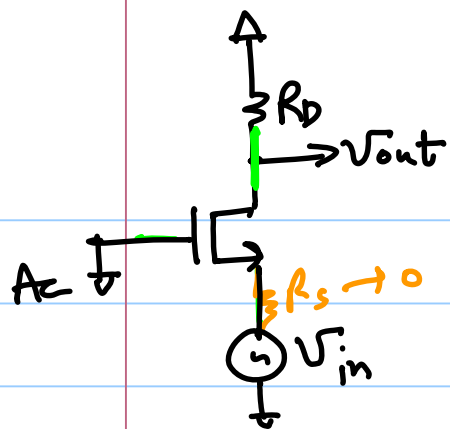

$$V_1 = -V_{in}$$

ka

$$-g_m V_1 + g_{mb} V_{in} - \frac{(V_{out} - V_{in})}{r_o} - \frac{V_{out}}{R_D} = 0$$

$$V_{in} \left[\frac{1}{r_o} + g_m + g_{mb} \right] = \frac{V_{out}}{r_o} + \frac{V_{out}}{R_D} = V_{out} \left(\frac{1}{r_o || R_D} \right)$$

$$A_v = \frac{V_{out}}{V_{in}} = \left[(g_m + g_{mb}) + \frac{1}{r_o} \right] \cdot (R_D || r_o)$$

$$= \frac{(g_m + g_{mb}) r_o + 1}{r_o} \cdot \frac{R_D \cdot r_o}{R_D + r_o}$$


$$= \frac{((g_m + g_{mb})r_o + 1) \cdot R_D}{R_D + r_o}$$

for $r_o \gg R_D$ & $g_m r_o \gg 1$


$$\rightarrow \frac{(g_m + g_{mb}) \cancel{r_o} \cdot R_D}{\cancel{r_o}}$$

$$A_v = (\eta + 1) g_m R_D$$

the gain

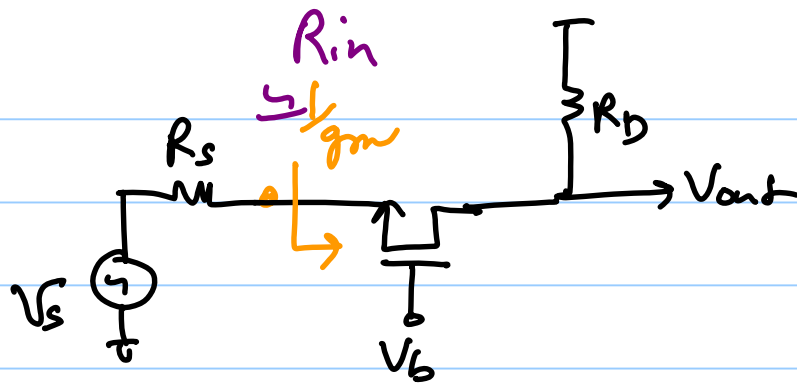

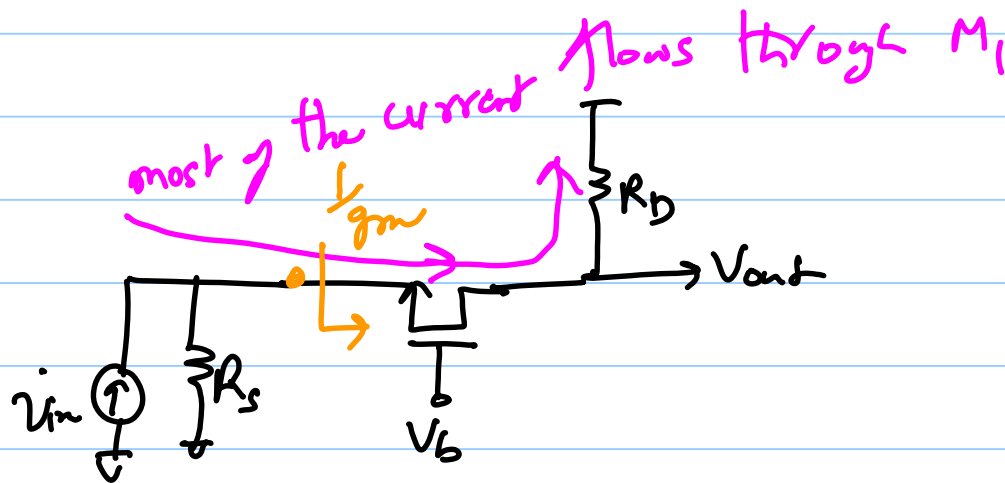
issues as a voltage amplifier due to low R_{in}



C_G
Acts as a good current buffer


↳ preferred as an amplifier if the input is small signal current.

Ex.

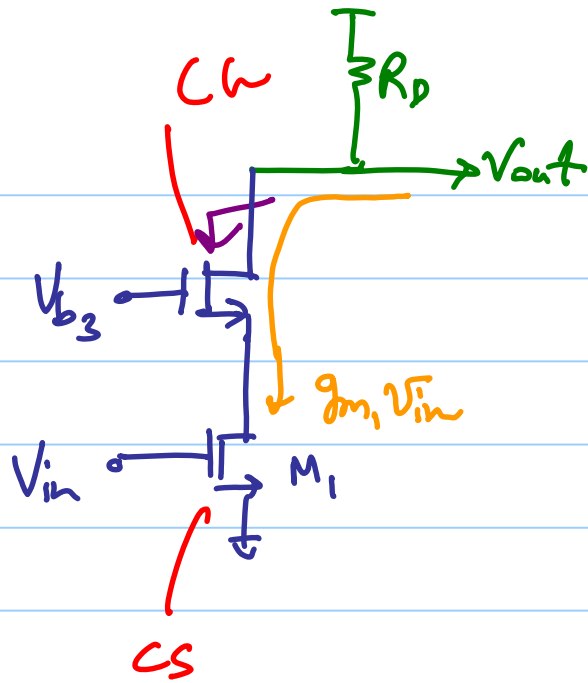


$$V_{out} = -g_{m1} V_{in} \left(R_D \parallel g_{m2} r_{o2}^2 \right)$$

$\uparrow$
 $g_{m2} r_{o2}^2$

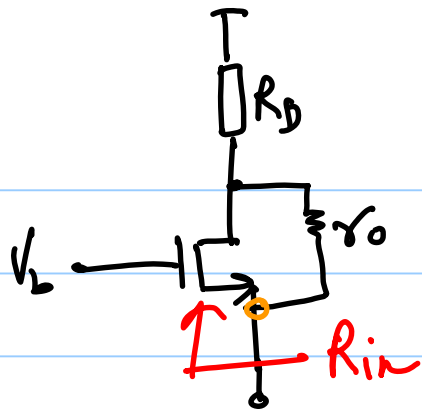

$$\gamma \neq 0$$

$$V_i = -V_x$$

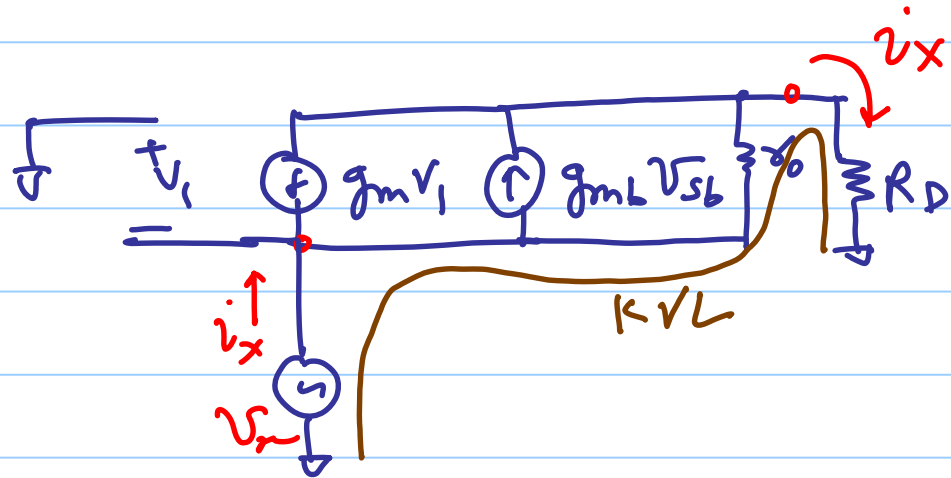

current thru r_o :

$$i_x + g_m V_i + g_{mb} V_i = i_x - (g_m + g_{mb}) V_x$$

adding up the voltages across r_o & R_D

$$V_x = R_D i_x + r_o [i_x - (g_m + g_{mb}) V_x]$$

$$R_{in} = \frac{v_x}{i_x} = \boxed{\frac{R_D + r_o}{1 + (g_m + g_{m3})r_o}}$$

Case (A)

$$R_D = 0, \quad g_m r_o \gg 1$$

$$R_{in} \simeq \frac{1}{g_m + g_{m3}}$$