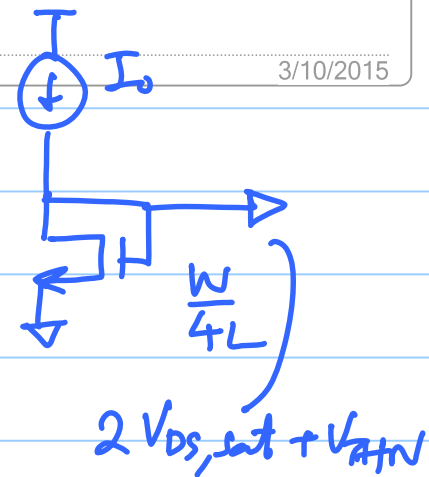


### Note Title


3/10/2015


$$\rightarrow 3V_{DS,sat} + V_{THN}$$


$$V_{DS} = V_{DS,sat} + V_{gate} - 2V_{DS,sat}$$
$$= V_{gate} - V_{DS,sat} > V_{DS,sat} \text{ for Saturation}$$

$$V_{THN} > 2V_{DS,sat}$$

$$400 \text{ mV} > 160 \text{ mV}$$

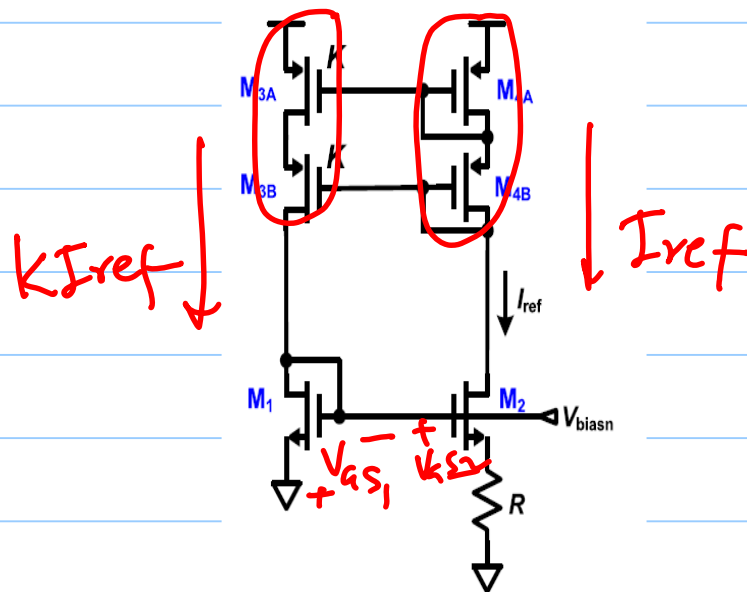
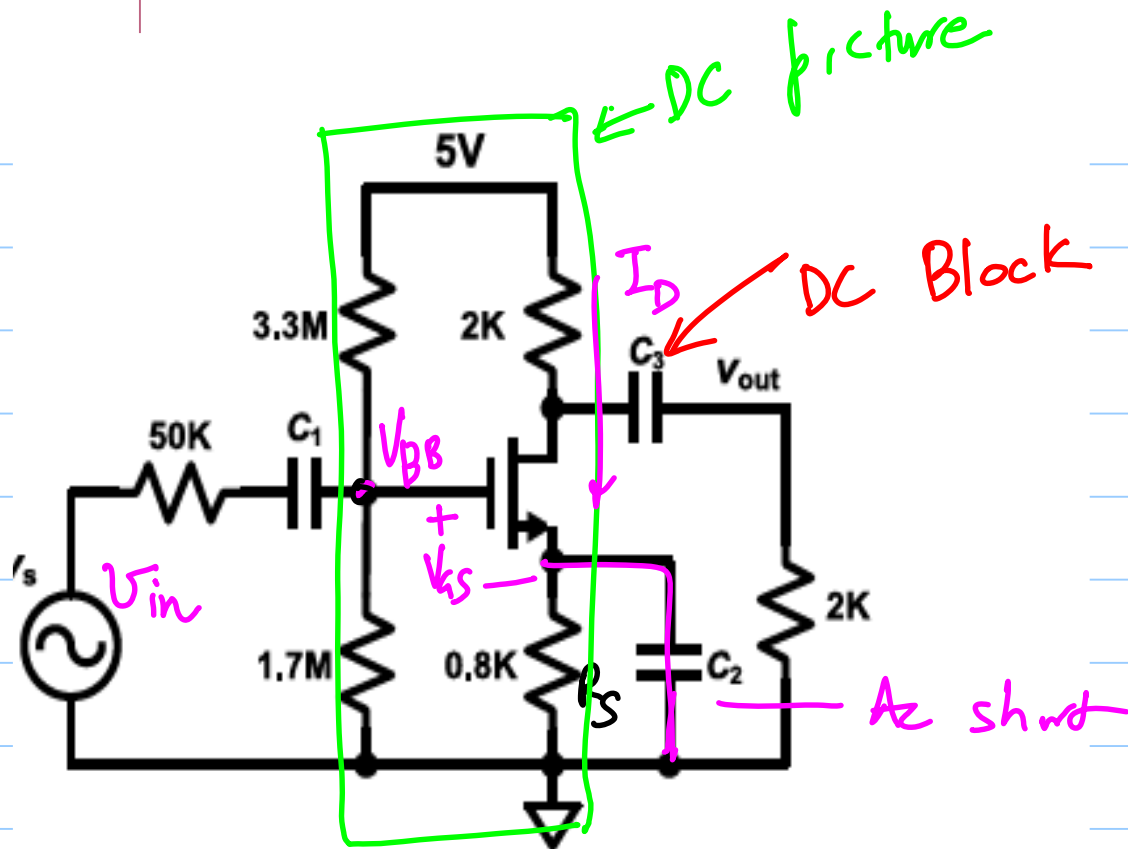
$$I_{ref} = \frac{2}{\beta R^2} (\sqrt{k} - 1)^2$$




$$V_{BB} = 1.7V$$


$$V_{as} = V_{BB} - I_D R_s \rightarrow (1)$$

$$I_D = \frac{k_p}{2} \frac{W}{L} (V_{as} - V_{THN})^2 \rightarrow (2)$$


Figure 2

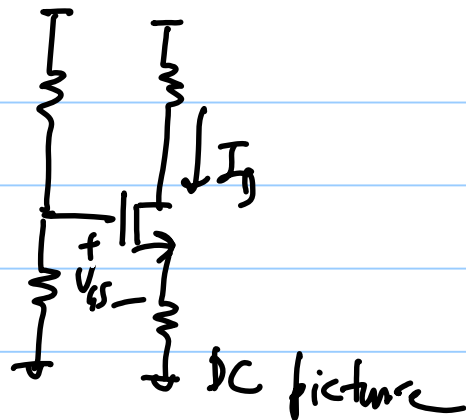

Ac picture

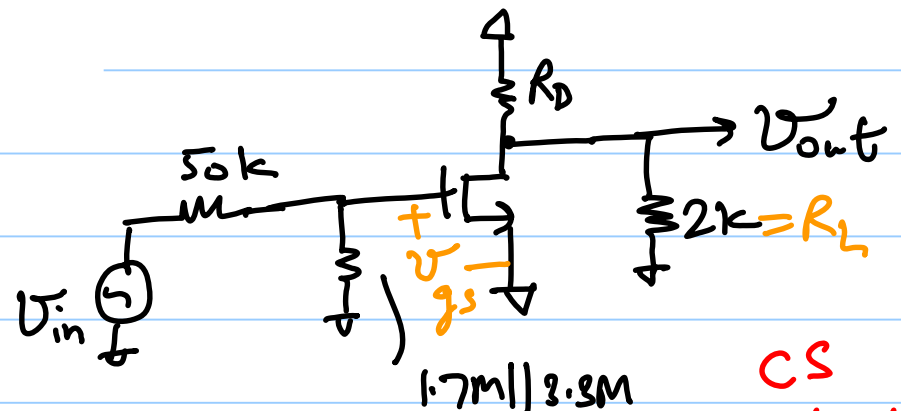

CS Amplifier

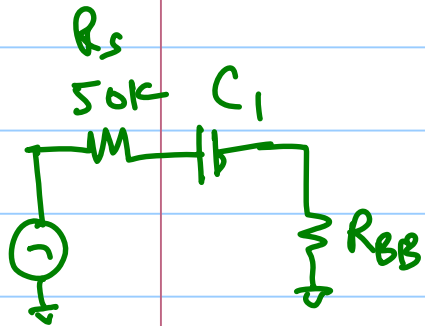

$$\tau = (R_{BB} + R_s) C_1$$

$$\omega_{x_1} = \frac{1}{(R_{BB} + R_s) C_1} < \frac{\omega_{in}}{10}$$



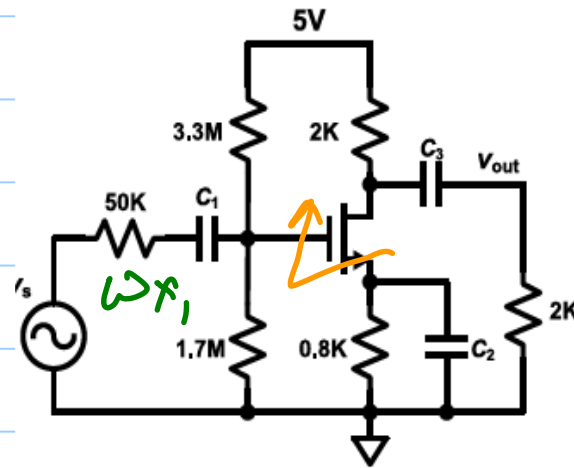


Figure 2

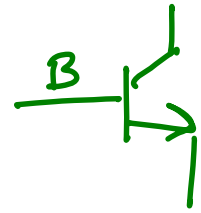

$$R_{BB} = 3.3M \parallel 1.7M$$

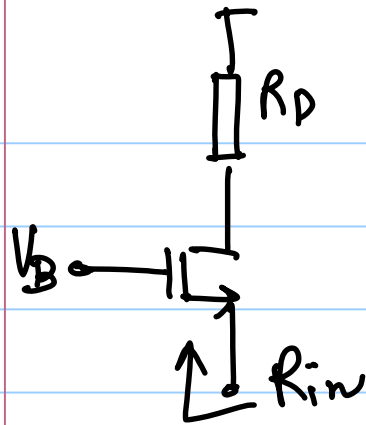

$$R_{in} \simeq \frac{R_D + r_o}{1 + (g_m + g_{mb})r_o}$$

(a)  $R_D = 0$ ,  
(SF case)

$$R_{in} = \frac{1}{g_m + g_{mb}} \simeq \frac{1}{g_m}$$

(b)  $R_D = r_o$

$$R_{in} \simeq \frac{2r_o}{(g_m + g_{mb})r_o} = \frac{2}{g_m + g_{mb}} \simeq \frac{1}{g_m}$$


(c)  $R_D = g_m r_o^2$   
(cascode CM)  
load

$$R_{in} \simeq \frac{g_m r_o^2 + r_o}{(g_m + g_{mb})r_o} = \frac{g_m r_o}{g_m + g_{mb}} \\ = \frac{r_o}{(1 + \eta)} \simeq \text{of the order of } r_o$$

| Amplifier | gain     | $Z_{in}$                    | $Z_{out}$                                              |
|-----------|----------|-----------------------------|--------------------------------------------------------|
| CS        | Large    | $\infty$                    | Moderate $\rightarrow$ "gain" Amplifier                |
| CS + SD   | Moderate | $\infty$                    | High $\rightarrow$ linear amp                          |
| CD / SF   | $< 1$    | $\infty$                    | low $\approx \frac{1}{g_m} \rightarrow$ Voltage Buffer |
| CG        | Moderate | low $\approx \frac{1}{g_m}$ | Moderate/high $\rightarrow$ Current Buffer             |

Small-signal, low-frequency gain

# Cascode Stage

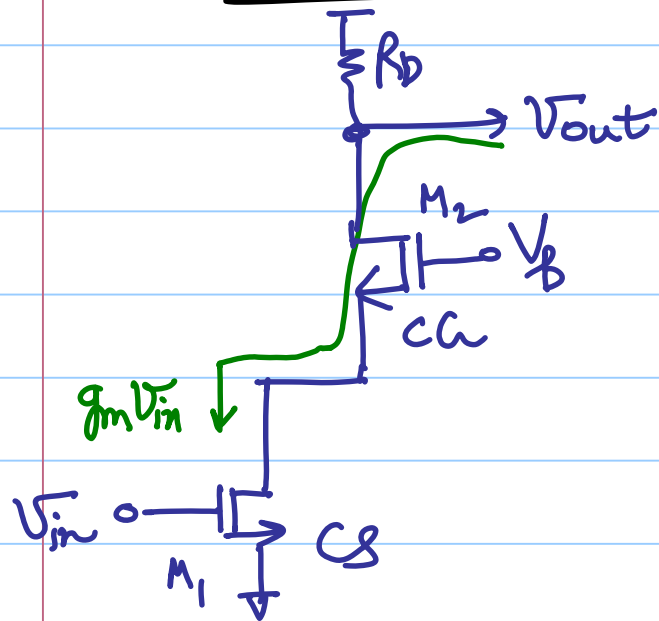

$$V_{out} = -g_m V_{in} (R_D \parallel g_m r_o^2)$$

$$A_v = -g_m (R_D \parallel g_m r_o^2)$$

↑  $g_m r_o^2$

### Lemma:

In a linear circuit Voltage gain  $= -g_m R_{out}$


where,

$g_m \rightarrow$  transconductance of the circuit when the output is shorted to ground

&  $R_{out} \rightarrow$  output resistance of the circuit when the input is at zero.




# Cascode Amplifier

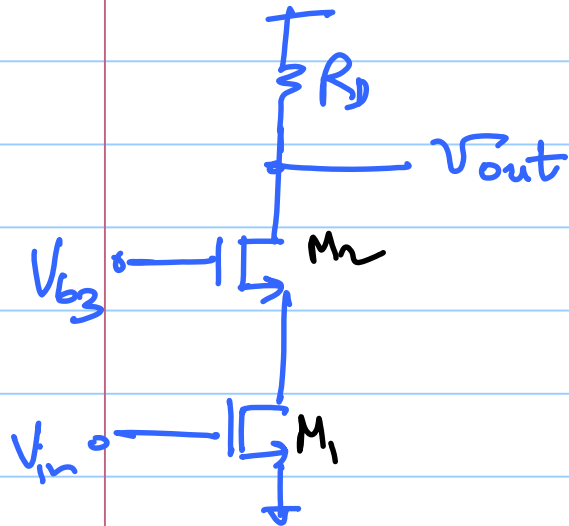

$$R_{out} = R_D || (g_{m2} r_{o1})$$

$$A_v = -g_{m1} R_{out}$$

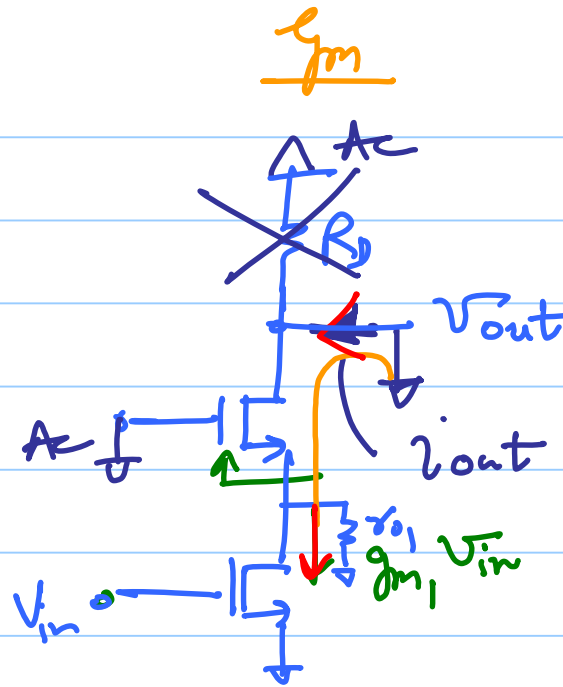


$$g_m \triangleq \frac{i_{out}}{v_{in}}$$

assume most of the current is relayed  
by  $M_2$

$$i_{out} = g_{m1} v_{in}$$

$$\Rightarrow \boxed{g_m = g_{m1}}$$

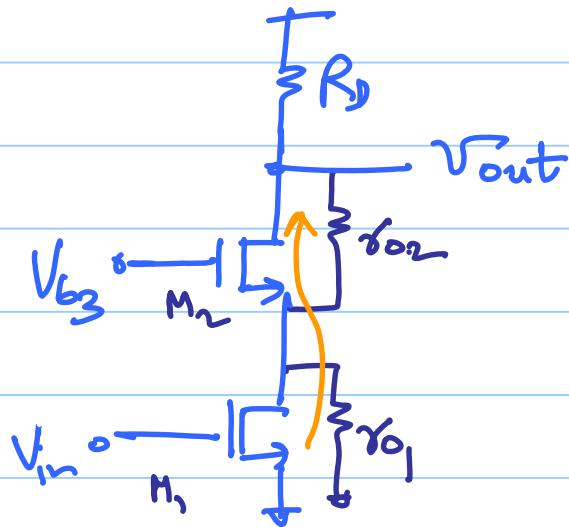→ See Textbook for more accurate analysis






$$A_{gm} = \frac{g_{m1} r_{o1} [r_{o2} (g_{m2} + g_{m2r}) + 1]}{r_{o1} r_{o2} (g_{m2} + g_{m2r}) + r_{o1} + r_{o2}}$$

$$g_{m2} r_{o2} \gg 1$$


$$\approx g_{m1}$$


# Cascode

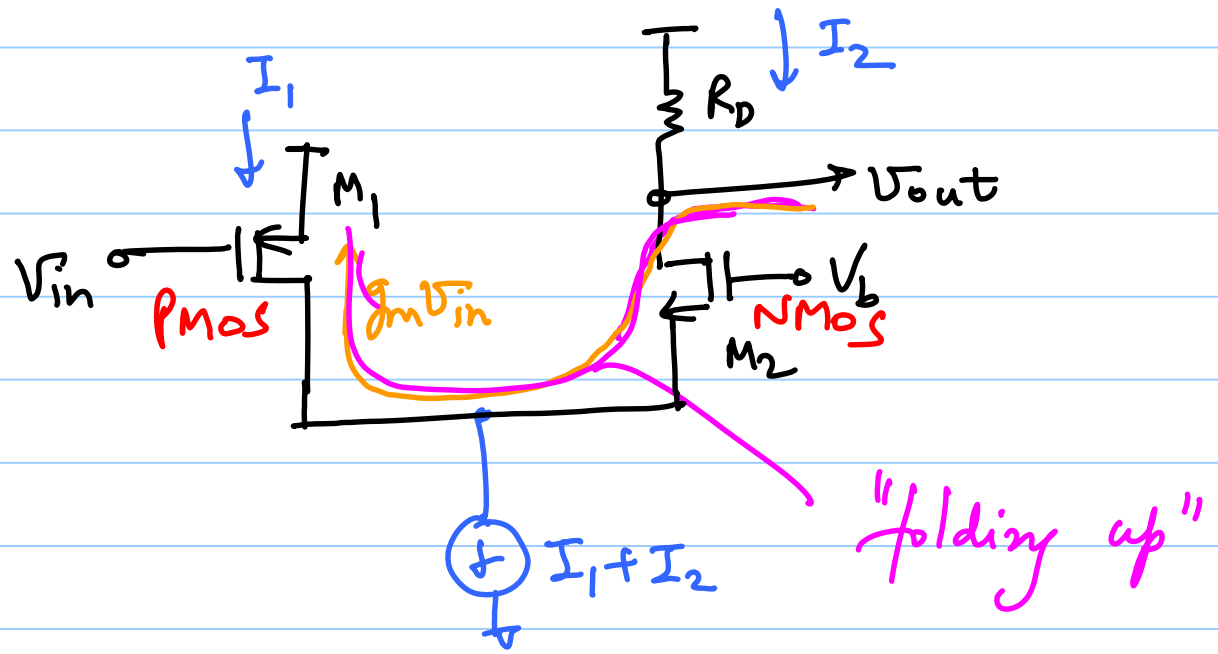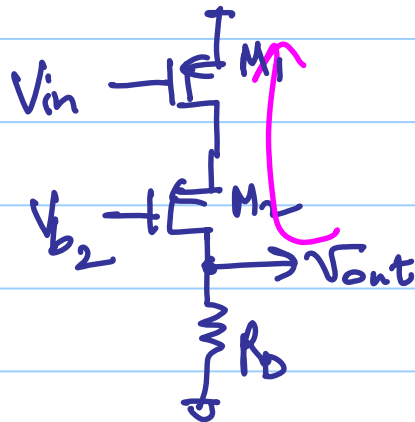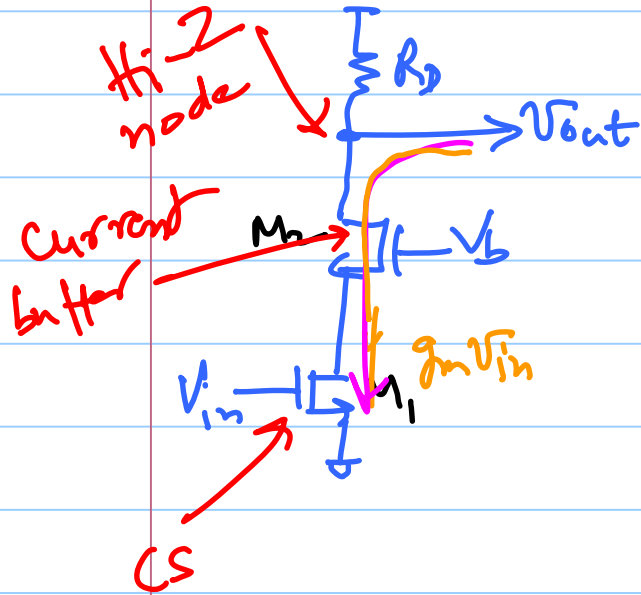


"folded cascode"

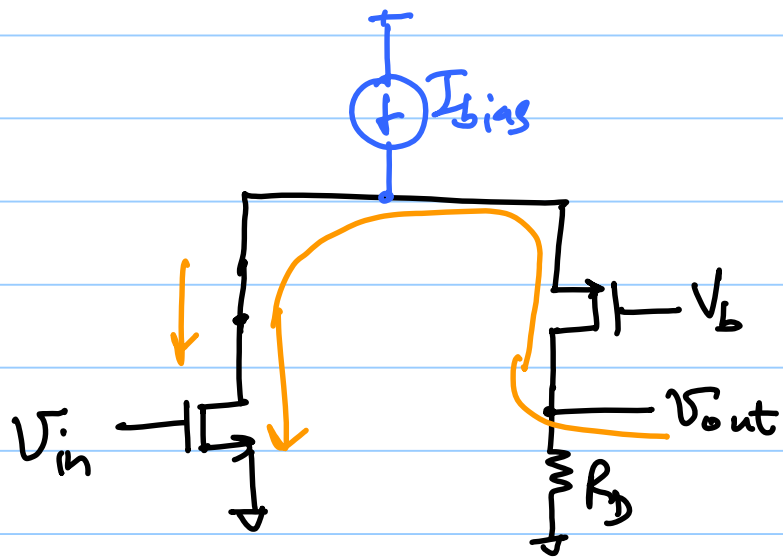- (+) leads to better headroom
- (-) 2x bias current




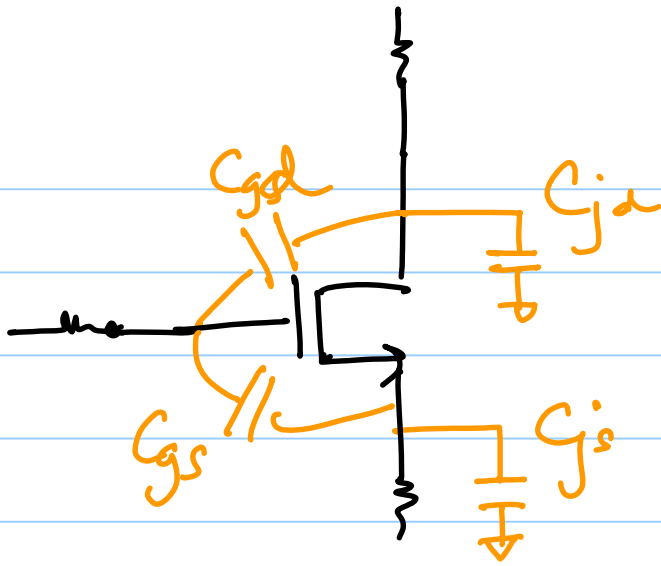

## Miller Effect:

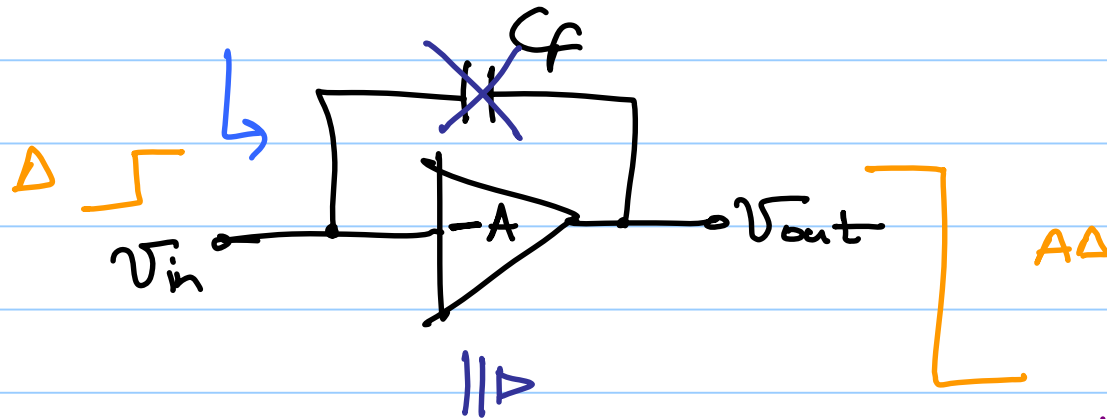


Capacitance multiplying effect

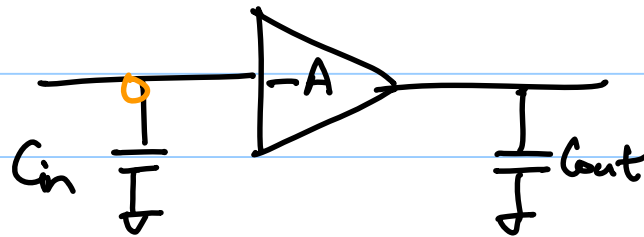


$$C_{in} = C_f (1 + |A|)$$


$$C_{out} = C_f \left(1 + \frac{1}{|A|}\right)$$

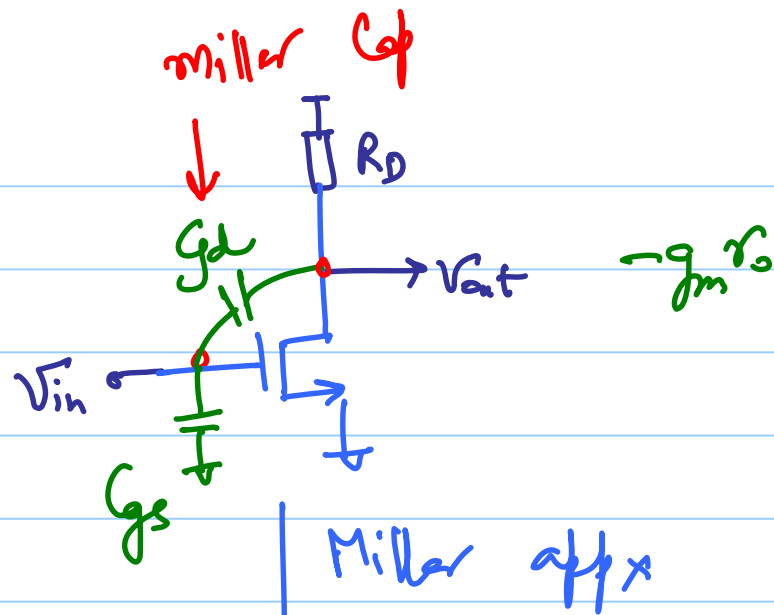

Miller appx omits a zero

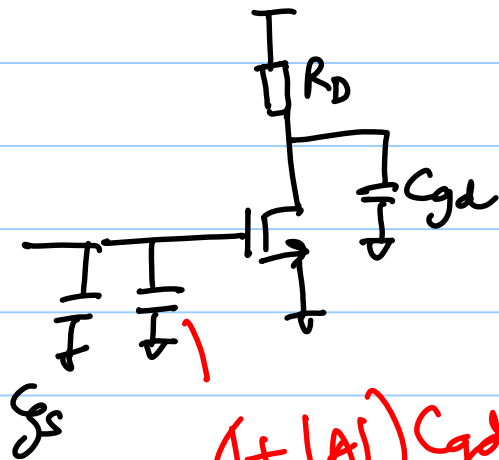


$(1 + |A|) C_{gd}$   $g_m (r_o \parallel R_D)$

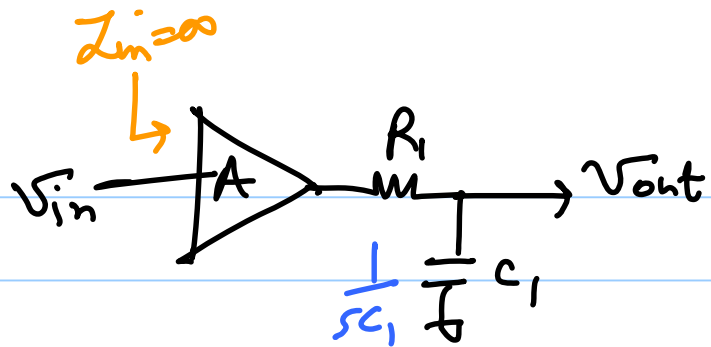

1st order

$$\frac{V_{out}}{V_{in}}(s) = \frac{A}{1 + sR_1C_1} = \frac{A}{1 + (s/\omega_p)}$$

$\omega_p = \frac{1}{R_1C_1}$

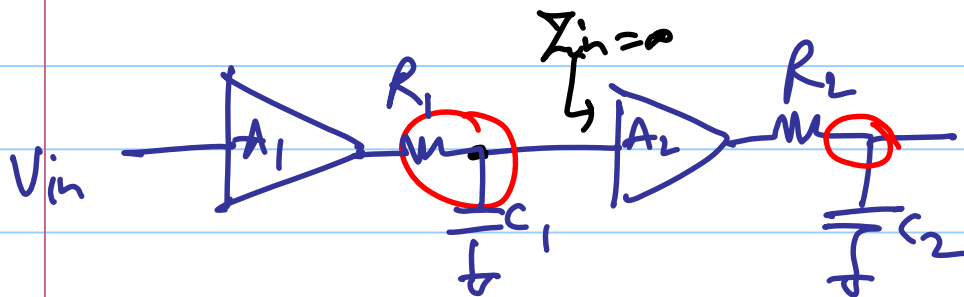

$$\frac{V_{out}}{V_{in}}(s) = \frac{A_1}{\left(1 + \frac{s}{\omega_{p1}}\right)} \cdot \frac{A_2}{\left(1 + \frac{s}{\omega_{p2}}\right)}$$



