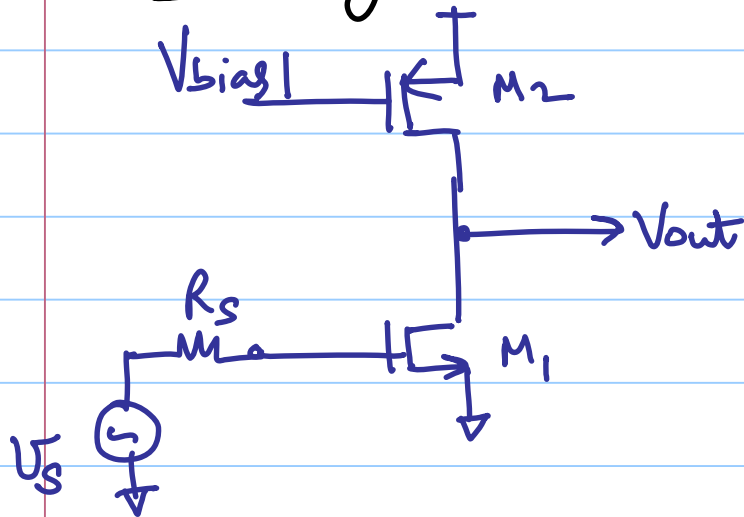


ECE 511 - Lecture 16


Note Title


3/12/2015

CS stage




Exact Biasing (Simulation)

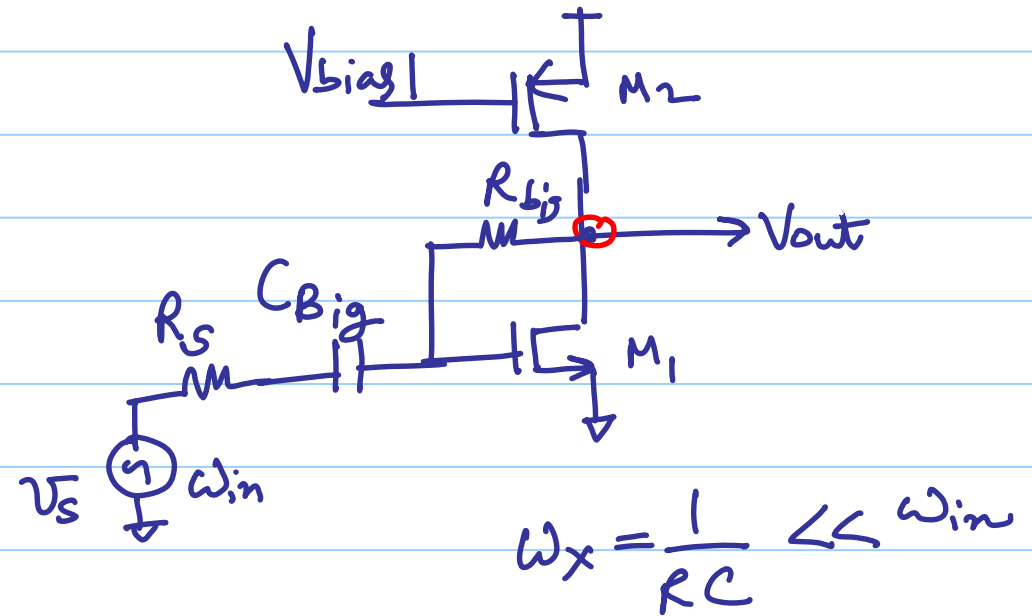

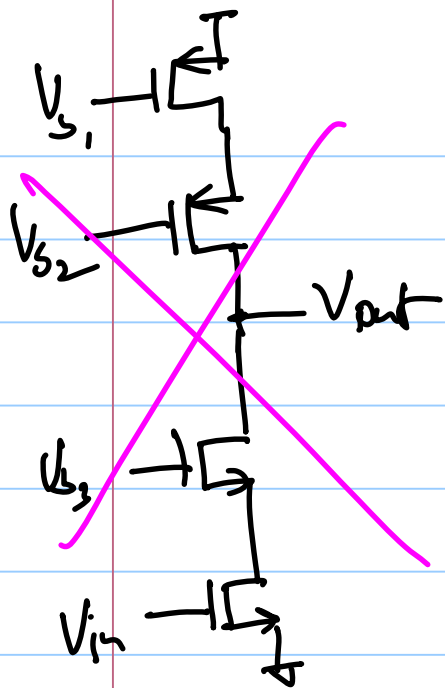

Az picture with parasitic caps

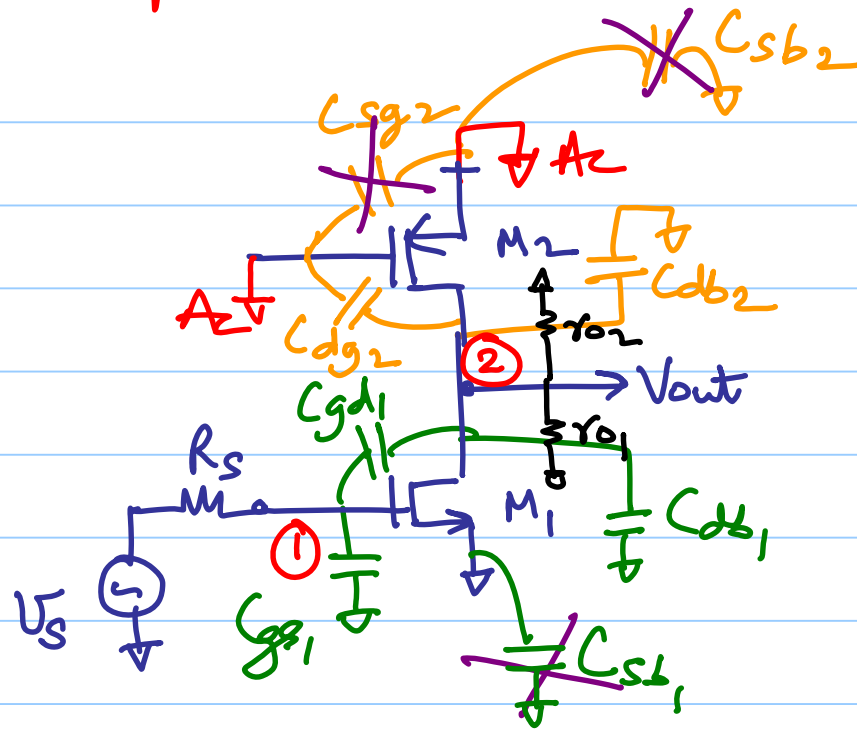

low-frequency (DC)

gain


$$A_v = -g_{m1} (r_{o1} || r_{o2})$$

"Grounded caps"


$C_{gs1}, C_{db1}, C_{dg2}, C_{db2}$

$C_{gd1} \Rightarrow$ between input & output
(Miller Cap)

After Miller Simplification

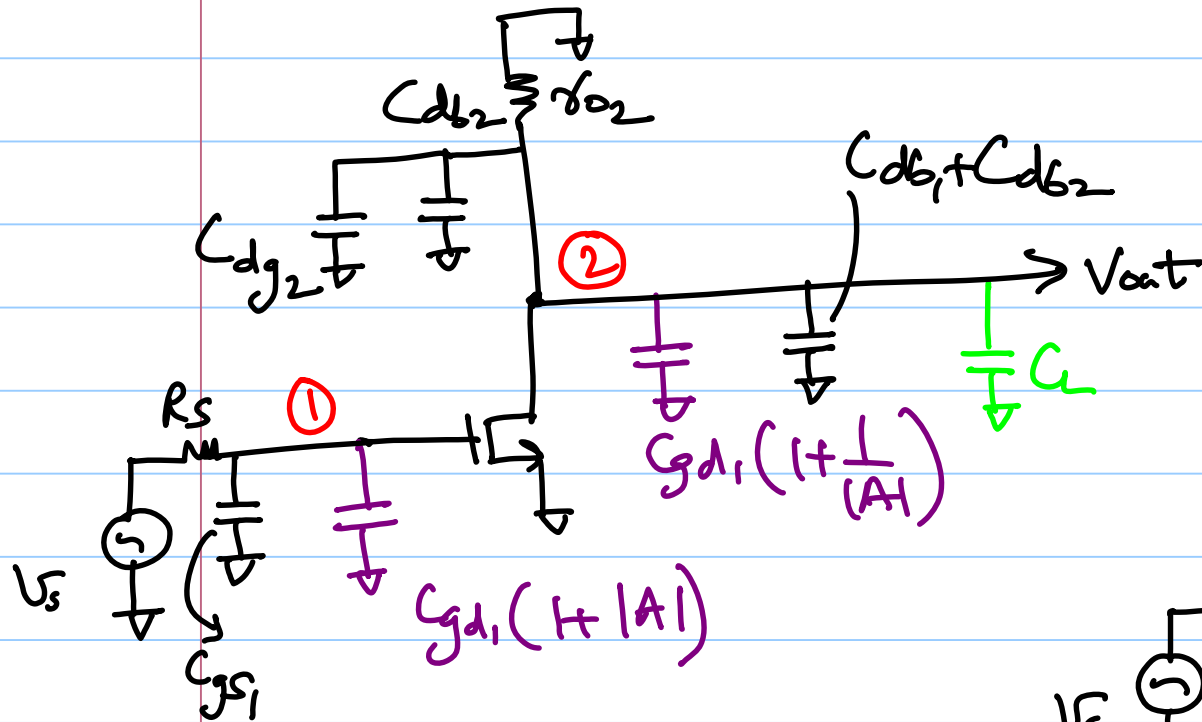

$$V_{gs} = \frac{V_s}{1 + sR_sC_{in}}$$

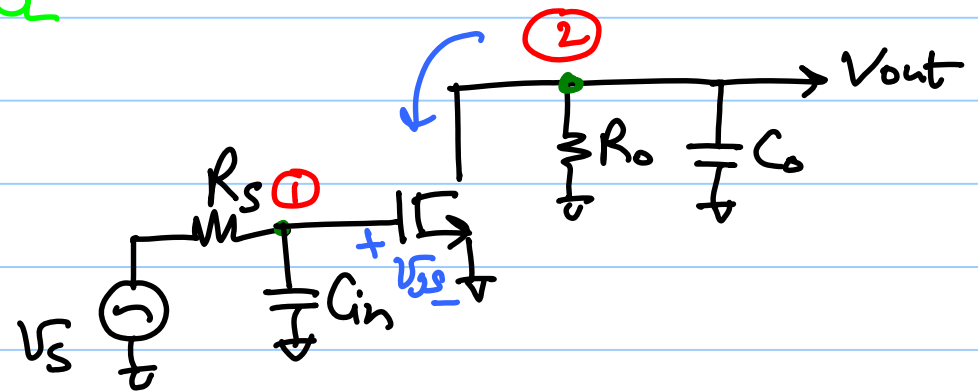

$$R_o = r_{o1} || r_{o2}$$

$$C_{in} = C_{gs1} + C_{gd1}(1+|A|)$$

$$C_o = C_{gd1}\left(1 + \frac{1}{|A|}\right) + \underbrace{C_{db1} + C_{db2}}_{C_{db}}$$


$$V_{out} = i_d \left(R_o \parallel \frac{1}{sC_o} \right) = - \frac{R_o}{(1 + sR_oC_o)} \cdot g_{m1} \cdot \underbrace{\frac{v_s}{(1 + sR_sC_{in})}}_{v_{gs}}$$

$$\Rightarrow \frac{V_{out}}{v_s}(s) = \frac{-g_{m1}(r_{o1} \parallel r_{o2})}{(1 + sR_oC_o)(1 + sR_sC_{in})}$$

$$\boxed{\frac{V_{out}}{v_s}(s) = \frac{A_v}{\left(1 + \frac{s}{\omega_{p1}}\right)\left(1 + \frac{s}{\omega_{p2}}\right)}}$$


$$\omega_{p1} = \frac{1}{R_sC_{in}} = \frac{1}{R_s[C_{gs1} + (1 + |A|)C_{gd1}]}$$
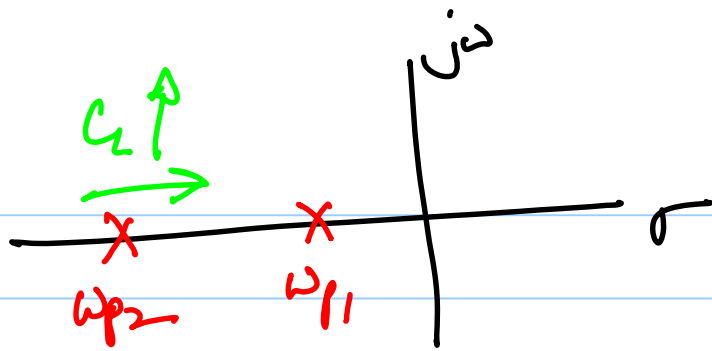
$$\omega_{p2} = \frac{1}{R_oC_o} = \frac{1}{(r_{o1} \parallel r_{o2})(C_{gd1} + C_L)}$$



This analysis misses a zero (ω_z)

Equivalent Circuit

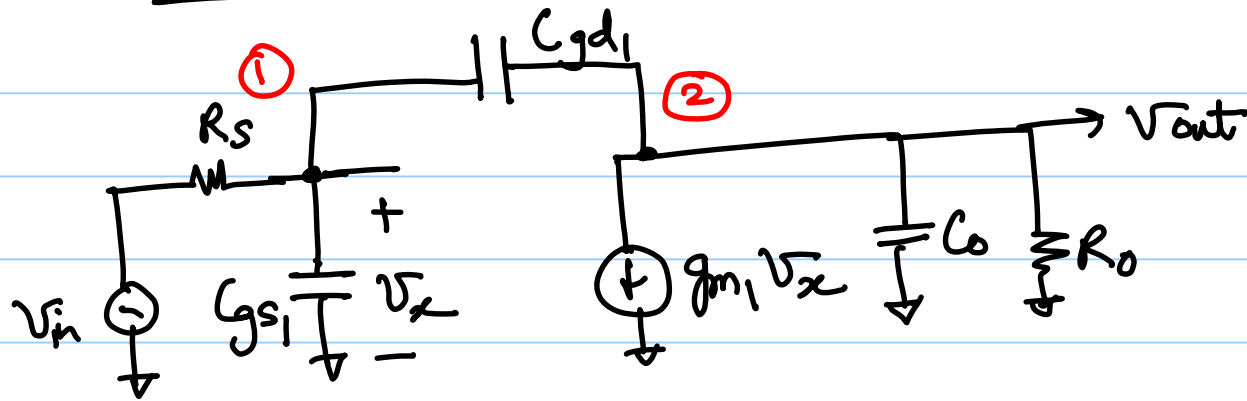

$$R_o = r_{o1} \parallel r_{o2}$$
$$C_o = C_{db} + C_{dg2}$$

① $\Rightarrow \frac{v_x - v_{in}}{R_S} + v_x C_{gs1} s + (v_x - v_{out}) C_{gd1} s = 0$

② $\Rightarrow (v_{out} - v_x) C_{gd1} s + g_{m1} v_x + v_{out} \left(\frac{1}{R_o} + C_o s \right) = 0$

Solve for v_x & substitute in ②

$$v_x = \frac{-v_{out} \left(C_{gd1} s + \frac{1}{R_o} + s C_o \right)}{g_{m1} - s C_{gd1}}$$

$$\Rightarrow \frac{V_{out}}{V_{in}}(s) = \frac{(sC_{gd1} - g_{m1})R_o}{R_s R_o \xi s^2 + [R_s(1 + g_{m1}R_o)C_{gd1} + R_s C_{gs1} + R_o(C_{gd1} + C_o)]s + 1}$$

$\xi = C_{gs1}C_{gd1} + C_{gs1}C_o + C_{gd1}C_o$

g^{nd} -order transfer function

$$N(s) = 0$$

$$\Rightarrow sC_{gd1} - g_{m1} = 0$$

$$s = \frac{g_{m1}}{C_{gd1}}$$


R.H.P. zero

$$\Rightarrow \omega_z = + \frac{g_{m1}}{C_{gd1}} \quad \leftarrow \text{T.F. zero}$$

$$f_z = \frac{g_{m1}}{2\pi C_{gd1}}$$

Assume that the poles are real and far apart

$$|\omega_{p1}| \ll |\omega_{p2}|$$

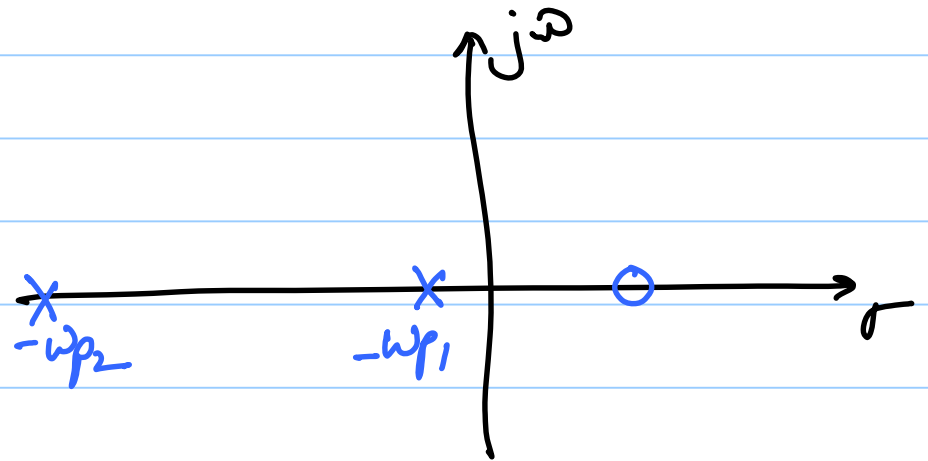

$$D(s) \triangleq \left(\frac{s}{\omega_{p1}} + 1 \right) \left(\frac{s}{\omega_{p2}} + 1 \right)$$

$$= \frac{s^2}{\omega_{p1}\omega_{p2}} + \left(\frac{1}{\omega_{p1}} + \frac{1}{\omega_{p2}} \right) s + 1$$

②

$$\text{If } \omega_{p1} \ll \omega_{p2} \Rightarrow \frac{1}{\omega_{p1}} \gg \frac{1}{\omega_{p2}}$$

Coeffⁿ of 's' term

$$\frac{1}{\omega_{p1}} + \frac{1}{\omega_{p2}} \approx \frac{1}{\omega_{p1}}$$

from ① + ②

$$\omega_{p1} = \frac{1}{R_s \left((1 + \underline{g_{m1} R_o}) C_{gd1} \right) + R_s C_{gs1} + R_o (C_{gd1} + C_o)}$$

↓
Miller term
C_{in}

↑ Extra term

This is the contribution
of node ② in ω_{p1}

$$\text{coeff of } 's^2' = \frac{1}{\omega_{p1} \cdot \omega_{p2}}$$

$$\Rightarrow \omega_{p2} = \frac{1}{\omega_{p1}} \cdot \frac{1}{R_S R_O \xi}$$

$$= \frac{1}{\omega_{p1}} \cdot \frac{1}{R_S R_O [C_{gs1} C_{gd1} + C_{gs1} C_O + C_{gd1} C_O]}$$

$$= \frac{R_S (1 + g_m R_O) C_{gd1} + R_S C_{gs1} + R_O (C_{gd1} + C_O)}{R_S R_O [C_{gs1} C_{gd1} + C_{gs1} C_O + C_{gd1} C_O]}$$

If $C_{gs1} \gg (1 + g_m R_O) C_{gd1} + \frac{R_O}{R_S} (C_{gd1} + \underline{\underline{C_O}})$
 (not always true)

$$\omega_{p2} = \frac{\cancel{R_s} \cancel{C_{gs1}}}{\cancel{R_s} R_o [\cancel{C_{gs1}} C_{gd1} + \cancel{C_{gs1}} C_o + \cancel{C_{gd1}} C_o]}$$

$$\omega_p \approx \frac{1}{R_o (C_{gd1} + C_o)}$$

valid only when
 C_{gs1} dominates the
 response
 * not always true


$$\frac{V_{out}}{V_{in}}(s) = \frac{A_v \left(1 - \frac{s}{\omega_z}\right)}{\left(1 + \frac{s}{\omega_{p1}}\right) \left(1 + \frac{s}{\omega_{p2}}\right)}$$

zero

$$\omega_z = \frac{g_{m1}}{C_{gd1}}$$

"RHP"

$$s = -\frac{g_{m1}}{C_{gd1}}$$

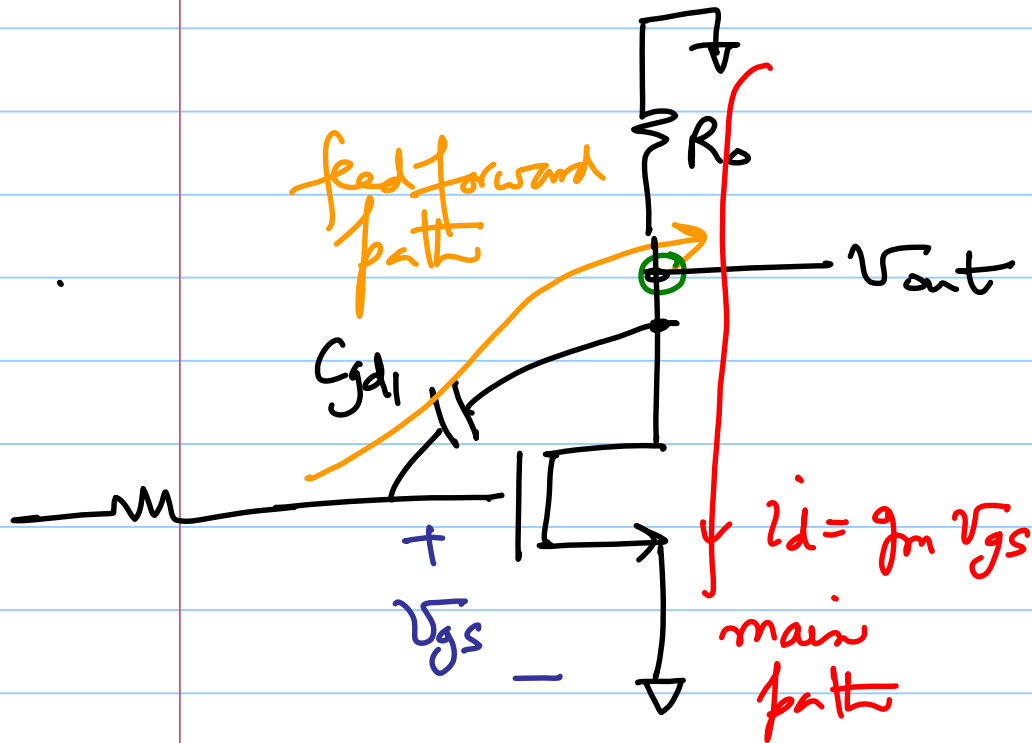


C_{gd1} provides a feedforward path that conducts the input signal to the output at high frequencies

→ signal thru C_{gd1} adds to the main path in the opposite phase

→ RHP zero

Quick Derivation of z_o

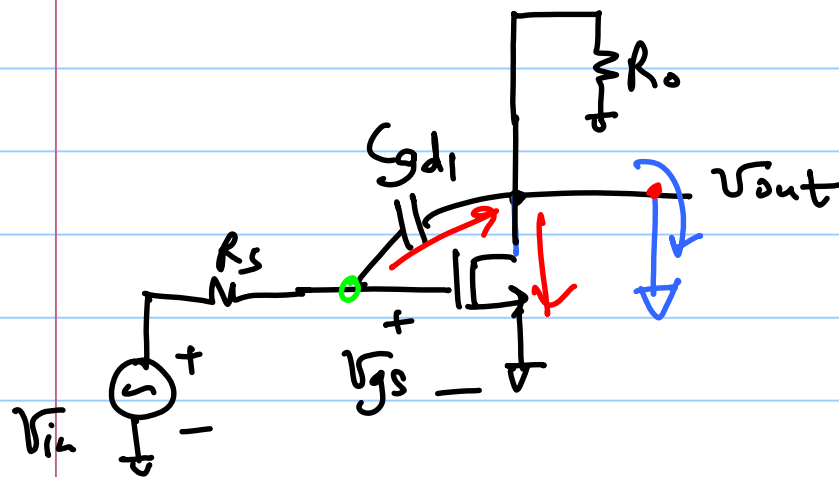

$$@ \quad s = s_z = j\omega_z$$

$$\frac{v_{out}}{v_{in}}(s) = 0$$

$$\Rightarrow v_{out}(s_z) = 0$$

$\Rightarrow$ o/p can be shorted to ground

Currents through M_1 & C_{gd1}
are equal and opposite

$$\Rightarrow v_{gs} C_{gd1} \cdot s_z = g_m v_{gs}$$

$$s_z = \frac{g_m}{C_{gd1}} \Rightarrow$$

zero

is at

$$\frac{g_{m1}}{C_{gd1}}$$

$$\frac{V_{out}(j)}{V_{in}} = \frac{\left(1 - \frac{s}{\omega_z}\right)}{D(s)}$$

$$@ s = j\omega_z$$

$$V_{out}(j\omega) = 0$$

