

ECE 511 - Lecture 17

Note Title

3/17/2015

frequency response of CS stage


Miller Cap

$$\underline{A_c}$$
$$C_c = C_{gd1}$$

$$\omega_z = \frac{g_{m1}}{C_c}$$

$$\omega_{p1} = \frac{1}{R_s [(1 + |A_v|) C_c + C_{gs1}] + R_o (C_c + C_o)}$$
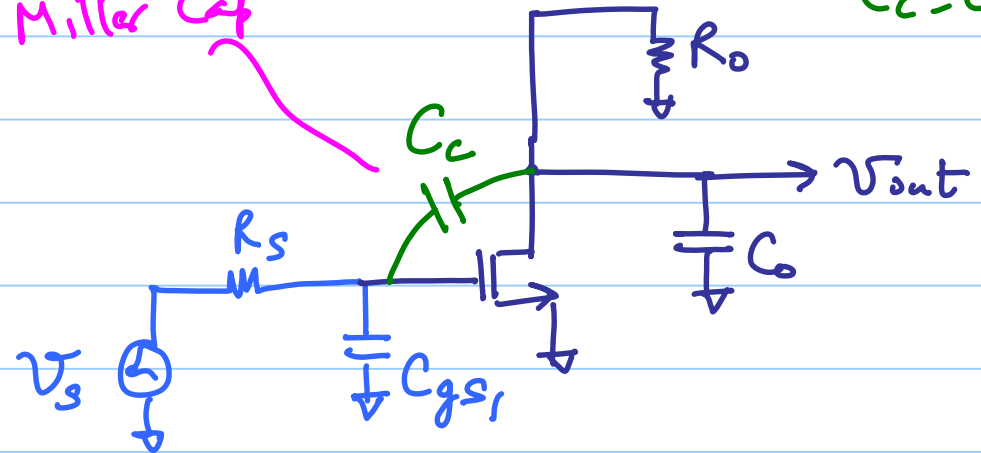
$$\omega_{p2} = \frac{R_s (1 + g_{m1} R_o) C_c + R_s C_{gs1} + R_o (C_c + C_o)}{R_s R_o [C_{gs1} C_c + C_{gs1} C_o + C_c C_o]}$$



We made an assumption

$$|\omega_{p1}| \ll |\omega_{p2}|$$

↑ Dominant pole

Sweep C_c and study


① $C_c = 0$ & large C_o

$$\omega_{p1} \approx \frac{1}{R_s C_{s1} + R_o C_o}$$

approximations

$$\omega_{p2} \approx \frac{\cancel{R_s C_{s1}} + R_o C_o}{R_s R_o \cdot C_{s1} \cdot C_o}$$

$$\approx \frac{1}{R_o C_o}$$

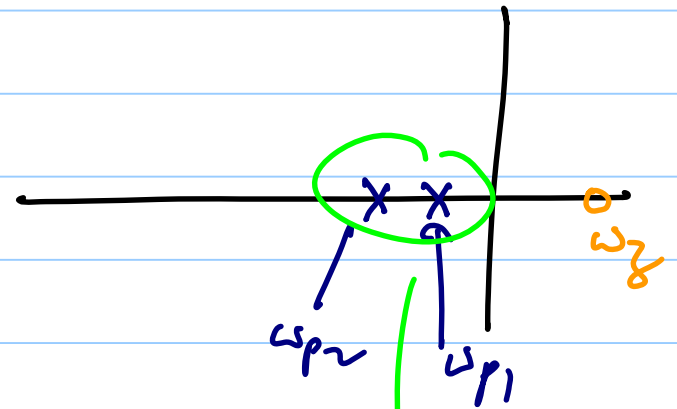

not good
for stability

* Now, increase C_c

when $C_c \gg C_{gs1}$

← adding more C_c to enhance Miller effect

$$\omega_H \approx \frac{1}{R_S(1 + (A_v)C_c + R_o(C_c + C_o))}$$


$$\omega_{p2} \approx \frac{\cancel{R_S}(1 + g_{m1}R_o)\cancel{C_c} + \cancel{R_o}(C_c + C_o)}{\cancel{R_S}R_o\cancel{C_c}[C_o + C_{gs1}]} \rightarrow \text{ignore}$$

$$\Rightarrow \frac{(1 + g_{m1}R_o)}{R_o(C_o + C_{gs1})} \Rightarrow \frac{g_{m1}}{C_o + C_{gs1}} \propto \frac{g_{m1}}{C_o}$$


	$C_c = 0$	$C_c \gg C_{gs1}$
ω_{p1}	$\approx \frac{1}{R_S C_{gs1} + R_O C_O}$	$\approx \frac{1}{R_S(1+ A)C_c + R_O[C_c + C_O]}$ $\omega_{p1} \downarrow$
ω_{p2}	$\approx \frac{1}{R_O C_O}$	$\approx \frac{g_{m1}}{C_O + C_{gs1}} \xrightarrow{\Delta} \frac{g_{m1}}{C_O} \triangleq g_{m1} R_O \left[\frac{1}{R_O C_O} \right]$ ω_{p2} is increased by $g_{m1} R_O$ $\omega_{p2} \uparrow$ $\rightarrow$ a large value
ω_z	$\frac{g_{m1}}{C_{gd1}}$	$\frac{g_{m1}}{C_c}$ $\omega_z \downarrow$

$C_c \uparrow$

Root locus

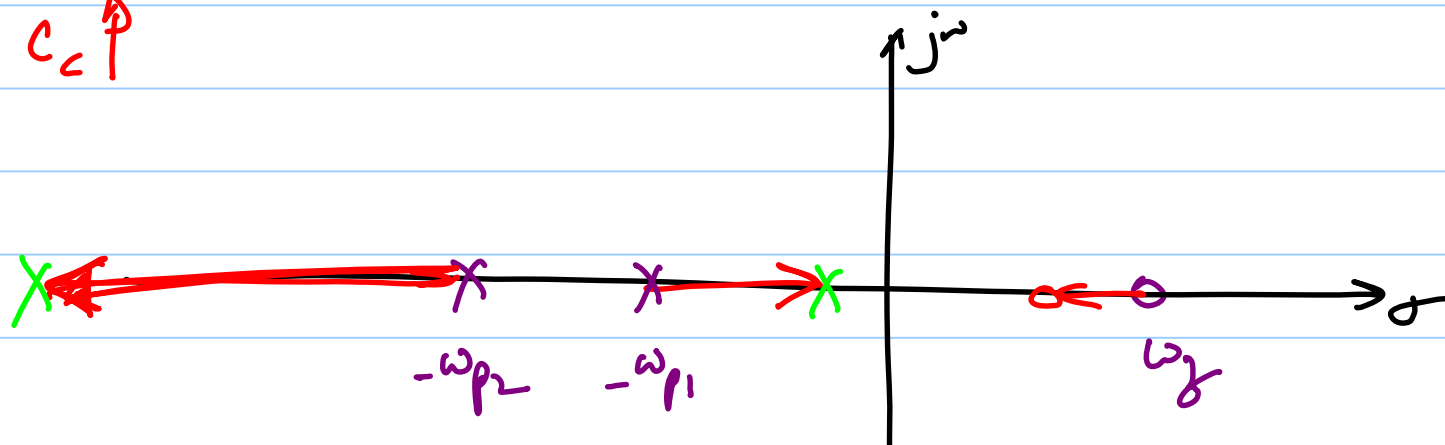



Miller Compensation

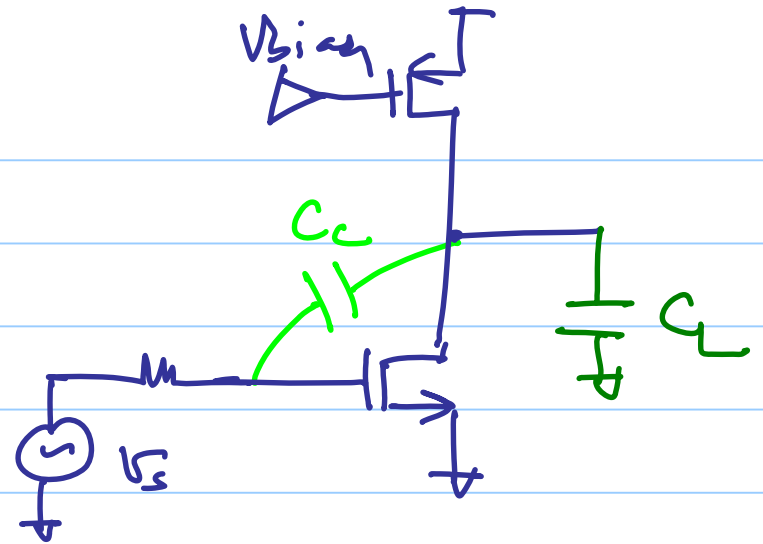


$C_c \uparrow$
 $\omega_{p1} \downarrow$
 $\omega_{p2} \uparrow$ by a large factor

↳ "Pole splitting"

$$C_o \gg C_c$$

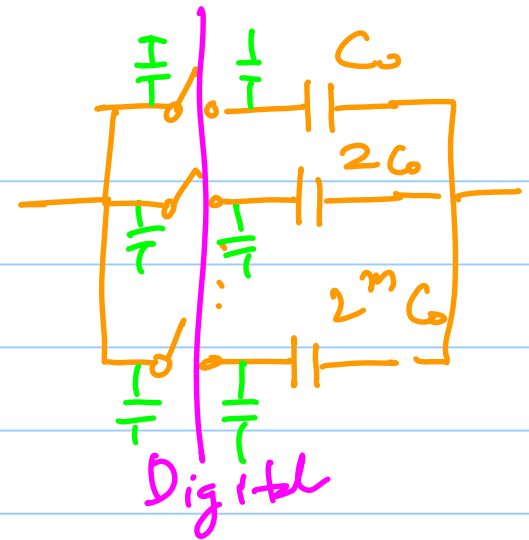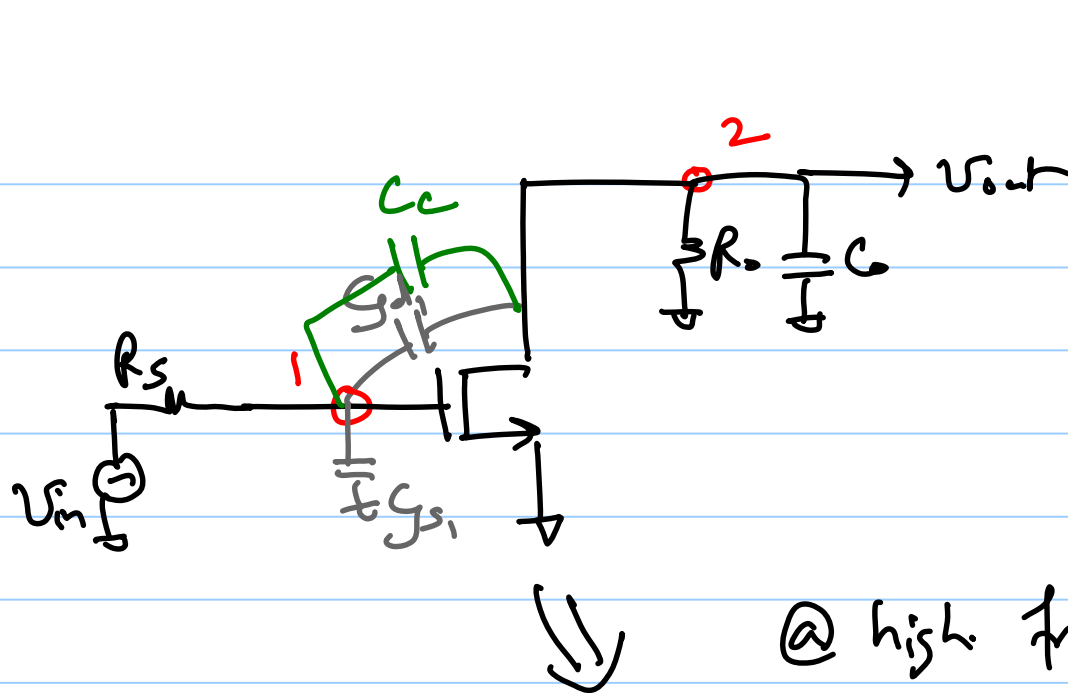


@ high frequencies C_c shorts

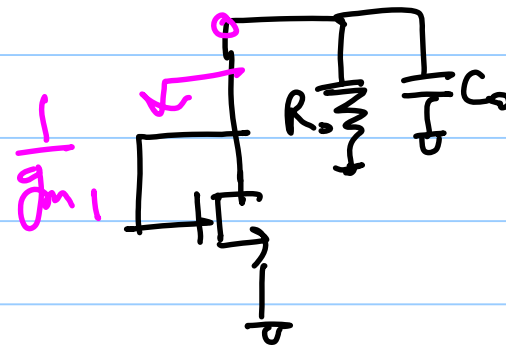

$$\omega_2 \approx \frac{1}{\frac{1}{g_{m1}} C_o} = \frac{g_{m1}}{C_o}$$

generic Model for "2nd-order" amplifier

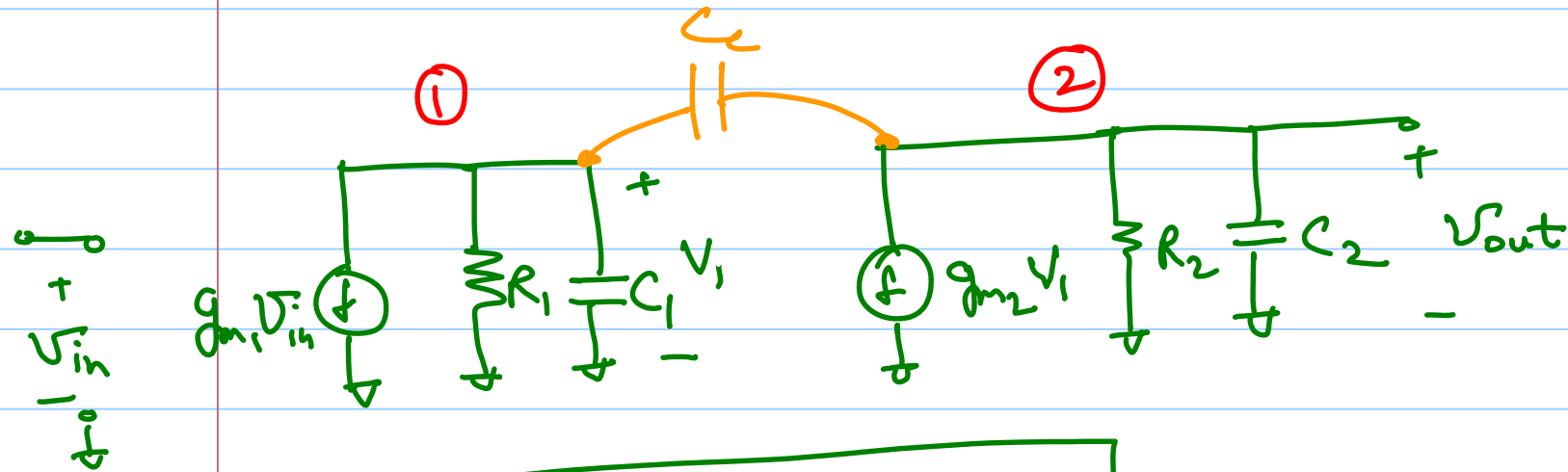

$$A_v = g_{m1}R_1 \cdot g_{m2}R_2$$

$$\omega_{p1} \approx \frac{1}{R_2(C_2 + C_c) + R_1(C_1 + C_c(1 + g_{m2}R_2))}$$

$$\omega_{p1} \stackrel{\Delta}{=} \frac{1}{g_{m2}R_2R_1C_c}$$

$$\omega_{p2} \approx \frac{g_{m2} C_c}{C_c C_1 + C_1 C_2 + C_c C_2}$$

$$\propto \frac{g_{m2}}{C_2}$$


for $C_2 \approx C_c \gg C_1$

$$\omega_z = \frac{g_{m2}}{C_c}$$

$$\omega_{un} \approx \frac{g_{m1}}{C_c}$$

where is ω_z ??

$$sC_c V_1$$

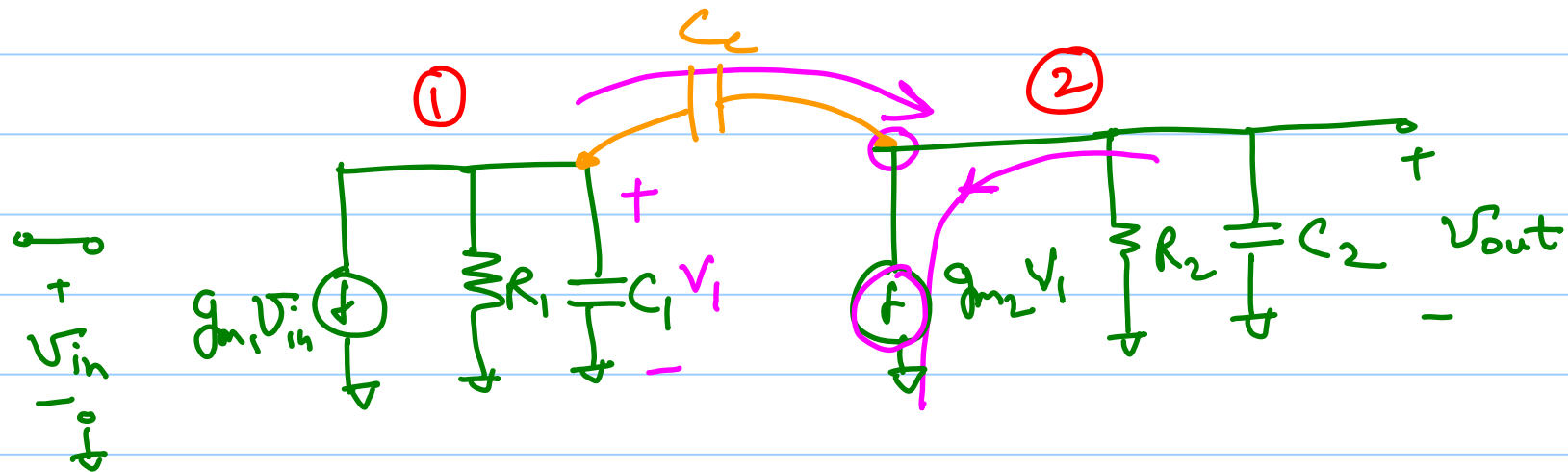

$$s_z C_c V_1 = g_{m2} V_1$$

$$s_z = \left| \frac{g_{m2}}{C_c} \right| = j\omega_z$$

$$\boxed{\omega_z \triangleq \frac{g_{m2}}{C_c}}$$

$$\frac{V_o}{V_i}(s) = A_v(s) = \frac{A_v \left(1 - \frac{s}{\omega_z}\right)}{\left(1 + \frac{s}{\omega_{p1}}\right) \left(1 + \frac{s}{\omega_{p2}}\right)}$$

RHP zero


Compensated by C_c $\Rightarrow$ pole splitting

$$\omega_{p1} \ll \omega_{p2}$$

dominant pole

$$\angle \frac{V_o}{V_i} = - \tan^{-1} \left(\frac{\omega}{\omega_z} \right) - \tan^{-1} \left(\frac{\omega}{\omega_{p1}} \right) - \tan^{-1} \left(\frac{\omega}{\omega_{p2}} \right)$$

RHP zero

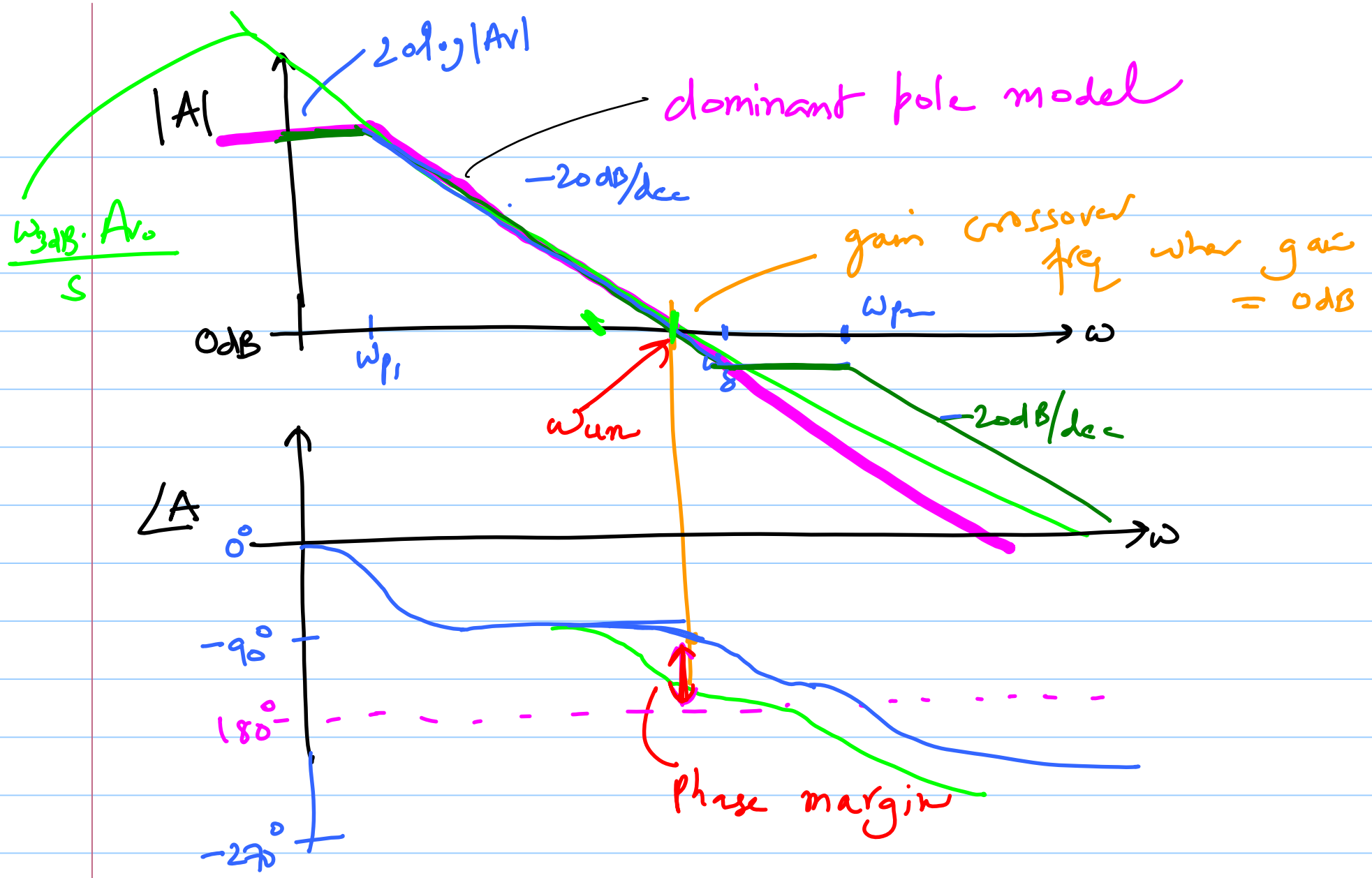

dominant pole model

$$A(s) = \frac{A_0}{\left(1 + \frac{s}{\omega_{p1}}\right)} \stackrel{\Delta}{=} \frac{A_{v0}}{\left(1 + \frac{s}{\omega_{3dB}}\right)}$$

3dB BW

$$A(s) = \frac{A_{v0}}{1 + \frac{s}{\omega_{3dB}}}$$

at frequencies $\omega \gg \omega_{3dB}$

$$1 + \frac{s}{\omega_{3dB}} \hookrightarrow \frac{s}{\omega_{3dB}}$$

$$\hookrightarrow \frac{A_{v0}}{\frac{s}{\omega_{3dB}}} = \frac{A_{v0} \omega_{3dB}}{s}$$

$$= \frac{\omega_{un}}{s}$$

$$\Rightarrow \omega_{un} = A_{v0} \cdot \omega_{p1}$$

$$\omega_{un} \stackrel{\Delta}{=} A_v \cdot \omega_{p1} = A_v \cdot \omega_{3dB}$$

same

$$= \cancel{g_{m1} R_1} \cancel{g_{m2} R_2} \times \frac{1}{\cancel{g_{m2} R_2} \cancel{R_1} C_c}$$

$$\boxed{\omega_{un} \stackrel{\Delta}{=} \frac{g_{m1}}{C_c}}$$

unity-gain frequency

$$\omega_{un} = A_v \times \omega_{3dB}$$

$$\omega_{un} = \text{Gain} \times \text{BW}$$

"GBW"

gain - Bandwidth =
Tradeoff