

ECE 511 - Lecture 18

Note Title

3/19/2015

Recap

CS stage
↳ 2nd order response

↳ $\omega_{p1}, \omega_{p2} \text{ \& } \omega_z$




↳ Miller compensation $C_c \uparrow$
pole splitting

↳ RHP zero degrades phase

↳ $\omega_{um} \leftarrow$ unity gain frequency

↳ for dominant pole
 $\omega_{um} = A_v \times \omega_{3dB}$

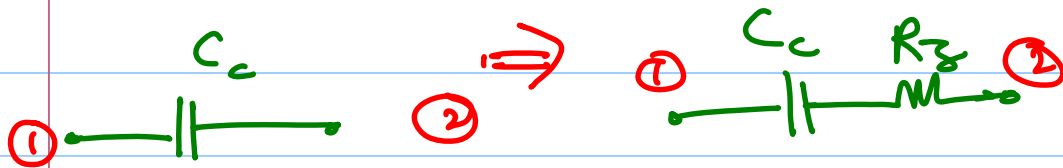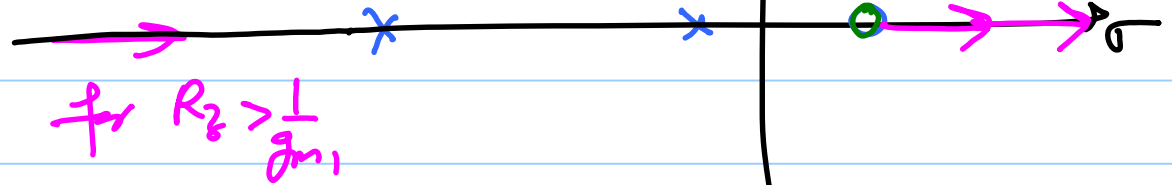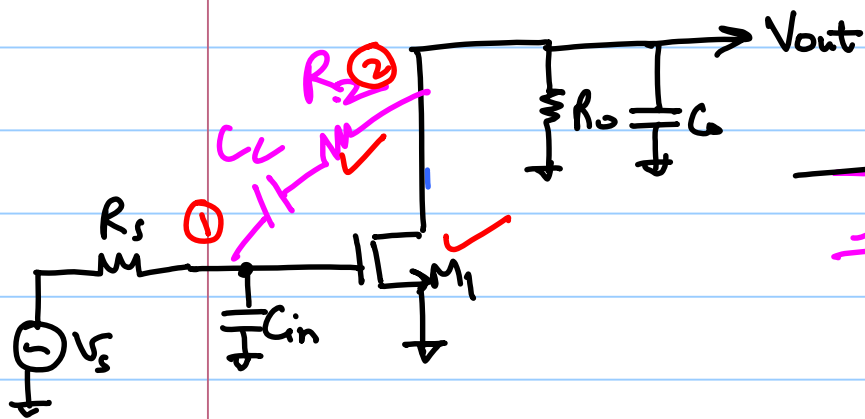RHP zero at $\omega_z = \frac{g_{m1}}{C_c}$




$$\omega_z = \frac{1}{C_c \left(\frac{1}{g_{m1}} - R_z \right)}$$

instead of $\frac{g_{m1}}{C_c}$

Now if set $R_z = \frac{1}{g_{m1}} \Rightarrow \omega_z \rightarrow \infty$

$\Rightarrow$ pushes RHP zero to ∞

Use a triode

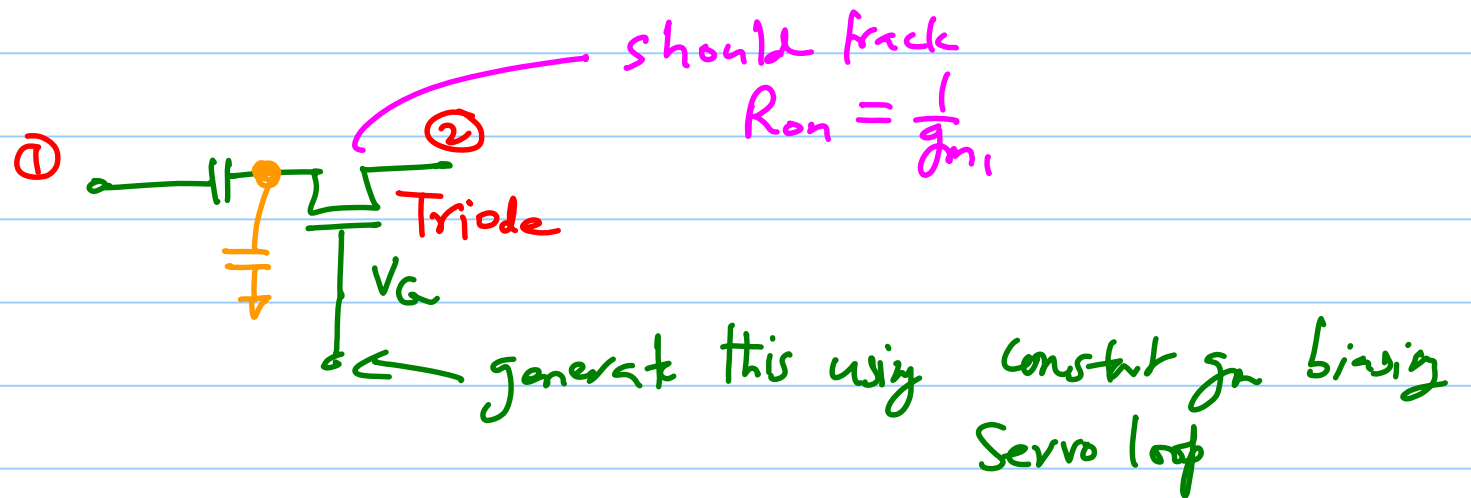


* RHP zero canceling

* What if $R_z = \frac{2}{g_{m1}} \Rightarrow \omega_z = -\frac{g_{m1}}{C_c}$


$\Delta\phi = +\tan^{-1}\left(\frac{\omega}{\omega_z}\right)$ for LHP zero



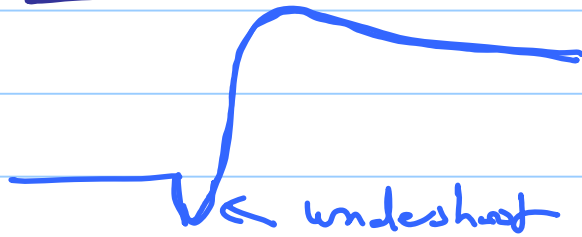for $\phi M = 60^\circ$
 2 poles $n = 0$ zero




2 poles & RHP zero

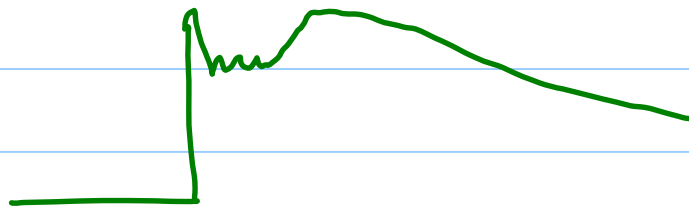

2 poles & 2HP zero around ω_n

Source follower frequency response

$$\lambda = 0$$

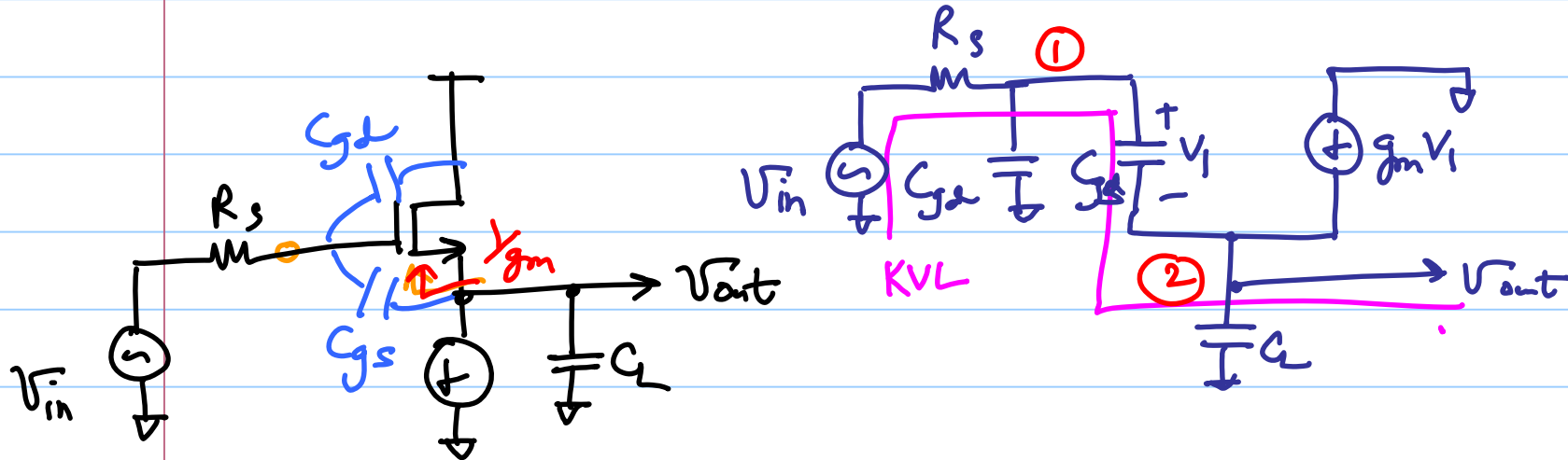

@ node ②

$$V_1 C_{gs} s + g_m V_1 = V_{out} s C_L$$

$$\Rightarrow V_1 = \frac{s C_L}{g_m + C_{gs} s} V_{out} \longrightarrow \textcircled{1}$$

* KVL beginning from V_1

$$V_{in} = R_s [V_1 C_{gs} s + (V_1 + V_{out}) s C_{gd}] + V_1 + V_{out} \longrightarrow \textcircled{2}$$

① → ②

$$\frac{V_{out}}{V_{in}}(s) = \frac{g_m + sC_{gs}}{R_s [C_{gs}C_L + C_{gs}C_d + C_dC_L]s^2 + [g_m R_s C_d + C_L + C_{gs}]s + g_m}$$


Zero:

$$N(s) = 0$$


$$g_m + sC_{gs} = 0$$

$$\Rightarrow s = j\omega_z = -\frac{g_m}{C_{gs}}$$

LHP zero

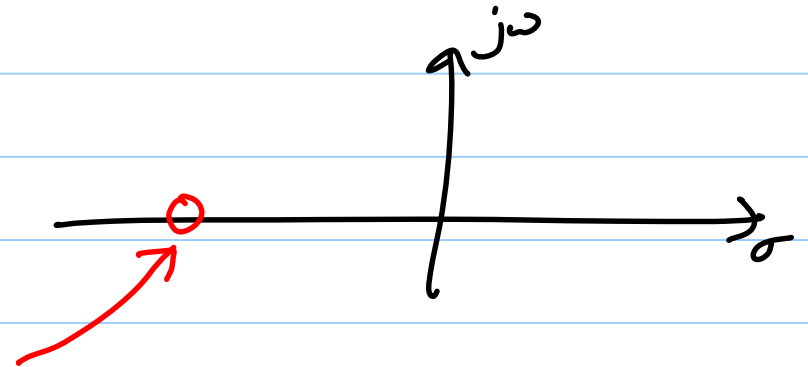

* Why LHP zero?

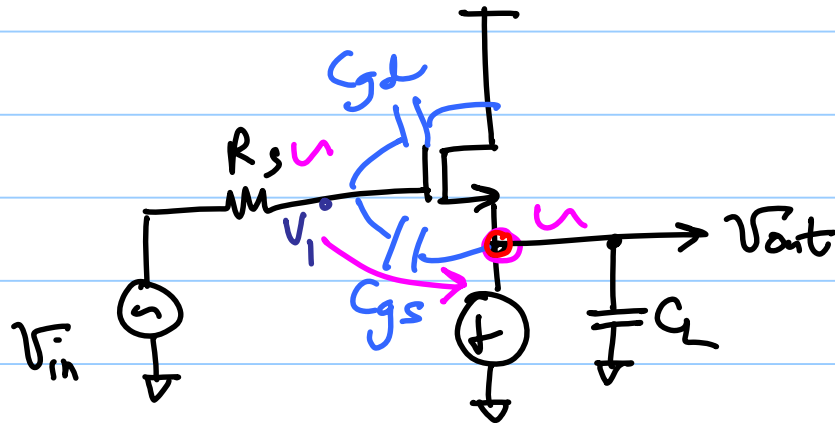


$$g_m V_i + s C_{gs} V_i = 0$$

$$\Rightarrow \underline{s_z = -\frac{g_m}{C_{gs}}}$$

main path & FF currents add up the same phase.

ASIDE

C_s

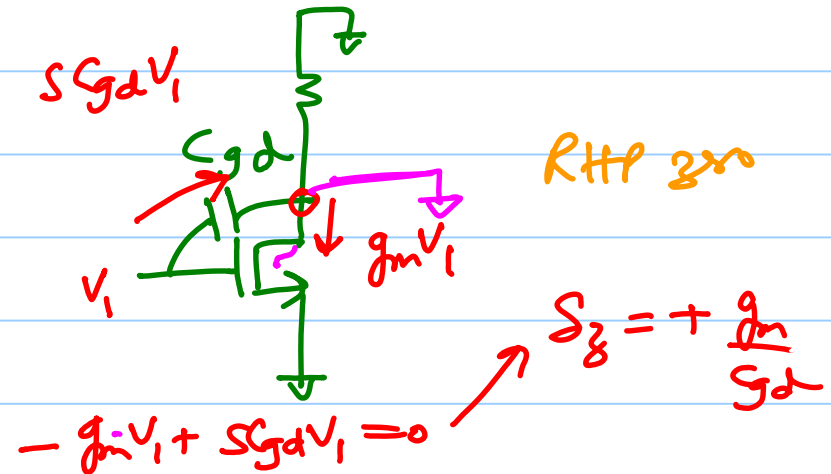

Dominant pole is at


$$\omega_{p1} \approx \frac{g_m}{g_m R_s C_{gd} + C_L + C_{gs}}$$

$$= \frac{1}{R_s C_{gd} + \frac{C_L + C_{gs}}{g_m}} \quad \leftarrow$$

$$\approx \frac{g_m}{C_L + C_{gs}} \quad \leftarrow$$

single pole when $R_s = 0$

Input Impedance:

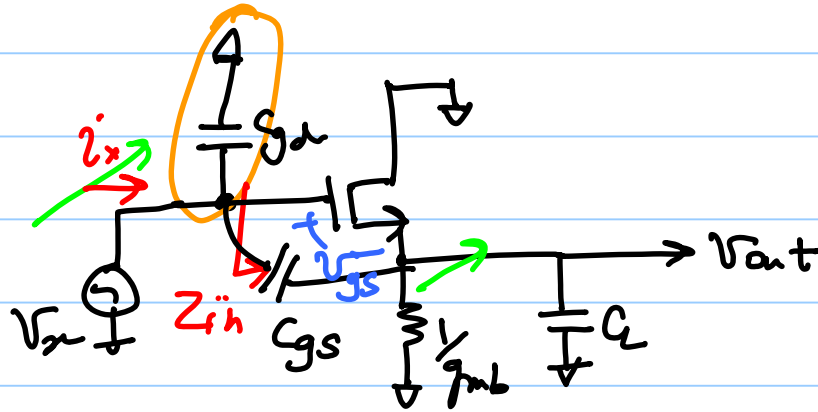

$$V_{gs} = \frac{i_x}{sC_{gs}}$$

$$\& \quad v_d = g_m V_{gs} = \frac{g_m i_x}{sC_{gs}}$$

$\Rightarrow$

$$V_x = \frac{i_x}{C_{gs}} + \left(i_x + \frac{g_m i_x}{sC_{gs}} \right) \left(\frac{1}{g_{mb}} \parallel \frac{1}{sC_L} \right)$$

$$Z_{in1} = \frac{1}{sC_{gs}} + \left(1 + \frac{g_m}{sC_{gs}}\right) \frac{1}{g_{mb} + sC_L}$$

@ low-frequencies $g_{mb} \gg |sC_L|$

$$\Rightarrow Z_{in1} \approx \frac{1}{sC_{gs}} \left(1 + \frac{g_m}{g_{mb}}\right) + \frac{1}{g_{mb}}$$

$$= \frac{1}{g_{mb}} + \frac{1}{\frac{sC_{gs}}{\left(1 + \frac{g_m}{g_{mb}}\right)}}$$

$$\text{Total input impedance} = \frac{1}{sC_{gs}} + \frac{1}{g_{mb}} + \frac{1}{\frac{sC_{gs}}{\left(1 + \frac{g_m}{g_{mb}}\right)}}$$

Equivalent input cap $\Rightarrow C_{gd} + \frac{C_{gs}}{\left(1 + \frac{g_m}{g_{mb}}\right)}$


↳ fraction of $C_{gd} + C_{gs}$

→ Low input cap
→ Low output Resistance
↳ large BW $\propto \frac{g_m}{C_L}$

} good voltage Buffer


output impedance :

neglecting C_{gd} & g_{mb}

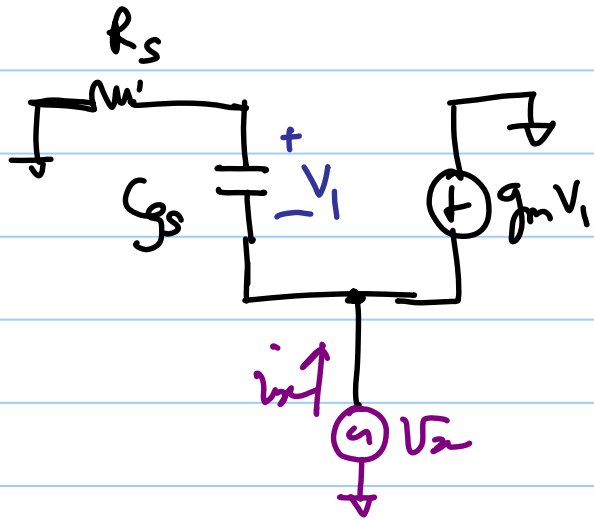



$$Z_{out} = \frac{V_x}{i_x} = \frac{R_s C_{gs} s + 1}{g_m + s C_{gs}}$$
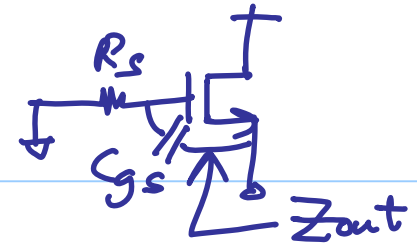
$$Z_{out} = \frac{s \cdot R_s C_{gs} + 1}{g_m + s C_{gs}}$$



@ low-f: $Z_{out} = \frac{1}{g_m}$

@ high-f: $Z_{out} = R_s$


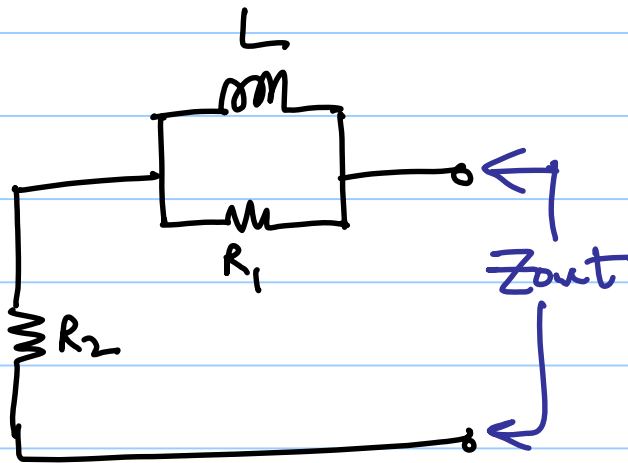
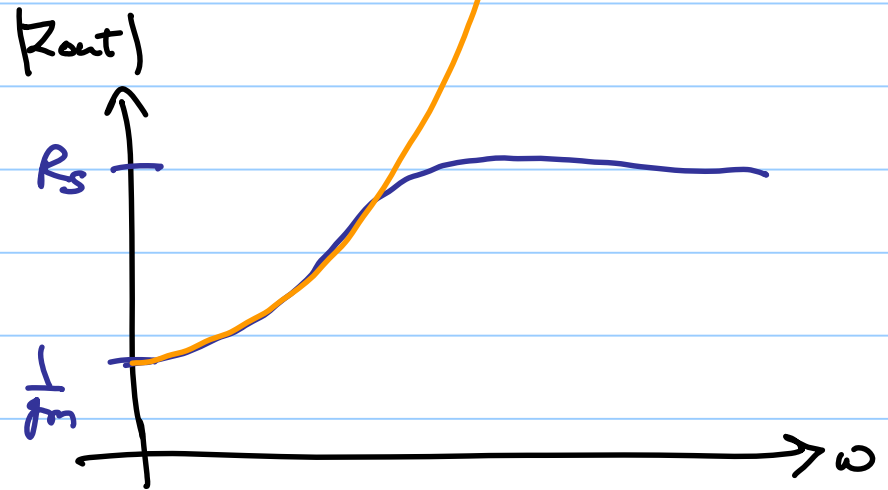


$$R_2 = \frac{1}{g_m}$$


$$R_1 = R_s - \frac{1}{g_m}$$


$$L = \frac{C_{gs}}{g_m} \left(R_s - \frac{1}{g_m} \right)$$

↑ Active-L

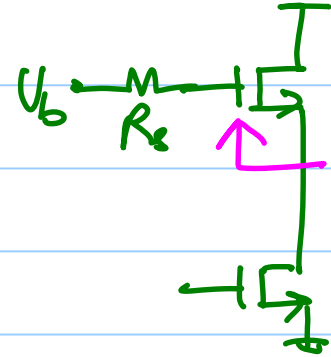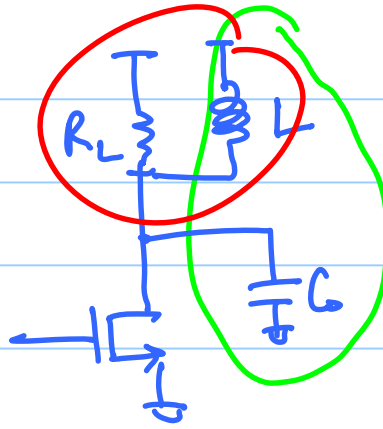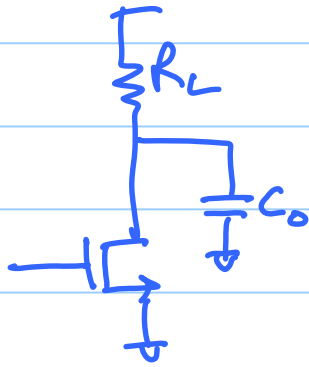

A


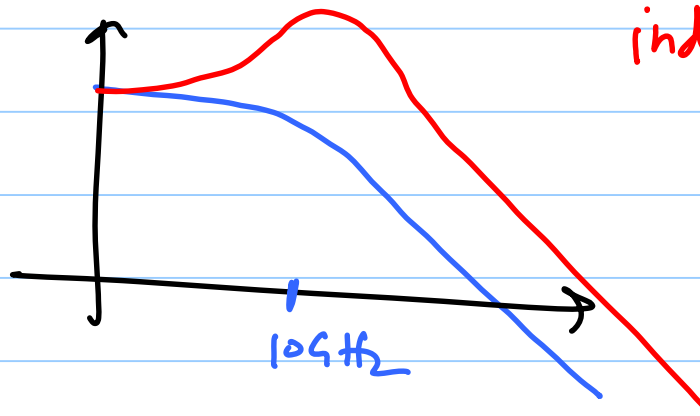


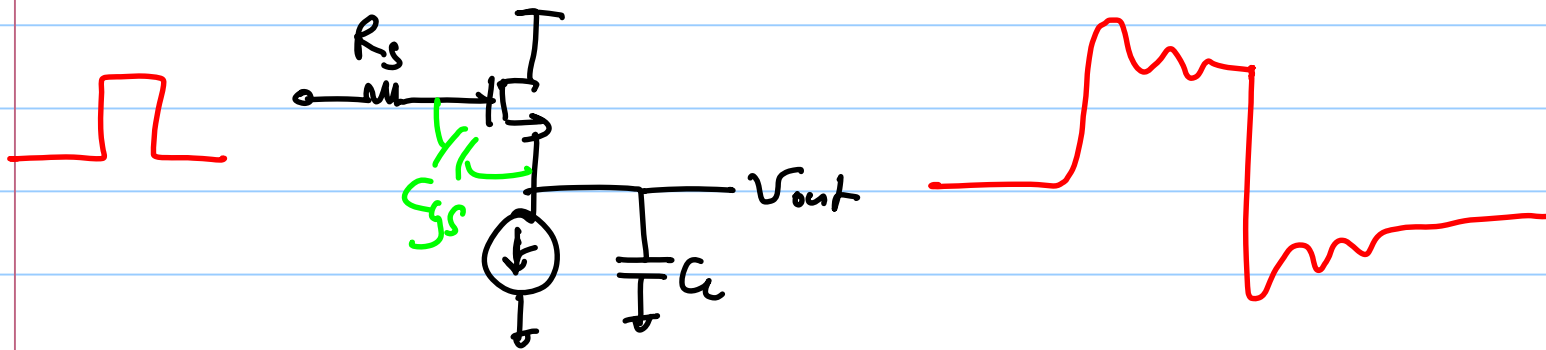

* inductive behavior can manifest as ringing

Common Gate Frequency Response

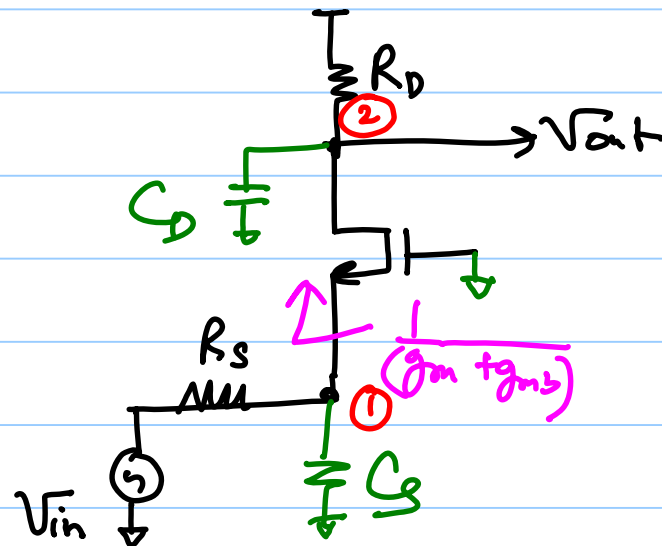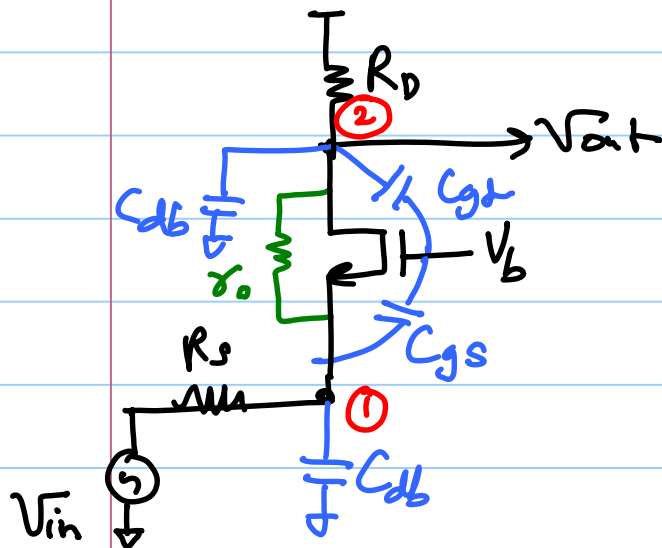① & ② are isolated if $\lambda=0$
 $r_o \rightarrow \infty$



@ node - 1

$$\omega_{p1} = \omega_{in} = \frac{1}{\left(R_s \parallel \frac{1}{g_m + g_{mb}} \right) C_s}$$

assuming $R_D \leq r_o$

@ node 2

$$\omega_p = \omega_{out} = \frac{1}{R_D C_D}$$

$$\frac{V_{out}}{V_{in}}(s) = \boxed{\frac{(g_m + g_{mb})R_D}{1 + (g_m + g_{mb})R_S}} \times \frac{1}{\left(1 + \frac{s}{\omega_{p1}}\right)\left(1 + \frac{s}{\omega_{p2}}\right)}$$

DC gain with R_S

(*) No Miller effect of capacitor

↳ potentially wideband

↳ low input impedance

↳ trans-impedance amplifier