

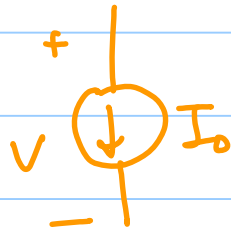
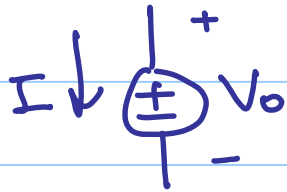
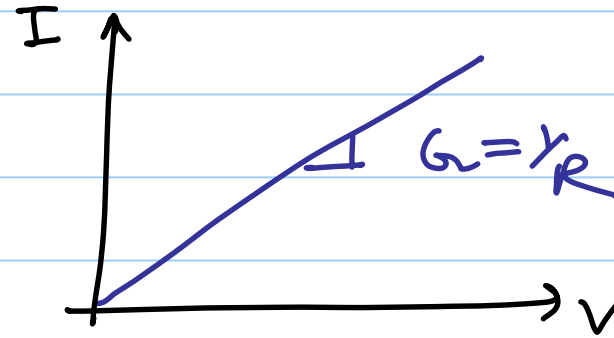


ECE 511 - Lecture 1

Note Title




1/13/2015

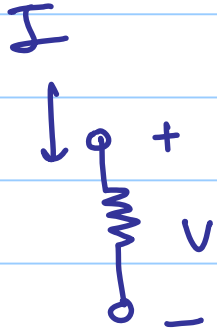

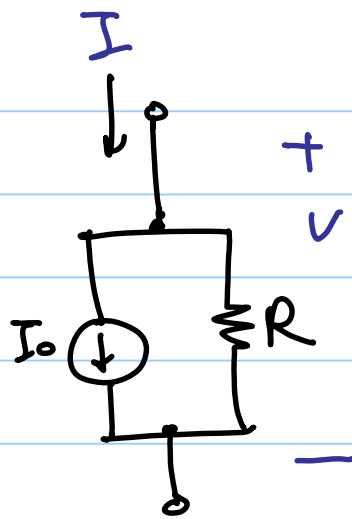



$$I = I_0 + \frac{V}{R}$$

I-V curves for a MOSFET

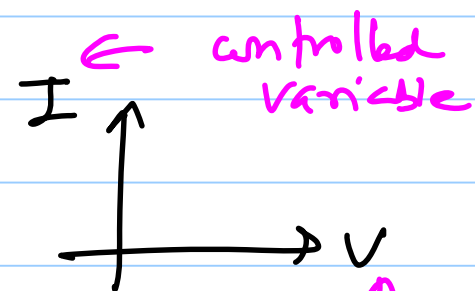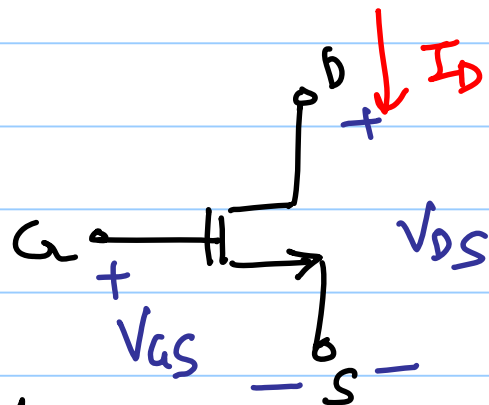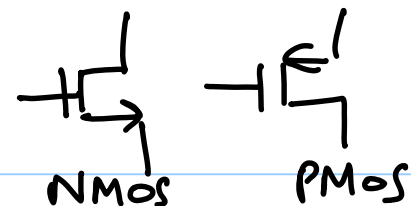

Ignoring body-effect

$$I_D = f(V_{GS}, V_{DS})$$

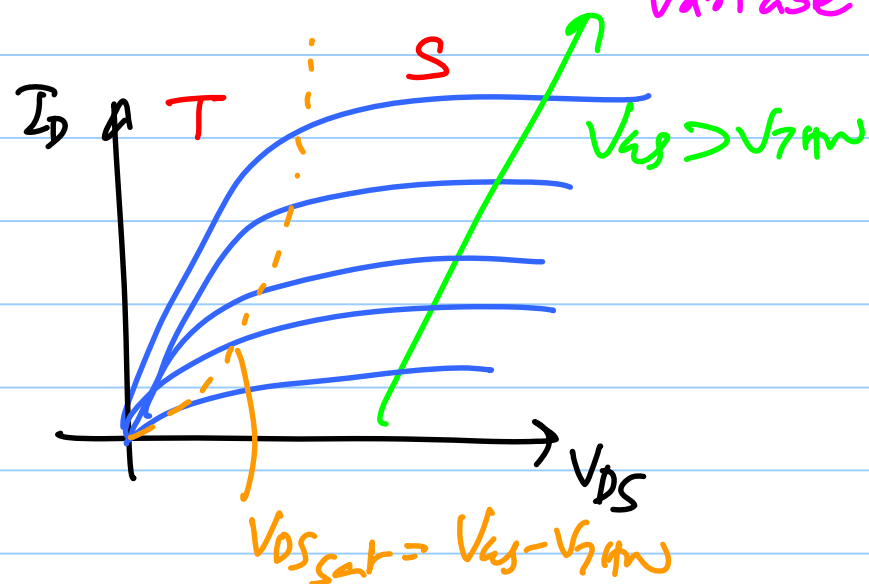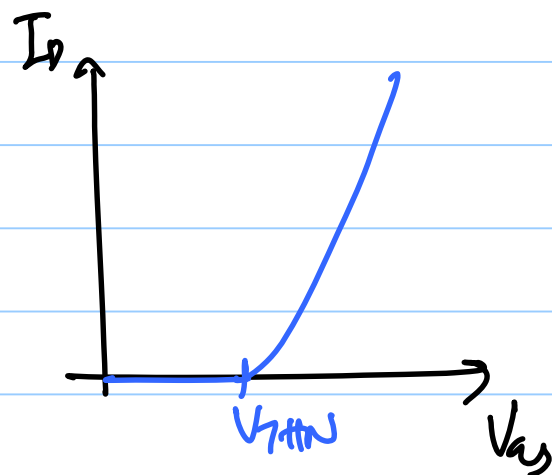

Long-channel equations

Cutoff: $V_{GS} < V_{THN}$

Triode: $V_{GS} > V_{THN}$ & $V_{DS} < V_{DS,sat} = V_{GS} - V_{THN}$

$$I_D = K_{PN} \cdot \frac{W}{L} \left[(V_{GS} - V_{THN}) V_{DS} - \frac{V_{DS}^2}{2} \right]$$

Sat: $V_{DS} > V_{DS,sat}$

$$I_D = \frac{K_{PN}}{2} \frac{W}{L} (V_{GS} - V_{THN})^2 \left[1 + \lambda V_{DS} \right]$$

channel length modulation

overdrive voltage

$$\boxed{V_{OV} = V_{GS} - V_{THN}} \leftarrow V_{DS,sat} \text{ only for long channel}$$

$\frac{W}{L} \rightarrow$ aspect ratio $\rightarrow$ device sizing



In saturation


$$I_D = I_{D,sat} + I_{D,sat} \cdot \lambda (V_{DS} - V_{DS,sat})$$

$$\gamma_0 = \left(\frac{\partial I_D}{\partial V_{DS}} \right)^{-1}$$



$$\boxed{\gamma_0 = \frac{1}{\lambda \cdot I_{D,sat}}}$$

$$I_{D,sat} = f(V_{GS})$$

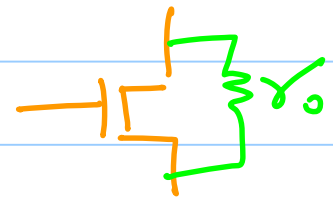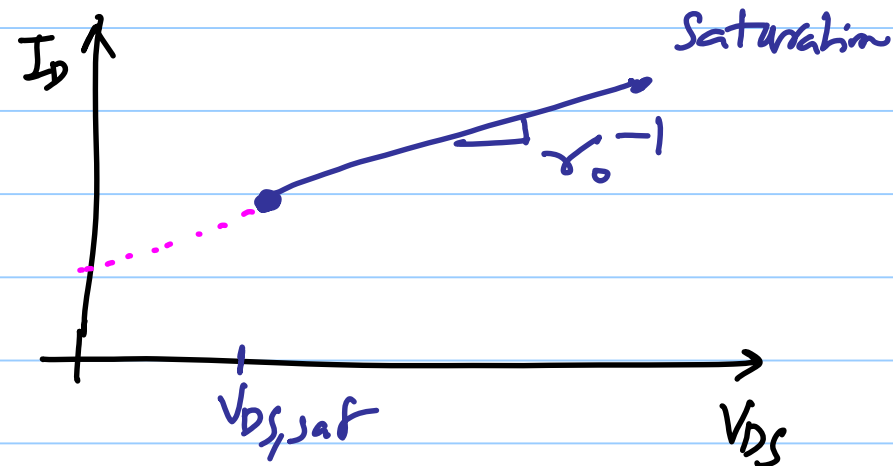

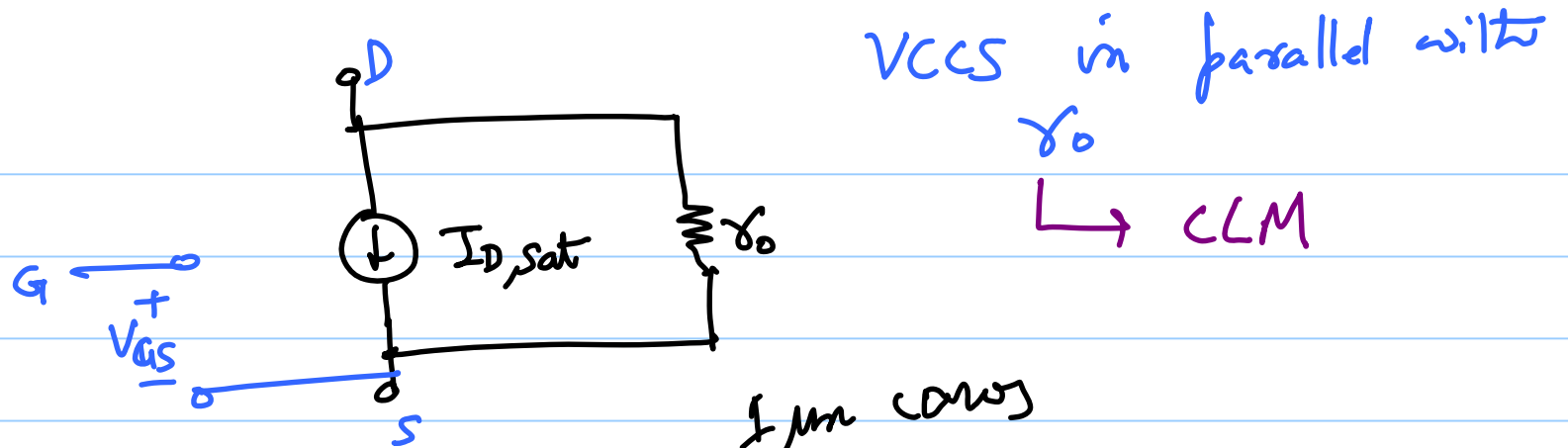

$$r_o \propto \frac{1}{I_D}$$

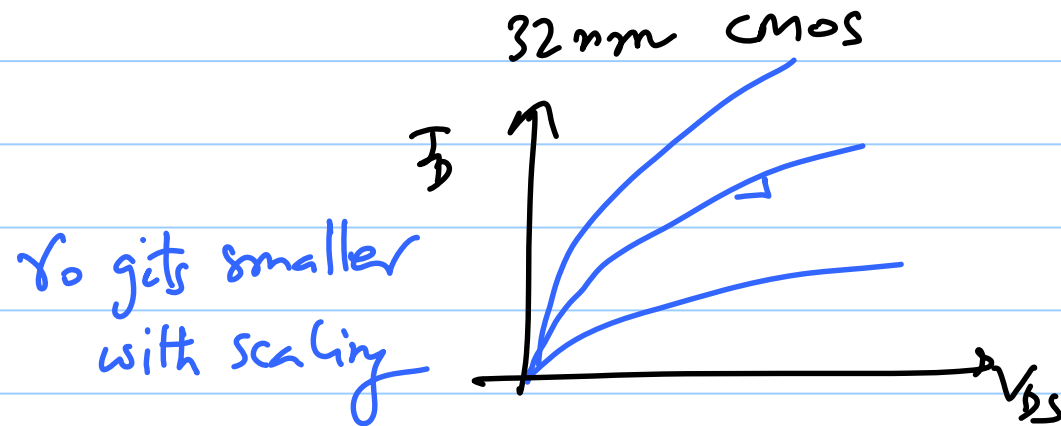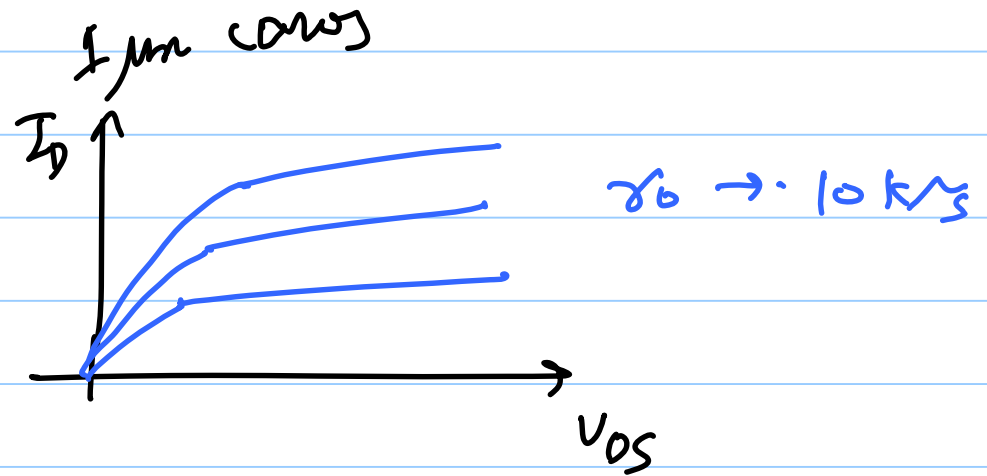

In Triode

$$V_{DS} < V_{DS, \text{sat}}$$

for $V_{DS} \ll V_{DS, \text{sat}}$

$$I_D = k p_n \frac{W}{L} \left[(V_{GS} - V_{THN}) V_{DS} - \frac{V_{DS}^2}{2} \right]$$

Assume $V_{DS} \ll V_{DS, \text{sat}}$: Deep triode



$$I_D \approx k p_n \frac{W}{L} (V_{GS} - V_{THN}) V_{DS}$$

"Linear region"


$$R_{ch} = \left(\frac{\partial I_D}{\partial V_{DS}} \right)^{-1} \approx \frac{1}{k p_n \frac{W}{L} (V_{GS} - V_{THN})}$$

$$R_{ch} \propto \frac{1}{V_{GS} - V_{THN}} \Leftarrow \checkmark$$

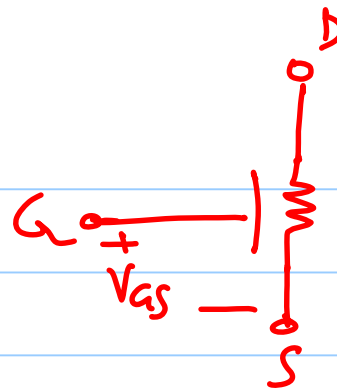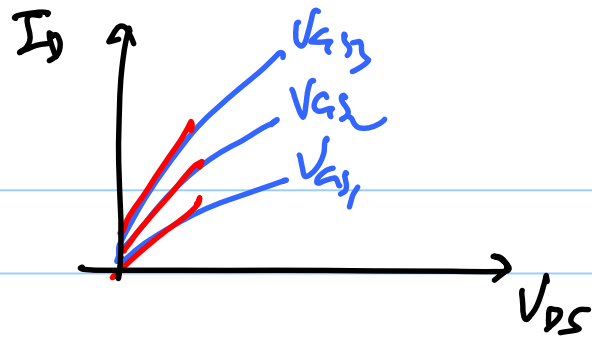
Variable resistance
controlled by the gate
overdrive



Example:

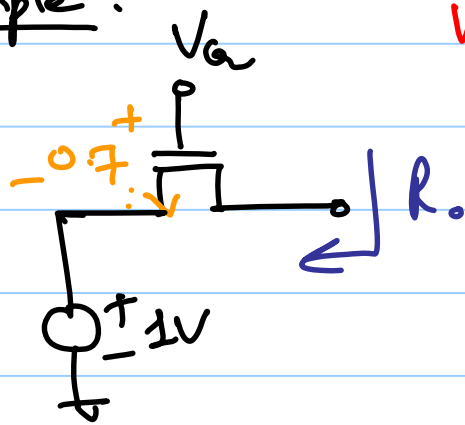


$$V_{TH} = 0.7V$$

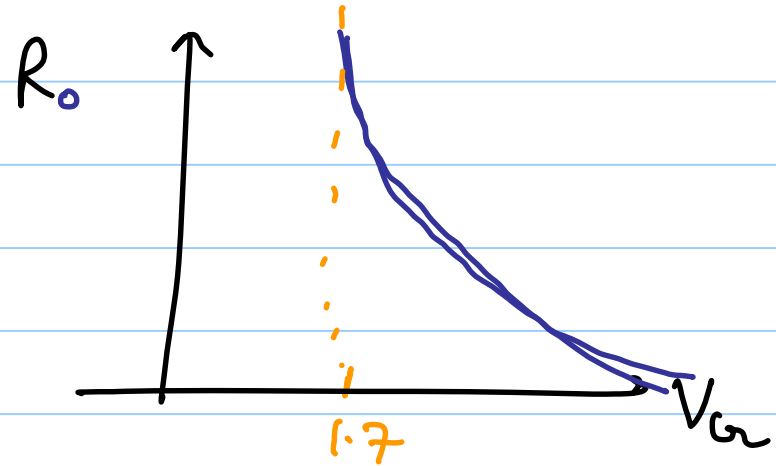


$$R_{ch} = \frac{1}{k \left(\frac{W}{L} \right) (V_{GS} - V_{TH})}$$
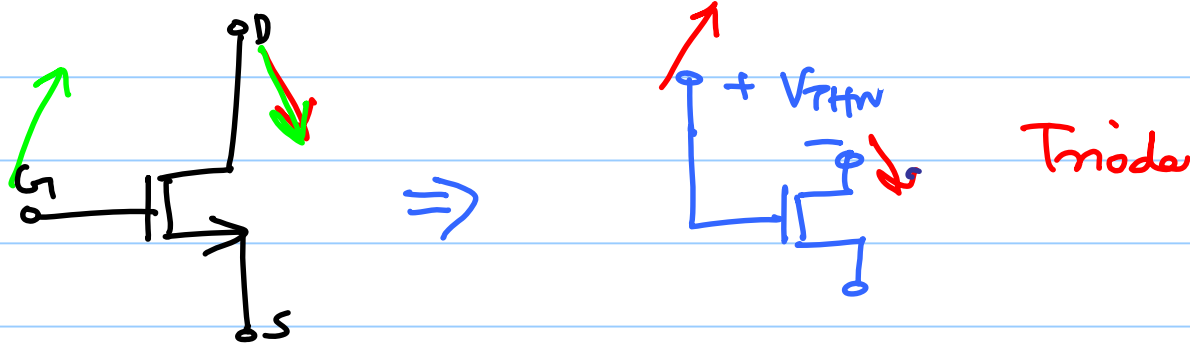
$$\underline{V_{DS} > V_{GS} - V_{THN}}$$




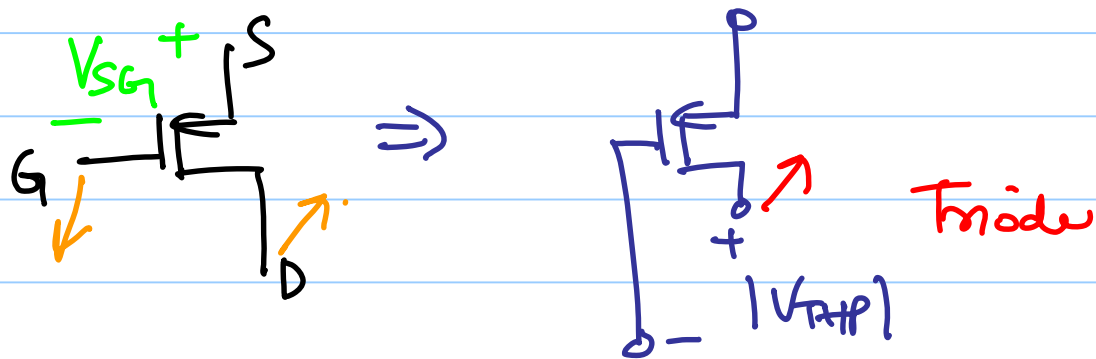$\Rightarrow$ the NMOS can have the gate at max V_{THN} higher than the drain before it triodes.



$\downarrow$
the gate can not be lower than the drain by more than $|V_{THP}|$.


Diode Connection

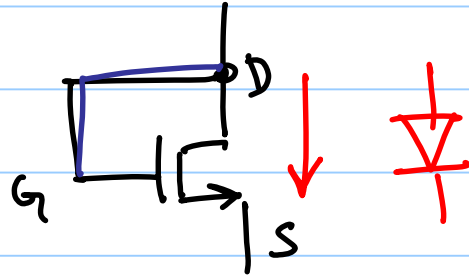


Connect gate & drain


$$V_{DS} = V_{GS} > V_{DS, sat}$$

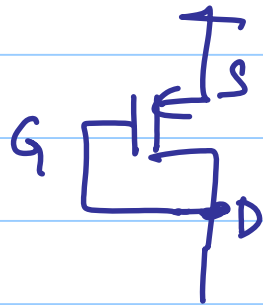
$\Rightarrow$ always in saturation
for $V_{GS} > V_{THN}$



$$I_D = f(V_{GS})$$

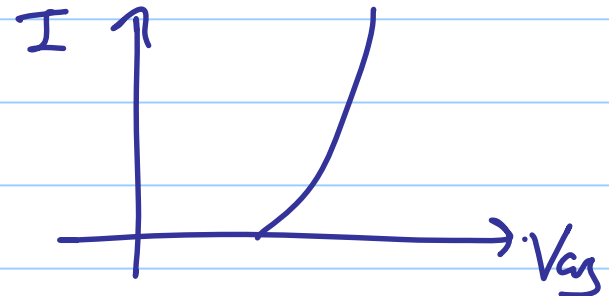

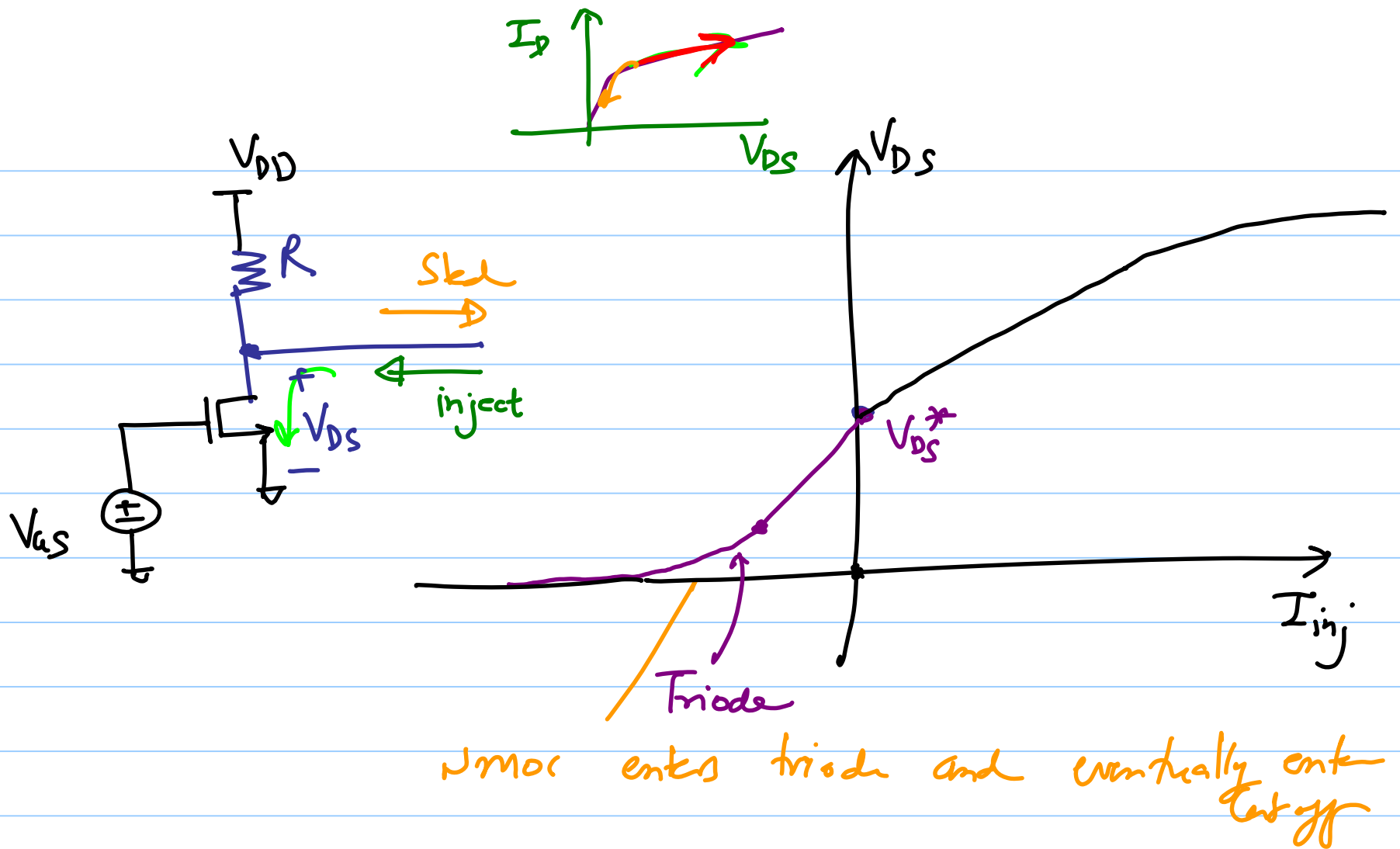


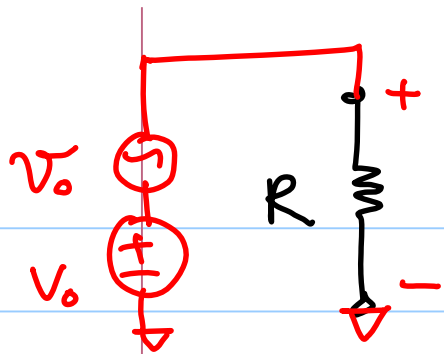

Small-signal
(ac) current
 $\frac{v_o}{R}$



$$i_o = \frac{v_o}{R}$$

$$i_o = G v_o$$

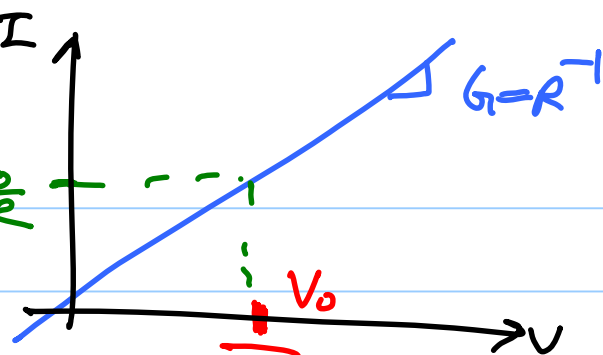

linear device

Small-signal (ac)
voltage

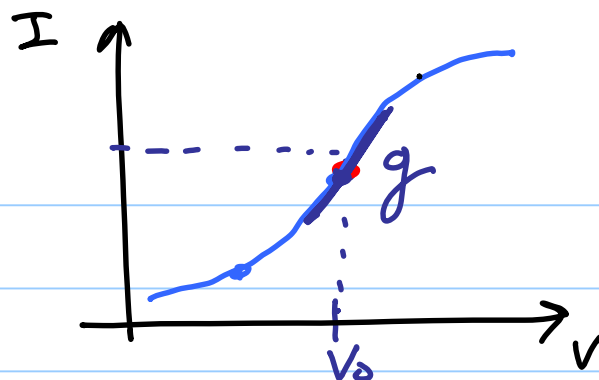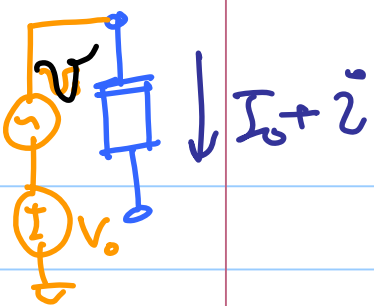

$$I = f(V) \quad \checkmark$$

Bias
Operating
Q- point

* Need to "bias" it properly

↳ setting the DC operating point for the device (V_0, I_0)

Large-signal characteristic

$$I = f(V)$$

Taylor Series expansion about the bias point

$$I = \underbrace{f(V_0) + \frac{f'(V_0)}{1} (V - V_0)}_{\text{DC}} + \frac{f''(V_0)}{2} (V - V_0)^2 + \frac{f'''(V_0)}{6} (V - V_0)^3 + \dots$$

$$V = V_0 + v$$

DC AC ← Small-signal

$$I = \overset{\text{small-signal}}{\underbrace{f(v_0) + f'(v_0) \cdot v}} + \underbrace{\frac{f''(v_0)}{2}}_{[2]} v^2 + \underbrace{\frac{f'''(v_0)}{6}}_{[3]} v^3 + \dots$$

$$(I - I_0) = f'(v_0) \cdot v + \dots \text{higher order terms}$$

$$i = f'(v_0) v + \dots$$

If v is "very small", then we can ignore higher-order terms

$$i = f'(v_0) v$$

$$i = g \cdot v \quad \text{where} \quad g = \left. f'(v) \right|_{v=v_0}$$

small-signal parameter
depends upon the bias-point

Small-signal analysis $\Rightarrow$ linearizing the device about the DC bias point