
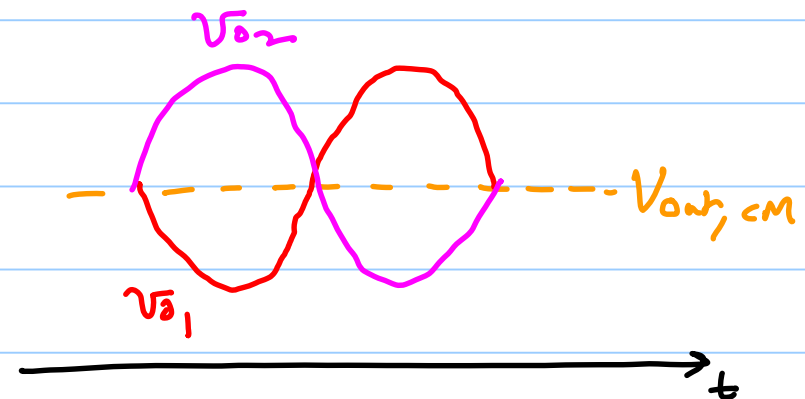
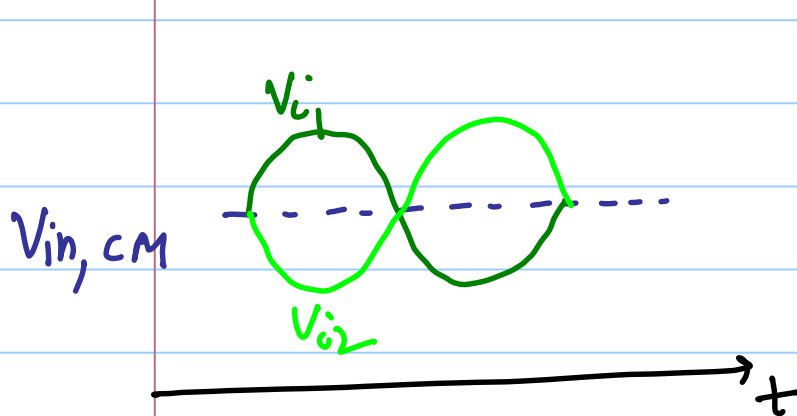


ECE 511 - Lecture 20





Note Title

4/2/2015

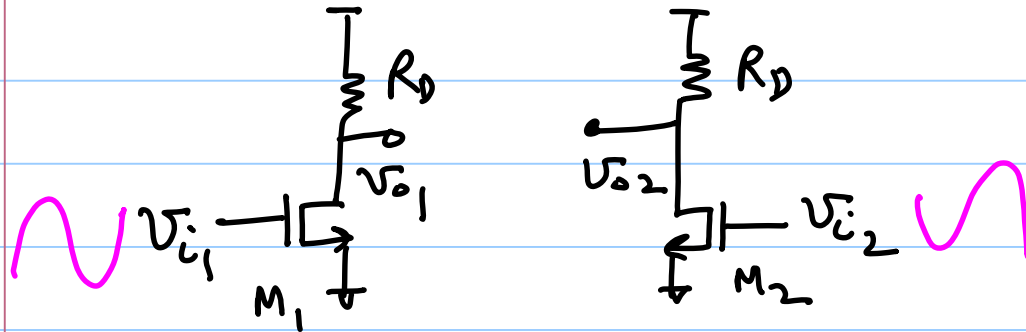Basic Diff-pair $\rightarrow$ Diff. CS amplifier




What if $V_{in,CM}$ is not well defined.

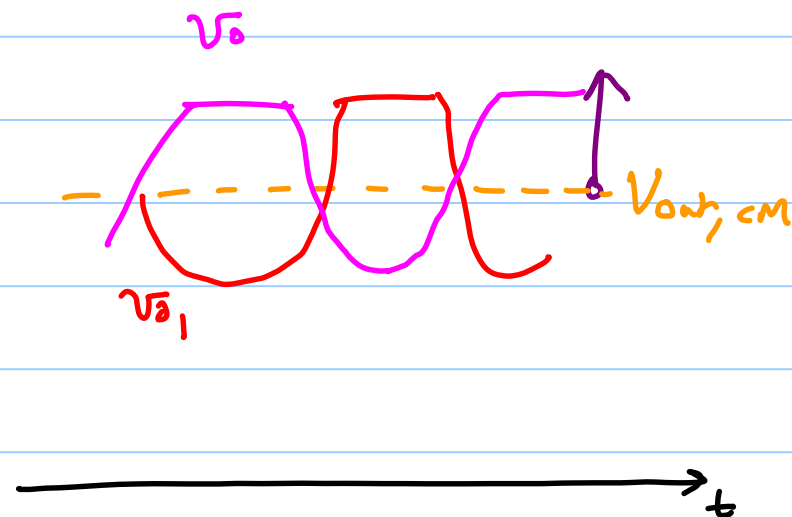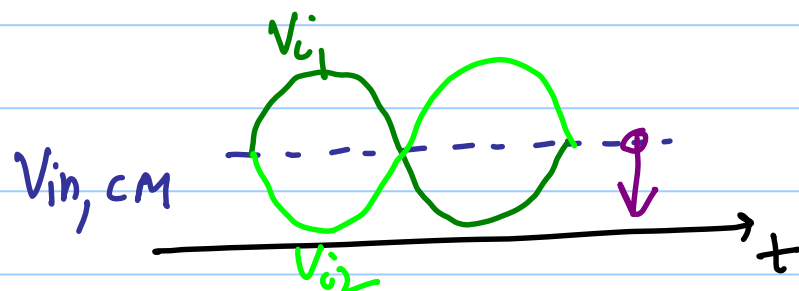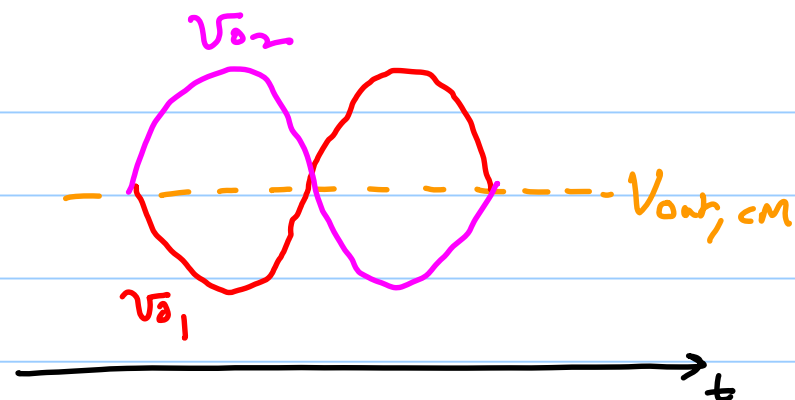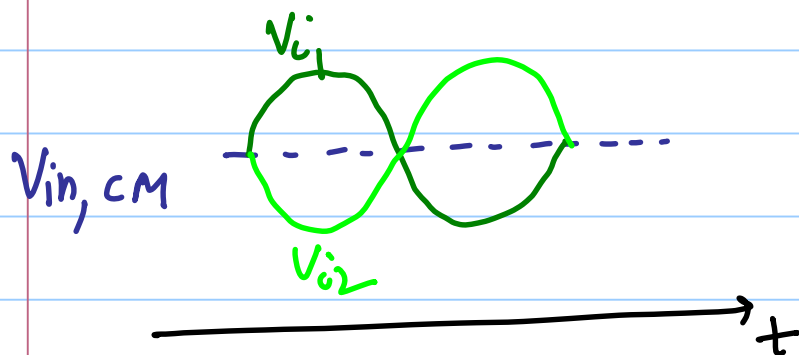

If $V_{in,CM}$ changes, I_D in n_2 & M_2 change
 g_m is changed
 & output CM-level varies


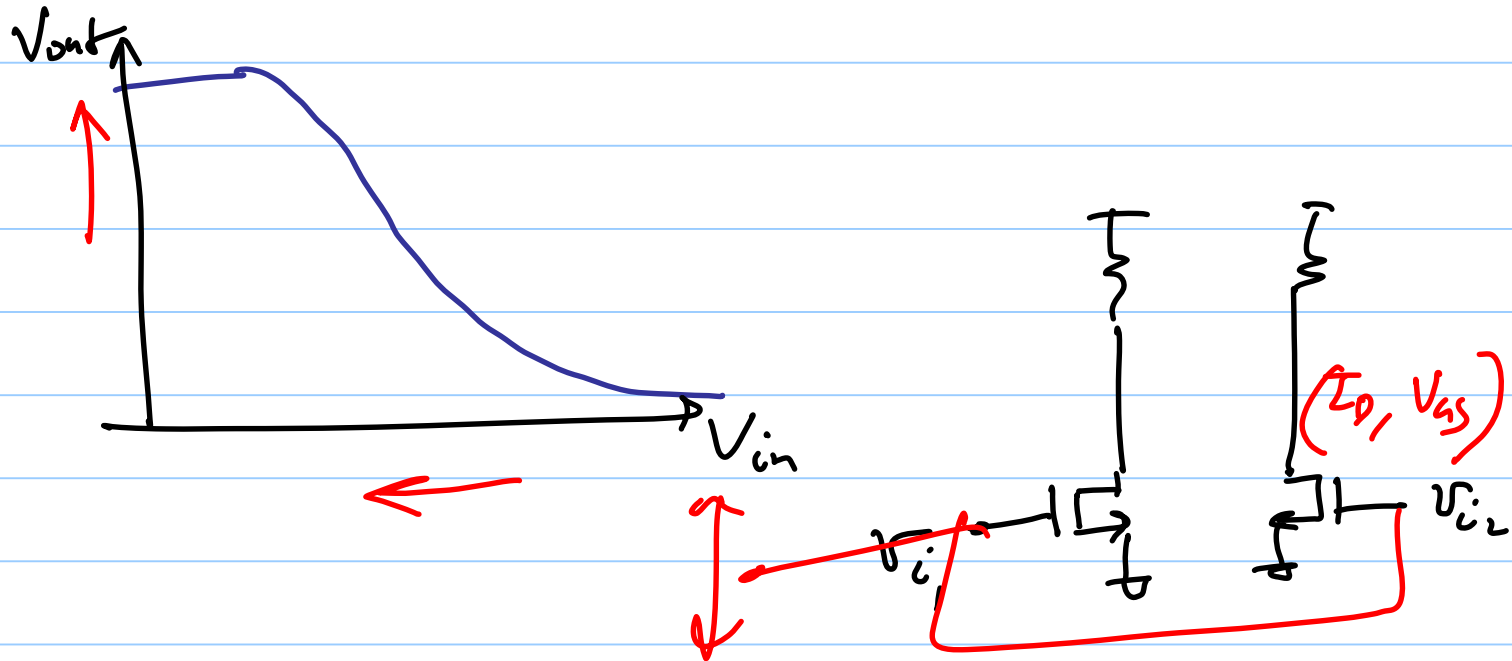
Ideally $\rightarrow$ important that the biasing (V_{GS} , I_D) of the devices has a minimal dependence on the input CM-level.



Solution

Set
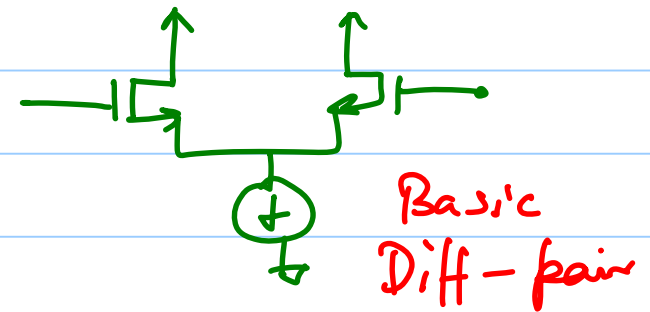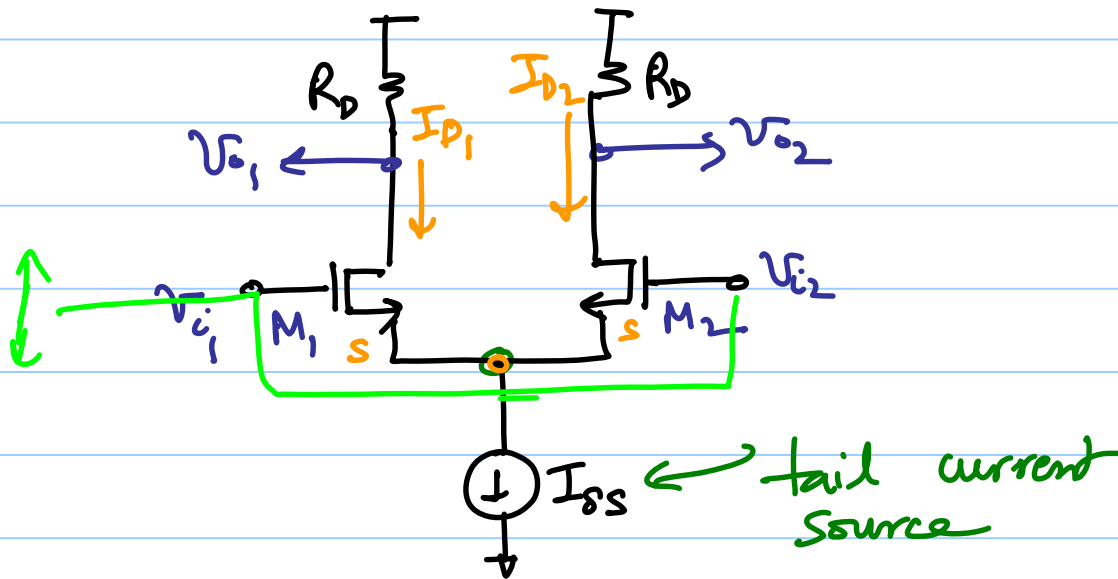
$$I_{D1} + I_{D2} = I_{SS} = \text{const}$$



Using a current source to make


$$\boxed{I_{SS} = I_{D1} + I_{D2}} \text{ independent of } V_{in, cm}$$

* If $\boxed{V_{i1} = V_{i2}} \Rightarrow$ the bias current in each device $= \frac{I_{SS}}{2}$


$$\text{output common mode level} = V_{DD} - \frac{I_{SS}}{2} \times R_D$$

Qualitative Analysis:

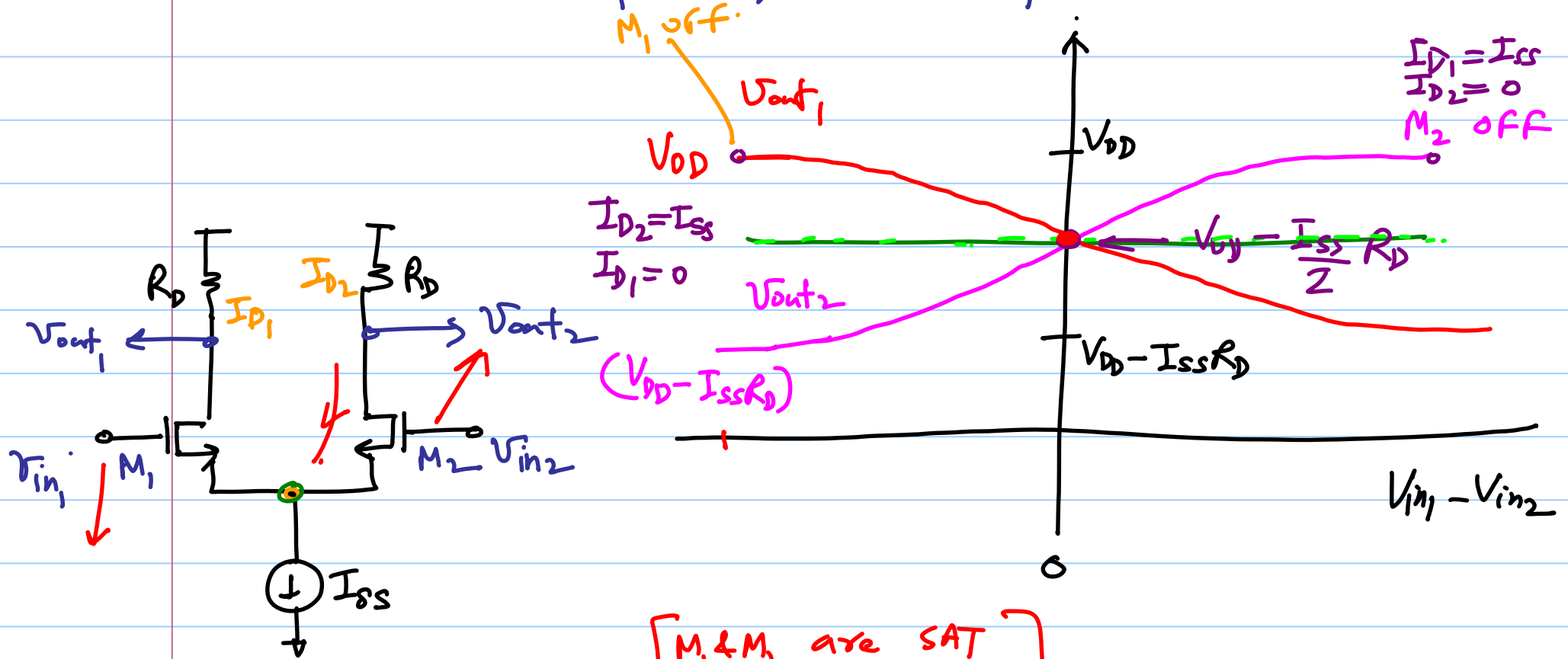Assume that $(V_{i1} - V_{i2})$ varies from $-\infty$ to ∞




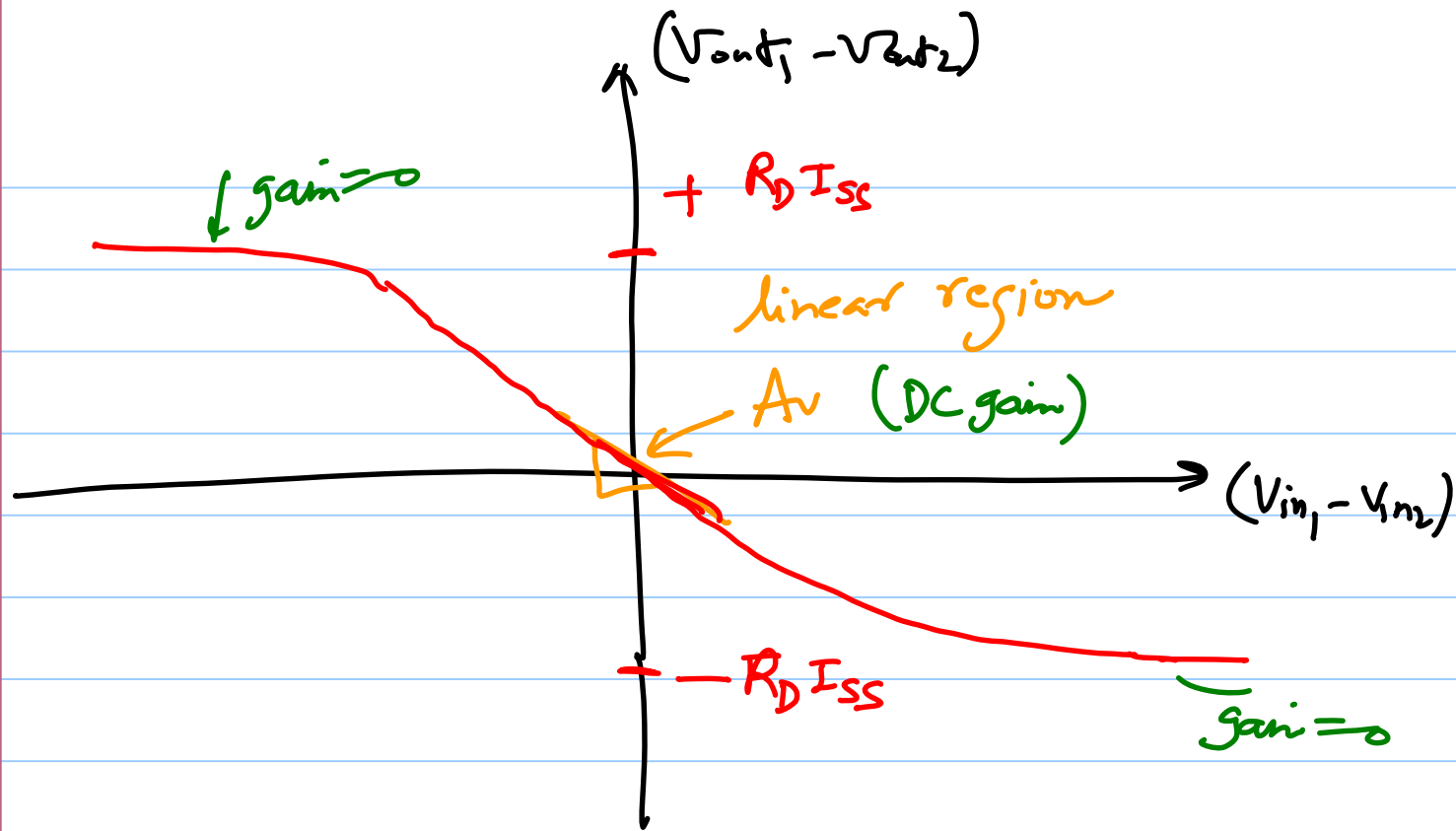
$[M_1 \& M_2 \text{ are SAT}]$
 $[I_{SS} \text{ is ideal}]$



$$\frac{d(V_{out1} - V_{out2})}{d(V_{in1} - V_{in2})}$$

input - output characteristics





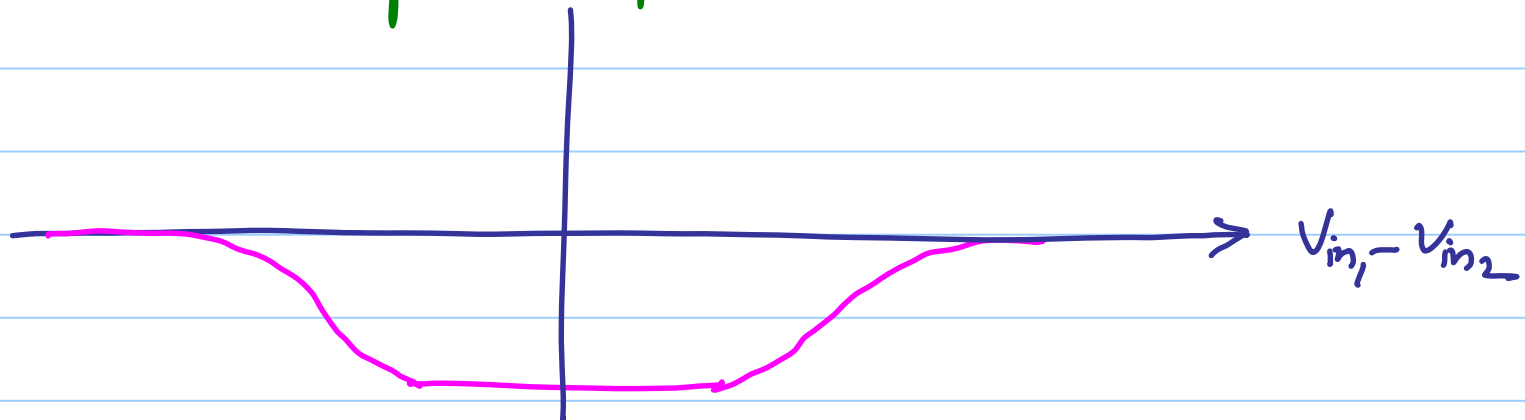


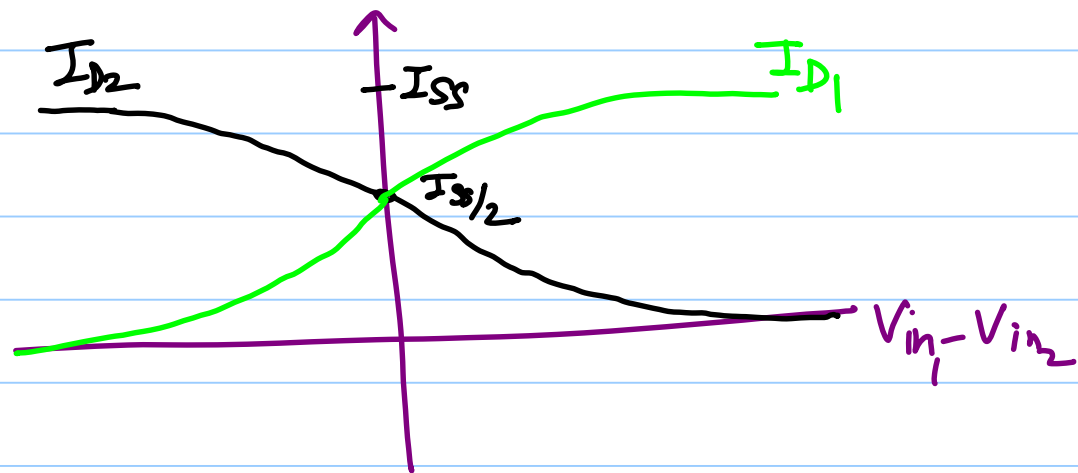

$$v_{out} = - \left(\overbrace{A_1 v_{in}} - \underbrace{A_3 v_{in}^3}_{\text{for large signal operation}} - \dots \right)$$

for large signal operation

Common-mode behavior of the Diff-pair

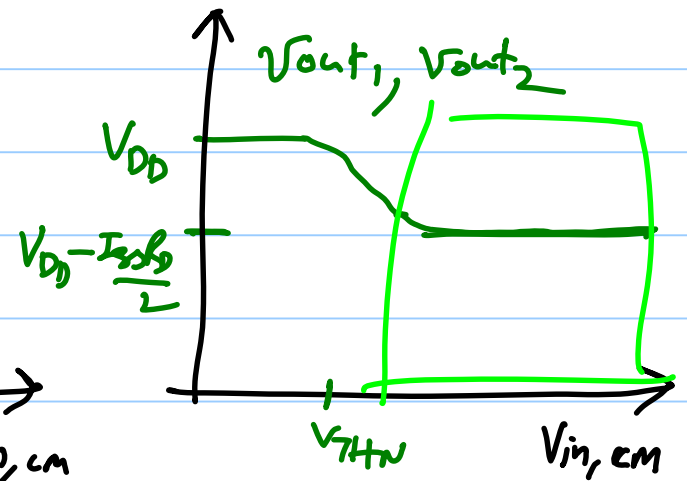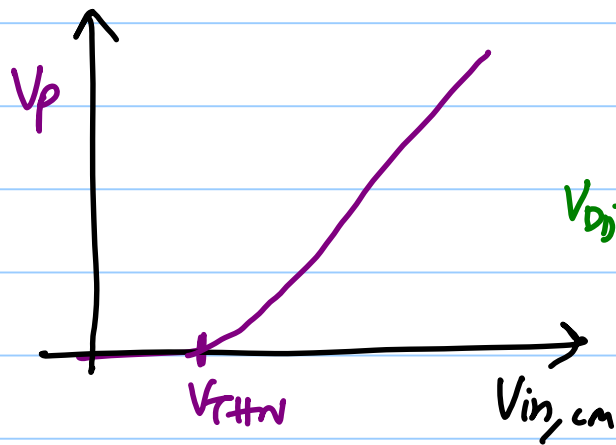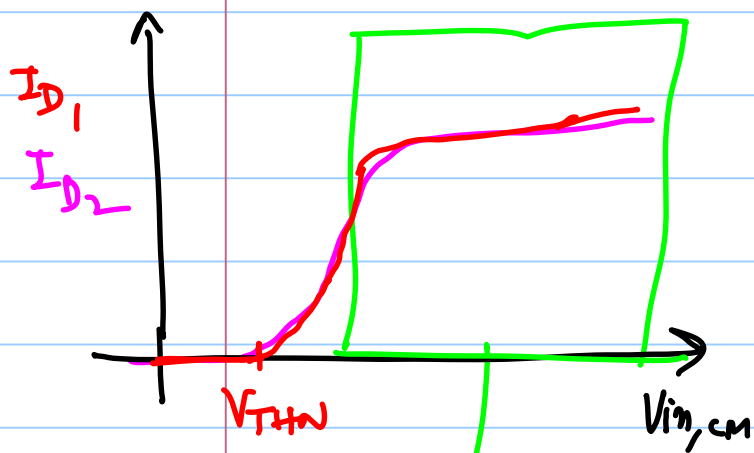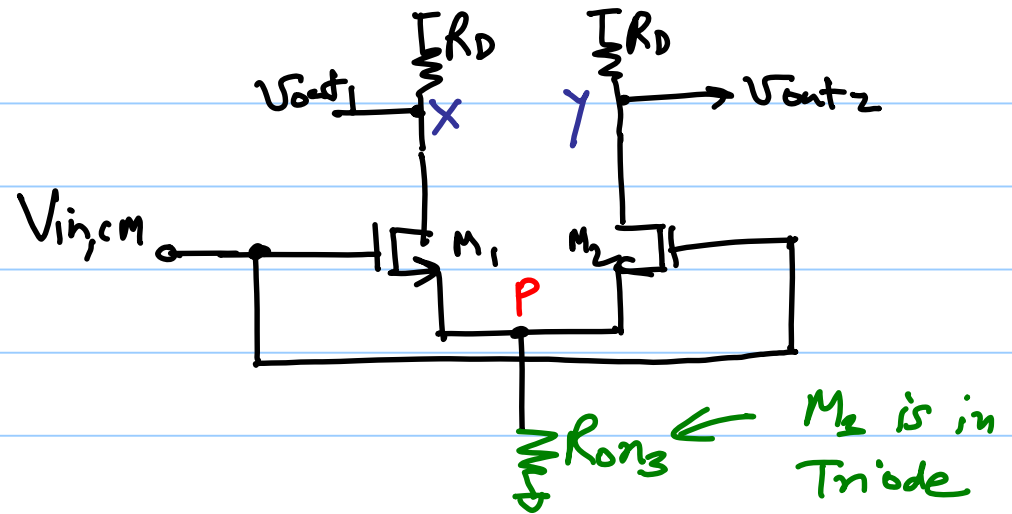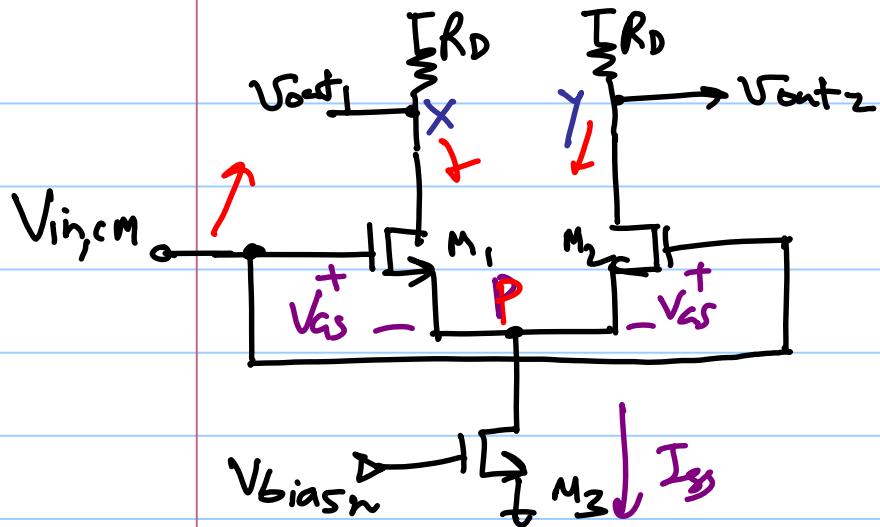

Input CM-range

Ⓐ

$V_{in,cm} = 0$, M_3 is in deep Triode
 M_1 & M_2 are cut off

Ⓑ

$V_{in,cm} > V_{THN}$, M_3 is in triode


V_p increases with $V_{in,cm}$
(acts like a SF)

for $V_{in,cm} \geq V_{as,1,2} + V_{DS,sat,3}$
 M_3 enters Saturation

① M_1, M_2 enter triode when


$$V_{in,cm} > V_{out,1} + V_{THN} = \left(V_{DD} - \frac{R_D I_{D3}}{2} \right) + V_{THN}$$

sets an upper limit on $V_{in,cm}$

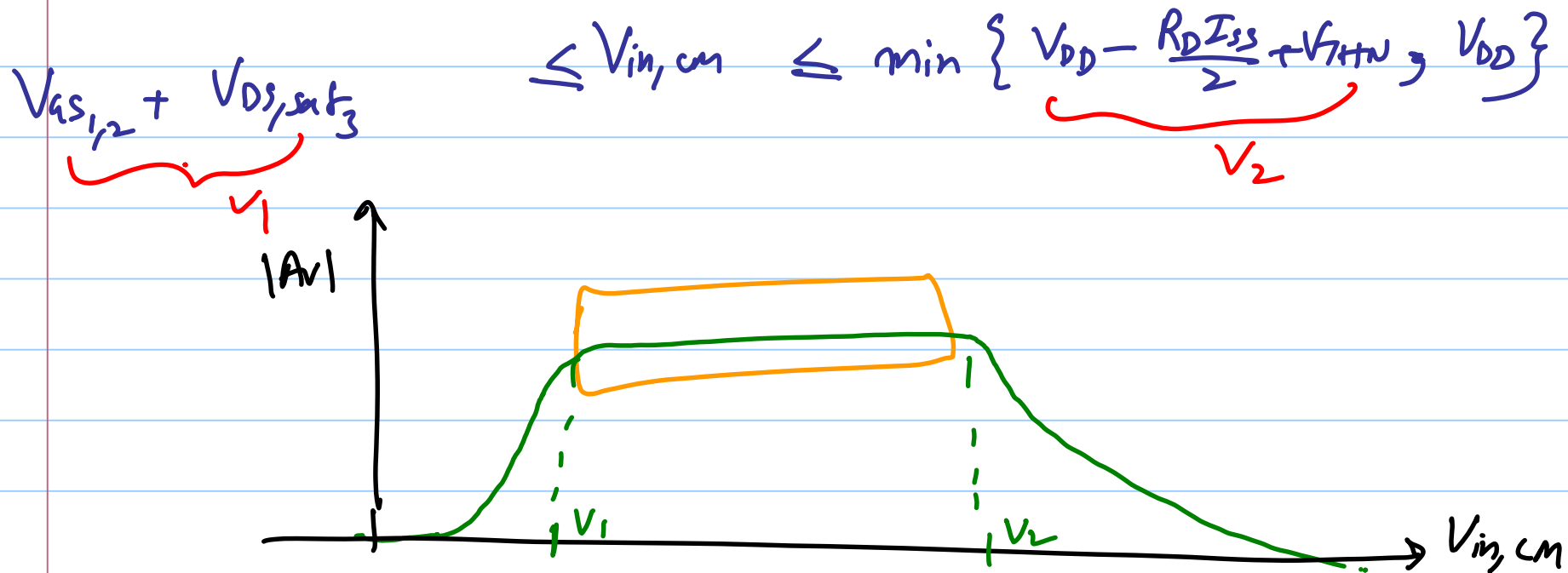

Large Signal Analysis

$$\boxed{I_{D1} + I_{D2} = I_{SS}}$$

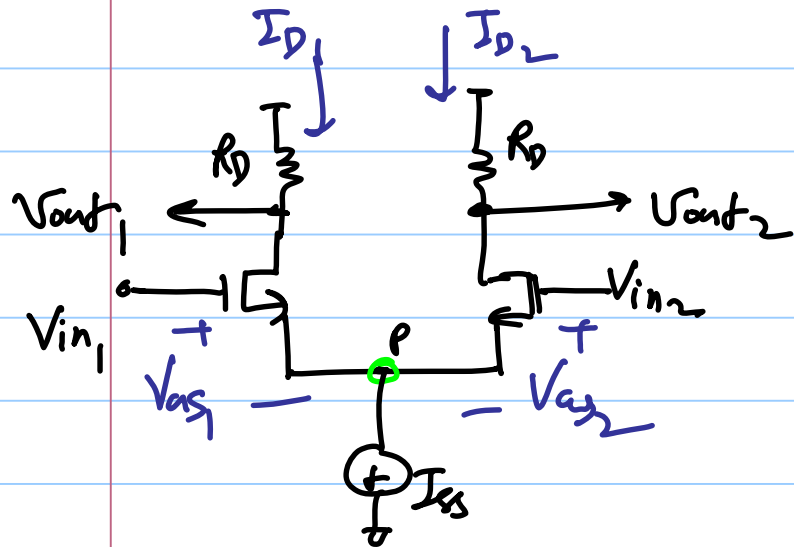

$$\left. \begin{aligned} V_{out1} &= V_{DD} - R_D I_{D1} \\ V_{out2} &= V_{DD} - R_D I_{D2} \end{aligned} \right\}$$

$$(V_{out1} - V_{out2}) = R_D (I_{D2} - I_{D1})$$

Assume symmetry, $\lambda = 0$

$$\text{Voltage @ node P} = V_{in1} - V_{gs1} = V_{in2} - V_{gs2}$$

$$\Rightarrow (V_{in} - V_{in2}) = V_{gs1} - V_{gs2}$$

$$= \left(\sqrt{\frac{2I_{D1}}{\beta}} + V_{THN} \right) - \left(\sqrt{\frac{2I_{D2}}{\beta}} + V_{THN} \right)$$

$$\Rightarrow V_{in_1} - V_{in_2} = \sqrt{\frac{2}{\beta}} [\sqrt{I_{D_1}} - \sqrt{I_{D_2}}]$$

Square both sides & use $I_{D_1} + I_{D_2} = I_{SS}$

$$(V_{in_1} - V_{in_2})^2 = \frac{2}{\beta} (I_{SS} - 2\sqrt{I_{D_1}I_{D_2}})$$

$$\Rightarrow \frac{\beta}{2} (V_{in_1} - V_{in_2})^2 - I_{SS} = -2\sqrt{I_{D_1}I_{D_2}}$$


Square both sides & use the identity

$$\begin{aligned} 4I_{D_1}I_{D_2} &= (I_{D_1} + I_{D_2})^2 - (I_{D_1} - I_{D_2})^2 \\ &= I_{SS}^2 - (I_{D_1} - I_{D_2})^2 \end{aligned}$$

$$\underbrace{I_{D1} - I_{D2}}_{\Delta I_D} = \frac{\beta}{2} \underbrace{(V_{in1} - V_{in2})}_{\Delta V_{in}} \times \sqrt{\frac{4I_{ss}}{\beta} - (V_{in1} - V_{in2})^2}$$

$$(V_{in1} - V_{in2})^2 \ll \frac{4I_{ss}}{\beta}$$

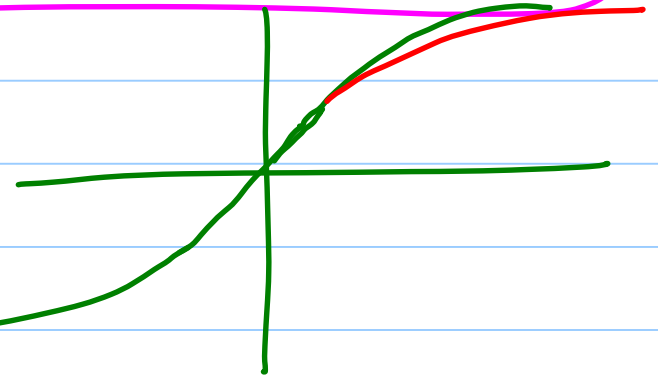$I_{D1} - I_{D2}$ is more linear
with $V_{in1} - V_{in2}$



$$\frac{\partial \Delta I_D}{\partial \Delta V_{in}} = \frac{\beta}{2} \frac{\frac{4I_{ss}}{\beta} - 2\Delta V_{in}^2}{\sqrt{\frac{4I_{ss}}{\beta} - \Delta V_{in}^2}}$$

$$\Delta V_{in} \triangleq 0$$

$$= \frac{\beta}{2} \sqrt{\frac{4I_{ss}}{\beta}} = \sqrt{\beta I_{ss}} = \sqrt{2\beta \left(\frac{I_{ss}}{2}\right)} = g_m \text{ of } M_1 \text{ \& } M_2$$

$$\text{Small signal gain} = \underline{\underline{g_m R_D}}$$

