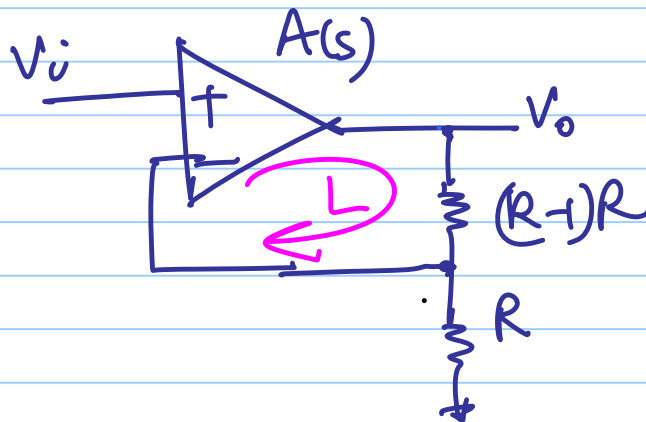


ECE 511 - Lecture 26

Note Title

4/28/2015

① gain



$$\frac{V_o}{V_i} = \frac{k L(s)}{1 + L(s)}$$

closed-loop gain (pointing to $k L(s)$)
loop-gain (pointing to $L(s)$)

$$A(s) = \frac{A_o}{1 + \frac{s}{\omega_o}}$$

at DC,

$$\frac{V_o}{V_i} = \frac{A_o}{1 + \left(\frac{A_o}{k}\right)}, \quad L = \frac{A_o}{k}$$

$$= k \cdot \frac{1}{1 + \frac{k}{A_0}}$$

$$\frac{1}{1+x} \approx 1-x$$

$|x| < 1$

$$= \underline{k} \cdot \left(1 - \underbrace{k \cdot \frac{1}{A_0}}_{\text{relative gain error } \epsilon} \right) = k(1-\epsilon)$$

$$(1+x)^{-1}$$

$$\epsilon = k \cdot \frac{1}{A} \approx \frac{1}{\text{loop-gain}}$$

$$\text{for } k=10$$

$$\epsilon = \frac{10}{A}$$

$$\text{for error} < 1\% \Rightarrow A > 1000 \Rightarrow 60\text{dB}$$

② Small-signal BW

$$\frac{V_o}{V_i}(s) = \frac{kL(s)}{1+L(s)}$$

$$L(s) = \frac{A(s)}{k} \nearrow \frac{A_o}{1+s/\omega_o}$$

$$= \frac{\frac{A_o}{1+s/\omega_o}}{1 + \frac{A_o/k}{1+s/\omega_o}} = \frac{A_o}{1 + \frac{s}{\omega_o} + \frac{A_o}{k}} = \frac{A_o}{\left(1 + \frac{A_o}{k}\right) + \frac{s}{\omega_o}}$$

$$= \underbrace{\frac{A_o}{\left(1 + \frac{A_o}{k}\right)}}_{\text{DC gain}} \cdot \frac{1}{1 + \underbrace{\frac{s}{\omega_o \left(1 + \frac{A_o}{k}\right)}}_{\text{pole}}}$$

$$= \underline{A_{cl}} \cdot \frac{1}{1 + \frac{s}{\omega_{u,loop}}}$$

$$\omega_{u,loop} = \omega_o \left(1 + \frac{A_o}{k} \right)$$

$$\approx \omega_o \cdot \frac{A_o}{k} \quad \text{for} \quad \frac{A_o}{k} \gg 1$$



$$= \frac{(\omega_o \cdot A_o)}{k}$$

$$= \frac{\omega_{un}}{k}$$

3-dB Bandwidth

$f_{un} = f_{2dB} \times k = \text{const.}$
GBW tradeoff

③ Settling !

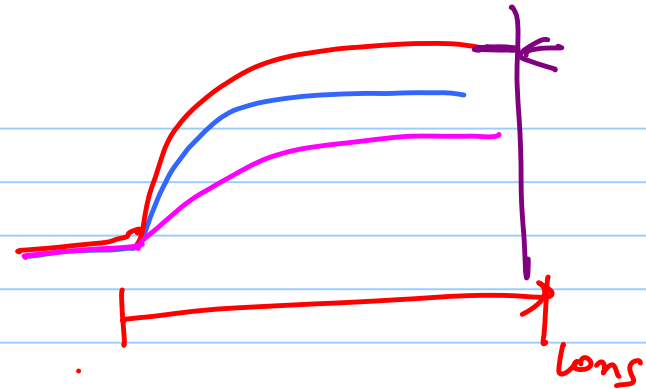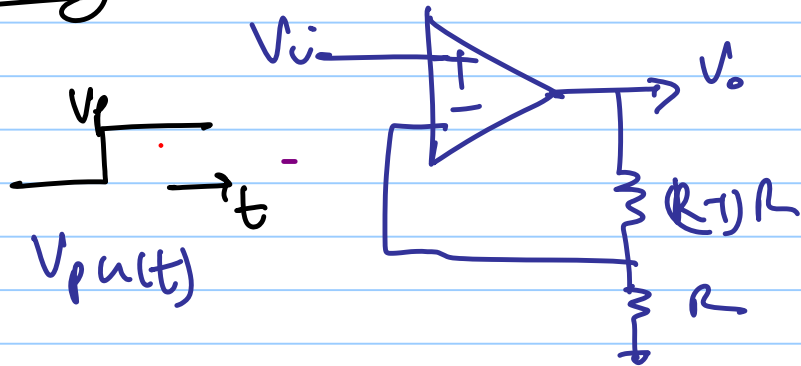

Assuming linear settling (small-signal)

$$V_{out}(s) = \frac{V_p}{s} \times \frac{kL(s)}{1+L(s)}$$

$$V_{out}(t) = \underbrace{kV_p}_{\text{final value}} \cdot \underbrace{\left(1 - e^{-\omega_{y,loop} t}\right)}_{\text{settling}} \cdot u(t)$$

linear settling

for 99% accuracy in settling in a time T_s .

$$1 - e^{-\omega_{u,loop} \cdot T_s} = 0.99$$

$$T_{99\%} = T_s \cdot \ln(100)$$


$$= 4.7 T_s = \frac{4.7}{\omega_{u,loop}}$$

$$T_s = \frac{1}{\omega_{u,loop}}$$



Settling accuracy $\rightarrow \omega_{u,loop} \rightarrow \omega_{un}$
 $k \nearrow$
 $\omega_{un} \rightarrow \frac{g_{m1}}{C_c}$

$$V_{out}(t) = kV_p (1 - e^{-\omega_{y,loop} t}) u(t)$$

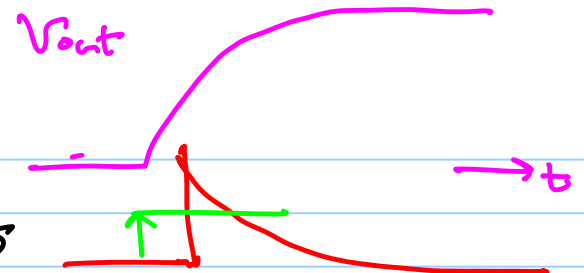
$$\frac{dV_{out}}{dt}(t) = \left(+ \underbrace{kV_p}_{\text{pink}} \cdot \omega_{y,loop} \cdot e^{-\omega_{y,loop} t} \right) u(t)$$




$$I = C_L \cdot \frac{dV_{out}}{dt}$$

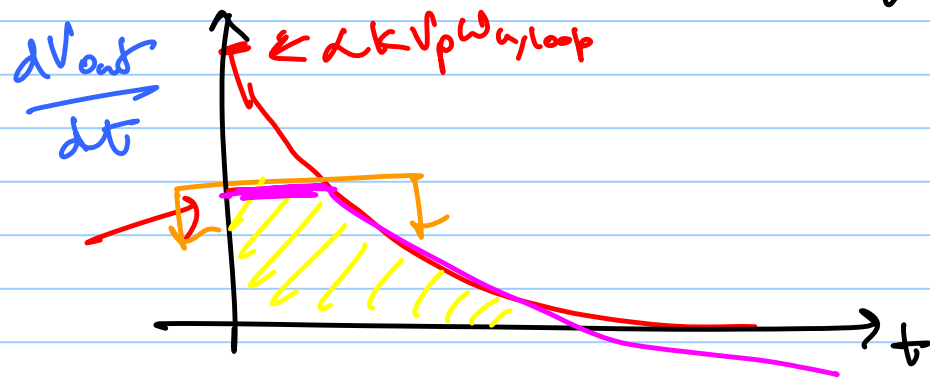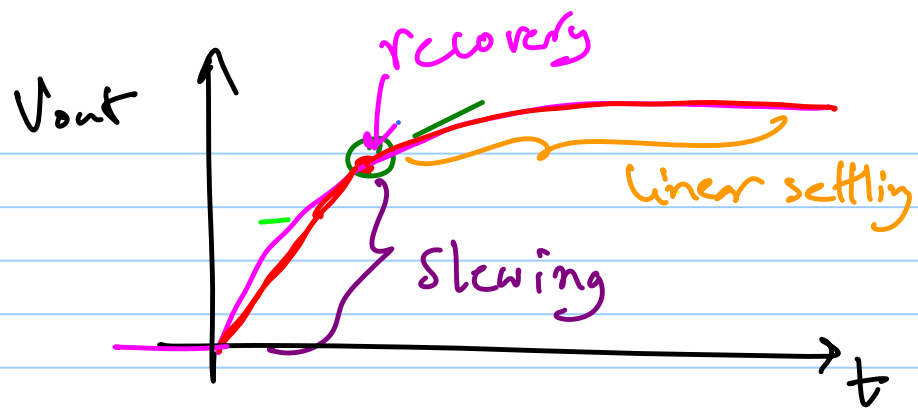

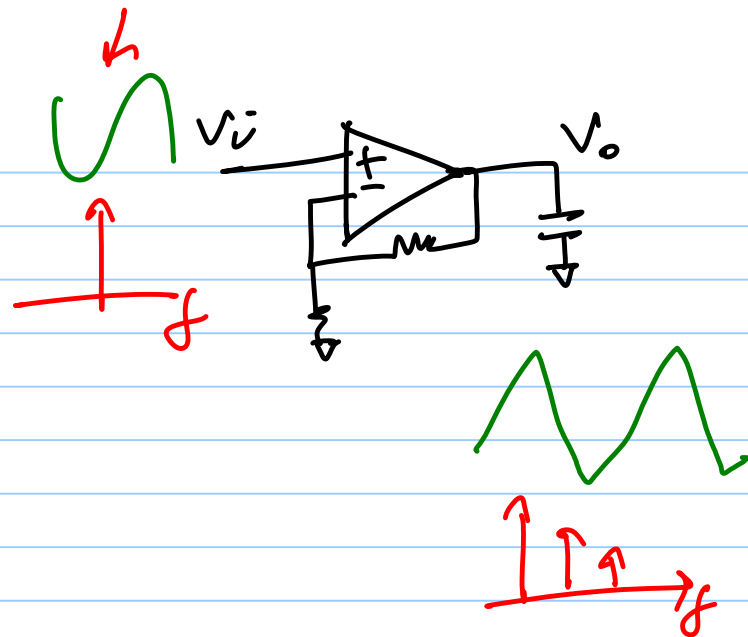
$$SR = \max\left(\frac{dV_{out}}{dt}\right)$$



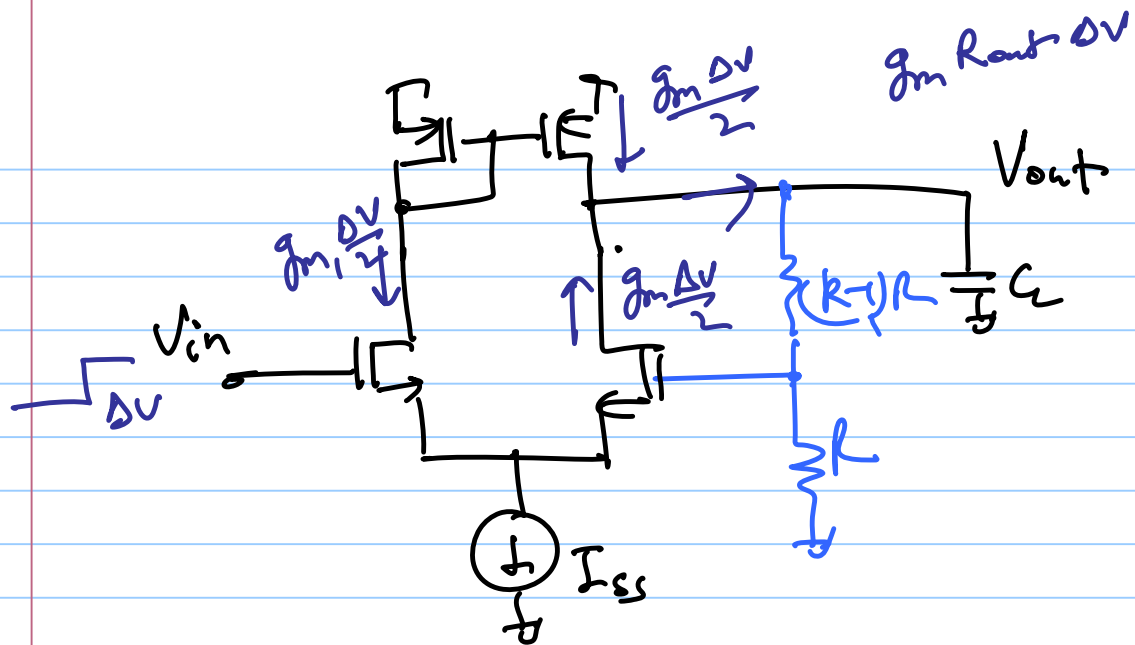

$$R \rightarrow \infty$$

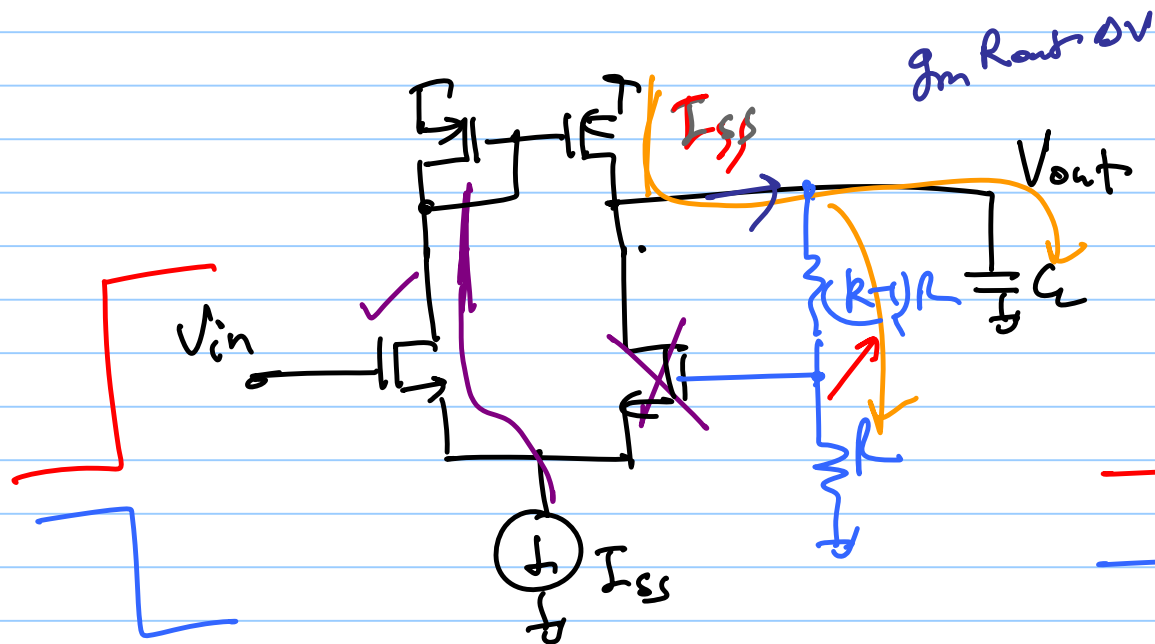

$$g_m R_{out} \gg 1$$

$$\frac{I_{SS}}{C} \approx sR^+$$

slowing

$$sR^- = \frac{I_D}{C}$$

In two-stage
with class-AB
output

$$SR \approx \frac{I_{SS}}{C_c}$$


—

finite settling time

V_{in}




V_{out}

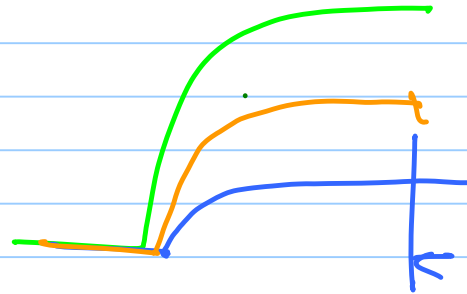

$(1 - e^{-\omega_{cyl} \cdot \beta T_s})$ ← same settling error
linear settling

$k=1$

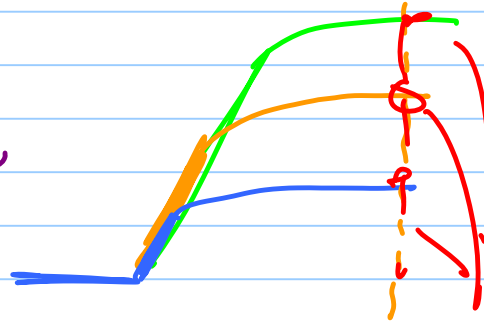* Typically for mixed-signal circuits
slewing should occur
< 25% of settling period




slow-limited
settling

final values have
input-dependent scaling
factor


④ random offset $\leftarrow$ mismatch

$\rightarrow$ estimate & cancel offset

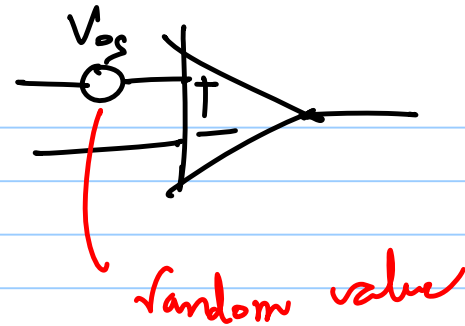

⑤ Noise

Standard 2nd order response

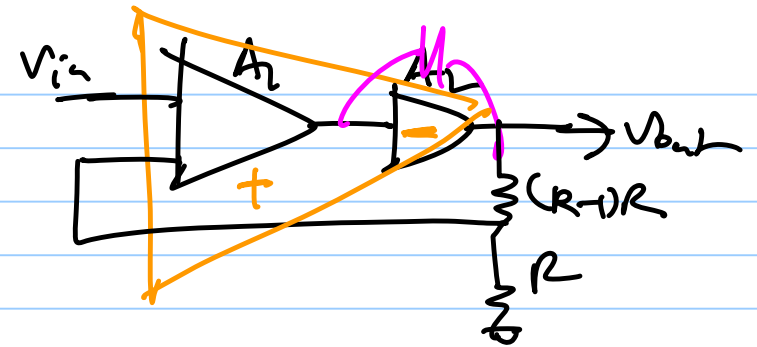

with zero
cancellation


Closed-loop response h

$$\frac{V_o}{V_i}(\omega) = \frac{1}{\left(\frac{s}{\omega_0}\right)^2 + 2\zeta\left(\frac{s}{\omega_0}\right) + 1}$$

$\zeta = \frac{1}{2Q}$

↓ damping factor

← Quality factor

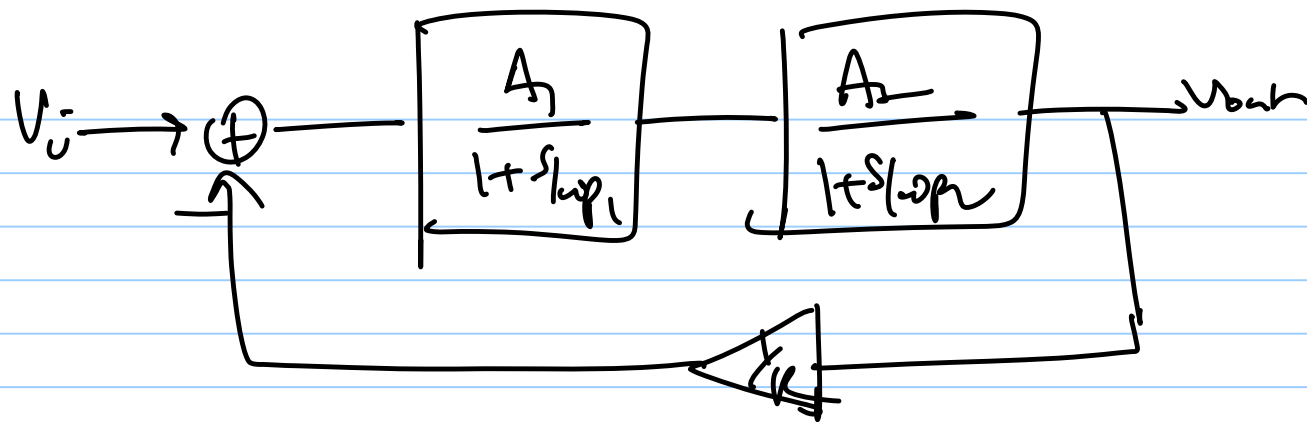

$$\frac{V_o}{V_i} = \frac{k}{\left(1 + \frac{k}{A_o}\right) + s\left(\frac{1}{\omega_{p1}} + \frac{1}{\omega_{p2}}\right)\frac{k}{A_o} + \frac{s^2}{\omega_{p1}\omega_{p2}}\frac{k}{A_o}}$$

$$\zeta = \frac{1}{2} \sqrt{\frac{k}{A_o}} \left(\sqrt{\frac{\omega_{p2}}{\omega_{p1}}} + \sqrt{\frac{\omega_{p1}}{\omega_{p2}}} \right)$$

$$\text{for } \frac{\omega_{p2}}{\omega_{p1}} = \frac{A_0}{k}$$

$$\zeta = \frac{1}{2} \sqrt{\frac{k}{A_0}} \left(\sqrt{\frac{A_0}{k}} + \sqrt{\frac{k}{A_0}} \right)$$

$$= \frac{1}{2} x \left(x + \frac{1}{x} \right)$$

$$\leq 1$$

$$x = \sqrt{\frac{A_0}{k}}$$

$$x + \frac{1}{x} \leq 2x$$

$\zeta > 1$ overdamped
 $\zeta = 1$ critically damped
 $\zeta < 1$ underdamped

fastest settling is for $\zeta = \frac{1}{\sqrt{2}}$

$$\Rightarrow \phi_m = 63.6^\circ$$

for $\phi_m = 60^\circ$
 $\hookrightarrow \zeta = 0.56$