


ECE 511: Lecture 27

Note Title


4/30/2015

Bandgap References: PVT-independent Reference


BMR were not temperature insensitive

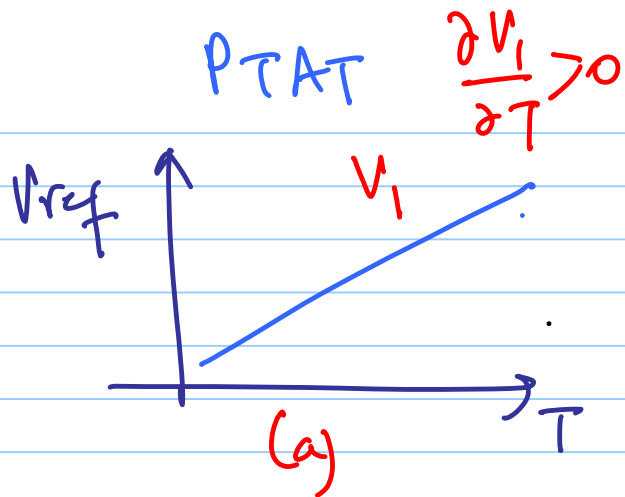

proportional to absolute temperature

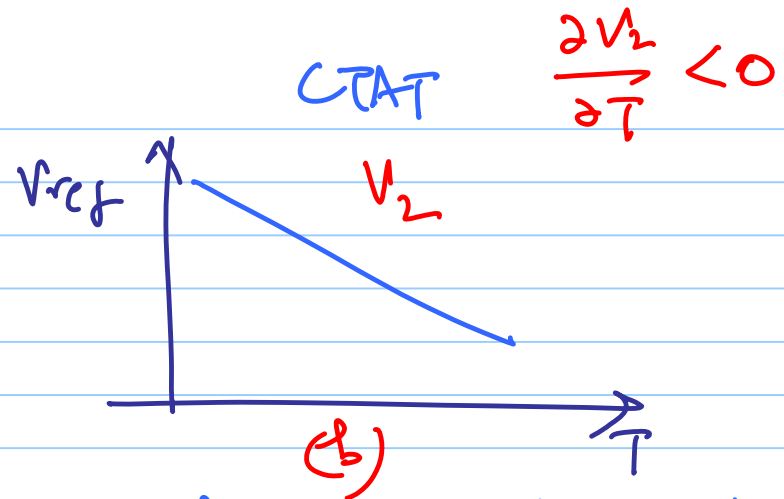

Complementary to absolute temperature

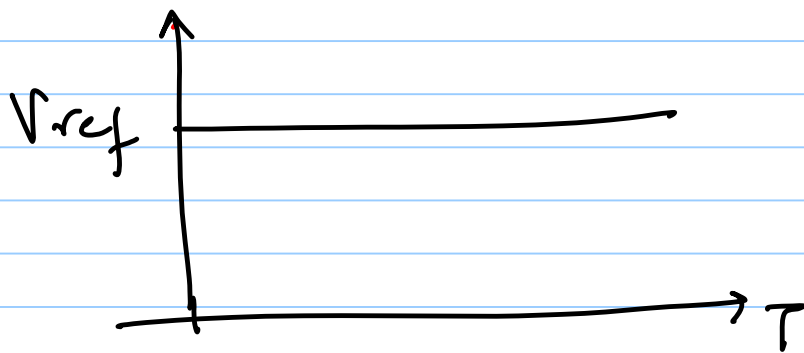

Zero temperature coefficient
Zero TempCo (ZTC)

We can design a ZTC reference


$$V_{ref} = \alpha_1 V_1 + \alpha_2 V_2$$

↓ PTAT ↓ CTAT

→ ①

$$\frac{\partial V_{ref}}{\partial T} = \alpha_1 \frac{\partial V_1}{\partial T} + \alpha_2 \frac{\partial V_2}{\partial T} = 0 \quad \text{for some } \alpha_1, \alpha_2$$

①

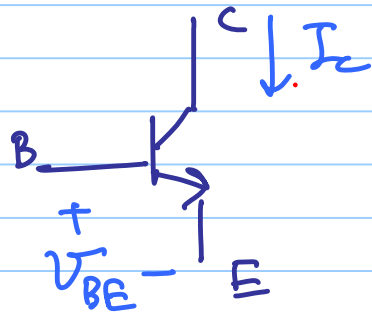

$$I_C = I_S e^{\frac{V_{BE}}{V_T}}$$

$$V_T = \frac{kT}{q} = 26 \text{ mV} \text{ at } 27^\circ\text{C} \text{ } 300\text{K}$$

$$I_S \propto \mu kT \cdot n_i^2 \rightarrow \textcircled{1}$$


$$\mu \propto \mu_0 T^m, \quad m = -\frac{3}{2}$$

$$n_i^2 \propto T^3 e^{-E_g/kT}$$

$$I_S = b T^{(4+m)} e^{-E_g/kT} \rightarrow \textcircled{2}$$

$$V_{BE} = V_T \ln \left(\frac{I_C}{I_S} \right)$$

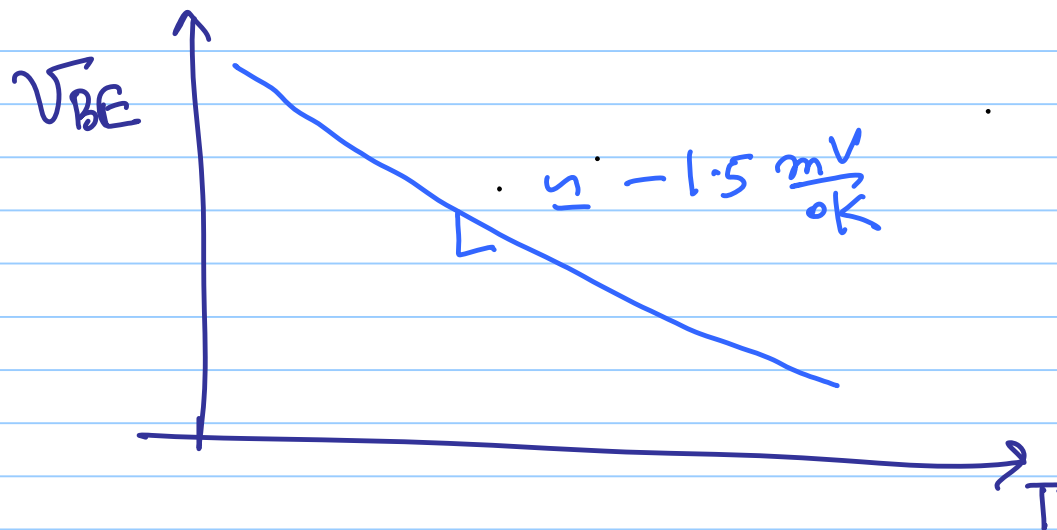
$$\frac{\partial V_{BE}}{\partial T} = \frac{V_{BE} - (1+m)V_T - E_g/q}{T}$$



$$\frac{\partial V_{BE}}{\partial T} \approx -1.5 \frac{mV}{^\circ K}$$

@ $T = 300K$


$$V_{BE} = 0.65 - 0.78$$

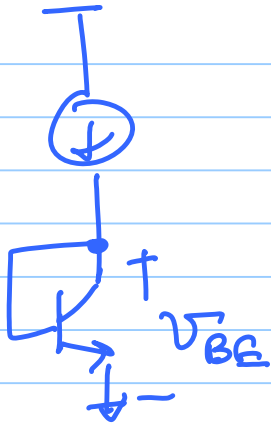

V_{BE} itself is a CTAT

② PTAT

2 BJT with unequal current

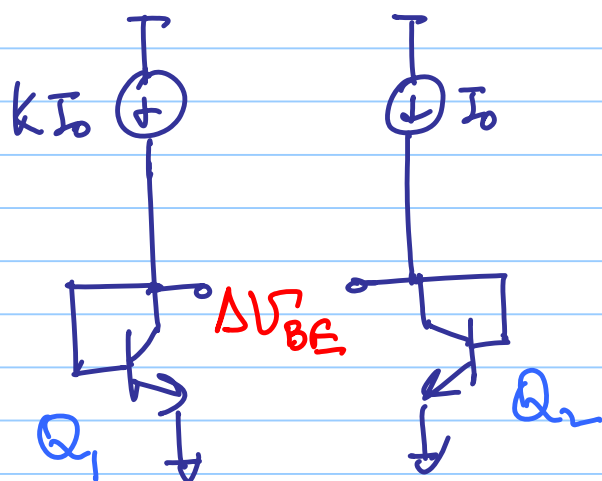

$$V_{BE1} \propto \ln(I_1/I_S)$$



$$V_{BE2} \propto \ln(I_2/I_S)$$

$$V_{BE1} - V_{BE2} \propto \ln(k)$$


$$\Delta V_{BE} = V_T \ln\left(\frac{kI_0}{I_{S1}}\right) - V_T \ln\left(\frac{I_0}{I_{S2}}\right), \quad I_{S1} = I_{S2}$$

$$\Rightarrow \Delta V_{BE} = V_T \ln(K) = \frac{kT}{q} \ln(K) \quad \text{PTAT}$$
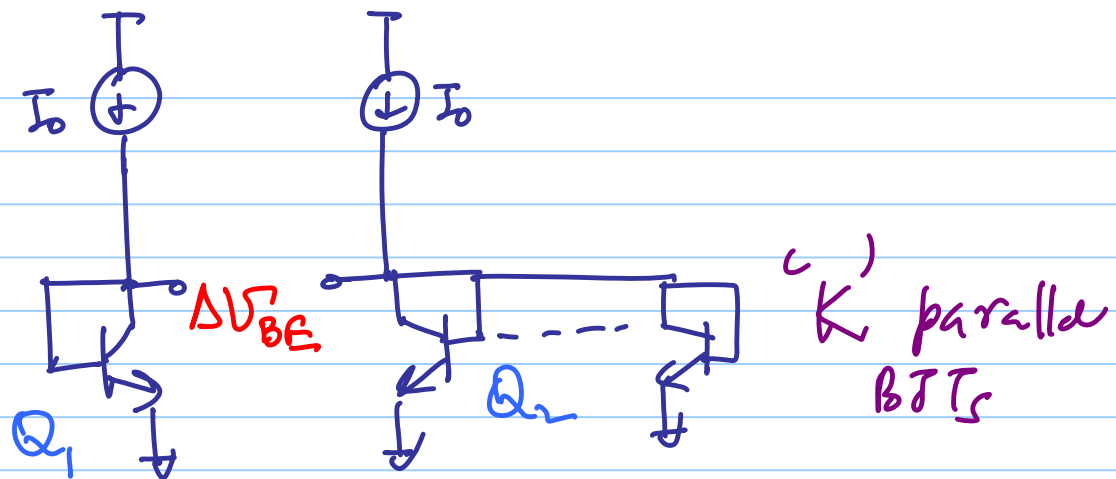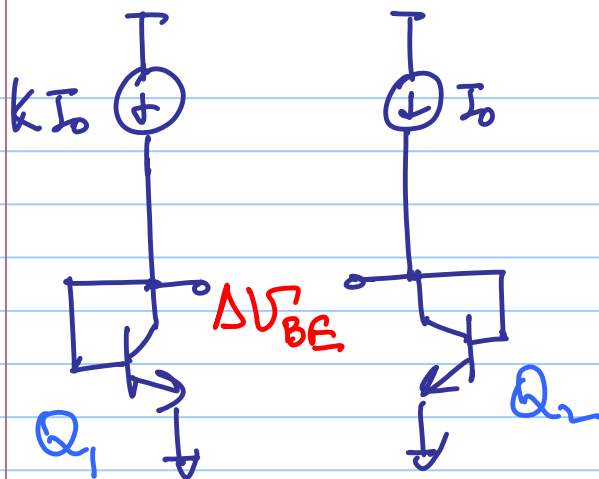
$$\boxed{\frac{\partial \Delta V_{BE}}{\partial T} = \frac{k}{q} \ln(K)}$$


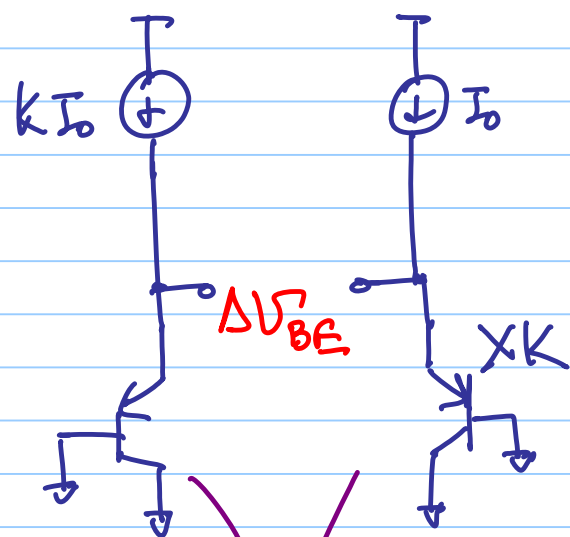
$$\Delta V_{BE} = V_T \ln\left(\frac{I_1}{I_2}\right) = V_T \ln\left(\frac{I_0}{I_0/k}\right) = V_T \ln(k)$$



parasitic pnp diode
in CMOS technology

Bandgap Reference

$$V_{ref} = \alpha_1 V_{BE} + \alpha_2 \overbrace{(V_T \ln K)}^{\Delta V_{BE}}$$

$$\frac{\partial V_{ref}}{\partial T} = 0 = \alpha_1 \frac{\partial V_{BE}}{\partial T} + \alpha_2 \left(\frac{k}{q} \ln K \right)$$

$$\alpha_2 \ln(K) = - \frac{\alpha_1 \cdot \left(\frac{\partial V_{BE}}{\partial T} \right)}{k/q}$$

-1.5 mV/K

0.087 mV/K

$$= \alpha_1 \times \frac{1.5 \text{ mV/K}}{0.087 \text{ mV/K}}$$

$$\Rightarrow \alpha_2 \ln k = 17.2 \alpha_1$$


Choose $\alpha_1 = 1$

$$\Rightarrow \alpha_2 \ln(k) = 17.2$$

We have

$$\begin{aligned} V_{REF} &= \alpha_1 \cdot V_{BE} + \alpha_2 \ln(k) V_T \\ &= V_{BE} + 17.2 V_T \end{aligned}$$

If we can somehow make $v_{01} = v_{02}$

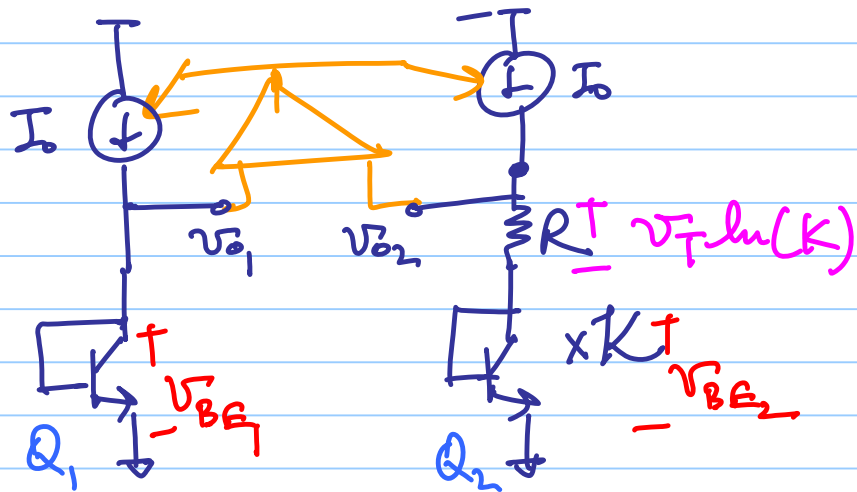

$$V_1 = V_2 = V_{BE_1} = V_{BE_2} + I_0 R$$


$$\Rightarrow I_0 R = \sqrt{B E_1} - \sqrt{B E_2} \\ = \sqrt{f} h(K)$$

$$\Rightarrow V_{O2} = \underbrace{\alpha_1}_{=1} \underbrace{V_{BE2}}_{\text{CTAT}} + \underbrace{\alpha_2}_{=1} \underbrace{V_T \ln(K)}_{\text{PTAT}}, \text{ here } \alpha_1 = \alpha_2 = 1$$

for $\frac{\partial V_{02}}{\partial T} = 0$, we need $\ln(k) = 17.2$ No!
 $k = e^{17.2}$

$\Rightarrow$ We need a large d_2

Ex.

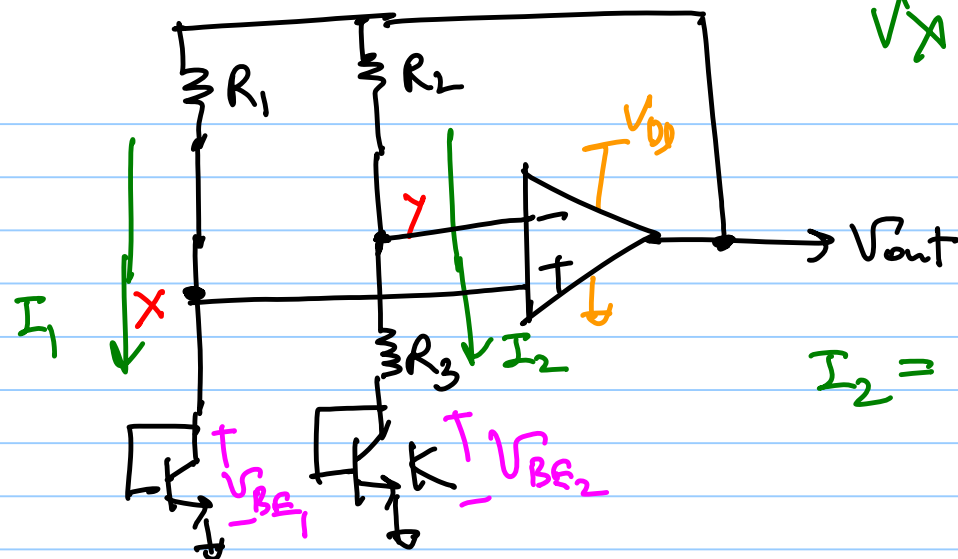

V_{BE1} & V_{BE2} are equal

$$I_2 = \frac{V_{BE1} - V_{BE2}}{R_3} = \frac{V_T \ln(K)}{R_3}$$


$$V_{out} = V_{BE2} + I_2 (R_3 + R_2)$$

$$= V_{BE2} + \frac{V_T \ln(K)}{R_3} (R_3 + R_2)$$

$$= V_{BE2} + V_T \ln(k) \underbrace{\left(1 + \frac{R_2}{R_3}\right)}_{\alpha_2}$$


$\alpha_1 = 1$

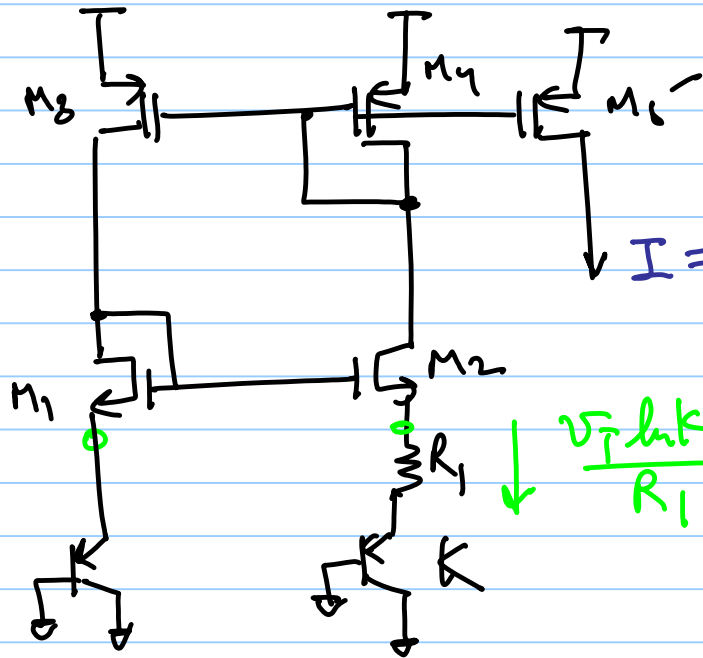for example, for $k=81$, $\frac{R_2}{R_3} = 4$



$$I = \frac{PTAT}{R} \text{ type}$$

$$\downarrow \frac{V_T \ln k}{R_1}$$

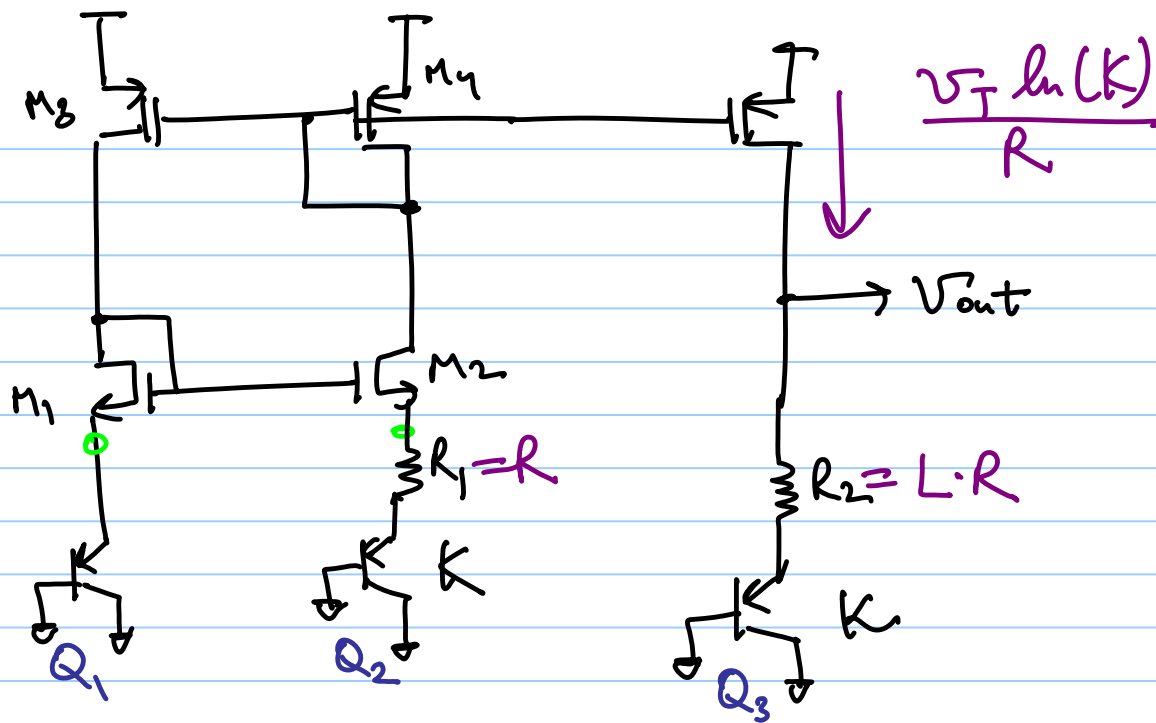

$$V_{out} = V_{BE3} + V_T \ln(K) \cdot L \alpha_2$$

$L \cdot \ln(K) = 17.2$
choose any $\{L, K\}$

Σ_x .


$K=8$ (select)

$n=1$

$$L = \frac{\left| \left(\frac{\partial V_{BE}}{\partial T} \right) \right|}{\ln(K) \left(\frac{\partial V_T}{\partial T} \right)}$$

$$= \frac{1.8 \text{ mV}}{0.087 \text{ mV} \ln(8)} = 8.4834$$
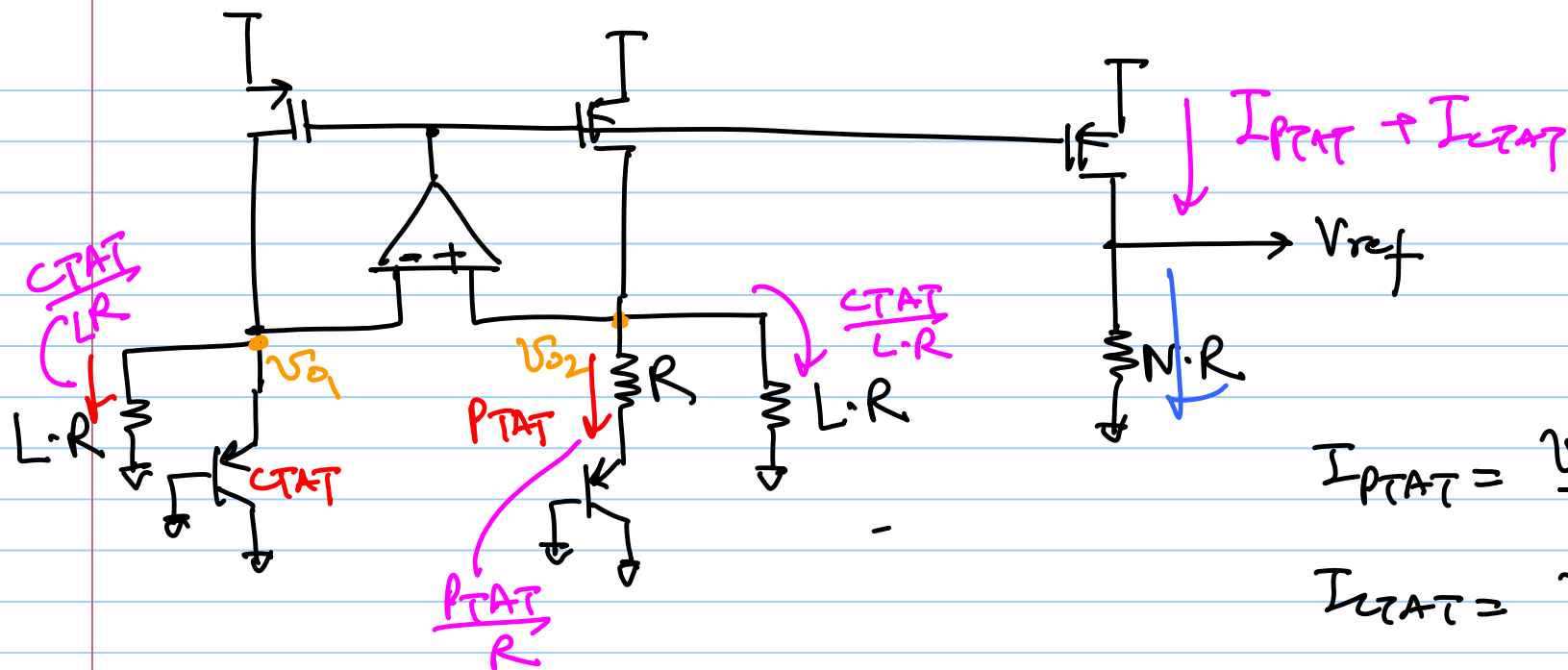
$$V_{ref} = V_{BE3} + \underbrace{L \cdot V_T \ln(K)}_{\text{ratio of } R} \approx 1.28 \text{ V}$$



$$I_{PTAT} = \frac{V_T \ln K}{R}$$

$$I_{CTAT} = \frac{V_{BE1}}{L \cdot R}$$

$$V_{ref} = (I_{PTAT} + I_{CTAT}) \cdot N \cdot R$$

$$= \left(\frac{V_T \ln K}{R} + \frac{V_{BE1}}{L \cdot R} \right) \cdot N \cdot R$$

$$= \underbrace{(N)}_{\alpha_2} V_T \ln(K) + \underbrace{\left(\frac{N}{L}\right)}_{\alpha_1} V_{BE1}$$

$$\frac{\partial V_{ref}}{\partial T} = N \ln(K) \left(\frac{K}{Q} \right) + \frac{N}{L} \left(\frac{\partial V_{BE}}{\partial T} \right) = 0$$

$$N \left[\frac{K}{Q} \ln K + \frac{1}{L} \cdot \left(-1.5 \frac{mV}{K} \right) \right] = 0$$

independent of N

$$L = \frac{1.8}{\ln(k) \cdot 0.0085} \leftarrow \text{doesn't depend upon } N$$

ϵ_x . $k=8 \Rightarrow L=9.41$

$$V_{ref} = V_T \ln k \cdot N + \frac{N}{L} \cdot V_{BE1}$$

$$N = \frac{V_{ref}}{V_T \ln(k) + \frac{V_{BE1}}{L}} \rightarrow 0.7$$

for $V_{ref} = 0.5V \Rightarrow N = \frac{0.8}{0.052 + \frac{0.7}{9.41}} = 3.91$

low- V_{DD} BGR

Why bandgap?

$$V_{REF} = V_{BE} + V_T \ln(k)$$

$$\text{for } \frac{\partial V_{REF}}{\partial T} = 0$$

...

$$\Rightarrow V_{ref} = \frac{E_g}{2} + (4+m) V_T$$

$$V_{ref} \rightarrow \frac{E_g}{2} \leftarrow \text{Bandgap Voltage} = 1.12V \quad \text{as } T \rightarrow 0$$