


ECE 511 - Lecture 2

Note Title

1/15/2015

NMOS in Saturation

Bias point $\rightarrow$
(V_{GS}, I_D)

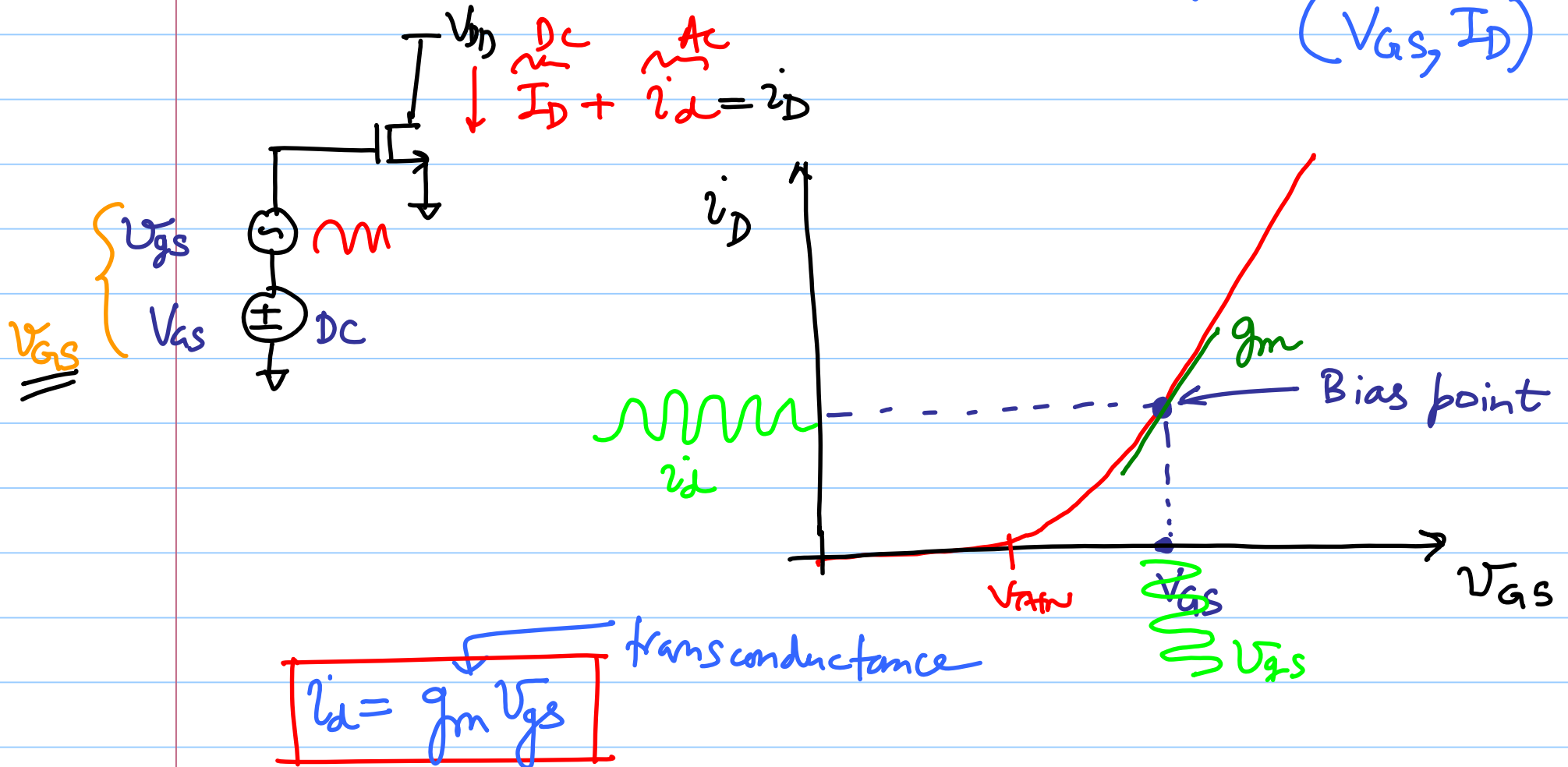

$$g_m = \left. \frac{\partial i_D}{\partial V_{GS}} \right|_{V_{GS} = V_{GS} \leftarrow}$$

$$i_D = \frac{k_p n}{2} \frac{W}{L} (V_{GS} - V_{THN})^2$$

$$= \underbrace{k_p n \cdot \frac{W}{L}}_{\beta_n} (V_{GS} - V_{THN})$$

$$g_m = \beta_n (V_{GS} - V_{THN}) = \beta V_{OV} \longrightarrow \textcircled{1}$$

$$\checkmark I_D = \frac{\beta_n}{2} (V_{GS} - V_{THN})^2 \longrightarrow \beta_n = \frac{2I_D}{(V_{GS} - V_{THN})^2}$$

$$\Rightarrow V_{GS} - V_{THN} = \sqrt{\frac{2I_D}{\beta_n}}$$




$$\Rightarrow g_m = \beta_n \cdot \sqrt{\frac{2I_D}{\beta_n}} = \sqrt{2\beta_n I_D} \longrightarrow \textcircled{2}$$

$$g_m = \beta_n \cdot (V_{GS} - V_{THN})$$

$$= \frac{2I_D}{(V_{GS} - V_{THN})^2} \times (V_{GS} - V_{THN}) = \frac{2I_D}{V_{GS} - V_{THN}} \rightarrow \textcircled{3}$$



$$g_m \begin{cases} = \beta V_{OV} \\ = \sqrt{2\beta I_D} \\ = \frac{2I_D}{V_{OV}} \end{cases}$$

$$\beta = k_{Pn} \cdot \frac{W}{L}$$

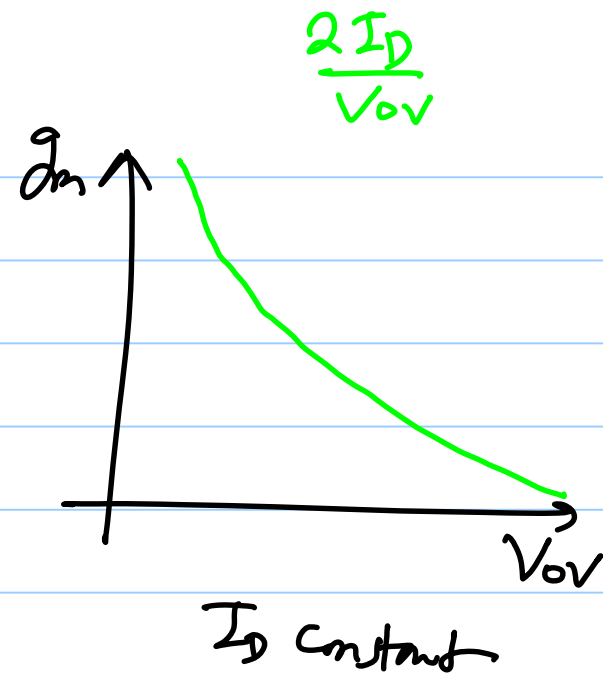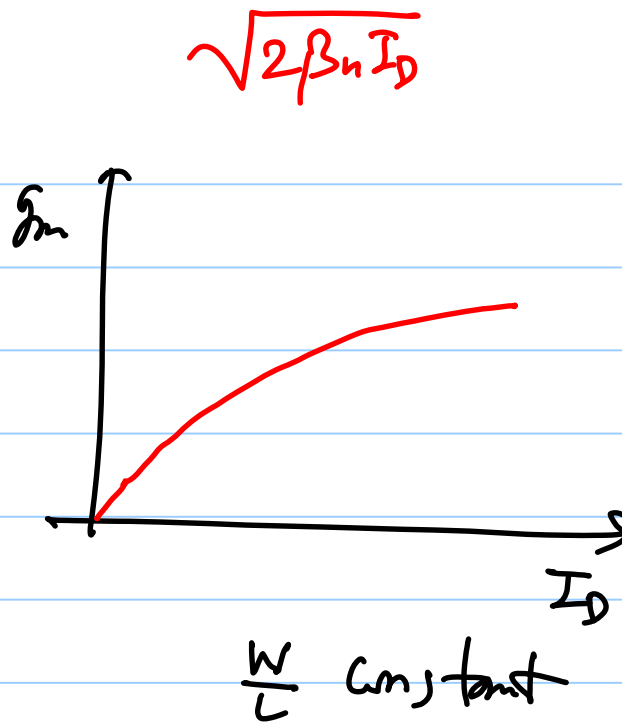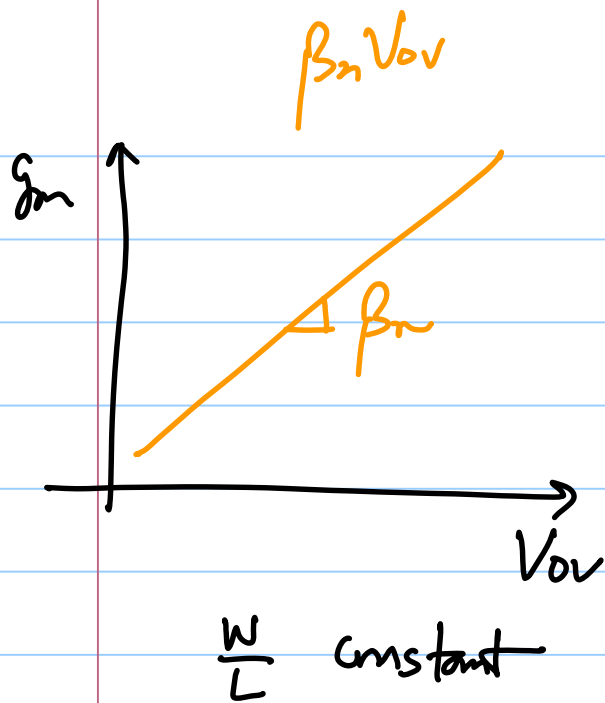


Body-effect ✓

$$V_{THN}(V_{SB}) = V_{THN0} + \gamma_n \left(\sqrt{2|V_{FB}| + V_{SB}} - \sqrt{2|V_{FB}|} \right)$$

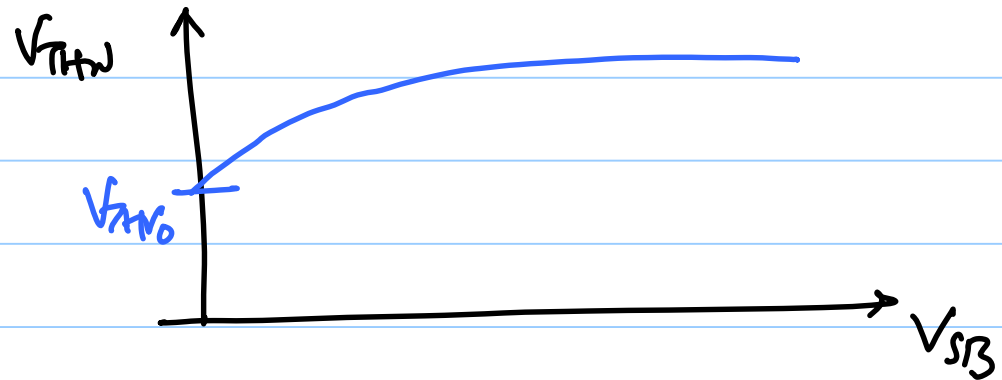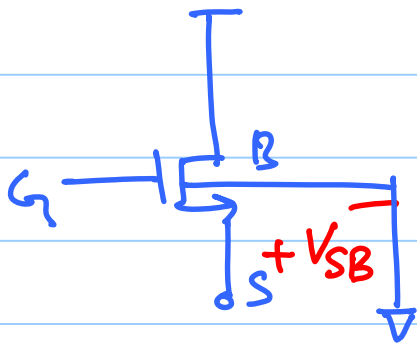

Small-signal model of a NMOS

$$i_d = g_m v_{gs}$$


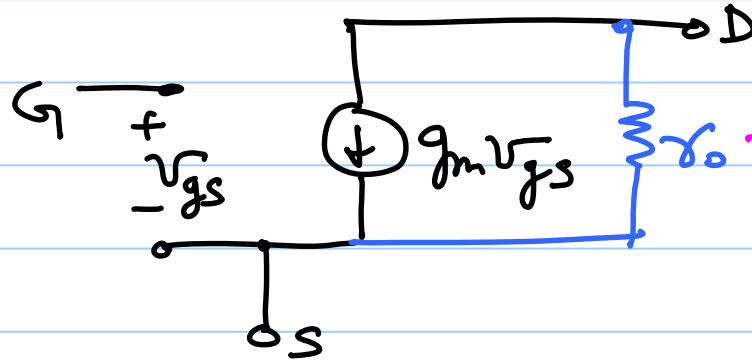


$$r_o = \left(\frac{\partial i_d}{\partial v_{ds}} \right)^{-1}_{v_{gs}=V_{gs}}$$

$$= \frac{1}{\lambda I_{D,sat}}$$

$$\downarrow \Rightarrow \lambda \uparrow \Rightarrow r_o \downarrow$$

Body-effect transconductance:

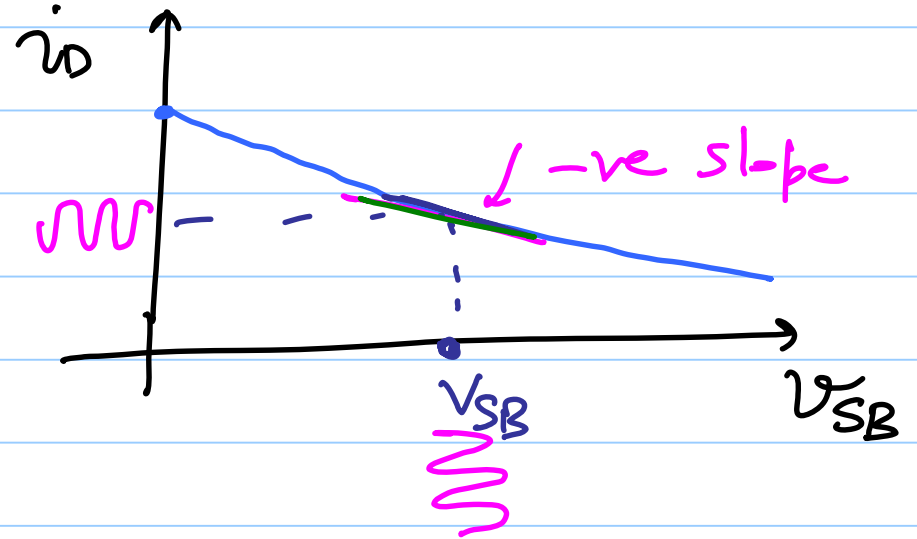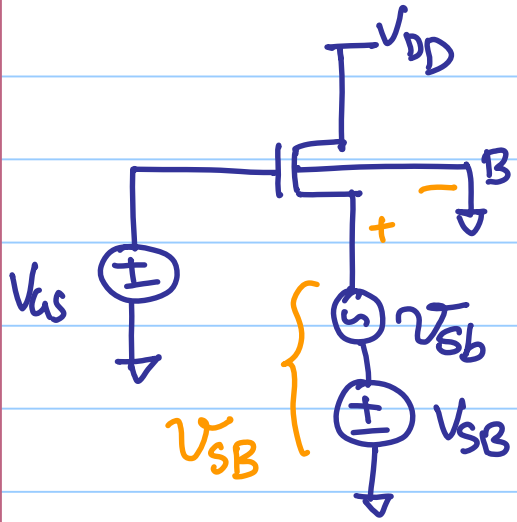

$$v_d = g_{mb} \cdot v_{sb}$$

$$g_{m_b} = \left. \frac{\partial i_D}{\partial v_{SB}} \right|_{v_{SB} = V_{SB}}$$

$$= \frac{2}{2V_{SB}} \left[\frac{K_p n}{2} \cdot \frac{W}{L} (V_{AS} - V_{THN})^2 \right] \bigg|_{V_{SB}=V_{SB}}$$

$$= \underbrace{K_P n \cdot \frac{W}{L} (V_{GS} - V_{THn})}_{g_m} \cdot \left(-\frac{\partial V_{THn}}{\partial V_{SB}} \right) \bigg|_{V_{SB}=V_{SB}}$$

$$= g_m \cdot \underbrace{\left(-\frac{\partial}{\partial} (2|V_{FB}| + V_{SB})^{-1/2} \right)}_{\eta}$$


$$g_{mB} = \eta g_m$$

$$\boxed{g_{mB} = -|\eta| g_m}$$



$$\eta = \frac{-\partial}{2 \sqrt{2|V_{FB}| + V_{SB}}}$$

$$|\eta| < 1$$

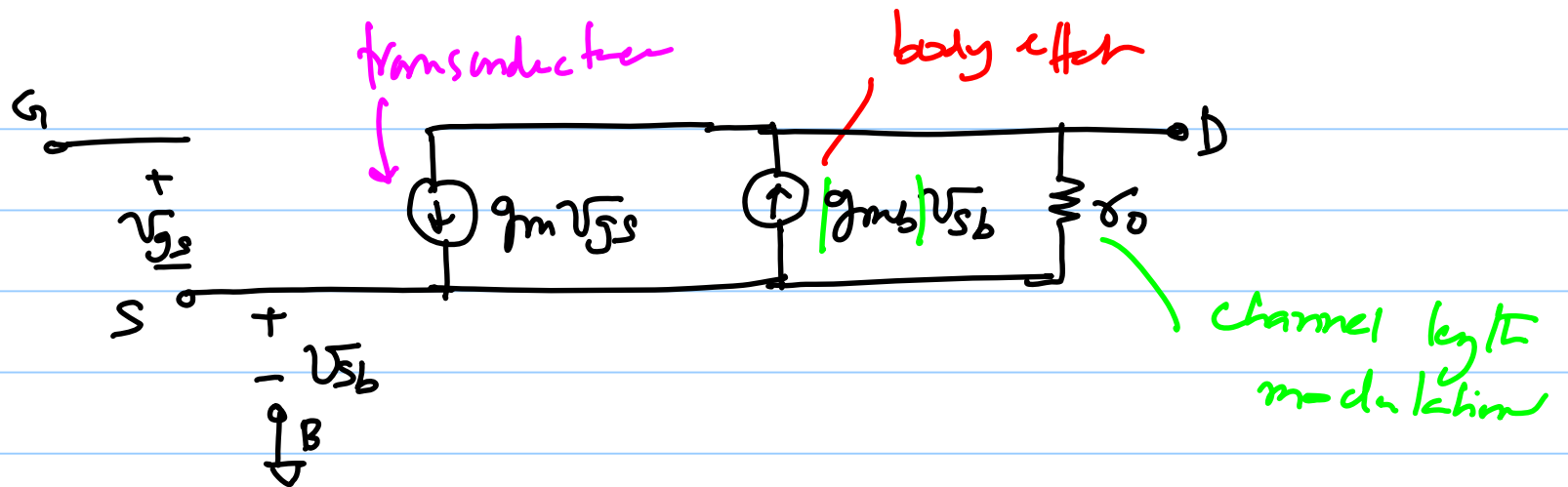the -ve sign indicates the opposing nature of
 $V_{SB} \uparrow \Rightarrow i_D \downarrow$



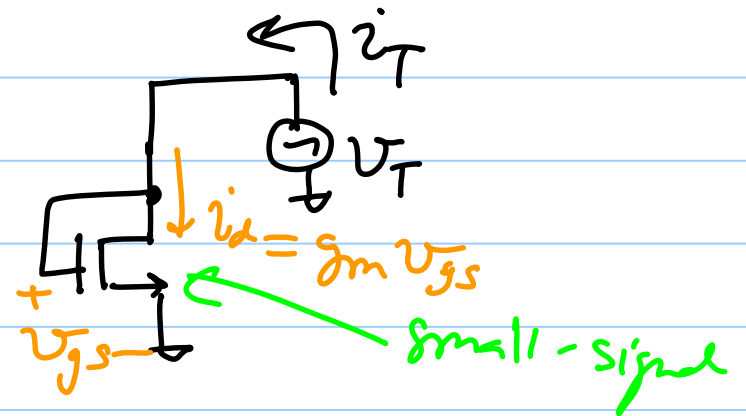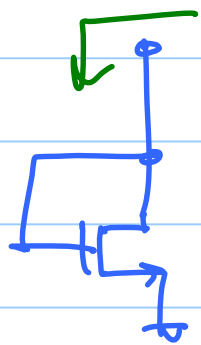
diode load R_{out} $\swarrow$ small-signal impedance looking into the drain




$$R_{out} = \frac{V_T}{i_T}$$

$$= \frac{v_{gs}}{g_m v_{gs}} = \frac{1}{g_m}$$

$$i_T = i_d = g_m v_{gs}$$

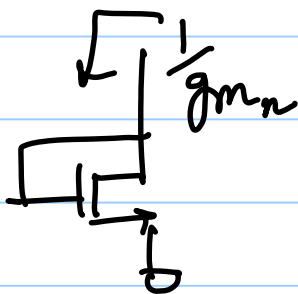
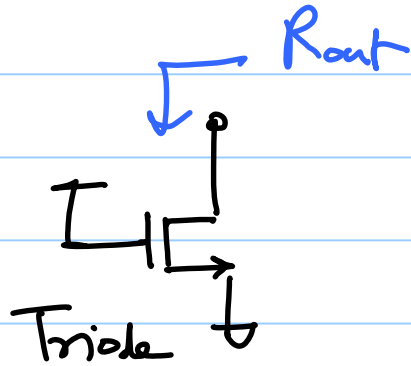
$$\frac{1}{g_{mp}} \longrightarrow \beta (V_{as} - V_{thn})$$



$$R_{out} = R_{in} = \frac{1}{k \mu_n \frac{W}{L} (V_{as} - V_{thn})}$$

↑ much larger

≪

$$\frac{1}{g_m}$$

Example of small-signal analysis

① Given a circuit, draw the DC picture
↳ short ac ^{voltage} sources
open ac currents

Caps will open
Find all bias conditions for all devices

② Use DC values from ①, to calculate
Small-signal parameters (g_m , r_o , $g_{m6} \dots$)

↳ Linearization about the bias point

③ Draw AC picture

↳ replace devices by their small-signal models

↳ Short DC voltage sources
open DC current sources

Solve for the AC values in circuit

④ Superposition of DC & AC quantities