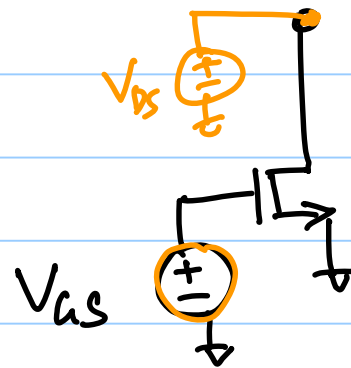



ECE 511 - Lecture 5

Note Title

1/29/2015



$$I_D = f(V_{gs}, V_{ds})$$

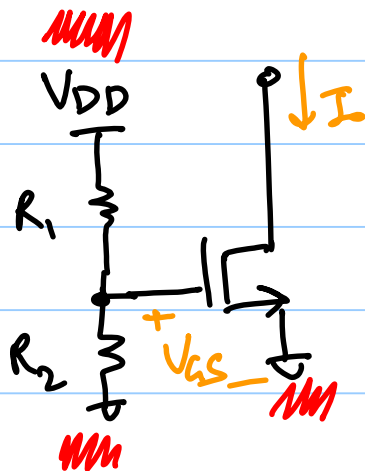


$$I_o = \beta \left(\frac{R_2}{R_1 + R_2} V_{DD} - V_{thn} \right)^2$$


I_{out} depends upon $\rightarrow V_{DD}$, process,
PVT-dependent

Solⁿ: Create a stable "precise" reference generator and then copy the currents

Golden reference

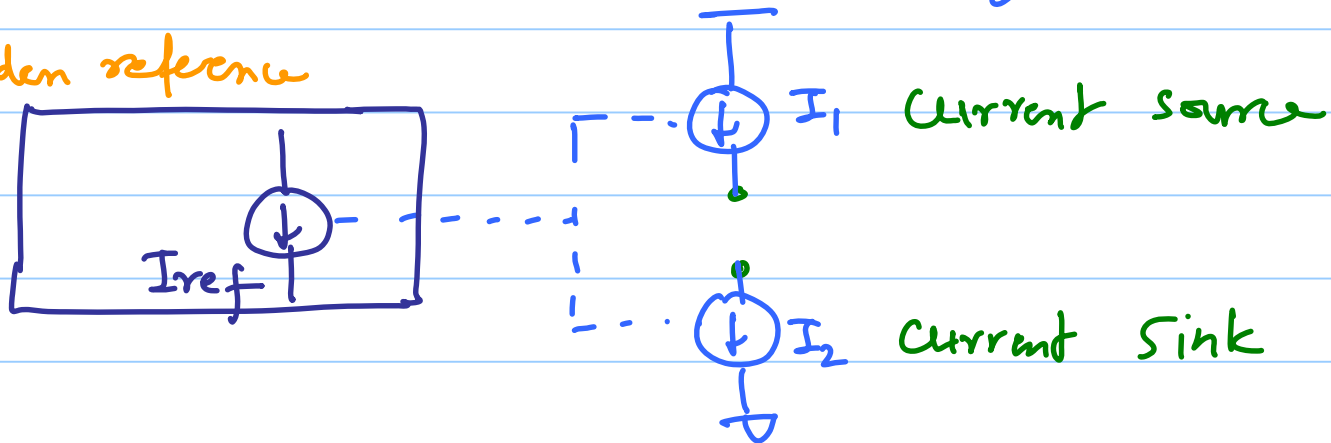


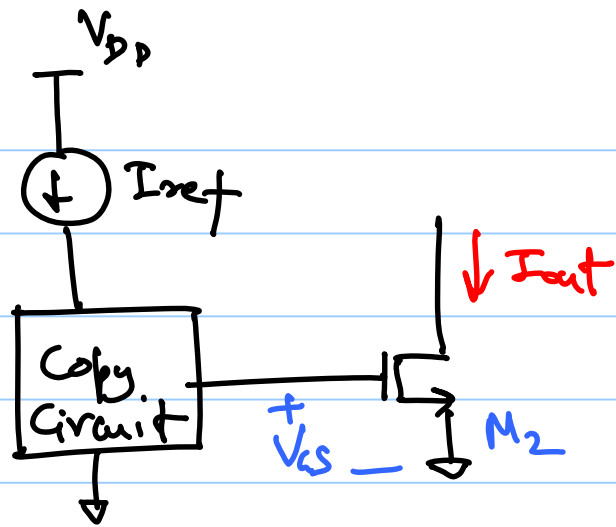* first study the "copying" operation
later come back to precise reference




(assume $\lambda=0$)

$$I_{DS} = f(V_{GS})$$

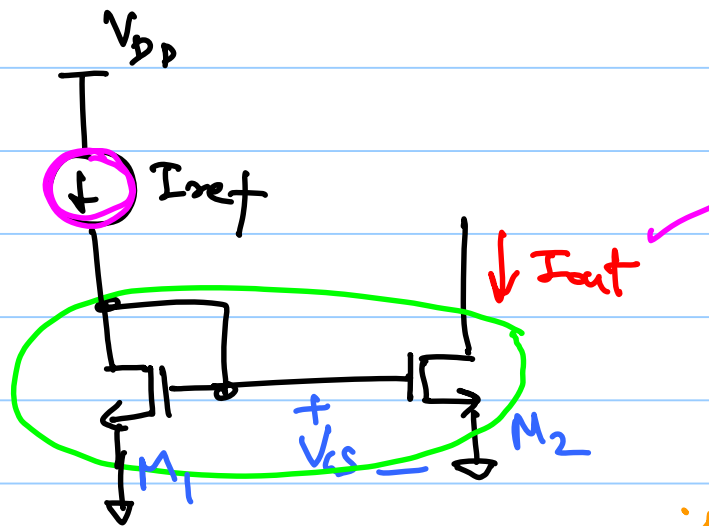

$$V_{GS} = \sqrt{\frac{2I_{ref}}{\beta}} + V_{THN}$$

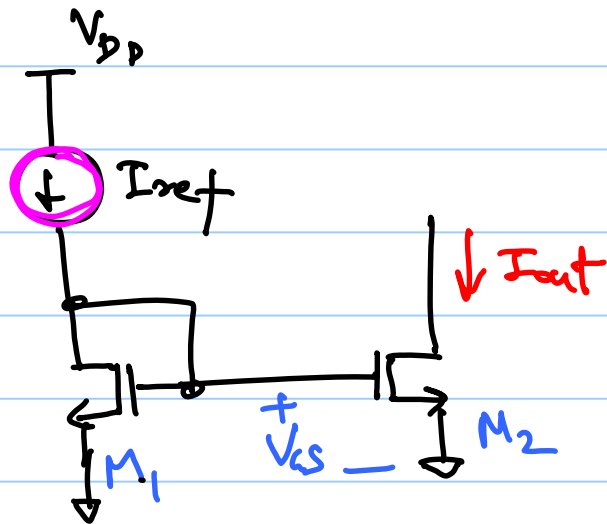if no channel length modulation
 $I_{out} \triangleq I_{ref}$



$$\lambda = 0$$

$$I_{ref} = \frac{1}{2} k_p n \left(\frac{W}{L} \right)_1 (V_{GS} - V_{THN})^2$$

$$I_{out} = \frac{1}{2} k_p n \left(\frac{W}{L} \right)_2 (V_{GS} - V_{THN})^2$$


$$\frac{I_{out}}{I_{ref}} = \frac{\left(\frac{W}{L} \right)_2}{\left(\frac{W}{L} \right)_1}$$

$$= \frac{W_2}{W_1} \quad \text{for the same lengths}$$



$$\lambda = 0$$


$$\frac{J_{out}}{I_{ref}} = \frac{W_2}{W_1}$$

for same
L


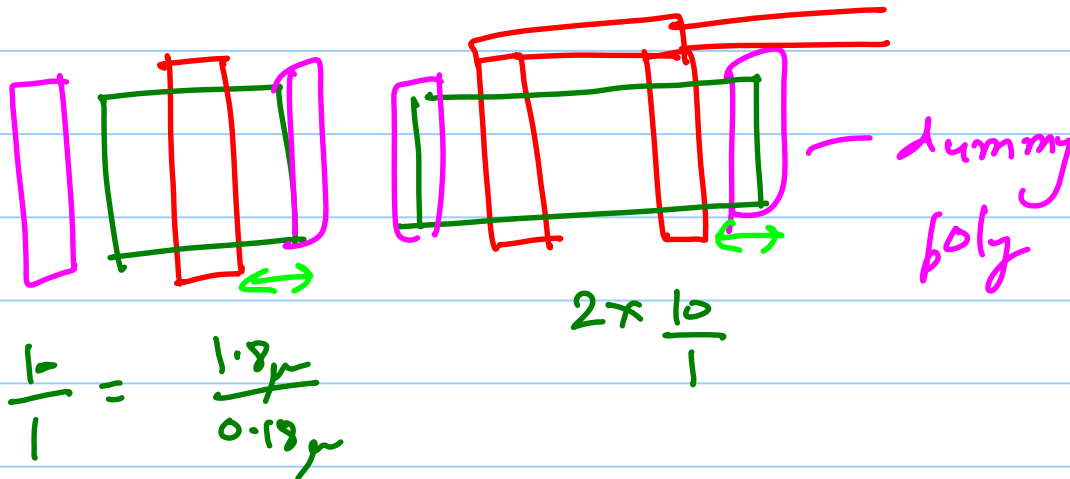
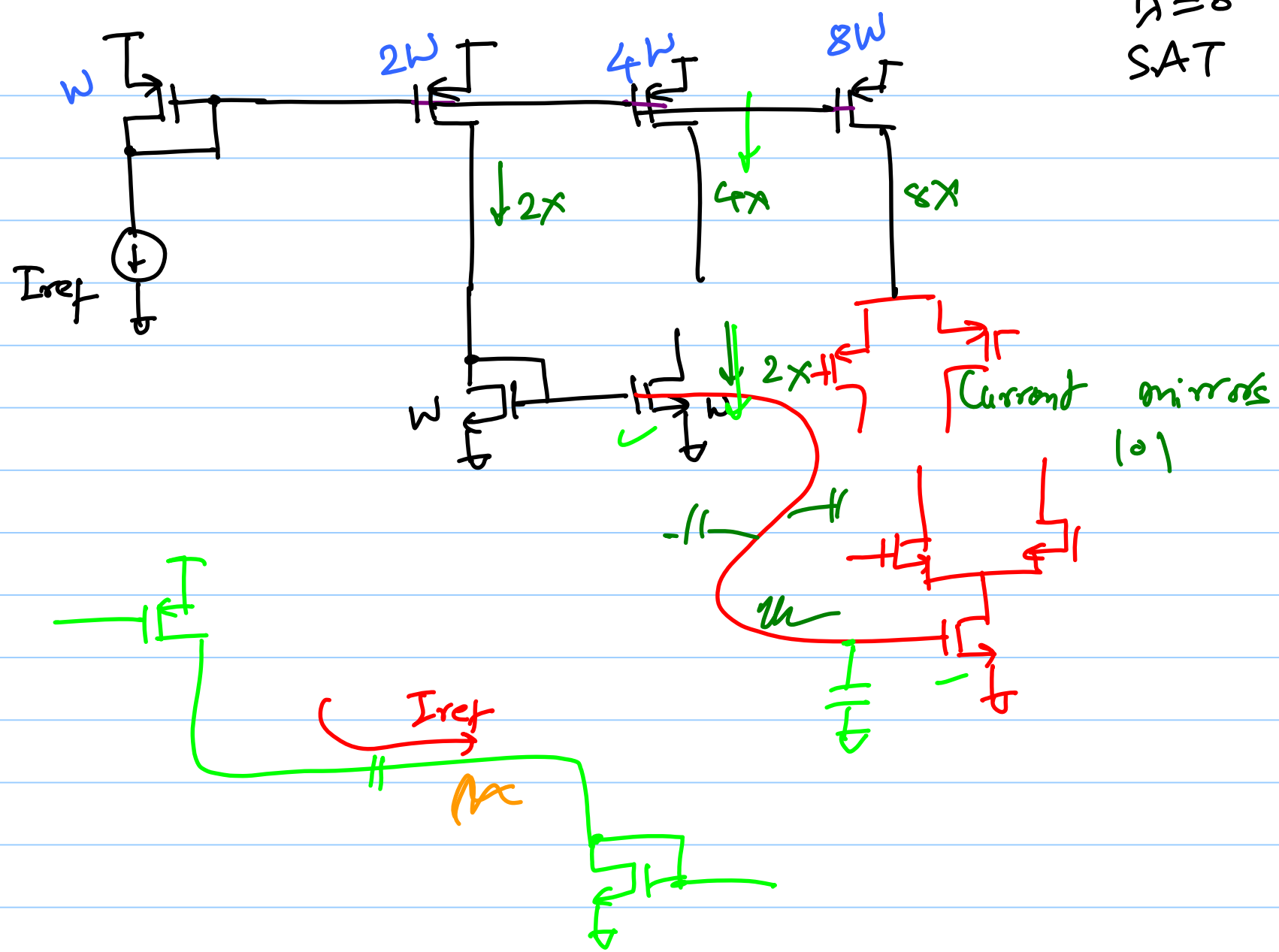



$\lambda = 0$
SAT



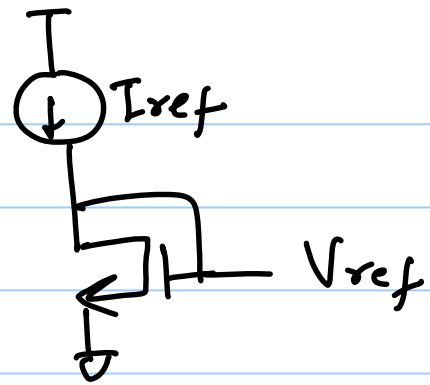


$\lambda \neq 0$

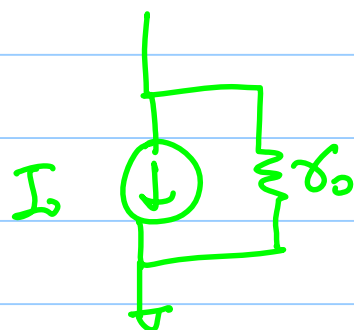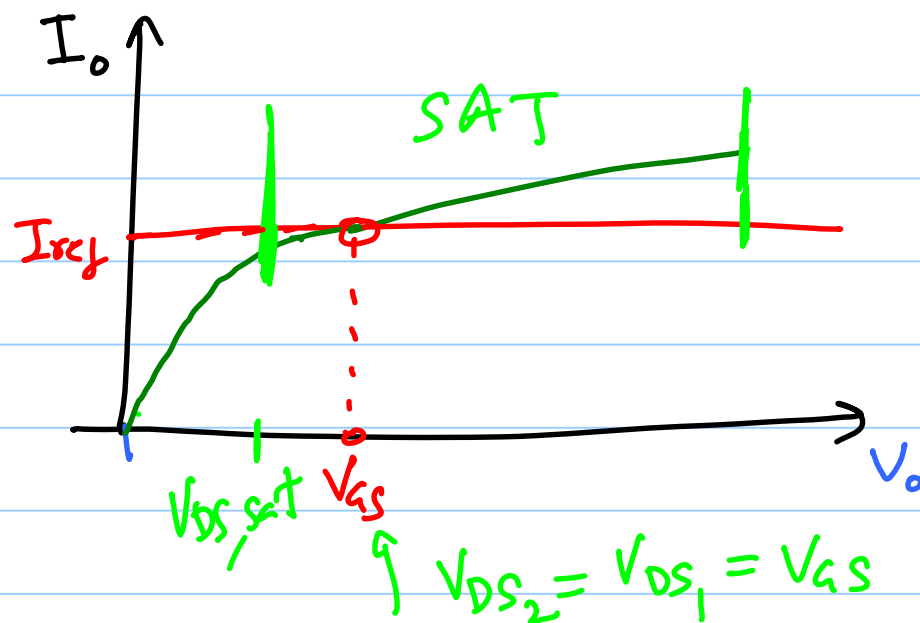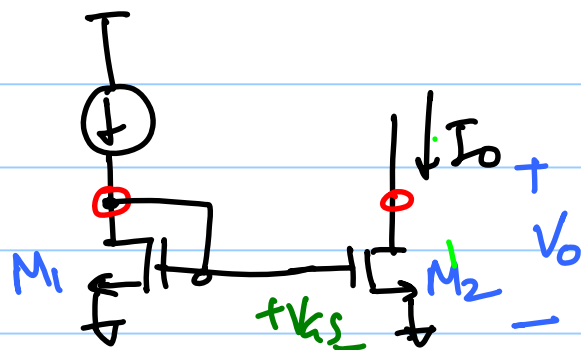

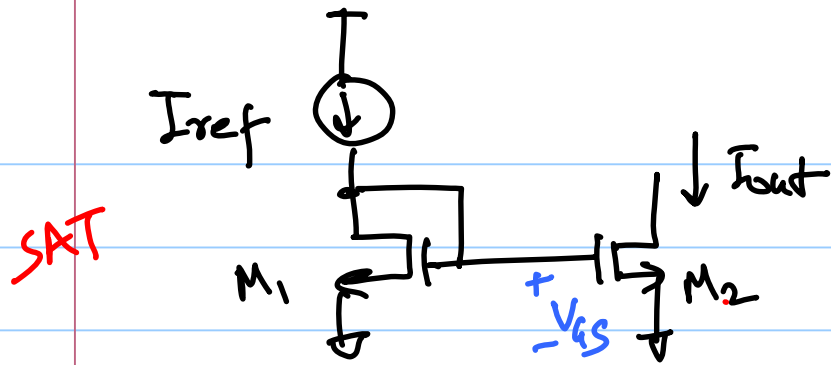

What can go wrong?

$\Delta(W/L)$, ΔV_{THN}

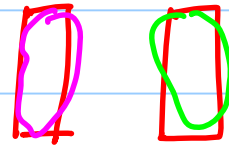

$$I_D = \frac{k_n}{2} \left(\frac{W}{L} \right) (V_{GS} - V_{THN})^2$$

$$\sigma_{V_{THN}} \propto \frac{1}{\sqrt{WL}}$$

$$y = f(x_1, x_2, \dots)$$

Sensitivity analysis

$$\Delta y \approx \frac{\partial f}{\partial x_1} \cdot \Delta x_1 + \frac{\partial f}{\partial x_2} \cdot \Delta x_2 + \dots$$

$$\Delta I_D = \frac{\partial I_D}{\partial (W/L)} \cdot \Delta(W/L) + \frac{\partial I_D}{\partial (V_{GS} - V_{THN})} \cdot \Delta(V_{GS} - V_{THN})$$

$$= \frac{K_{ln}}{2} \cdot (V_{GS} - V_{THN})^2 \cdot A\left(\frac{W}{L}\right) - K_{Pn} \cdot \frac{W}{L} (V_{GS} - V_{THN}) \Delta V_{THN}$$

$$\Rightarrow \boxed{\frac{\Delta I_D}{I_D} = \frac{\Delta(W/L)}{W/L} - \frac{2 \Delta V_{THN}}{(V_{GS} - V_{THN})}} \quad \downarrow$$

$$\sqrt{\frac{\Delta I_D}{I_D}} = \sqrt{\left(\frac{\Delta W/L}{W/L}\right)} + \frac{4 \cdot \sqrt{\Delta V_{THN}}}{V_{OV}^2}$$


To minimize current mismatch

- ① V_{OV} should be large
- ② Large WL

$$y = x_1 - x_2$$

$$\sigma_y^2 = \sigma_{x_1}^2 + \sigma_{x_2}^2$$


* How do we generate I_{ref} ?

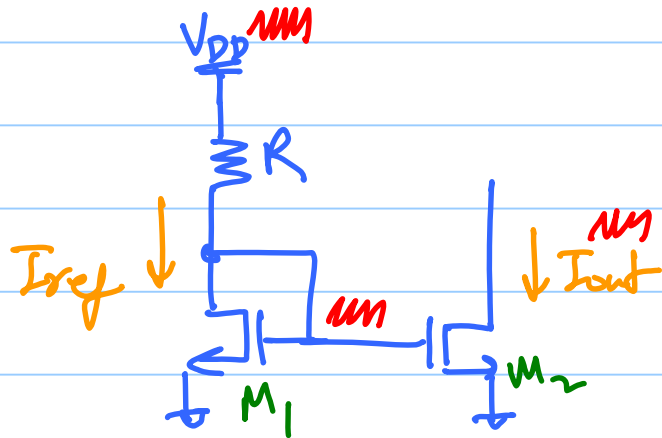

V_{DD} dependent X

$$\Delta I_{out} = \frac{\Delta V_{DD}}{R + \frac{1}{g_{m1}}} \cdot \frac{(w/L)_2}{(w/L)_1}$$

supply noise
sensitivity

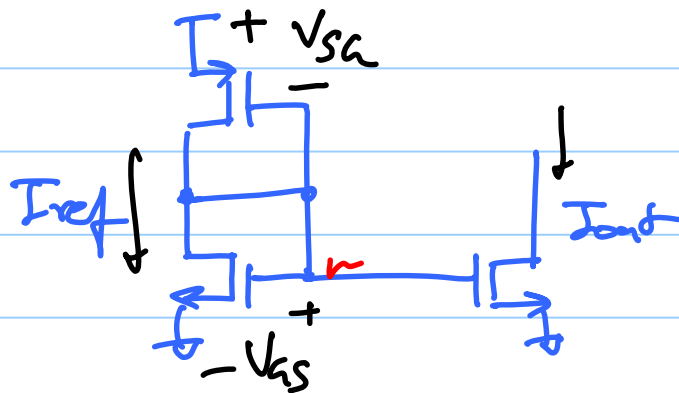

$$V_{DD} = V_{GS} + V_{SG}$$

$$= \sqrt{\frac{2I_{ref}}{\beta_n}} + V_{THN} + \sqrt{\frac{2I_{ref}}{\beta_p}} + V_{THP}$$


Solve for \$I_{ref}\$

$$I_{ref} = \frac{(V_{DD} - V_{THN} - V_{THP})^2}{\left(\sqrt{\frac{2}{\beta_p}} + \sqrt{\frac{2}{\beta_n}}\right)^2}$$

Supply Independent Biasing


⇒ In order to get rid of V_{DD} sensitivity, the circuit must bias itself

⇒ I_{ref} must be derived from I_{out}

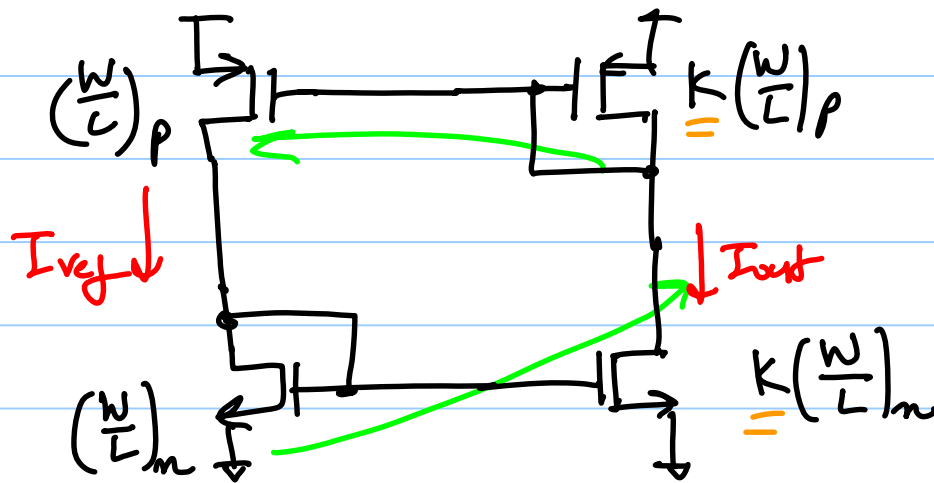

$$I_{out} = k I_{ref}$$

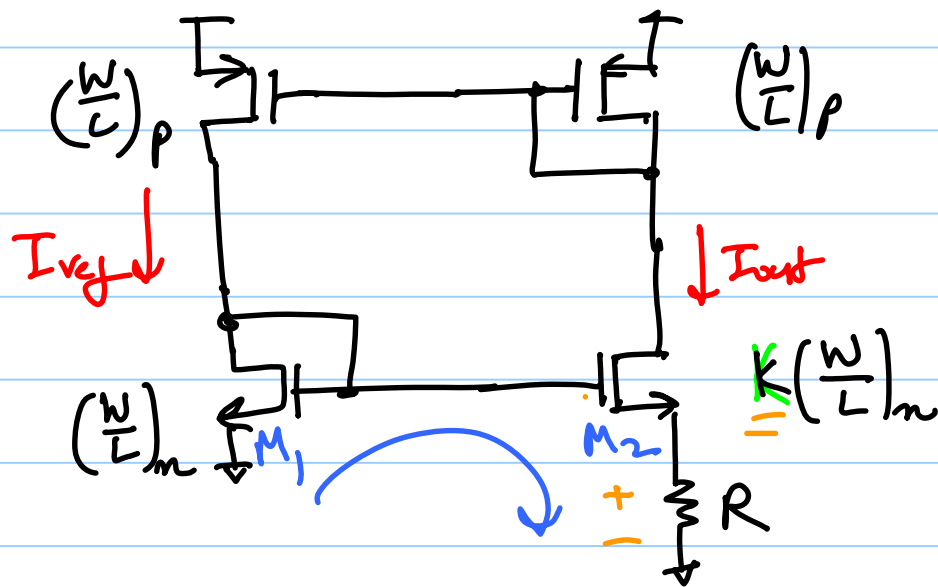How do we set unique values for I_{ref} & I_{out} ?



$$V_{GS1} = V_{GS2} + I_{out} \cdot R$$

$$\sqrt{\frac{2I_{out}}{k\mu_n(W/L)_1}} + \cancel{V_{TH1}} = \sqrt{\frac{2I_{out}}{k\mu_n(W/L)_2}} + \cancel{V_{TH2}} + I_{out} \cdot R$$

$$\left(\frac{W}{L}\right)_2 = K \cdot \left(\frac{W}{L}\right)_1$$

x neglecting body-effect $V_{TH1} = V_{TH2}$

$$I_{out} \stackrel{\Delta}{=} I_{ref} \quad "A=0"$$

$$\sqrt{\frac{2I_{out}}{K_{Pn}\left(\frac{W}{L}\right)}} \left(1 - \frac{1}{\sqrt{k}}\right) = I_{out} \cdot R$$

$$I_{out} = \begin{cases} \frac{2}{K_{Pn}\left(\frac{W}{L}\right) R^2} \left(1 - \frac{1}{\sqrt{k}}\right)^2 \\ 0 \end{cases}$$

indep of V_{DD}