
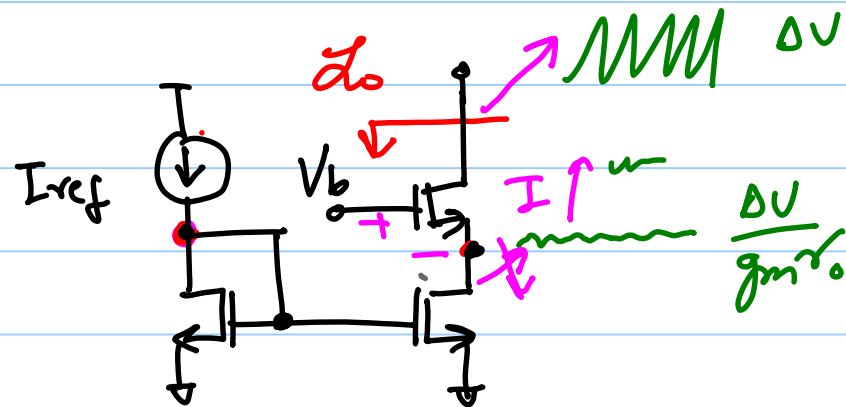
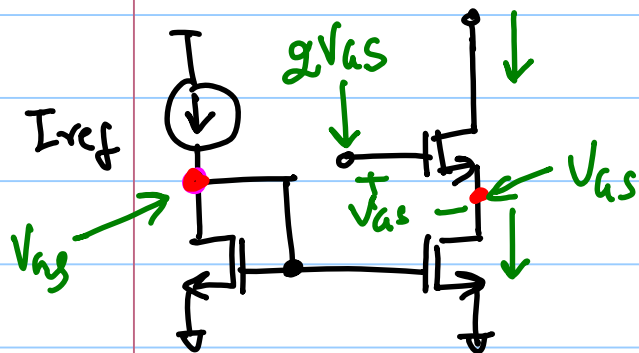
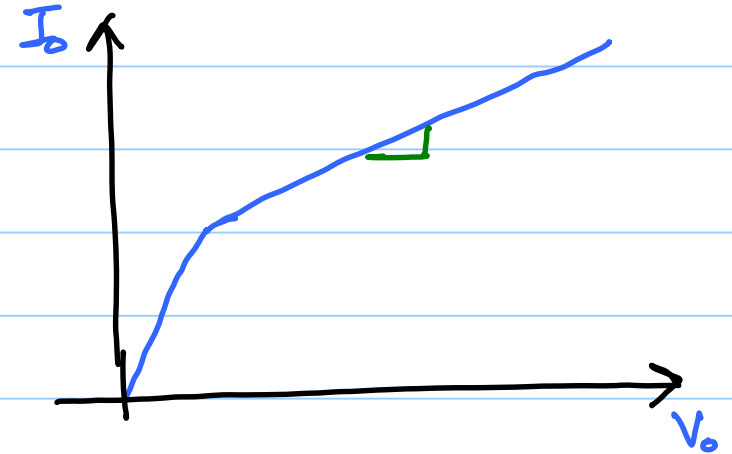


ECE 511 - Lecture 7


Note Title

2/5/2015

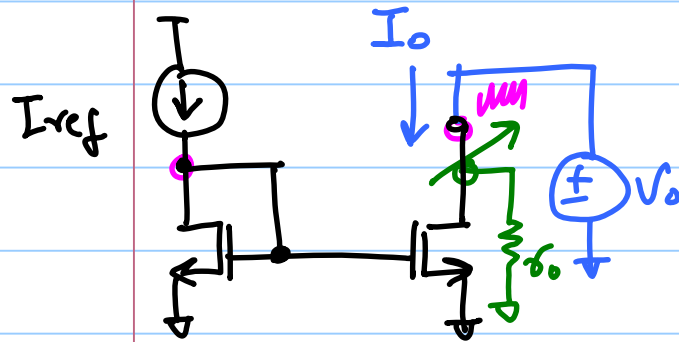


$$V_b = 2V_{gs}$$


$$I_o \triangleq I_{ref}$$

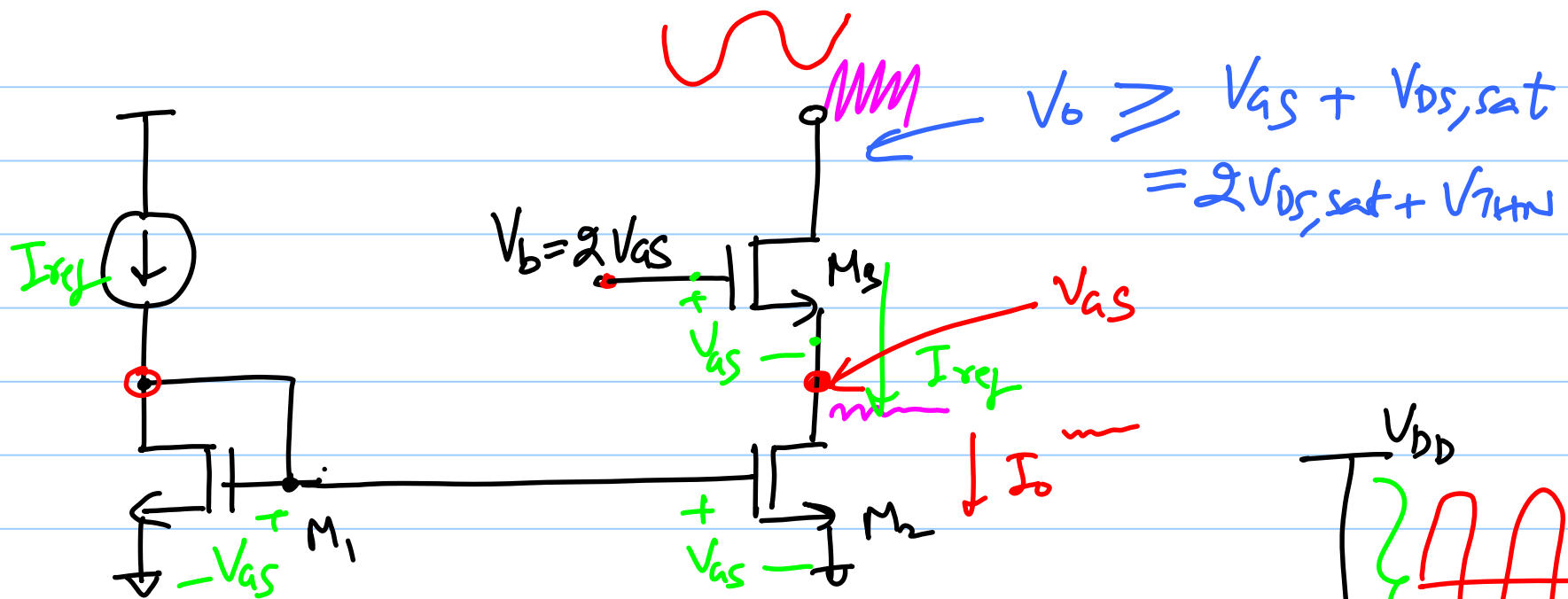


$$V_o \geq V_{as} + V_{DS,sat} = 2V_{DS,sat} + V_{THN}$$

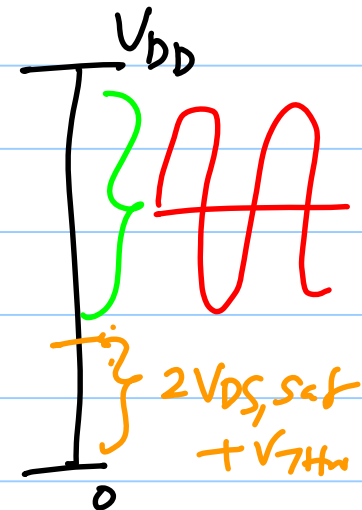headroom reduces by $V_{DS,sat} + V_{THN}$




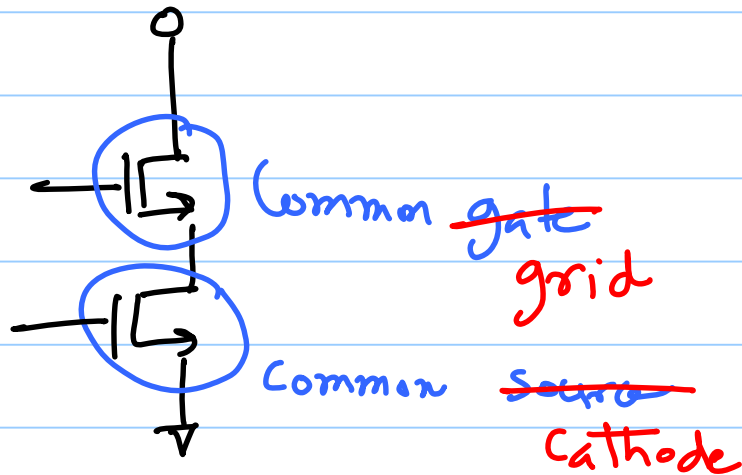


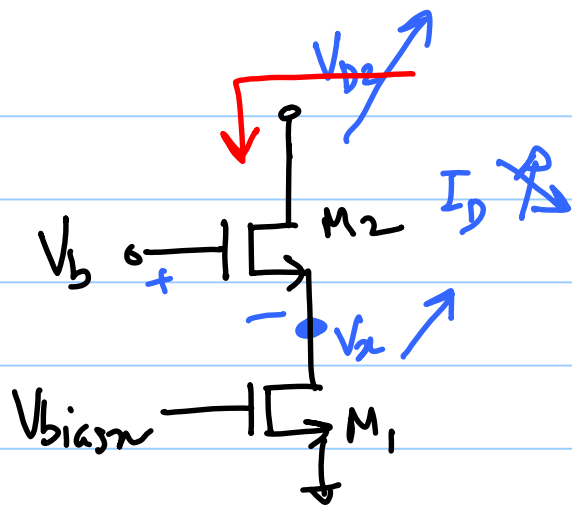
"CASCODE" = Cascade of common cathode & common grid amplifier.




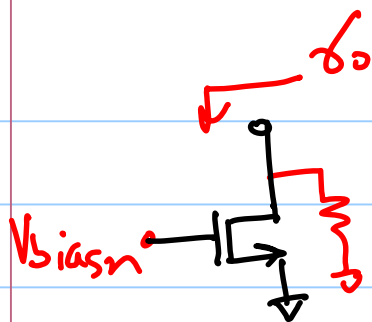
$$\Delta V_x = \frac{\Delta V_{b2}}{1 + g_{m2} r_{o2}}$$



A_v

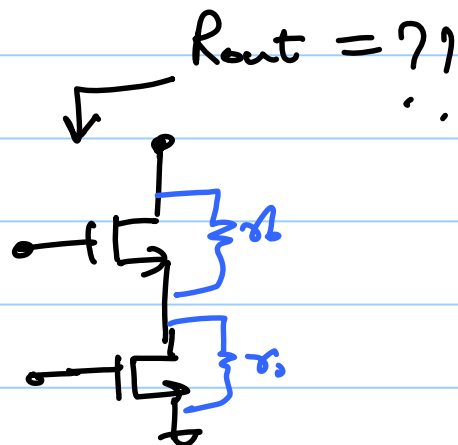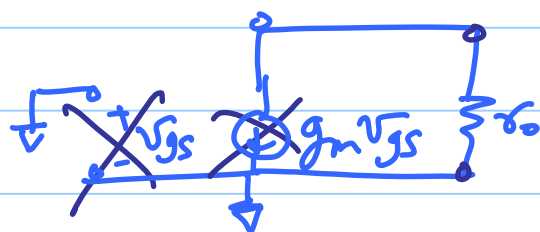

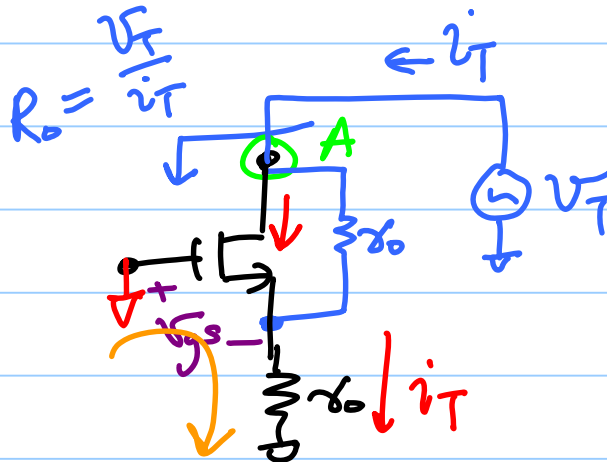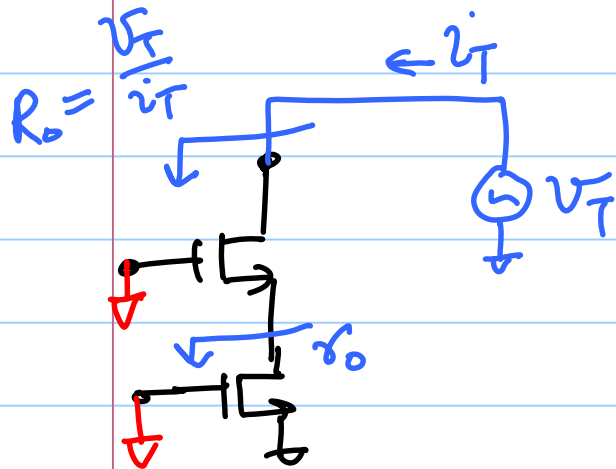

kVL:

$$V_{gs} + i_T r_o = 0 \Rightarrow V_{gs} = -i_T r_o \rightarrow \textcircled{1}$$

kCL @ A

$$i_T - g_m V_{gs} - \frac{(V_T - i_T r_o)}{r_o} \rightarrow \textcircled{2}$$


Eliminating v_{gs} :

$$i_T + g_m r_o i_T - \frac{v_T}{r_o} + i_T = 0$$

$$\frac{v_T}{r_o} = i_T (2 + g_m r_o)$$

$$\Rightarrow R_o = \frac{v_T}{i_T} = (2 + g_m r_o) r_o$$
$$= 2r_o + g_m r_o^2$$

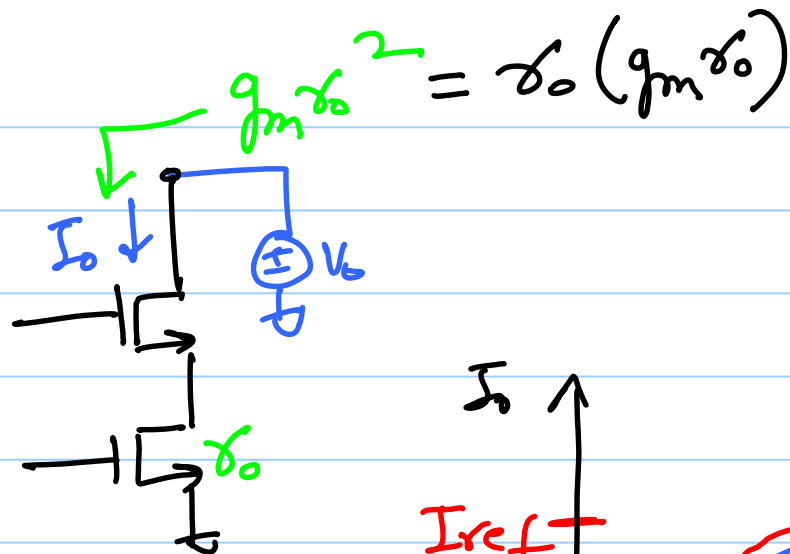
$$\approx \underline{g_m r_o^2} \quad \text{for } g_m r_o \gg 1$$




$$r_o = 1k\Omega$$

$$g_m r_o = 100$$

$$R_o = g_m r_o^2 = 100k\Omega$$

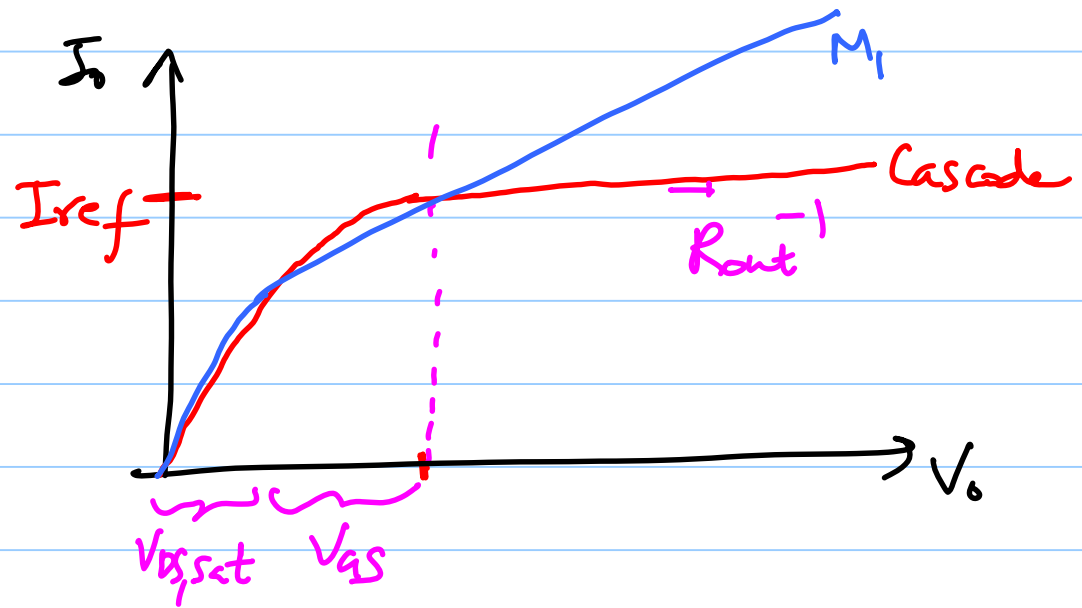

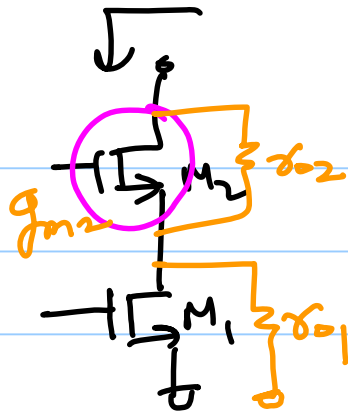


$$R_{out} = (g_{m2} r_{o2}) r_{o1} + r_{o1} + r_{o2}$$


$$V_{DD} = 1.8 \text{ V}$$

$$V_{thn} = 350 \text{ mV}$$


$$V_{DS,sat} = 120 \text{ mV}$$

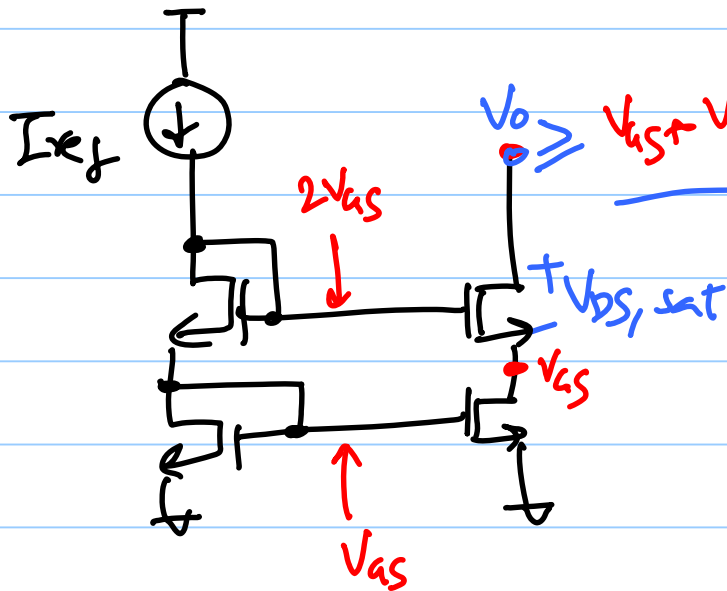

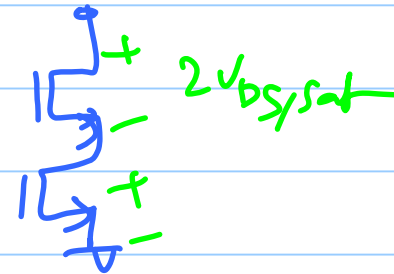
$$V_o \geq V_{gs} + V_{DS,sat} = 2V_{DS,sat} + V_{thn}$$



Wide Swing Current Mirror

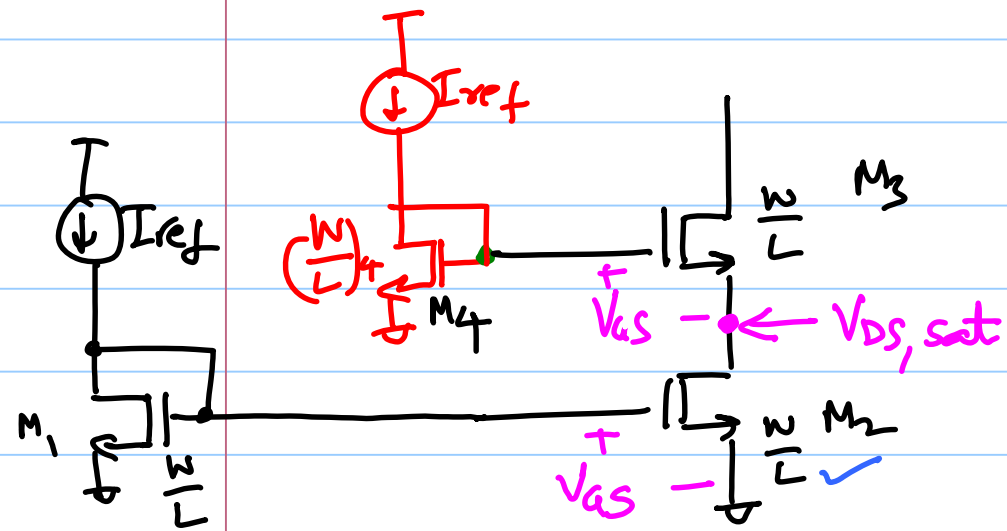
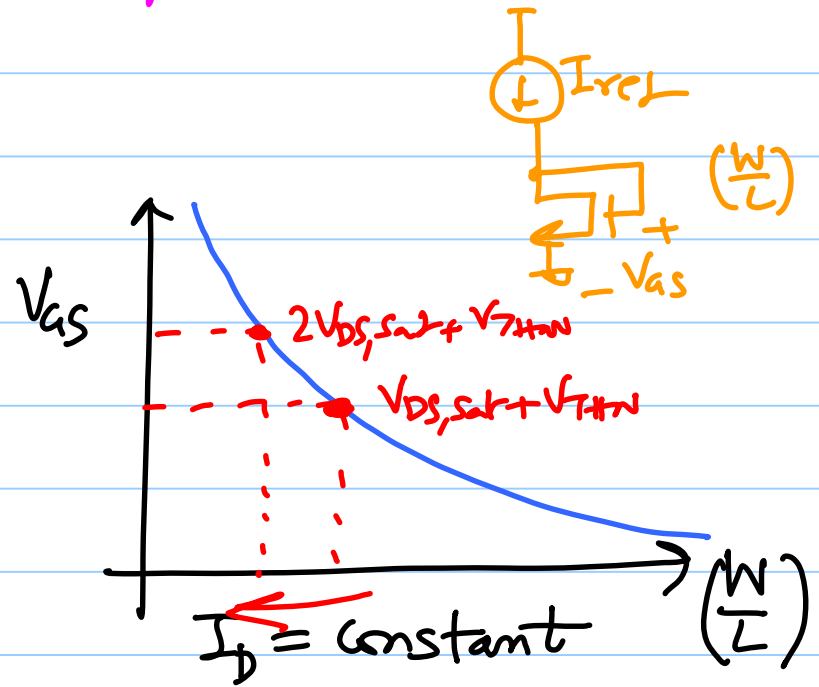
$$V_G = V_{GS} + V_{DS,sat} \\ = \underline{2V_{DS,sat} + V_{THN}}$$



$$V_{GS} = \sqrt{\frac{2I_D}{K_n \frac{W}{L}}} + V_{THN}$$

$$V_{AS4} = 2(V_{DS,cat}) + V_{THN} = \sqrt{\frac{2I_{ref}}{\beta_4}} + V_{THN}$$


$$2\sqrt{\frac{2I_{ref}}{\beta_2}} + \cancel{V_{THN}} = \sqrt{\frac{2I_{ref}}{\beta_4}} + \cancel{V_{THN}}$$

$$\frac{4}{\beta_2} = \frac{1}{\beta_4}$$


$$\beta_4 = \frac{\beta_2}{4}$$

$$\boxed{\left(\frac{W}{L}\right)_4 = \frac{W}{4L}}$$

Wide Swing CM

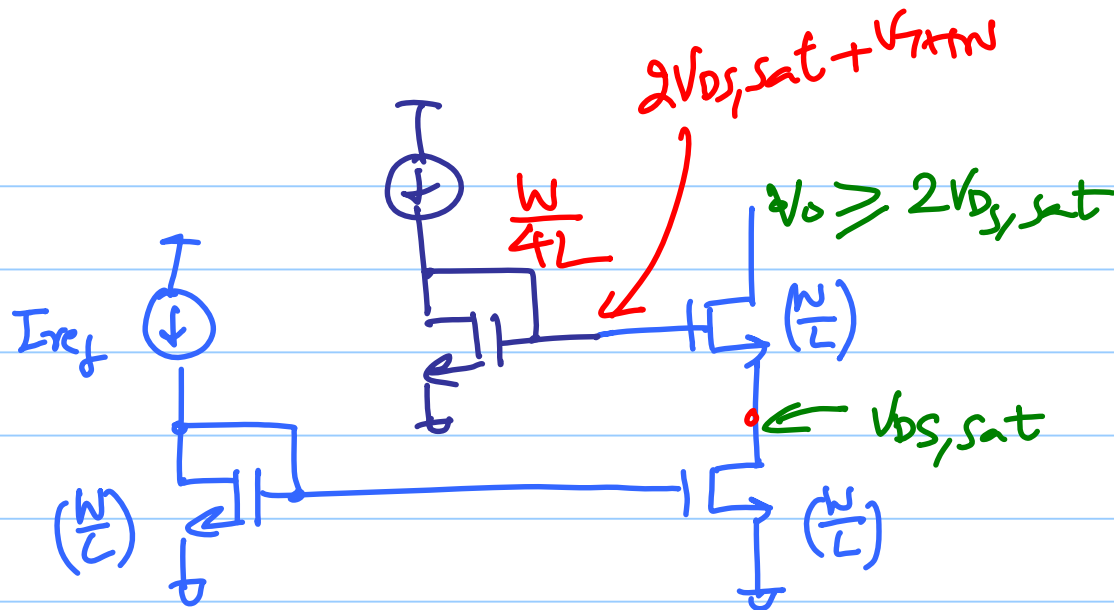

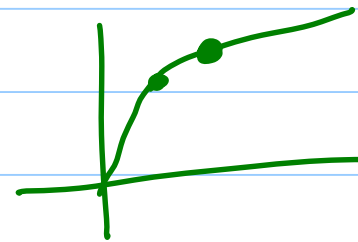In short channel may want to bias in deep saturation



$$\left(\frac{W}{5L}\right)$$

