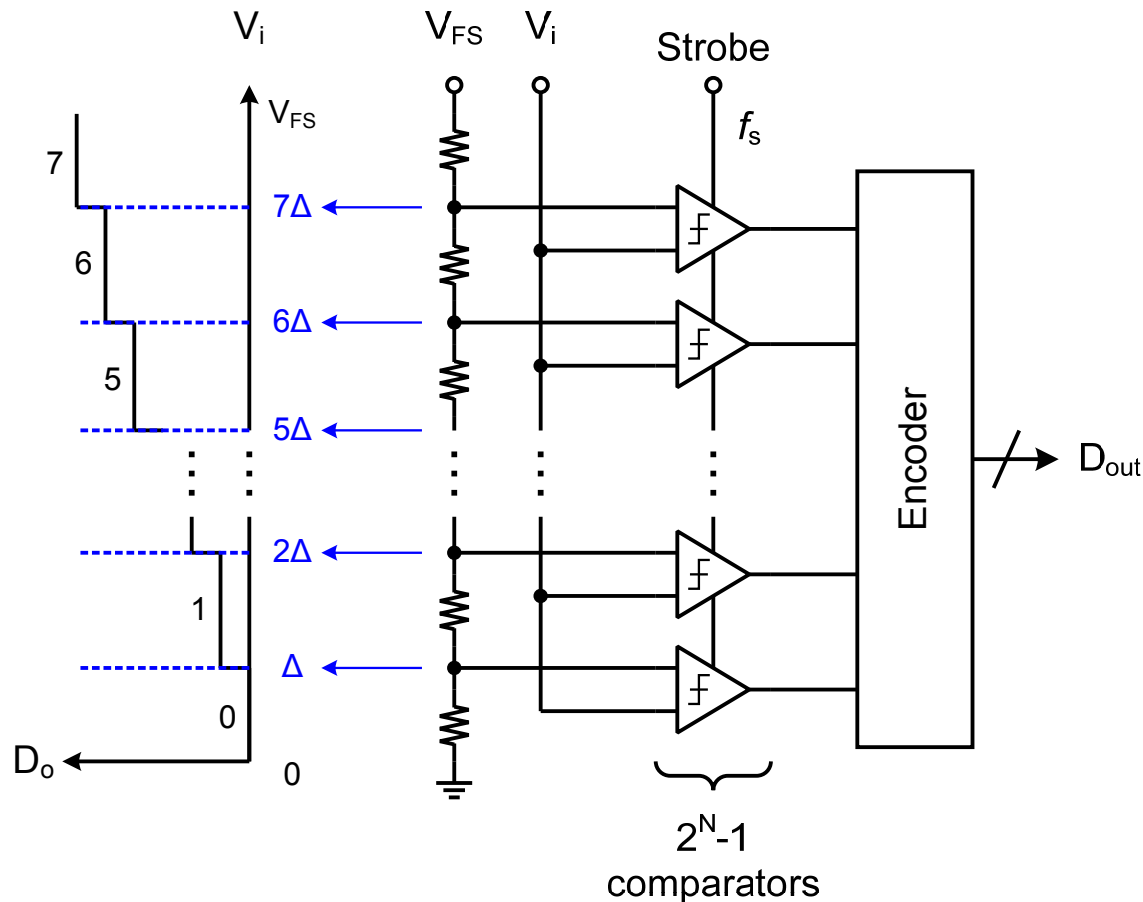


Flash ADCs


Vishal Saxena, Boise State University
(vishalsaxena@boisestate.edu)

Flash ADC Architecture




- Reference ladder consists of 2^N equal size resistors
- Input is compared to $2^N - 1$ reference voltages
- Massive parallelism
- Very fast ADC architecture
- Latency = $1 T_s = 1/f_s$
- Throughput = f_s
- Complexity = 2^N


Thermometer Code

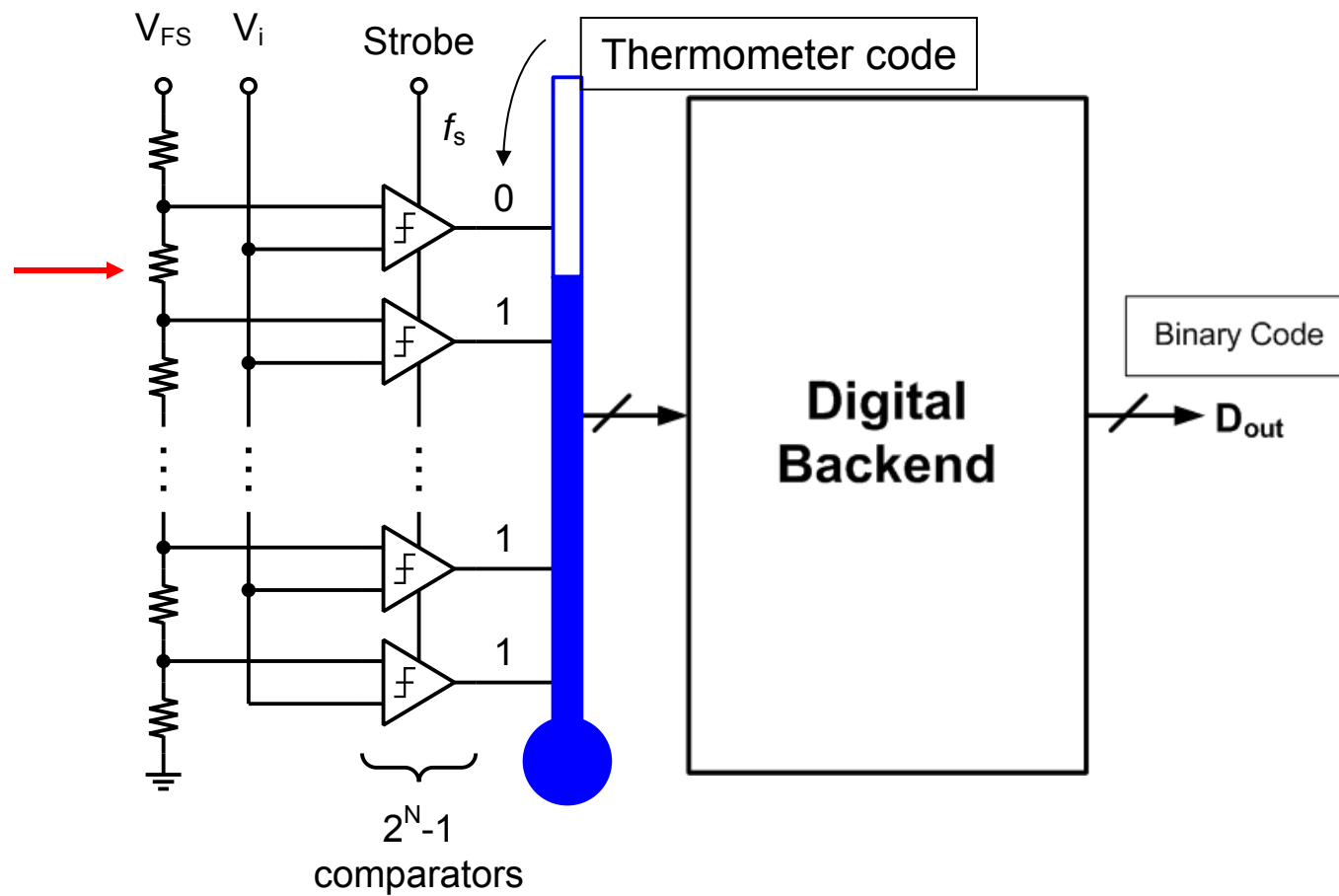

Thermometer Code

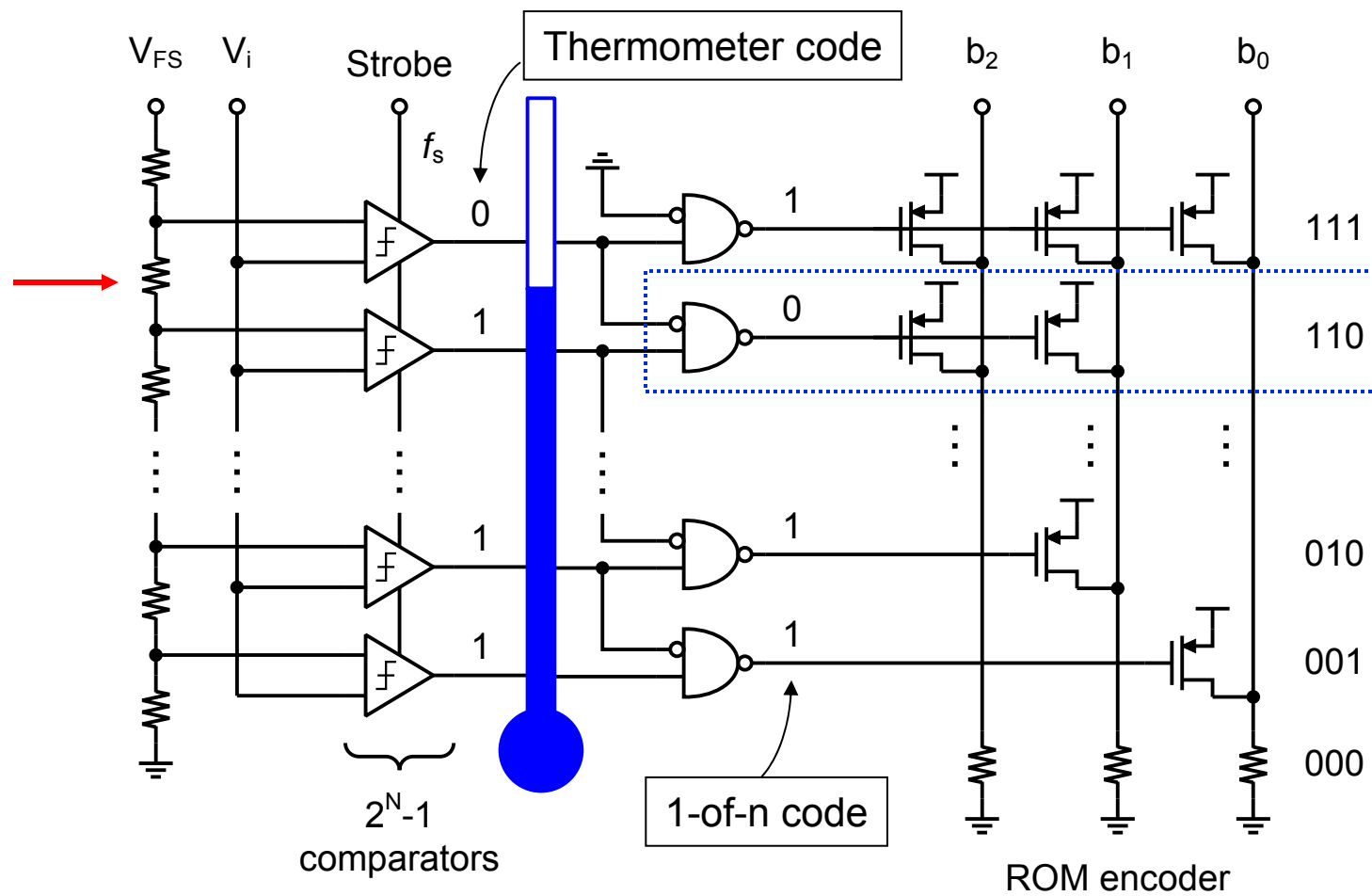


Flash ADC Challenges

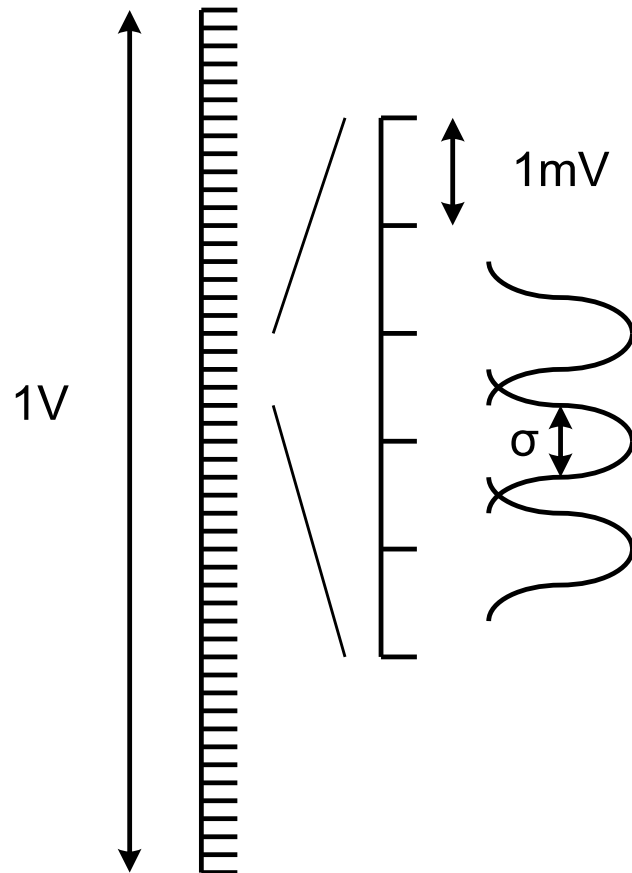

- $V_{DD} = 1.8 \text{ V}$
- 10-bit $\rightarrow 1023$ comparators
- $V_{FS} = 1 \text{ V}$ $\rightarrow 1 \text{ LSB} = 1 \text{ mV}$
- $\text{DNL} < 0.5 \text{ LSB}$ $\rightarrow V_{os} < 0.5 \text{ LSB}$
- $0.5 \text{ mV} = 3\text{-}5 \sigma$ $\rightarrow \sigma = 0.1\text{-}0.2 \text{ mV}$
- $2^N - 1$ very large comparators
- Large area, large power consumption
- Very sensitive design
- Limited to resolutions of 4-8 bits

Flash ADC Challenges

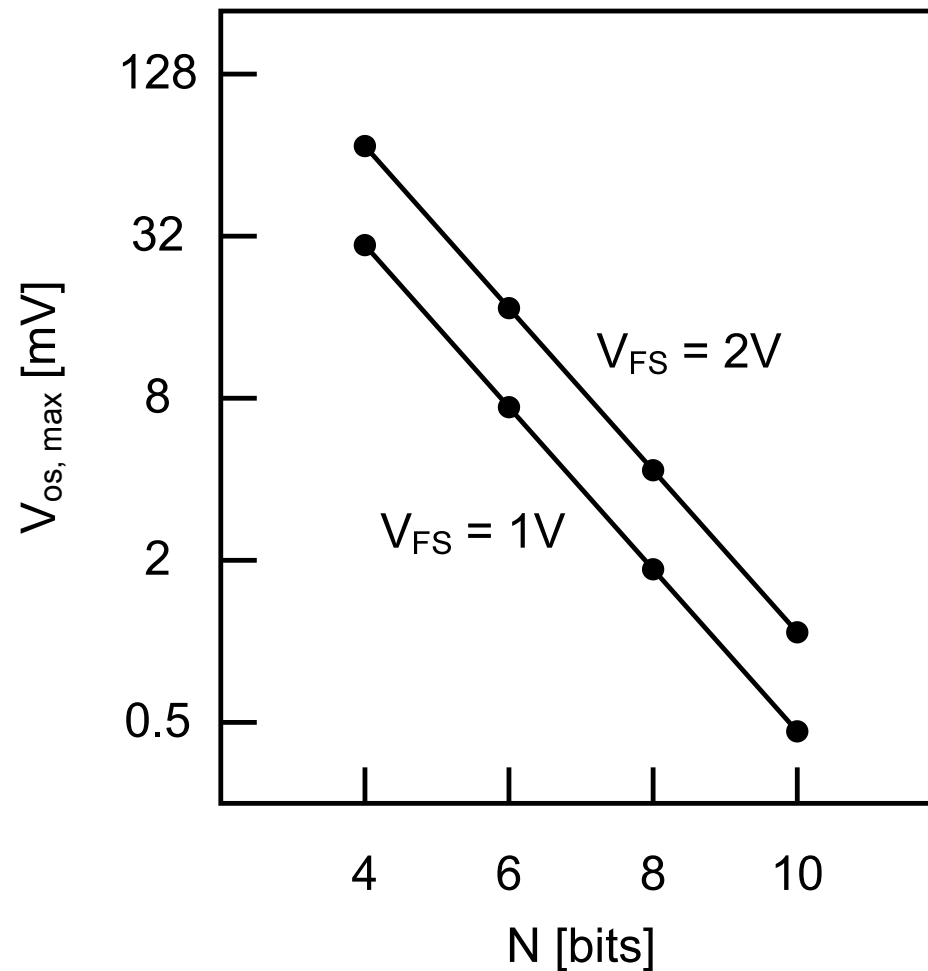

- $DNL < 0.5 \text{ LSB}$
- Large V_{FS} relaxes offset tolerance
- Small V_{FS} benefits conversion speed (settling, linearity of building blocks)

ADC Input Capacitance


$$\sigma^2(V_{th}) = \frac{A_{vth}^2}{WL} \quad C_g = 10 \text{ fF} / \mu\text{m}^2$$

- $N = 6$ bits $\rightarrow$ 63 comparators
- $V_{FS} = 1 \text{ V}$ $\rightarrow$ 1 LSB = 16 mV
- $\sigma = \text{LSB}/4$ $\rightarrow$ $\sigma = 4 \text{ mV}$
- $A_{VT0} = 10 \text{ mV} \cdot \mu\text{m}$ $\rightarrow$ $L = 0.24 \mu\text{m}$,
 $W = 26 \mu\text{m}$

N (bits)	# of comp.	C_{in} (pF)
6	63	3.9
8	255	250
10	1023	??!

- Small V_{os} leads to large device sizes, hence large area and power
- Large comparator leads to large input capacitance, difficult to drive and difficult to maintain tracking bandwidth

Fully-Differential Architecture

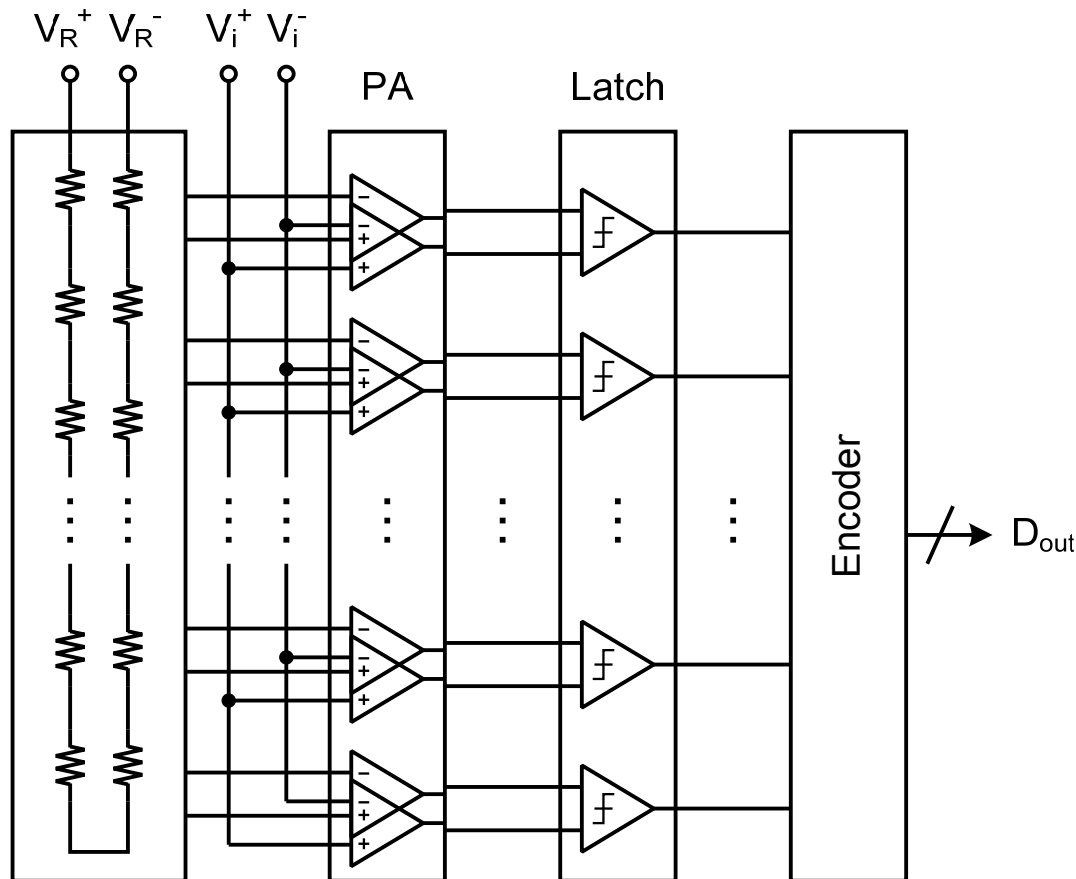


- V_{FS} doubled
- 3-dB gain in SNR
- Better CMRR
- Noise immunity
- Input feedthrough cancelled
- C_{in} nonlinearity partially removed
- Effect of V_{cmi} diff. mitigated

Flash ADC Design Considerations

- Use a dedicated S/H (or T/H) for better dynamic performance
 - Can be avoided when using the A/D inside a $\Delta\Sigma$ loop
- Large input range for the quantizer has several benefits
 - Increased step-size (V_{LSB}) relaxes offset requirements on the comparators
 - Reduced matching requirements result in small input cap to the S/H, easier to drive
 - Reduced input cap results in smaller clock routing parasitics – power savings in clock drivers
- Comparator Design
 - See comparator design slides


Flash ADC: Reference Ladder

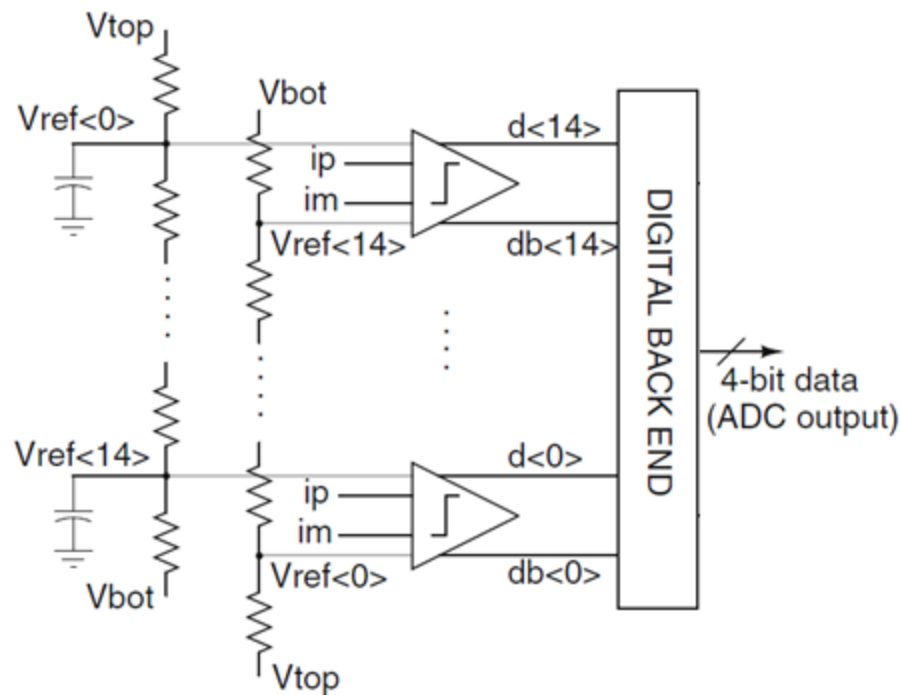


- Differential reference ladder
- Decaps on the reference taps
 - large RC time-constant will not allow reference restoration after kickback noise
 - Small R will lead to power dissipation
 - Optimize RC
- Subtract references from the input in a differential manner
 - Several topologies
- Several architectures for the digital backend
 - May need to pipeline digital logic at high sampling rates >500 MS/s

Reference Generator (for V_{refp} and V_{refm})


[Brooks 1994]

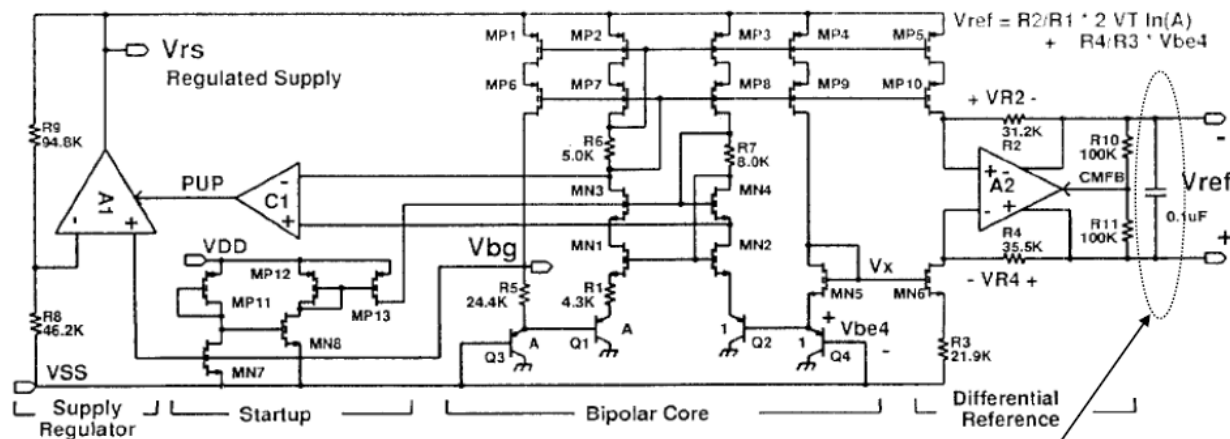

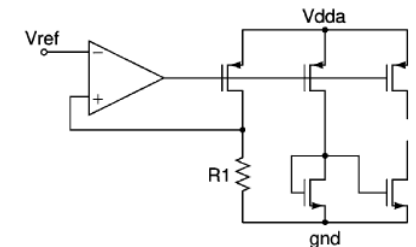External decoupling caps provide dynamic currents
 $\Rightarrow$ Low power reference buffer



(a)

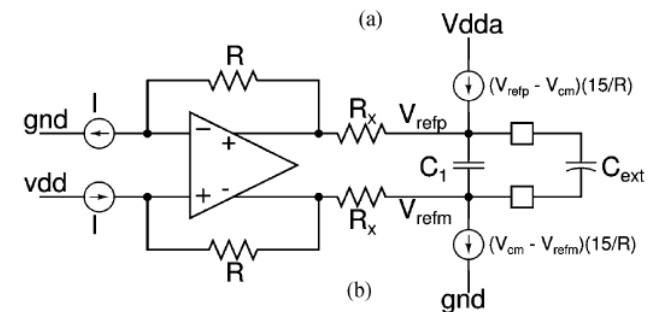


(b)



Flash ADC: Reference Subtraction

Reference Subtraction: Scheme I

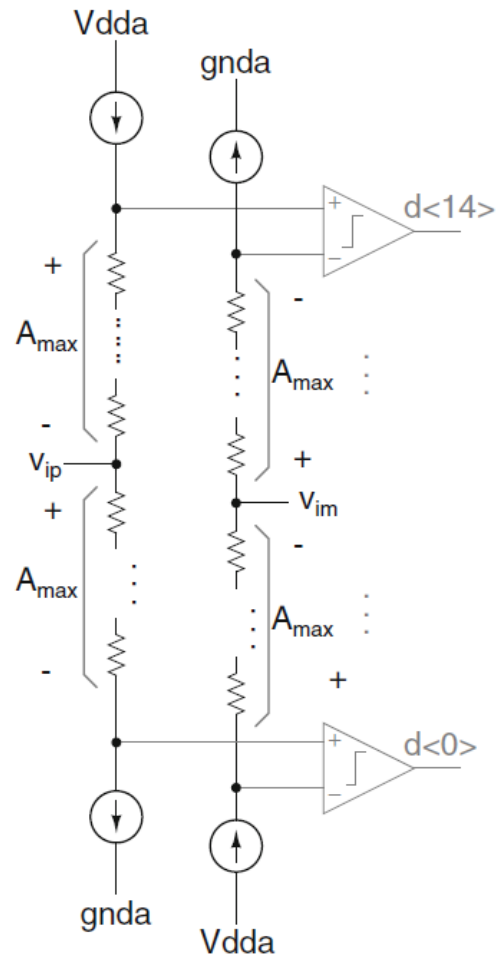


- Employ reference ladder for subtraction
- Choose current (I) such that differential voltage drop across $R = 1 V_{\text{LSB}}$
- Ladder is part of the signal path
 - Comparator input cap load the resistor taps
 - Excess delay

$$A_{\max} = \frac{0.5V_{dd} - \Delta V}{2}$$

Paton, S., Di Giandomenico, A., Hernandez, L., Wiesbauer, A., Potscher, T., & Clara, M. (2004). A 70-mW 300-MHz CMOS continuous-time $\Sigma\Delta$ ADC with 15-MHz bandwidth and 11 bits of resolution. *IEEE Journal of Solid State Circuits*, 39(7), 1056–1063.


Reference Subtraction: Scheme II

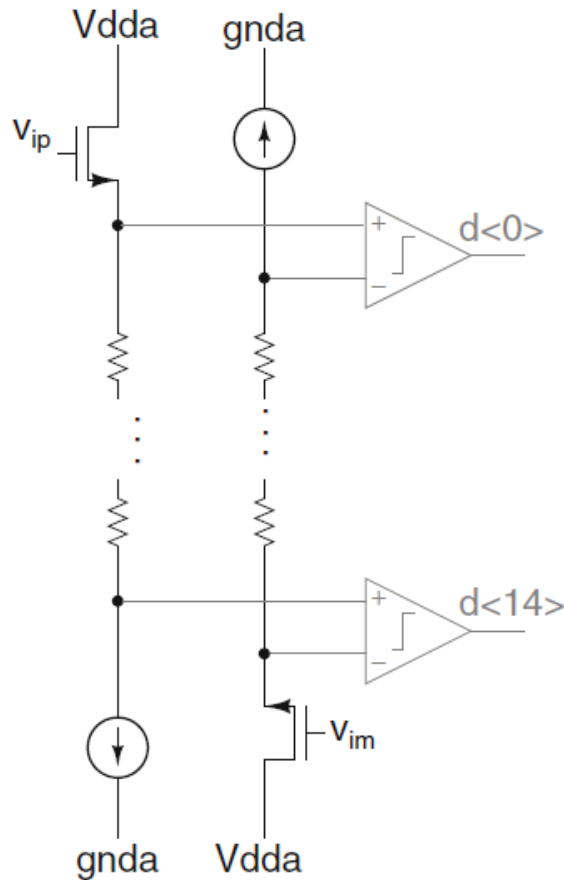

- Source followers to buffer v_{in}
 - reduced swing, varies with PVT
- Ladder is part of the signal path
 - Comparator input cap load the resistor taps
 - Excess delay

Arias, J., Kiss, P., Prodanov, V., Boccuzzi, V., Banu, M., Bisbal, D., et al. (2006). A 32-mW 320-MHz continuous-time complex $\Sigma\Delta$ ADC for multi-mode wireless-LAN receivers. *IEEE Journal of Solid State Circuits*, 41(2), 339–351.


Reference Subtraction: Scheme III

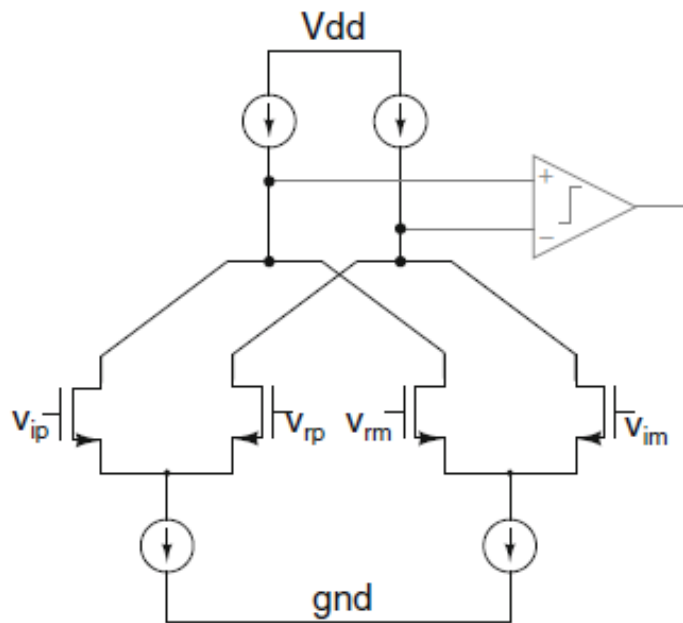

- Differential difference amplifier for subtracting the reference
 - followed by a zero crossing detector
- Relaxes the impedance requirements on the ladder
- Mismatch in differential pairs and tail current sources results in comparator offset
 - current trimming (see the reference below)
- Finite BW of the amplifier causes excess delay


Mitteregger, G., Ebner, C., Mechnig, S., Blon, T., Holuigue, C., & Romani, E. (2006). A 20-mW 640-MHz CMOS continuous-time $\Sigma\Delta$ ADC with 20-MHz signal bandwidth, 80-dB dynamic range and 12-bit ENOB. *IEEE Journal of Solid State Circuits*, 41(12), 2641–2649.

Reference Subtraction: Scheme IV

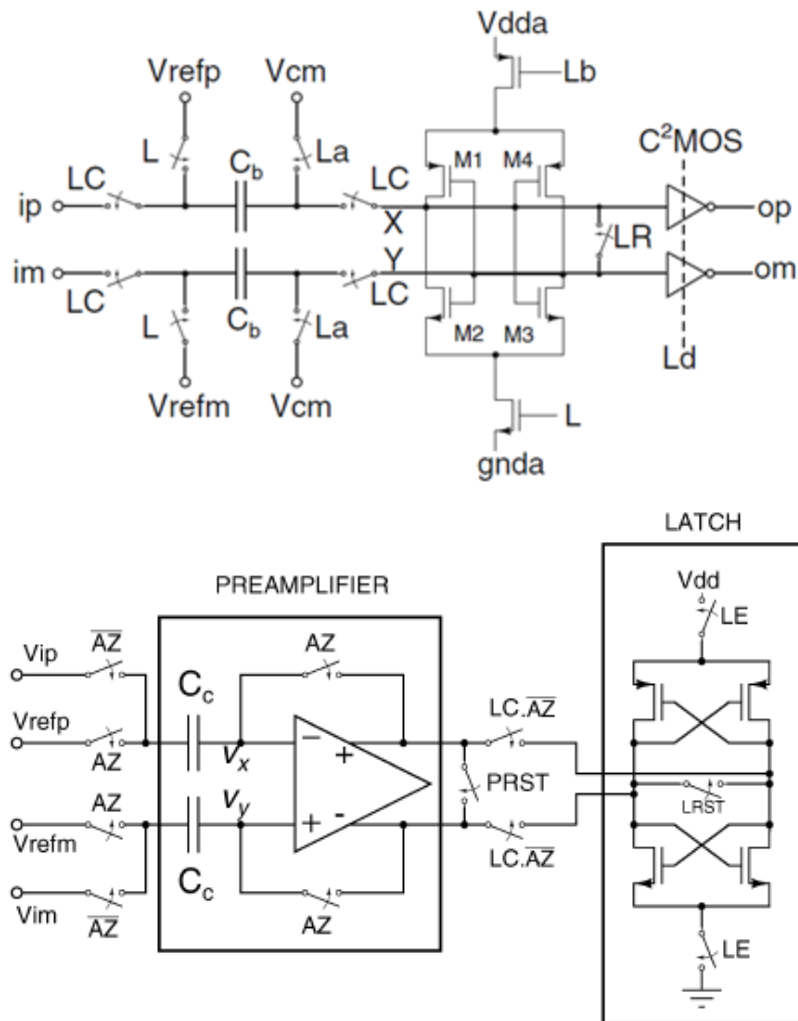

- Switched-capacitor reference subtraction
 - Pay attention to charge injection
- ADC can handle large input swing
- Slow when auto-zeroing preamp is used
 - Large settling time constant
 - Reference subtraction in background

Example: Fully-Differential Comparator

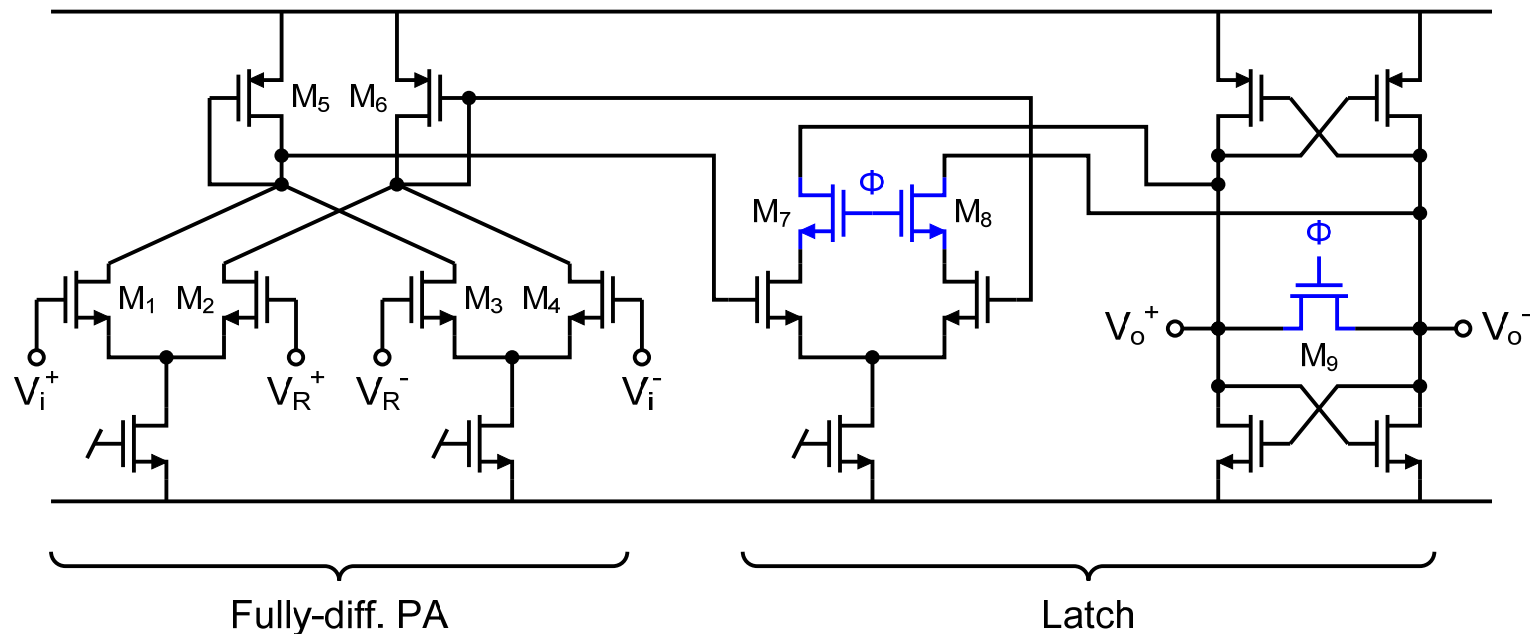


- Double-balanced, fully-differential preamp
- Switches (M₇, M₈) added to stop input propagation during regeneration
- Active pull-up PMOS added to the latch



Flash ADC: Errors


Flash ADC Errors

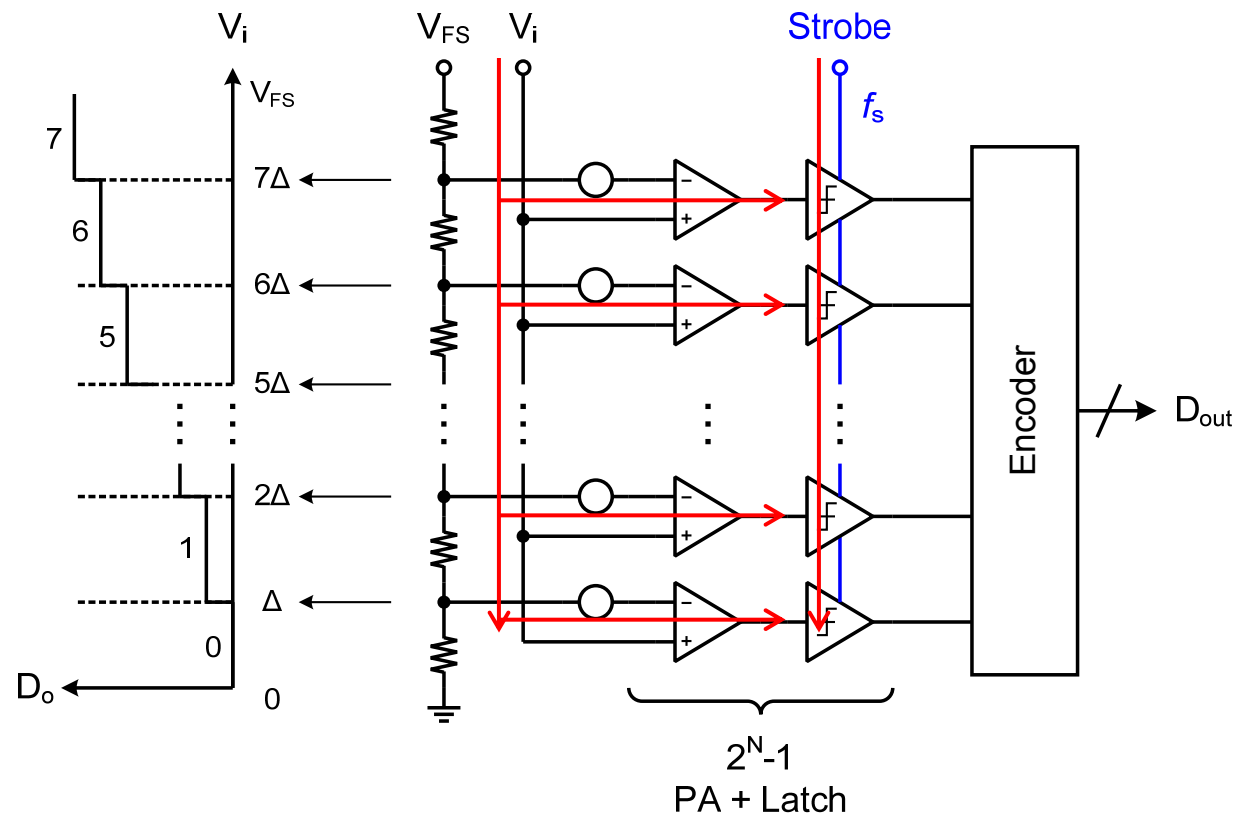

- SHA-less
- Signal and clock propagation delay
- $2^N - 1$ PAs + latches must be matched
- Synchronized strobe signal is critical


Going parallel is fast, but also gives rise to inherent problems...

Preamp Input Common Mode

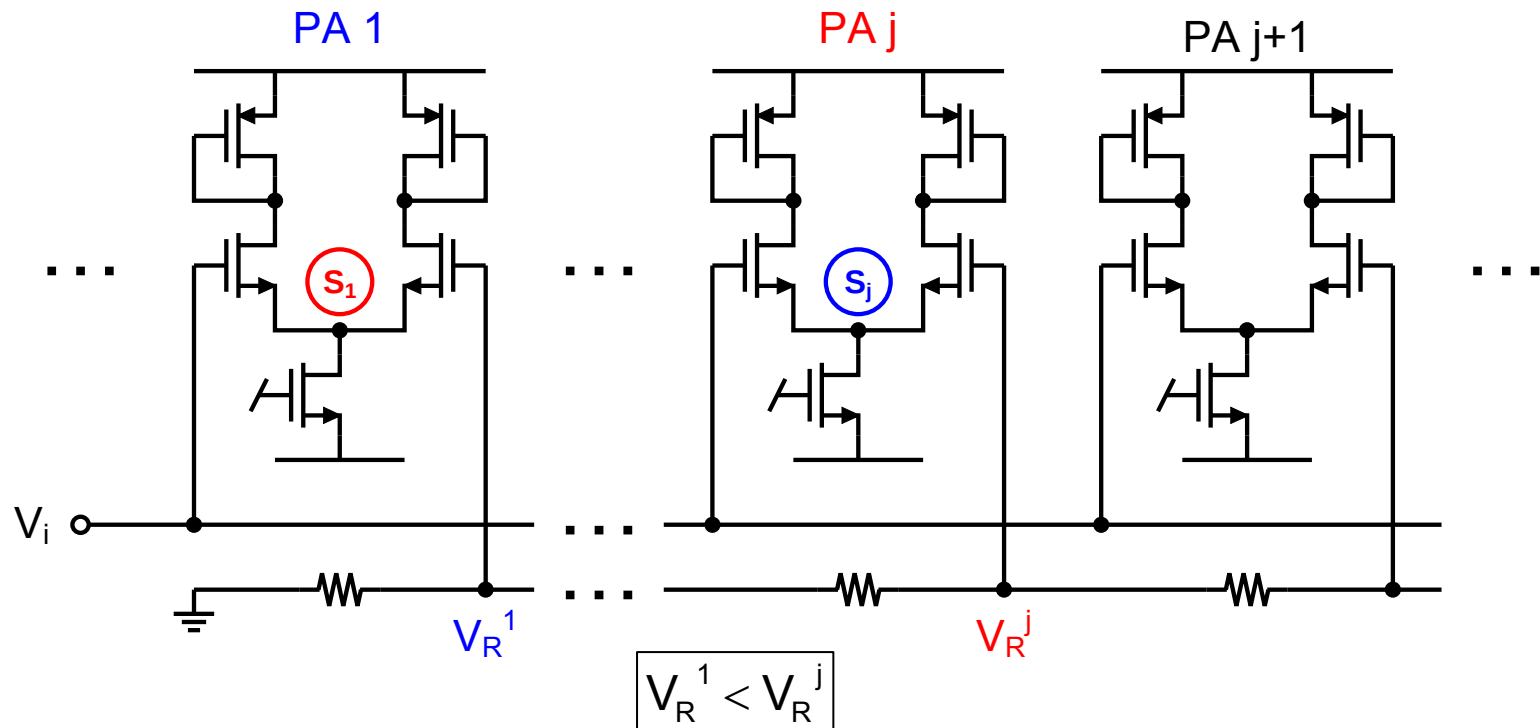

Input CM difference creates systematic mismatch (offset, gain, C_{in} , tracking BW, and CMRR) among preamps



Sampling Aperture Error

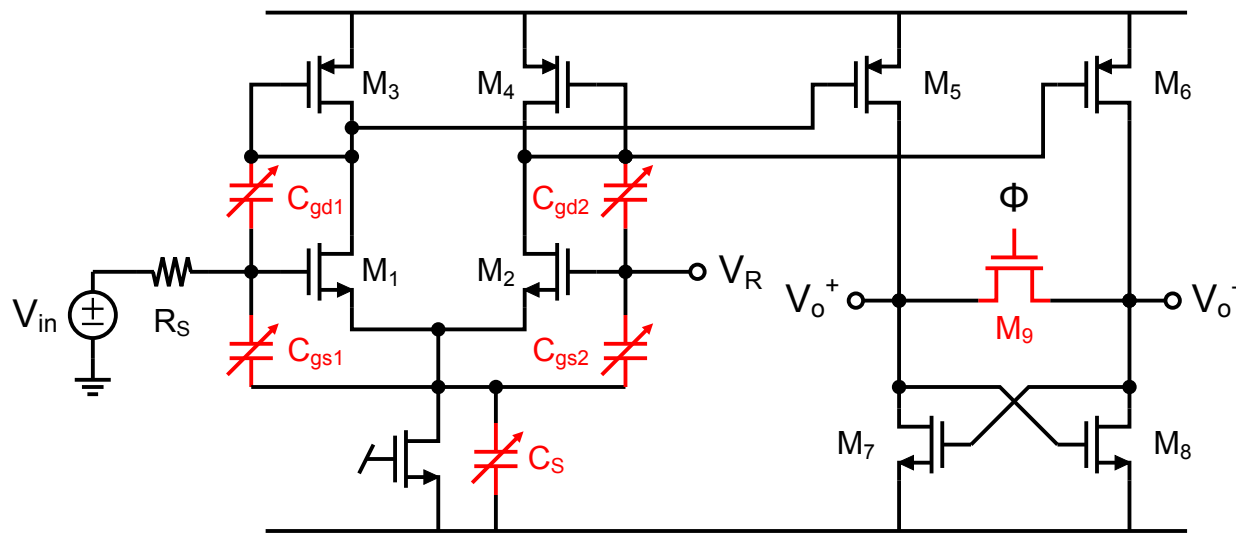

Φ	Mode
"high"	Track
"low"	Regen


- Preamp delay and V_{th} of sampling switch (M_9) are both signal-dependent $\rightarrow$ signal-dependent sampling point (aperture error)
- A major challenge of distributing clock signals across 2^N-1 comparators in flash ADC with minimum clock skew (routing, V_{th} mismatch of M_9 , etc.)

Nonlinear Input Capacitance

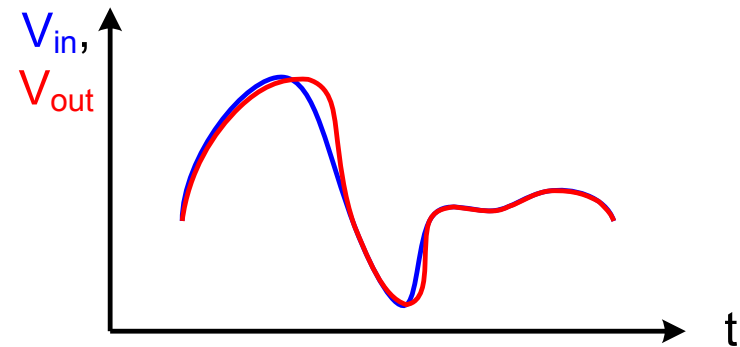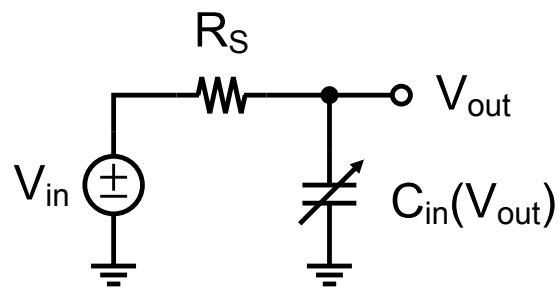


Signal-dependent input bandwidth ($1/R_S C_{in}$) introduces distortion

Input Signal Feedthrough

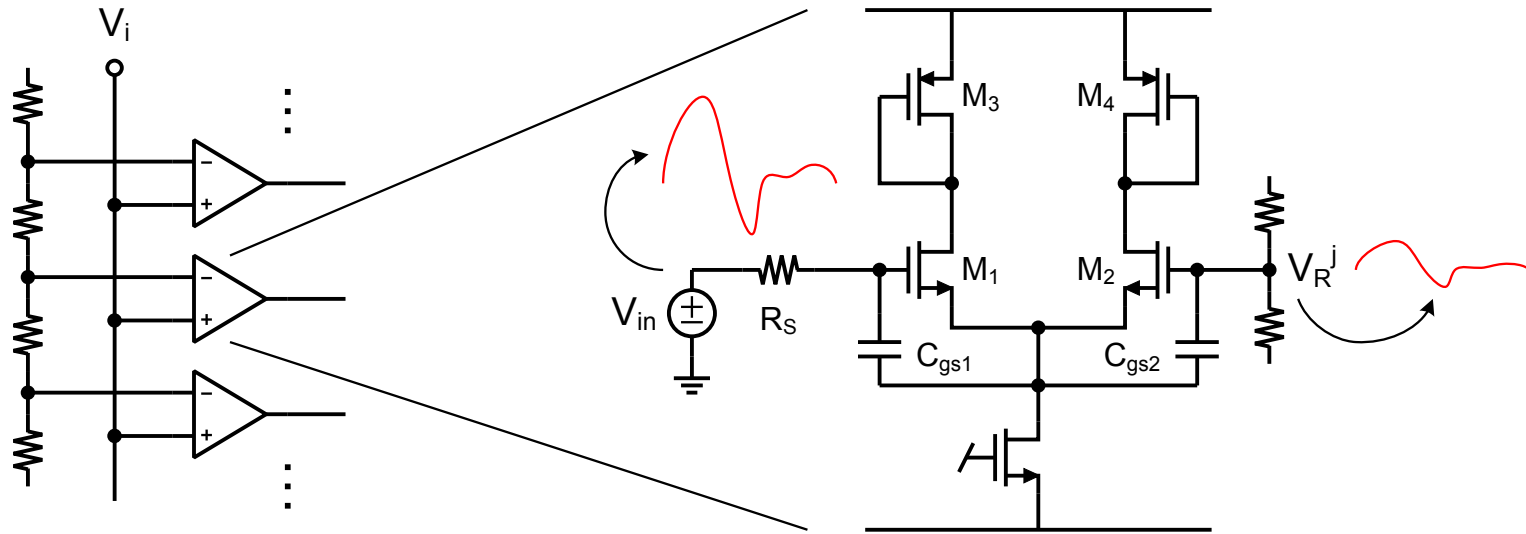

Feedthrough of V_{in} to the reference ladder through the serial connection of C_{gs1} and C_{gs2} disturbs the reference voltages

Comparator Metastability

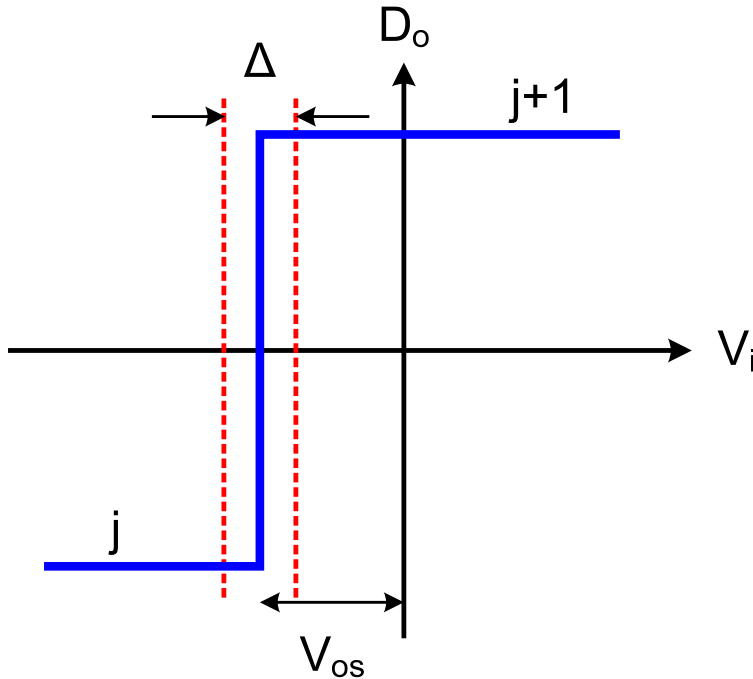


Assuming that the input is uniformly distributed over V_{FS} , then

$$BER = \frac{\Delta}{1\text{LSB}}$$

$$V_o(t) = V_i(0) \cdot A_{v1} A_{v2} \cdot \exp(t \cdot g_m / C_L)$$


- Cascade preamp stages (typical flash comparator has 2-3 PA stages)
- Use pipelined multi-stage latches; PA can be pipelined too
- **Avoid branching off comparator logic outputs**

Comparator Metastability

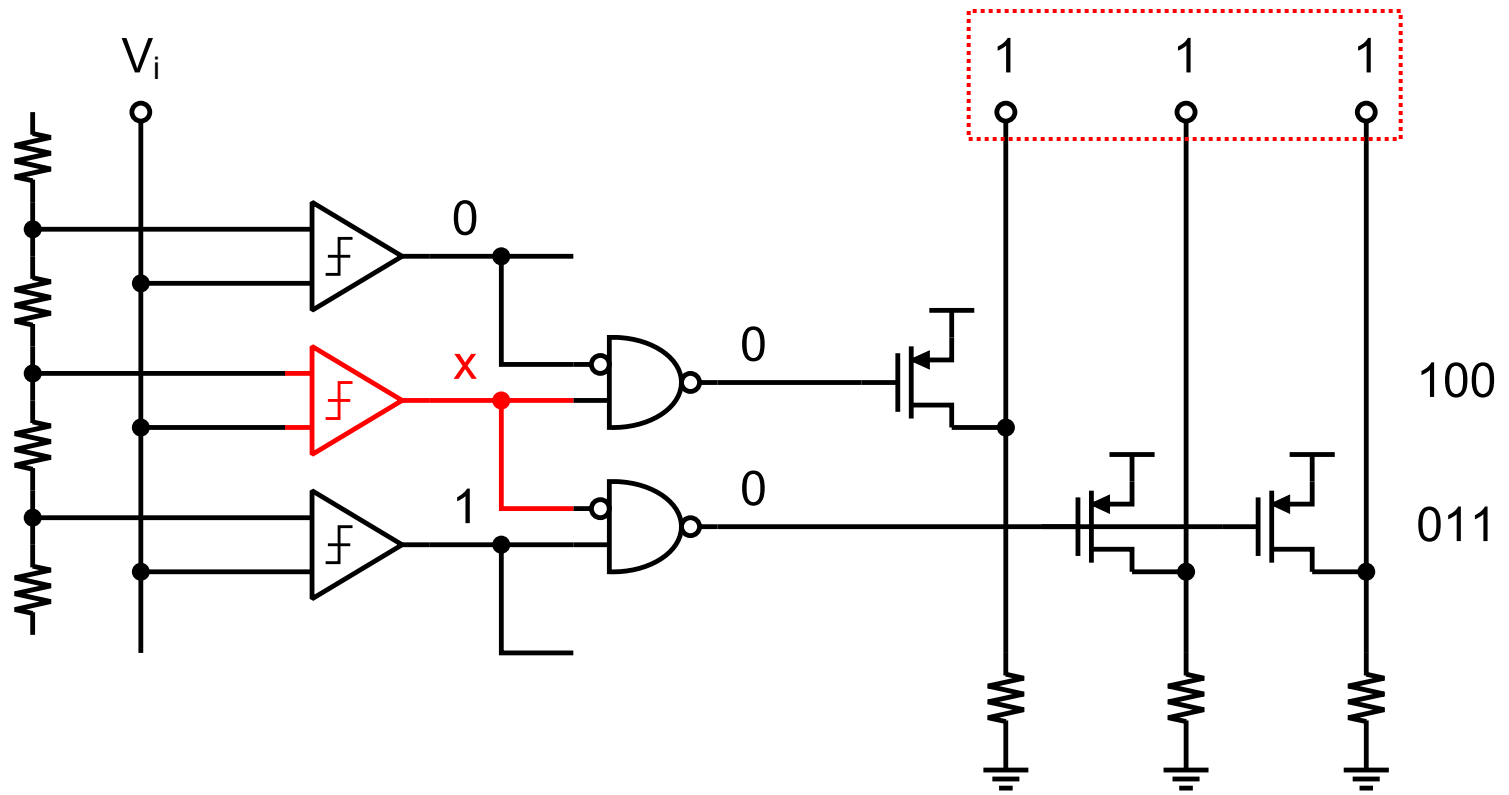


Logic levels can be misinterpreted by digital gates (branching off, diff. outputs)

Bubbles (Sparkles) in Thermometer Code

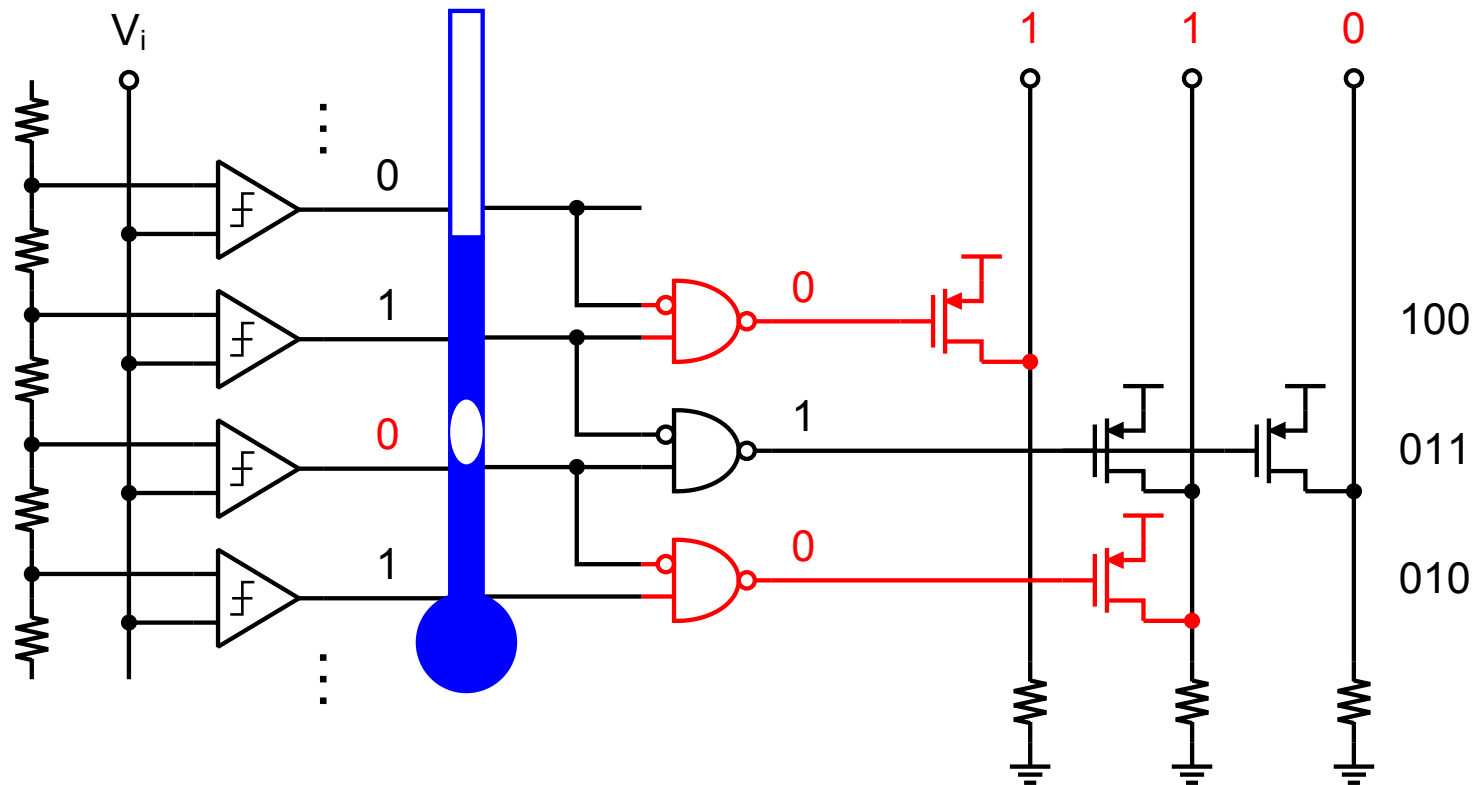


Static/dynamic comparator errors cause bubbles in thermometer code

Bubbles (Sparkles)

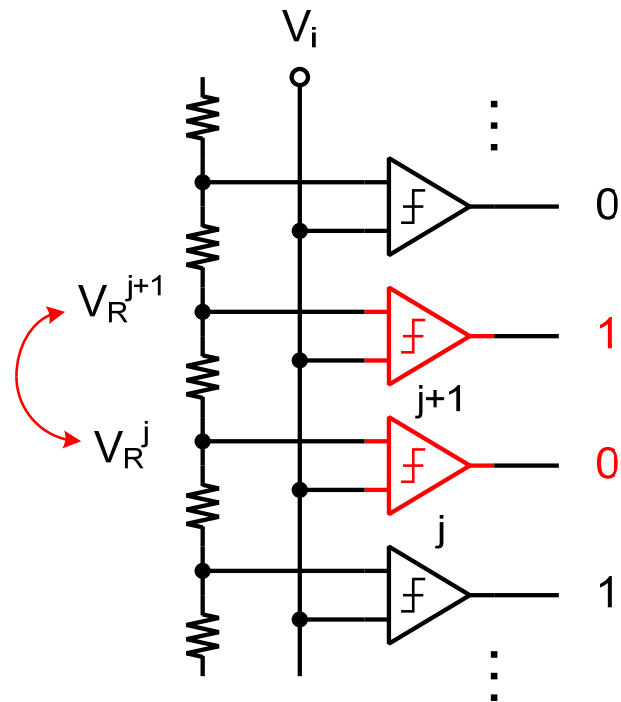


Comparator offset

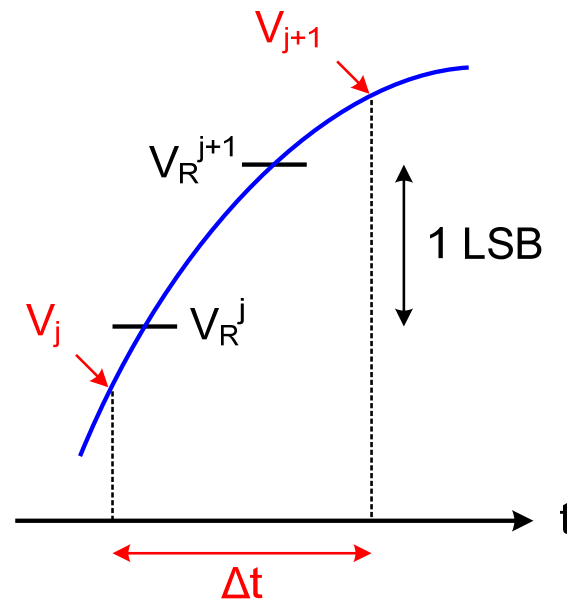

Timing error

Bubble-Tolerant Boundary Detector

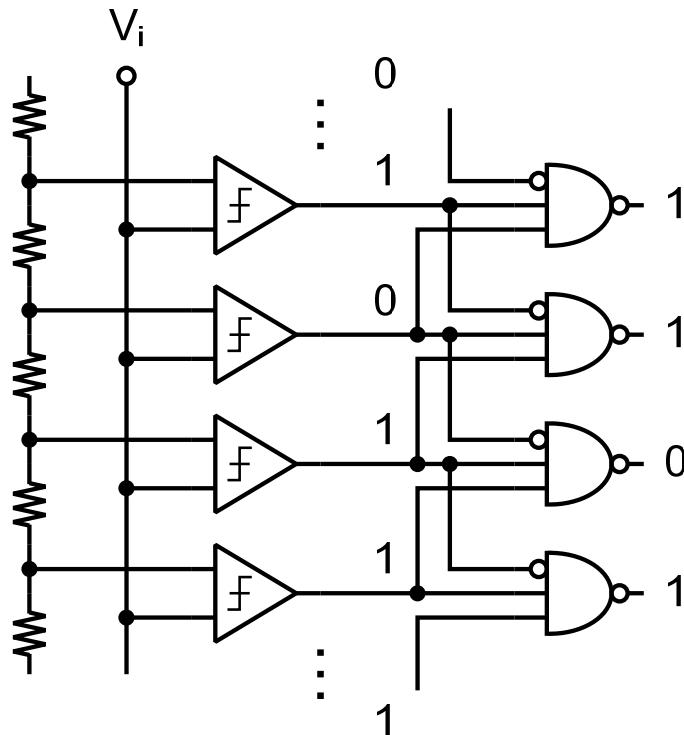

- 3-input NAND
- Detect “011” instead of “01” only
- “Single” bubble correction
- Biased correction

Ref: J. G. Peterson, “A monolithic video A/D converter,” *IEEE Journal of Solid-State Circuits*, vol. 14, pp. 932-937, issue 6, 1979.

Built-In Bias

	(A)	(B)	(C)	(D)
	0	0	0	0
	0	0	0	0
	0	0	1	0
① →	0	0	0	1
② →	1	0	0	1
③ →	0	1	1	0
	1	1	1	0
	1	0	1	1
	1	1	1	1
	1	1	1	1

Case	"011" Det.	"001" Det.
A	③	①
B	Fail	②
C	②	Fail
D	Fail	Fail

Inspecting more neighboring comparator outputs improves performance

Majority Voting Logic

$$C_j^* = C_{j-1}C_j + C_jC_{j+1} + C_{j-1}C_{j+1}$$

	(A)	(B)	(C)	(D)
	0	0	0	0
	0	0	0	0
	0	0	1	0
① →	0	0	0	1
② →	1	0	0	1
③ →	0	1	1	0
	1	1	1	0
	1	1	1	1
	1	0	1	1
	1	1	1	1
	1	1	1	1

Case	"011" Det.	Majority voting
A	③	②
B	Fail	②
C	②	②
D	Fail	Fail

Ref: C. W. Mangelsdorf, "A 400-MHz input flash converter with error correction," *IEEE Journal of Solid-State Circuits*, vol. 25, pp. 184-191, issue 1, 1990.

Gray Encoding

$$G_1 = T_1 \overline{T_3} + T_5 \overline{T_7}$$

$$G_2 = T_2 \overline{T_6}$$

$$G_3 = T_4$$

**Only one transition
b/t adjacent codes**

Thermometer							Gray			Binary		
0	0	0	0	0	0	0	0	0	0	0	0	0
1	0	0	0	0	0	0	0	0	1	0	0	1
1	1	0	0	0	0	0	0	1	1	0	1	0
1	1	1	0	0	0	0	0	1	0	0	1	1
1	1	1	1	0	0	0	1	1	0	1	0	0
1	1	1	1	1	0	0	1	1	1	1	0	1
1	1	1	1	1	1	0	1	0	1	1	1	0
1	1	1	1	1	1	1	1	0	0	1	1	1
T_1	T_2	T_3	T_4	T_5	T_6	T_7	G_3	G_2	G_1	B_3	B_2	B_1

- One comparator output is ONLY used once → No branching!
- Gray encoding fails benignly in the presence of bubbles
- Codes are also robust over metastability errors

Gray Encoding

Thermometer	Gray	Decimal
1 1 1 1 1 1 1 1 1 1 1 1 0 0	1 0 1 1	13
1 1 1 1 1 1 1 1 1 1 1 0 1 0	1 0 0 0	15
1 1 1 1 1 1 1 1 1 1 1 0 0 1	1 0 1 0	12

$$\begin{aligned}
 G_1 &= T_1 \overline{T_3} + T_5 \overline{T_7} \\
 G_2 &= T_2 \overline{T_6} \\
 G_3 &= T_4
 \end{aligned}$$


Conversion of Gray code to binary code is quite time-consuming → “quasi” Gray code

Ref: Y. Akazawa, et al., “A 400MSPS 8b flash AD conversion LSI,” in *IEEE International Solid-State Circuits Conference*, Dig. Tech. Papers, 1987, pp. 98-99.



Flash ADC: Binary Decoders


Gray Encoded ROM Decoder

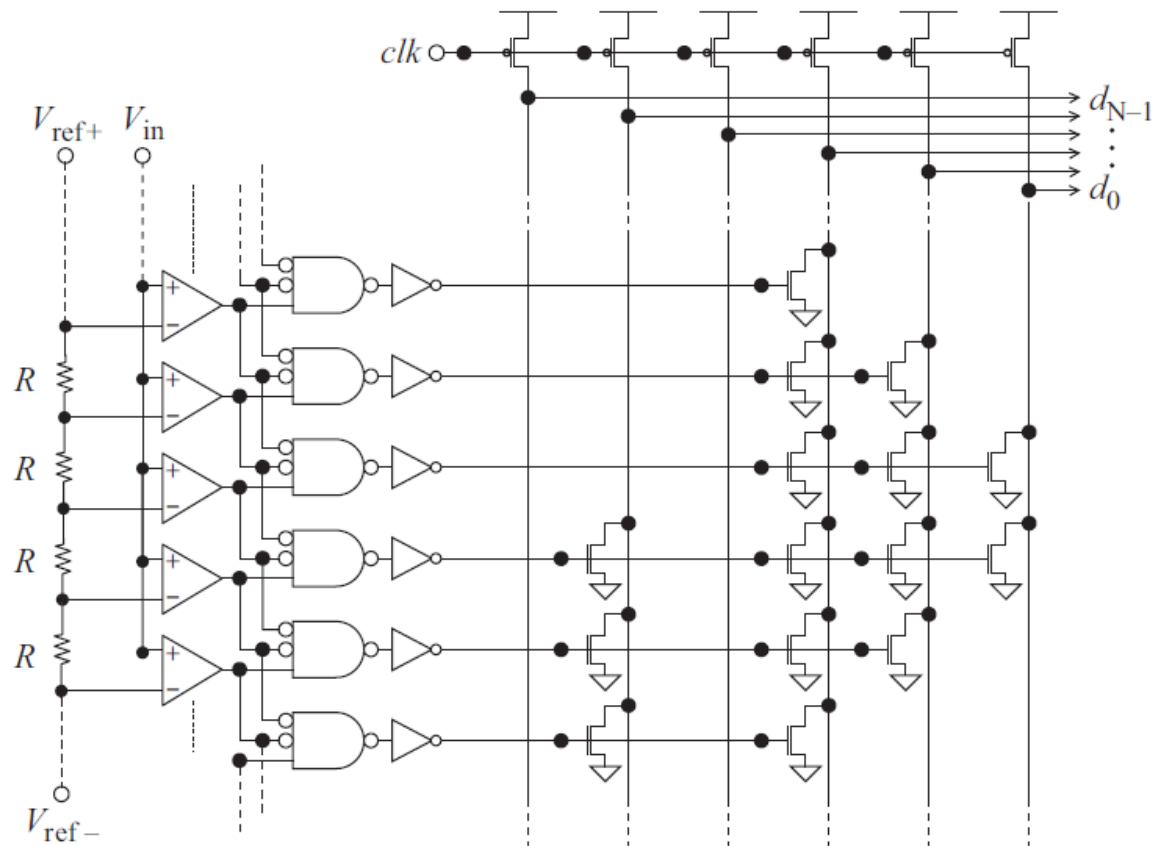

Thermometer-to-Binary Decoders for Flash Analog-to-Digital Converters


Erik Säll and Mark Vesterbacka

Wallace Tree Adder (1^s Adder)

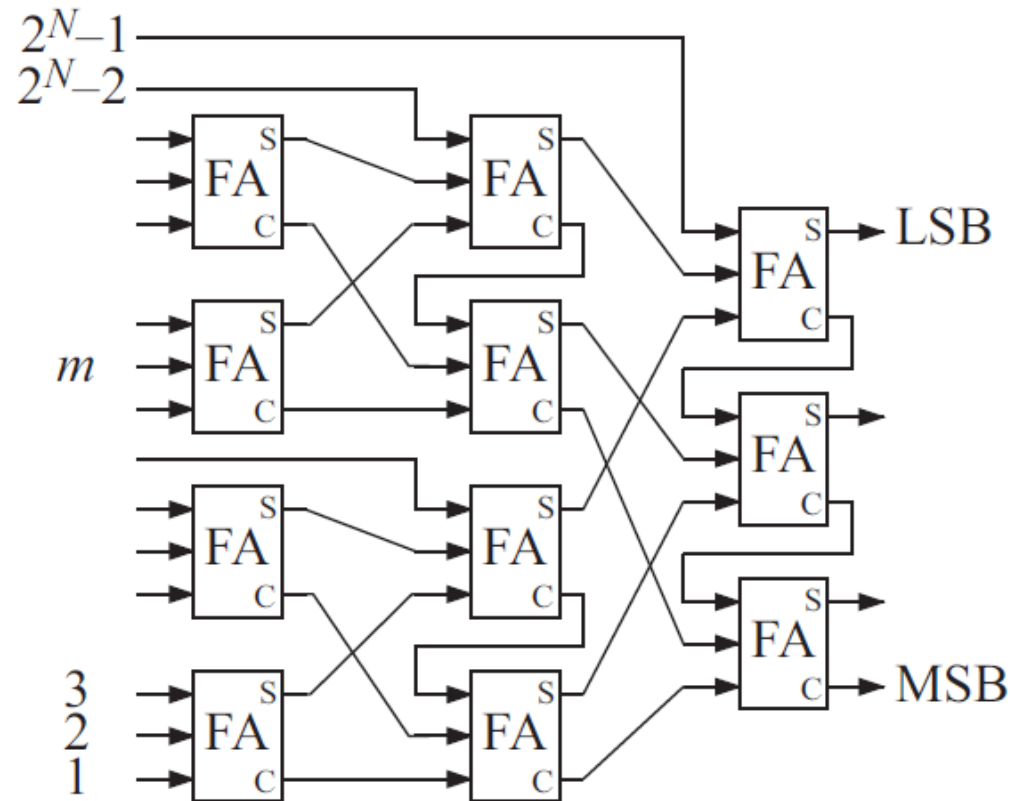


Wallace tree decoder for an $N = 4$ -bit flash ADC.

Folded Wallace Tree Decoder

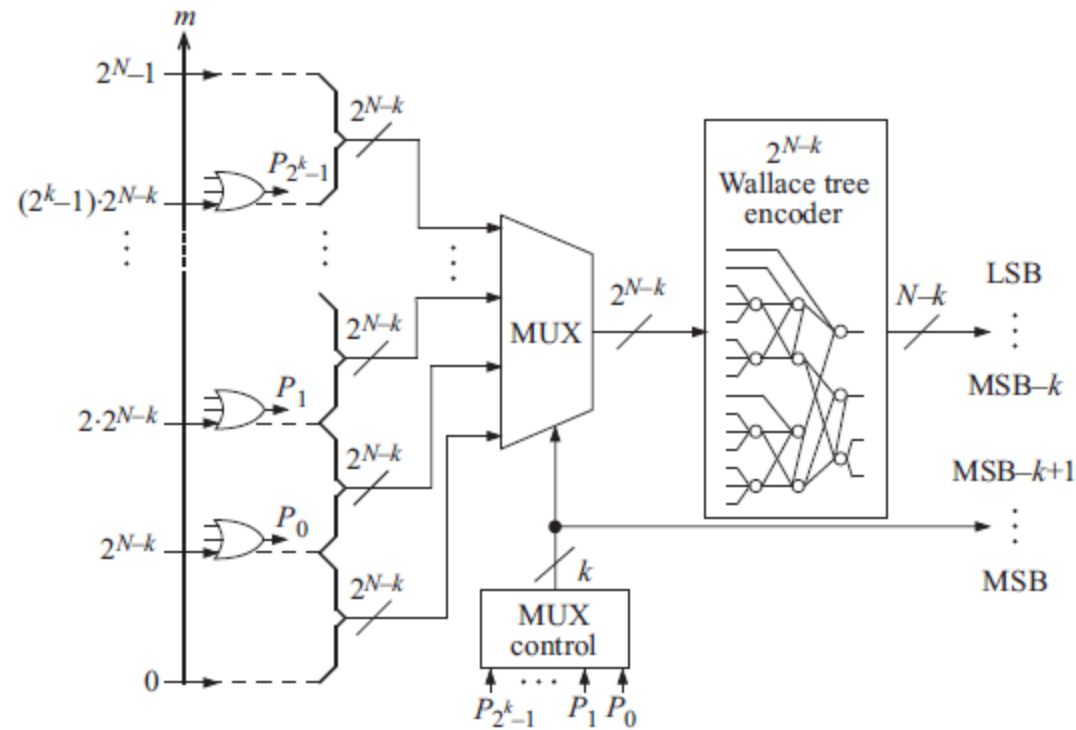


MUX-based Decoder

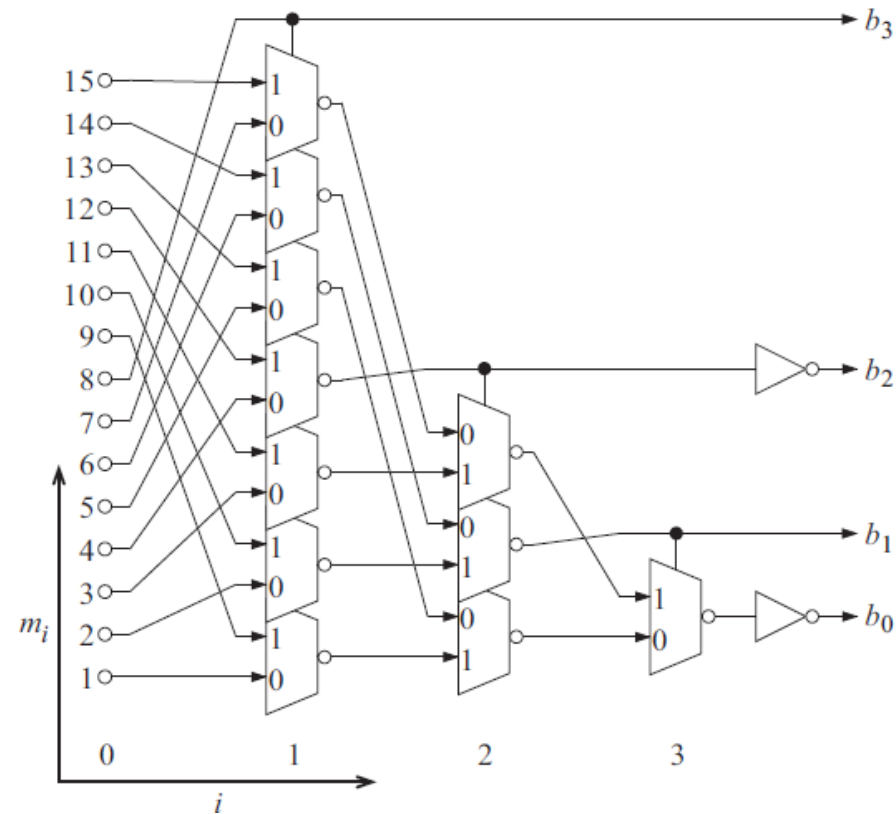

Multiplexer-based decoder for $N = 4$ bits.

Comparison of Decoder Schemes


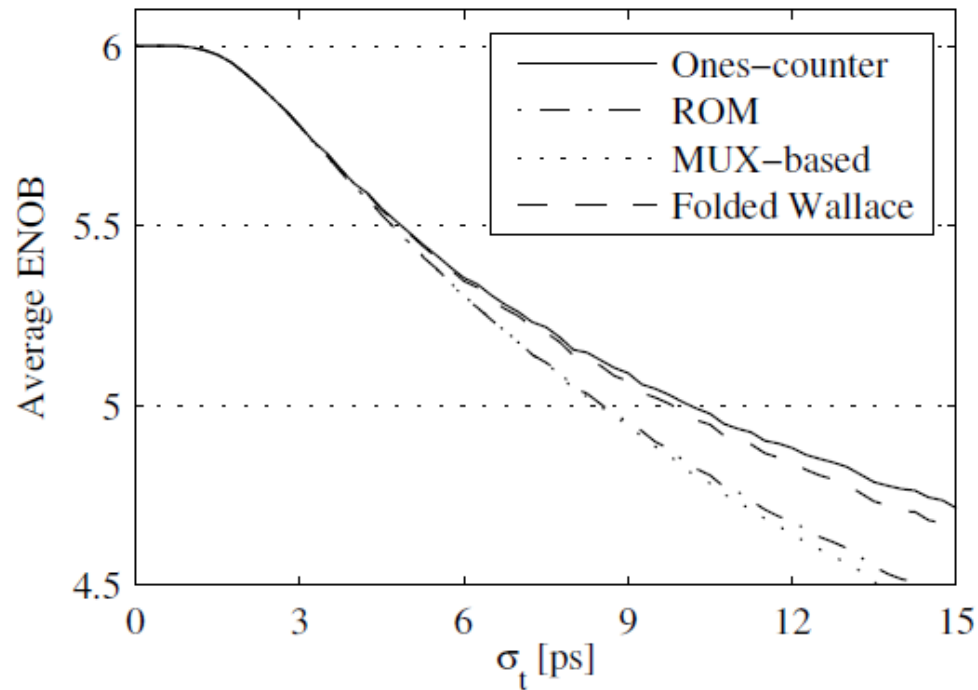


- Mostly custom design at higher speeds
- Pipeline the digital backend at high-sampling rates to meet clock timing
 - $T_{pd} < T_{CK} - (t_{pcq} + t_{setup})$
 - $T_{cd} > t_{hold} - t_{ccq}$




Flash ADC: Other Techniques

Offset Averaging (1)

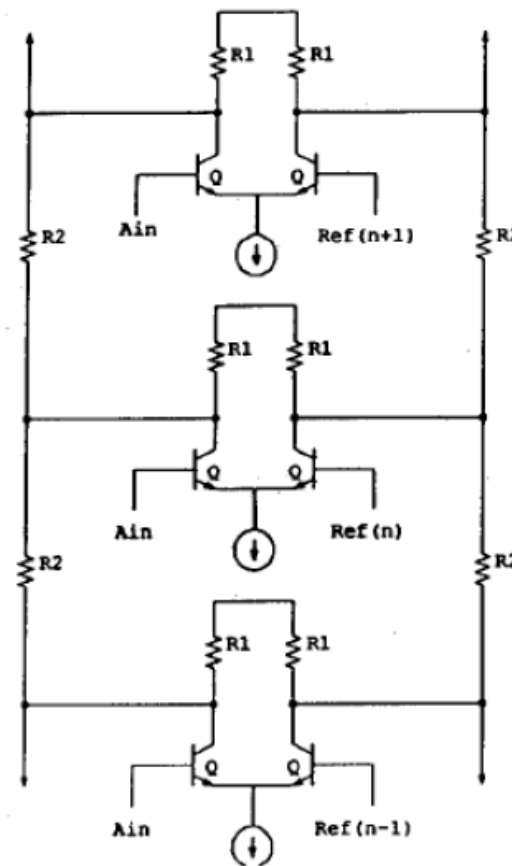
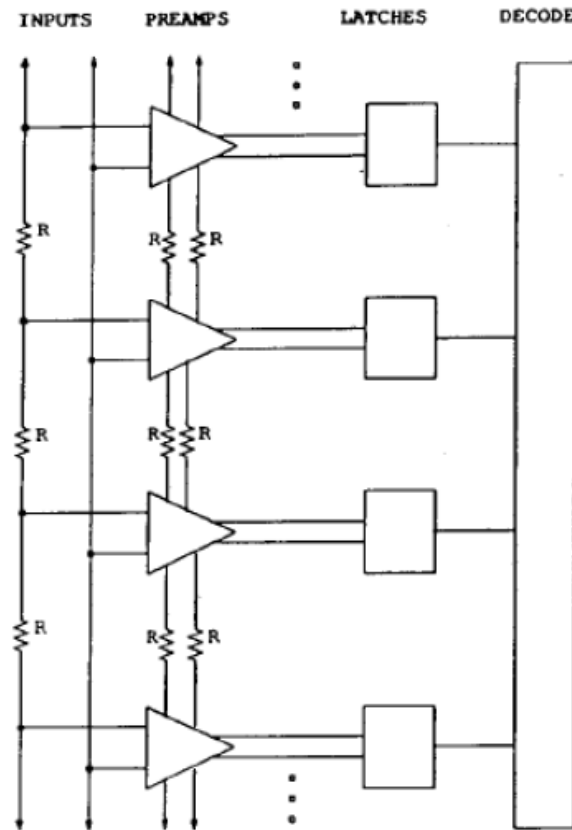


[Kattmann & Barrow, ISSCC 1991]

Offset Averaging (2)

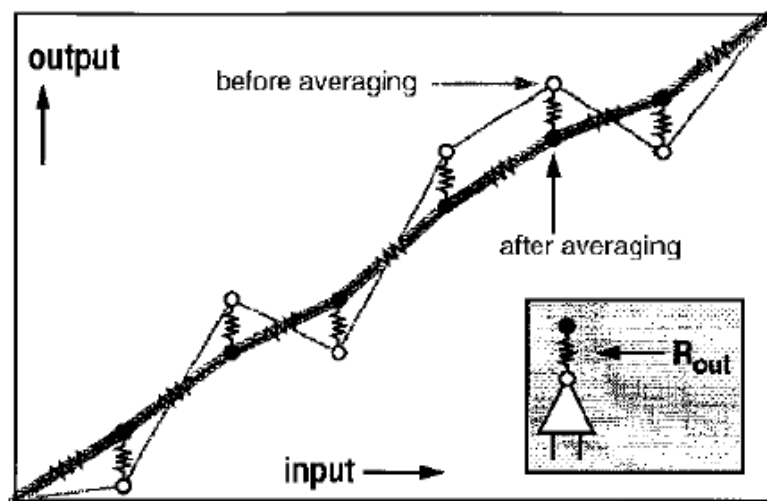


[Bult & Buchwald, JSSC 12/1997]

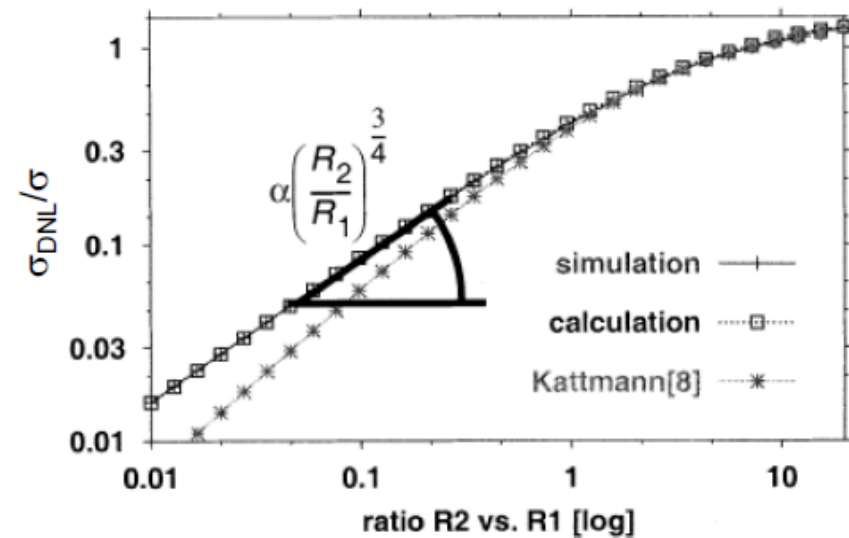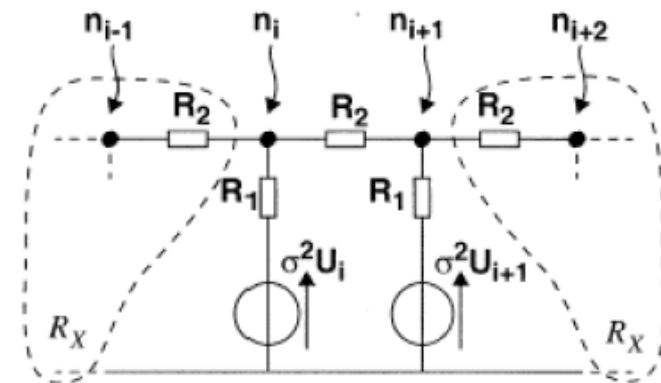

[Scholtens & Vertregt, JSSC 12/2002]

Flash ADC with Averaging

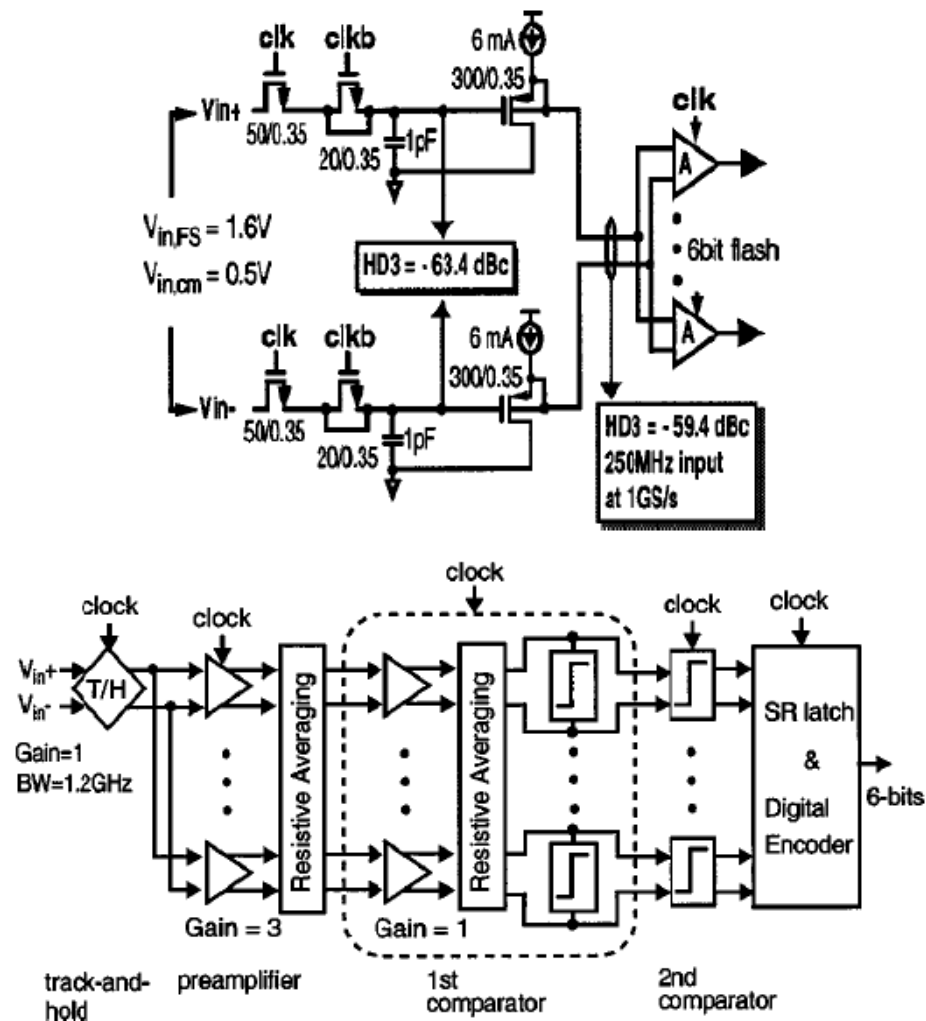


[Choi & Abidi, JSSC 12/2001]

Resolution	6 bits
Conversion Rate	1.3 GS/s
INL/DNL @ $F_s = 1 \text{ GHz}$	0.35 LSB / 0.2 LSB
Input Range	1.6 V_{p-p} differential
Input Capacitance (T/H)	1 pF
Bit Error Rate @ $f_s = 1 \text{ GHz}$	$< 10^{-10}$
SFDR @ $f_{in} = 100 \text{ MHz}$	$> 44 \text{ dB}$ up to 1.3 GS/s
SNDR @ $f_{in} = 630 \text{ MHz}$ @ $f_{in} = 650 \text{ MHz}$	35 dB @ 1 GS/s 32 dB @ 1.3 GS/s
Power Dissipation (50% due to logic and clock)	500 mW @ 1 GS/s 545 mW @ 1.3 GS/s
Voltage Supply	3.3 V
Active/Total Die Area	2x0.4 mm ² / 2.2x2.2 mm ²
Technology	0.35- μm CMOS


Averaging networks designed to reduce input referred offset by 3x

Offset Calibration

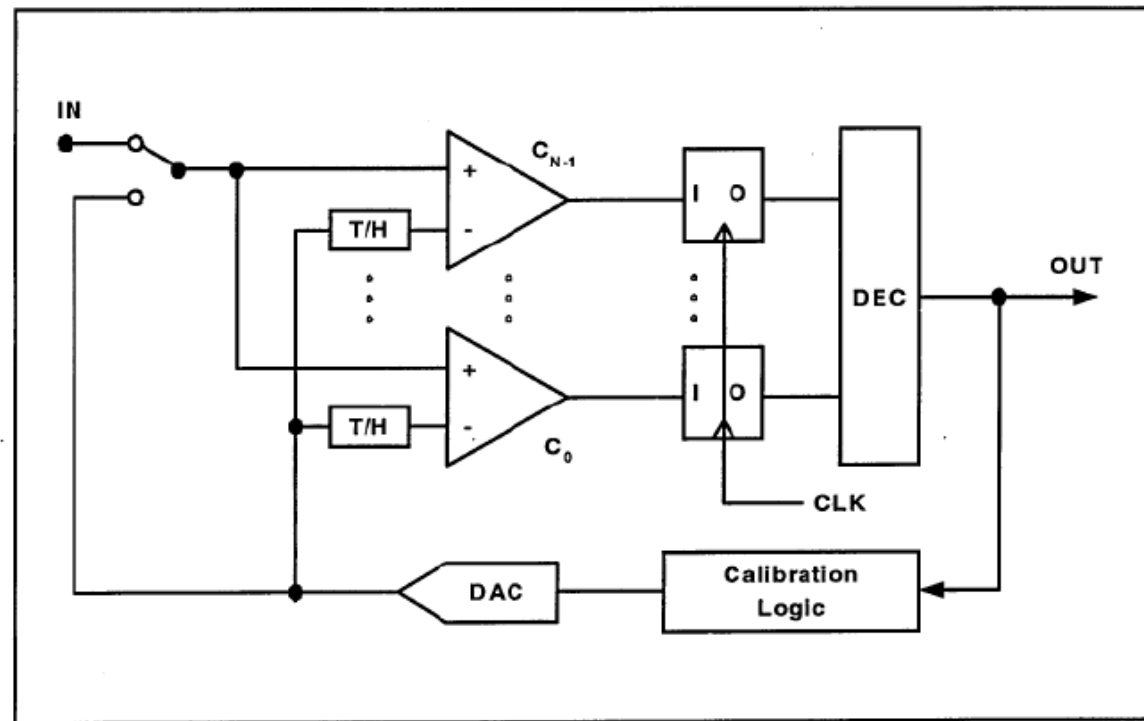


S. Sutardja, "360 Mb/s (400 MHz) 1.1 W 0.35 μ m CMOS PRML read channels with 6 burst 8-20 $\times$ over-sampling digital servo," ISSCC Dig. Techn. Papers, Feb. 1999.

Comparator with Offset Correcting DAC

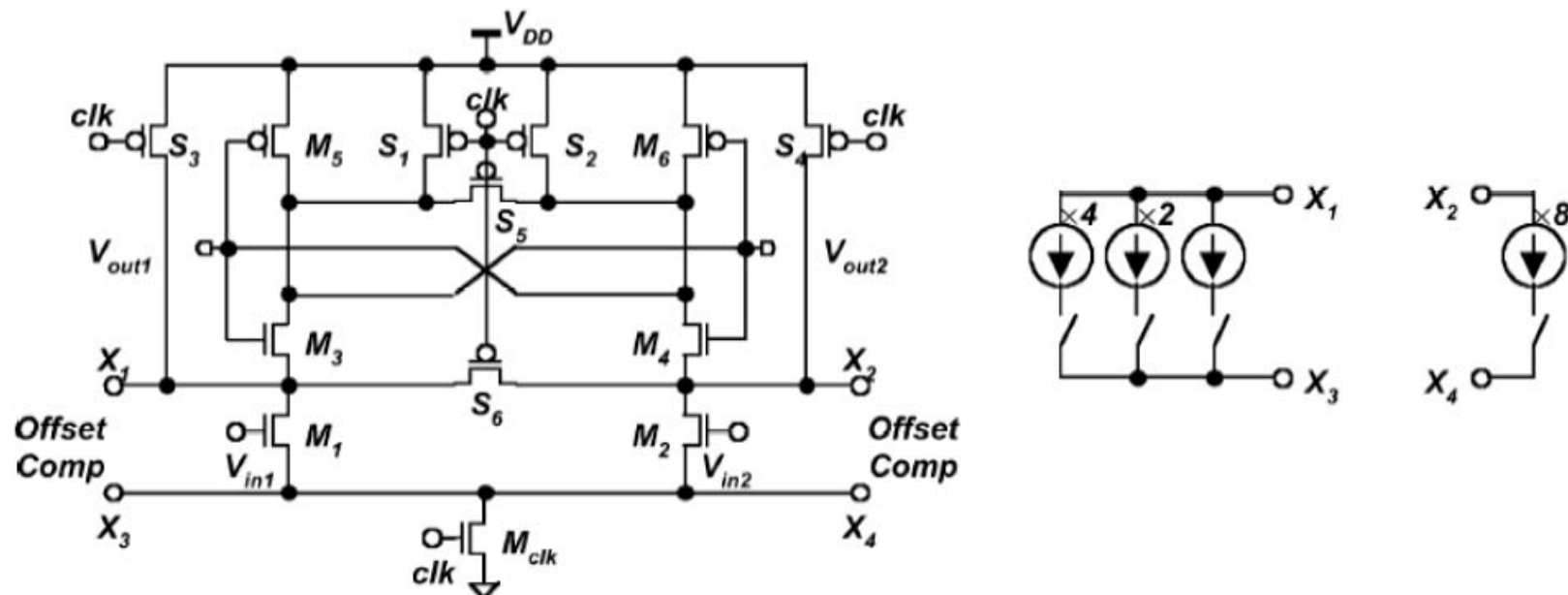

[K.-L.J. Wong and C.-K.K. Yang, "Offset compensation in comparators with minimum input-referred supply noise," JSSC, May 2004.]


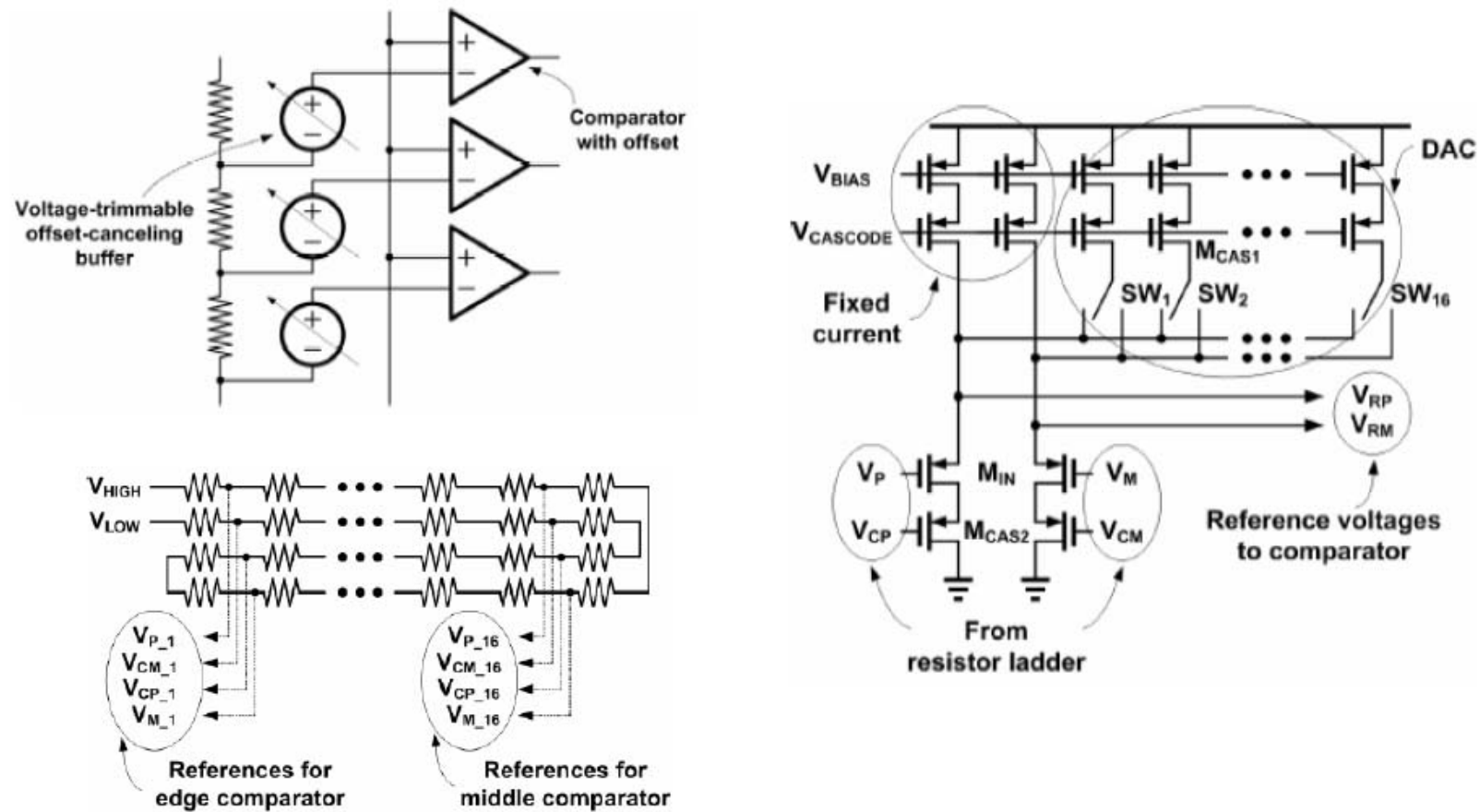
High-Performance Flash with Calibration (1)



[Park & Flynn, "A 3.5 GS/s 5-b Flash ADC in 90 nm CMOS," CICC 2006]

Comparator Redundancy (1)

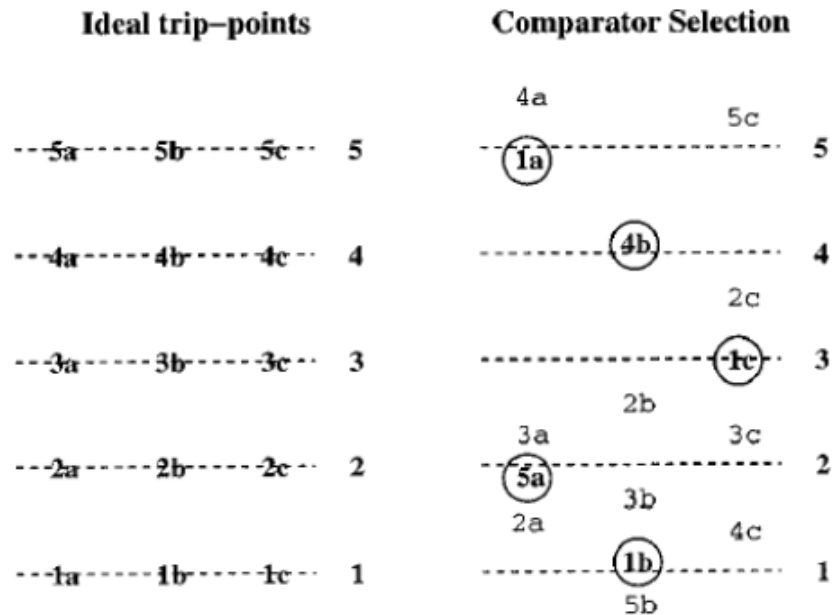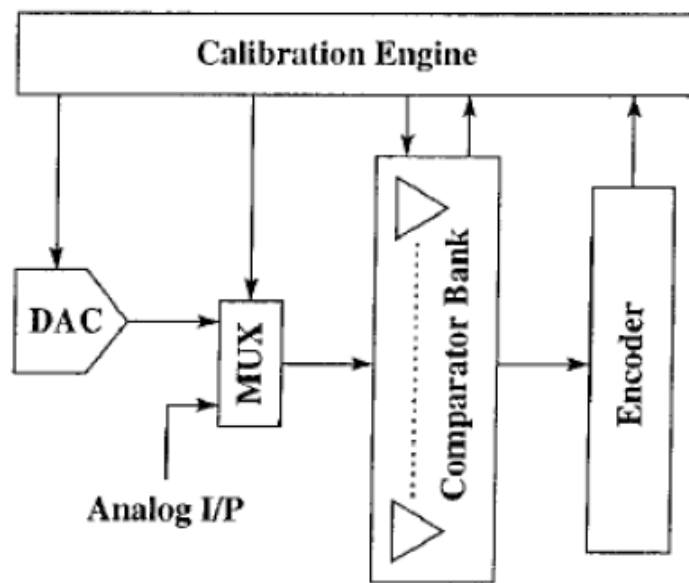- Idea: Build a "sea of imprecise comparators", then determine which ones to use...



C. Donovan, M. P Flynn, "A 'digital' 6-bit ADC in 0.25- μ m CMOS," IEEE J. Solid-State Circuits, pp. 432-437, March 2002.

Comparator Redundancy (2)


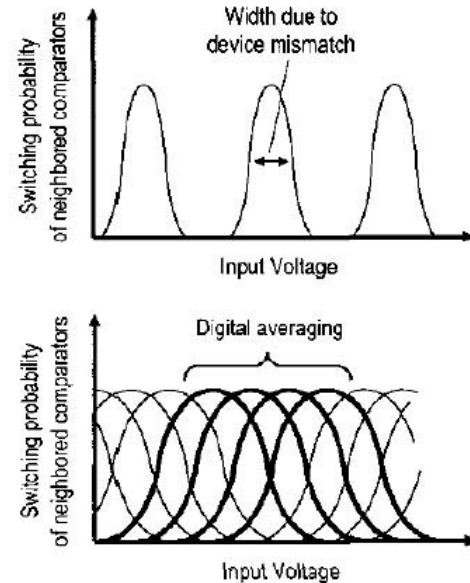
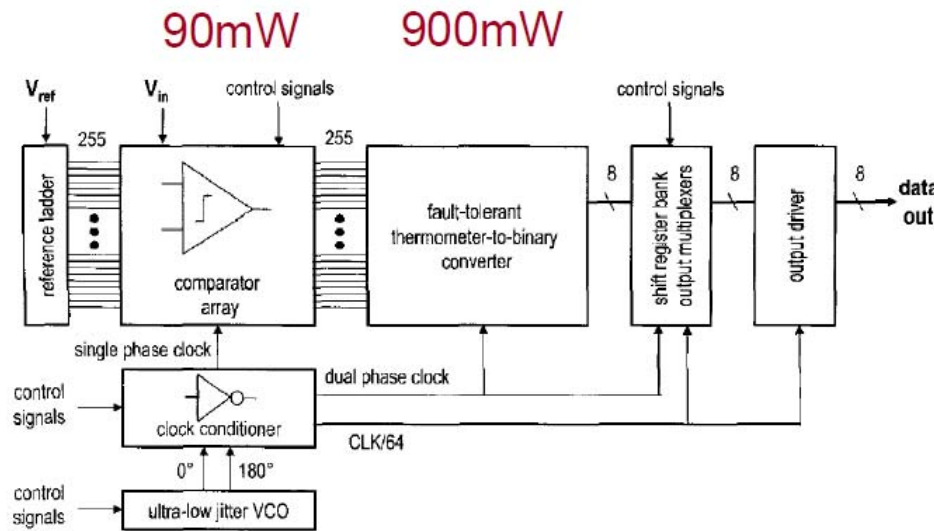
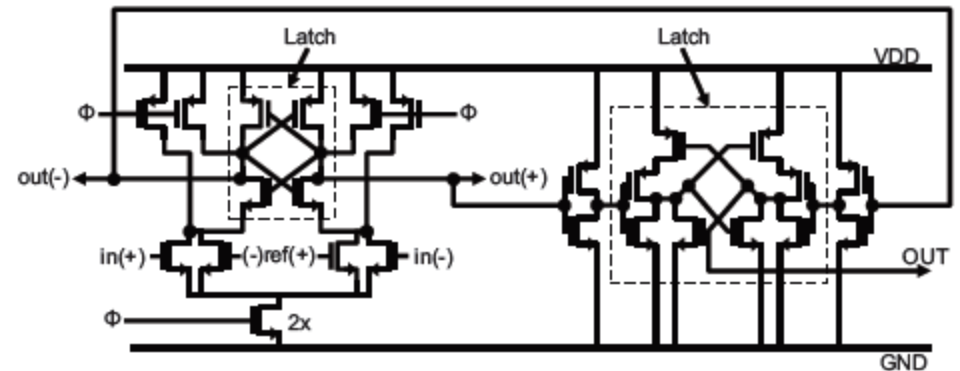
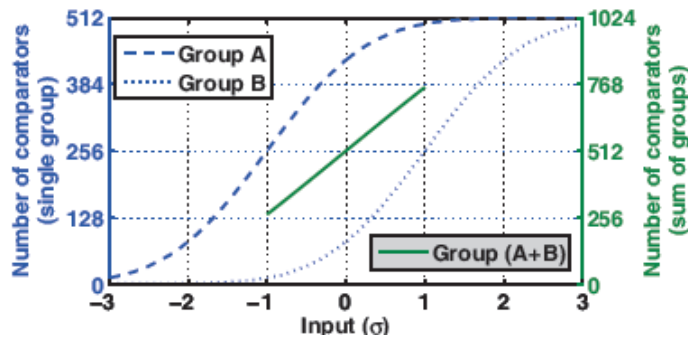
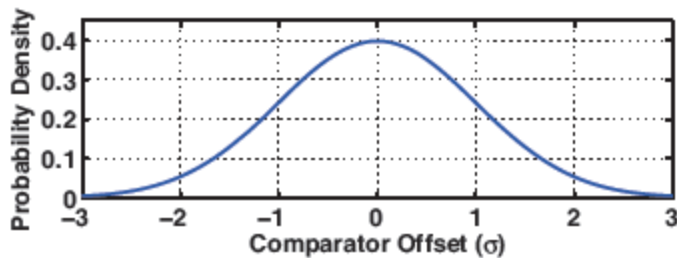


Fig. 1 Illustration of the ADC operation scheme.

Paulus et al., "A 4GS/s 6b flash ADC in 0.13um CMOS," *VLSI Circuits Symposium*, 2004

Stochastic Flash ADC

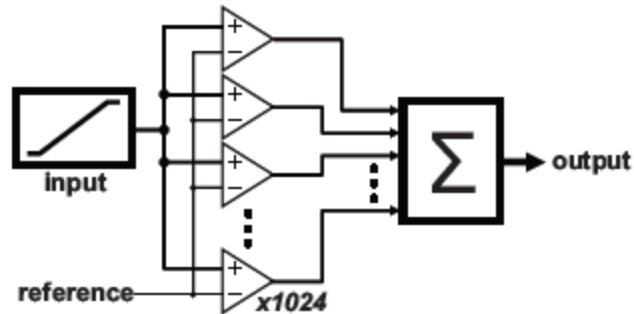

- Fully synthesized ADC using 'digital' comparator cells (large offsets)
- Use more than 1 comparator for a reference threshold
 - Use 'detection theory' to make accurate decisions around a threshold, by using more than one observation
- Low speed designs (<20 MS/s)

A 6b Stochastic Flash Analog-to-Digital Converter Without Calibration or Reference Ladder

Skyler Weaver¹, Benjamin Hershberg¹, Daniel Knierim², and Un-Ku Moon¹



Flash ADC: Case Study


Case Study: Distortion Compensating Flash ADC

IEEE JOURNAL OF SOLID-STATE CIRCUITS, VOL. 41, NO. 9, SEPTEMBER 2006

1959

A Distortion Compensating Flash Analog-to-Digital Conversion Technique

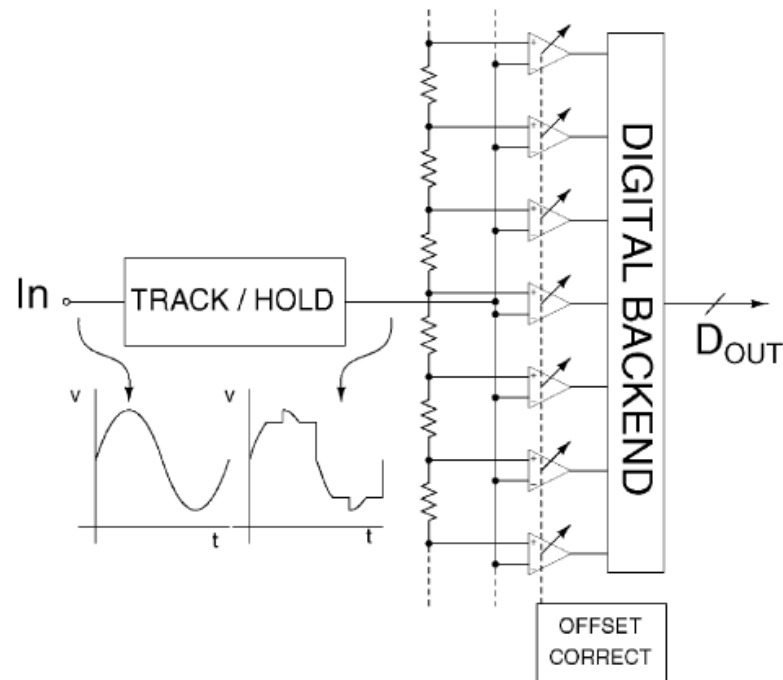Venkata Srinivas, Shanthi Pavan, Ashish Lachhwani, and Naga Sasidhar



T/H Distortion

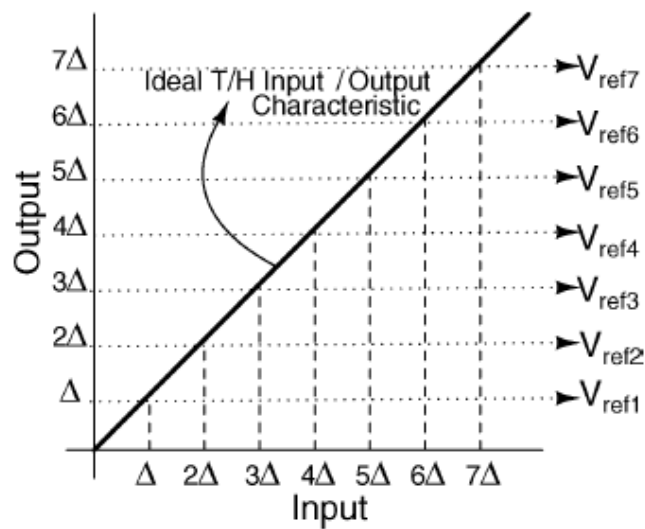


Fig. 2. Flash ADC behavior with an ideal track-and-hold.

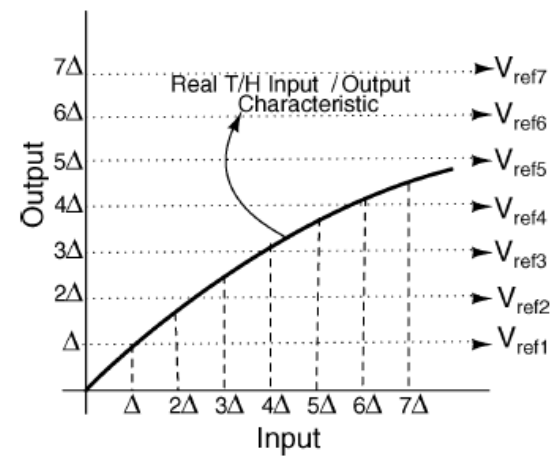


Fig. 3. Flash ADC behavior with a real track-and-hold having static nonlinearity.

Pre-distorted References



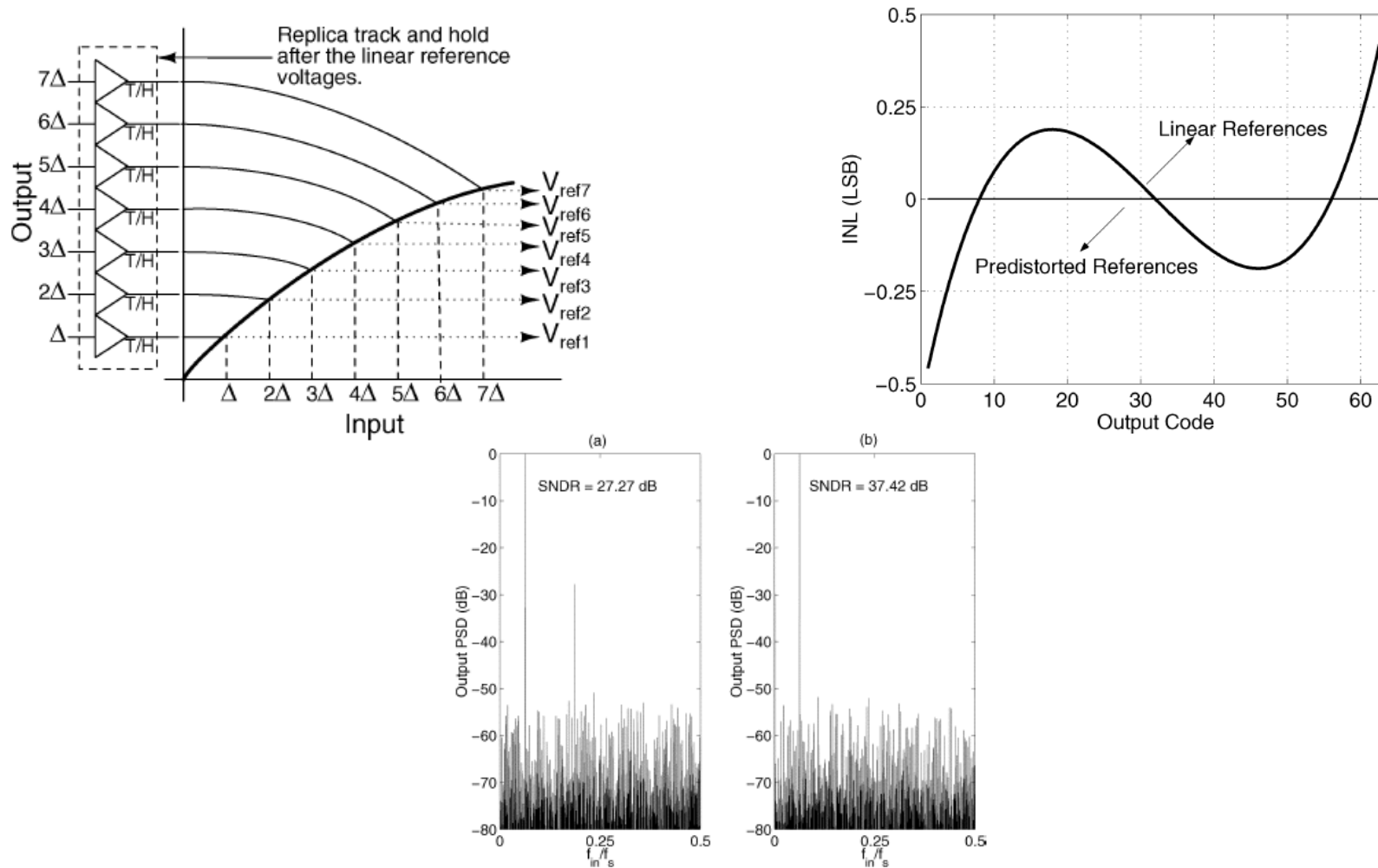
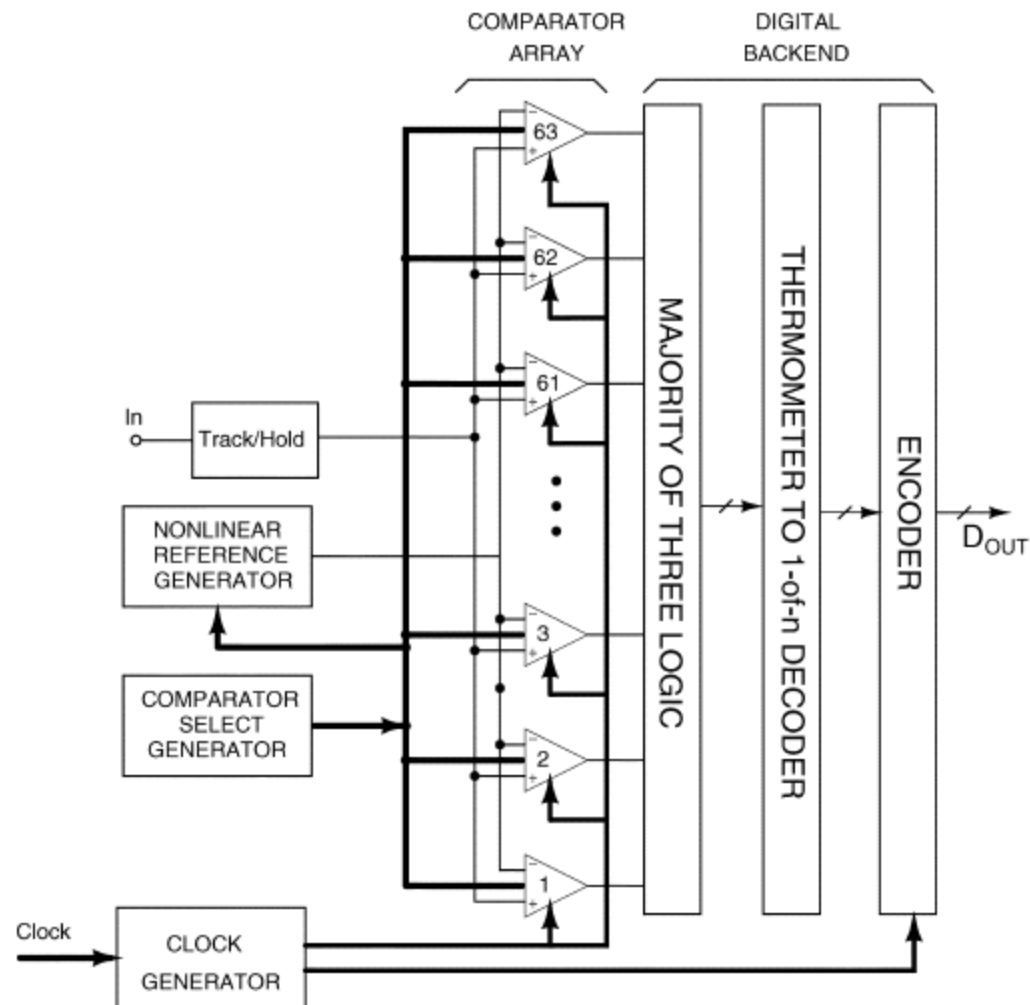


Fig. 5. ADC output spectrum with track-and-hold having static nonlinearity with (a) linear references and (b) pre-distorted references.



ADC Architecture

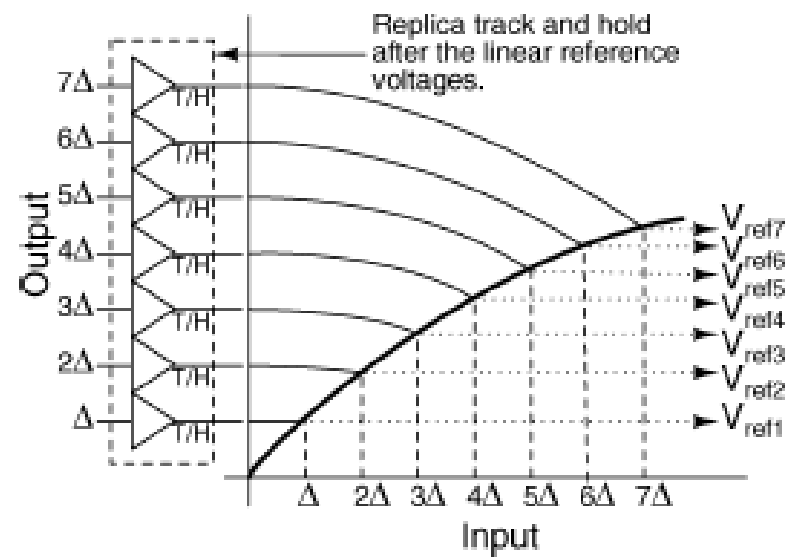

T/H Circuit

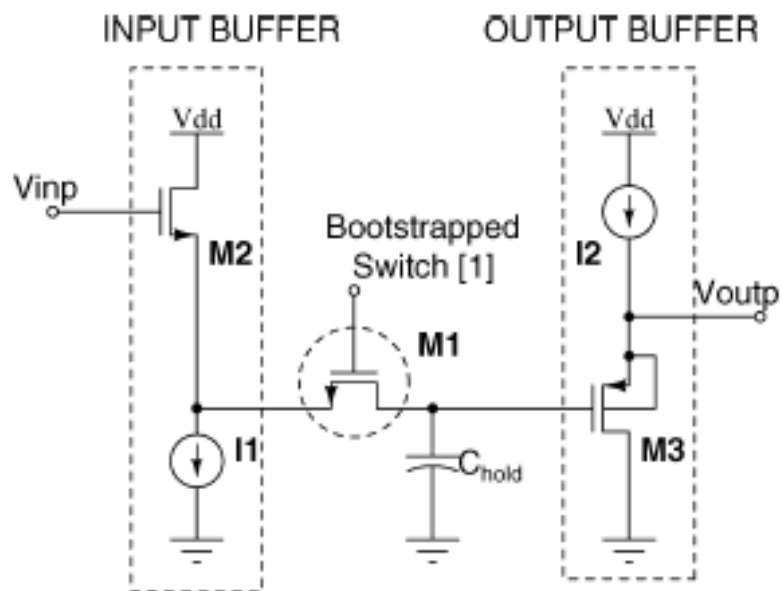


Comparator

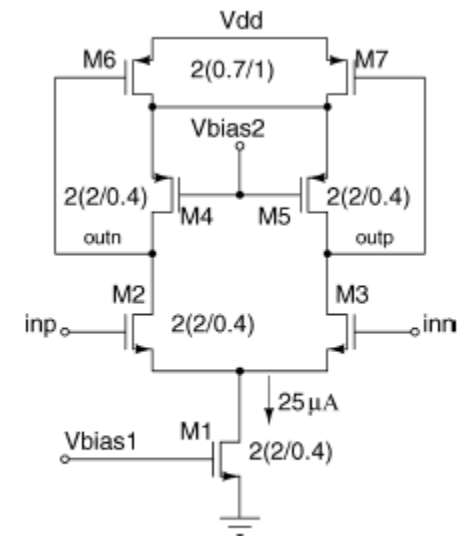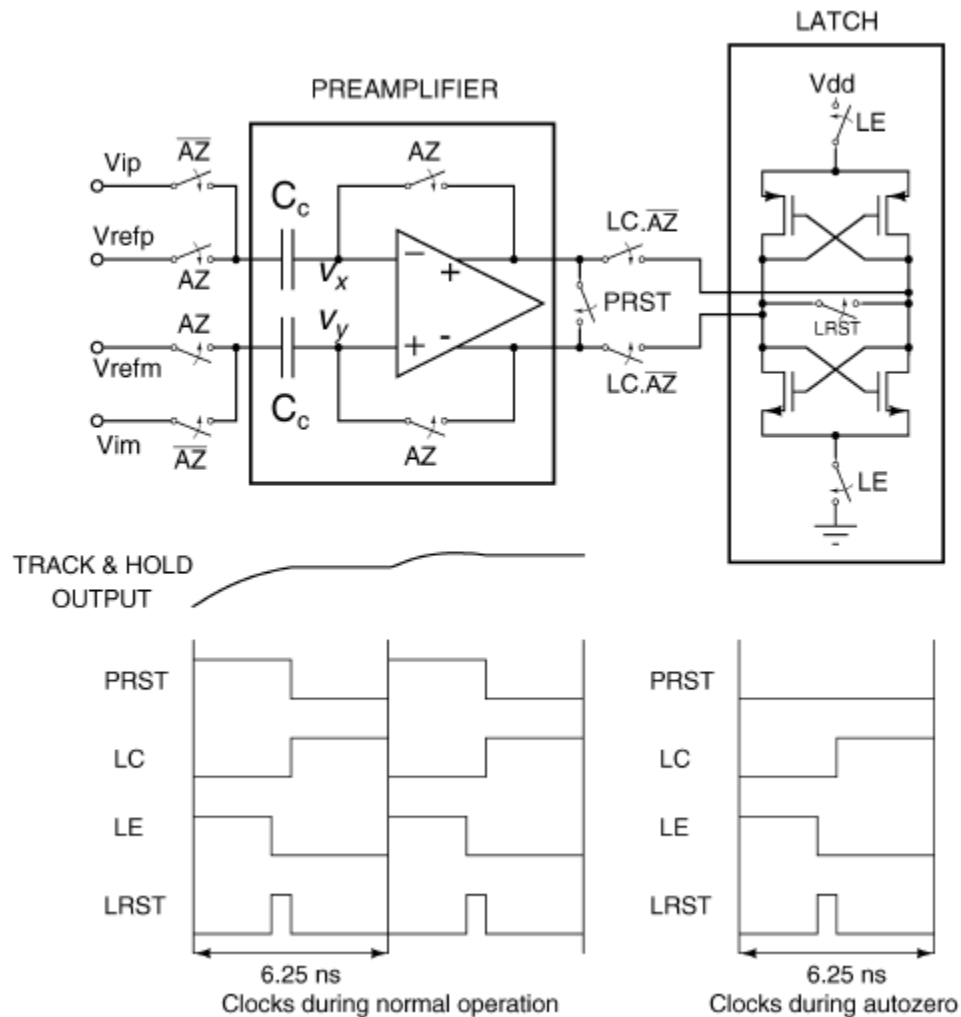

Schematic of the preamplifier.

Non-linear Reference Generator

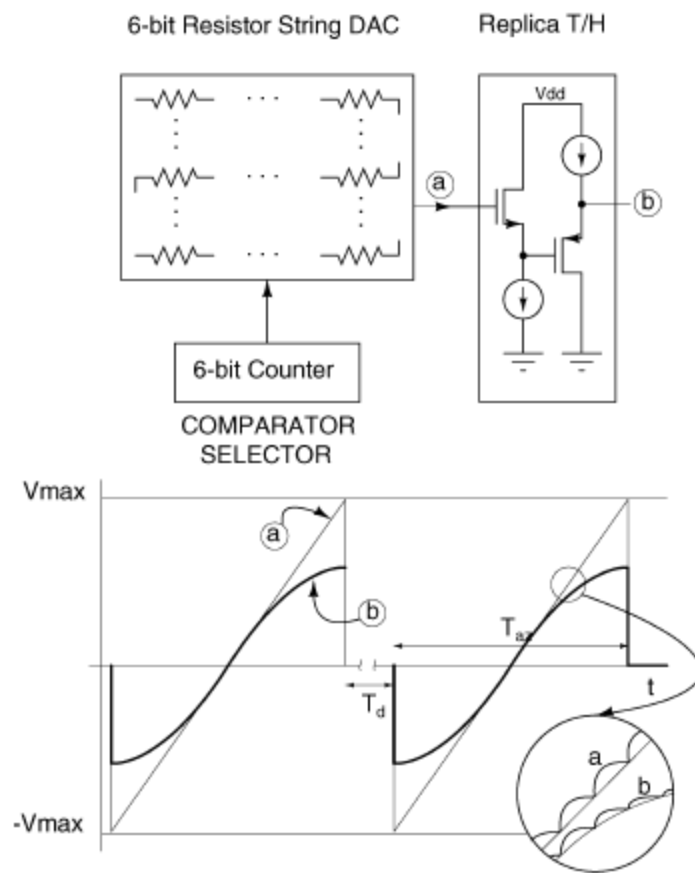

g. 12. Nonlinear reference generator.

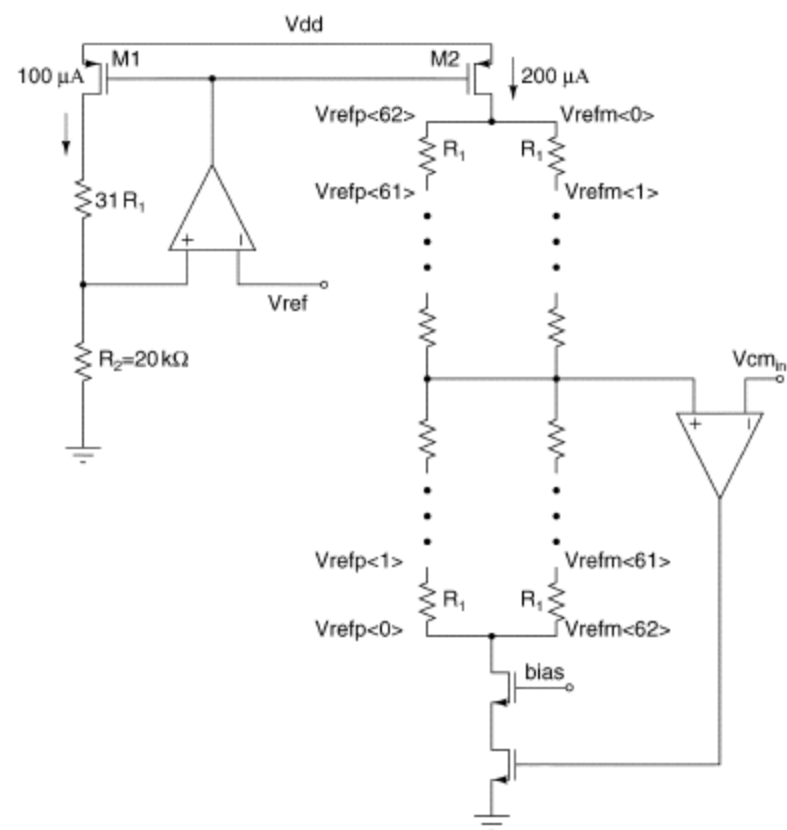


Fig. 13. Linear reference generator.

ADC Testing

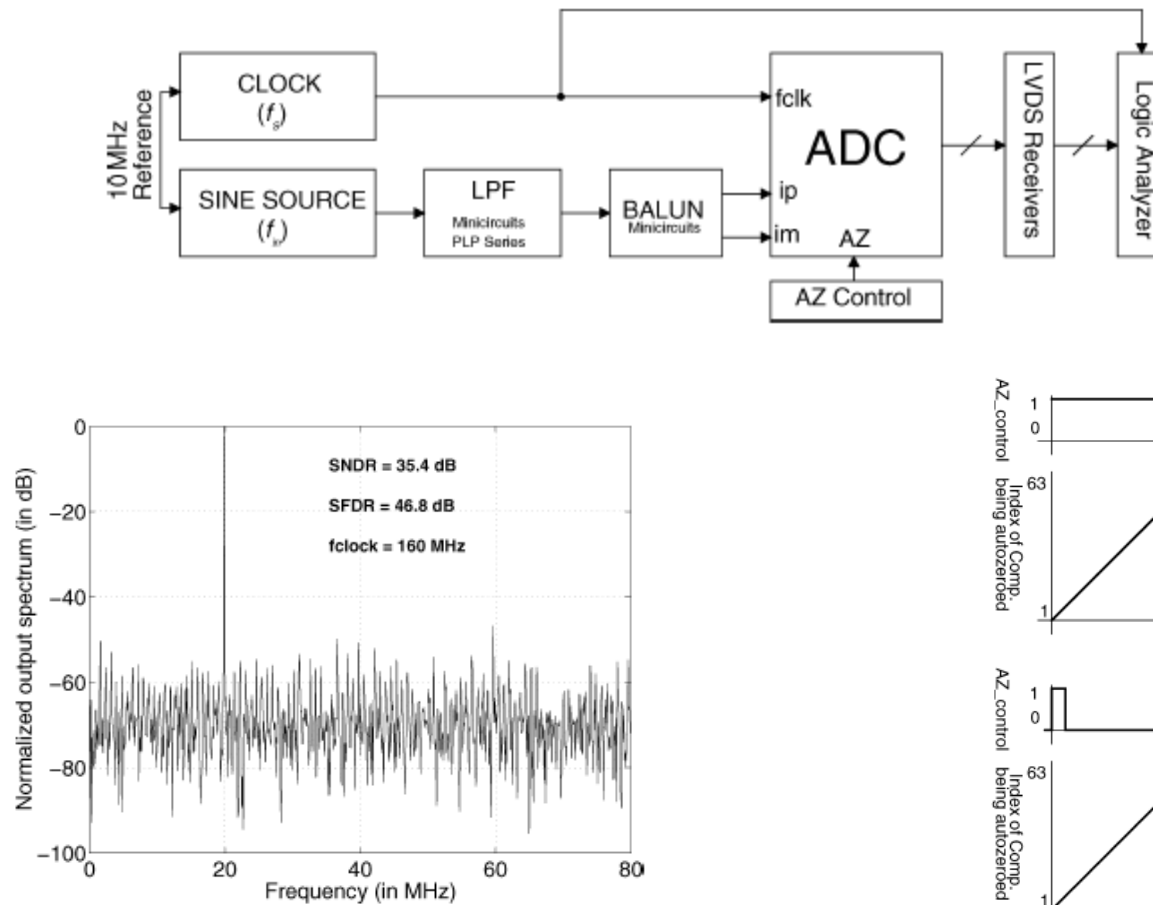


Fig. 19. Normalized output spectrum of the ADC.

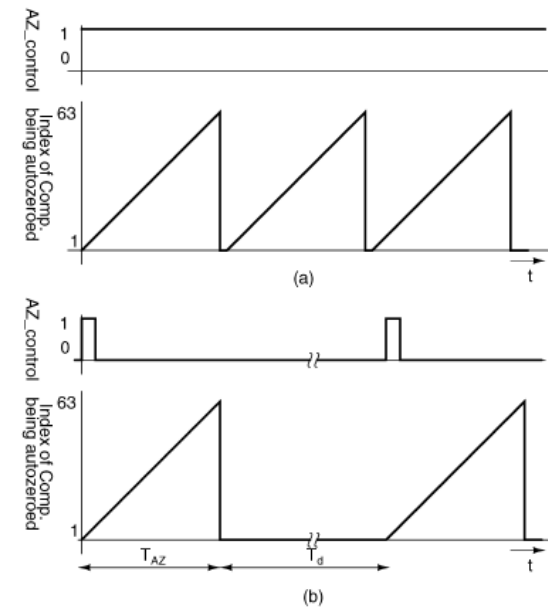


Fig. 20. Illustration of (a) continuous background autozero mode and (b) discontinuous background autozero mode.

Test Results

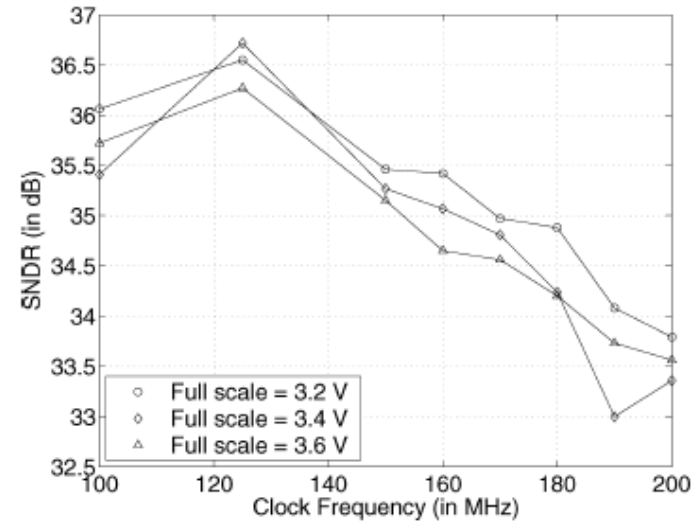
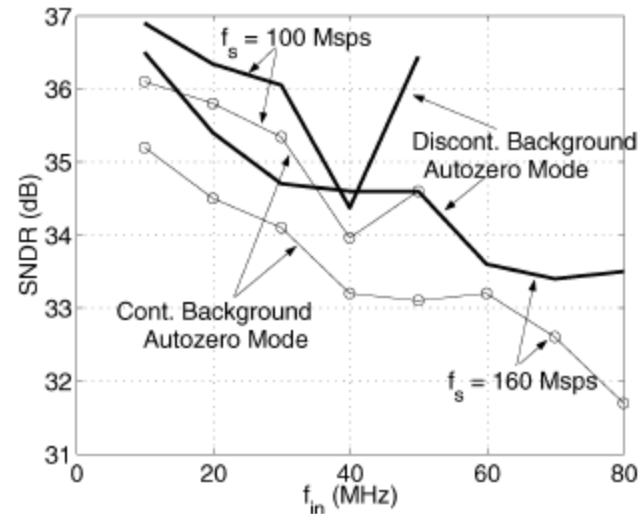


Figure of Merit

$$\frac{\text{Energy}}{(\text{conversion_step})} = \frac{P_{\text{diss}}}{2^{\text{ENOB}} \times f_{\text{samp}}}$$

SUMMARY OF ADC PERFORMANCE

Resolution	6 bits
Technology	0.35- μm CMOS 2P4M
Supply voltage	3.3 V
Nominal input swing	3.4 V_{pp} differential
DNL (nominal input range)	0.3 LSB
INL (nominal input range)	0.3 LSB
SNDR	36.0 dB @ $f_{in} = 49.9$ MHz, $f_s = 100$ MHz 33.6 dB @ $f_{in} = 79.9$ MHz, $f_s = 160$ MHz
Power consumption	50 mW @ $f_s = 160$ MHz
Active Area	2.0 $\times$ 0.4 mm ²
Chip package	DIP40

Title

References

1. Rudy van de Plassche, "CMOS Integrated Analog-to-Digital and Digital-to-Analog Converters," 2nd Ed., Springer, 2005.
2. M. Gustavsson, J. Wikner, N. Tan, *CMOS Data Converters for Communications*, Kluwer Academic Publishers, 2000.