

Loop Stability Analysis


Differential Opamp Simulation

Vishal Saxena & Zhu Kehan
Boise State University
(vishalsaxena@boisestate.edu)


Spectre STB Analysis

- ❑ The STB analysis linearizes the circuit about the DC operating point and computes the loop-gain, gain and phase margins (if the sweep variable is frequency), for a feedback loop or a gain device [1].
- ❑ Refer to the Spectre Simulation Reference [1] and [2] for details.
- ❑ Uses return ratio analysis method to calculate loop-gain and phase margin ([3, 4]).

Example Single-ended Opamp Schematic

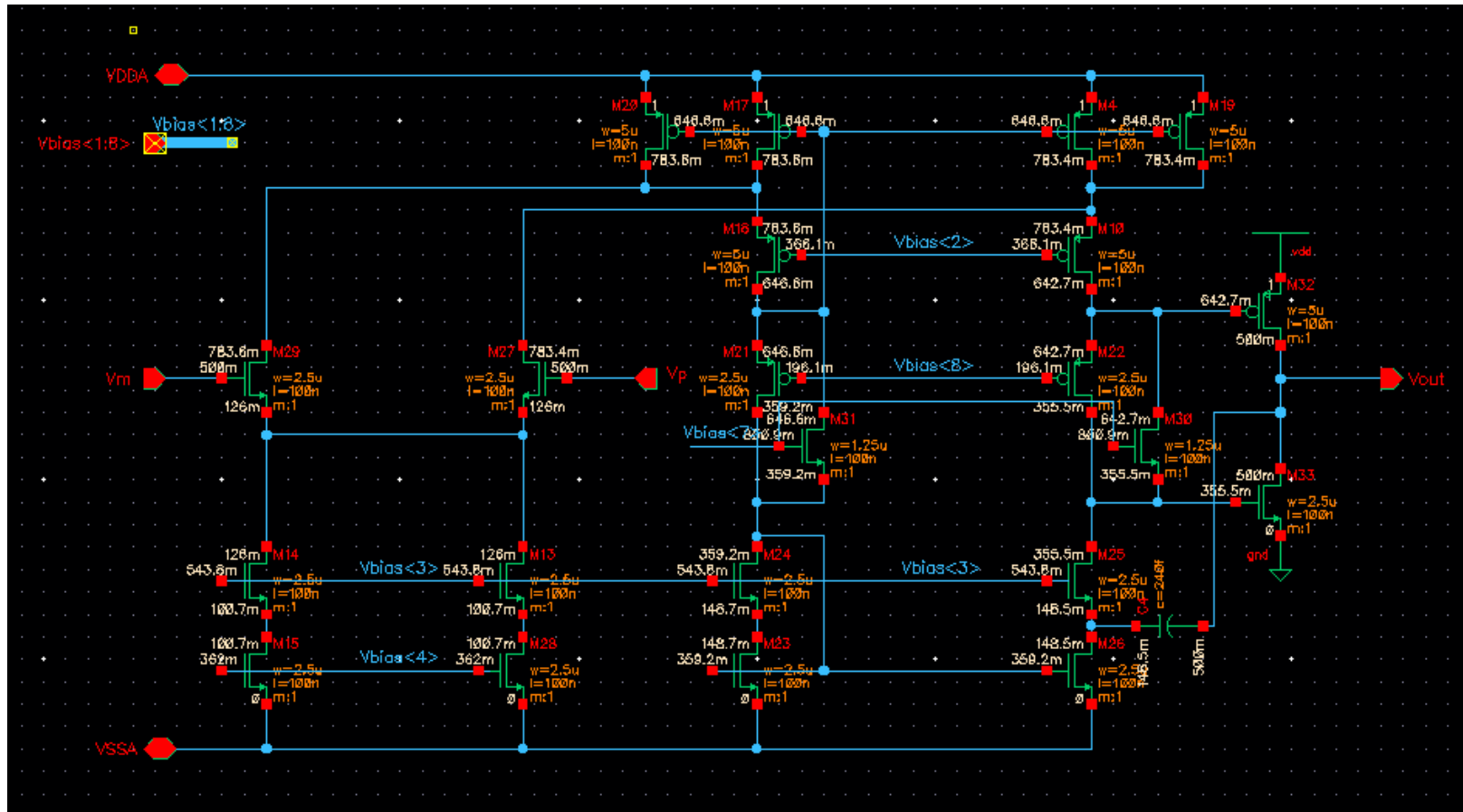


STB Analysis Test Bench

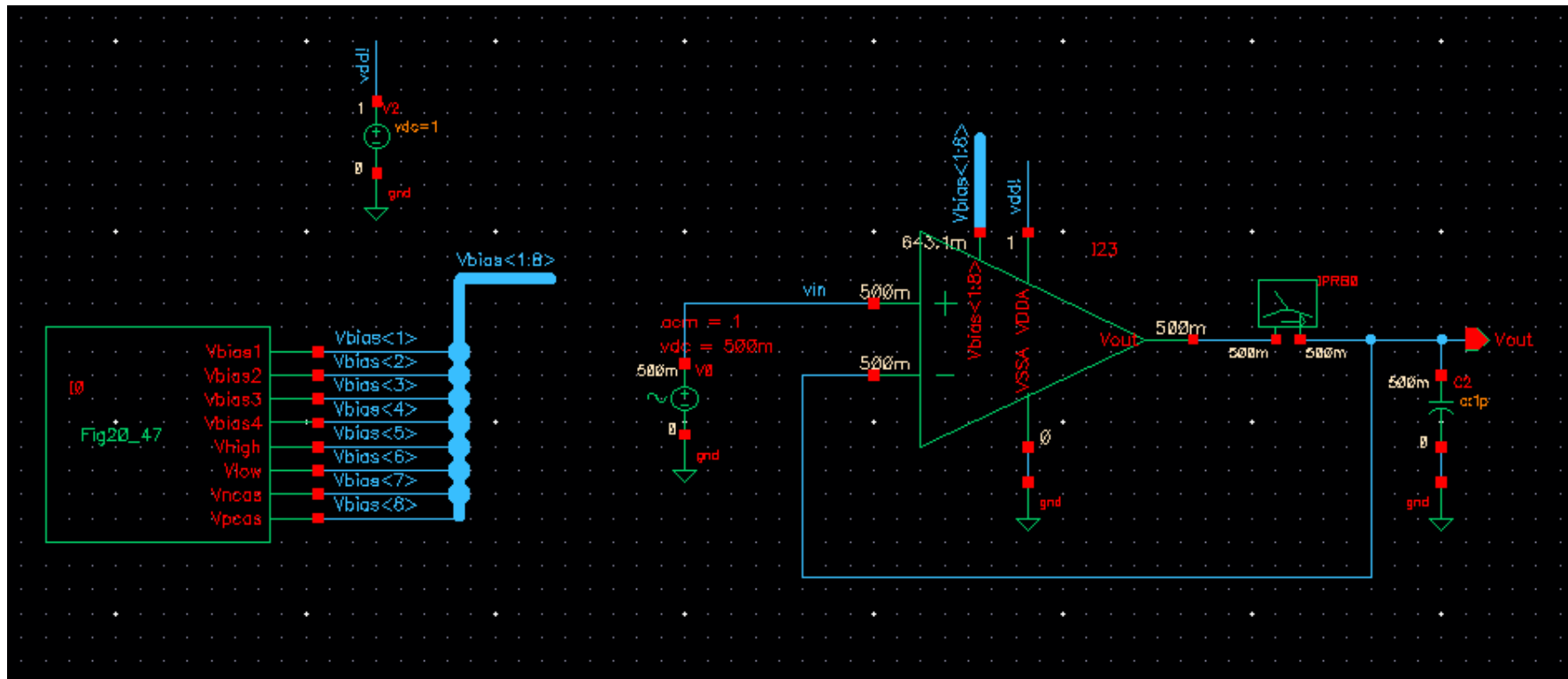


- ❑ Pay attention to the **iprobe** component (from analogLib)
 - Acts as a short for DC, but breaks the loop in stb analysis
- ❑ Place the probe at a point where it **completely breaks (all) the loops**.

DC Annotation

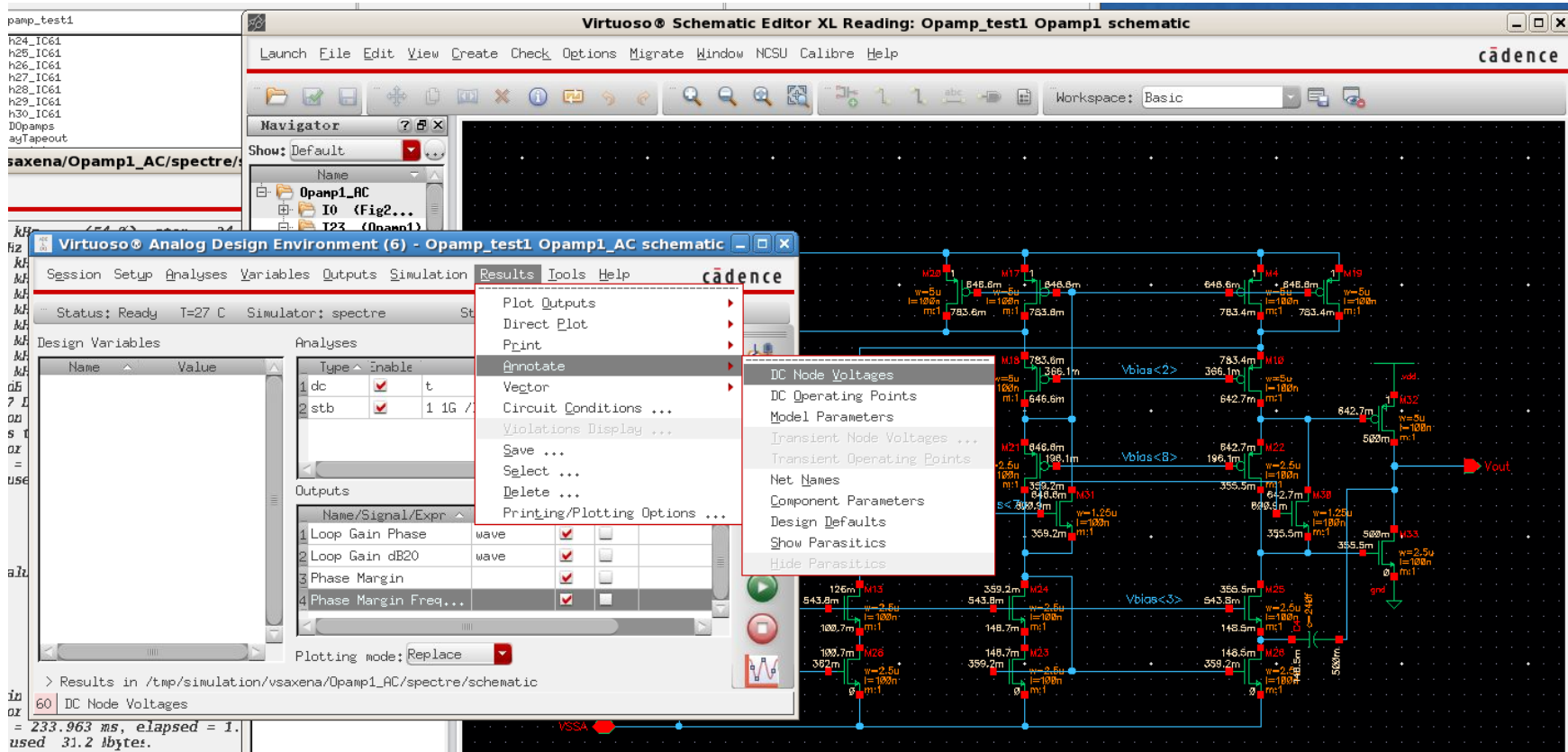


- Annotating the node voltages and DC operating points of the devices helps debug the design
- Check device gds to see if its in triode or saturation regions

Simulation Setup

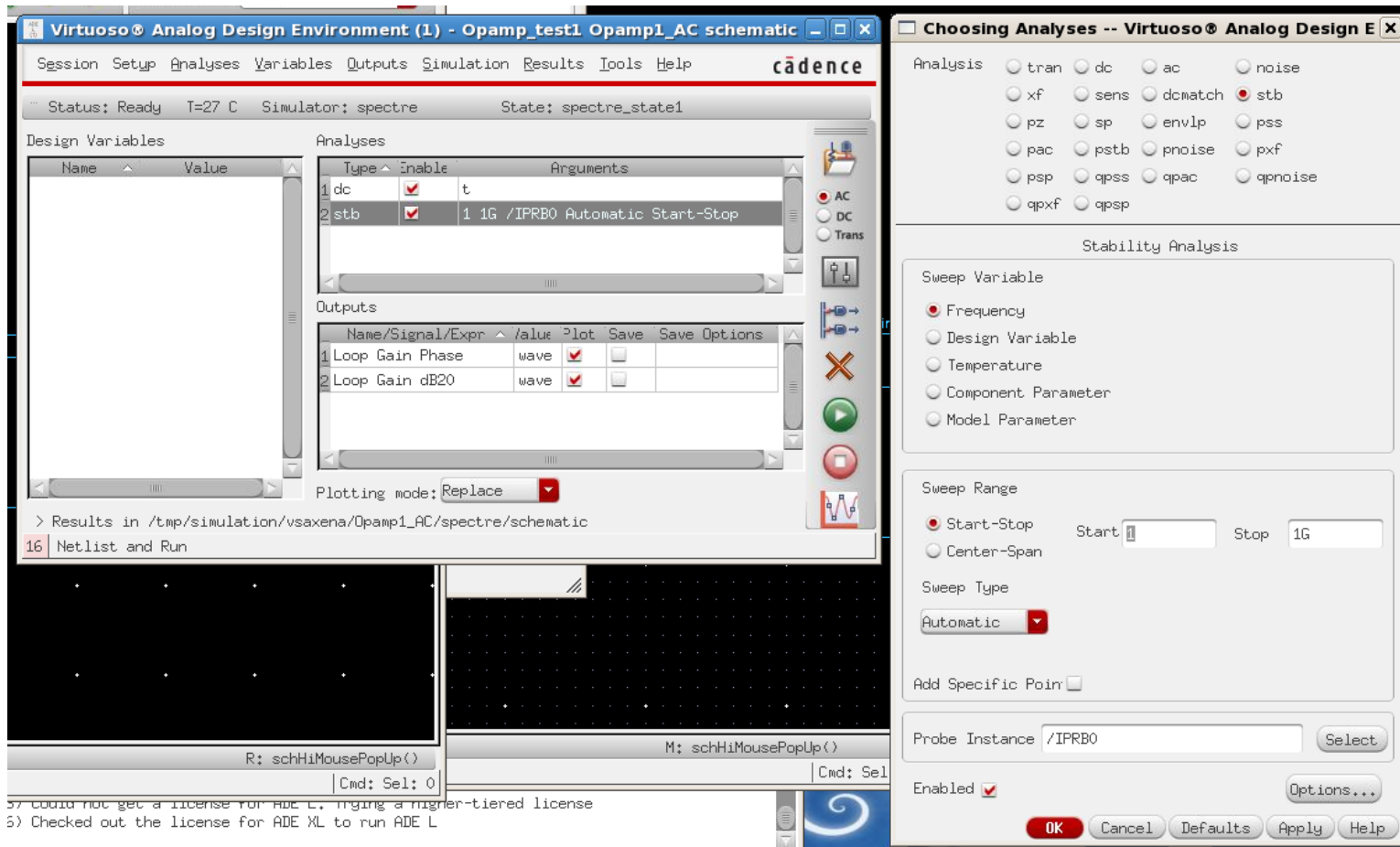


- Always have dc analysis on for debugging purpose

Bode Plot Setup

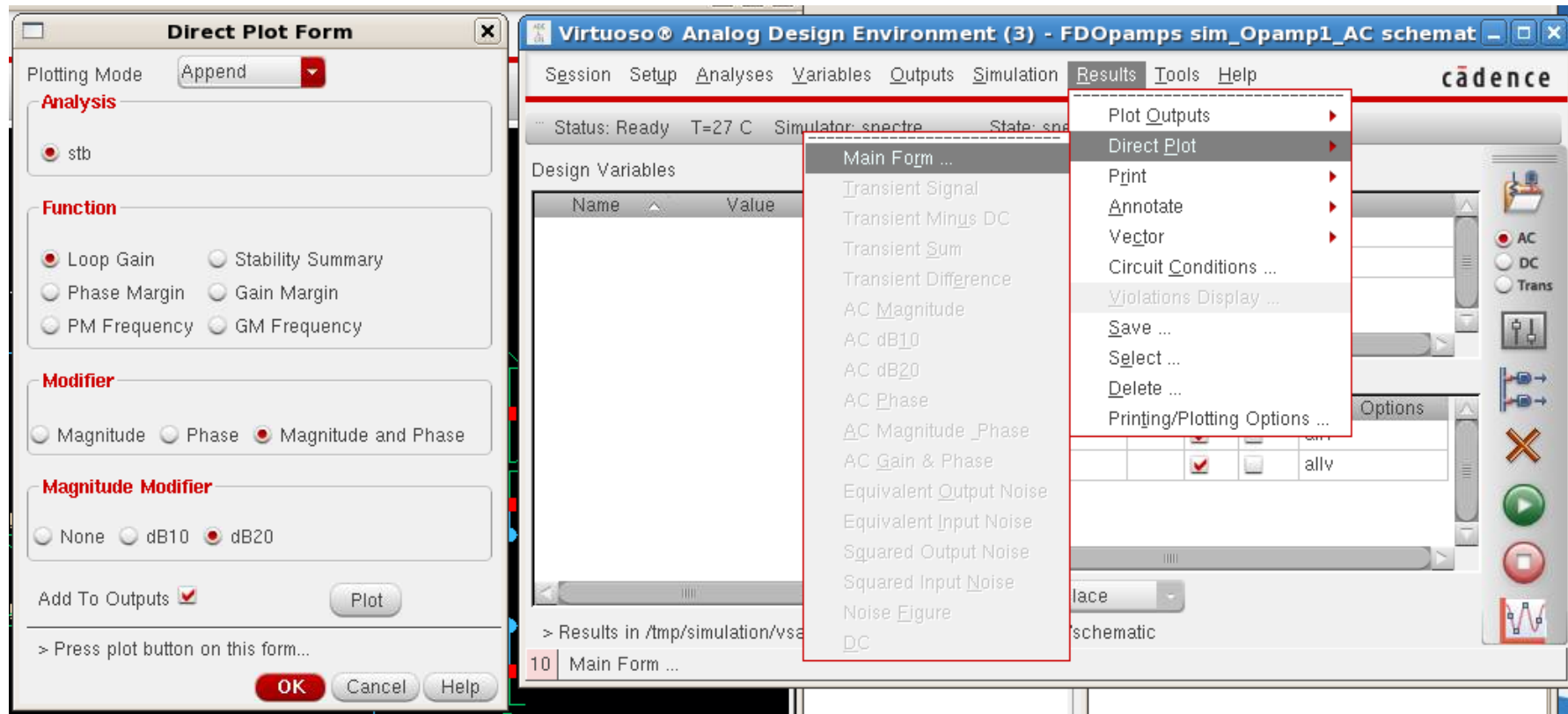

- Results → Direct Plot → Main Form

Loop Response Bode Plots

 


□ Here, $f_{un}=152.5$ MHz, $PM=41.8^\circ$

□ Try to use the stb analysis while the circuit is in the desired feedback configuration


- Break the loop with realistic DC operating points

Transient Step Response Test Bench

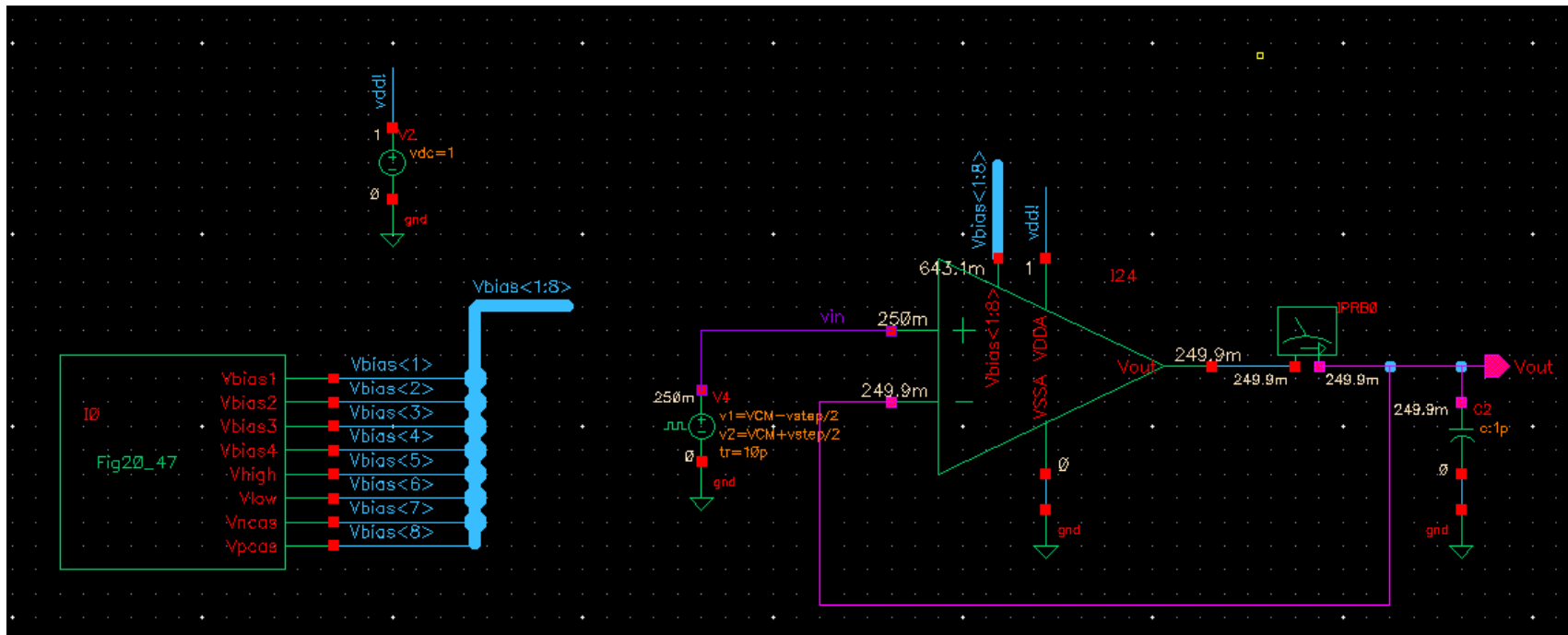


- ❑ Transient step-response verifies the closed-loop stability
- ❑ Use small as well as large steps for characterization
- ❑ iprobe acts as a short (can remove it from transient sims)

Small Step Response

 

- Observe the ringing (PM was 41°)
 - Compensate more!
 - Correlate small-step response with the open-loop frequency response for your understanding.

Large Step Response

 


- Use large steps for large signal response
 - Not captured by the small-signal analysis
 - Note the slewing in the output here



Fully-Differential Opamp Simulation

Continuous-time CMFB


CMDM Probe

 

- ❑ Located in library: [AnalogLib](#)→[cmdmprobe](#)
- ❑ Variable CMDM =
 - -1 measures differential mode response
 - +1 measures common mode response
- ❑ In IC615, [diffstbprobe](#) is available which handles unbalanced differential circuits better than the [cmdmprobe](#).
- ❑ More information on the differential probes and the STB analysis algorithm can be found in [4].


Fully Differential Circuit Analysis

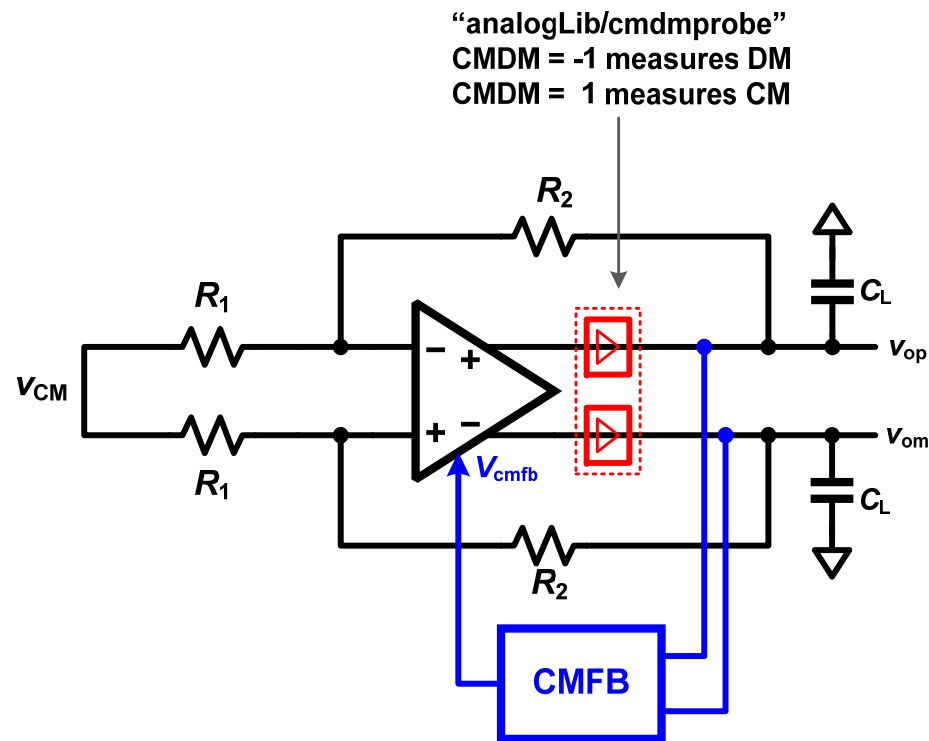- ❑ Use CMDM probe for differential analysis [1, 3]
- ❑ Placement of the CMDM probe should break the differential as well the common-mode loops.



Fully Differential Circuit Analysis Method 1

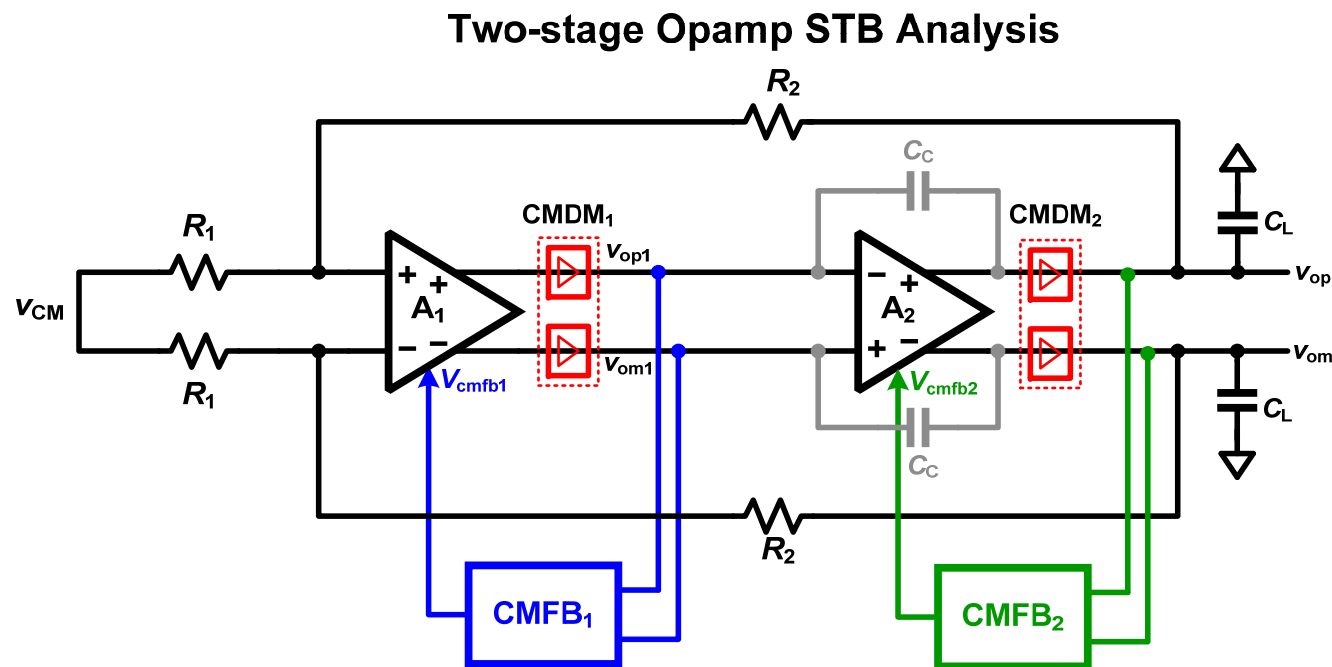
- For internal loops, isolate those loops individually and perform STB analysis
 - Ensure overall DC feedback for accurate biasing and that all loops are compensated
 - CMDM_1 measures only the first-stage CM response
 - CMDM_2 measures overall DM response and second-stage CM response




Fully Differential Circuit Analysis Method2

- cmdmprobes placed outside DM loop, only in CMFB loops
 - $CMDM_1$ measures only the first-stage CM response
 - $CMDM_2$ measures only the second-stage CM response
 - But need another CMDM probe to measure DM loop stability
 - Results match with iprobe results very well.

Two-stage Opamp STB Analysis

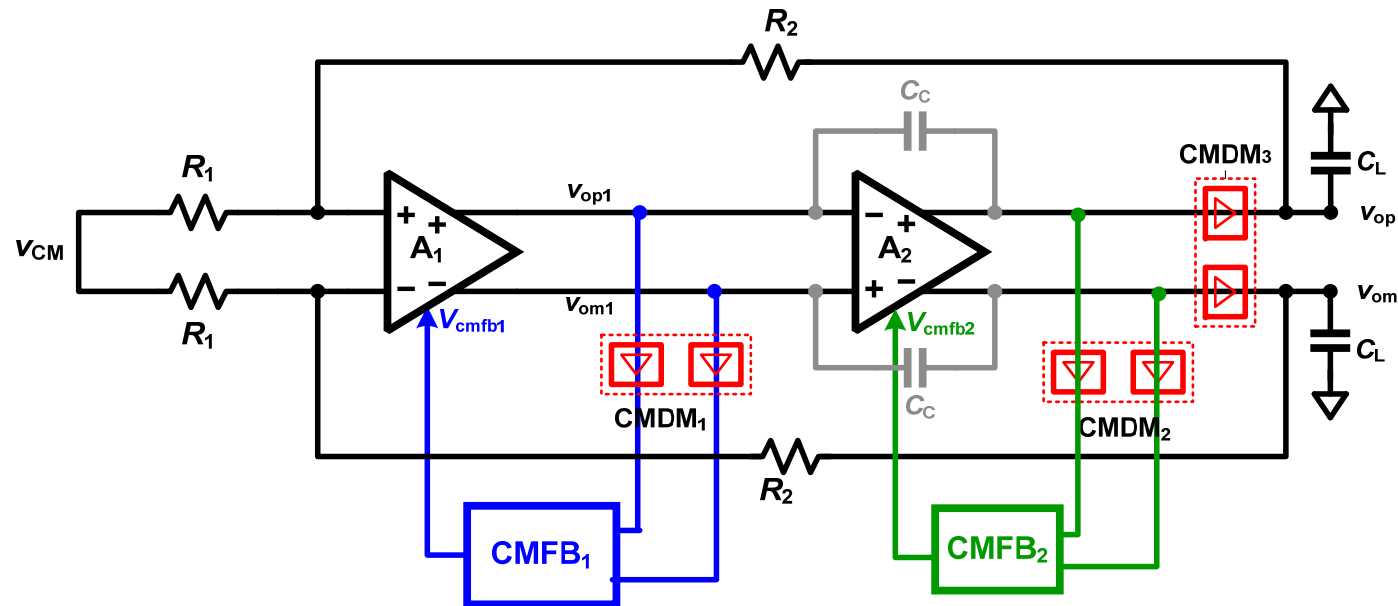


Fully Differential Opamp Schematic

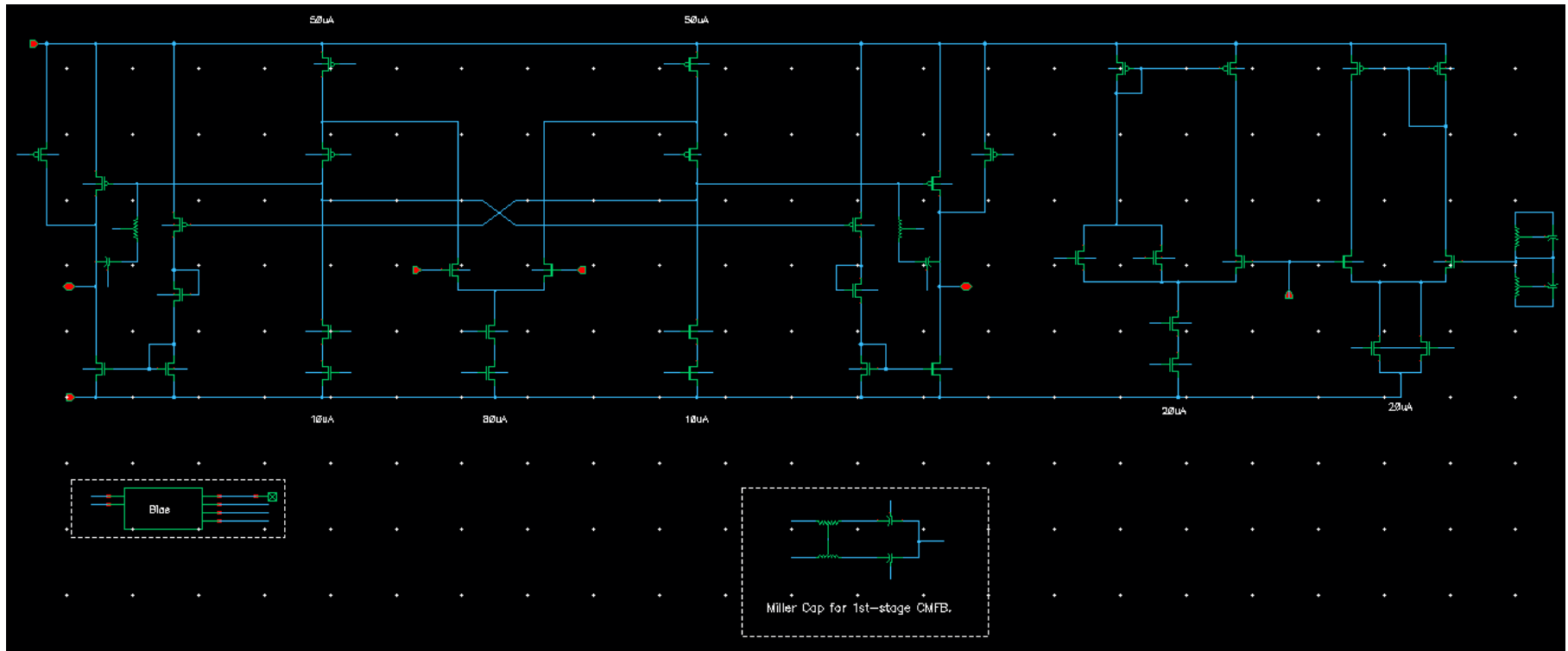


- ❑ Two-stage fully differential opamp
- ❑ Class AB output stage for large voltage swing
- ❑ With individual CMFB.
- ❑ 1st stage CMFB compensated

STB Analysis Using Method 1

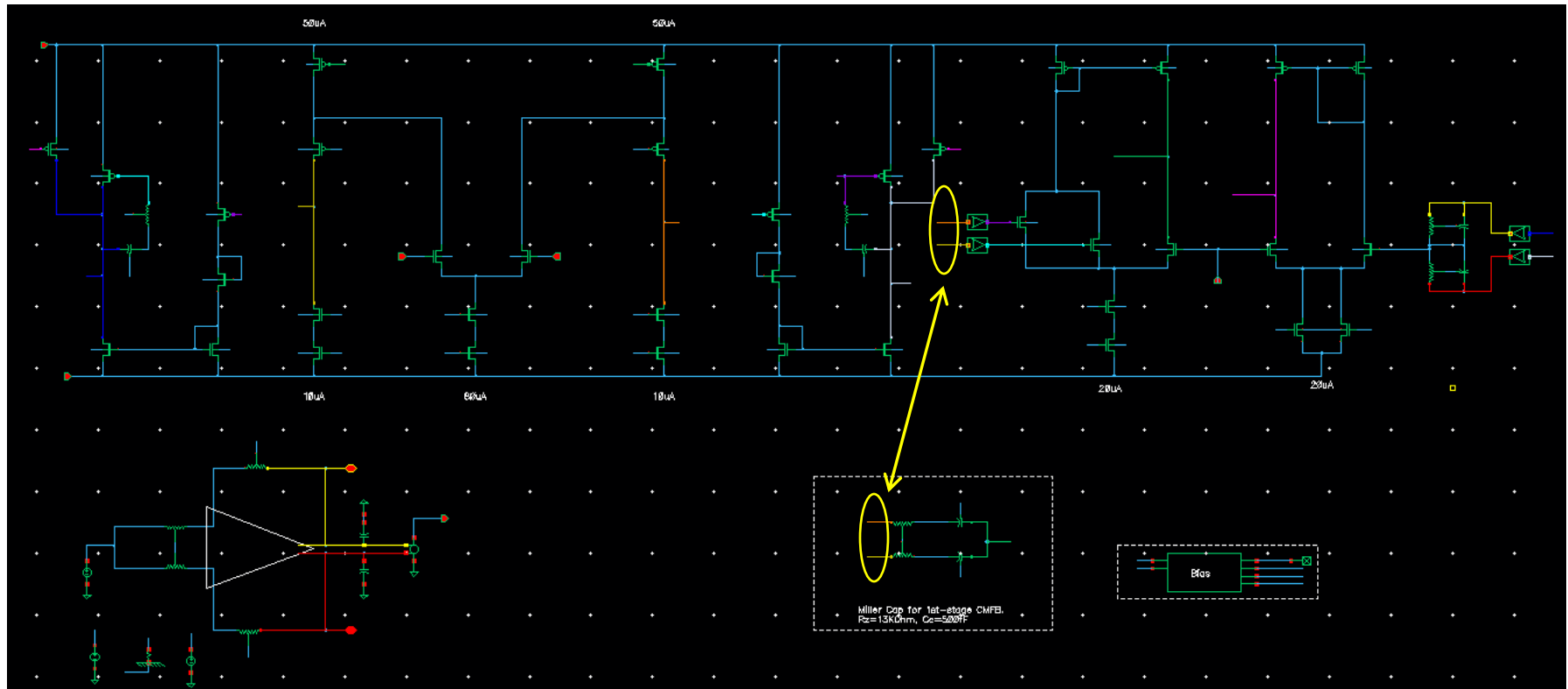


- ❑ Be noted that the nulling resistors should be connected before the inputs of cmdmprobe in the 1st CMFB loop, or it will generate incorrect results.

STB Analysis Using Method 2

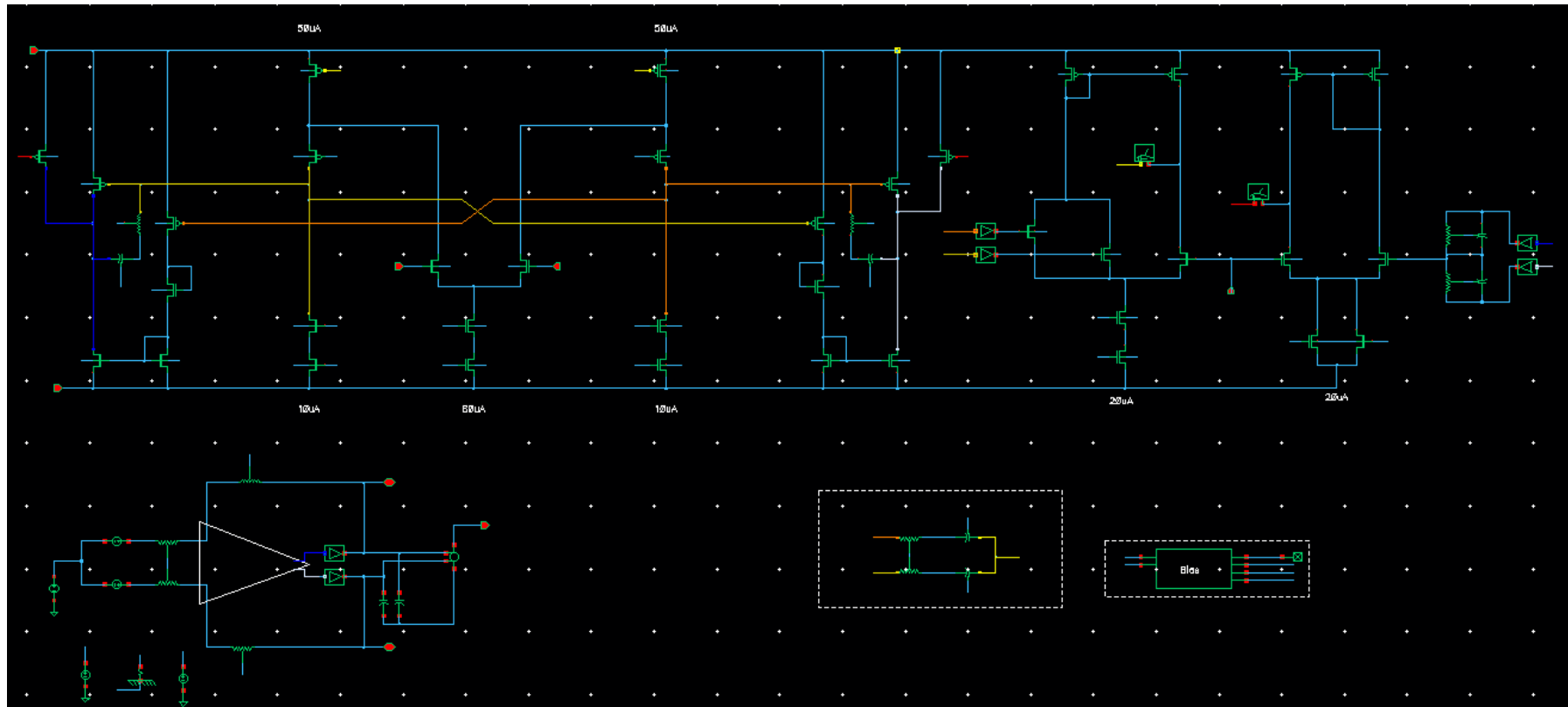

- ❑ Need one extra cmdmprobe to measure DM loop comparing to method 1.


DM Loop Bode Plots M1&M2

 

Phase margin = 65.1422 Deg at frequency = 36.1282 MHz.


- Differential Mode loop gain and phase margin plots
- Same results obtained by using Method 1 and Method 2

1st Stage CMFB Loop Bode Plots

 

Phase margin = 64.5059 Deg at frequency = 21.2729 MHz.


Method 1

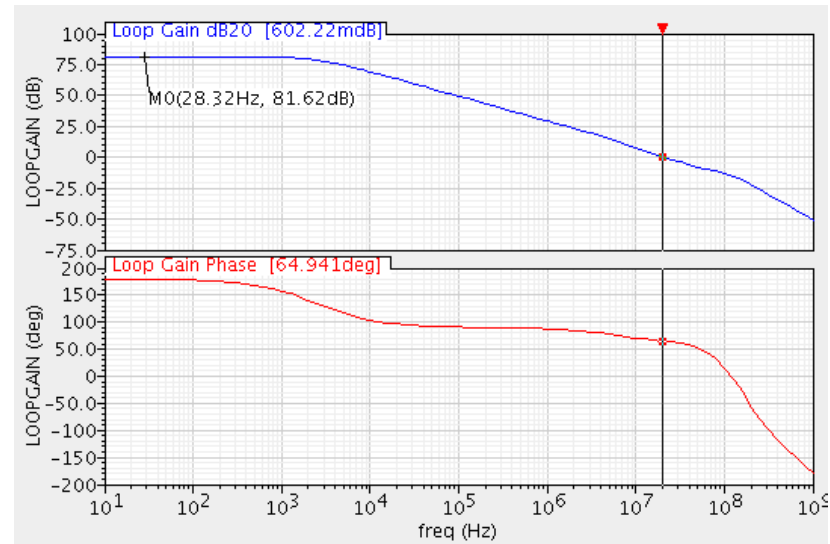

Phase margin = 64.5788 Deg at frequency = 21.2722 MHz.


Method 2

2nd Stage CMFB Loop Bode Plots

 

|Phase margin = 42.6336 Deg at frequency = 119.604 MHz.

Method 1

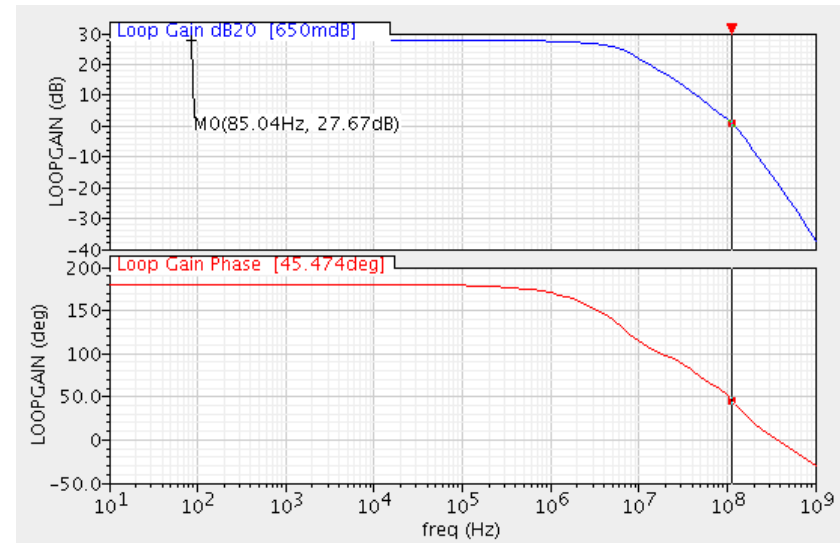

|Phase margin = 42.376 Deg at frequency = 119.867 MHz.

Method 2

Simulation Setup

The screenshot shows the Cadence Virtuoso Analog Design Environment interface. The title bar indicates the project is 'FD_Opamp_HW1_09102012 two_stageop_ClassAB_stb_s'. The menu bar includes Session, Setup, Analyses, Variables, Outputs, Simulation, Results, Tools, and Help. The status bar shows 'Status: Ready T=40.0 C Simulator: spectre State: spectre_state1'.

The 'Design Variables' table is as follows:

Name	Value
vdd	1.2

The 'Analyses' table is as follows:

Type	Enable	Arguments
dc	<input type="checkbox"/>	t
ac	<input type="checkbox"/>	10 100M 10 Logarithmic Points Per Decade Start-Stop
stb	<input checked="" type="checkbox"/>	10 1G 10 /116/vinj Logarithmic Points Per Decade Start-Stop


The 'Outputs' table is as follows:

Name/Signal/Expr	Value	Plot	Save	Save Options
Loop Gain Phase	wave	<input checked="" type="checkbox"/>	<input type="checkbox"/>	
Loop Gain dB20	wave	<input checked="" type="checkbox"/>	<input type="checkbox"/>	
Phase Margin	64.58	<input checked="" type="checkbox"/>	<input type="checkbox"/>	

The 'Plotting mode' is set to 'Replace'. The status bar at the bottom shows 'Running stb (Est. time left: 0Sec) 2%'.


- Use previous **oppt** (operating point) in the stb analysis

Bode Plot Setup

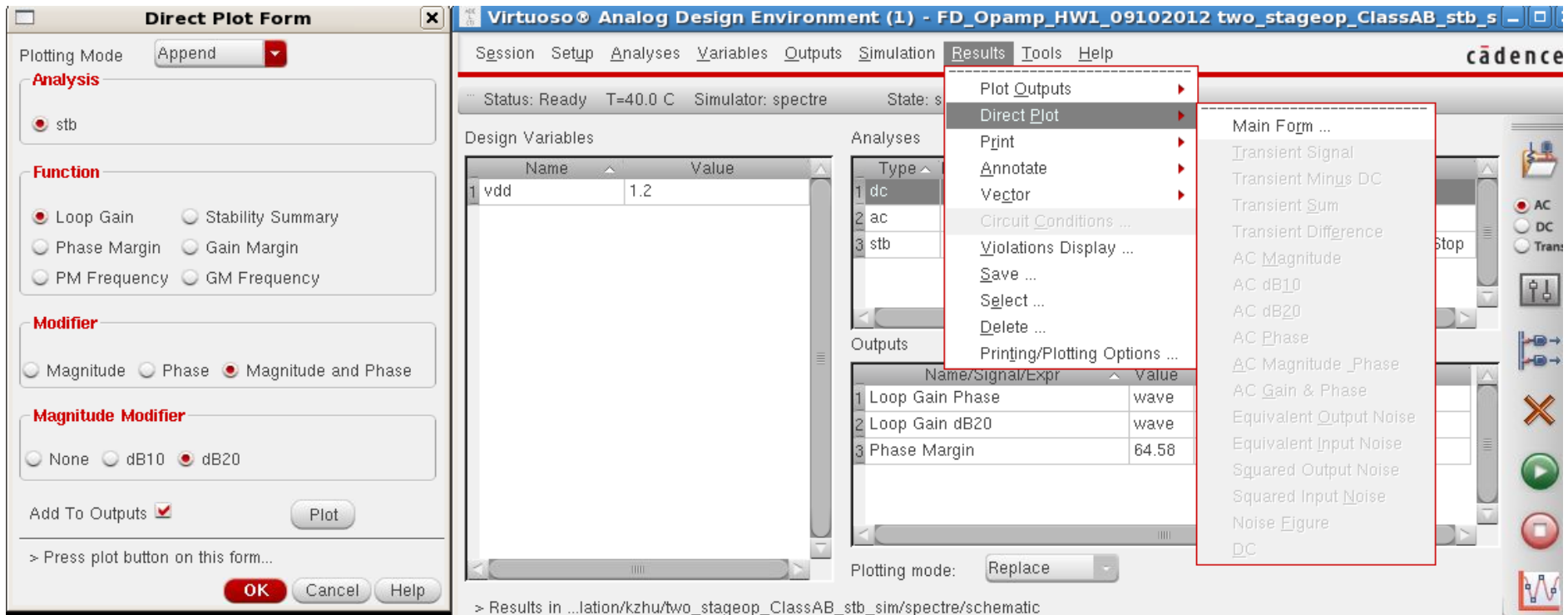


- Results → Direct Plot → Main Form

DM Transient

 

- Unity-gain inverting amplifier transient response with a 200mV differential step (rise/fall time=0.1ns, pulse width=100ns)

CM Transient

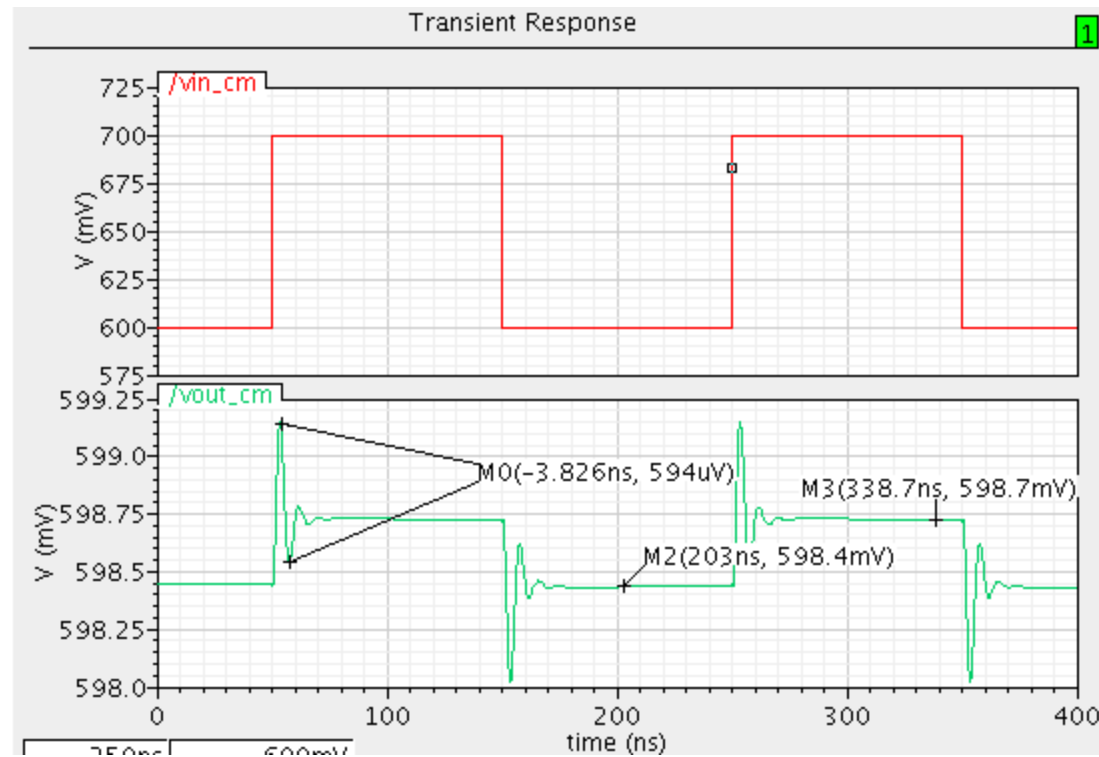



- Unity-gain inverting amplifier transient response with a 100mV common mode step (rise/fall time=0.1ns, pulse width=100ns)



Fully-Differential Opamp Simulation


Switched-capacitor CMFB

Switched Capacitor CMFB Simulation

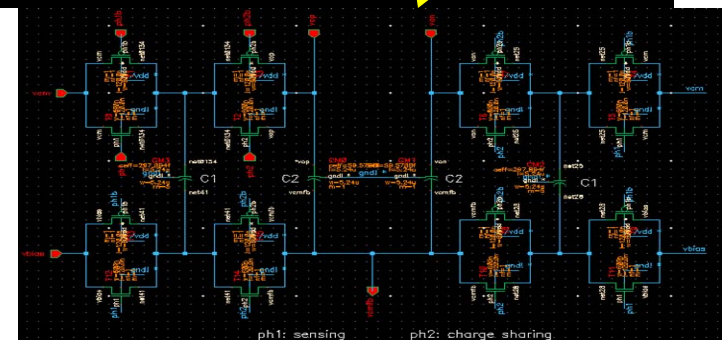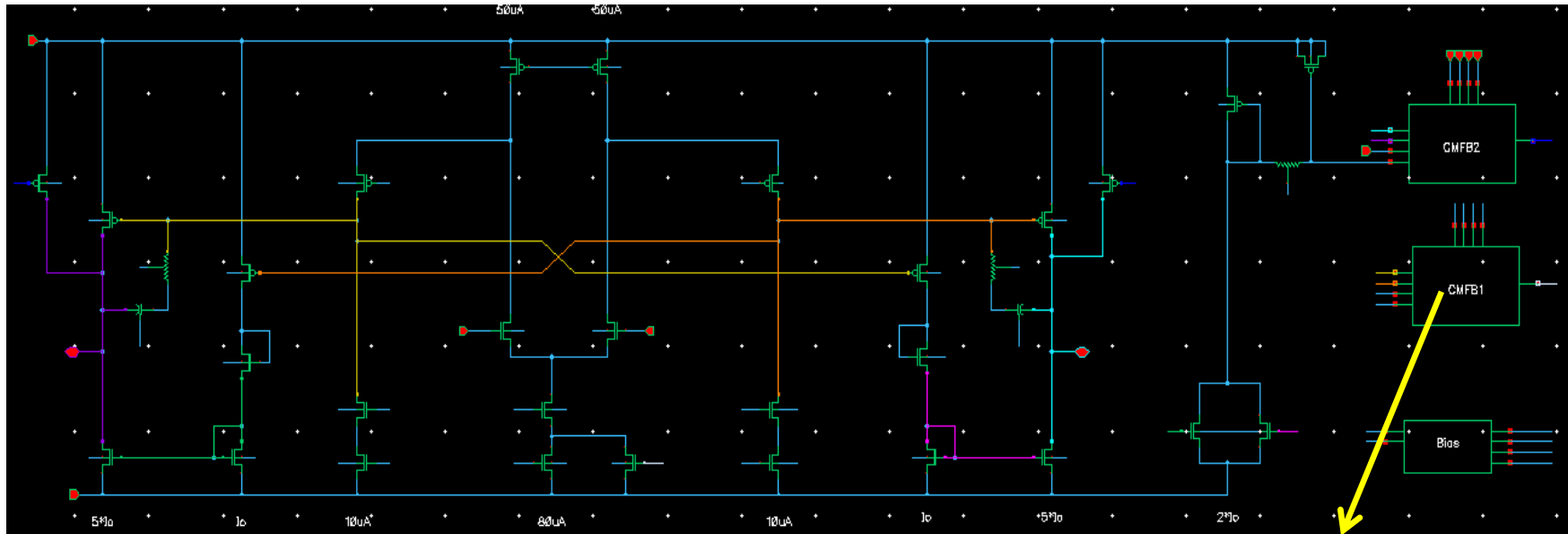

- ❑ 2-stage Class AB output Opamp
- ❑ Individual SC-CMFB

PSTB Analysis Using Method 1

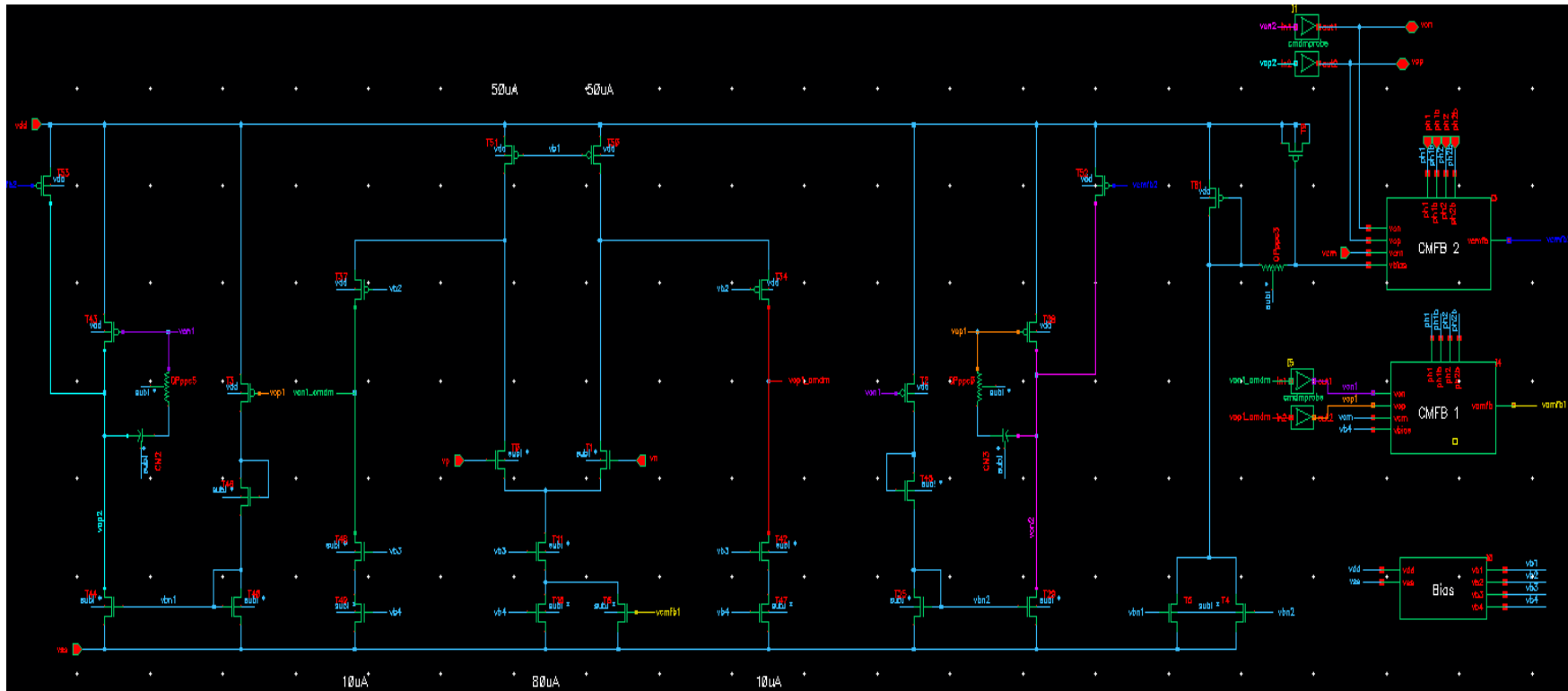

- PSTB analysis is essential for sampled circuit

Simulation Setup---PSS

The screenshot displays the 'Choosing Analyses' dialog box in the Virtuoso Analog Design Environment. The 'Analysis' section has 'pss' selected. The 'Engine' section has 'Shooting' selected. The 'Fundamental Tones' table is as follows:

#	Name	Expr	Value	Signal	SrcId
1		1/(1/Fck-0	5M	Large	v0
7		1/(1/Fck-0	5M	Large	
6		1/(1/Fck-0	5M	Large	
3		1/(1/Fck-0	5M	Large	v7


The 'Output harmonics' section shows 'Number of harmonics' set to 0. The 'Accuracy Defaults' section has 'moderate' selected. The 'Additional Time for Stabilization (tstab)' is set to 1u. The 'Save Initial Transient Results (saveinit)' is set to 'yes'. The 'Enabled' checkbox is checked.

The main window shows the 'Analyses' table with 'pss' and 'dc' selected:

Type	Enable	Arguments
1 pstb	<input checked="" type="checkbox"/>	10 200M 10 /I2/I1/vinj
2 pss	<input checked="" type="checkbox"/>	5M 0
3 dc	<input type="checkbox"/>	t
4 tran	<input type="checkbox"/>	0 1u conservative


- ❑ We can only set the number of harmonics to 0 by choosing Shooting method
- ❑ tstab parameter can be obtained by tran analysis first

PSS Accuracy suggestions

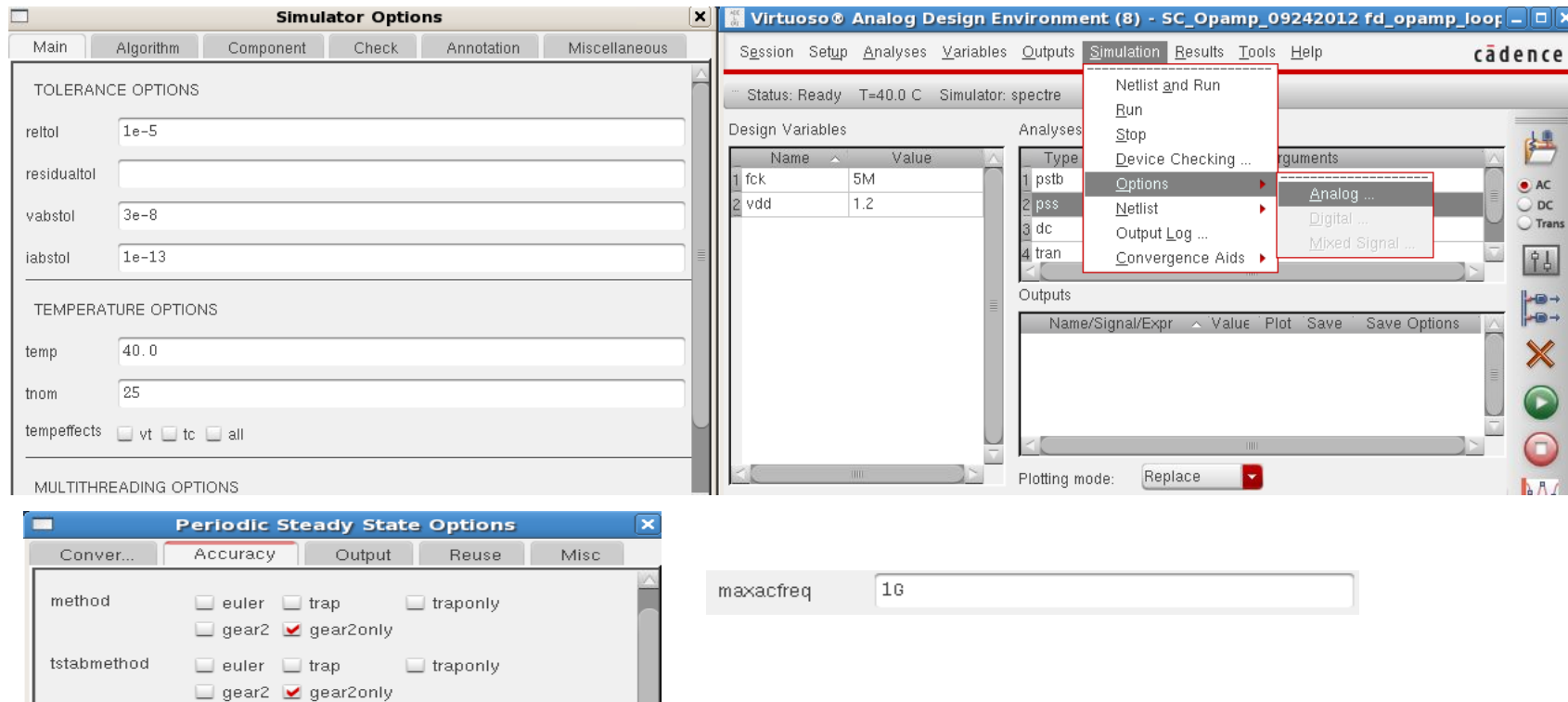

- ❑ Go to Simulation → Options → Analog → Main in the ADE window to setup tolerance options accordingly. If the frequency of periodic small signal analyses followed by PSS is high (e.g. 1G), the *maxacfreq* parameter (options → accuracy) of the PSS can be used to specify the highest frequency, otherwise, the frequency analysis in PAC maybe truncated.

PSS Time Plot

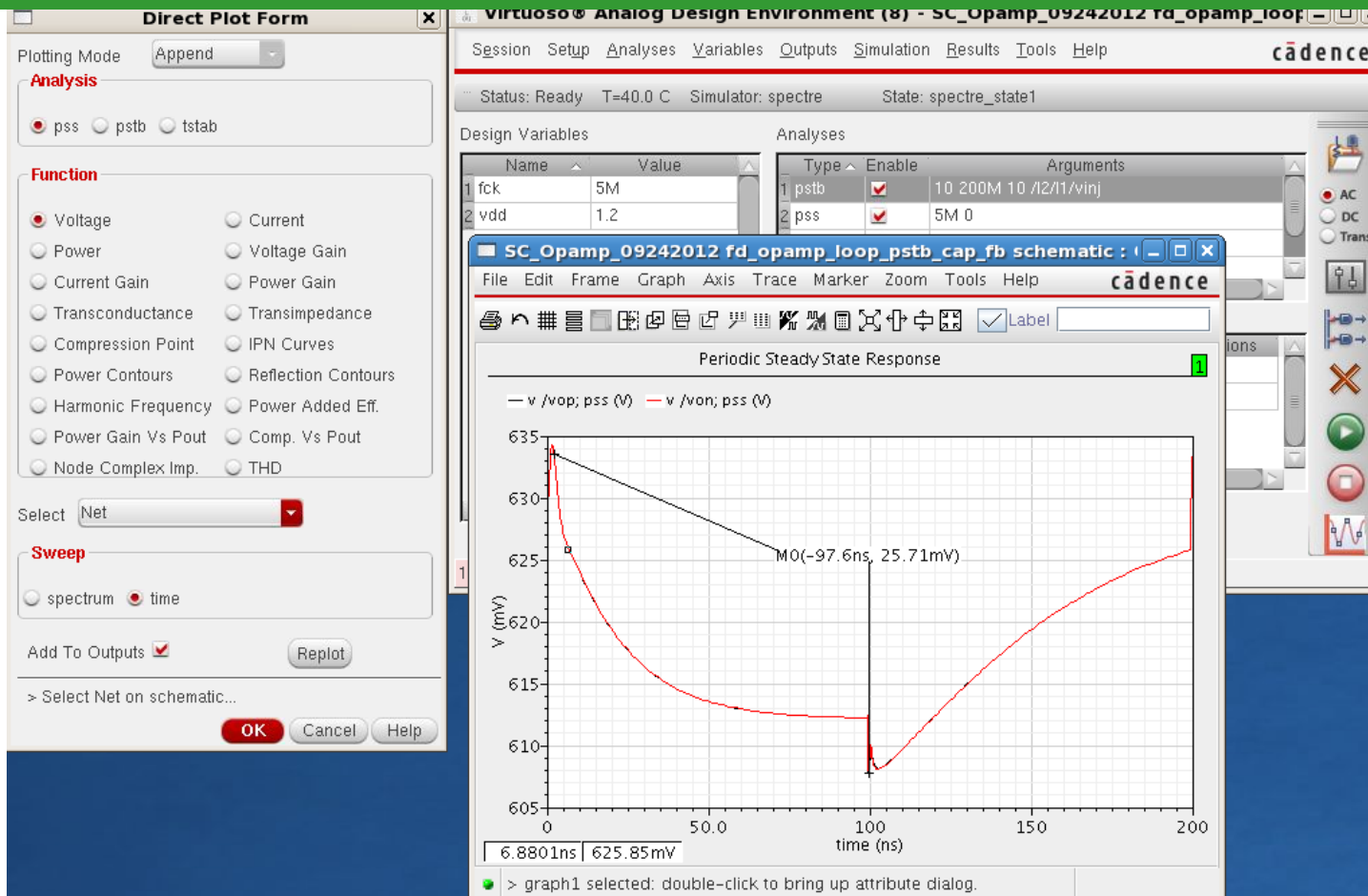

- ❑ Results → Direct Plot → Main Form
- ❑ X-axis scale range is 1/sampling clock frequency

PSTB Setup

Choosing Analyses -- Virtuoso® Analog Design E

Analysis

- tran
- dc
- ac
- noise
- xf
- sens
- dcmatch
- stb
- pz
- sp
- envlp
- pss
- pac
- pstb
- pnoise
- pxf
- psp
- qpss
- qpac
- qpnoise
- qpxf
- qpsp

Periodic Stability Analysis

PSS Beat Frequency (Hz)

Periodic Stability Analysis Notification

Start-Stop

Sweep Type

Logarithmic Points Per Decade

Number of Steps

Add Specific Points

Probe Instance

Enabled

Virtuoso® Analog Design Environment (8) - SC_Opamp_09242012 fd_opamp_loo

Session Setup Analyses Variables Outputs Simulation Results Tools Help

Status: Ready T=40.0 C Simulator: spectre State: spectre_state1

Design Variables

Name	Value
1 fck	5M
2 vdd	1.2

Analyses

Type	Enable	Arguments
1 pstb	<input checked="" type="checkbox"/>	10 200M 10 /I2/I1/vinj
2 pss	<input checked="" type="checkbox"/>	5M 0
3 dc	<input type="checkbox"/>	t
4 tran	<input type="checkbox"/>	0 1u conservative

Outputs

Name/Signal/Expr	Value	Plot	Save	Save Options
------------------	-------	------	------	--------------


Plotting mode:

> Results in ...mulation/kzhu/fd_opamp_loop_pstab_cap_fb/spectre/schematic

139 Options


- ❑ PSTB is always followed by PSS

PSTB Plot

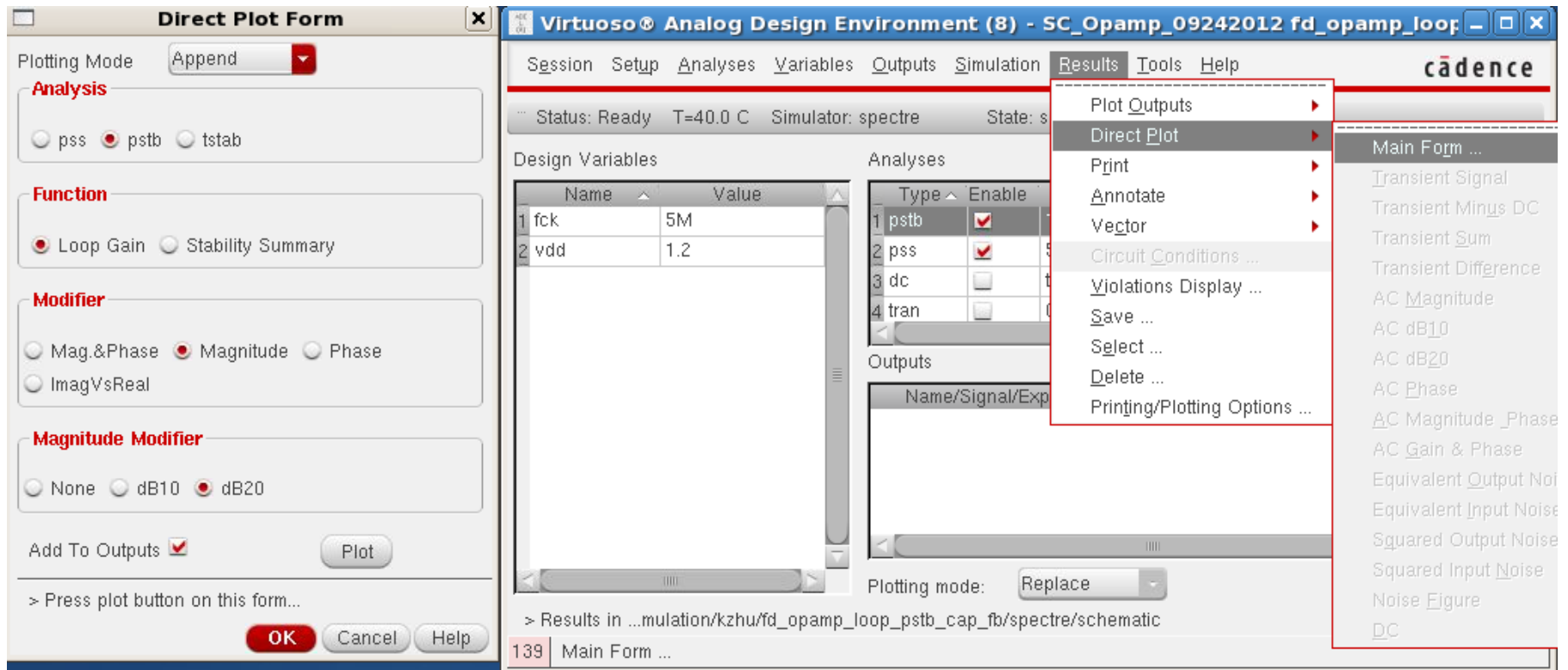


□ Results → Direct Plot → Main Form

DM Loop Bode Plots

 

Phase margin = 67.0107 Deg at frequency = 48.633 MHz.


Resistive feedback

 

Phase margin = 64.0631 Deg at frequency = 125.724 MHz.


Capacitive feedback

1st Stage CMFB Loop Bode Plots

 

Phase margin = 79.0094 Deg at frequency = 5.36771 MHz.


Resistive feedback

 

Phase margin = 84.622 Deg at frequency = 6.17596 MHz.


Capacitive feedback

2nd Stage CMFB Loop Bode Plots

 

|Phase margin = 139.738 Deg at frequency = 3.73402 MHz.

Resistive feedback

 


Phase margin = 158.414 Deg at frequency = 1.51941 MHz.

Capacitive feedback

Summary of pstb analysis


Application	Items	DC Gain (dB)	PM (°)	GBW (MHz)
Sample hold	1 st stage CMFB	45.9	84.6	6.1
	2 nd stage CMFB	1.31	158.4	1.5
	DM loop	62.9	64.1	125
Resistive feedback	1 st stage CMFB	46.1	79	5.3
	2 nd stage CMFB	4.1	139.7	3.7
	DM loop	63	67	48.6

Resistive Feedback DM Transient

 


- Unity-gain inverting amplifier transient response with a 200mV differential step (rise/fall time=0.1ns, pulse width=200ns)

Resistive Feedback CM Transient

 


- Unity-gain inverting amplifier transient response with a 100mV common mode step (rise/fall time=0.1ns, pulse width=200ns)

Sample-Hold Configuration

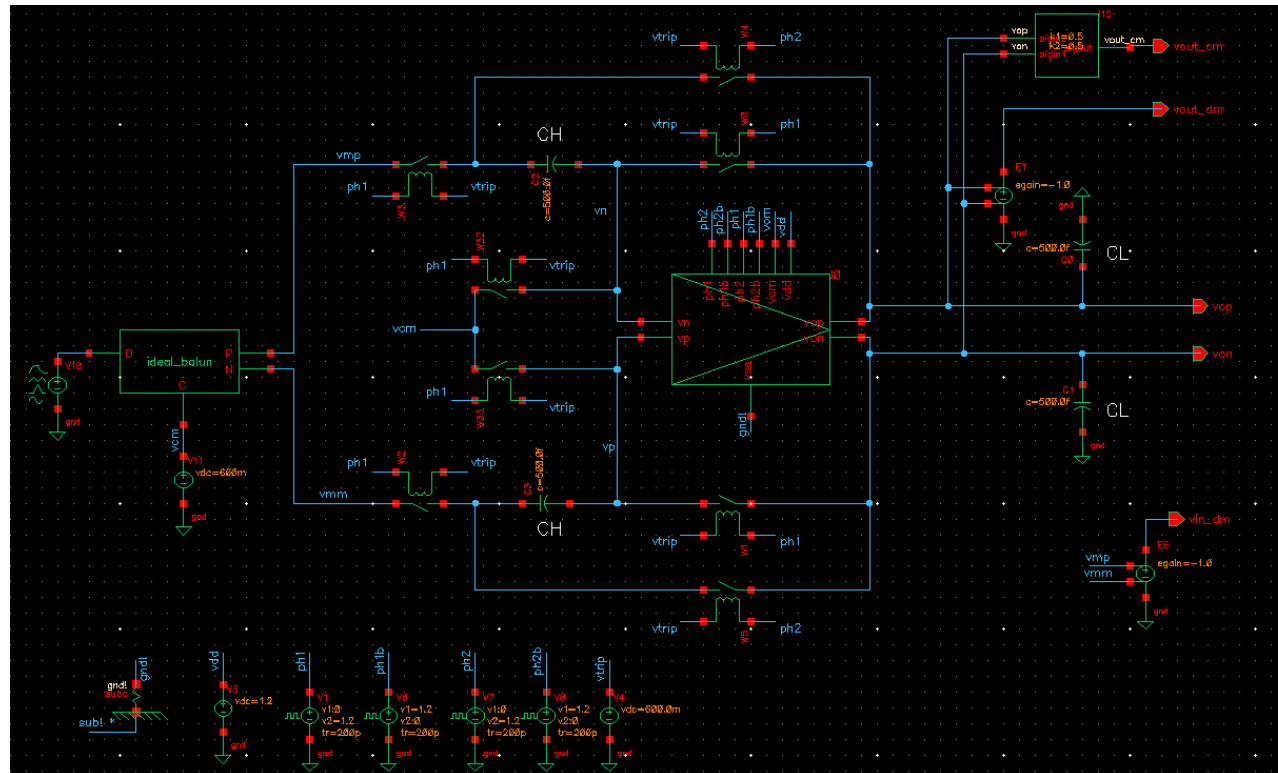


- ❑ Ideal switches with on resistance of $1\text{k}\Omega$

Sample-Hold Transient Response

 

- **DM and CM outputs waveforms when $f_{in}=1/4$ MHz, $f_s=5$ MHz**

Sample-Hold Transient Response

 

- **DM and CM outputs waveforms when $f_{in}=11/4$ MHz, $f_s=5$ MHz**

References

- [1] Spectre User Simulation Guide, pages 160-165
- [2] M. Tian, V. Viswanathan, J. Hangtan, K. Kundert, “Striving for Small-Signal Stability: Loop-based and Device-based Algorithms for Stability Analysis of Linear Analog Circuits in the Frequency Domain,” Circuits and Devices, Jan 2001.
- [3] P. R. Gray, P. J. Hurst, S. H. Lewis, R. G. Meyer, “Analog and Design of Analog Integrated Circuits,” 4th Ed., Wiley, 2010.
- [4] F. Wiedmann, “Loop gain simulation,” Online:
<https://sites.google.com/site/frankwiedmann/loopgain>