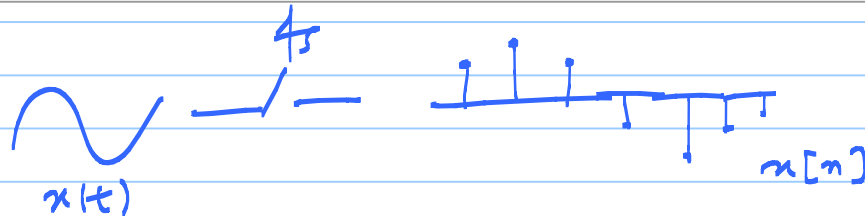


# ECE 614 - Lecture 10

Note Title

9/27/2012




\* PSS

$\Rightarrow f_s = 100 \text{ MHz}, 10 \text{ ns}$


STB  
 $\hookrightarrow A_c$

PSTB  $\rightarrow$  break the loop using CDM probe

PAC

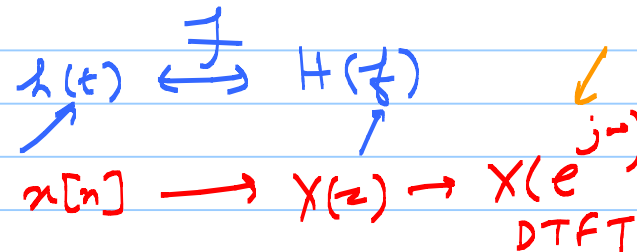

## Behavioral modeling

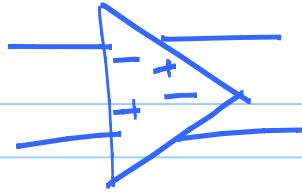


Macromodel





(VCCS  
VCVS)

Verilog-A

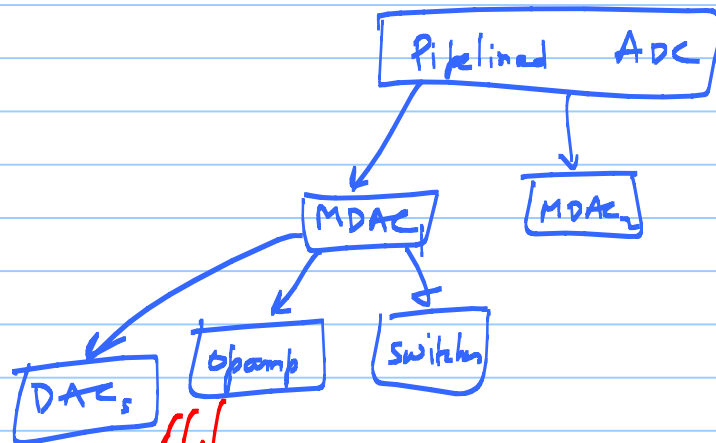\* Config view → switch subcircuit schematic views



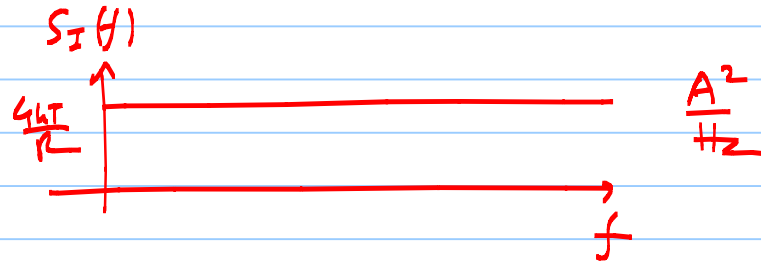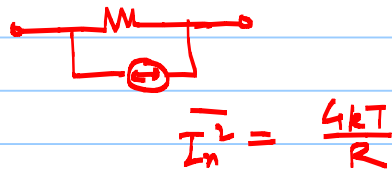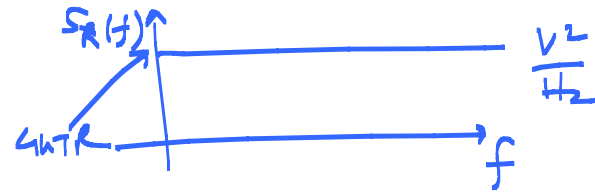
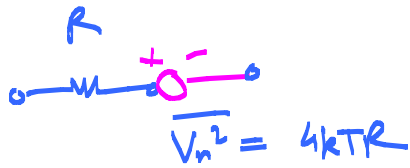
Transistor-level  
behavioral  
Verilog-A  
Schematic VL



long-channel MOSFET

$\Rightarrow$   $I_n$  saturation

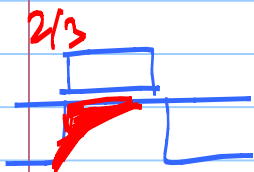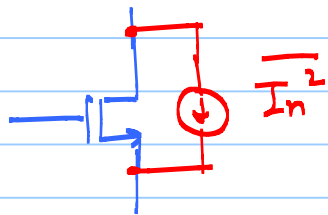$\overline{I_n^2} \Rightarrow$  thermal noise  
current contributed  
by the channel




$$\overline{I_n^2} = 4KT \gamma \underline{\underline{g_m}}$$

$\rightarrow \underline{\underline{\frac{2}{3}}}$  for long-channel




$\Rightarrow \underline{\underline{2.5}}$  for a submicron  
process

has a dependence on  $V_{DS}$




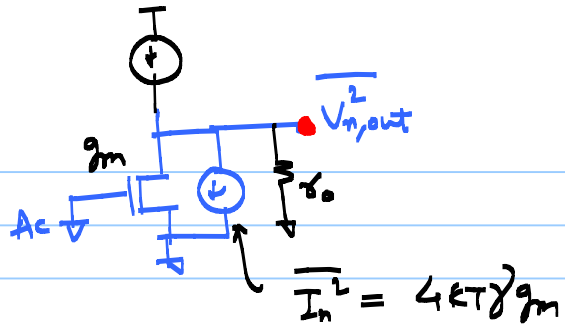


$$\begin{aligned}
 \overline{V_{n,out}^2} &= \overline{I_n^2} \cdot r_o^2 \\
 &= 4kT\gamma g_m r_o^2 \\
 &= \frac{8}{3} kT \underline{\underline{g_m}} r_o^2
 \end{aligned}$$

$g_m \downarrow$

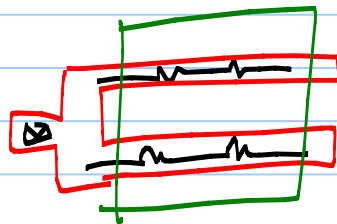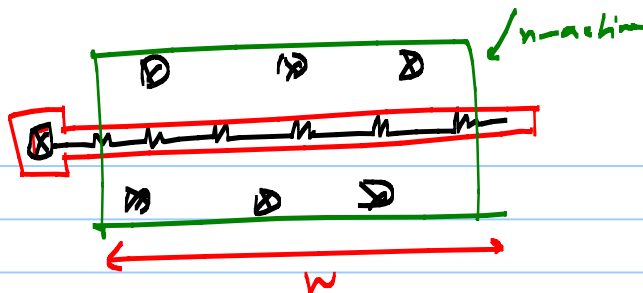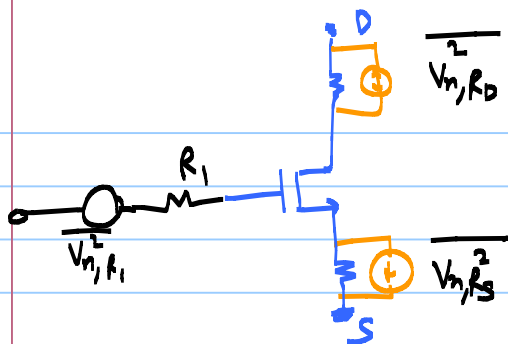

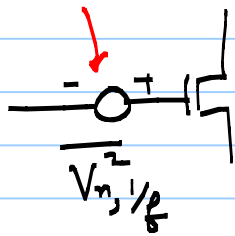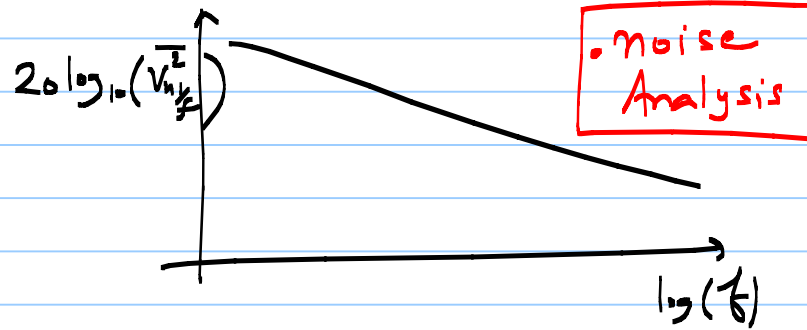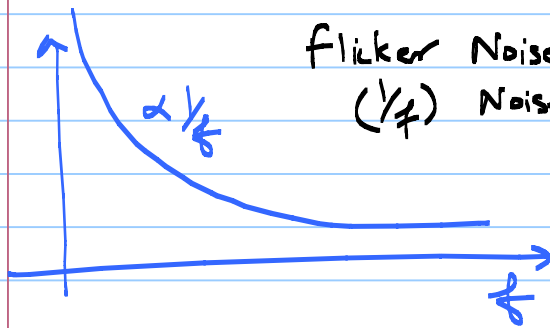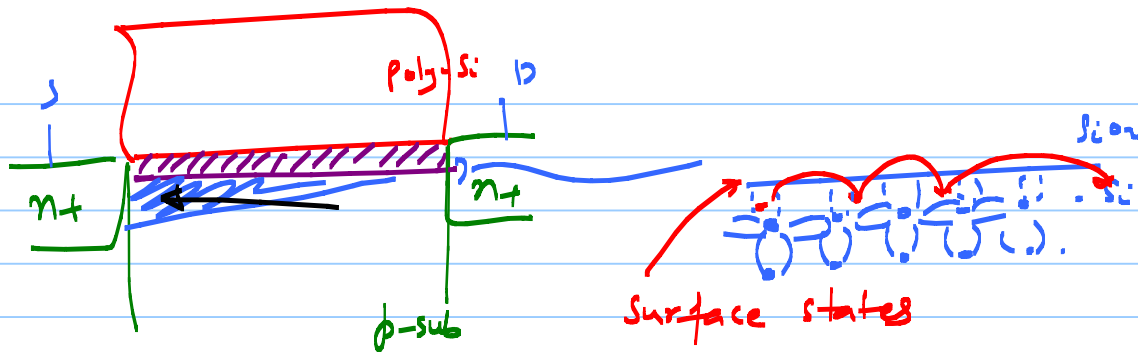
Use multi finger  
layout for  
Large  $w$



$$\overline{V_{n,1/f}^2} = \frac{k}{C_{ox} W L} \cdot \frac{1}{f} \propto \frac{1}{\text{Area}} \cdot \frac{1}{f}$$

\* for PMOS due to the buried channel  
the flicker noise is smaller

$$K_p < K_n$$

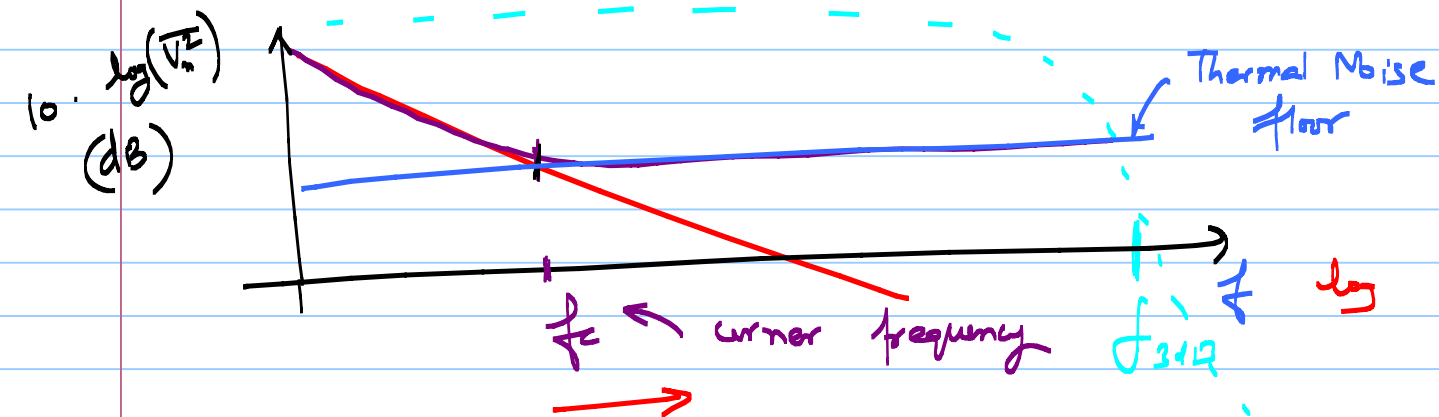


$$\overline{I_n^2} = 4kT \left( \frac{2}{3} g_m \right) = \frac{k}{C_{ox} W L} \cdot \frac{1}{f_c} \cdot g_m^2$$



$$\Rightarrow f_c = \frac{\frac{k}{C_{ox} W L} \cdot g_m^2}{\frac{3}{8kT}}$$

Sub/ $\mu$ m CMOS
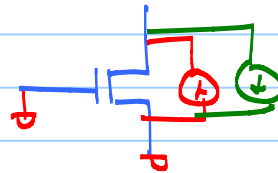
$$\Rightarrow \underline{500\text{K} \rightarrow 1\text{MHz}}$$




Total Output Noise

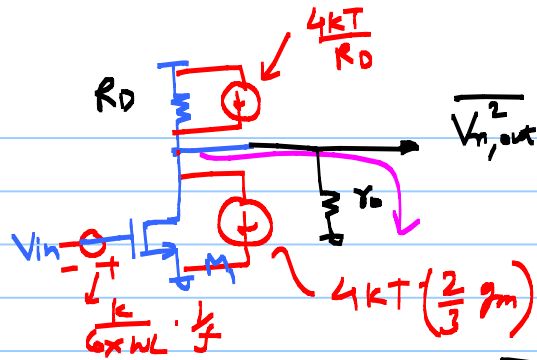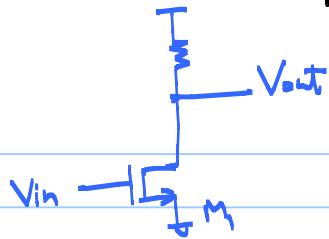




$$i_d = g_m V_{gs}$$

$$R_D \ll r_o$$
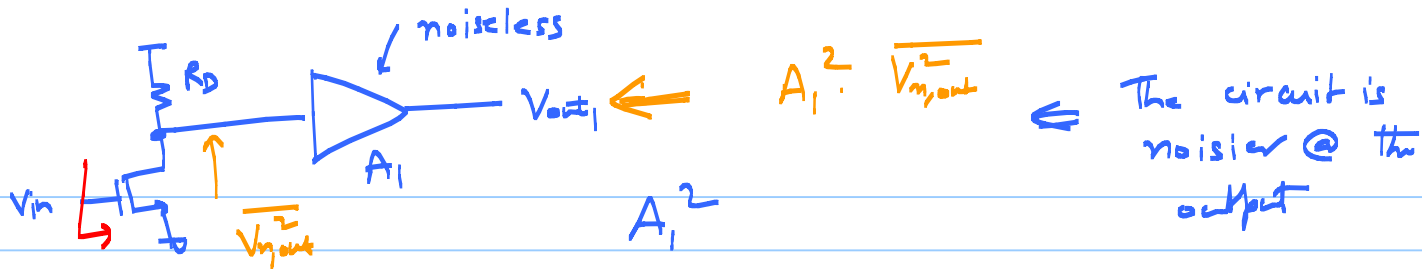
$$\underline{\underline{\overline{V_{n,out}^2}}} = \left[ \underbrace{4kT \left( \frac{2}{3} g_m \right)}_{\overline{I_{n1}^2}} + \underbrace{\frac{K_N}{C_{ox} W L} \cdot \frac{1}{f} g_m^2}_{g_m^2 \cdot \overline{V_{n1,f}^2}} + \underbrace{\frac{4kT}{R_D}}_{\overline{I_{n2}^2}} \right] \cdot R_D^2$$



SNR  $\leftarrow$  remains the same

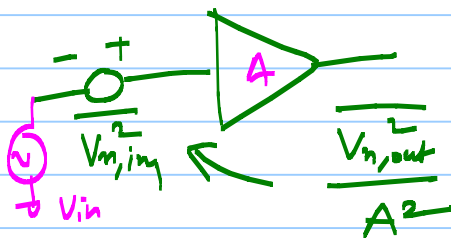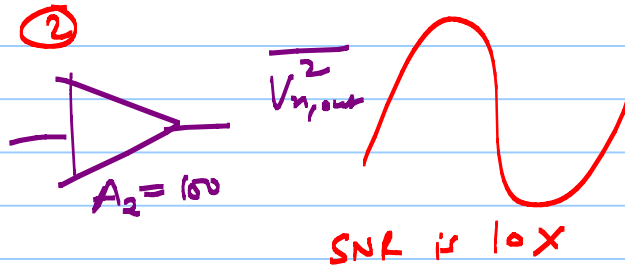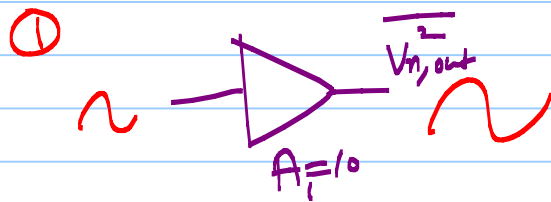

SNR =  $10 \cdot \log_{10} \left( \frac{\left( \frac{V_p}{\sqrt{2}} \right)^2}{\overline{V_{n,in}^2}} \right) = 20 \cdot \log_{10} \left( \frac{\frac{V_p}{\sqrt{2}}}{\overline{V_{n,in}}}$


input referred noise  $\nearrow$

$V_p$

Input-referred Noise

$$\overline{V_{n,in}^2} = \frac{\overline{V_{n,out}^2}}{A_v^2}$$

↑  
fictitious quantity

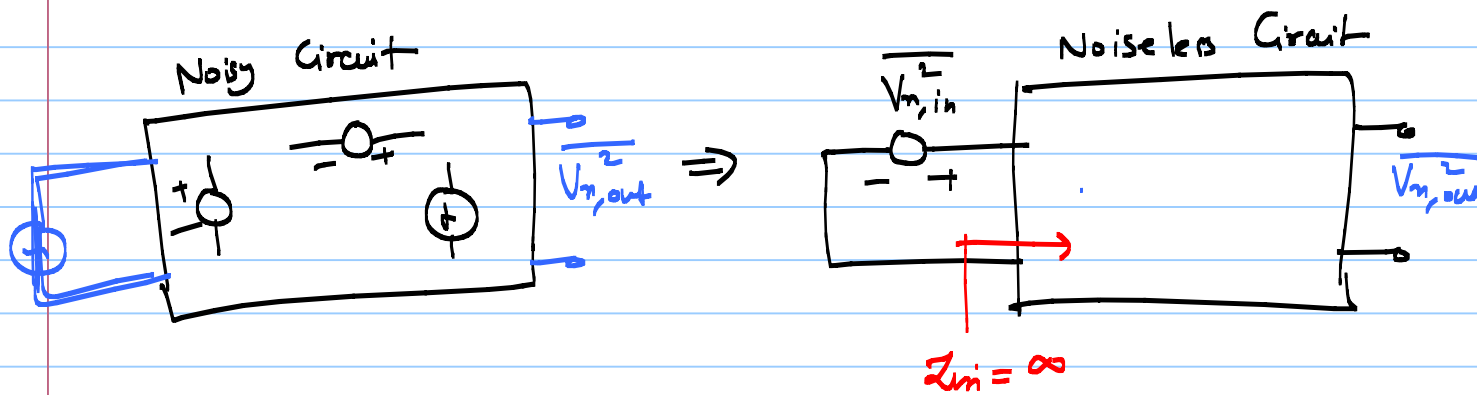

\* Necessary and sufficient representation of any linear 2-port circuit

