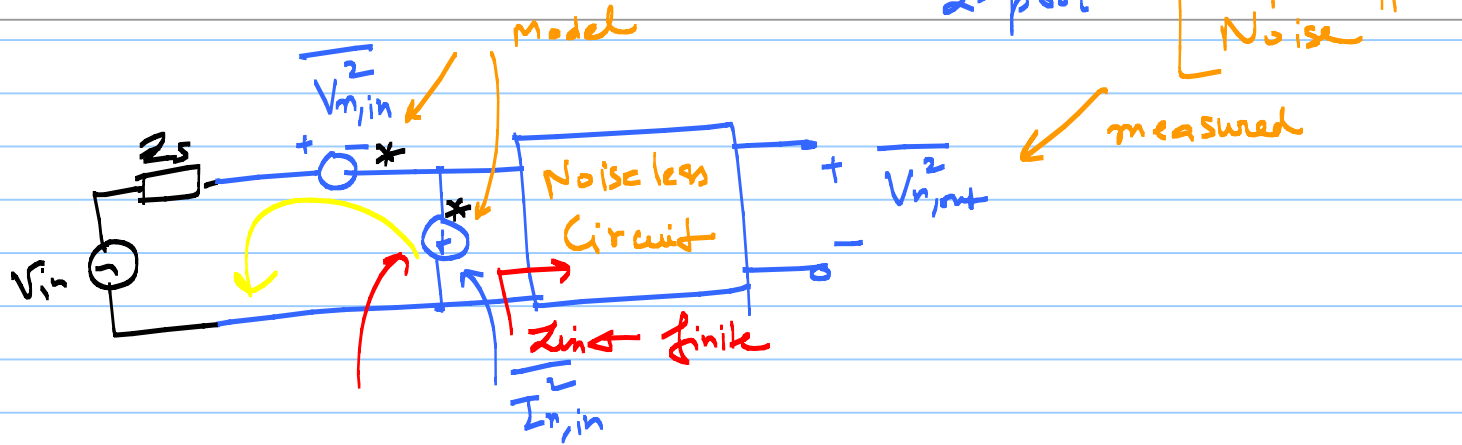



ECE 614 - Lecture 11

Note Title

10/2/2012





Lemma

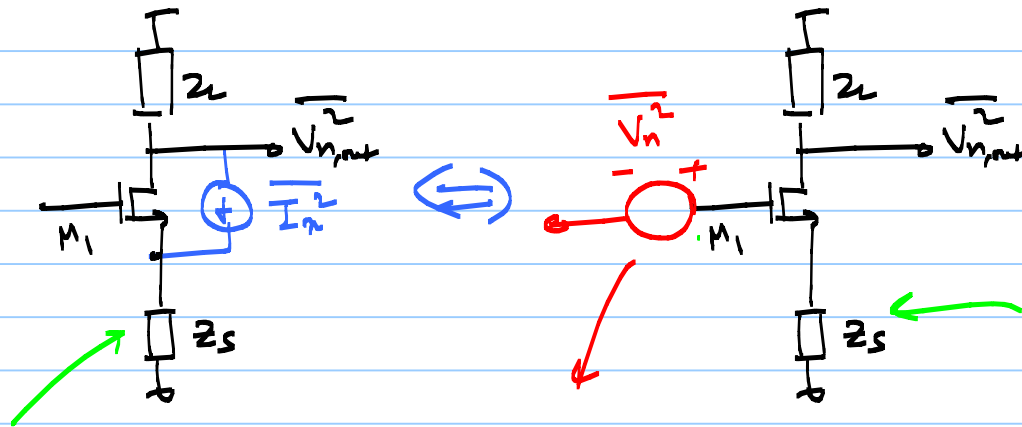

$$\overline{V_n^2} = \frac{\overline{I_n^2}}{g_m^2}$$

x can do this transposition of the noise source irrespective of z_S .

CS Amplifier

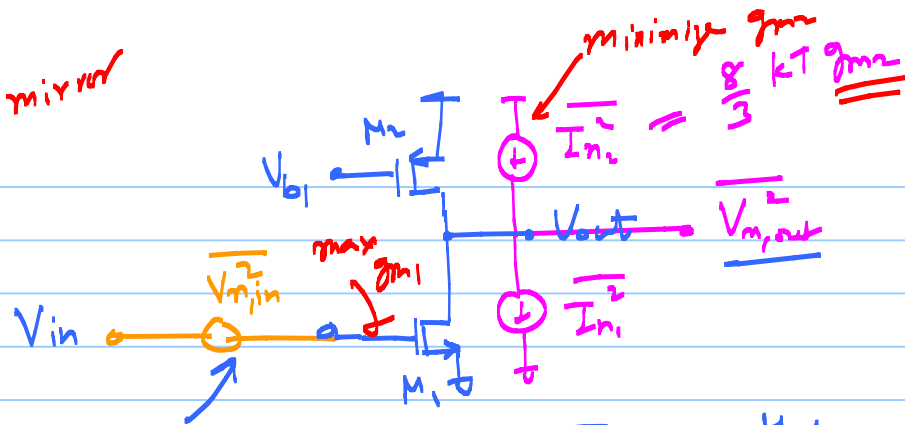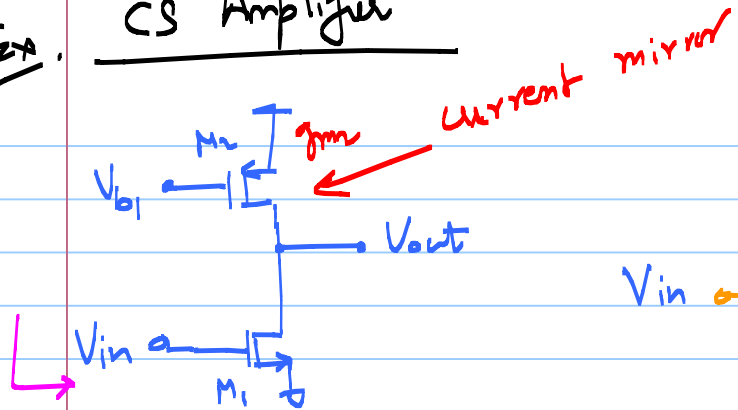

$$\begin{aligned} \overline{V_{n,out}^2} &= (\overline{I_{n1}^2} + \overline{I_{n2}^2}) \cdot (\overline{r_{o1}} \parallel \overline{r_{o2}})^2 \leftarrow \text{Total output Thermal noise voltage} \\ &= 4kT \left(\frac{2}{3}g_{m1} + \frac{2}{3}g_{m2} \right) \cdot (\overline{r_{o1}} \parallel \overline{r_{o2}})^2 \end{aligned}$$


$$\overline{V_{n,in}^2} = \frac{\overline{V_{n,out}^2}}{A_v^2} = \frac{4kT \left(\frac{2}{3}g_{m1} + \frac{2}{3}g_{m2} \right) \cdot (\overline{r_{o1}} \parallel \overline{r_{o2}})^2}{g_{m1}^2 \cdot (\overline{r_{o1}} \parallel \overline{r_{o2}})^2}$$

$$\boxed{\overline{V_{n,in}^2} = 4kT \left(\frac{2}{3g_{m1}} + \frac{2}{3} \frac{g_{m2}}{g_{m1}^2} \right)}$$



$$\frac{V^2}{Hz}$$

To minimize $\overline{V_{n,in}^2}$ $\Rightarrow g_{m1} \uparrow$
 $\Rightarrow g_{m2} \downarrow$
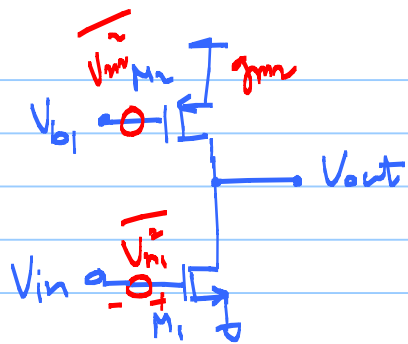
$$\overline{V_{n1}^2} \cdot \frac{1}{f} = \frac{K_n}{C_{ox}(WL)_1} \cdot \frac{1}{f}$$



* Input referred $1/f$ noise?

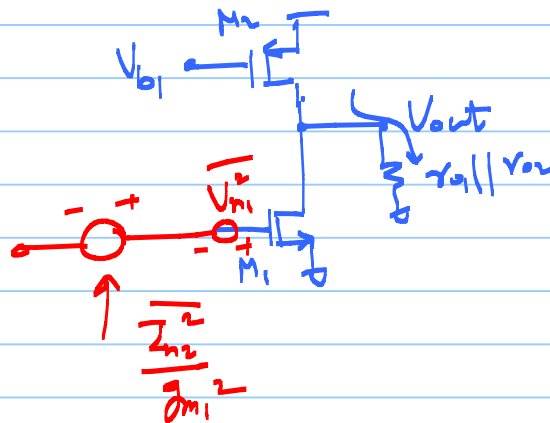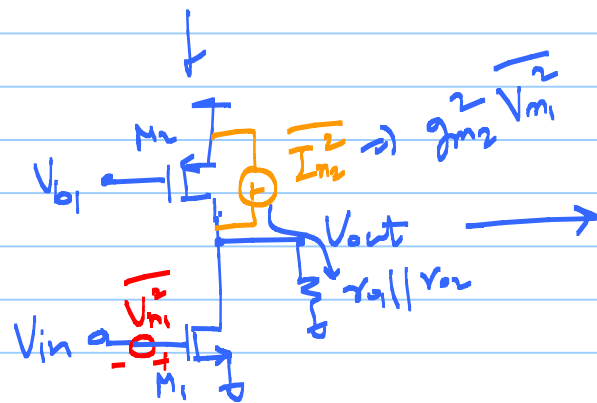

$$\overline{V_{n,in}^2} = \underbrace{4kT \cdot \frac{2}{3} \left(\frac{1}{g_{m1}} + \frac{g_{m2}}{g_{m1}^2} \right)}_{\text{Thermal Noise}} + \underbrace{\frac{K_n}{C_{ox}(WL)_1} \frac{1}{f} + \frac{K_p}{C_{ox}(WL)_2} \frac{1}{f} \cdot \frac{g_{m2}^2}{g_{m1}^2}}_{1/f \text{ noise}}$$

$$g_m = \begin{cases} \beta V_{ov}, & I_D = \text{const} \\ \frac{2I_D}{V_{ov}}, & \beta = \text{const} \\ \sqrt{2\beta I_D}, & V_{ov} = \text{const} \end{cases}$$


$\Rightarrow$ Reduce $1/f$ noise $\Rightarrow$

$$g_{m1} \uparrow, g_{m2} \downarrow$$

$(WL) \uparrow$ with $\left(\frac{W}{L}\right)$ same


$\uparrow$ increase device Area

$BW \downarrow$

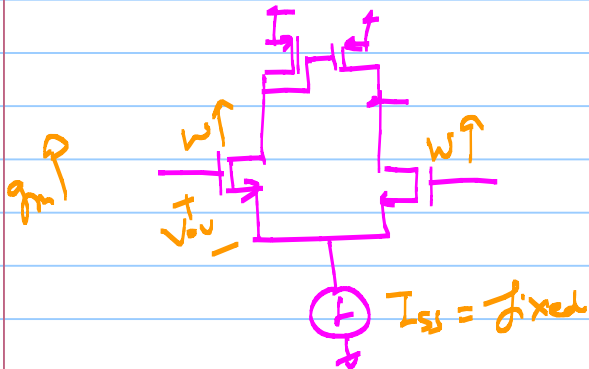

* Use PMOS input if process has lower $1/f$ noise for same W & L .


Common-gate:

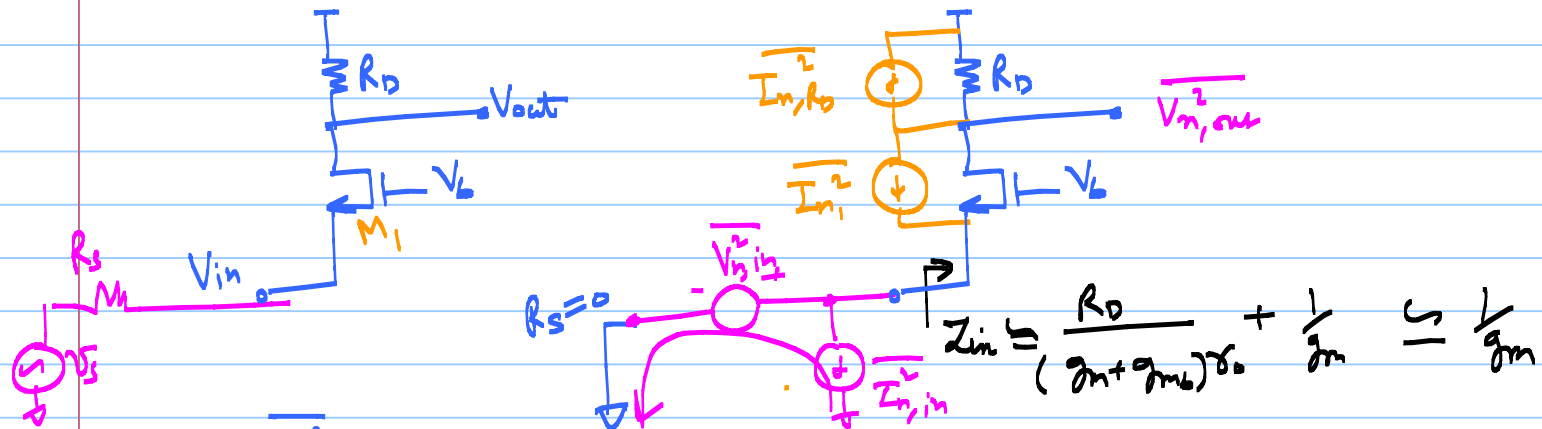

Find $V_{n,in}^2$: $\Rightarrow$ Short the input

$$Z_{in} \approx \frac{R_D}{(g_m + g_{m6})\beta_0} + \frac{1}{g_m} \approx \frac{1}{g_m}$$

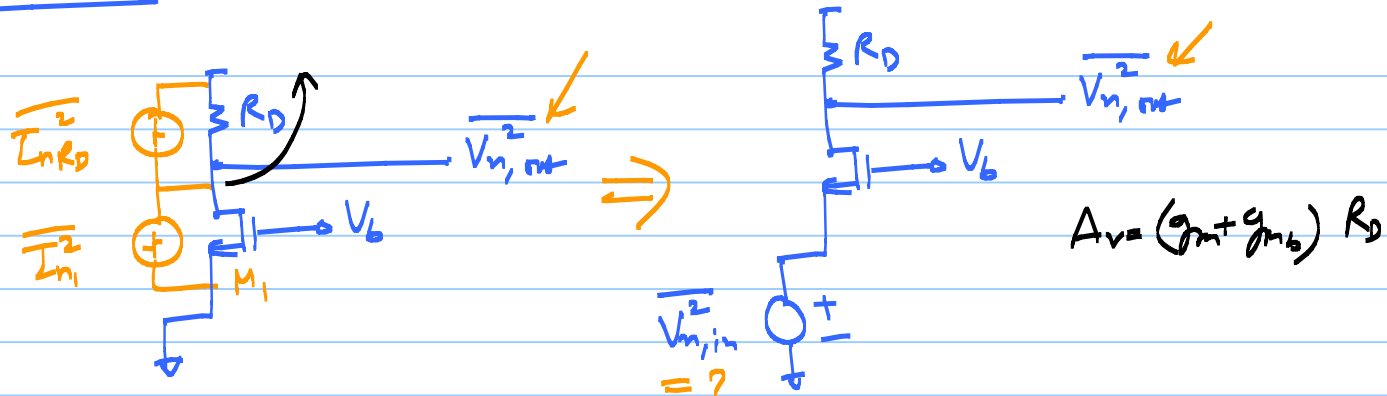
① Find $\overline{V_{n,in}^2}$: $\Rightarrow$ Short the input



$$\overline{V_{n,out}^2} = \left(\frac{8}{3} kT g_m + \frac{4kT}{R_D} \right) R_D^2 \Leftrightarrow \overline{V_{n,out}^2} = \underline{\underline{V_{n,in}^2}} \cdot (g_m + g_{mb})^2 R_D^2$$


$$\underline{\underline{V_{n,in}^2}} = \frac{4kT \left(\frac{2}{3} g_m + \frac{1}{R_D} \right)}{(g_m + g_{mb})^2}$$

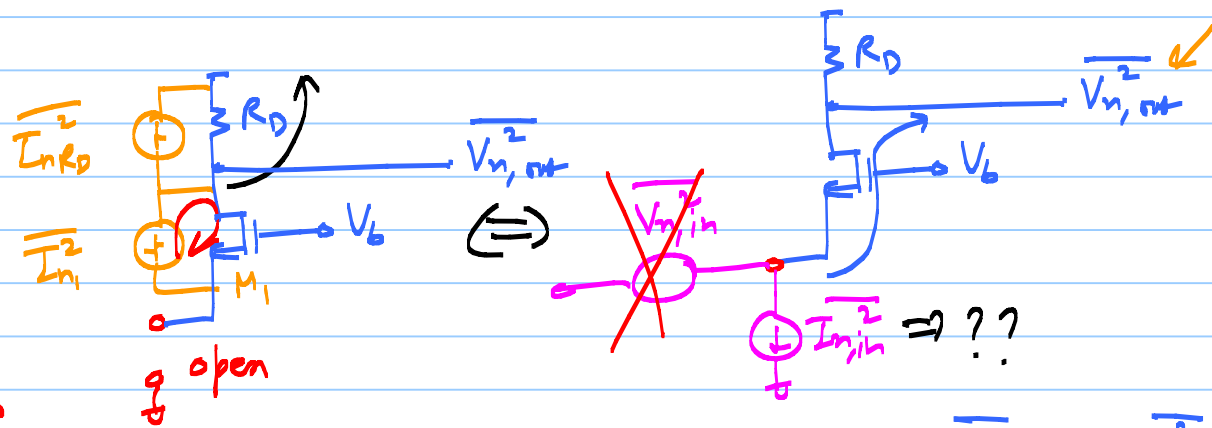② find $\overline{I_{n,in}^2}$: open the input ($R_s \rightarrow \infty$)



$\lambda \rightarrow 0$
 $r_{o,i} \rightarrow \infty$

g open

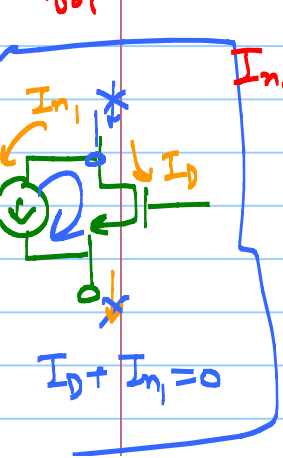


I_n doesn't flow through R_D
 $\Rightarrow$ has no effect on the output

$$\overline{V_{n,out}^2} = 4kT R_D$$


$$\overline{V_{n,out}^2} = \overline{I_{n,in}^2} \cdot R_D^2$$
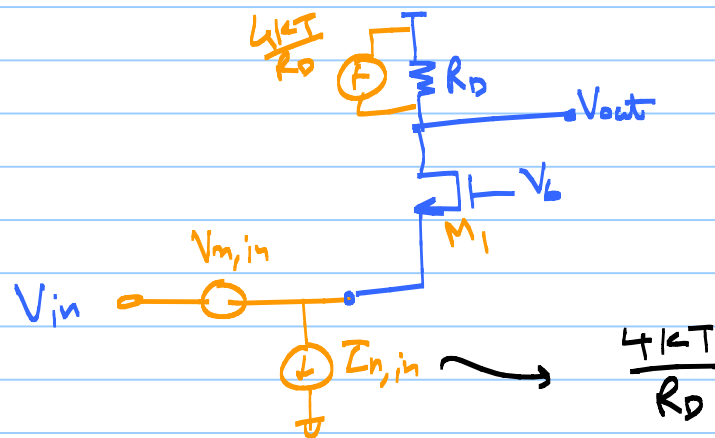
$$\overline{I_{n,in}^2} = \frac{4kT}{R_D}$$




R_D 's noise current is referred to the input

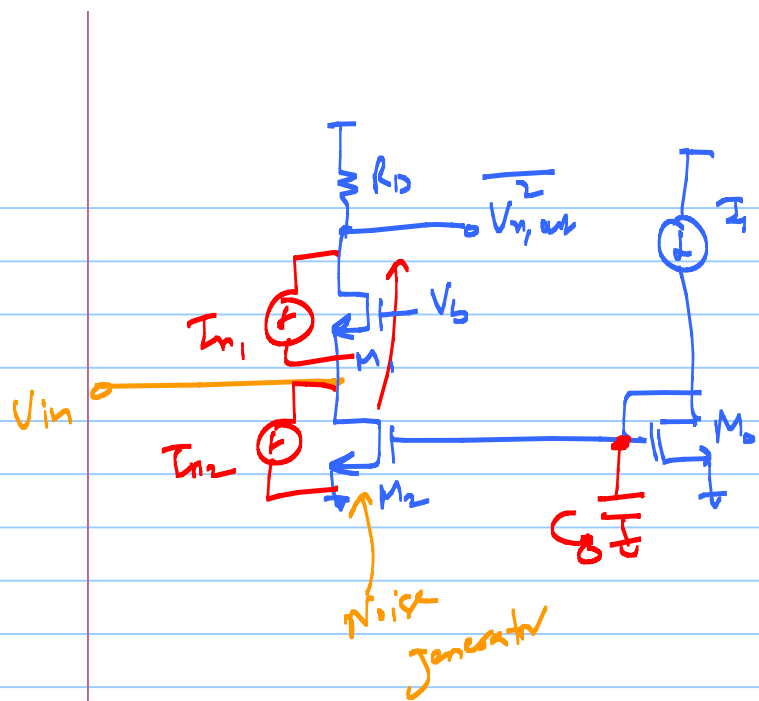$\Rightarrow$ not used for low-noise Amplification



Sf:

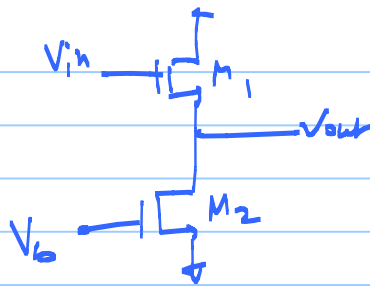

$$\overline{V_{n,in}^2} = \overline{V_{n,2}^2} + \frac{\overline{V_{n,out}^2}|_{M_2}}{A_v^2}$$

$A_v < 1$


$$= 4kT \cdot \frac{1}{2} \left(\frac{1}{g_{m1}} + \frac{g_{m2}}{g_{m1}^2} \right)$$

$$\Rightarrow g_{m1} \uparrow, g_{m2} \downarrow$$

$$A_v < 1 \Rightarrow$$

Cascode
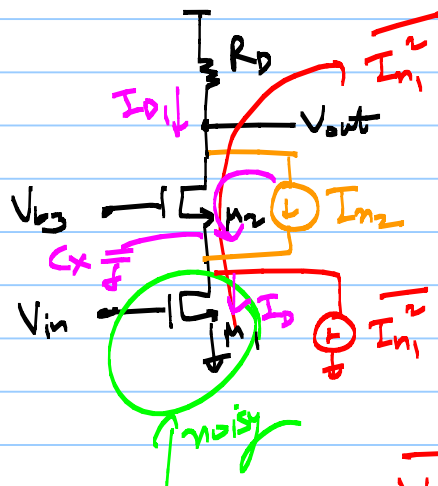
$$\lambda_2 = 0 \Rightarrow \underline{\underline{\omega_{o2} \rightarrow \infty}}$$



$$I_{D2} + I_{n2} = 0$$

@ low-frequencies with $\omega_{o2} \rightarrow \infty$

I_{n2} doesn't affect $\overline{V_{n,out}^2}$

$$\overline{V_{n,out}^2} \approx \overline{I_{n1}^2} \cdot (g_{m1} r_{o1} \parallel R_D)^2$$



Diff Amp

2-port circuit

