


ECE 614 - Lecture 12

$\nabla \Rightarrow$



Note Title

10/4/2012

BALUN

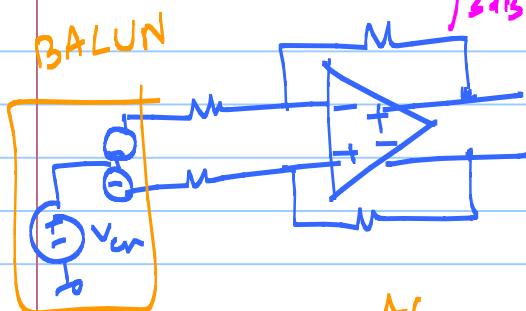



$$f_{213} = f_{un} \cdot \beta$$

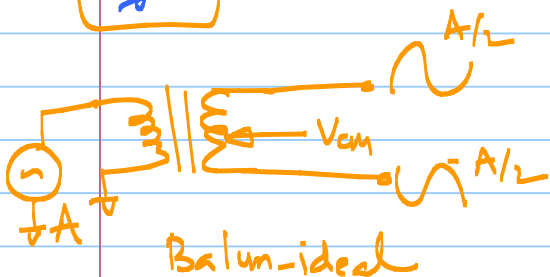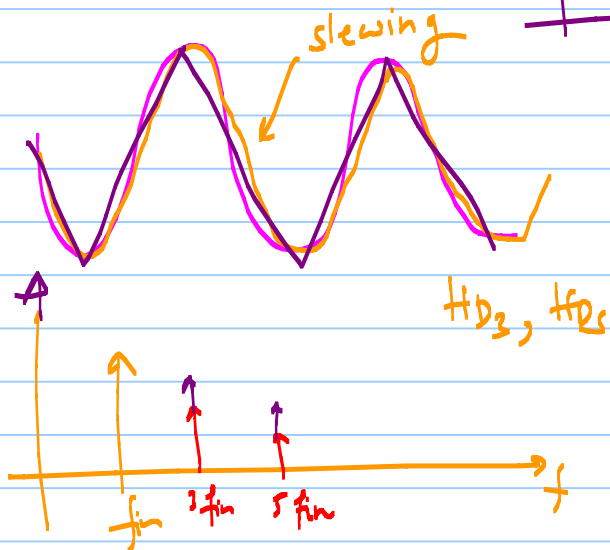

Distortion Analysis


.disto


2-port circuit

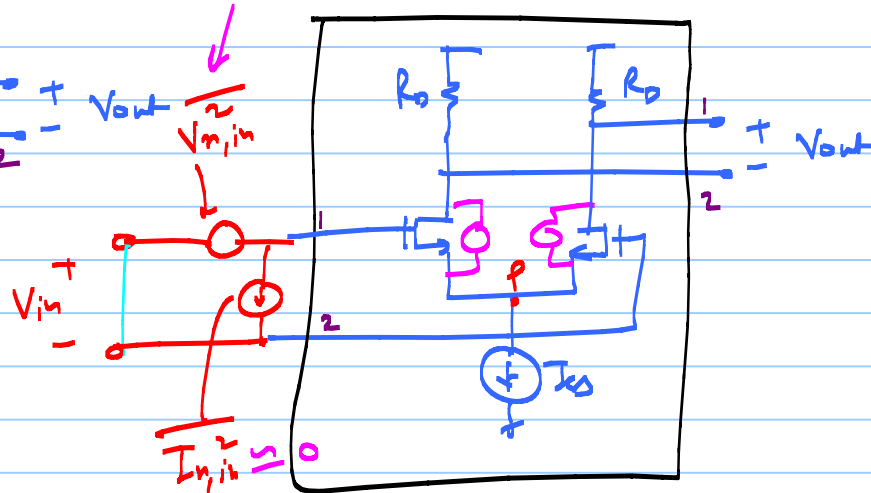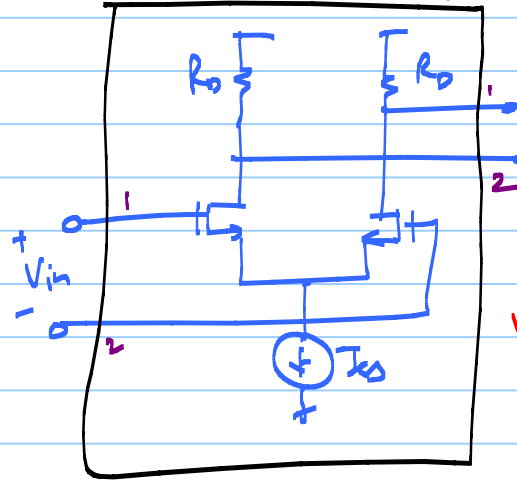

CMOS and @ low-f


spot noise

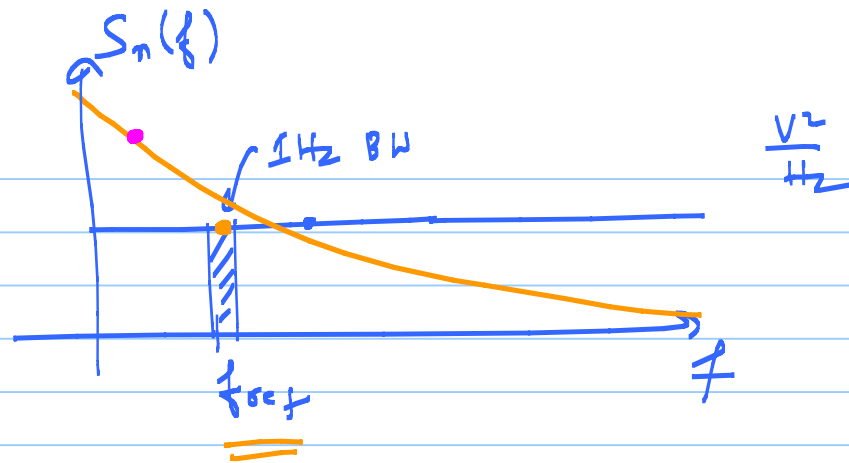

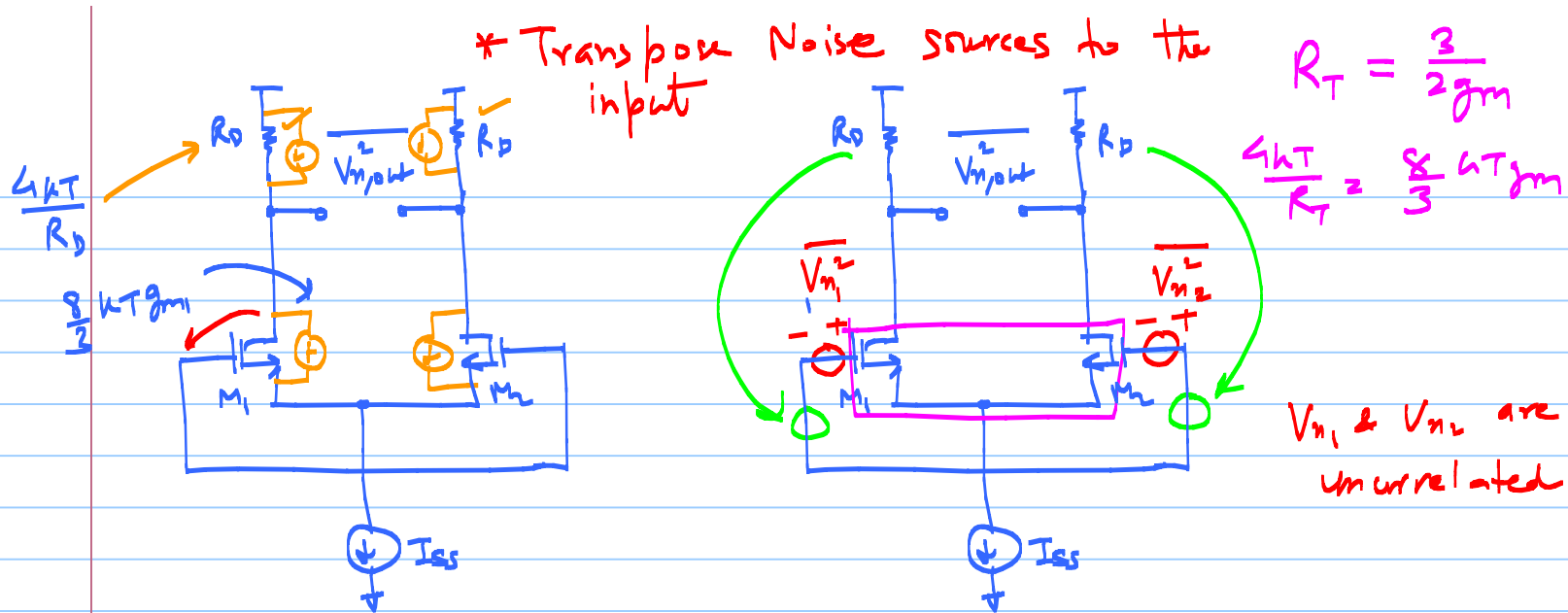

$$\overline{V_{n,in}^2} = \overline{V_{n1}^2} + \overline{V_{n2}^2} + 2 \times \frac{4kT}{g_{m1}^2 R_D} + \frac{1}{f} \text{ Noise}$$
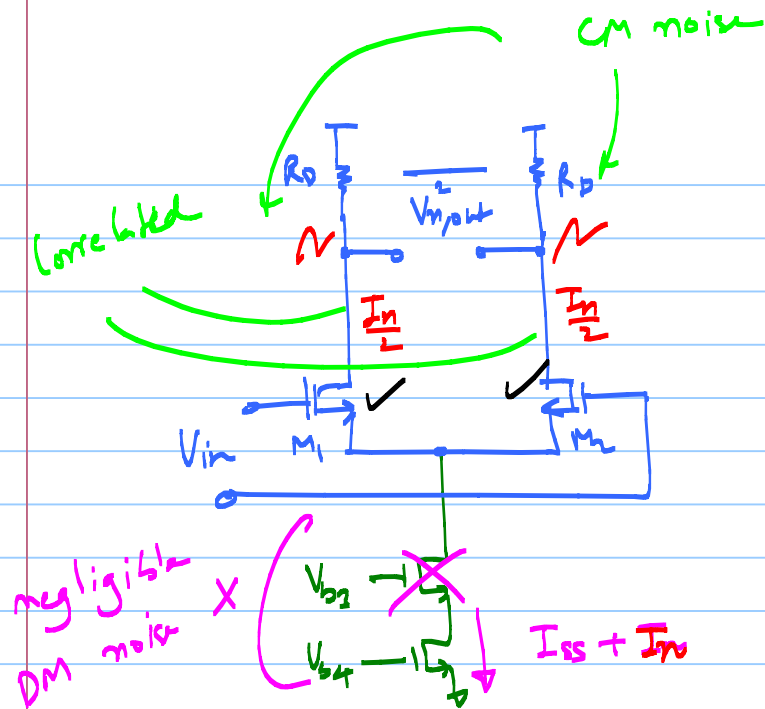
$$\overline{V_{n,in}^2} = 8kT \left(\frac{2}{3 g_{m1,2}} + \frac{1}{g_{m1,2}^2 R_D} \right) + \frac{2k}{C_{ox}(WL)_{1,2}} \frac{1}{f}$$





$$V_{in} = 0$$

$$V_{in} > 0$$



$$\begin{aligned} \Delta I_{D1} - \Delta I_{D2} &= g_m \Delta V_{in} \\ &= g_m \left(1 + \frac{I_{in}}{2I_{SS}} \right) \cdot \Delta V_{in} \end{aligned}$$

* for small inputs, the differential o/p noise is negligible

* Same goes for CMFB circuit noise

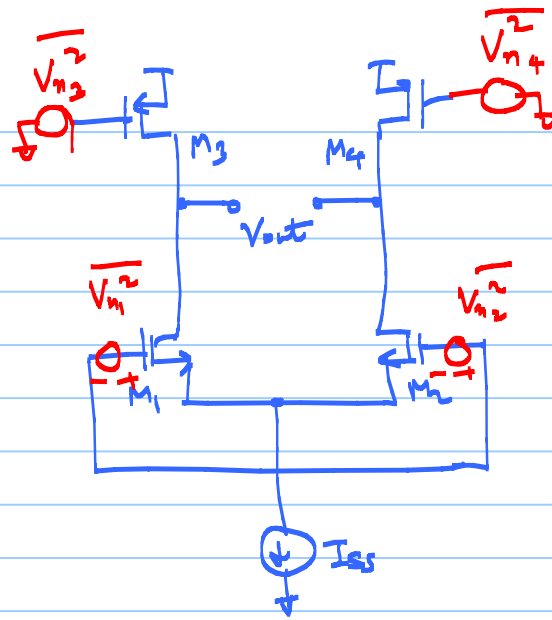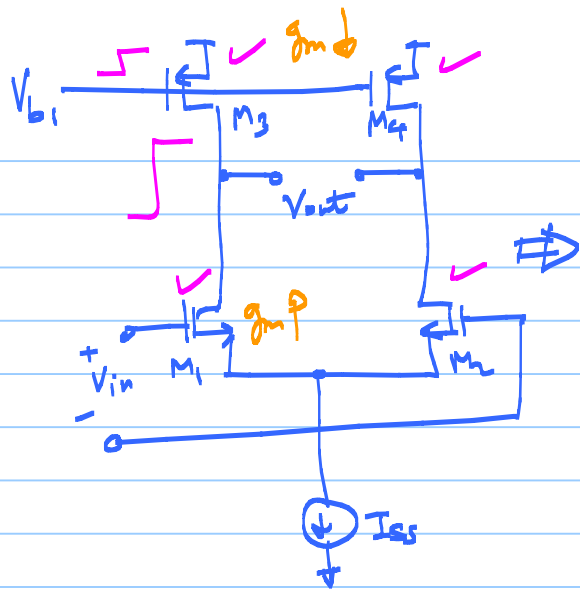

Differential picture

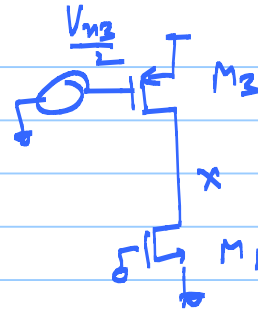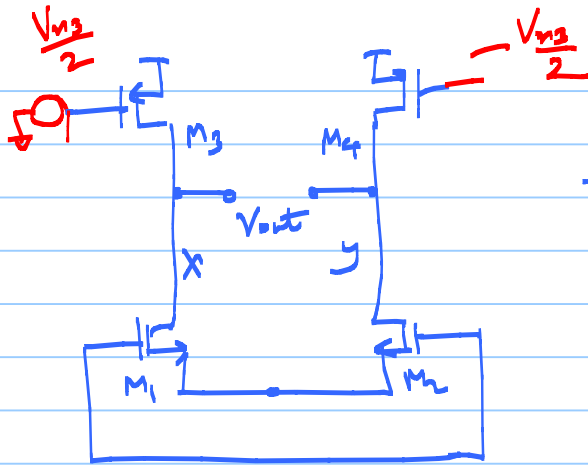

$$\overline{V_{n,out}^2}|_{M_3} = g_{m3}^2 (r_{o1} || r_{o3})^2 \cdot \overline{V_{n3}^2}$$

$$\overline{V_{n,out}^2}|_{M_4} = g_{m4}^2 (r_{o2} || r_{o4})^2 \cdot \overline{V_{n4}^2}$$


$$\begin{aligned} \overline{V_{n,in}^2}|_{M_3, M_4} &= \frac{\overline{V_{n,out}^2}|_{M_3} + \overline{V_{n,out}^2}|_{M_4}}{A_v^2} \leftarrow g_{m1}^2 (r_{o1} || r_{o3})^2 \\ &= 2 \times \frac{g_{m3}^2}{g_{m1}^2} \cdot \overline{V_{n3}^2} \end{aligned}$$

$$\overline{V_{n,in}^2} = 2\overline{V_{n1}^2} + 2 \cdot \frac{g_{m3}^2}{g_{m1}^2} \cdot \overline{V_{n3}^2} \quad \leftarrow 4kT \cdot \frac{2}{3} \cdot \frac{1}{g_{m3}}$$

$$= 8kT \left(\frac{2}{\underline{\underline{3g_{m1}}}} + \frac{2g_{m3}}{\underline{\underline{g_{m1}^2}}} \right) + \frac{2K_n}{C_{ox}(W/L)_{1,2}f} + \frac{2K_p}{C_{ox}(W/L)_{3,4}f} \cdot \frac{1}{f} \cdot \frac{g_{m3}^2}{g_{m1}^2}$$

$g_{m1} \uparrow$ $g_{m3} \downarrow$

Cascaded Amplifiers


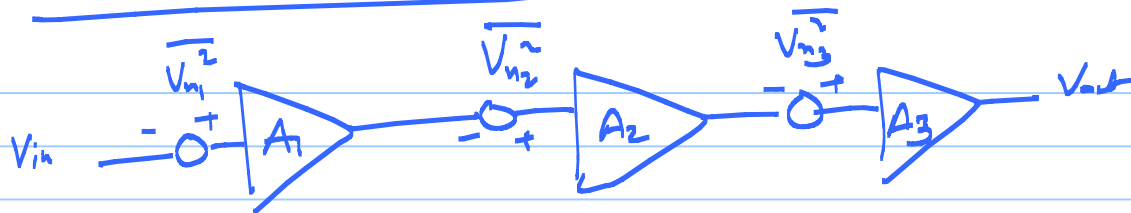


$$\overline{V_{n,out}^2} = \overline{V_{n1}^2} \cdot (A_1 A_2 A_3)^2 + \overline{V_{n2}^2} \cdot (A_2 A_3)^2 + \overline{V_{n3}^2} \cdot A_3^2$$


$$\overline{V_{n,in}^2} = \frac{\overline{V_{n,out}^2}}{(A_1 A_2 A_3)^2} = \underbrace{\overline{V_{n1}^2}}_{\text{first stage dominates}} + \frac{\overline{V_{n2}^2}}{A_1^2} + \frac{\overline{V_{n3}^2}}{A_1^2 A_2^2}$$

first stage dominates

Noise in opamps

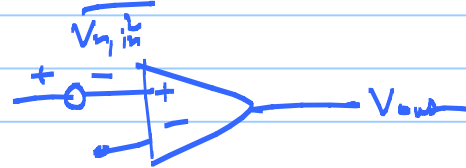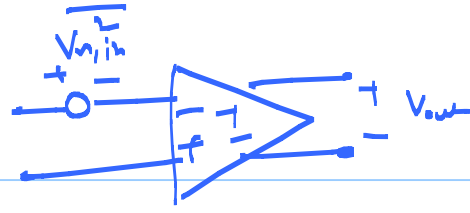


Telescopic

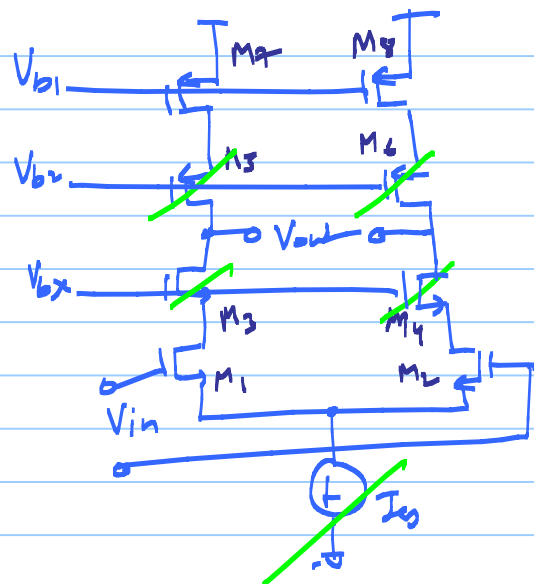

$M_{1,2}$
 $M_{7,8}$ ← Primary Noise Contributors

$$\overline{V_n^2} = 4kT \left(2 \cdot \frac{2}{3g_{m1,2}} + 2 \cdot \frac{2}{3} \frac{g_{m7,8}}{g_{m1,2}^2} \right) + \frac{2k_n}{(W/L)_{1,2} C_{ox} f} + \frac{2k_p}{(W/L)_{7,8} C_{ox} f} \cdot \frac{g_{m7,8}^2}{g_{m1,2}^2}$$

Two-stage opamp

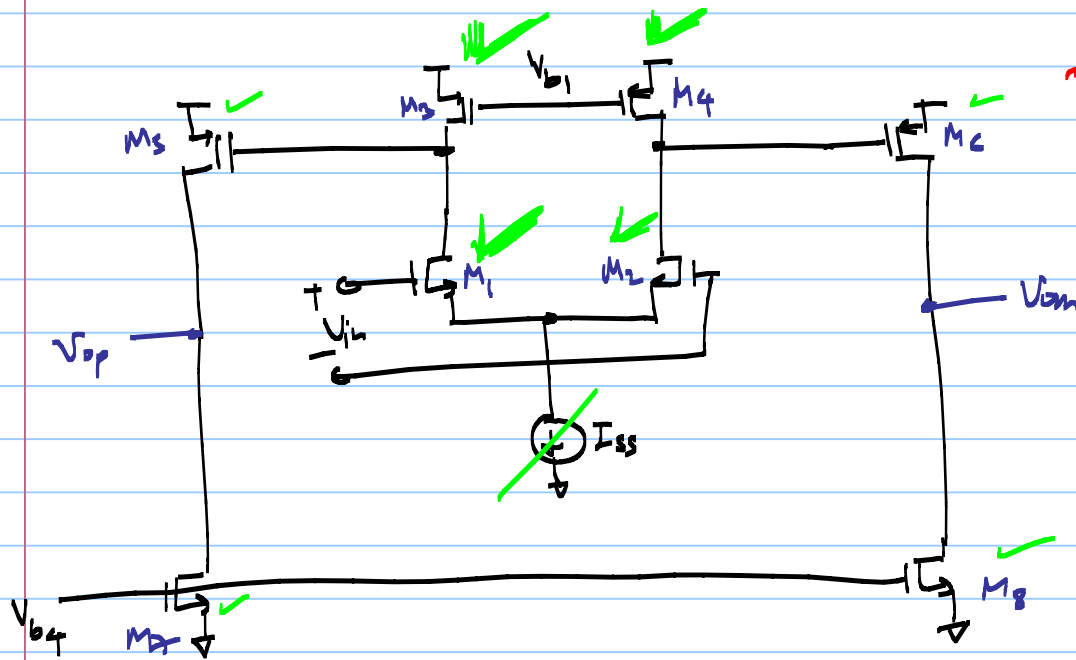

* Second stage noise
is divided by
 A_1^2

$$\overline{V_{n,in}^2} \Big|_{M_1-M_4} = 2 \cdot 4kT \cdot \frac{2}{3} \cdot \frac{(g_{m1} + g_{m3})}{g_{m1}^2}$$

$$\overline{V_{n,in}^2} \Big|_{M_5-M_8} = \frac{2 \cdot 4kT \cdot \frac{2}{3} \cdot (g_{m5} + g_{m7}) (r_{o5} \parallel r_{o7})^2}{g_{m1}^2 \cdot (r_{o1} \parallel r_{o3})^2 \cdot g_{m5}^2 \cdot (r_{o5} \parallel r_{o7})^2}$$

$$= \frac{16kT}{3} \cdot \frac{(g_{m5} + g_{m7})}{g_{m1}^2 g_{m5}^2 (r_{o1} \parallel r_{o3})^2}$$

$$\overline{V_{n,in}^2} = \frac{16kT}{3} \cdot \frac{1}{g_{m1}^2} \left[g_{m1} + g_{m3} + \frac{g_{m5} + g_{m7}}{g_{m5}^2 (r_{o1} \parallel r_{o3})^2} \right]$$

small contribution
for the 2nd stage