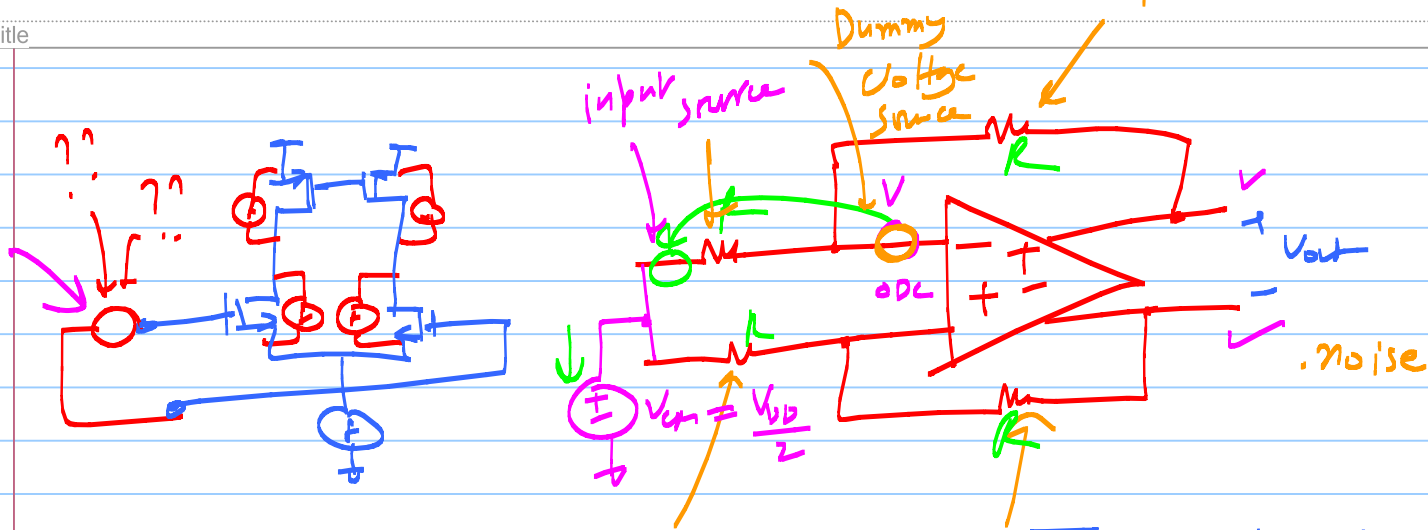


ECE 614 - Lecture 14


Note Title

10/18/2012




feedback doesn't change $\overline{V_{in}^2}$ of the forward path
 ↳ assuming that ' β ' resistors are noiseless
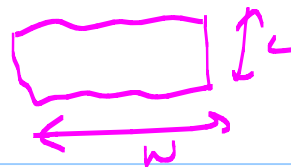
$$\sigma_{\Delta WL} \propto \frac{1}{\sqrt{WL}} = \frac{1}{\sqrt{\text{Area}}}$$



R_c


(R → ±1% ±15%
 C → ≤ ±1% ±15%

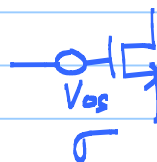

"Mismatch Analysis"

$\frac{C_1}{C_2}$

≤ 0.01%

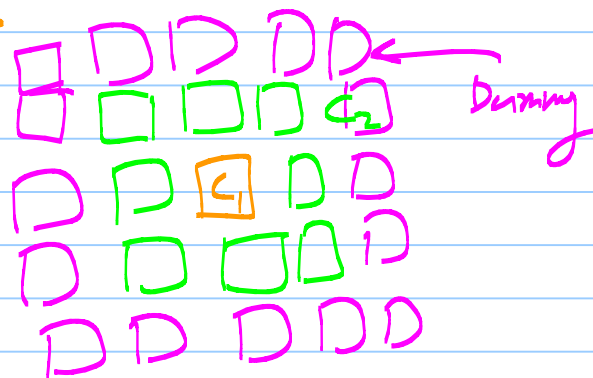

for the sampling circuit

Ideally $\Rightarrow V_{out} = V_{in}$

$$V_{out} = V_{in} \left(1 + \frac{WLCox}{C_H} \right) + \gamma \frac{WLCox}{C_H} \sqrt{2\phi_B + V_{in}} - \underbrace{\frac{WLCox}{C_H} (V_{DD} - V_{THN0} + \gamma \sqrt{2\phi_B})}_{\text{DC offset}}$$

$$V_{out} = \alpha_1 V_{in} + \alpha_2 \sqrt{V_{in}}$$

$$\sqrt{x_1 + x_2} \neq \sqrt{x_1} + \sqrt{x_2}$$

$$\sqrt{1+x} = 1 + a_1 x + \frac{a_2 x^2}{2} + \frac{a_3 x^3}{3} + \dots$$

distribution terms

f_{OM}

Speed - precision tradeoff

$(\frac{W}{L}) \uparrow$ $(WL) \uparrow$
 $\Delta V_{cI} \uparrow$

$$F = \frac{1}{2 \cdot \Delta V}$$


$R_{on} C_H$

$$\frac{W L C_{ox}}{C_H} (V_{DD} - V_{in} - V_{THN})$$


$$\frac{1}{\mu_n C_{ox} (\frac{W}{L}) (V_{DD} - V_{in} - V_{THN})} \cdot C_H$$

$$F = \frac{1}{2 \Delta V} = \frac{\mu_n}{L^2}$$

first order

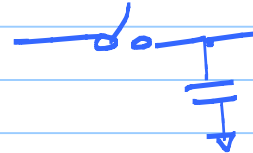

Clock-feedthrough

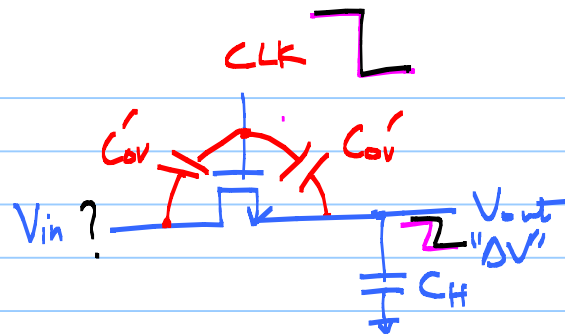

T/H

C_{ov} ← overlap caps
per unit width

$$\Delta V_{cf} = V_{CLK} \cdot \frac{WC_{ov}}{WC_{ov} + C_H}$$



$\Delta V \Rightarrow$ independent of input-level

↳ constant offset in the sampled output

$$W \uparrow \Rightarrow \Delta V_{cf} ?$$

$$C_H \gg WC_{ov}$$

$$\frac{KT}{C}$$

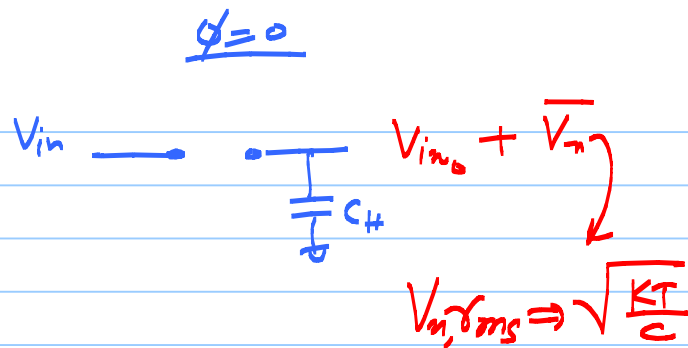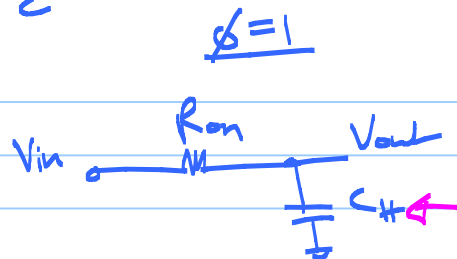

Large C_H
 $\downarrow$
 lower speed or
 more power

Single stage
 opamp: $f_{in} \approx \frac{g_{m1}}{2\pi C_L}$


$$SNR = 20 \log_{10} \left(\frac{V_{out,rms}}{V_{n,rms}} \right)$$

$\boxed{SNR} \uparrow \Rightarrow \boxed{C_H} \uparrow$
 $\downarrow$
 $6.02 \boxed{N_{eff}} + 1.76$

Charge Injection Cancellation

① Dummy Switch

→ deterministic error.

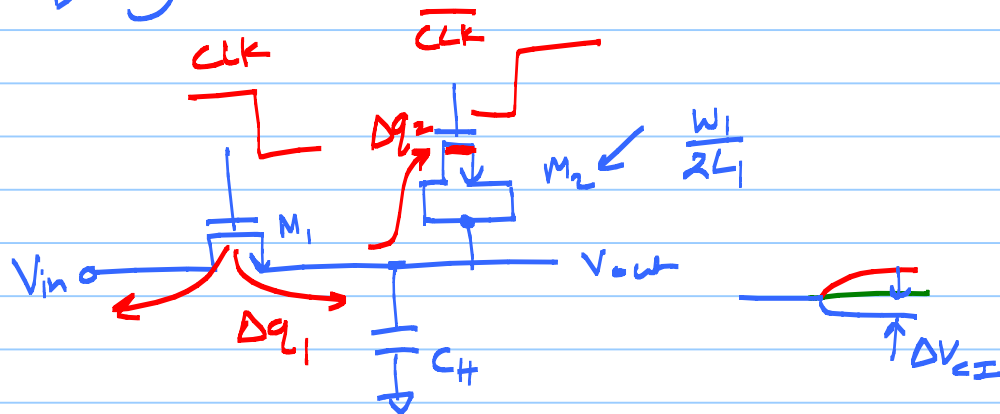


for perfect cancellation

$$\Delta q_1 = \Delta q_2$$


$$\Rightarrow \frac{W_1 L_1 C_{ox}}{2} (V_{CLK} - V_{in} - V_{THN1}) = W_2 L_2 C_{ox} (V_{CLK} - V_{in} - V_{THN2})$$

$$L_1 = L_2, \quad W_2 = \frac{W_1}{2}$$

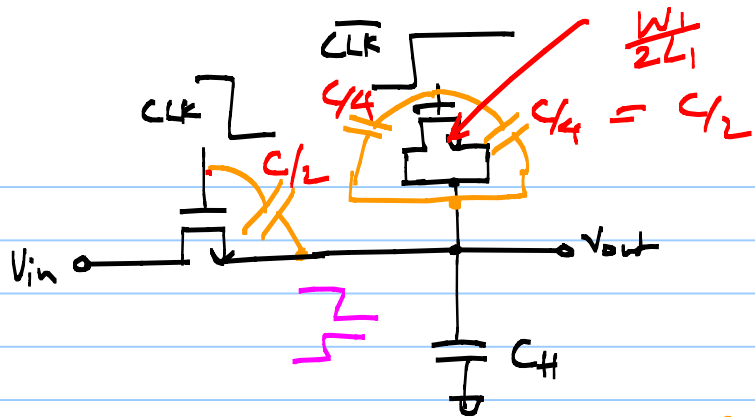
$$\text{Assumption} \Rightarrow \Delta q_1 = \frac{Q_{ch}}{2}$$


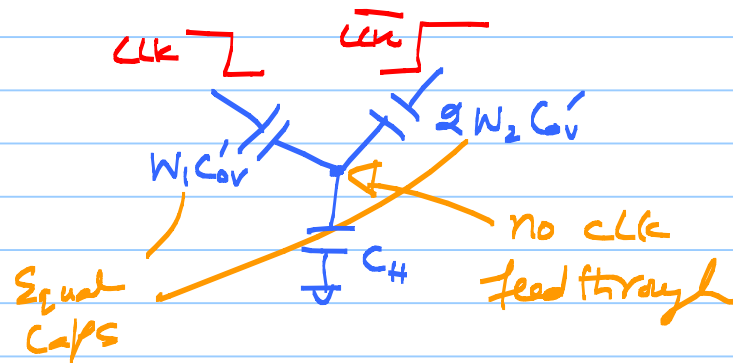
$$\left(\frac{W}{L}\right)_2 = \frac{1}{2} \left(\frac{W}{L}\right)_1$$



② Complementary Switches (TQ)

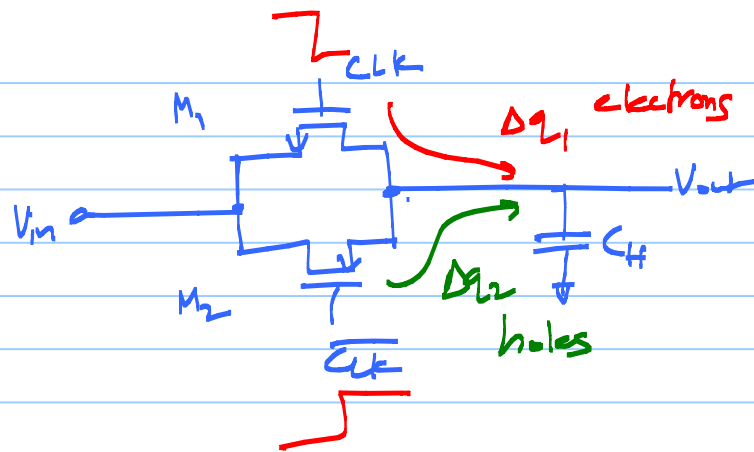

* for $\Delta Q_1 = \Delta Q_2$


$$W_1 L_1 C_{ox} (V_{CLK} - V_{in} - V_{THN}) \triangleq W_2 L_2 C_{ox} (V_{in} - |V_{THP}|)$$

⇒ Cancellation occurs only for one value of V_{in} !

↳ Not true for $\forall V_{in}$

* doesn't cancel the clock feedthrough as the overlapping caps for NMOS & PMOS are not equal.

③ Differential Circuits

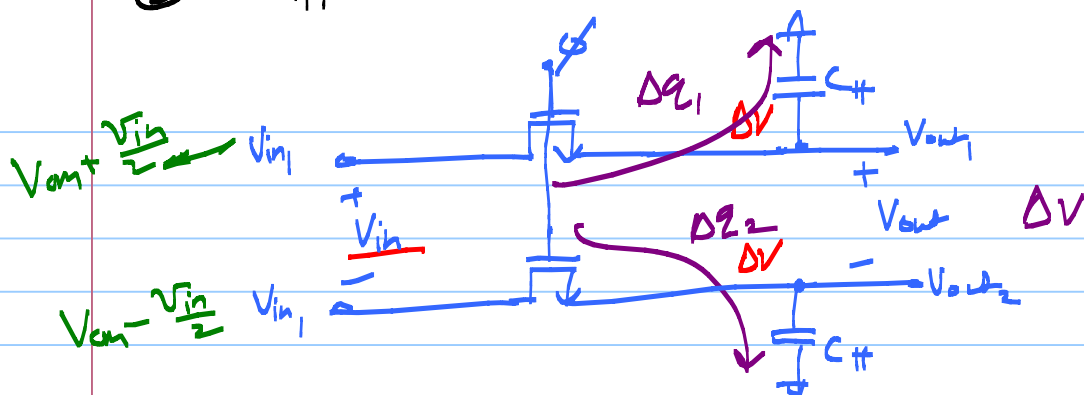

$$\Delta Q_1, \Delta Q_2 = W L C_{ox} \left[(V_{in_2} - V_{in_1}) + (V_{THN_2} - V_{THN_1}) \right]$$

$$= W L C_{ox} \left[\underbrace{(V_{in_2} - V_{in_1})}_{V_{in}} + \gamma \left(\underbrace{\sqrt{2\phi_B + V_{in_2}} - \sqrt{2\phi_B + V_{in_1}}}_{\text{non-linear term}} \right) \right]$$

$$f(V_{in}) = \gamma \sqrt{2\phi_B + V_{cm} + \frac{V_{in}}{2}}$$

$$= f(V_{in}) - f(-V_{in})$$

odd function

$$g(x) = f(x) - f(-x)$$

has only odd terms in the Taylor series expansion

odd function

Unity - Gain Sampler / Buffer