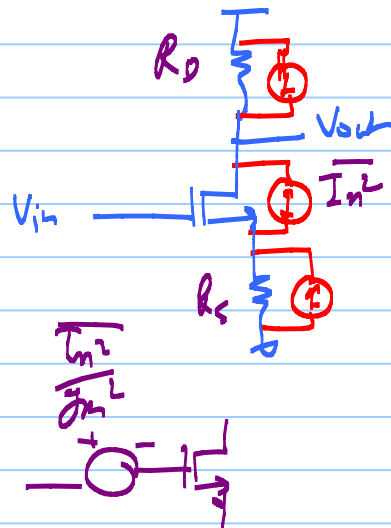


ECE 614 - Lecture 15

Note Title

10/23/2012



$$\overline{V_{n, out}^2} =$$

$$V_n = V_{n1} + V_{n2}$$


$$\overline{V_n^2} = \overline{(V_{n1} + V_{n2})^2}$$

$$= \overline{V_{n1}^2} + \overline{V_{n2}^2} + 2 \overline{V_{n1} V_{n2}}$$


uncorrelated

Unity-gain Sampler


(S/H)

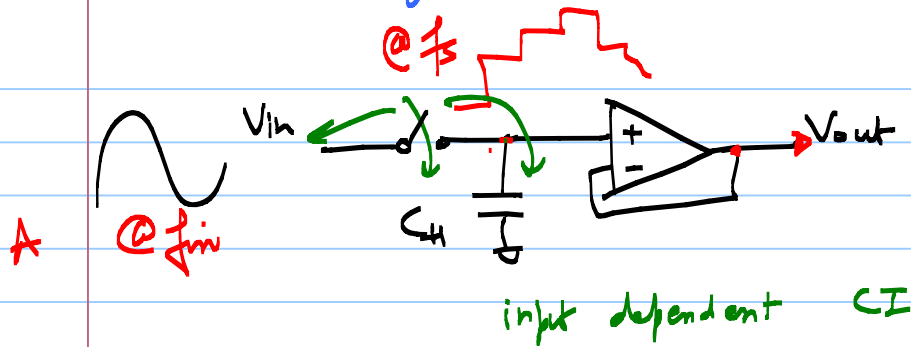

HD ← one-tone test
IM ← two-tone test

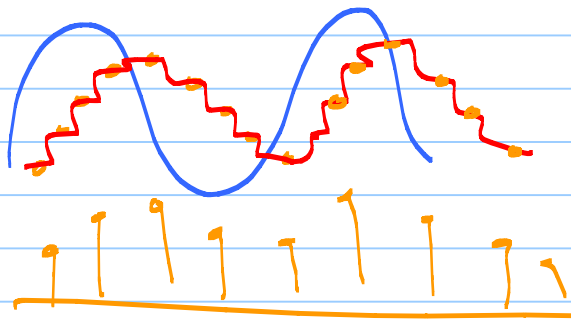

FFT
⇒


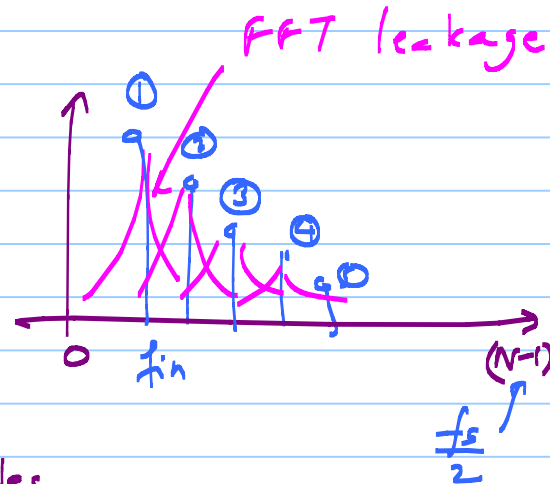


$$\frac{f_{in}}{f_s} = \frac{k}{L} = \frac{1}{128} \quad \text{No. of } "N" \text{ samples}$$


* Coherent sampling

$$= \frac{32}{128} = \frac{1}{4}$$

"Dynamic Characterization"

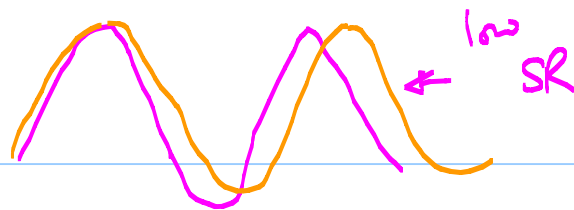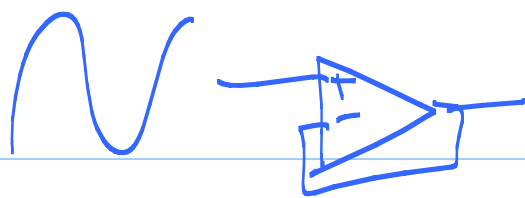


distortion due to slewing

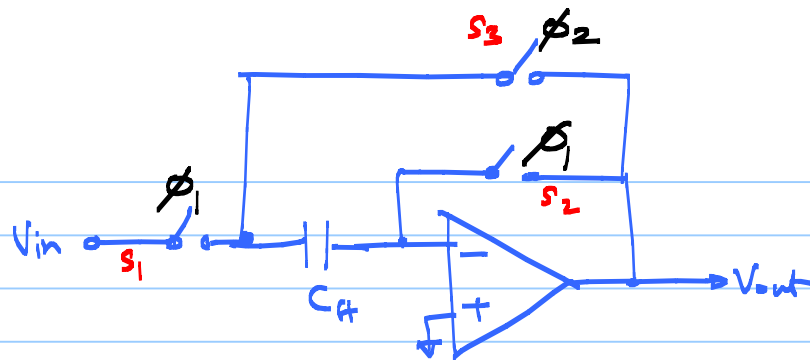

ϕ_1 Sampling mode


ϕ_2 Amplification/Hold mode

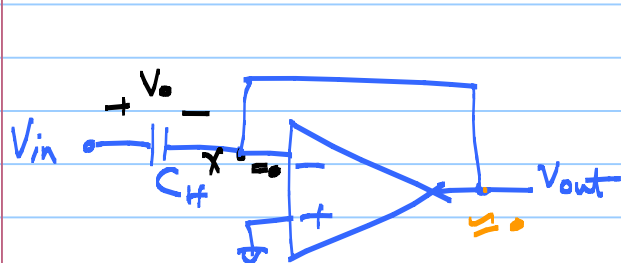

$$V_{out} = V_n = 0$$

Voltage across C_f tracks V_{in}

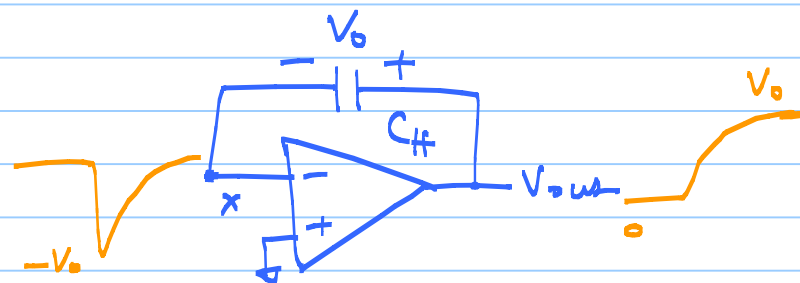
@ $t = t_0$ $\phi_1 \downarrow$, $V_{in} = V_0$ is stored in C_f



$$V_n = 0$$

V_{out} rises to $-V_0$

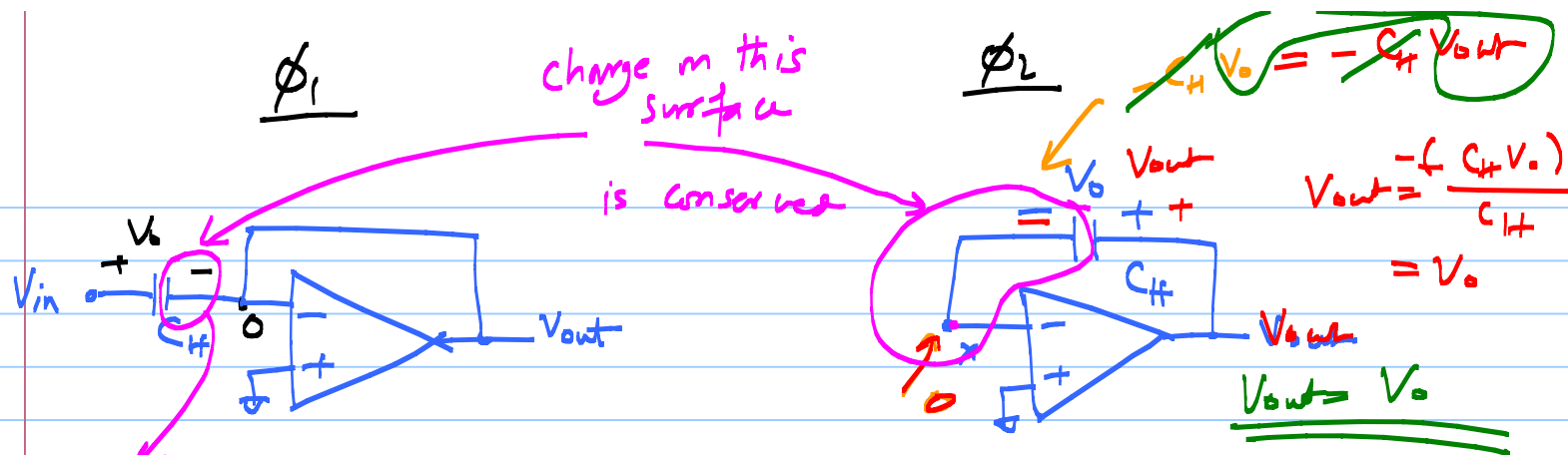* This value is frozen and proceeded to subsequent stages




charge on the surfaces connected to
the virtual ground (V_x) is conserved
↳ No DC path


ϕ_1

slow-motion:
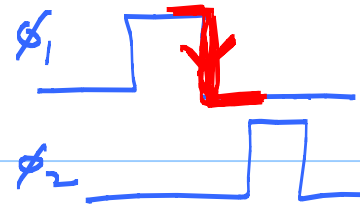
$$\Delta Q_2 = WLCox(V_{CLK} - V_{in} - V_{THN_0})$$



Constant
Charge
injection


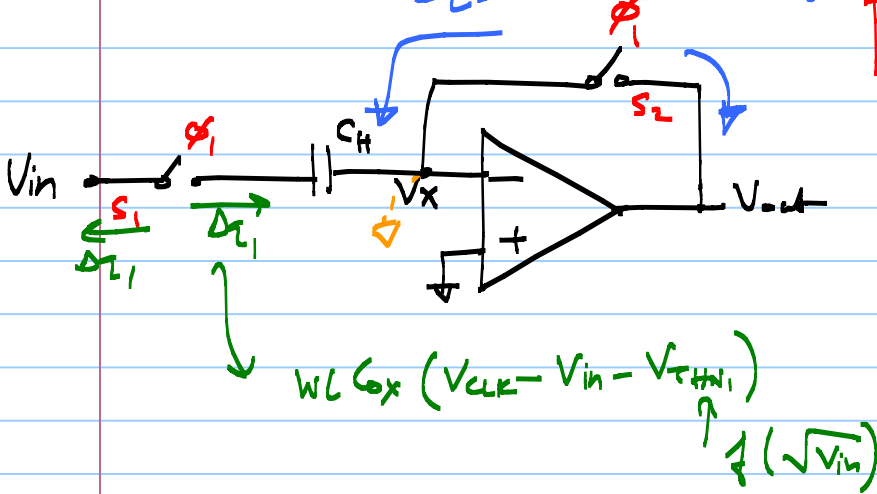




offset $\Delta Q_2 \Rightarrow$ Constant C.I.

$\Delta Q_1 \Rightarrow$ input dependent CI


NL $\nearrow$ Can we get rid of this?

Trick: Delayed sampling clock

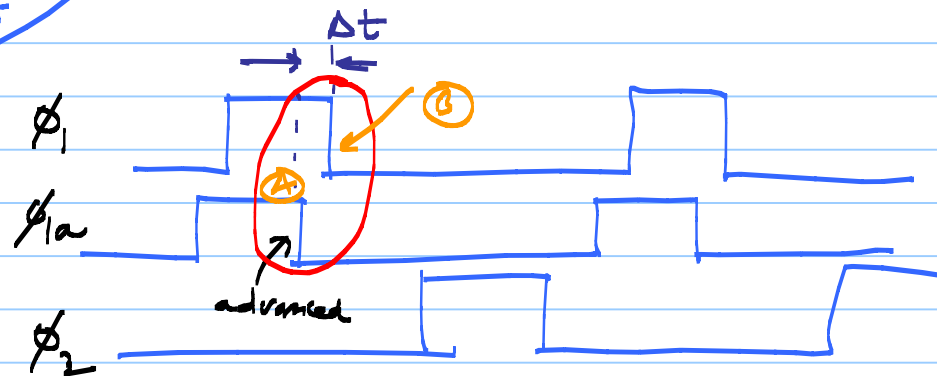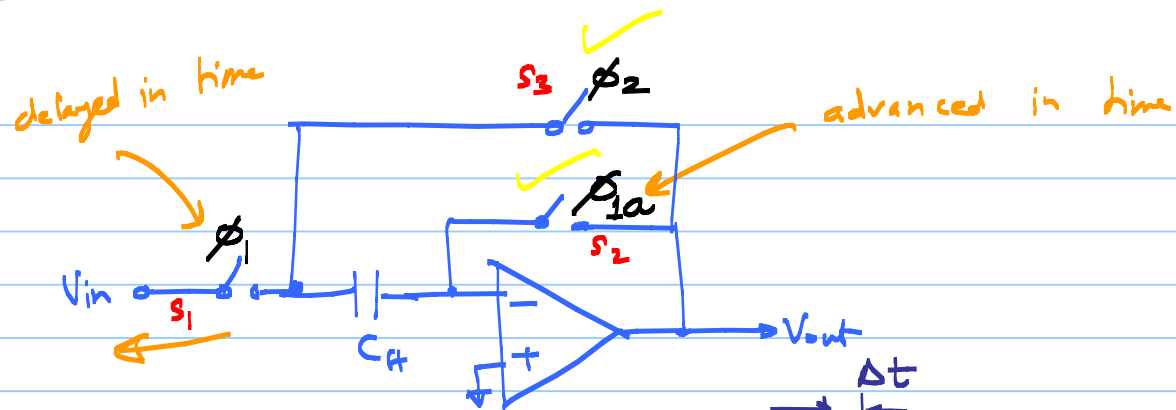


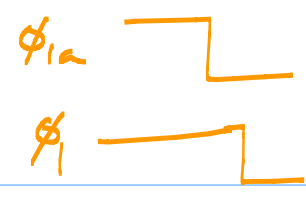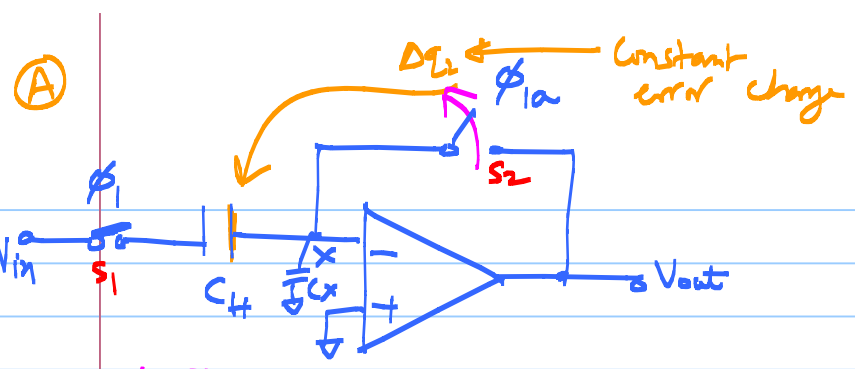

② charge sucked into the source

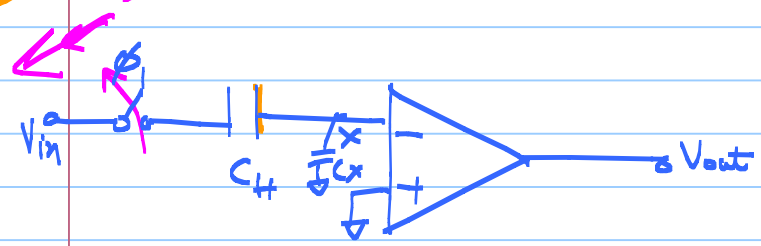

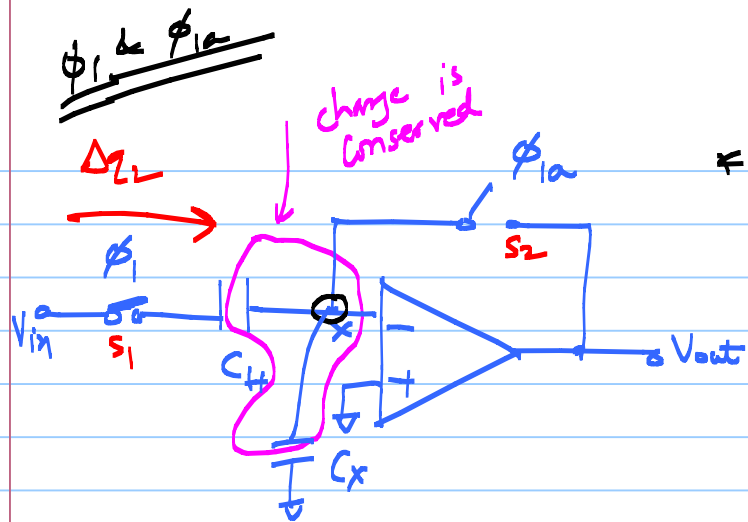
* avoids input-dependant charge injection



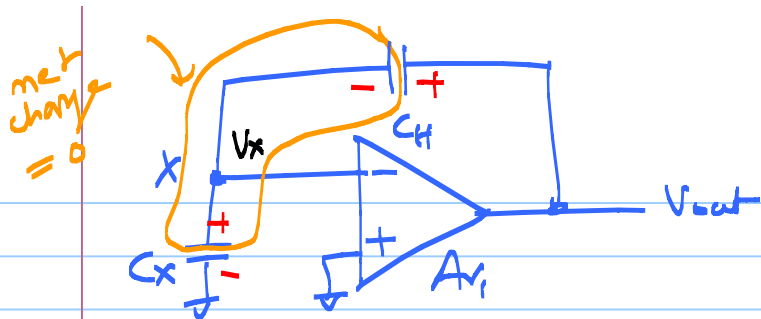Example $V_{in}=0$

* After S_2 is off.

* Before S_1 turns off,
total charge on right plate of C_H
+ top plate of $C_X = 0$



Total charge @ node X = 0

$$\Rightarrow C_X V_X - (V_{out} - V_X) C_H = 0 \longrightarrow \textcircled{1}$$

$$\& V_X = - \frac{V_{out}}{A_{v1}} \longrightarrow \textcircled{2}$$

$\Rightarrow \textcircled{1} \& \textcircled{2} \Rightarrow$


$$- (C_X + C_H) \frac{V_{out}}{A_{v1}} - V_{out} C_H = 0$$

$$V_{out} (?) = 0$$


$$\Rightarrow \underline{\underline{V_{out} = 0}}$$

$$\boxed{V_{out} = V_S} \& \text{ indep. of } \Delta Q_2, C_X, A_{v1}$$

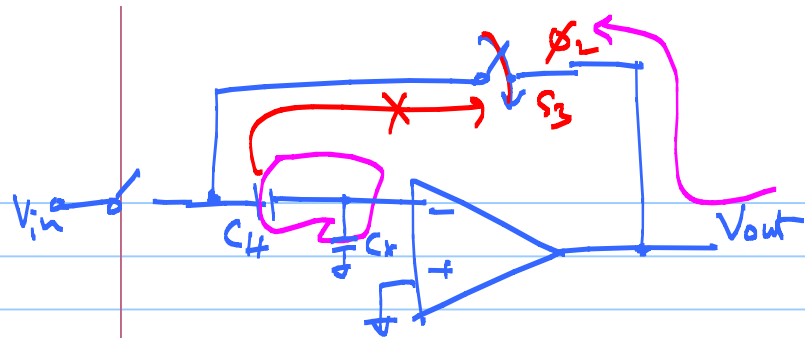$\Rightarrow$ charge injection ΔQ_2 (by S_1) introduces no error as " S_2 " is turned off first.



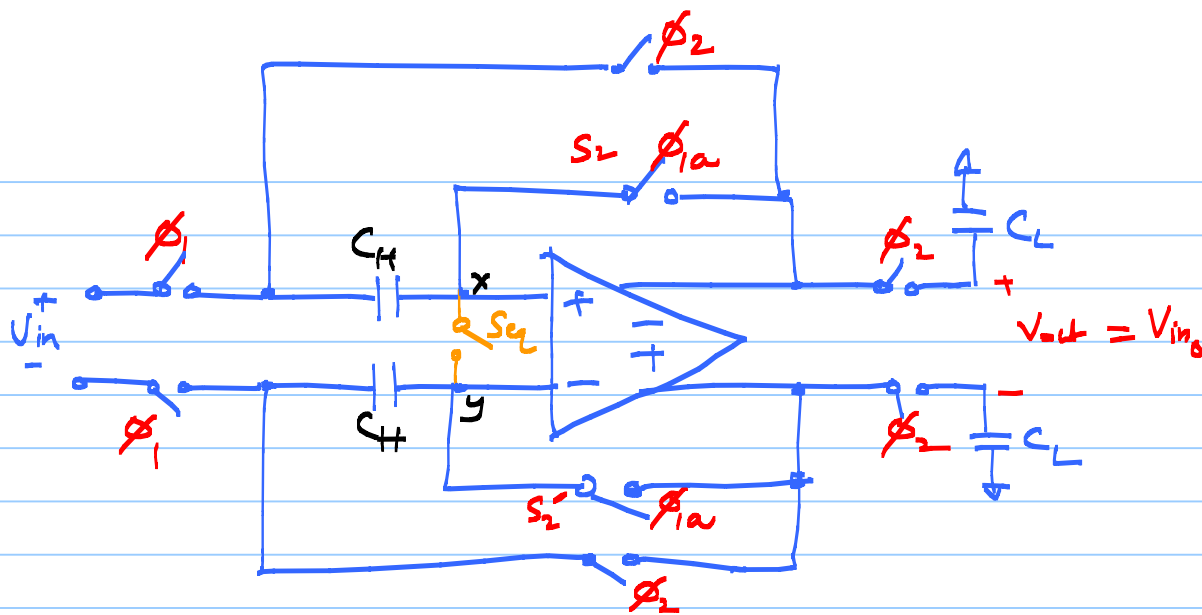* when, ϕ_L goes high
 the inversion layer charge for S_3
 is completely supplied by V_{out}
 (opamp)



* NL due to the input dependent charge injection is mitigated

* any fixed charge injected at x & y is a CM-disturbance


* In reality S_2 & S_2' exhibit finite charge injection mismatch

↳ add another switch S_{eq}

↳ turns off slightly after S_2 & S_2'

↳ but before S_1 & S_1'

Professional Clock Generator

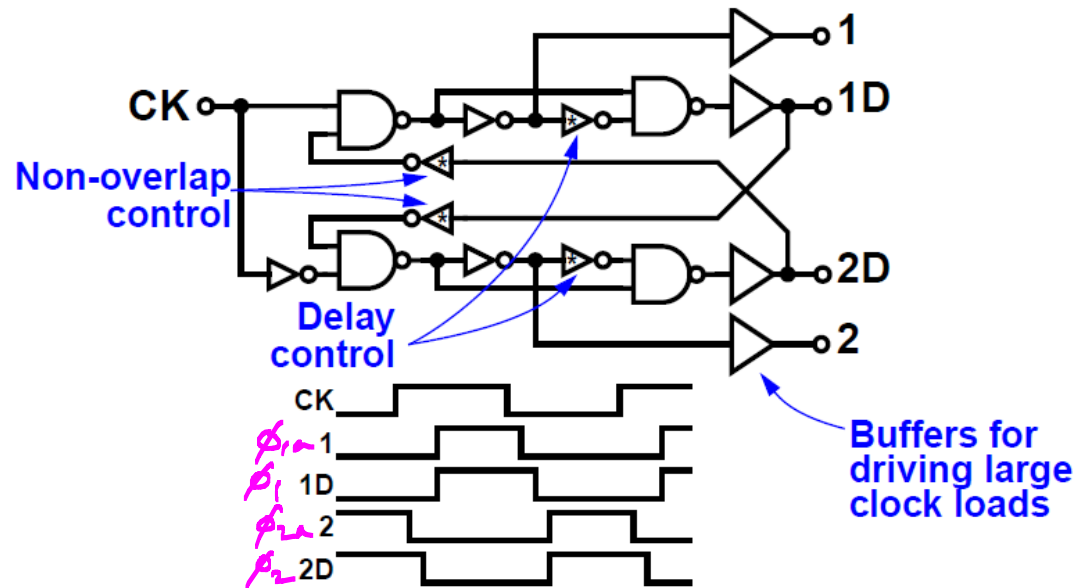

- To maximize the time available for settling, make the early and late phases start at the same time