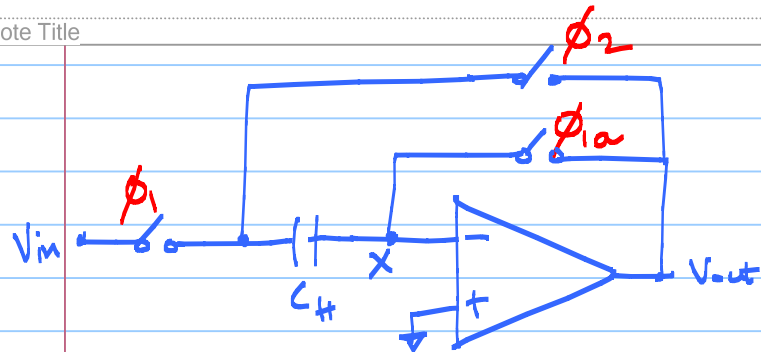




ECE 614 - Lecture 16

Note Title


10/25/2012




ϕ_1 Sampling mode

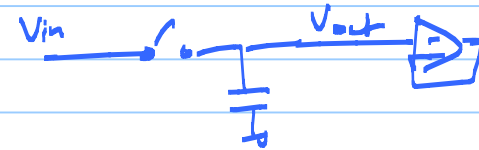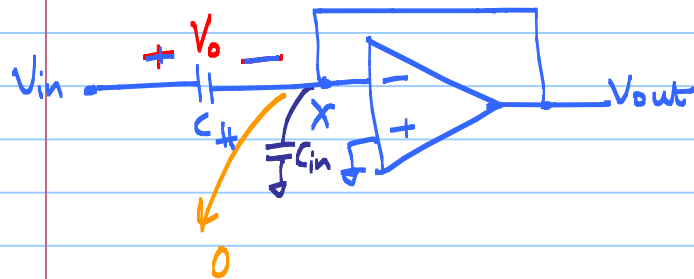


ϕ_2 (amplification)

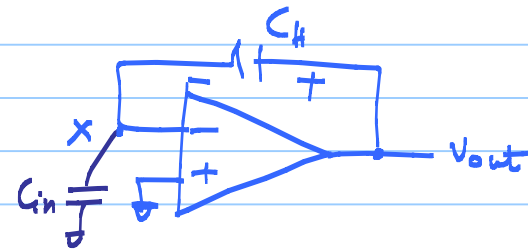

A_v

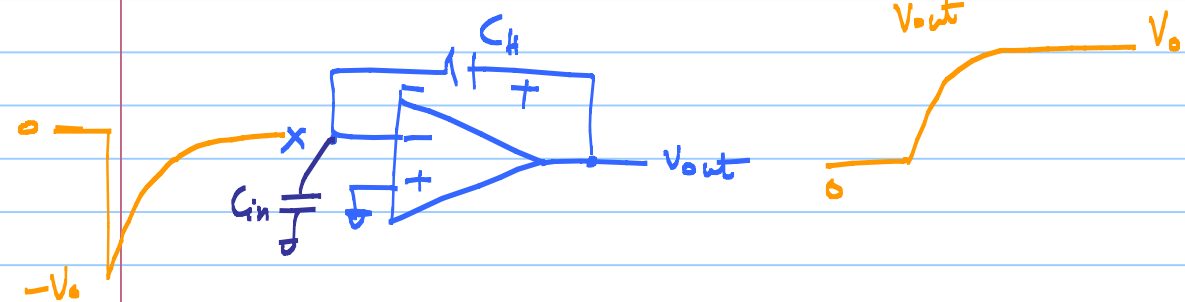


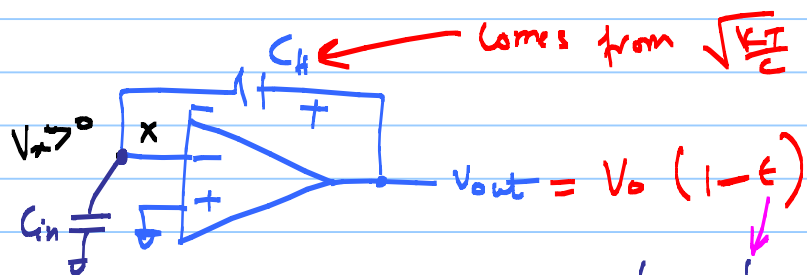

$$\frac{1}{\beta A_v} = \frac{1}{A_v \cdot \frac{C_H}{C_H + C_{in}}}$$

$$A_v \rightarrow \infty$$

$$C_{in} \downarrow$$

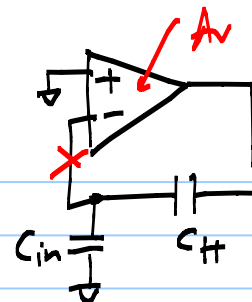


$$\beta = \frac{\frac{1}{s C_{in}}}{\frac{1}{s C_H} + \frac{1}{s C_{in}}}$$

$$\beta = \frac{C_H}{C_H + C_{in}} < 1$$

$$\text{loop-gain} = \beta A_v$$
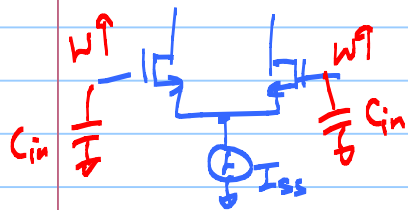
$$\text{gain error} \approx \frac{1}{\beta A_v}$$



$I_{SS} \rightarrow \text{fixed}$

$\omega_p, g_m \uparrow$

$V_{ov} \downarrow \Rightarrow g_m \uparrow$

$f_T \downarrow$

Ex.

$$C_{in} = 0.5 \text{ pF}$$




$$C_H = 2 \text{ pF}$$

gain error of 0.1% $\rightarrow$ 60 dB precision

$\rightarrow A_v \geq 1250 > 60 \text{ dB} \rightarrow > 80 \text{ dB}$

Speed Considerations

Sampling mode (ϕ_1)

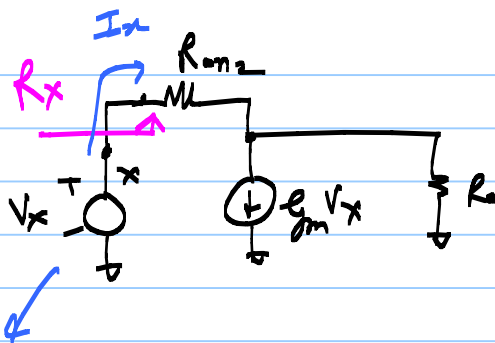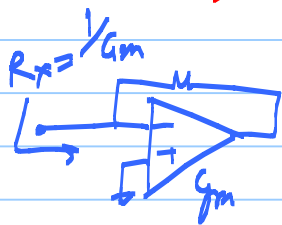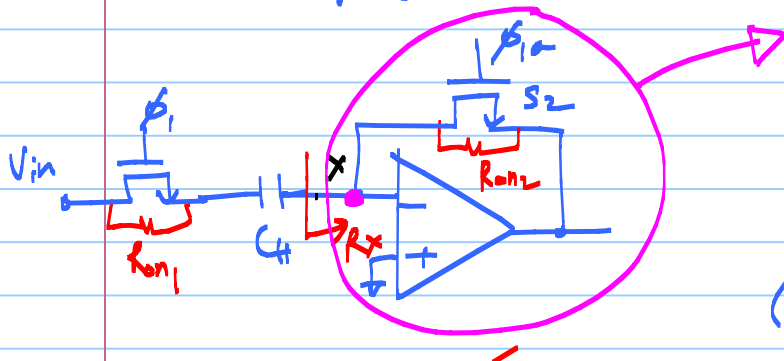

$$(I_x - g_m V_x) R_o + I_x R_{on2} = V_x$$

$$\Rightarrow R_x = \frac{V_x}{I_x} = \frac{R_o + \cancel{R_{on2}}}{\cancel{1} + g_m R_o} \approx \frac{1}{g_m}$$


$$g_m R_o \gg 1$$

$$R_{on2} \ll R_o$$


$$Z_{\text{samp}} = \left(R_{on1} + \frac{1}{g_m} \right) \cdot C_H$$


$$\textcircled{5} \tau_{\text{sam}} \leq \frac{T_s}{2} \Leftarrow \text{settling accuracy}$$

Amplification phase (ϕ)

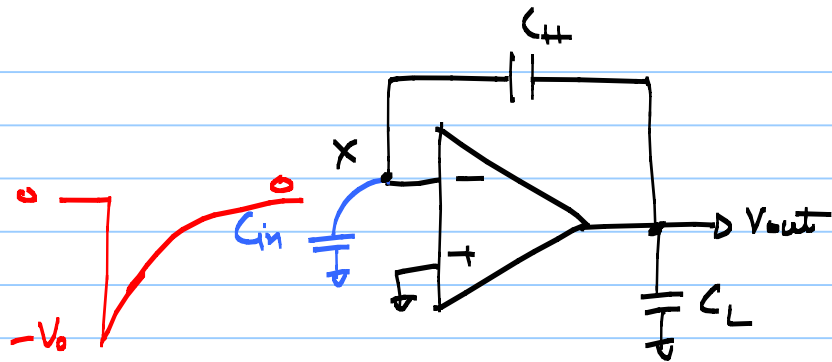
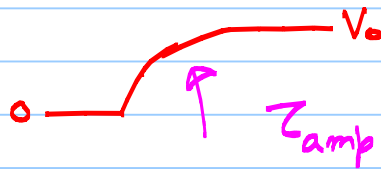
$$\begin{aligned} f_{3dB} &= \beta f_{un} \\ &= \frac{C_H}{C_H + C_{in}} \cdot f_{un} \end{aligned}$$



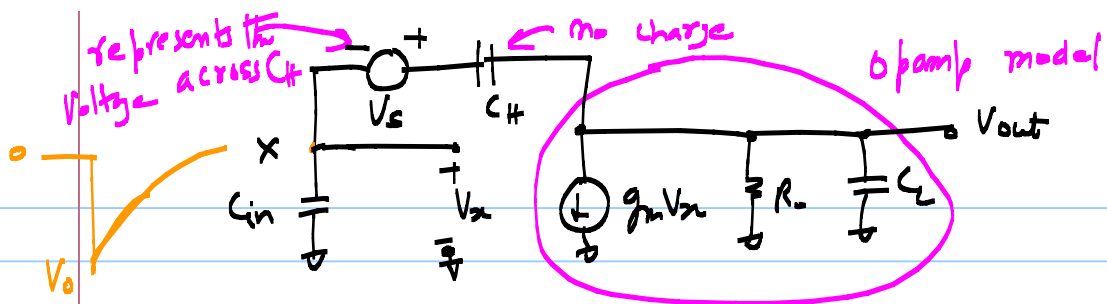

$$\frac{V_{out}}{V_s}(s) = ?$$

KCL: $V_{out} \left(\frac{1}{R_o} + s C_L \right) + g_m V_n = (V_s + V_n - V_{out}) \cdot s C_H \rightarrow \textcircled{1}$

KVL: current thru $C_{in} \Rightarrow s C_{in}$

$$V_n \cdot \frac{s C_{in}}{s C_H} + V_n + V_s = V_{out} \rightarrow \textcircled{2}$$

Solve $\textcircled{1}$ & $\textcircled{2}$

$$\frac{V_{out}}{V_s}(s) = R_o \cdot \frac{(g_m + sC_{in}) C_H}{R_o [C_L C_{in} + C_{in} C_H + C_H C_L] + g_m R_o C_H + C_H + C_{in}}$$

$$g_m R_o C_H \gg C_H C_{in}$$

$$\approx \frac{(g_m + sC_{in}) C_H}{(C_L C_{in} + C_{in} C_H + C_H C_L)s + g_m C_H}$$

$$\tau_{amp} = \frac{C_L C_{in} + C_{in} C_H + C_H C_L}{g_m C_H}$$


Single-pole opamp

$$\omega_{un} = \frac{g_m}{C_L}$$

$$C_{in} \ll C_L, C_H, \quad \tau_{amp} \approx \frac{C_L}{g_m} = \frac{1}{\omega_{un}}$$


minimize C_{in}
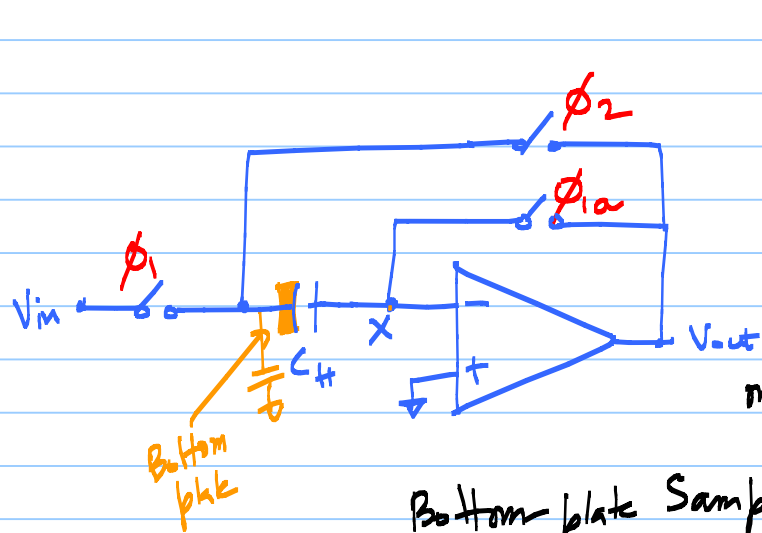
$$f_{un} = \beta \cdot f_{un} \leftarrow \begin{matrix} C_L \\ \frac{C_H}{C_H + C_{in}} \end{matrix}$$




Bottom plate Sampling

minimize C_{in}

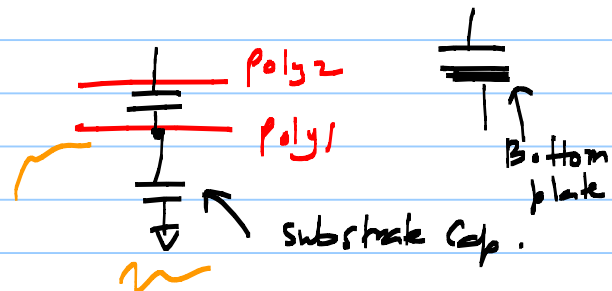


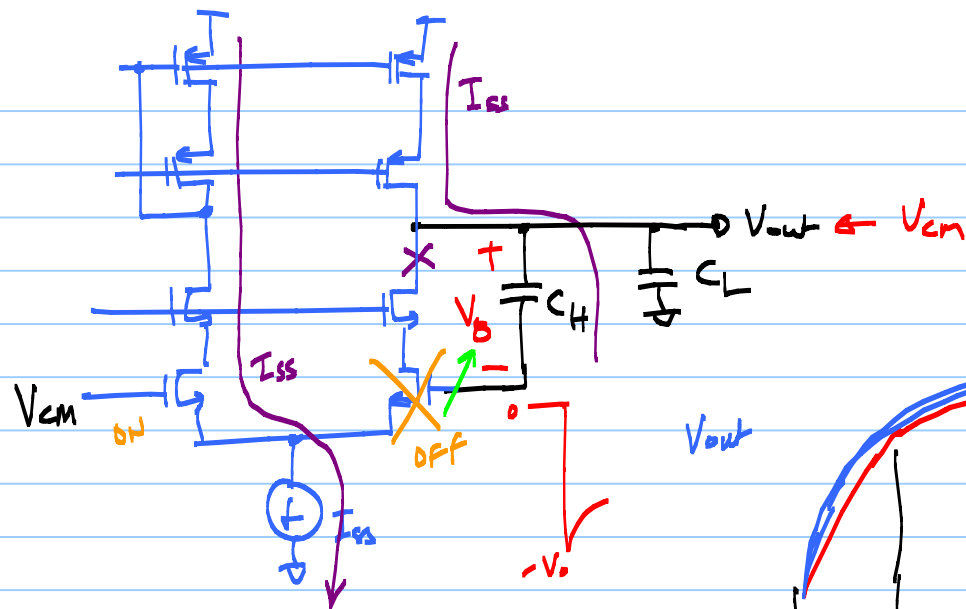* Substrate noise
* more $C_{poly-sub}$ cap.






$$V_{out} = \frac{I_{ss}}{C_L} \quad \text{slewing}$$
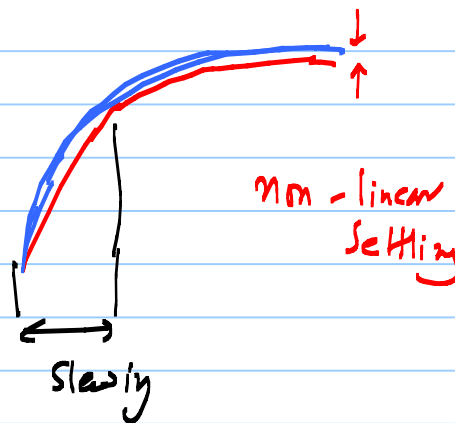
$$\cancel{g_m V_{in}} \quad \text{Linear}$$




Limit slewing period to $\frac{1}{4} T_{settle}$
 $\leq \frac{T}{8}$

Inverting Amplifier

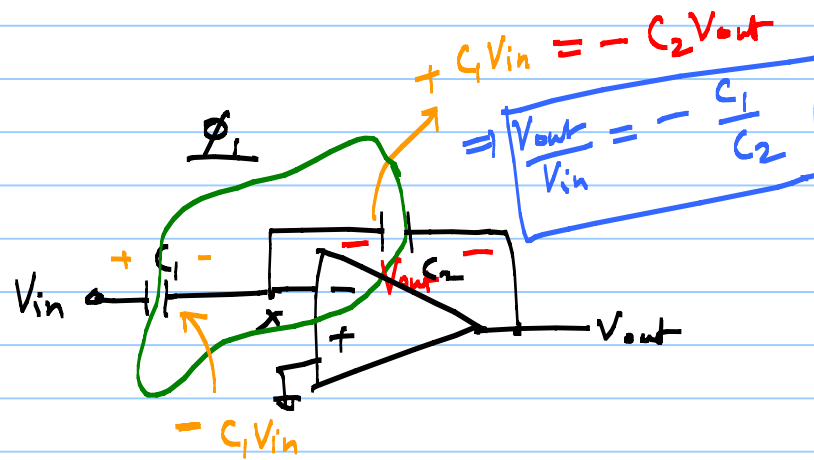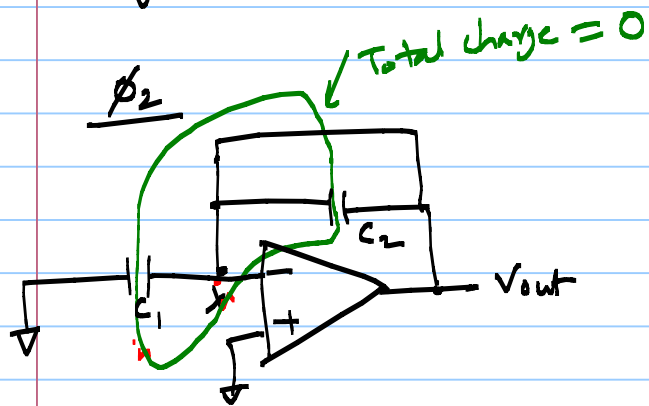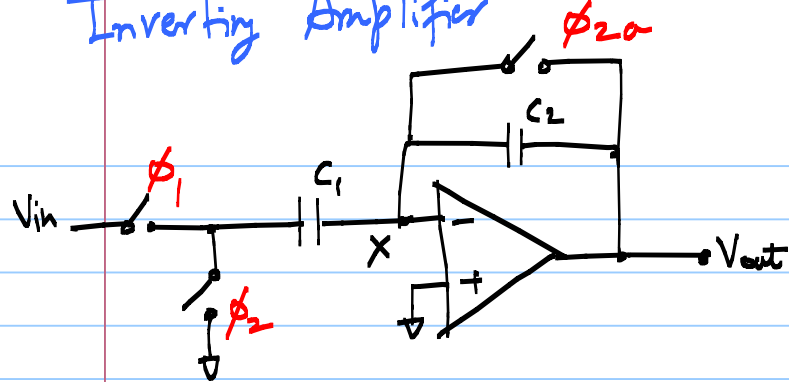

flip the sampling phase

Non-Inverting Amplifier

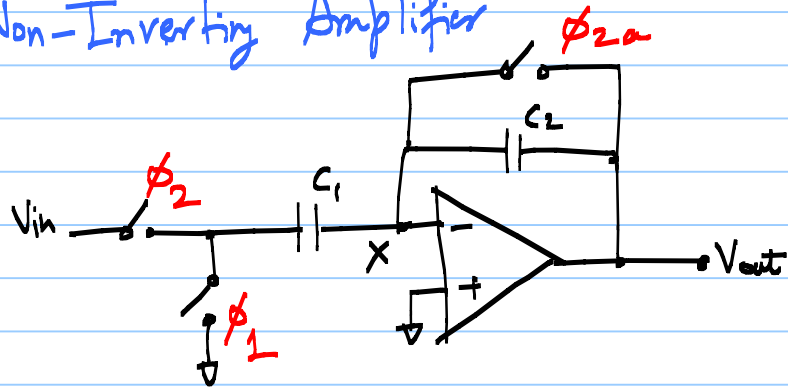

$$V_{out} = + \frac{C_1}{C_2} V_{in}$$