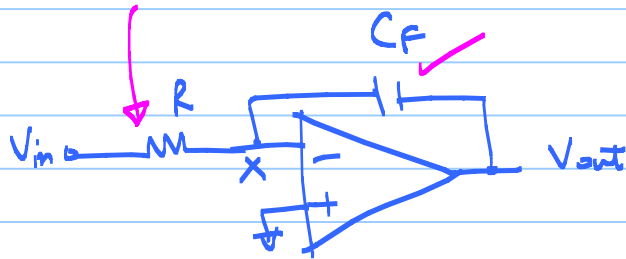


ECE 614 - Lecture 18


Note Title

11/1/2012




$$\frac{V_{out}}{V_{in}}(s) = -\frac{1}{s R C_F} = -\frac{\omega_z}{s}$$

CT integrator

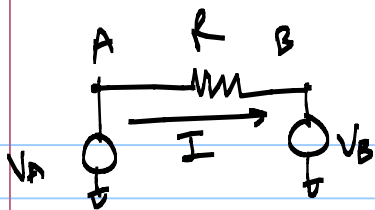

$$I = \frac{V_A - V_B}{R}$$

↑ avg charge transferred from A to B

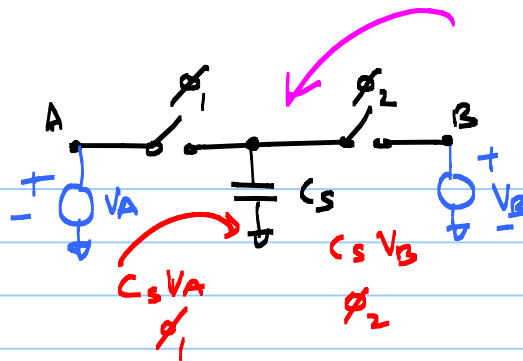



charge transferred from A to B

$$\Delta Q = C_S (V_A - V_B)$$

$$I_{av} = \frac{\Delta Q}{T_S} = \frac{C_S}{T_S} (V_A - V_B)$$

switched capacitor resistor (SCR)

$$R = \frac{1}{f_s C}$$

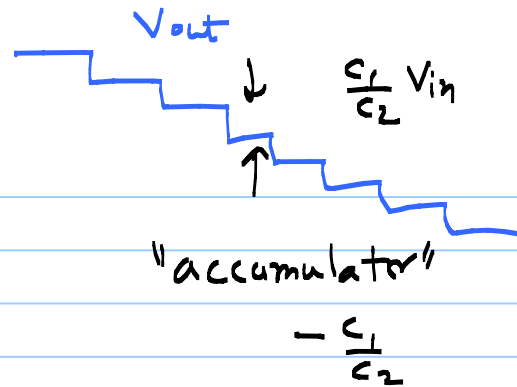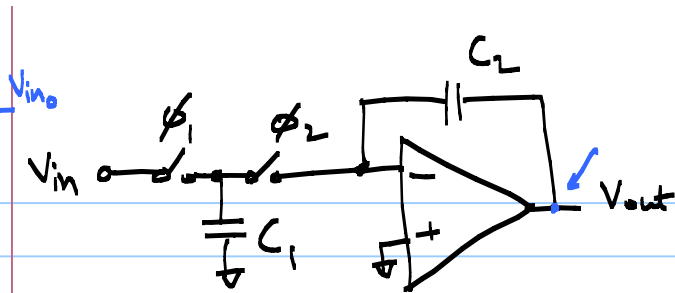

In every clock cycle

$$V_{out}[nT_s] = V_{out}[(n-1)T_s] - \frac{C_1}{C_2} \cdot V_{in}[(n-1)T_s]$$

$$\rightarrow V_{out}[n] = V_{out}[n-1] - \frac{C_1}{C_2} V_{in}[n-1]$$

$$V_{out}(z) = z^{-1} V_{out} - \frac{C_1}{C_2} z^{-1} V_{in}(z)$$

$$\Rightarrow \frac{V_{out}}{V_{in}}(z) = -\frac{C_1}{C_2} \left(\frac{z^{-1}}{1-z^{-1}} \right)$$

$$G_{ZI} = -\frac{C_1}{C_2}$$

DSP
delaying integrator/accumulator

DT equations


↓
change
Conservation
in the
circuit

z-transforms
DTFT -

↓

DFT

← FFT algorithm →

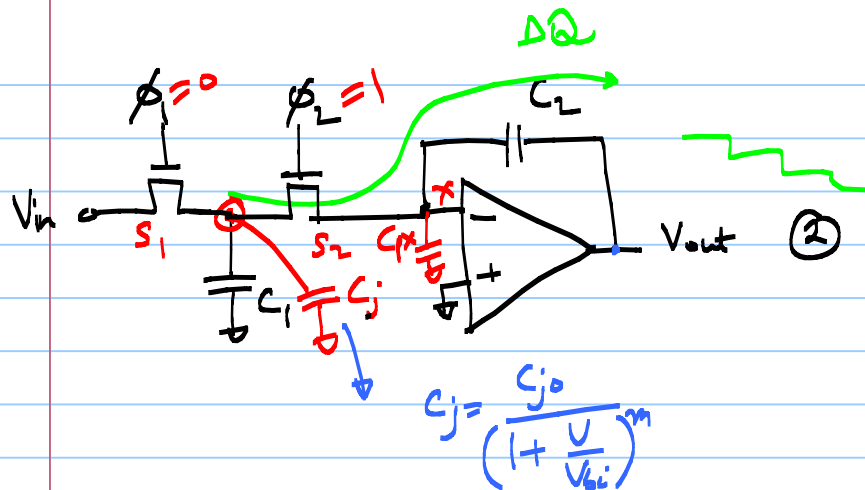

- ① input-dependent charge injection
due to S_1
↳ nonlinearity in the output

"Parasitic-Sensitive Integrator"


* charge stored in cap C_j

$$q_{Cj} = \int_0^{V_{in}} C_j \cdot dV = \int_0^{V_{in}} \frac{C_{j0}}{\left(1 + \frac{V}{V_{bi}}\right)^m} dV$$


↳ $q_{Cj} \neq C_j V_{in} = f_{NL}(V_{in})$

↳ transferred to C_2
⇒ non linearity in the output


Parasitic Insensitive Integrator !

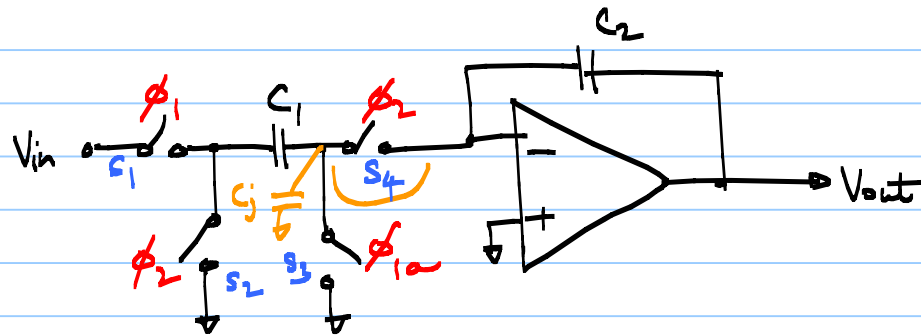

ϕ_1 (sampling phase)


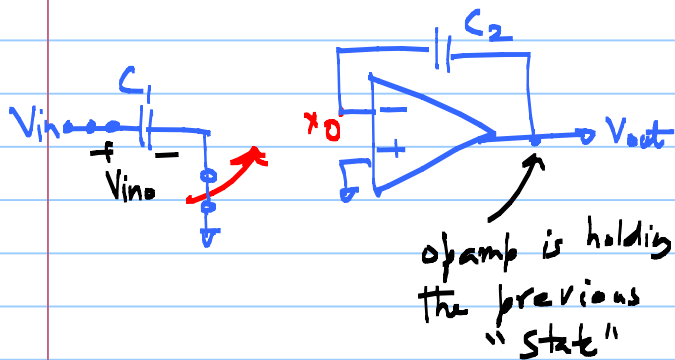


ϕ_2 (integration phase)

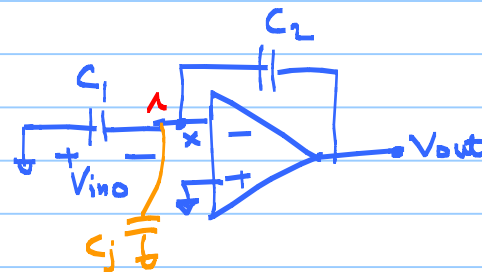

* Node x is a virtual ground
 q_{Cj} is negligible
 $\Rightarrow$ negligible nonlinearity in the output

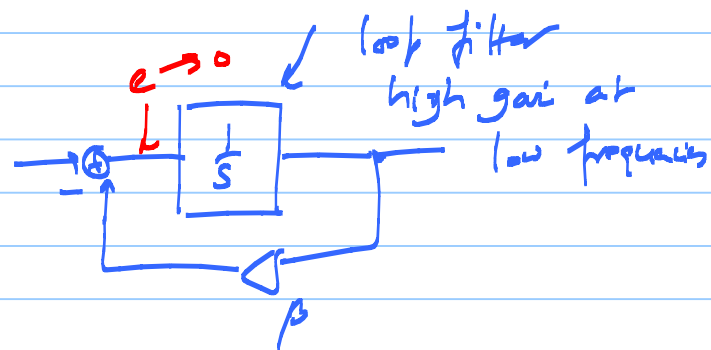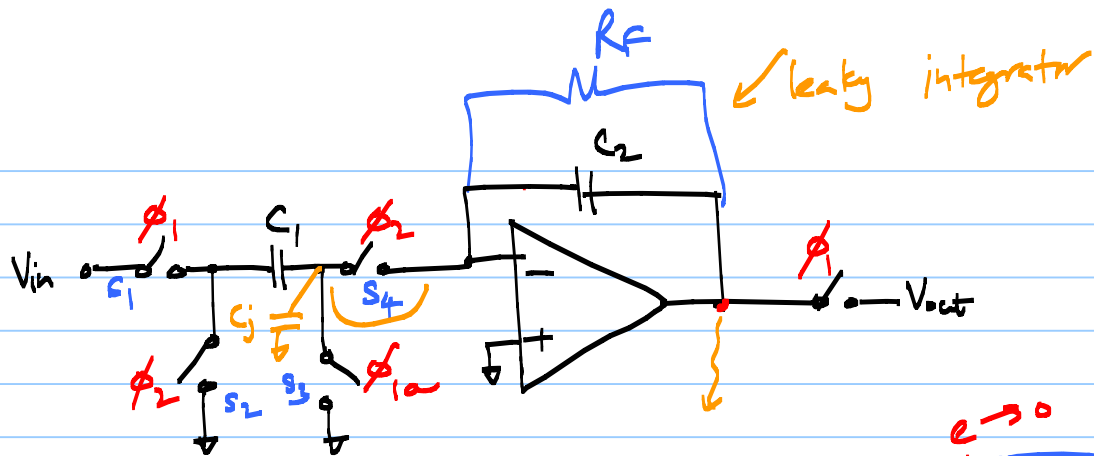* Charge injected by S_4 is indep
of V_{in}



$s[n]$

$$\frac{z^{-1}}{1-z^{-1}}$$




$$e^{-\lambda t}$$

$\frac{1}{s}$


$$\frac{1}{s-\lambda}$$

Delaying integrator

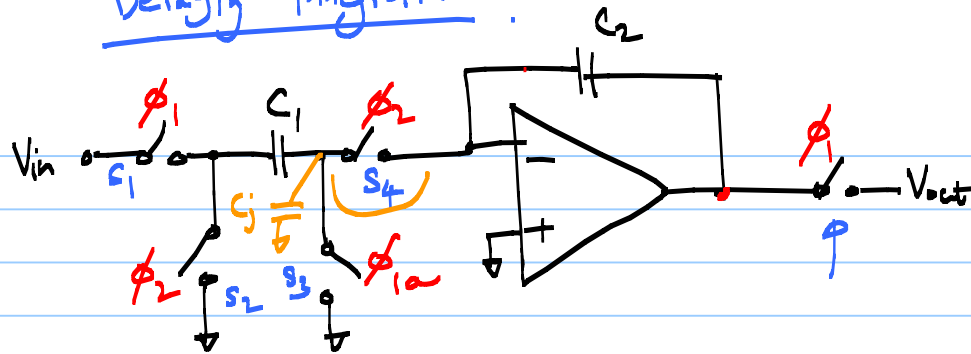

$$z^{-1}$$

Delay-free integrator

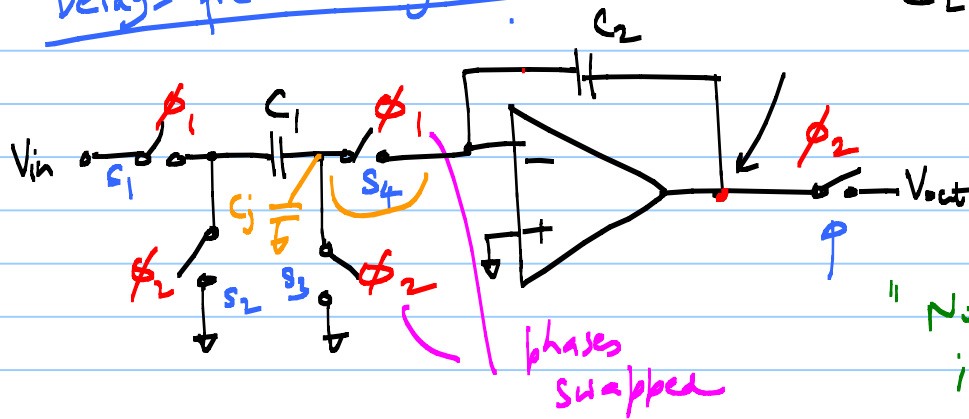

$$-\frac{C_1}{C_2} \cdot \frac{1}{1-z^{-1}}$$

$$-\frac{C_1}{C_2} \frac{z^{-1/2}}{1-z^{-1}}$$

"No delay-free loops
in DT system"


Sampling $\leftarrow T_{s/2} \leftarrow$ RC time constant of switch

Integration phase $\leftarrow T_{s/2} \leftarrow$ opamp has to settle
 $\downarrow$
 A_{oc}, f_{in}, SR


$f_m \rightarrow$ Slewing allowed only for 25% of settling time
 $T_{s/8}$

$$* \quad H(z) = G_I \cdot \frac{z^{-1}}{1-z^{-1}}$$

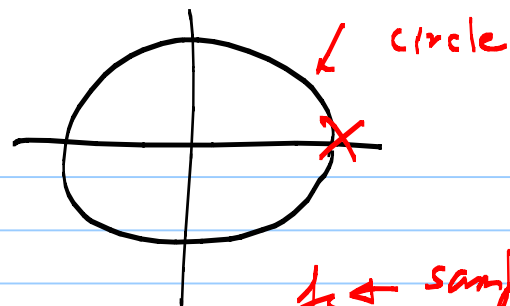$\downarrow$ $\downarrow$
 $-\frac{c_1}{c_2}$ $\frac{1}{z-1}$



$f_s \leftarrow$ sampling frequency

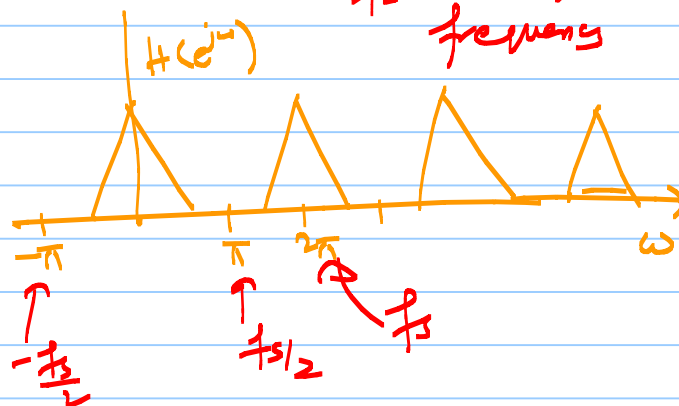

DTFT $\rightarrow$

$$* \quad H(e^{j\omega}) = G_I \cdot \frac{e^{-j\omega}}{1-e^{-j\omega}}$$

$\uparrow$ periodic with period 2π

$$\Rightarrow G_I \cdot \frac{e^{-j\omega}}{e^{-j\omega/2} (e^{+j\omega/2} - e^{-j\omega/2})}$$

$$= e$$


$$= \frac{e^{-j\omega/2}}{\underbrace{e^{+j\omega/2} - e^{-j\omega/2}}_{2 \sin \frac{\omega}{2}}} = \frac{e^{-j\omega/2}}{2 \sin(\omega/2)}$$

$$\frac{e^{j\theta} - e^{-j\theta}}{2} = \sin \theta$$

$$|H(e^{j\omega})| = \frac{1}{2 \sin(\omega/2)}$$

@ $\omega = \pi/2$
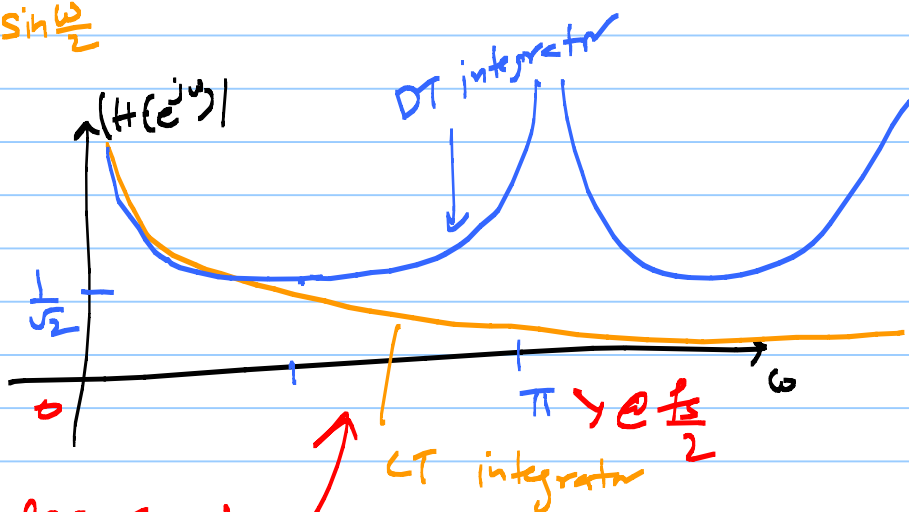
$$\frac{1}{2 \cdot \frac{1}{\sqrt{2}}} = \frac{1}{\sqrt{2}}$$



frequency response $\rightarrow$ PSS $\leftarrow f_s$
 $\rightarrow$ BAZ