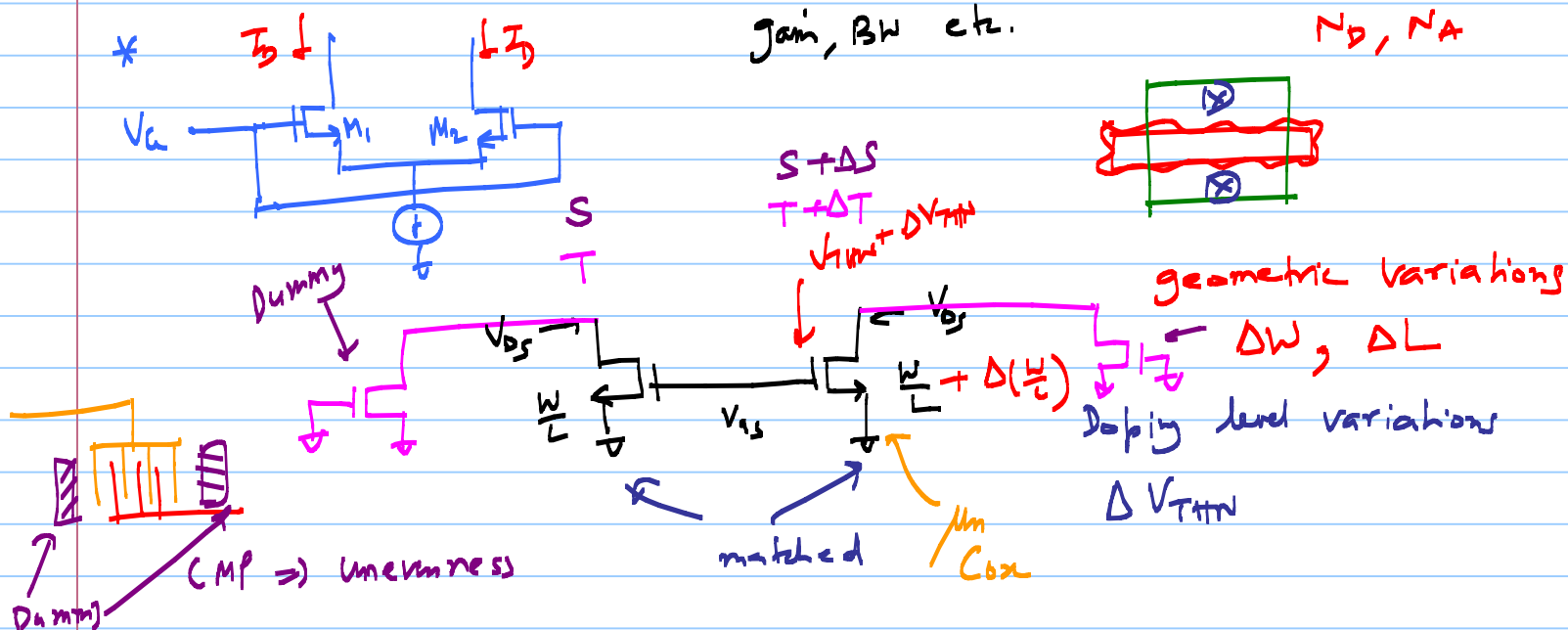


ECE 614 - Lecture 19

Note Title

11/8/2012

Mismatch and Offsets:



Study of Mismatch

① Identify mechanisms leading to mismatch between devices
→ measurements and characterization by the foundry


⇒ ② analyze the effect of device mismatch upon circuits

Mismatch leads

DC offsets

finite even-order distortion (FD
circuitry
also)

lower CM-rejection

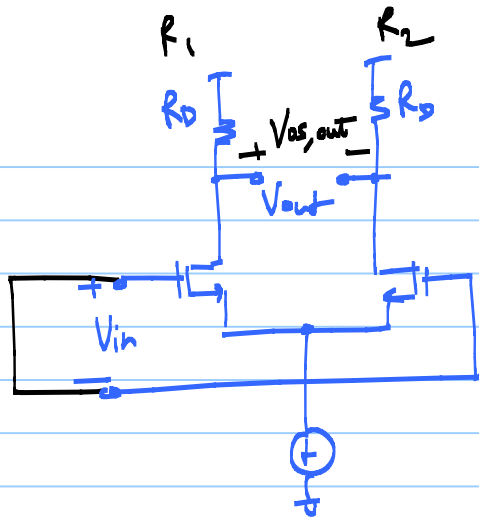


* with a DC offset


⇒ with $V_{in}=0$

$$V_{out} = V_{os, out}$$

* It's more meaningful to specify the input-referred offset voltage ($V_{os, in}$)

$$|V_{os, in}| = \frac{|V_{os, out}|}{|A_v|}$$

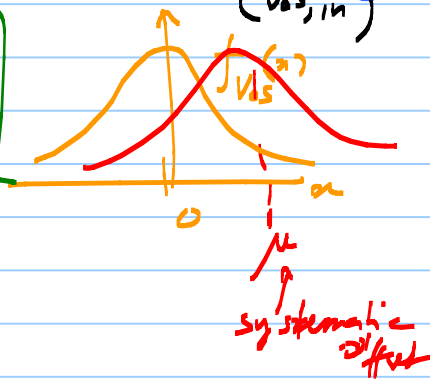

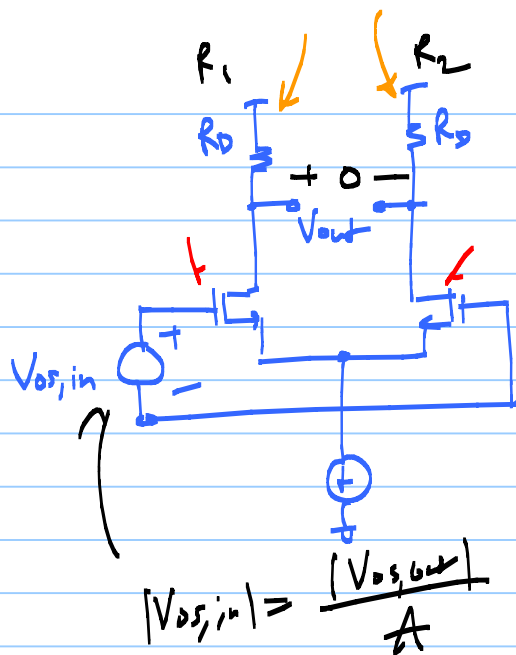

$$|V_{os,in}| = \frac{|V_{os,out}|}{A}$$


$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_G - V_{TH})^2 (1 + \lambda V_{DS})$$

$$\mu_n C_{ox} \frac{W}{L} V_{TH} \lambda$$

$$I_D \text{ \& } I_D + \Delta I_D$$

$$\frac{\frac{\Delta W}{W}}{\frac{\Delta L}{L}} = \frac{\Delta(W/L)}{(W/L)}$$
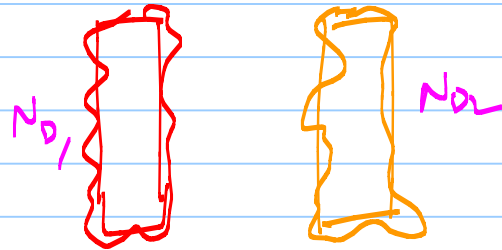
$$\text{Large } WL \Rightarrow \Delta(W/L) \downarrow$$



Geometric Variation

Palgrom's paper:

$$\underline{\Delta V_{THN}} = \frac{A_{V_{THN}}}{\sqrt{WL}}$$

$$\sigma_{\Delta V_{THN}}^2 \propto \frac{1}{WL}$$

$$D(\mu_n \text{ Cox } \frac{W}{L}) = \frac{A_{\mu}}{\sqrt{WL}}$$



$$\sigma_{\mu/\beta}^2 \propto \frac{1}{WL}$$

for large $WL \rightarrow$ variations experience
"averaging"


* C5 process $L_{min} = 0.6 \mu m$

$$A_{V_{THN}} \approx \alpha \cdot I_{D0} = 10 mV \quad \text{for } I_{D0} = 100 A^\circ$$
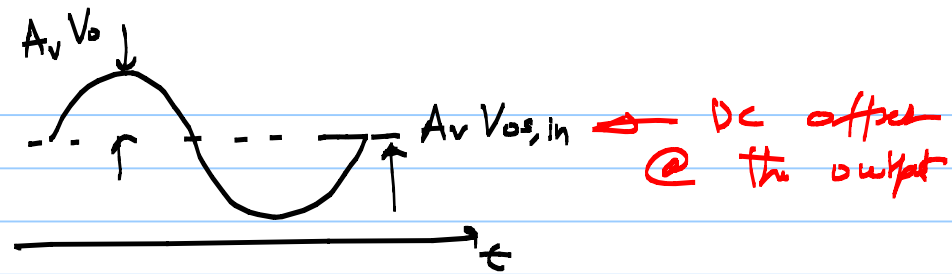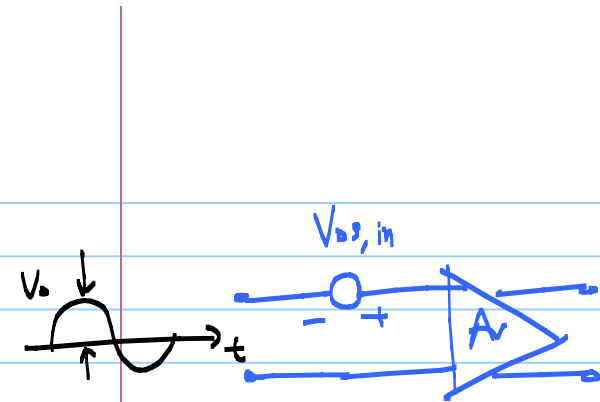
$$\frac{100 \mu m}{0.6 \mu m} \Rightarrow \sigma_{\Delta V_{THN}} = 1.4 mV$$




DC offset @ the output

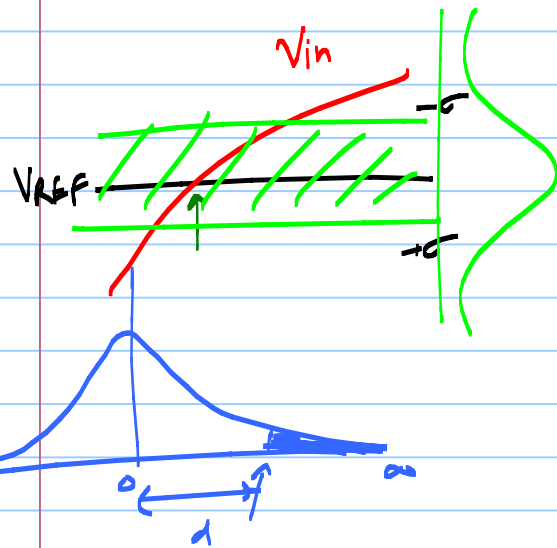

Here, the $V_{os,in}$ imposes a lower bound on the minimum $V_{in} - V_{ref}$ that can be easily detected.

$$p_E = Q\left(\frac{1}{\sigma}\right) = Q\left(\frac{|V_{in} - V_{ref}|}{\sigma_{V_{os,in}}}\right)$$

$\uparrow$ error $\uparrow$

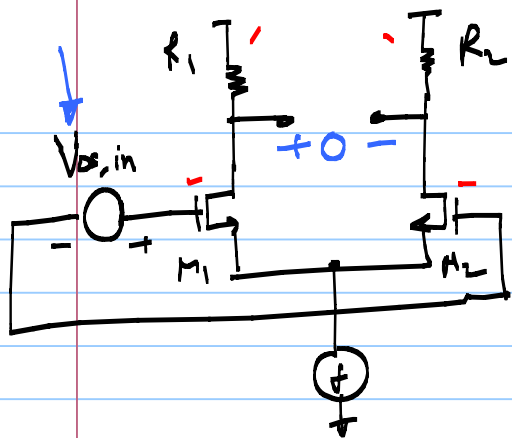

Left

$$\left(\frac{W}{L}\right)_1 = \frac{K}{L}$$

$$V_{TH1} = V_{THN}$$

$$R_1 = R_D$$

$$I_{D1} = I_D \quad \lambda = \gamma = 0$$

$$V_{out} = 0$$

$$I_{D1} R_1 = I_{D2} R_2$$

$$\Rightarrow I_{D1} \neq I_{D2}$$

Right

$$\left(\frac{W}{L}\right)_2 = \frac{W}{L} + \Delta\left(\frac{W}{L}\right)$$

$$V_{TH2} = V_{THN} + \Delta V_{THN}$$

$$R_2 = R_D + \Delta R_D$$

$$I_{D2} = I_D + \Delta I_D$$

$$V_{os, in} = V_{as_1} - V_{as_2}$$

$$= \sqrt{\frac{2I_{D1}}{\mu_n C_{ox} \left(\frac{W}{L}\right)_1}} + V_{THN1} - \sqrt{\frac{2I_{D2}}{\mu_n C_{ox} \left(\frac{W}{L}\right)_2}} - V_{THN2}$$

$$= \sqrt{\frac{2}{\mu_n C_{ox}}} \left[\sqrt{\frac{I_D}{W/L}} - \sqrt{\frac{I_D + \Delta I_D}{\frac{W}{L} + \Delta\left(\frac{W}{L}\right)}} \right] - \Delta V_{THN}$$

$$= \sqrt{\frac{2I_D}{\mu_n C_{ox} \frac{W}{L}}} \left[1 - \sqrt{\frac{1 + \frac{\Delta I_D}{I_D}}{1 + \frac{\Delta(W/L)}{W/L}}} \right] - \Delta V_{THN} \rightarrow \textcircled{1}$$

V_{ov}
 $= V_{as} - V_{THN}$

Assume $\frac{\Delta I_D}{I_D} \ll \frac{\Delta(W/L)}{W/L} \ll 1$

$$\epsilon \ll 1 \Rightarrow \sqrt{1+\epsilon} \approx 1 + \epsilon/2$$

$$\left(\sqrt{1+\epsilon}\right)^{-1} \approx 1 - \epsilon/2$$

$$V_{os, in} = V_{ov} \left\{ 1 - \left(1 + \frac{\Delta I_D}{I_D} \right) \left[1 - \frac{\Delta(W/L)}{2(W/L)} \right] \right\} - \Delta V_{THW}$$

$$(I_D + \Delta I_D)(R_D + \Delta R_D) = I_D R_D + R_D \Delta I_D + I_D \Delta R_D$$

$$\left(I_{D1} R_{D1} = I_{D2} R_{D2} \right) \quad V_{out} = 0$$

$$\Rightarrow \frac{\Delta I_D}{I_D} = - \frac{\Delta R_D}{R_D}$$

$$V_{os, in} = \frac{V_{ov}}{2} \left[\frac{\Delta R_D}{R_D} + \frac{\Delta(W/L)}{(W/L)} \right] - \Delta V_{THW}$$

$\downarrow$
 $(V_{GS} - V_{THW})$
 $\uparrow$
 directly referred to the input


$$V_{os, in} = \frac{V_{ov}}{2} \left[\frac{\Delta R_D}{R_D} + \frac{\Delta(W/L)}{(W/L)} \right] - \Delta V_{THN}$$

Contribution of $\Delta(W/L)$ depends upon the V_{ov}

ΔV_{THN} is directly seen at the input

$E(\cdot)^2$


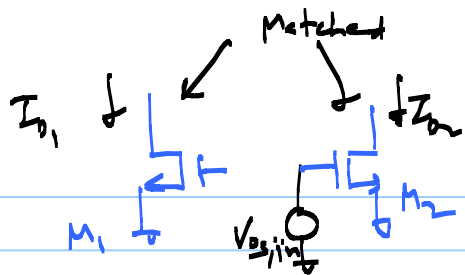
$$\sigma_{V_{os, in}}^2 = \left(\frac{V_{ov}}{2} \right)^2 \left[\frac{\sigma_{\Delta R_D}^2}{R_D^2} + \frac{\sigma_{\Delta W/L}^2}{(W/L)^2} \right] + \sigma_{\Delta V_{THN}}^2$$



$$I_{D1} = I_{D2}$$

$$V_{O_{s,in}} = \frac{V_{ov}}{2} \left[\frac{\Delta W/L}{(W/L)} \right] + \Delta V_{T+TN}$$

$\frac{\Delta V}{\Delta I}$

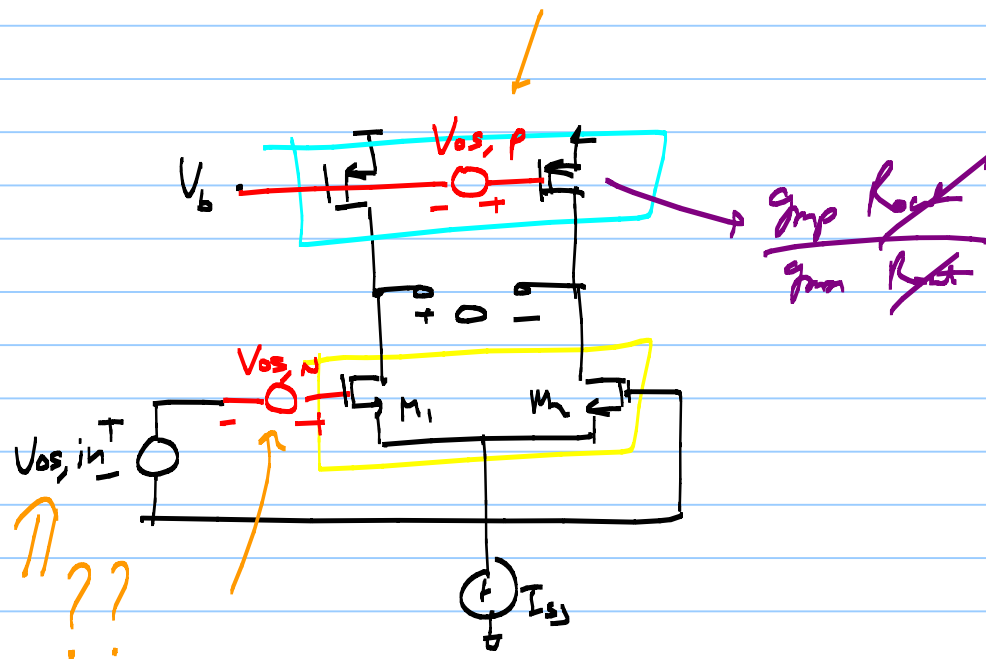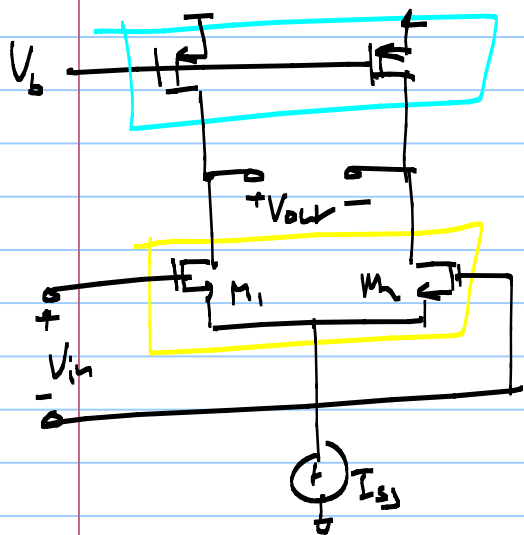

$$V_{os,n} = \frac{(V_{ds} - V_{thn})}{2} \left[\frac{\Delta(w/L)}{(w/L)} \right]_n + \Delta V_{thn}$$

$$V_{os,p} = \frac{(V_{ds} - V_{thp})}{2} \left[\frac{\Delta(w/L)}{w/L} \right]_p + \Delta V_{thp}$$

from noise analysis results

$$V_{os,in} = V_{os,n} + V_{os,p} \cdot \left(\frac{g_{mp}}{g_{mn}} \right)$$

$$\sigma_{V_{os,in}}^2 = \sigma_{V_{os,n}}^2 + \frac{g_{mp}^2}{g_{mn}^2} \cdot \sigma_{V_{os,p}}^2$$

$$f(V_{os}, w/L)$$

$$g_{mn} \uparrow, g_{mp} \downarrow$$