
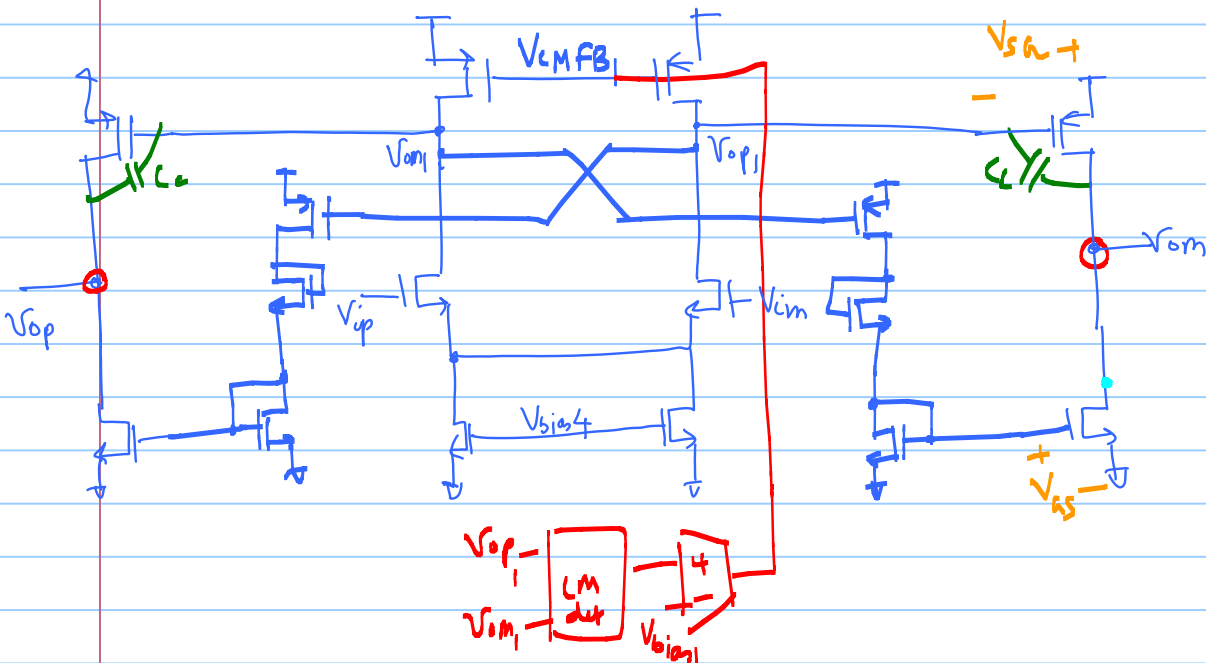




ECE 614 - Lecture 6




Note Title



9/13/2012

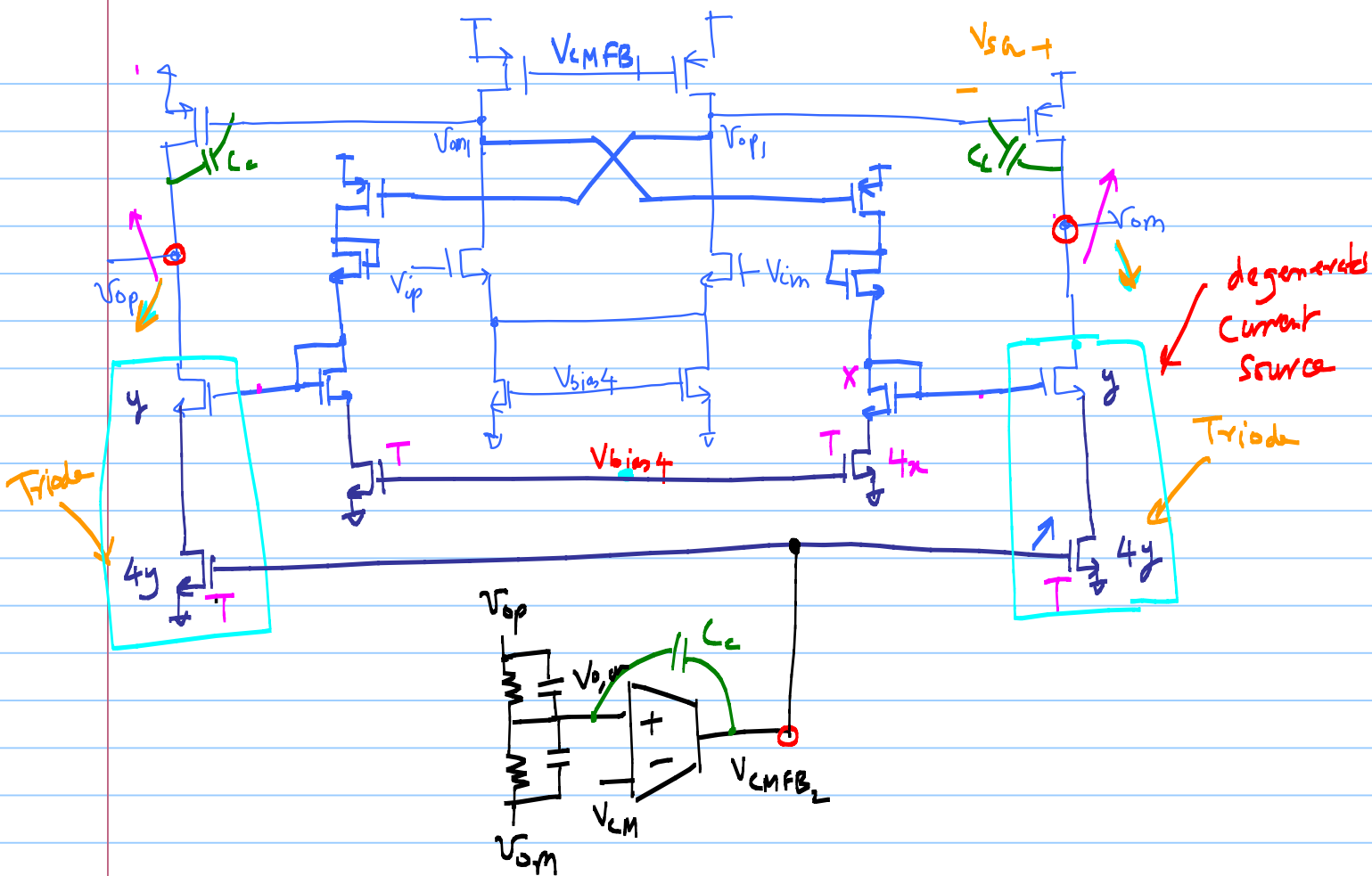



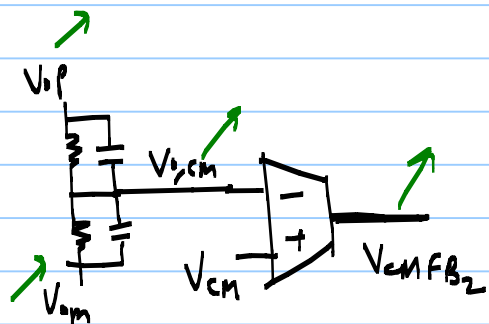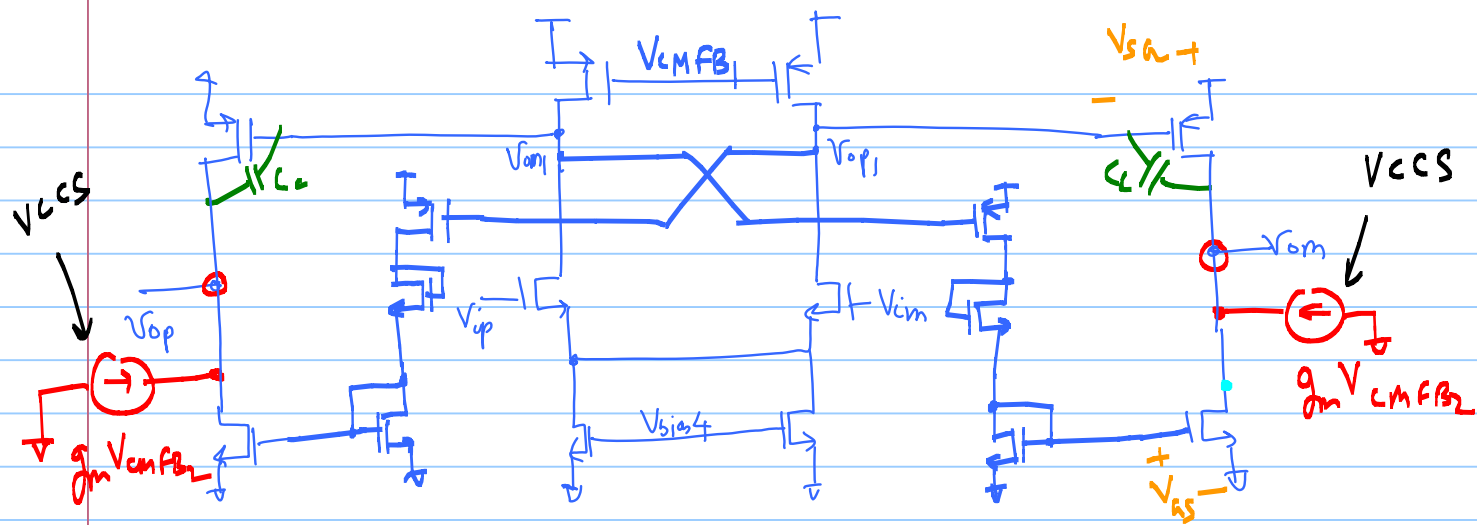


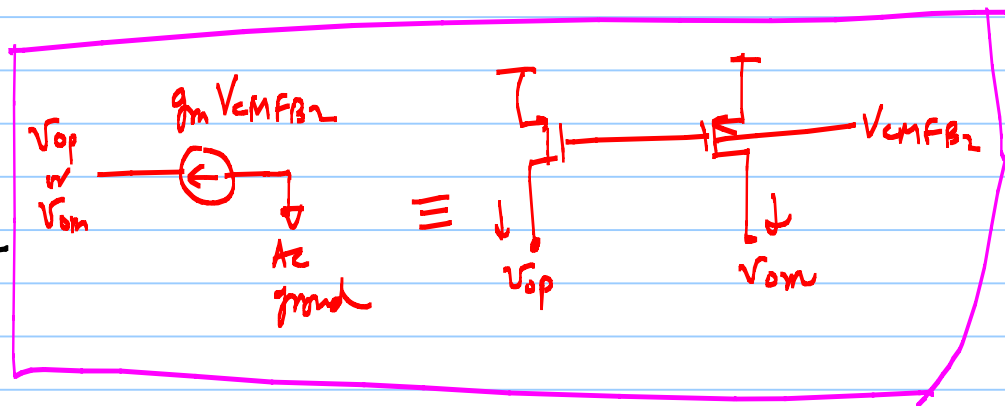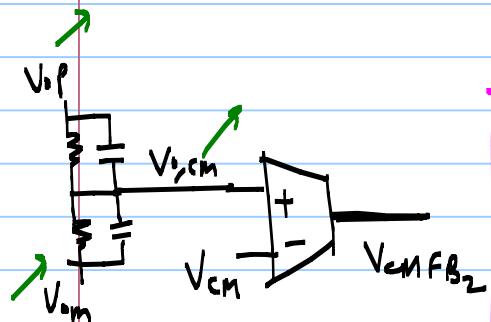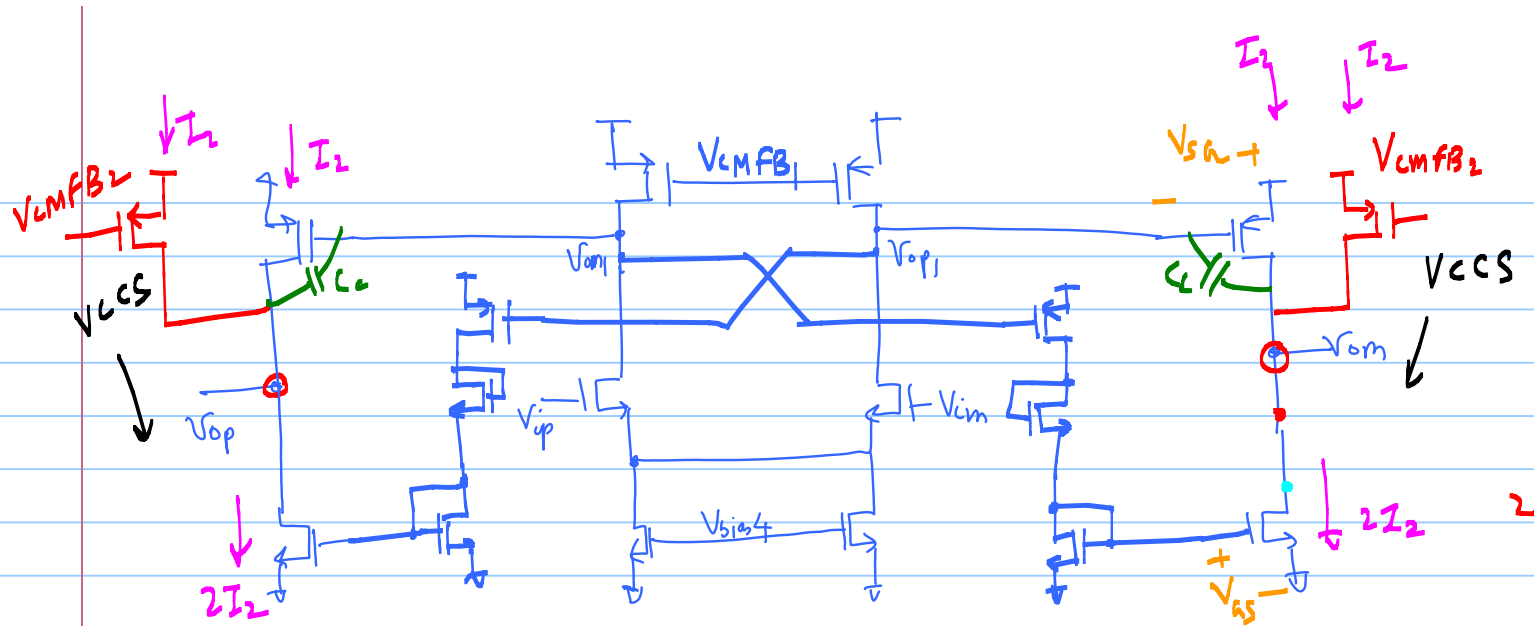

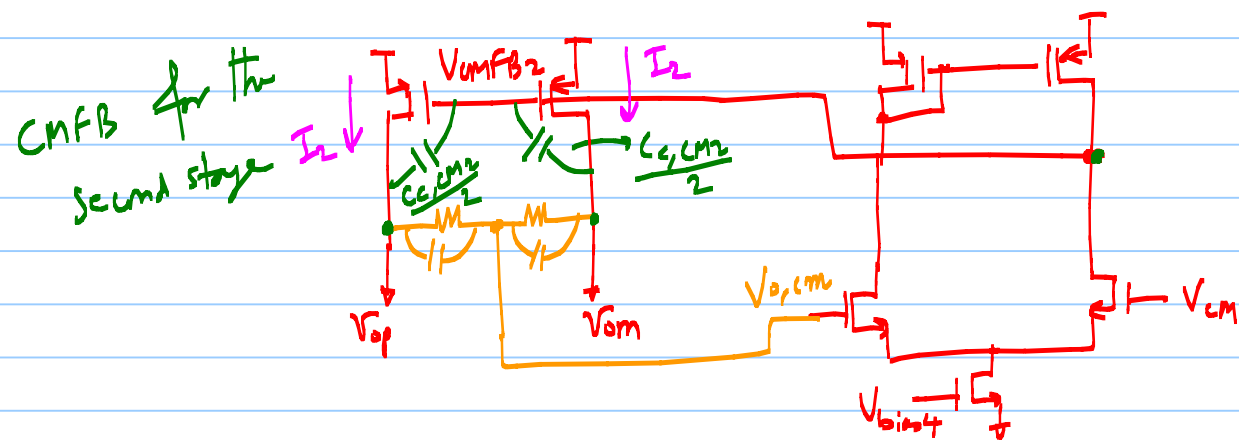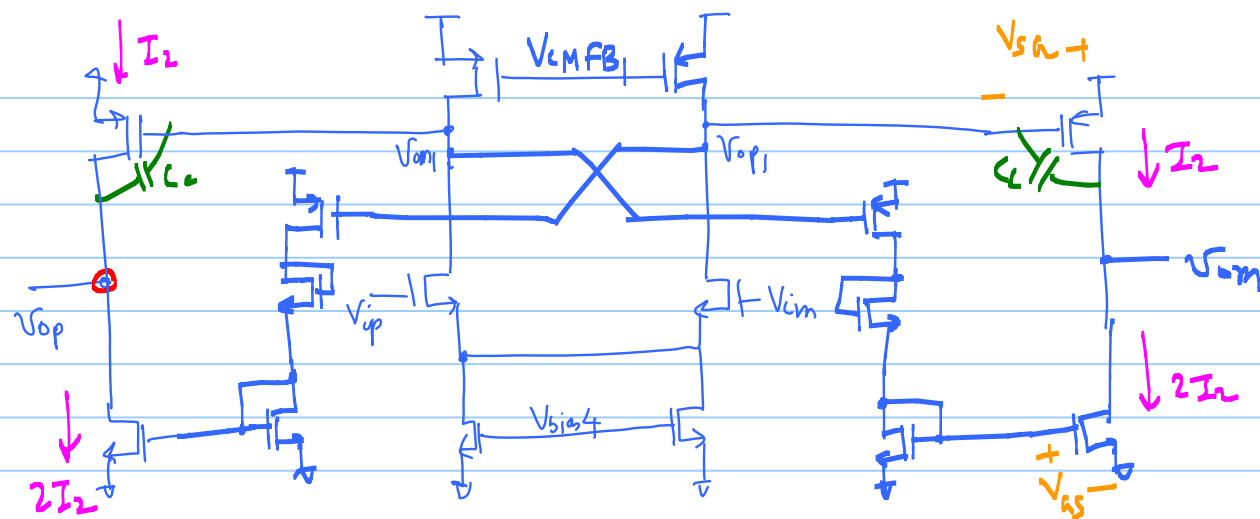

CM circuit for the 2nd stage

AC

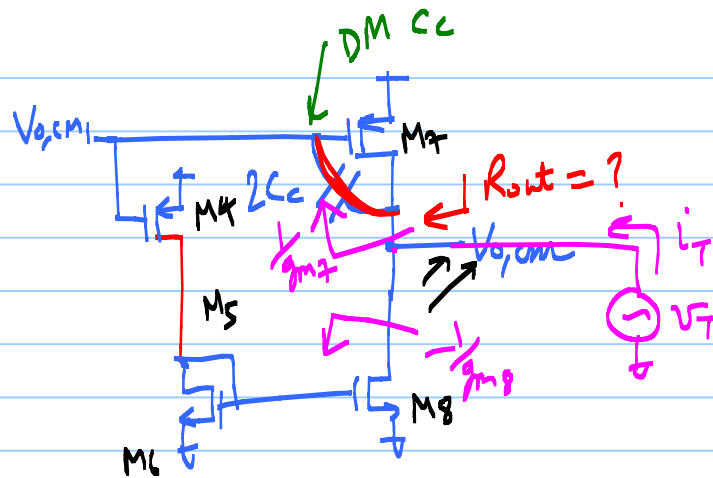

@ high frequencies C_c shorts



$$g_{m7} = g_{m8}$$

$$Re(R_{out}) < 0 \Rightarrow \text{+ve feedback}$$

↳ leads to instability


$$g_{m7} \neq g_{m8}$$

$$g_{m7} = 2g_{m8}$$

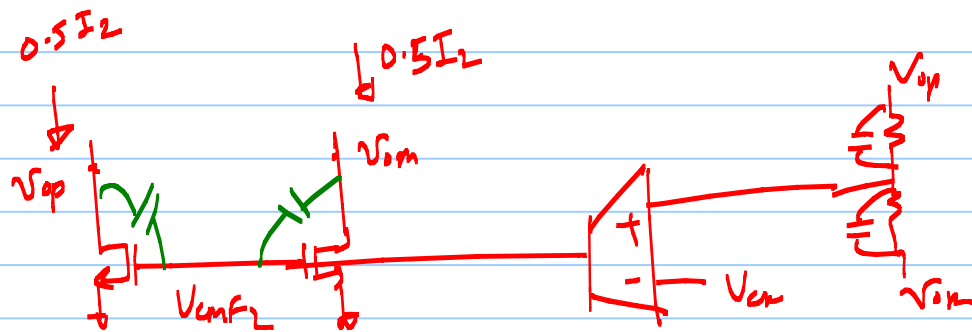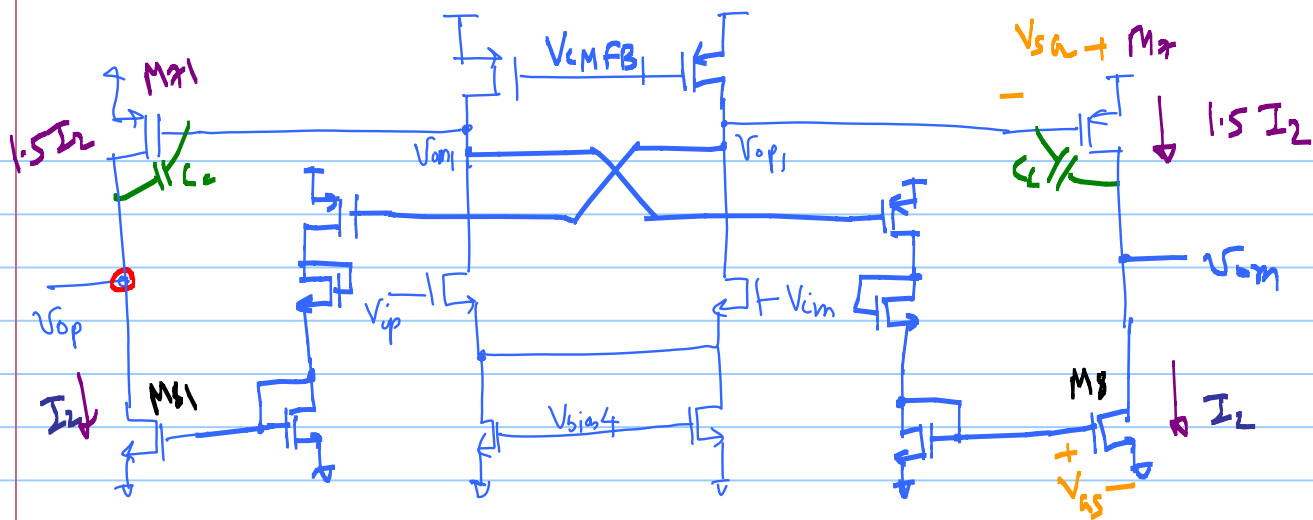


$R_{out} > 0$


Simulation

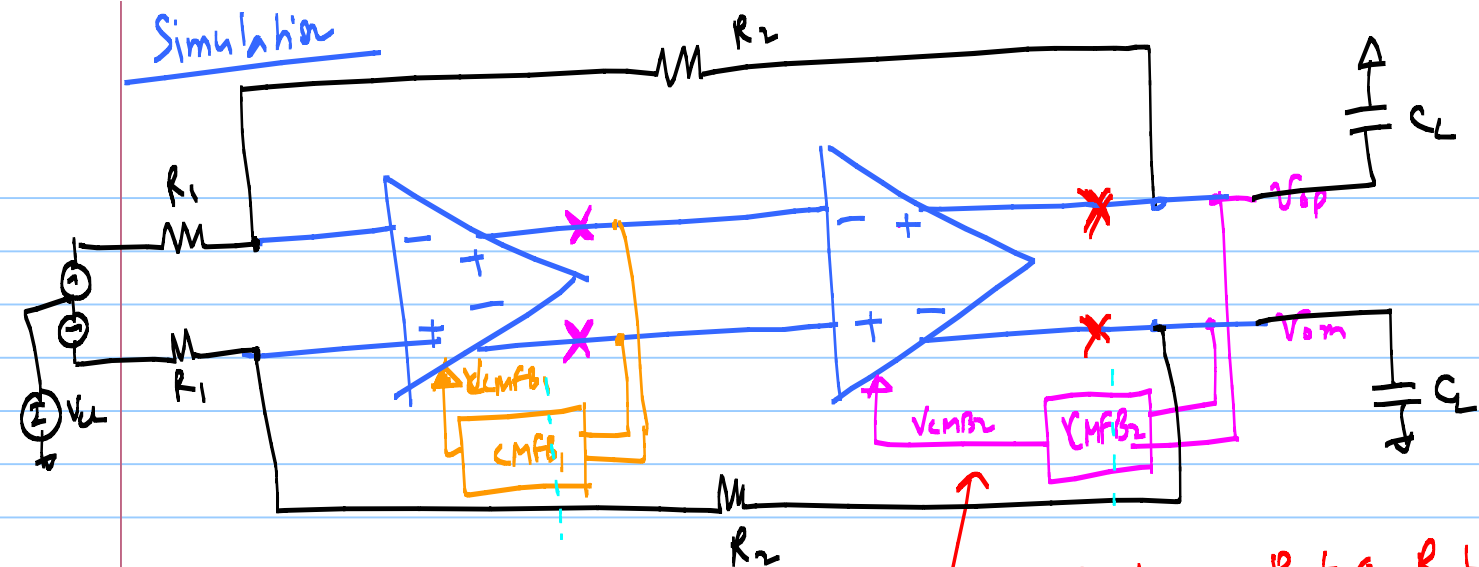


CMFB probe ← Return Ratio Analysis

Break both CM & DM loops



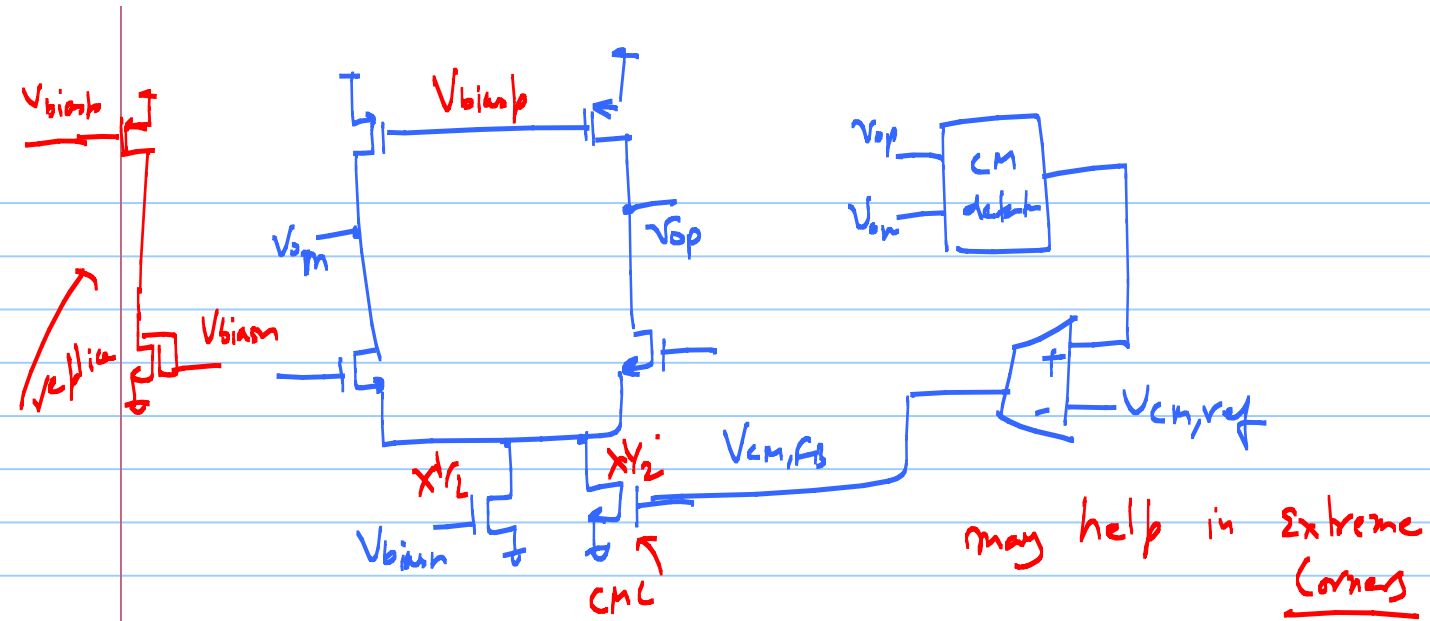


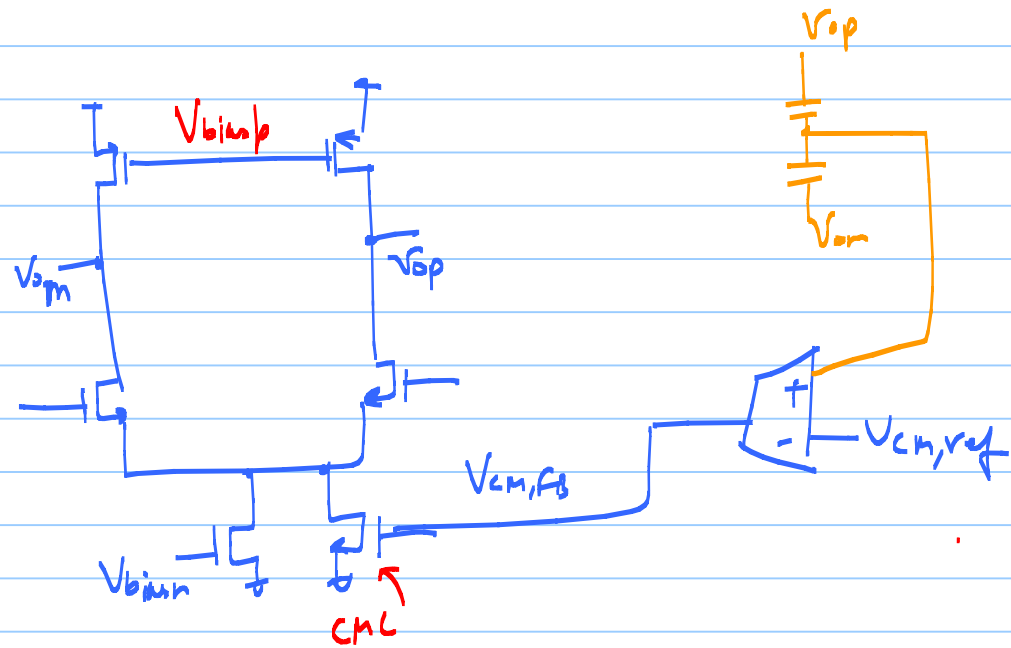

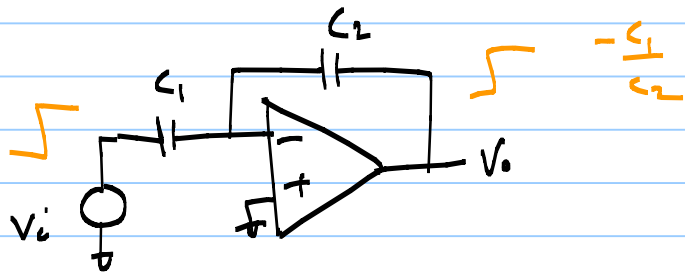Introduction to Switched Capacitor Amplifier




No DC feedback
path

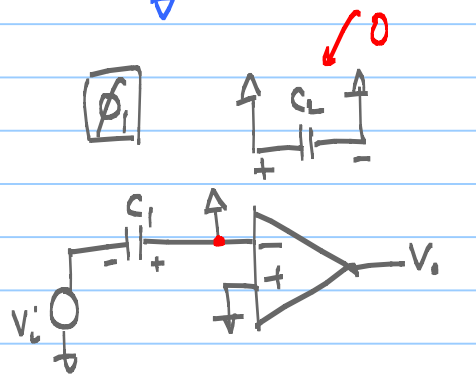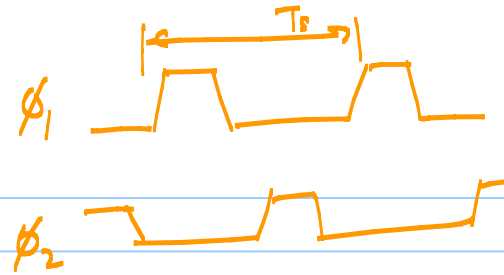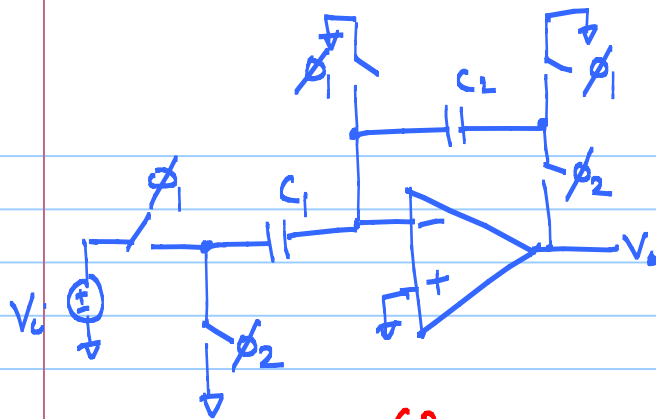

V_i is sampled on C_1

$$Q_i = -V_i C_1$$

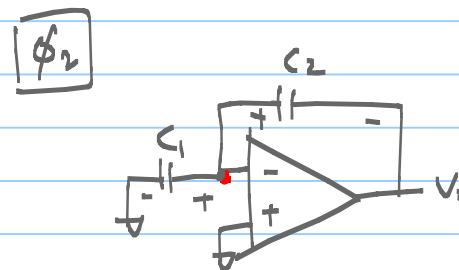

$$Q_f = 0 \cdot C_1 + V_o C_2 = -V_o C_2$$

charge is transferred from C_1 to C_2

$$Q_i = Q_f$$

$$\Rightarrow \boxed{\frac{V_o}{V_i} = -\frac{C_1}{C_2}}$$