




ECE 614 - Lecture 10

Note Title

9/25/2014






$\Rightarrow$

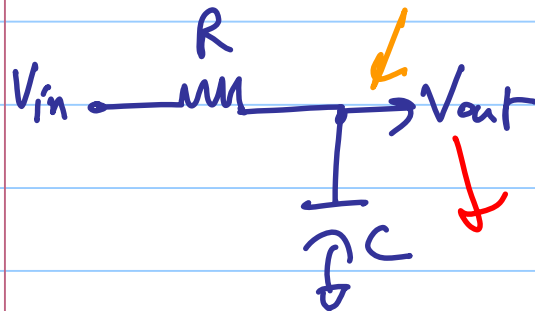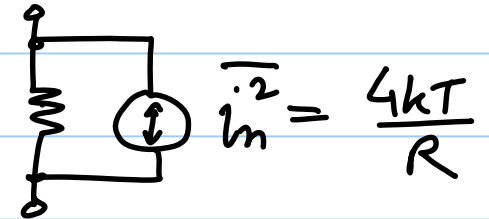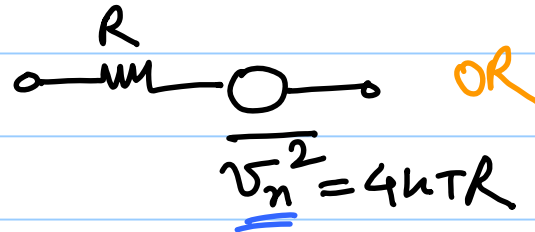

$$f_{3dB} = \frac{1}{2\pi RC}$$

$$V_{out,n,rms} = \sqrt{\frac{kT}{C}}$$

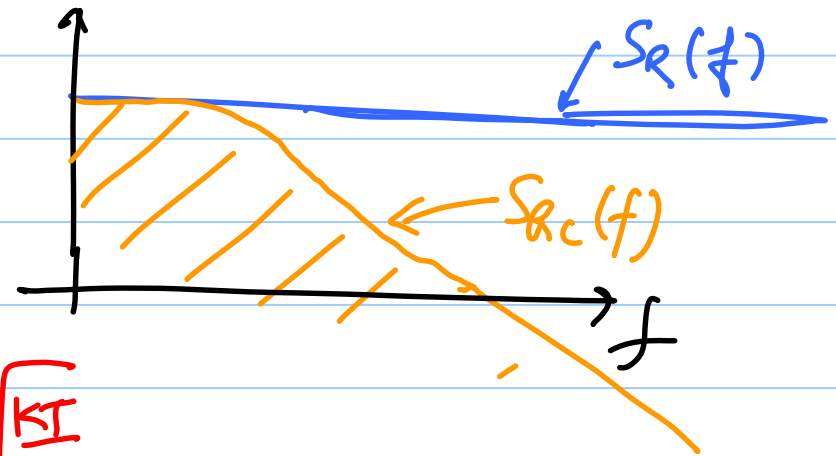

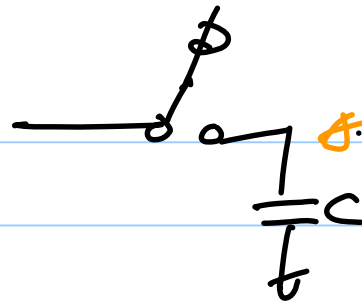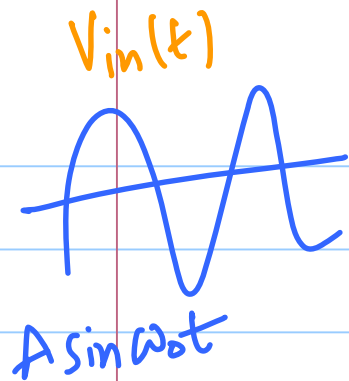

$V_{in}[nT_s]$
+

$V_{noise, rms} = \sqrt{\frac{kT}{C}}$

$$SNR = \frac{A^2/2}{kT/C} > 60 \text{ dB}$$

Quantizer $\Rightarrow$


$$SQNR = (6.02 N_{eff} - 1.76) \text{ dB}$$

$\uparrow$
10

$\geq 60 \text{ dB}$

MOSFET Noise
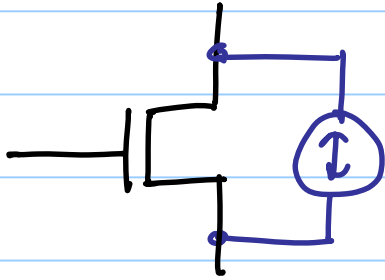
$$\text{Resistor symbol} \quad \frac{4kT}{R}$$



$$\overline{I_n^2} = 4kT\gamma g_m \quad \leftarrow \text{Thermal Noise}$$

$$\gamma = \underline{\underline{\frac{2}{3}}} \quad \text{for Long-channel}$$

$$\approx 2.5 \quad \text{for short-channel (180nm)}$$


$$\hookrightarrow f(V_{DS}) \leftarrow \text{also varies with } V_{DS}$$

$$\text{for handcalcs} \Rightarrow \overline{I_n^2} = \frac{8}{3} kT g_m \quad \text{for } \gamma = \frac{2}{3}$$


$$\underline{\underline{A_v^2}}_{Hz}$$

/home/pdks/IBM_PDK/8RF $\Leftarrow$ docs
Spice model

Ex. Max noise voltage from a MOSFET

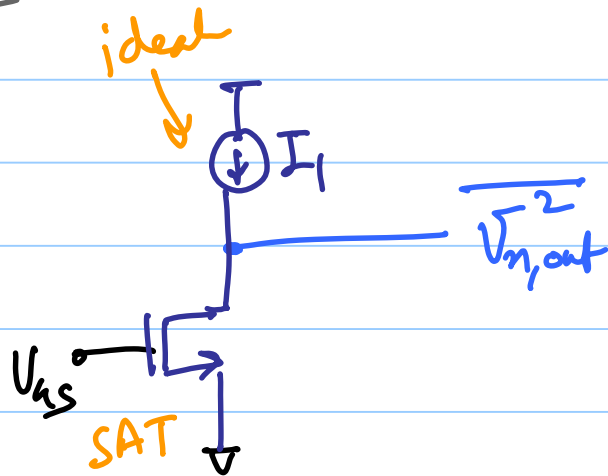


noise circuit


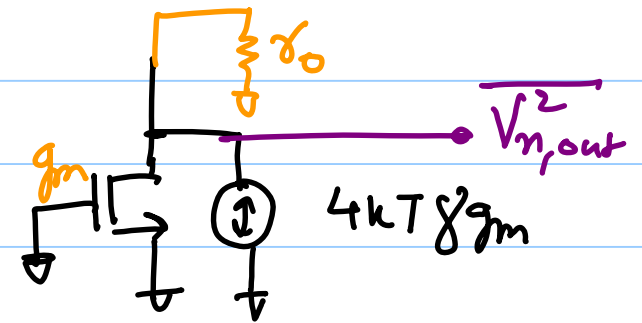


Noise
Power
density:

$$\overline{V_{n,out}^2} = \overline{I_n^2} \cdot r_o^2 = \frac{8}{3} kT g_m r_o^2$$

for constant r_o
minimize g_m

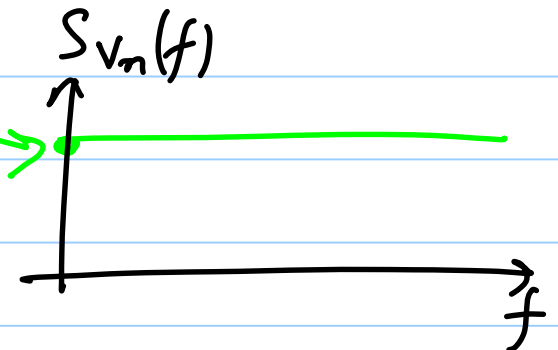

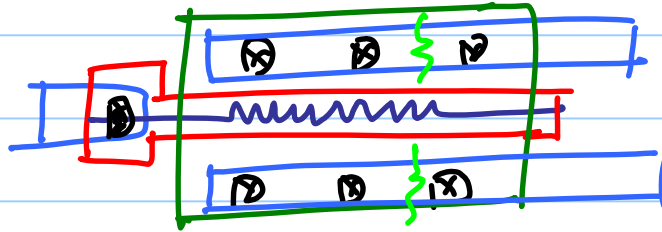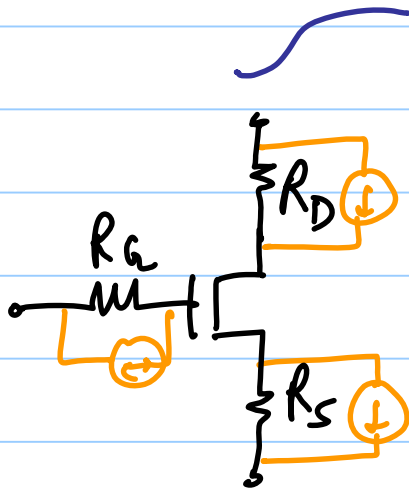


$$R_g = \frac{1}{3} R_{O,poly} \left(\frac{W}{L} \right)$$

↑ Distributed gate resistance



To minimize Noise from R_g

⇒ Multifinger layout

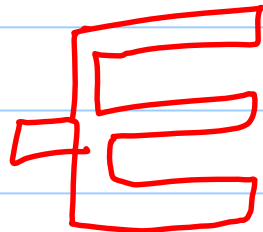


* We will neglect these thermal noise sources for simplicity.

flicker Noise :

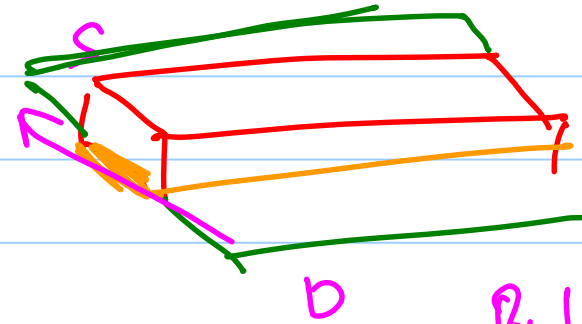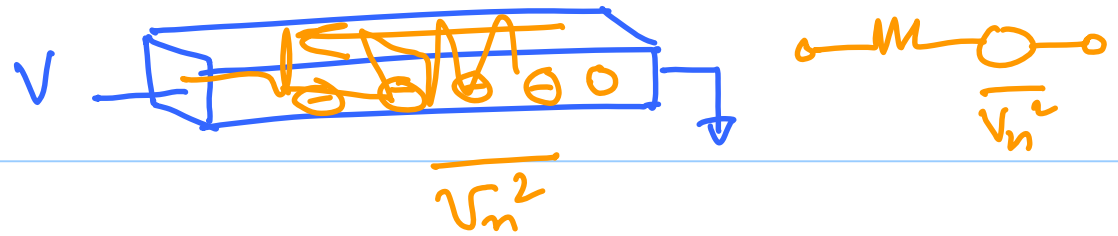


Bulk component
↳ Thermal

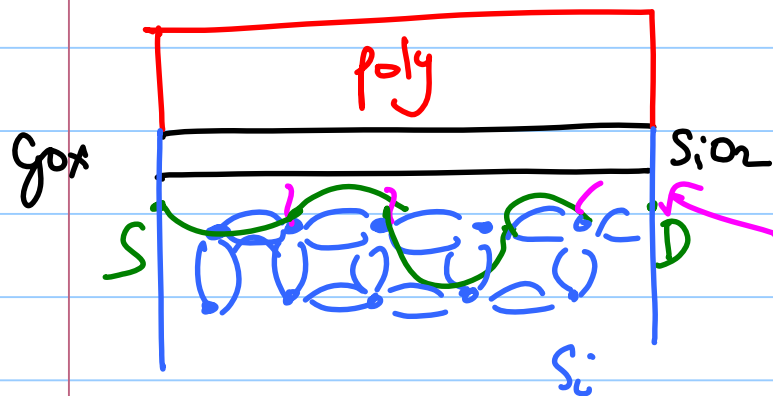


Dangling bond at the interface

* Traps, or extra energy state

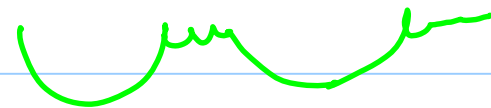
* Charge carriers get trapped on them released by these energy states




$20 \log(\overline{V_n^2})$

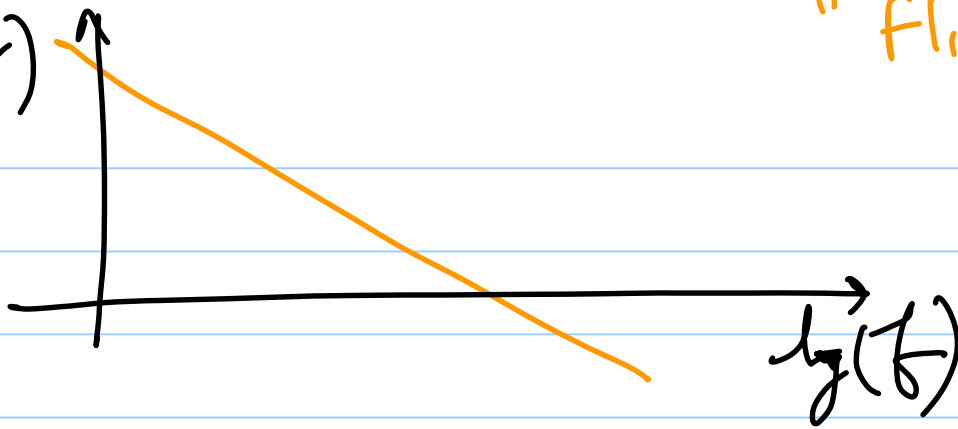

"Flicker Noise"

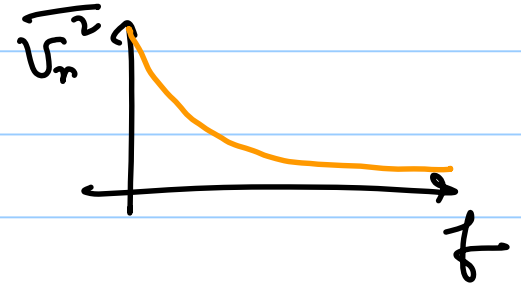

Flicker Noise

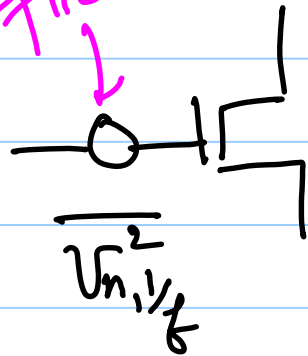

$$\overline{V_n^2} = \frac{K}{C_{ox} WL} \cdot \frac{1}{f}$$

$\frac{1}{f} \rightarrow \text{noise}$

Large Area $\Rightarrow WL \uparrow \Rightarrow \overline{V_n^2} \downarrow$

$\Rightarrow$ process dependent parameter
 $\Rightarrow 10^{-25} V^2 F$
in Razavi

$\rightarrow$ more frequent at lower frequencies ($\frac{1}{f}$)

$\rightarrow$ doesn't depend on bias condition

$\rightarrow$ only on WL area


$\Rightarrow$ To decrease $\frac{1}{f}$ -noise $\Rightarrow$ increase device area

$\Rightarrow$ In 180nm CMOS $\Rightarrow$ PMOS exhibit less flicker noise than NMOS.

$\Rightarrow$ holes were carried in a buried channel

* In present technologies

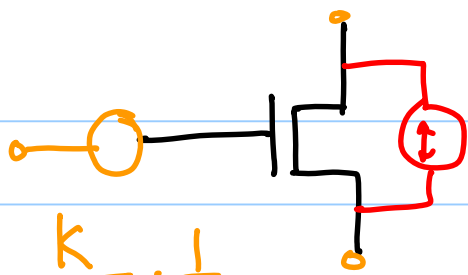
$\rightarrow$ verify with process datasheet



$$\frac{k}{C_{ox}WL} \cdot \frac{1}{f}$$


$$\overline{I_n^2} = \frac{8}{3} kT g_m$$

$\Rightarrow$

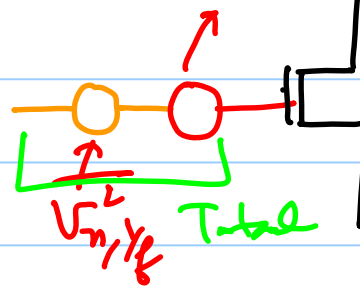

$$\overline{V_n^2} = \frac{\overline{I_n^2}}{g_m^2} = \frac{8}{3} \frac{kT}{g_m}$$

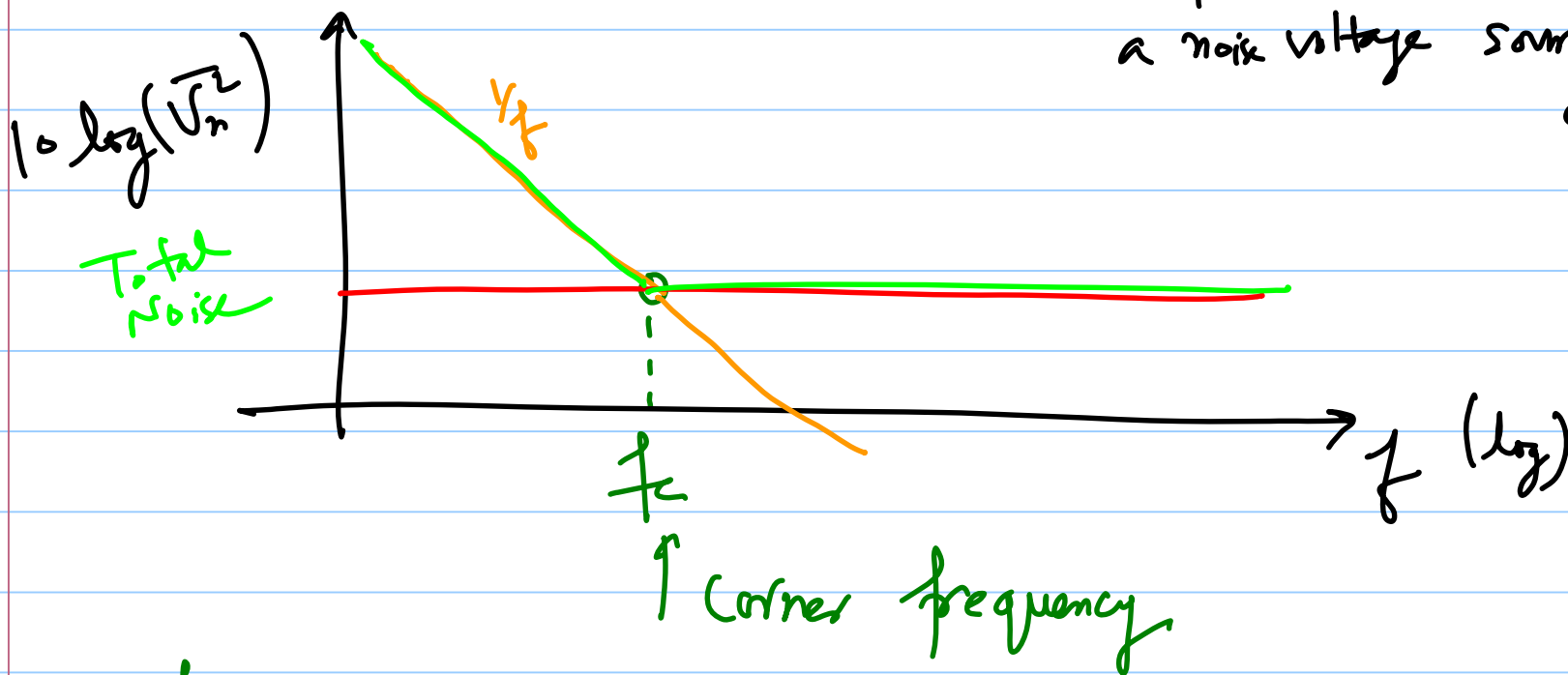Reflected thermal noise to a noise voltage source at the gate



* f_c tells us which part of the signal band is most corrupted by the flicker noise

$$\sqrt{v_n^2} \Rightarrow$$

$$\frac{8}{3} \frac{kT}{g_m} = \frac{K}{C_{ox}' WL} \cdot \frac{1}{f_c}$$

$\Rightarrow$


$$f_c = \frac{K}{C_{ox}' WL} g_m \cdot \frac{3}{8kT}$$

↑ depends on device bias current (g_m)
 ↳ process technology

$$f_c \approx 800\text{kHz} - 1\text{MHz for } \leq 0.25\mu\text{m}$$

$$\text{In nano-CMOS} \Rightarrow 1 - 100\text{MHz}$$



Ex.

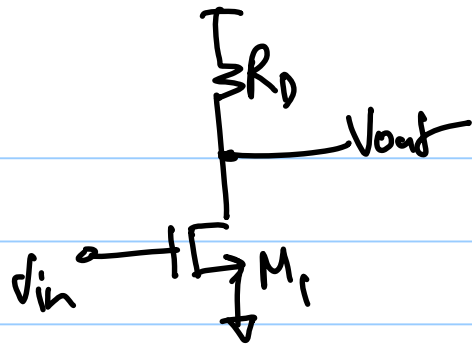

noise circuit
 $\Rightarrow$ small-signal circuit
 with the noise sources

$$\overline{V_{n,out}^2} = ?$$


$$R_D \ll \infty$$

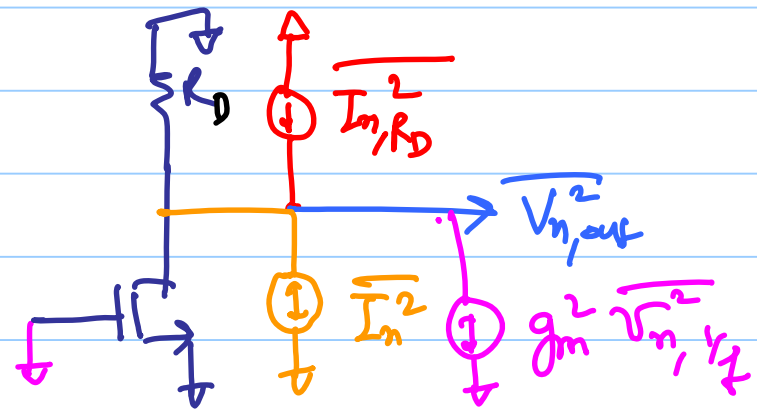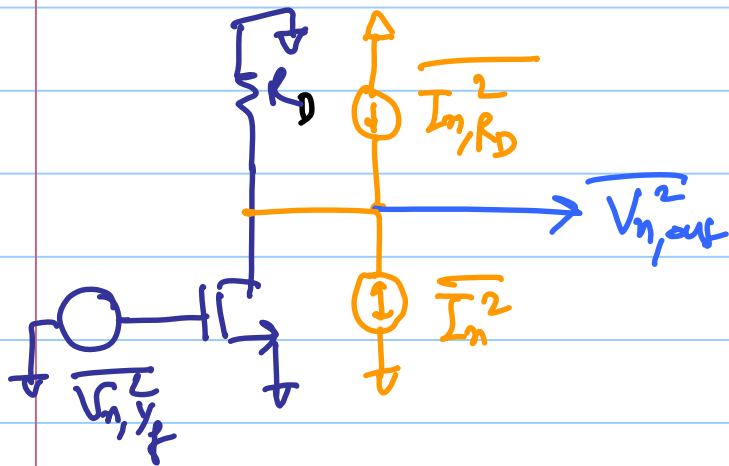

bring $1/f$ noise to the
 output as a
 noise current
 source

$$\overline{V_{n,out}^2} = \left[\underbrace{\frac{8}{3}KTg_m + \frac{K}{C_{ox}WL} \frac{1}{f} g_m^2}_{\text{total noise current}} + \frac{4KT}{R_D} \right] R_D^2 \quad \frac{V^2}{Hz}$$

Representation of Noise in Circuits

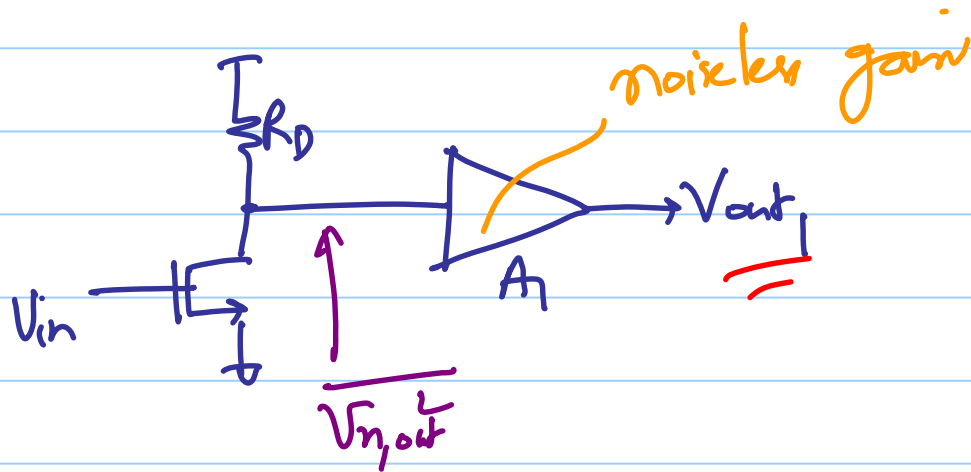

PSD noise at the output V_{out} , $\Rightarrow \overline{V_{n,out}^2} \cdot A_1^2$


$A_1 \uparrow \Rightarrow$ Circuit becomes noisier??

But A_1 also amplifies the signal

$\Rightarrow$ the output SNR is independent of A_1

$\Rightarrow$ We want to get the circuit gain out of 'the noise comparison

$\Rightarrow$ Specify the "input referred noise" of the circuit.
 $\Rightarrow$ NOT the output noise

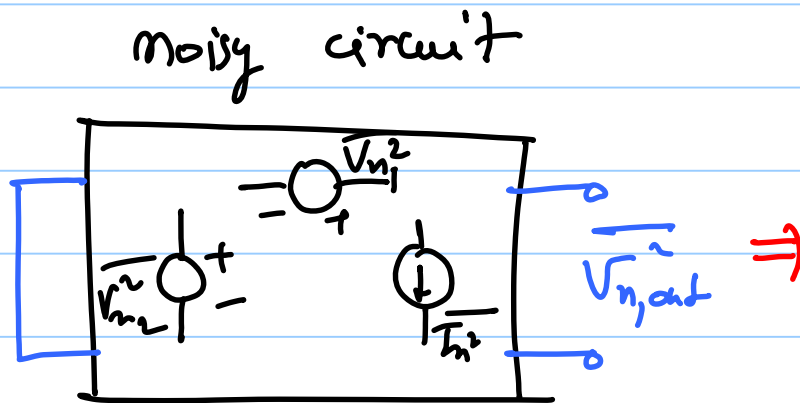

Noisy 2-port

