




# ECE 614 - Lecture 12

Note Title

10/2/2014

Noise circuit
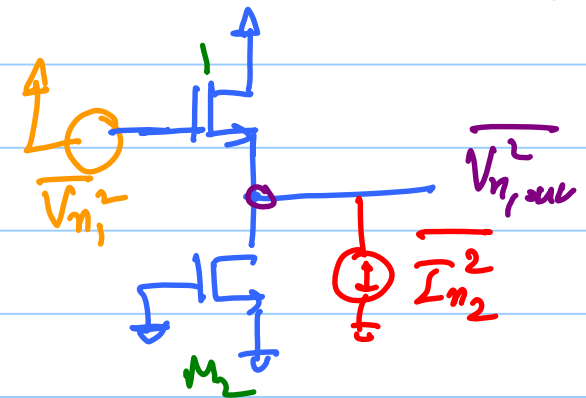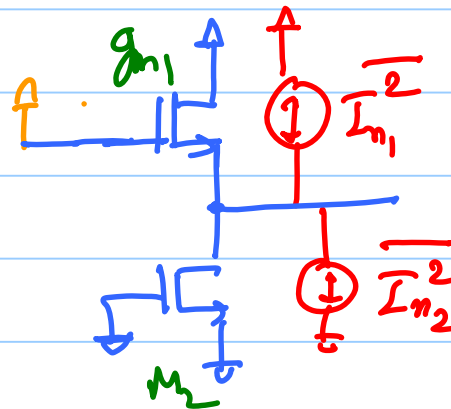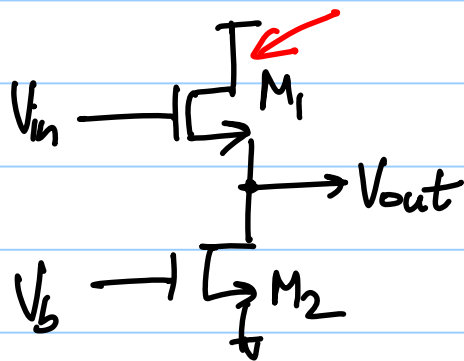
$$\overline{V_{n_1}^2} = \frac{\overline{I_{n_1}^2}}{g_{m_1}^2}$$



$$A_v = \frac{\frac{1}{g_{m_1}} \parallel r_{o_1} \parallel r_{o_2}}{\frac{1}{g_{m_1}} \parallel r_{o_1} \parallel r_{o_2} + \frac{1}{g_{m_2}}} < 1$$

$$\overline{V_{n,out}^2} = \overline{I_{n_2}^2} \cdot \left( \frac{1}{g_{m_1}} \parallel \frac{1}{g_{m_2}} \parallel r_{o_1} \parallel r_{o_2} \right)$$

$$\overline{V_{n,in}^2} = \overline{V_{n,1}^2} + \frac{\overline{V_{n,out|M_2}^2}}{A_v^2}$$

$$\overline{V_{n,in}^2} \stackrel{!}{=} \frac{8}{3} kT \cdot \left( \frac{1}{g_{m,1}} + \frac{g_{m,2}}{g_{m,2}^2} \right)$$

$$|A_v| < 1$$



$$\Rightarrow$$

$$g_{m,1} \uparrow$$

$$g_{m,2} \downarrow$$

Cascode.
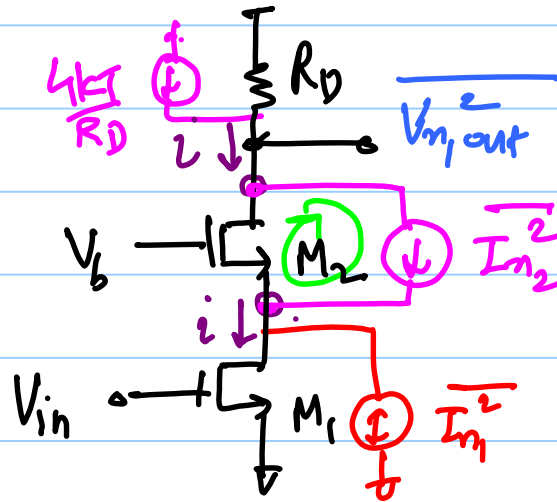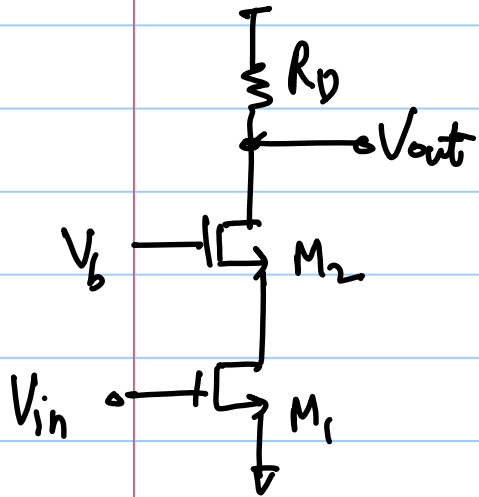
$$A_v = -g_{m1} \left( \underbrace{g_{m2} \delta_{o2} \delta_{o1}}_{g_{m2} \delta_o^2} \parallel R_D \right)$$





$$I_{D2} + I_{n2} = 0$$

@ low-frequencies &  $\delta_{o2} \rightarrow \infty \Rightarrow I_{n2}$  doesn't affect  $V_{n,out}$



Noise behavior same as CS amplifier formed by  $M_1$

$$\overline{V_{n,in}^2} = \frac{\overline{I_{n1}^2}}{g_{m1}^2} = \frac{8}{3} \frac{kT}{g_{m1}} + \frac{\frac{4kT}{R_D} \times \frac{R_D^2}{(g_{m1} R_D)^2}}{\Rightarrow \frac{4kT}{R_D g_{m1}^2}}$$

# Differential Pair :

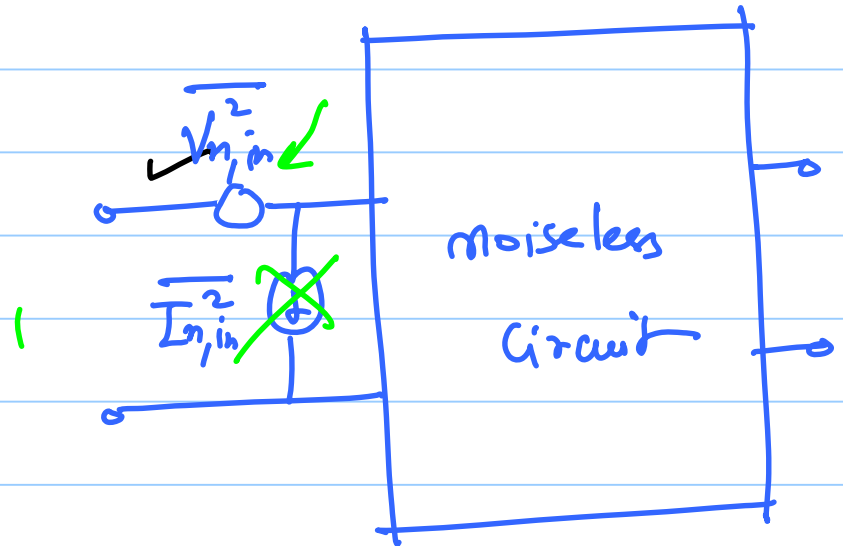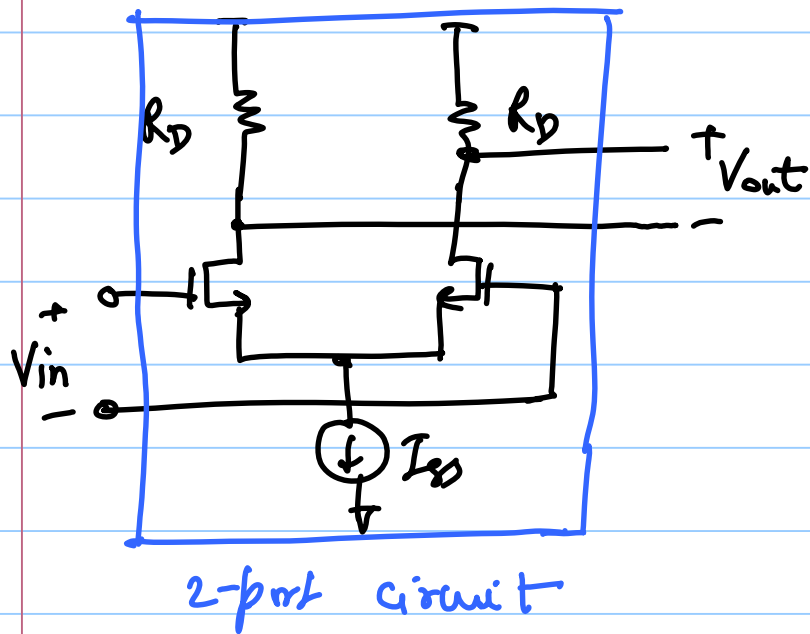

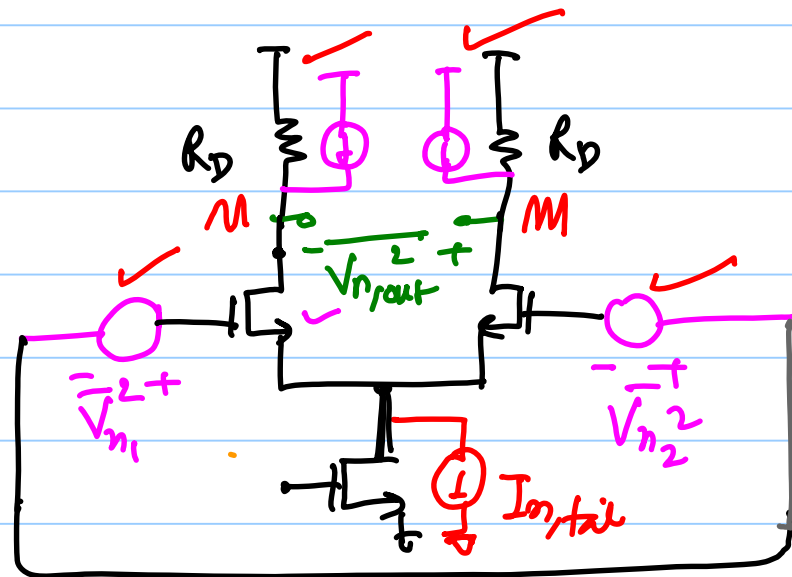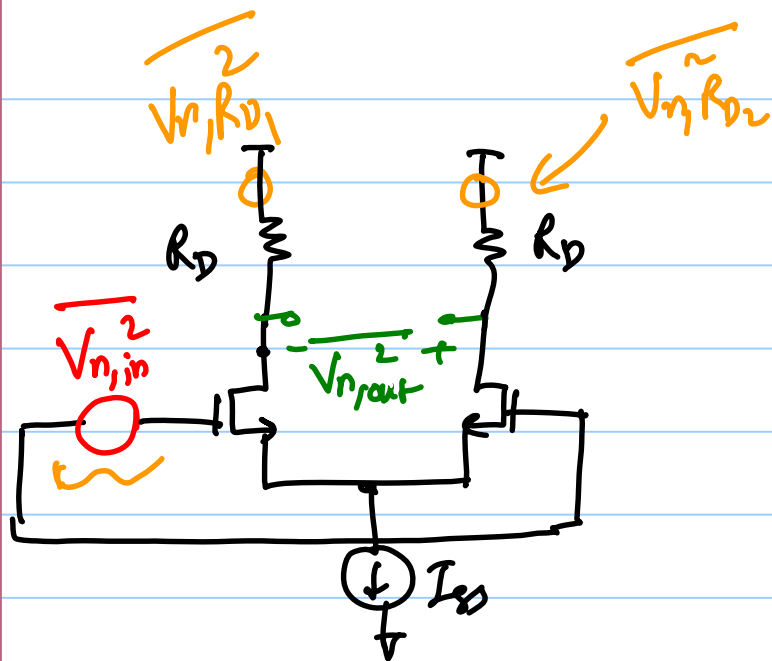@ low-f  $Z_{in} \rightarrow \infty$   
 $\Rightarrow \overline{I_{n,in}^2}$  is negligible



$$\overline{V_{n,in}^2} = \overline{V_{n1}^2} + \overline{V_{n2}^2} + 2 \times \frac{4kT}{g_m^2 R_D}$$

$$V_a \approx 0$$

$$V_a > 0$$


$$\Rightarrow \overline{V_{n,in}^2} = 8kT \left[ \frac{2}{3} g_m + \frac{1}{g_m^2 R_D} \right] + \frac{2k}{C_x W L} \cdot \frac{1}{f}$$

2x compared to a CS amplifier

$V_d = 0 \Rightarrow I_{ss}$  produces CM noise at the output  
 $\Rightarrow$  no contribution to the differential  
 $\overline{V_{n,in}^2}$

$\hookrightarrow$  Correlated noise in the two  
 halves gets cancelled out in  
 differential output.

$$V_d \approx V_{in} \Rightarrow$$

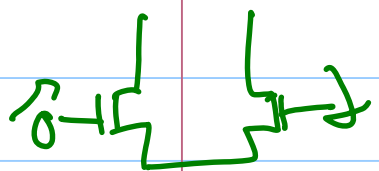

$$\underbrace{\Delta I_{D1} - \Delta I_{D2}} = g_m \Delta V_{in} = g_{m0} \left( 1 + \frac{I_n}{2I_{ss}} \right) \Delta V_{in}$$


for  $I_n \ll I_{ss}$

$\Rightarrow$  negligible effect

$$\frac{\overline{I_n^2}}{I_{ss}^2} = \frac{\frac{8}{3} kT g_{m, \text{ave}} \cdot \Delta f}{I_{ss}^2} \ll 1$$


Contribution to  $\overline{V_{n,in}^2}$

To minimize  $\overline{V_{n,in}^2}$

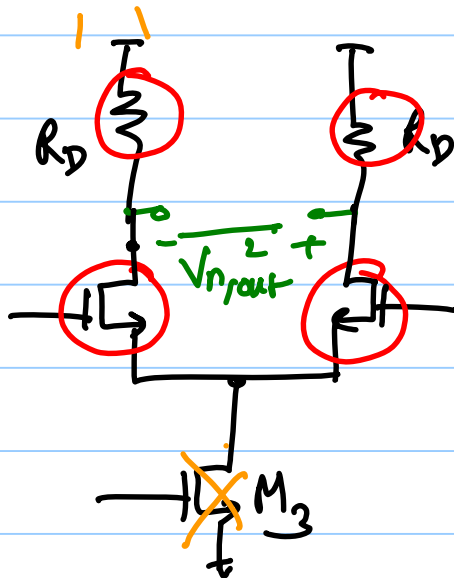



$g_m \uparrow$

$g_{m3}$  doesn't matter

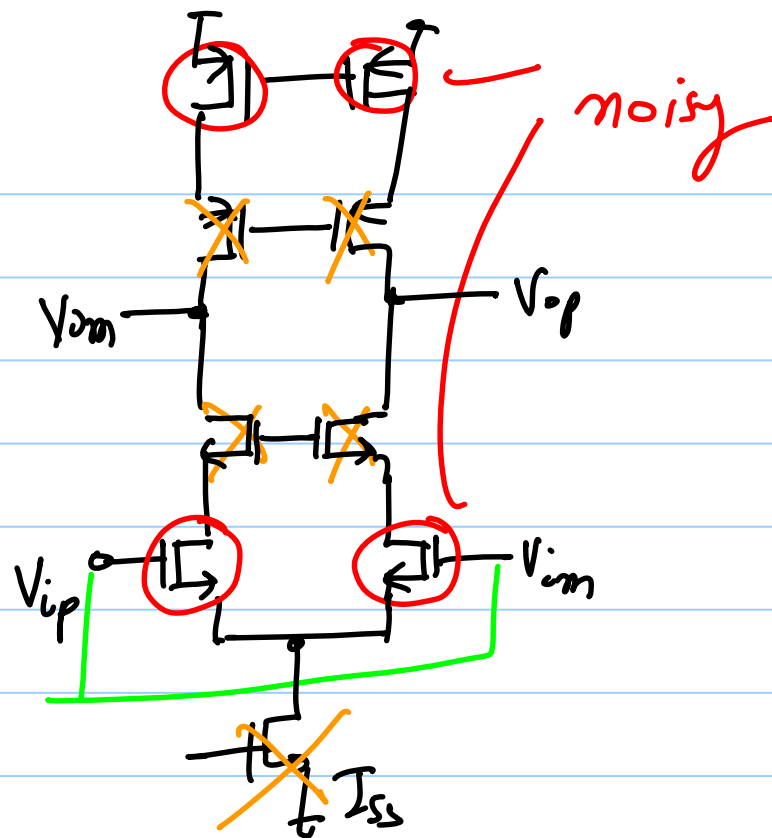

Ex.

## Thermal Noise

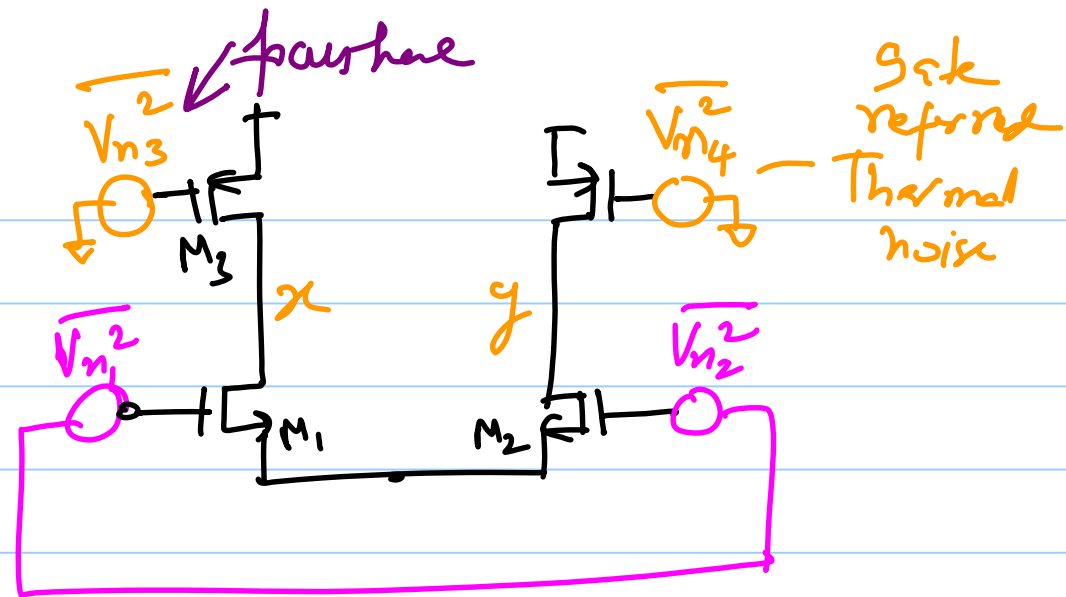
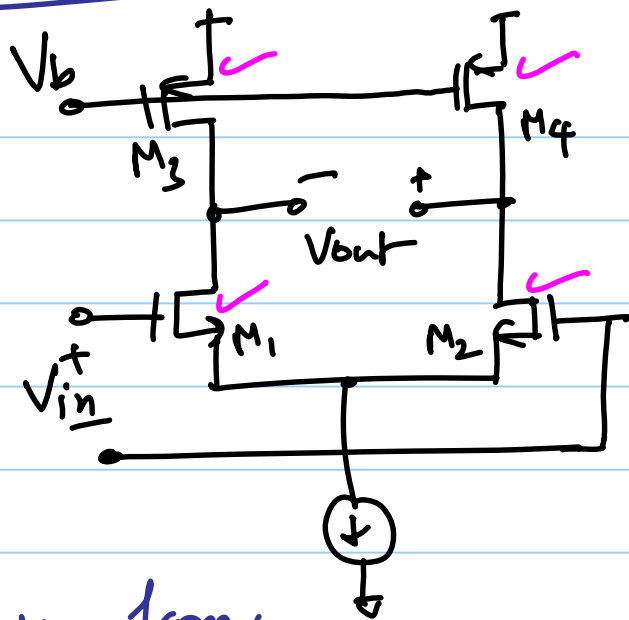


Contribution from  $M_1$  &  $M_2 \Rightarrow \overline{V_{n1}^2} + \overline{V_{n2}^2}$


We need to refer  $M_3$  &  $M_4$ 's noise to the input  
 $x$  first refer  $\overline{V_{n3}^2}$  to the input side

refer this to the input  $\Rightarrow$  Split into ~~CM~~ & DM noise circuits  
 gets cancelled

Differential picture

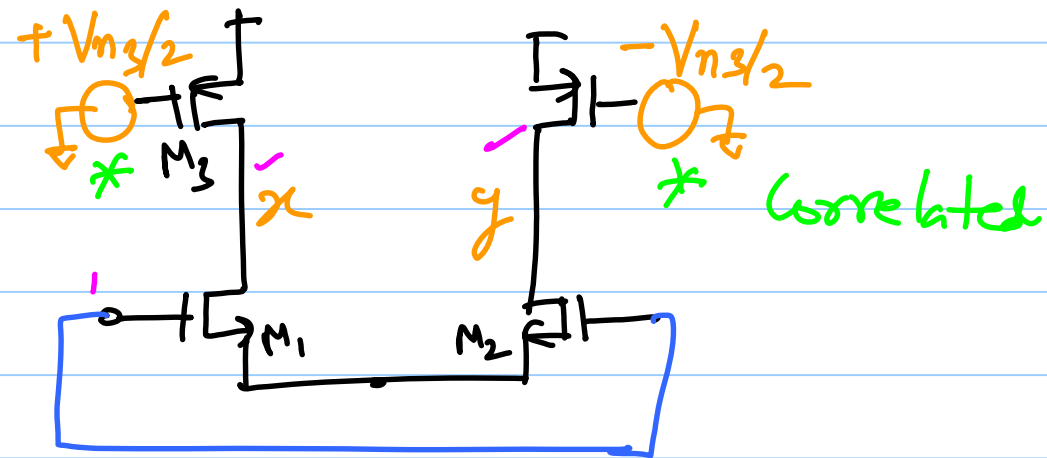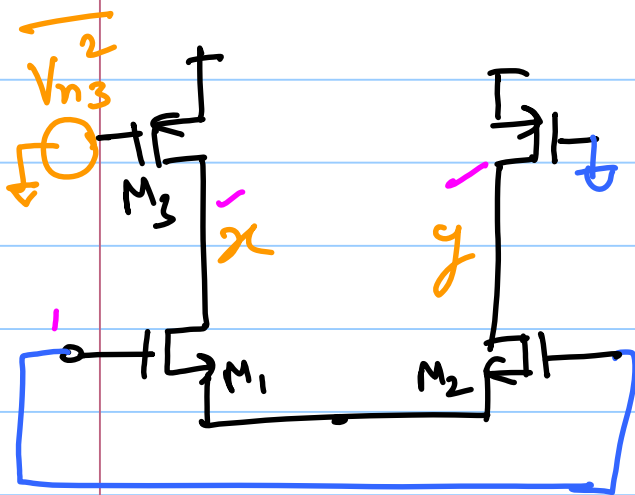

Half Circuit

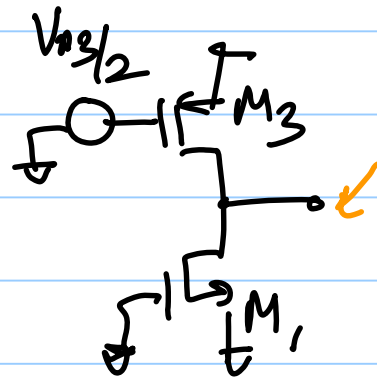

$$|g_{m3} \cdot (r_{o1} \parallel r_{o3})| \cdot \frac{V_{n3}}{2}$$

Since  $\frac{V_{n3}}{2}$  &  $-\frac{V_{n3}}{2}$  are correlated  
 $\Rightarrow$  Add them in voltage domain

$$\overline{V_{n,out}}^2|_{M_3} = g_{m3}^2 (r_{o1} || r_{o3})^2 \cdot \overline{V_{n3}}^2$$

$$\overline{V_{n,out}}^2|_{M_4} = g_{m4}^2 (r_{o2} || r_{o4})^2 \cdot \overline{V_{n4}}^2$$

Due to Correlation  
noise voltages  
add,  
not powers!

$$\overline{V_{n,in}}^2|_{M_3, M_4} = \frac{\overline{V_{n,out}}^2|_{M_3} + \overline{V_{n,out}}^2|_{M_4}}{A_v^2} = g_{m1}^2 (r_{o1} || r_{o3})^2$$

$$\overline{V_{n,in}}^2 = 2V_{n1}^2 + 2 \cdot \frac{g_{m3}^2}{g_{m1}^2} \times \overline{V_{n3}}^2$$


$$\overline{V_{n,in}}^2 = 8KT \left[ \frac{2}{3g_{m1}} + \frac{2g_{m3}}{3g_{m1}^2} \right]$$

Input referred  
Thermal Noise

Look up this  
example

$$\Rightarrow \overline{V_{n,i}^2} = \underbrace{2 \times \frac{8}{3} \frac{KT}{g_{m1}}}_{\text{diff pair}} + \underbrace{2 \times \frac{8}{3} KT \cdot \frac{g_{m3}}{g_{m1}^2}}_{\text{CM loads}}$$
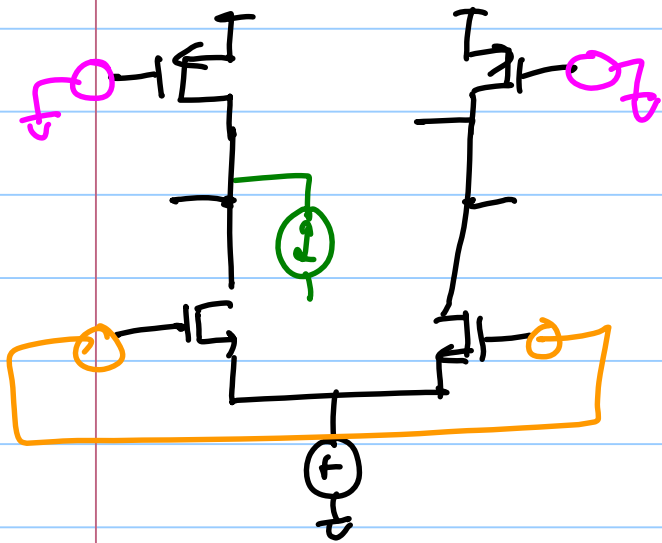
$$\frac{2}{3} KT \frac{g_{m3}}{g_{m3}^2} = \frac{2}{3} \frac{KT}{g_{m3}}$$



$$\cancel{\frac{8}{3} \frac{KT}{g_{m3}}} \times \frac{g_{m3}^2}{g_{m1}^2} = \frac{8}{3} KT \frac{g_{m3}}{g_{m1}^2}$$