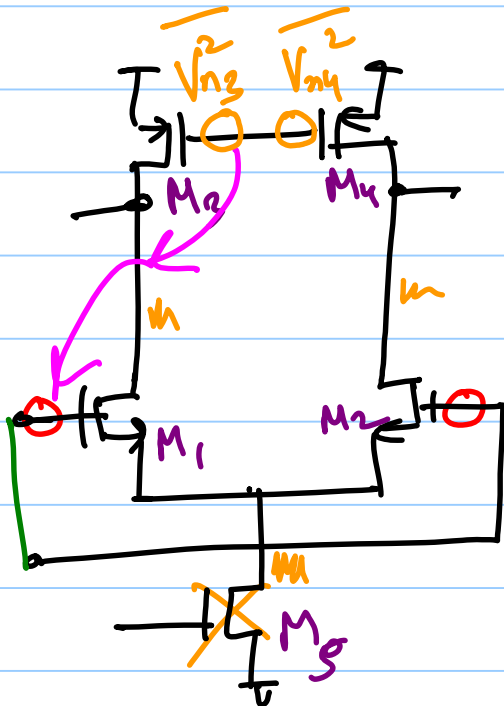


ECE 614 - Lecture 13

Note Title

10/7/2014



$$\overline{V_{n,in}^2} = \overline{V_{n1}^2} + \overline{V_{n2}^2} + \overline{V_{n3}^2} \frac{g_{m3}^2 (r_{o1} || r_{o3})^2}{g_{m1}^2 (r_{o1} || r_{o3})^2}$$


$$= \underline{\underline{\overline{V_{n1}^2} + \overline{V_{n2}^2}}} + \overline{V_{n3}^2} \frac{g_{m3}^2}{g_{m1}^2} + \overline{V_{n4}^2} \frac{g_{m4}^2}{g_{m2}^2}$$

$$= 4KT \left[2 \times \frac{1}{3g_{m1}} + 2 \times \frac{g_{m3}}{g_{m1}^2} \right]$$

$$g_{m1} = g_{m2}$$

$$\overline{V_{n,inv}}^2 = \frac{2K_n}{C_{ox}(WL)_f} + \frac{2K_n}{C_{ox}(WL)_f} \cdot \frac{I_{n3}^2}{I_{n1}^2}$$

Telescopie Op amp

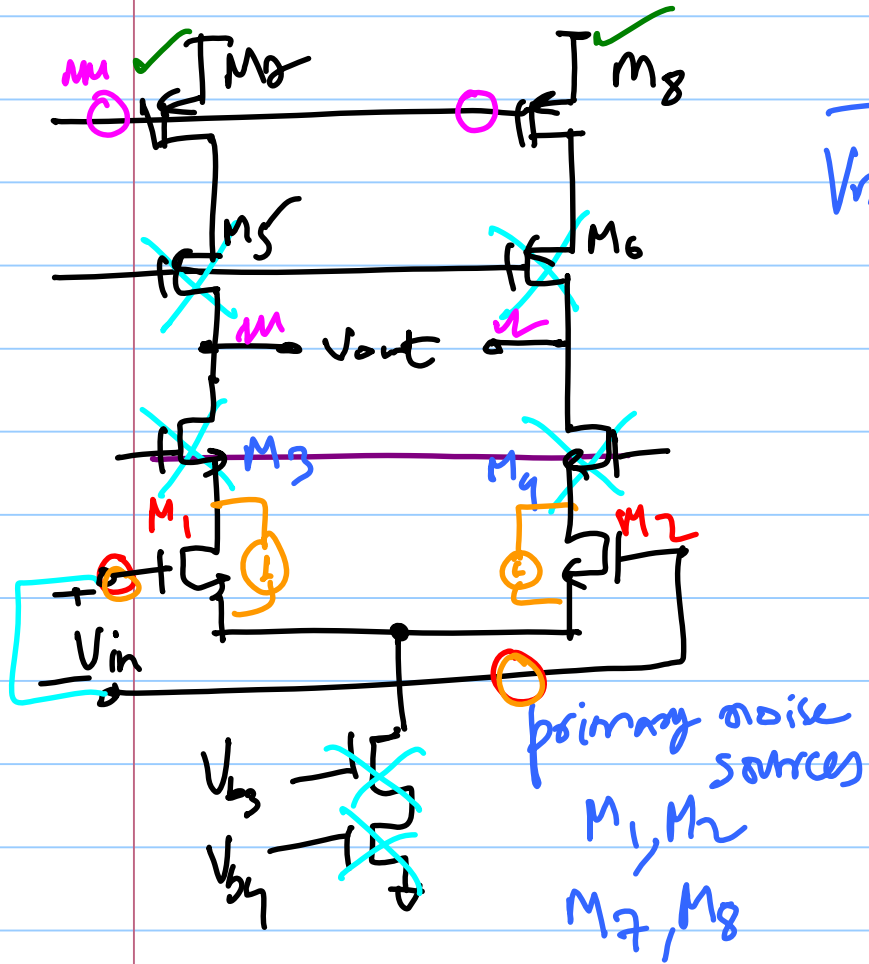


$$\overline{V_{n,in}^2} = \frac{8}{3} \frac{kT}{g_{m1,2}} \times 2 + \frac{8}{3} kT \frac{g_{m7,8}}{g_{m1,2}^2} \times 2$$

$$= 8kT \left[\frac{2}{3g_{m,2}} + \frac{2}{3} \frac{g_{m,2}}{g_{m,2}^2} \right]$$

$g_{m,2} \neq g_{m,3}$

Folded Cascode:

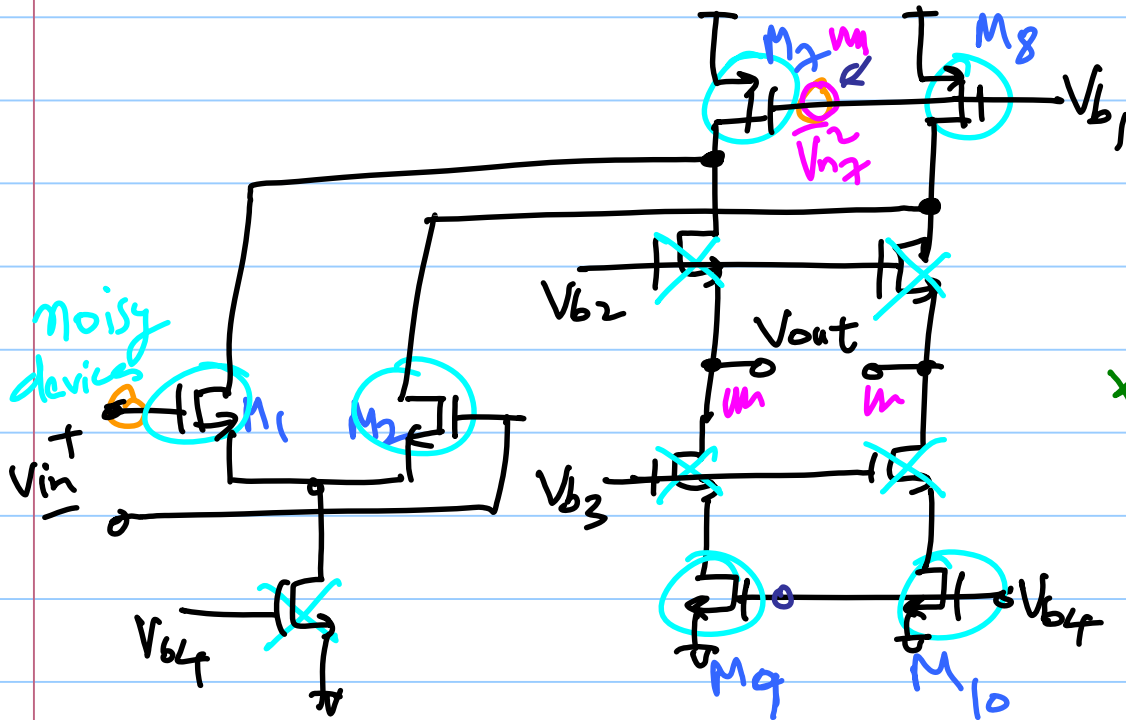

+ Mentally change gate voltage of each transistor by a small amount

* Estimate $\overline{V_{n,out}^2} | M_7$

* Divide by A_v^2 to reflect back to the input port

$$\frac{\overline{V_{n,out}^2} | M_7}{A_v^2}$$


$$\overline{V_{n,out}^2} | M_{7,8} = 2 \left[4kT \cdot \frac{2}{3g_{m7,8}} \times \underbrace{g_{m7,8}^2 R_{out}^2}_{\text{gain seen from } M_{7,8} \text{'s gate}} \right]$$

$$\overline{V_{n,out}^2} | M_{9,10} = 2 \left[4kT \cdot \frac{2}{3g_{m9,10}} \times g_{m9,10}^2 R_{out}^2 \right]$$

$$A_v^2 = g_{m1,2}^2 R_{out}^2$$

$$\overline{V_{n,in}^2} = 8kT \left[\underbrace{\frac{2}{3g_{m1,2}}}_{\text{input pair}} + \frac{2}{3} \frac{g_{m7,8}}{g_{m1,2}^2} + \frac{2}{3} \frac{g_{m9,10}}{g_{m1,2}^2} \right]$$


* more noisy than Telescopic

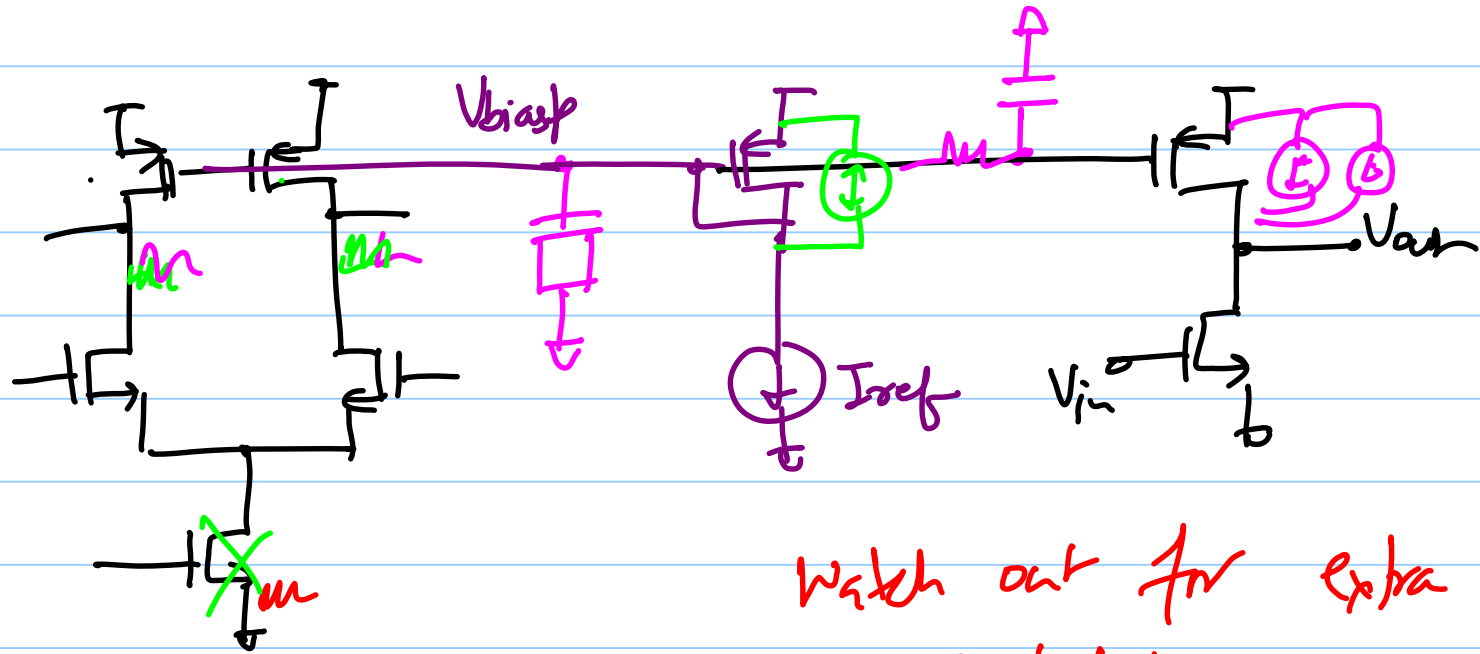

Watch out for extra devices
Contributing noise

Noise in Cascaded Amplifiers:


$$A_v = A_1 A_2 A_3$$

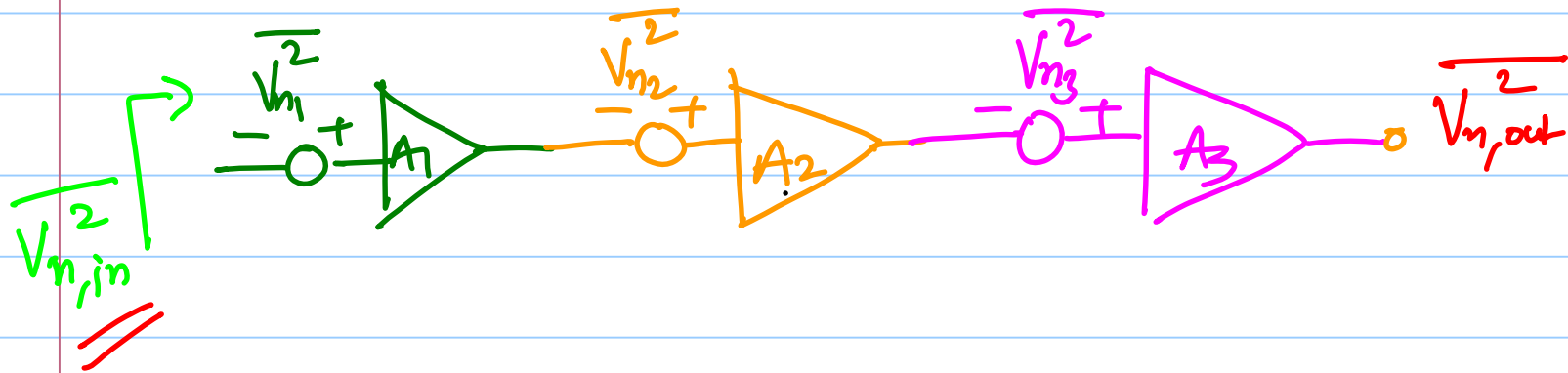

$$\overline{V_{n,out}}^2 = \overline{V_{n1}}^2 \cdot A_1^2 A_2^2 A_3^2 + \overline{V_{n2}}^2 \cdot A_2^2 A_3^2 + \overline{V_{n3}}^2 \cdot A_3^2$$

$$\overline{V_{n,in}}^2 = \frac{\overline{V_{n,out}}^2}{(A_1 A_2 A_3)^2} = \underbrace{\overline{V_{n1}}^2}_{\text{first stage dominates}} + \underbrace{\frac{\overline{V_{n2}}^2}{A_1^2}}_{\text{first stage gain}} + \frac{\overline{V_{n3}}^2}{A_1^2 A_2^2}$$

RX
chain


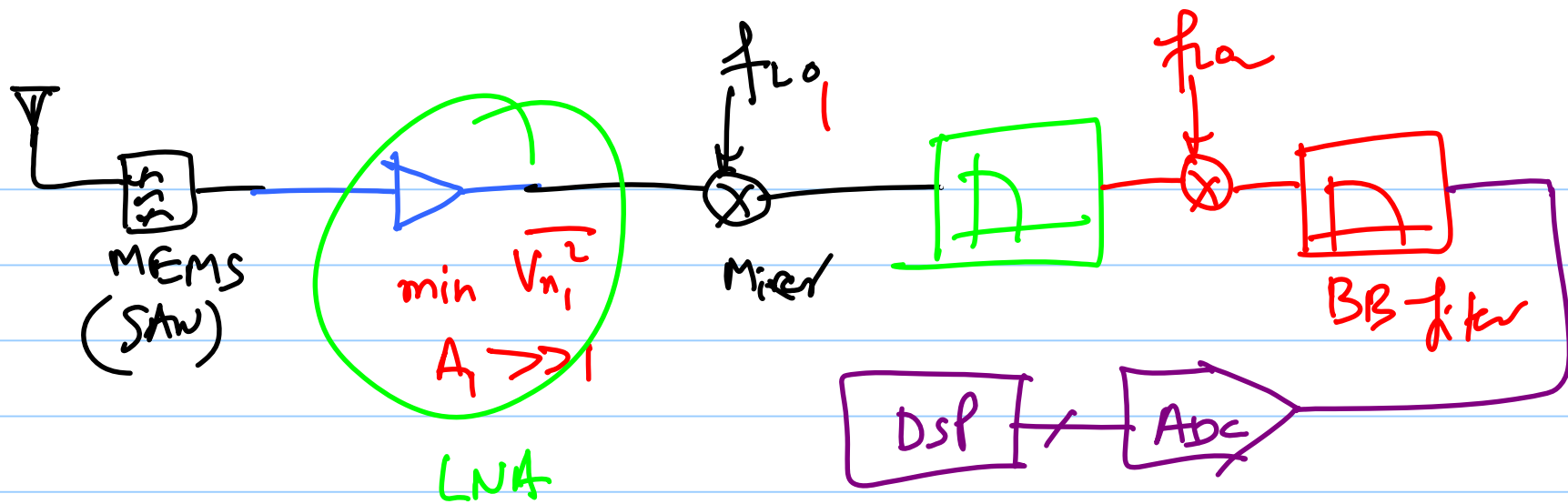


$$NF > 1 \text{ dB}$$

$$NF = 10 \log_{10} \left(\frac{SNR_{in}}{SNR_{out}} \right)$$

$$NF = 1 + \frac{\overline{V_n + I_n R_s}^2}{4kTR_s}$$

Two-Stage opamp

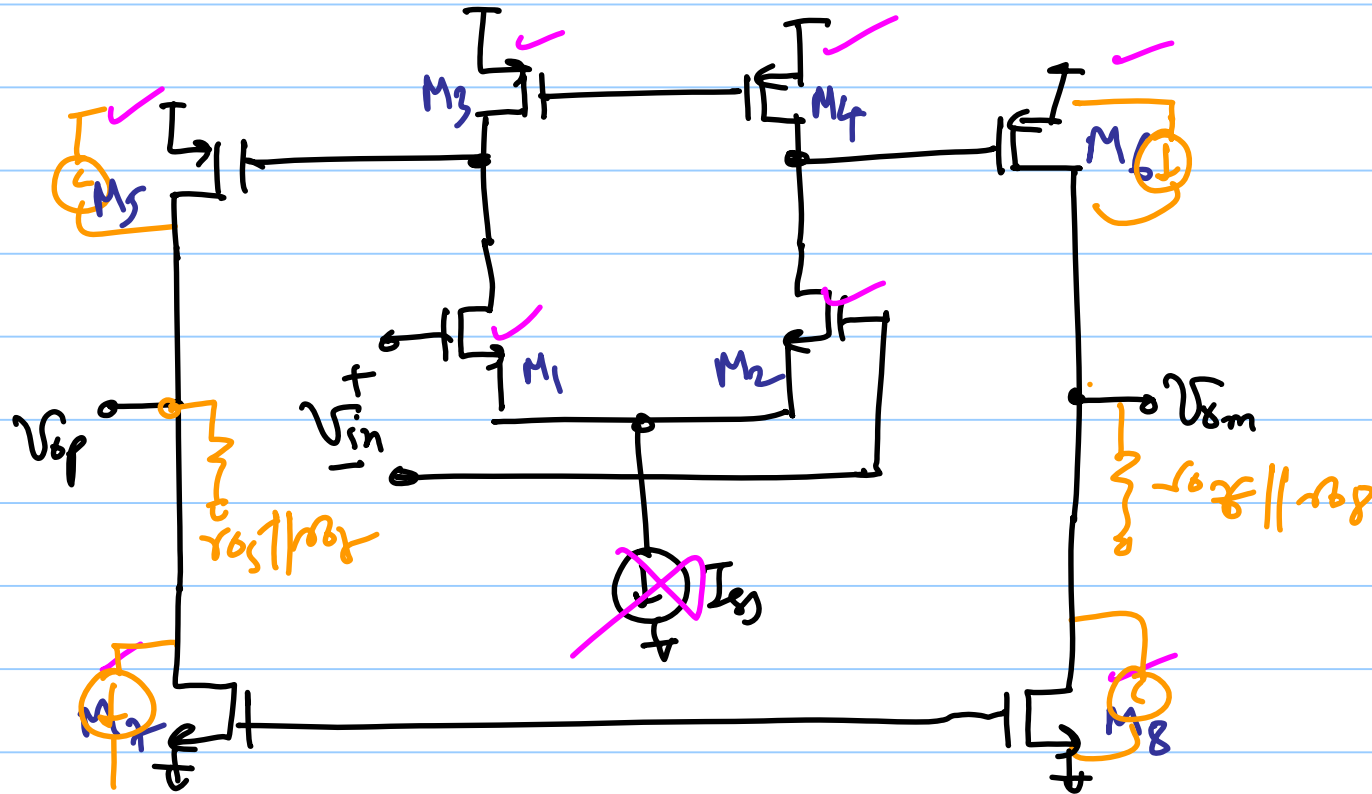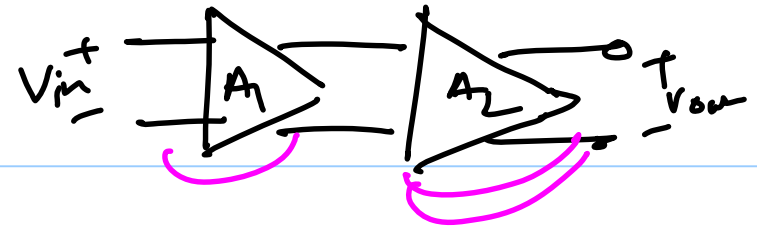

* Noise current of M_5 & M_7 flows thru $r_{o5} \parallel r_{o7}$



$$\overline{V_{n,out}^2} \big|_{M5-8} = \frac{2 \times 4kT \cdot \frac{2}{3} (g_{m5} + g_{m2}) (r_{o5} \parallel r_{o2})^2}{\underbrace{g_{m1}^2 (r_{o1} \parallel r_{o3})^2 \cdot g_{m5}^2 (r_{o5} \parallel r_{o2})^2}_{A_1^2 A_2^2}}$$

$$\overline{V_{n,in}^2} \big|_{M5-8} = \frac{16kT}{3} \frac{(g_{m5} + g_{m2})}{g_{m1}^2 g_{m5}^2 (r_{o1} \parallel r_{o3})^2}$$


$$\overline{V_{n,in}^2} = \frac{4kT}{3} \cdot \frac{1}{g_{m1}^2} \left[\underbrace{(g_{m1} + g_{m2})}_{1^{st} \text{ stage}} + \underbrace{\frac{g_{m5} + g_{m2}}{g_{m5}^2 (r_{o1} \parallel r_{o3})^2}}_{2^{nd} \text{ stage}} \right]$$



small is
A is large


Sampling Switches:

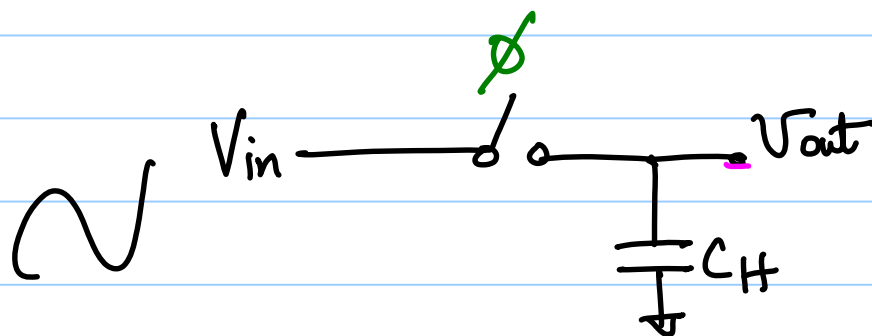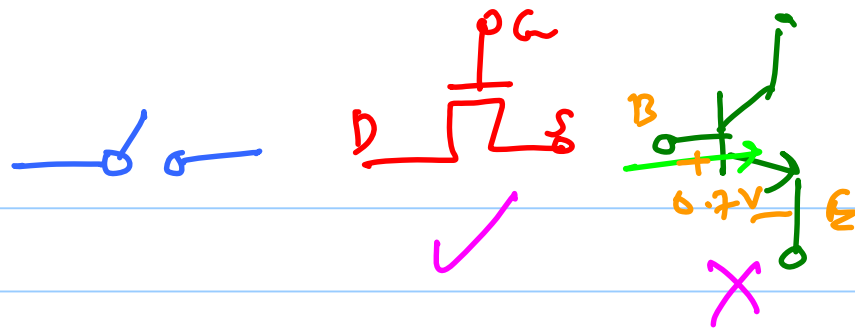

Track-and-Hold

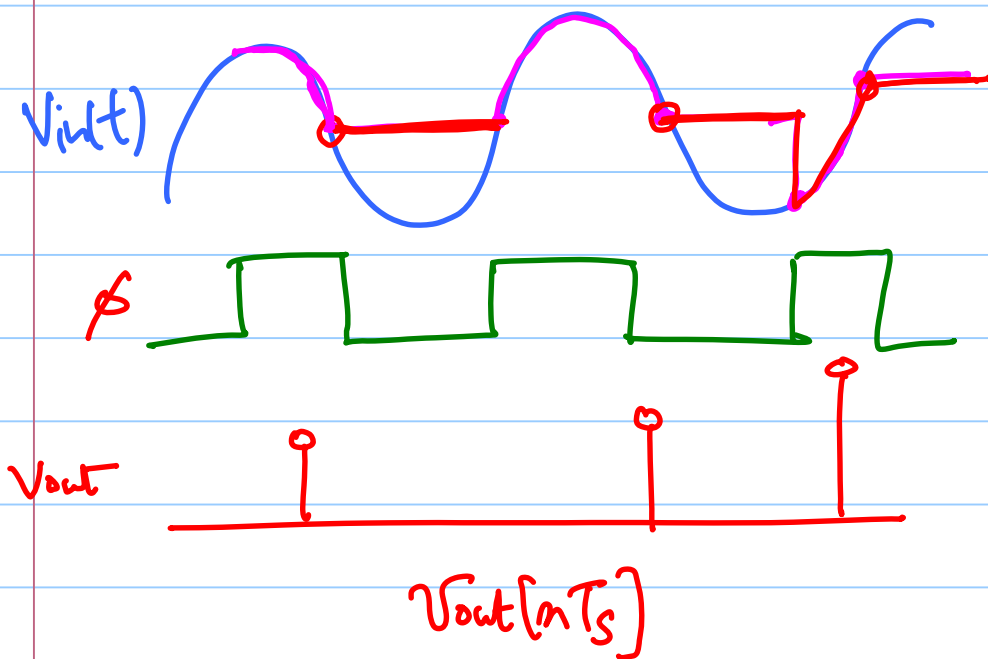


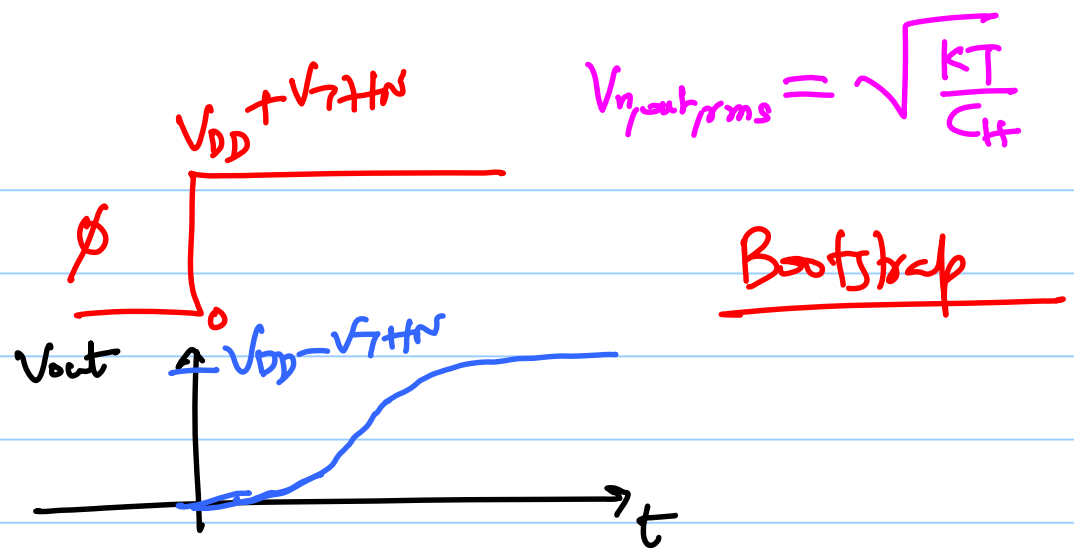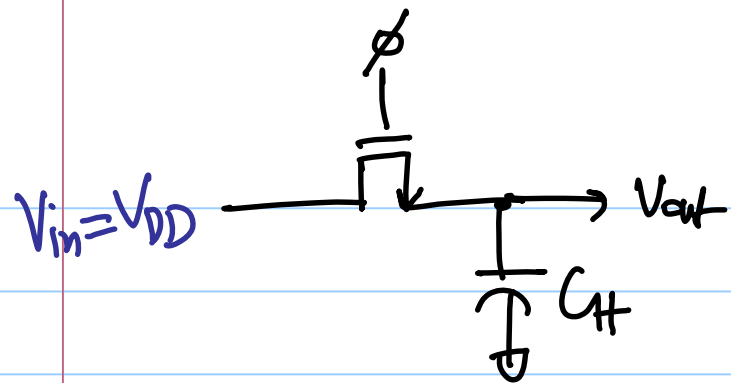

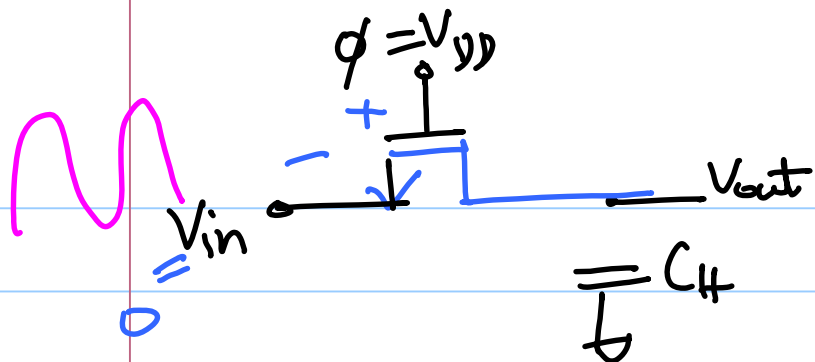

$$R_{on} = \frac{1}{K_p n \frac{W}{L} (V_{GS} - V_{THN})}$$
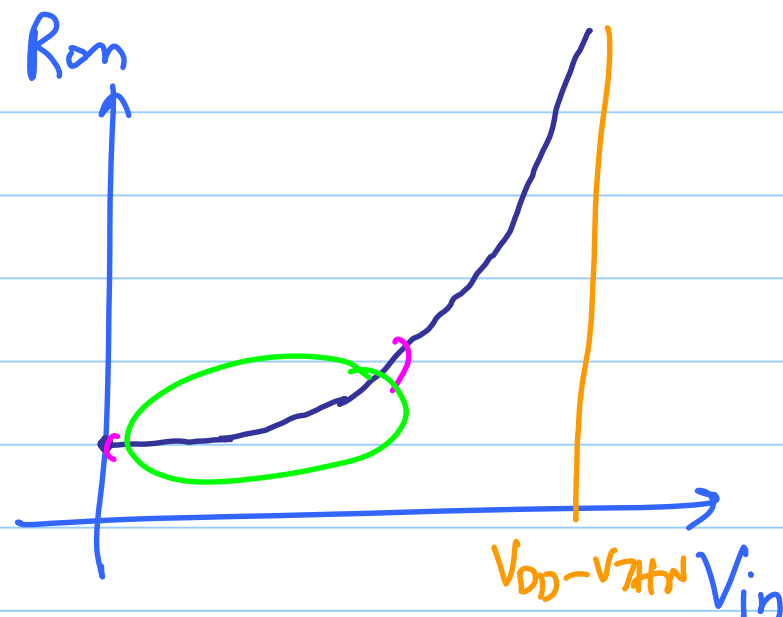
$$= \frac{1}{K_p n \frac{W}{L} (\underbrace{V_{DD} - V_{in}} - V_{THN})}$$



$$R_{on,p} = \frac{1}{k_p \frac{W}{L} (V_{in} - |V_{thp}|)}$$

