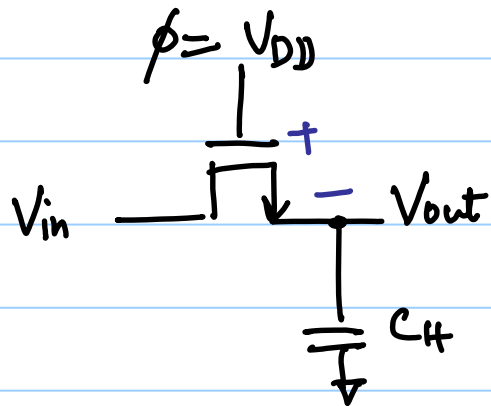


ECE 614 - Lecture 14.

Note Title

10/9/2014




$$V_{GS} = V_{DD} - V_{out}$$


$$\approx V_{DD} - V_{in}$$


$$R_{on,n} = \frac{1}{\beta_n (V_{DD} - V_{in} - V_{THn})}$$

$R_{on,n}$

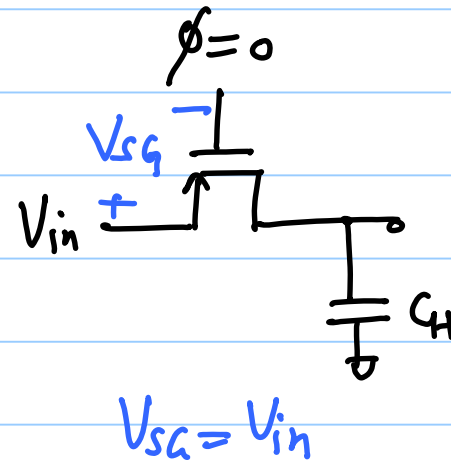

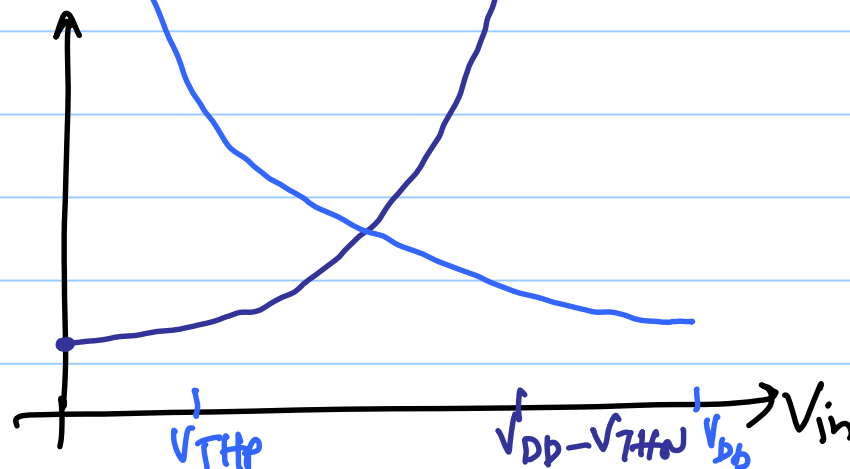
$$R_{on,p} = \frac{1}{\beta_p (V_{in} - V_{THp})}$$



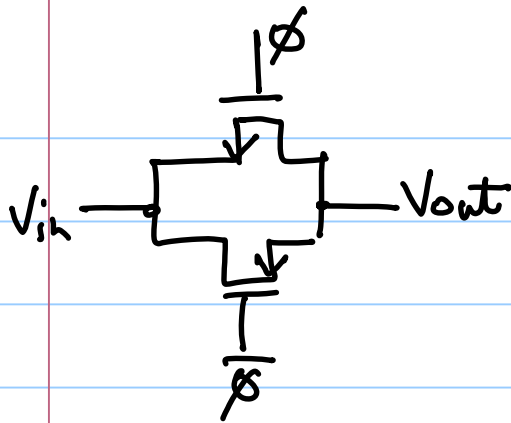


$R_{on,n}$

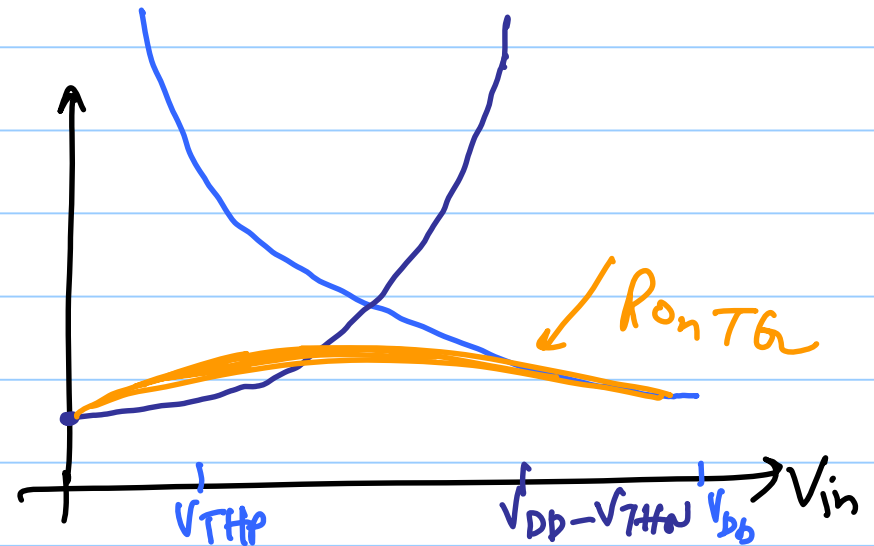





$$R_{on,eq} = R_{on,n} \parallel R_{on,p}$$


$$= \frac{1}{\beta_n (V_{DD} - V_{in} - V_{THn})} \parallel \frac{1}{\beta_p (V_{in} - |V_{THp}|)}$$

$$= \frac{1}{\beta_n (V_{DD} - V_{THn}) - [\beta_n - \beta_p] V_{in} - \beta_p |V_{THp}|}$$

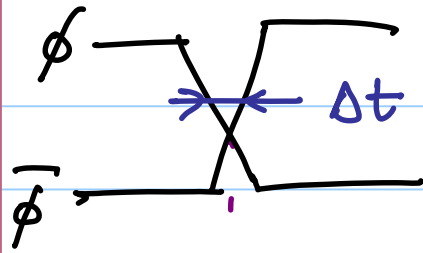

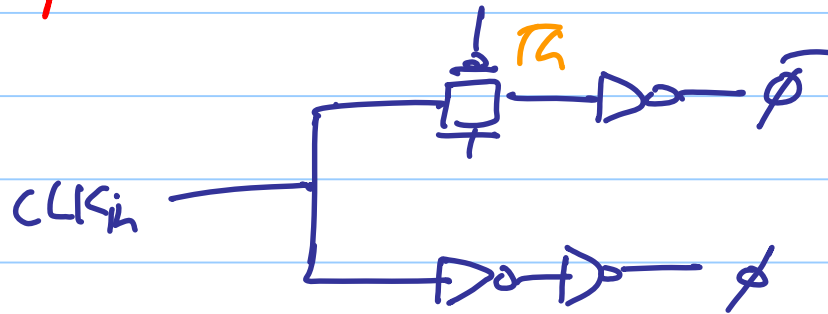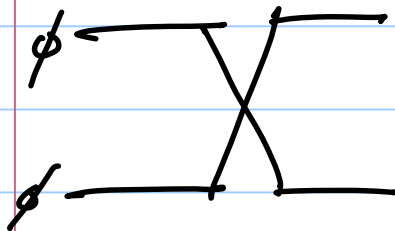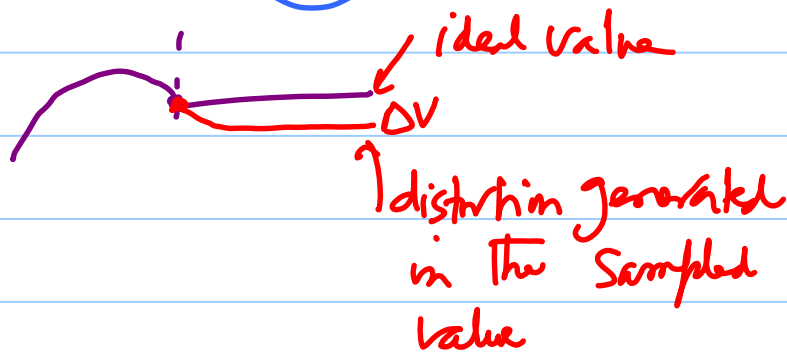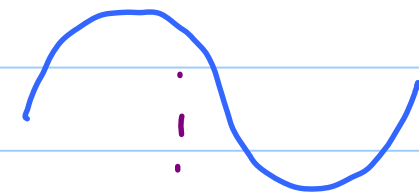$\Rightarrow$ ambiguity in the sampling instance



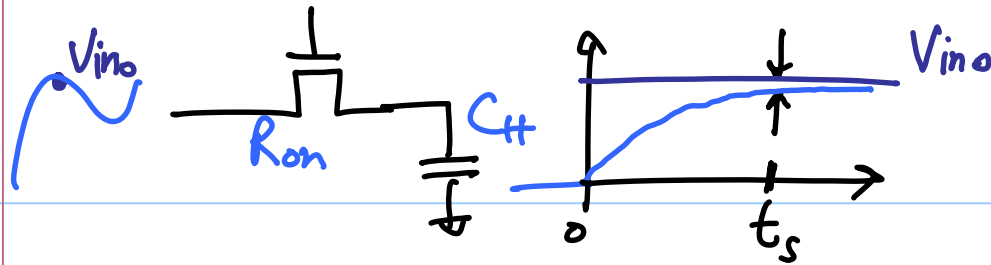

Time - constant

$$\tau = R_{on} \cdot C_H$$

W/L

$$\frac{V_{out}}{V_{in0}} = (1 - e^{-t_s/\tau})$$

$$V_{out} = (1 - \epsilon) V_{in0}$$

$$t_s = \tau \ln\left(\frac{1}{\epsilon}\right)$$

of time-constants
for settling
↓
 t_s/τ

% error	ϵ	t_s/τ
10%	0.1	2.3
1%	0.01	4.6
0.1%	0.001	6.9
0.01%	0.0001	9.21


Precision Considerations:

- ① channel "charge injection"
- ② clock feedthrough
- ③ kT/C Noise

Assuming $V_{out} = V_{in}$


$$Q_{ch} = WL C_{ox} (V_{gs} - V_{thn})$$
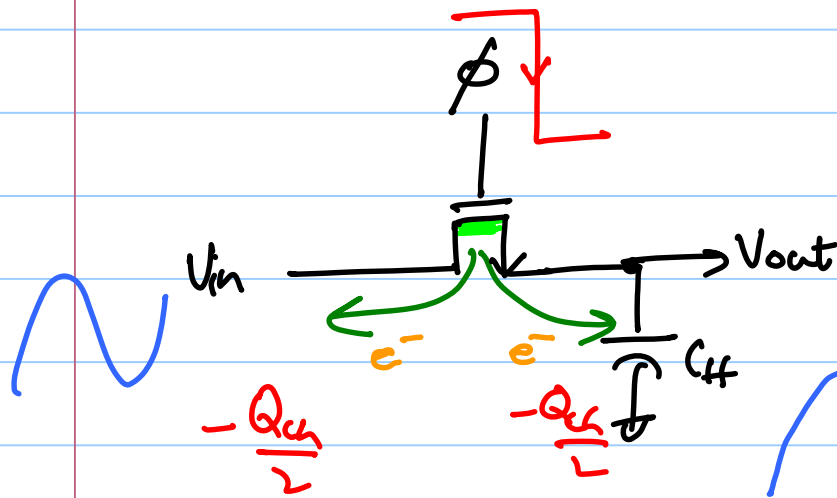
$$= WL C_{ox} (V_{DD} - V_{in} - V_{thn})$$



$$\Delta V \approx -\frac{Q_{ch2}}{C_{\#}}$$
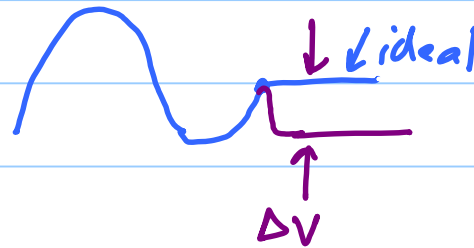
$$\Delta V = -\frac{WL C_{ox} (V_{DD} - V_{in} - V_{thn})}{2 C_{\#}}$$



ΔV
(pedestal error)

$$V_{thn0} + \gamma (\sqrt{2\phi_B + V_{in}} - \sqrt{2\phi_B})$$

$$\Delta V = \frac{-WL C_{ox} (V_{DD} - V_{in} - V_{THN})}{2C_H}$$

$$\Delta V \propto WL$$

$$\propto \frac{1}{C_H}$$

* Assumption of $-\frac{Q_{ch}}{Z}$ being injected into C_H

↳ in reality depends upon the $Z_D + Z_S$
at the time of clock transition

↳ no exact expression

↳ as a worst estimate, assume all of
 $-Q_{ch}$ is injected into C_H .

Impact of C.I. on precision


$$C_{ox} \stackrel{\Delta}{=} C_{ox}'$$

$$V_{out} \leq V_{in} - \Delta V$$

$$= V_{in} - \frac{WL C_{ox} (V_{DD} - V_{in} - V_{THW})}{C_H}$$

neglecting the
phase shift b/w
 V_{in} & V_{out}
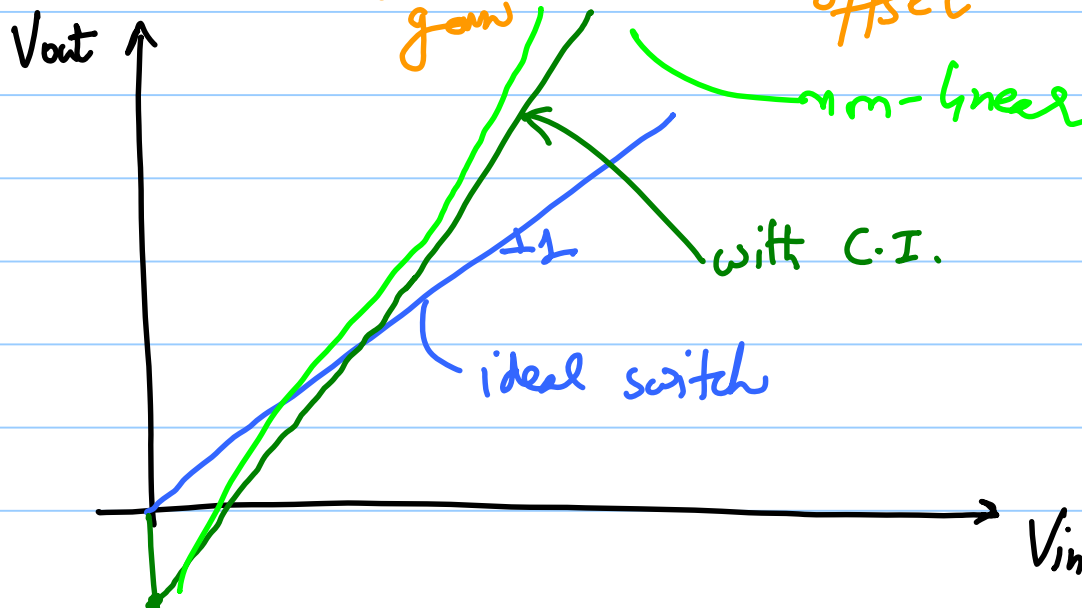
$$\Rightarrow V_{out} = V_{in} \left(1 + \frac{WL C_{ox}}{C_H} \right) - \frac{WL C_{ox}}{C_H} (V_{DD} - \underline{V_{THW}})$$



$$V_{out} = V_{in} \left(1 + \frac{WLC_{ox}}{C_H} \right) + \gamma \frac{WLC_{ox}}{C_H} \sqrt{2\phi_B + V_{in}}$$

$$- \frac{WLC_{ox}}{C_H} \left(V_{DD} - V_{THN0} + \gamma \sqrt{2\phi_B} \right)$$



fixed

* Nonlinearity in the input-output characteristics


Charge-injection introduces errors in S/C circuits

$\left. \begin{array}{l} \rightarrow \text{gain error} \\ \rightarrow \text{DC offset} \end{array} \right\}$ can tolerate using circuit techniques

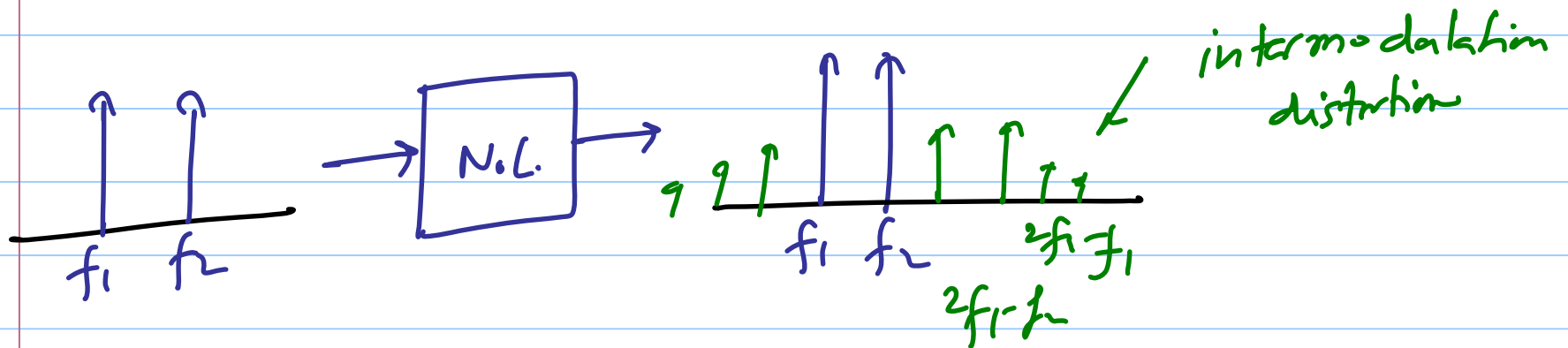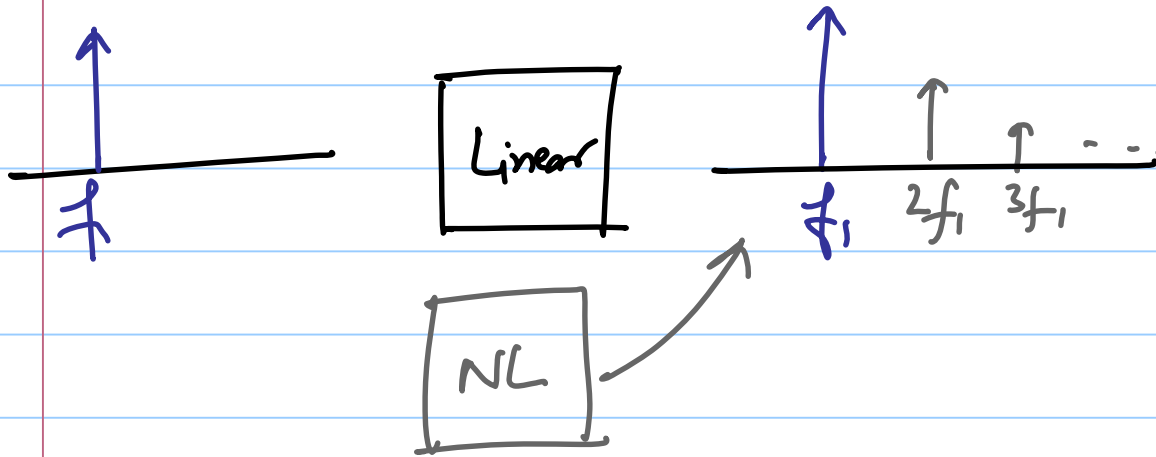$\left. \rightarrow \text{non-linearity} \right\}$ cannot be tolerated



② clock feedthrough :

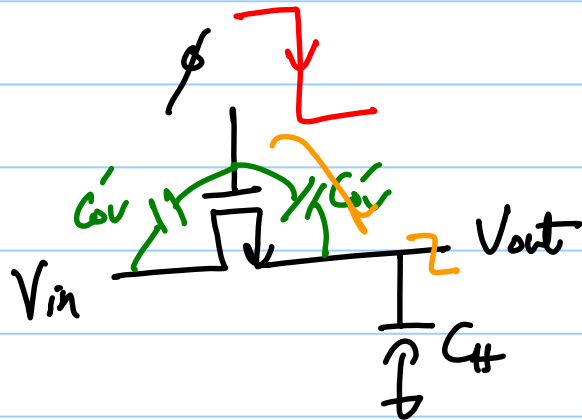

Capacitive Divider ↙ overlap Cap

$$\Delta V = V_{clk} \cdot \frac{W C_{ov}'}{W C_{ov}' + C_{\#}}$$

$C_{ov}' \Leftarrow$ overlap cap per unit width

$\Delta V \Leftarrow$ indep of V_{in}


$\rightarrow$ introduces a constant offset in the sampled output

$N \uparrow \rightarrow \Delta V \uparrow$

could use $C_{\#} \gg W C_{ov}'$

Charge injection Cancellation

①

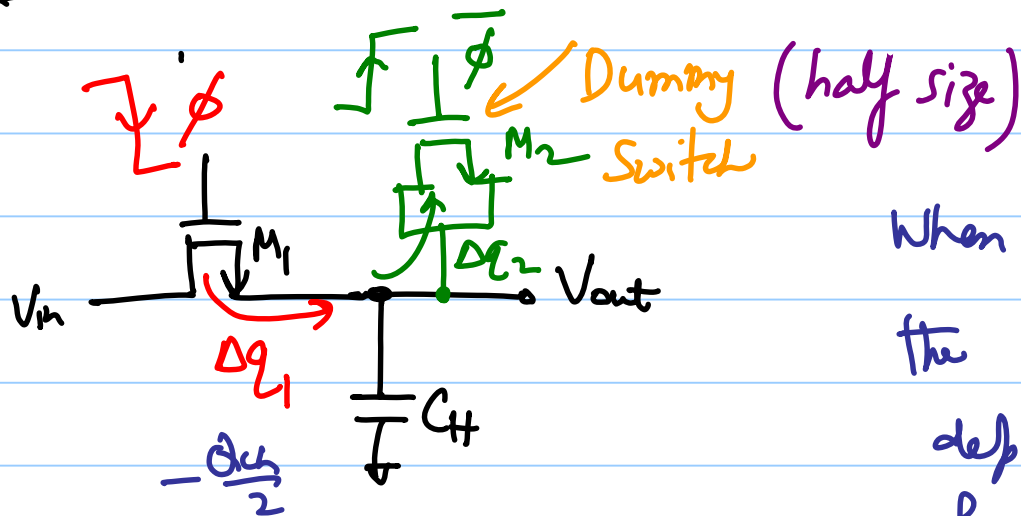

When M_1 turns off & M_2 turns on the channel charge Δq_1 deposited on C_{ff} is absorbed by M_2 to create its channel (Δq_2)

for perfect cancellation



$$\Delta q_1 = \Delta q_2$$

$$\frac{W_1 L_1 C_{ox}}{2} (V_{DD} - V_{in} - V_{THN1}) = W_2 L_2 C_{ox} (V_{DD} - V_{in} - V_{THN2})$$

for $W_2 = \frac{W_1}{2}$ & $L_2 = L_1$ it will work!

the assumption of $\frac{1}{2}$ way splitting makes it less robust

However

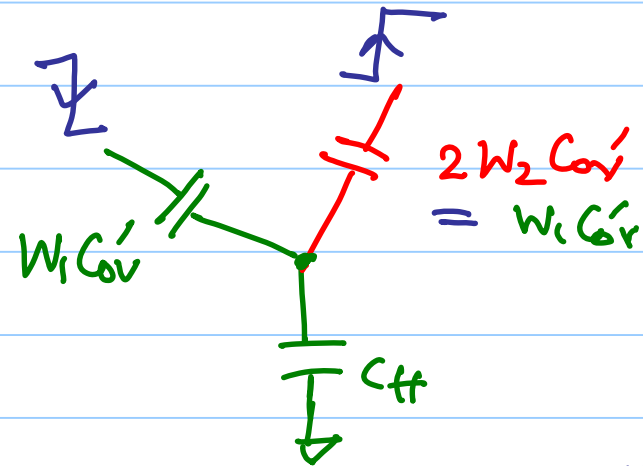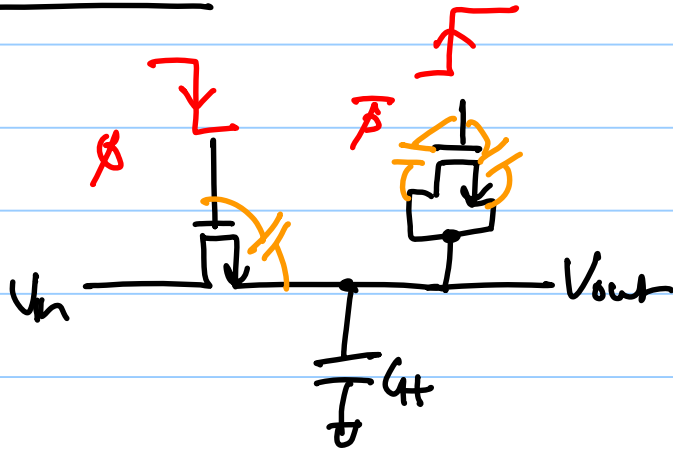


Clock feedthrough is cancelled using this scheme

$\Rightarrow$ Soln' use $\frac{1}{2}$ -size dummy to absorb injected charge.

②

Complementary Switches

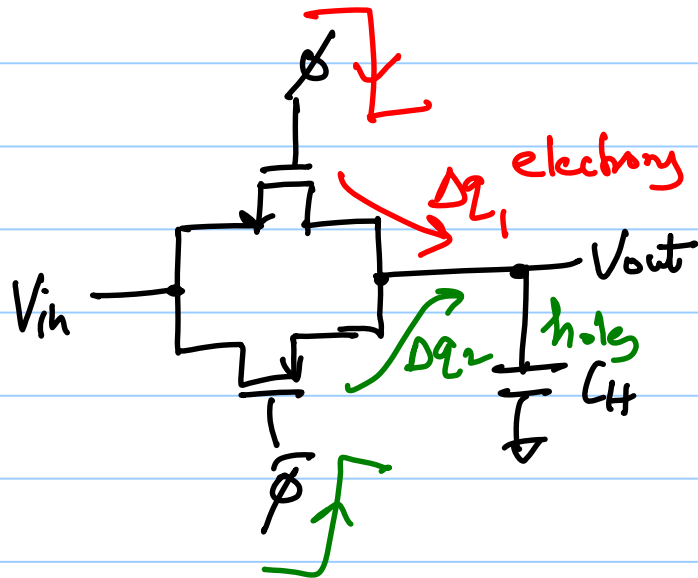

NMOS & PMOS

↳ inject opposite charge packets

for $\Delta Q_1 = \Delta Q_2$


$$W_1 L_1 C_{ox} (V_{clk} - V_{in} - V_{thp}) = W_2 L_2 C_{ox} (V_{in} - V_{thn})$$

We must have

cancellation only works for one input value $\therefore$

* Doesn't provide clock feedthru cancellation
as $C_{ovn} \neq C_{oup}$

③

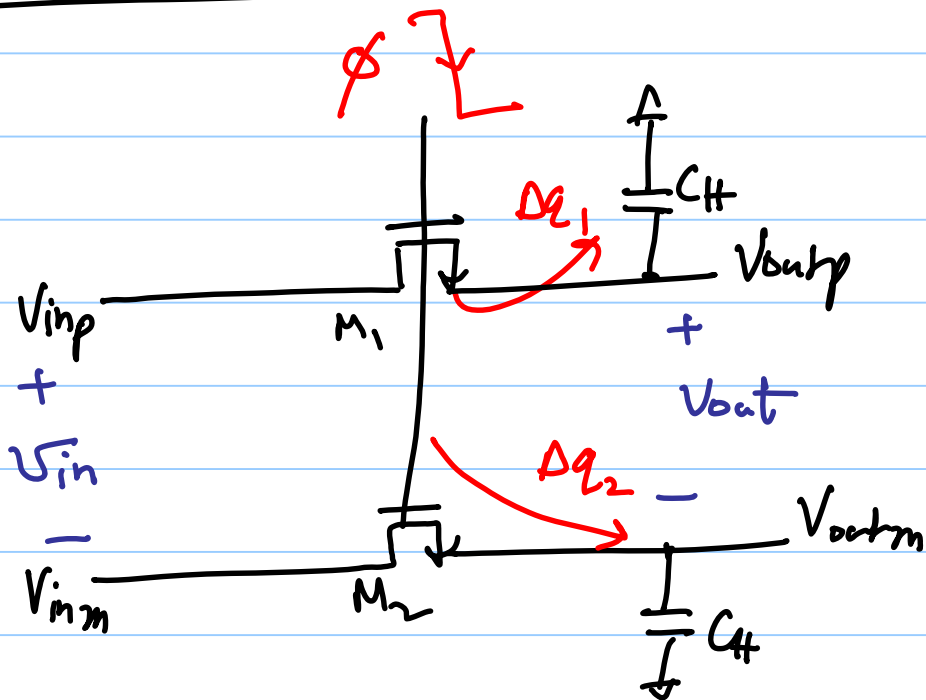

Differential error charge

$$\Delta Q = \Delta Q_1 - \Delta Q_2 = WLC_x [-(V_{inp} - V_{inm}) + (V_{THN2} - V_{THN1})]$$

$$= WLCox \left[\underbrace{-(V_{ip} - V_{inn})}_{1^{st} \text{ order}} + \gamma \underbrace{(\sqrt{2\phi_B + V_{inn}} - \sqrt{2\phi_B + V_{ip}})}_{\text{odd function}} \right]$$

* No Dc offset due to C.I.

* non-linear terms $\Rightarrow$ odd-order distortion remains

All even-order distortion is cancelled