

ECE 614 - Lecture 15


Note Title

10/14/2014

$V_{DD} - R$ bias


" $10\mu A$ "

verilogA


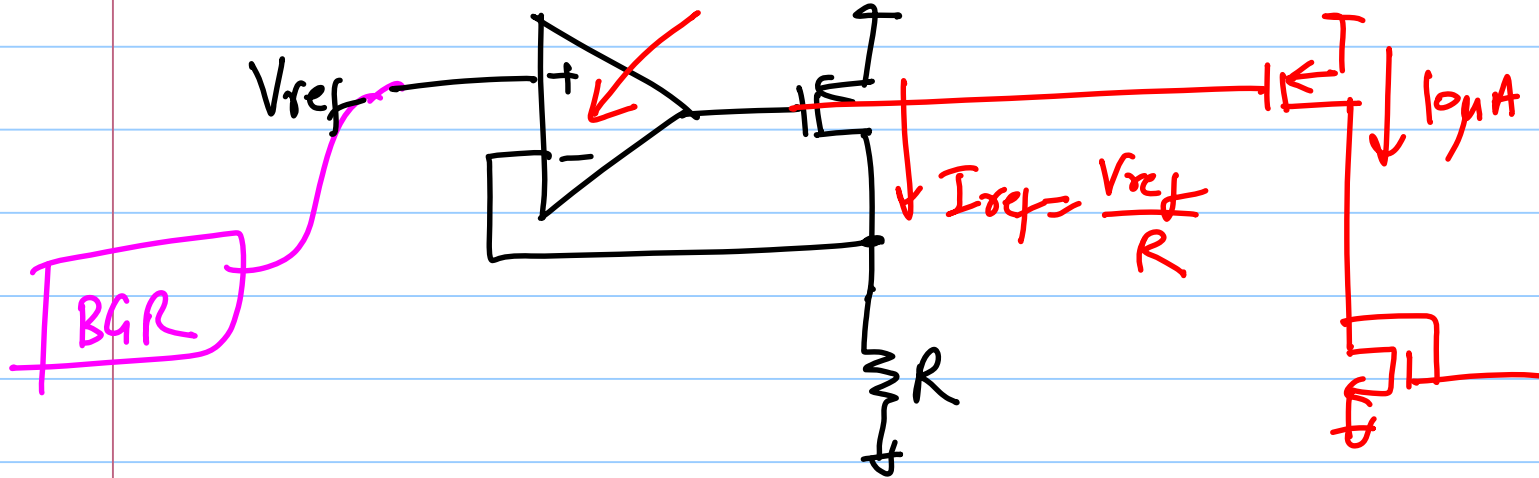


Unity-Gain Sampler (S/H), Buffer

S/H Buffer

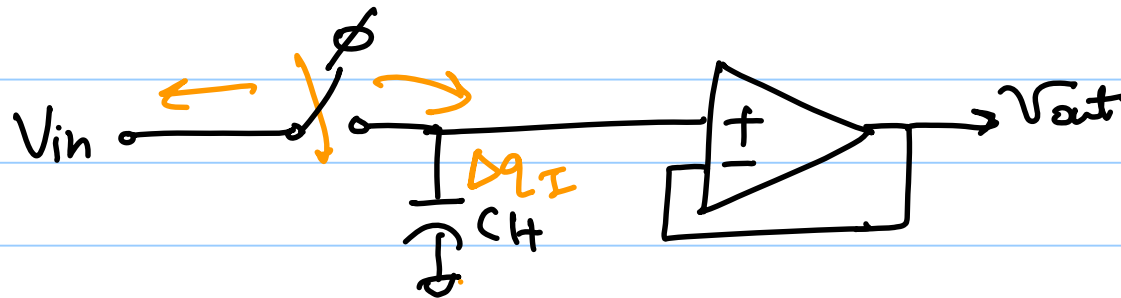


charge injection limits accuracy.

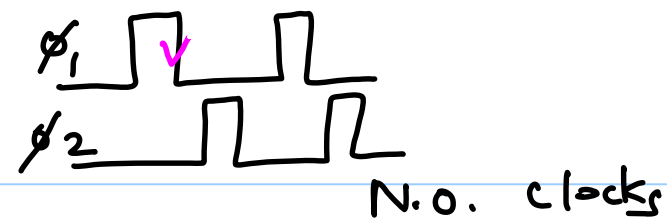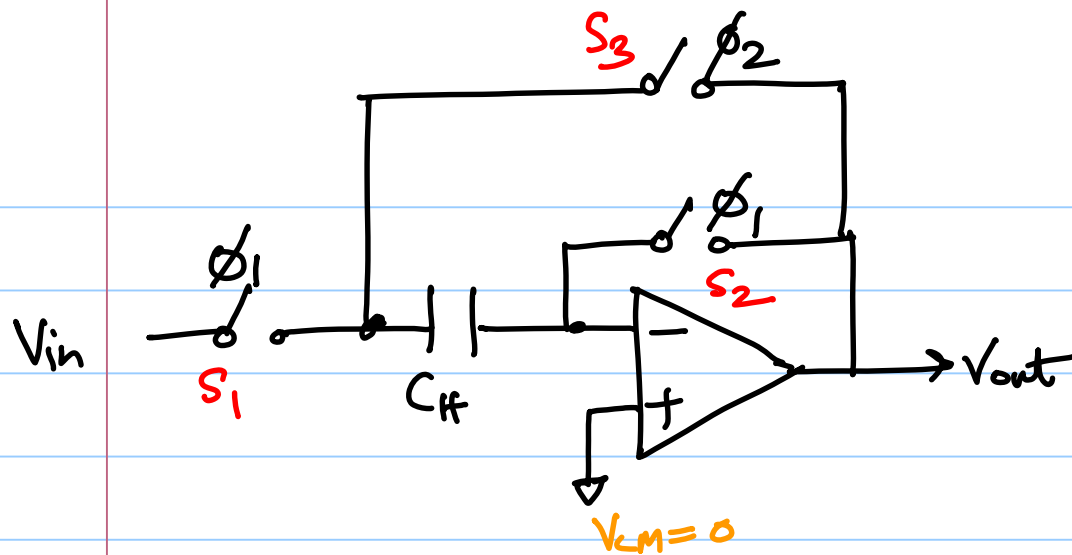


Assume Ideal opamp

Sampling mode ($\phi_1=1$)

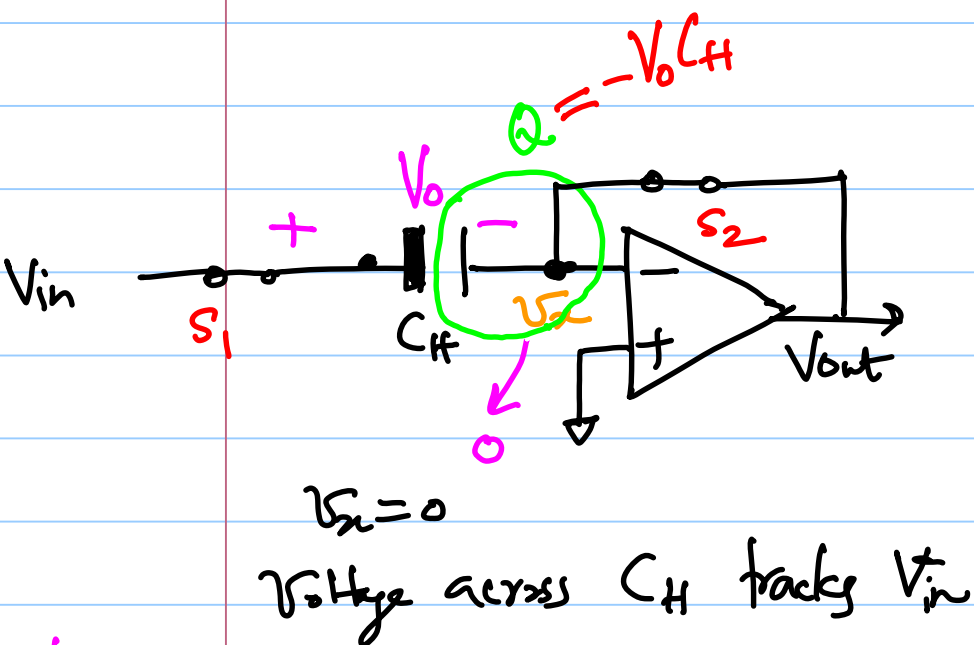

$\phi_2=1$ (Buffering mode)

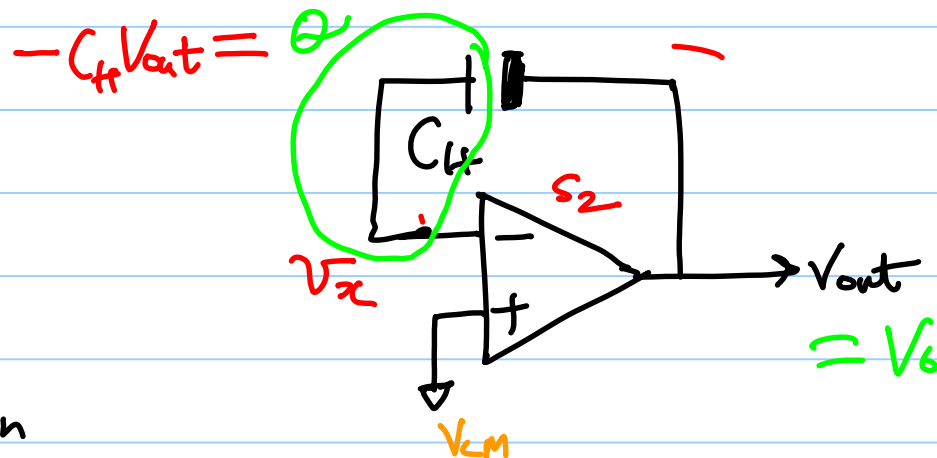


→ When $t=t_0$, $\phi_1 \searrow$

$V_{in} = V_0$ is stored on C_H



due to conservation of charge
at the surface connected to
 V_x

$$-C_H V_{out} = -C_H V_0$$


$$V_{out} \Rightarrow V_0$$

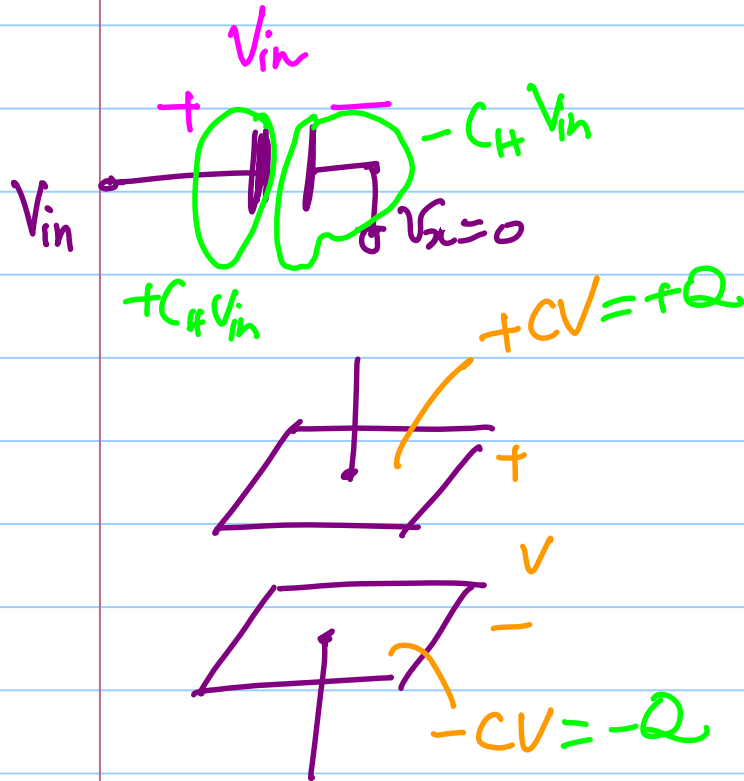

Aside

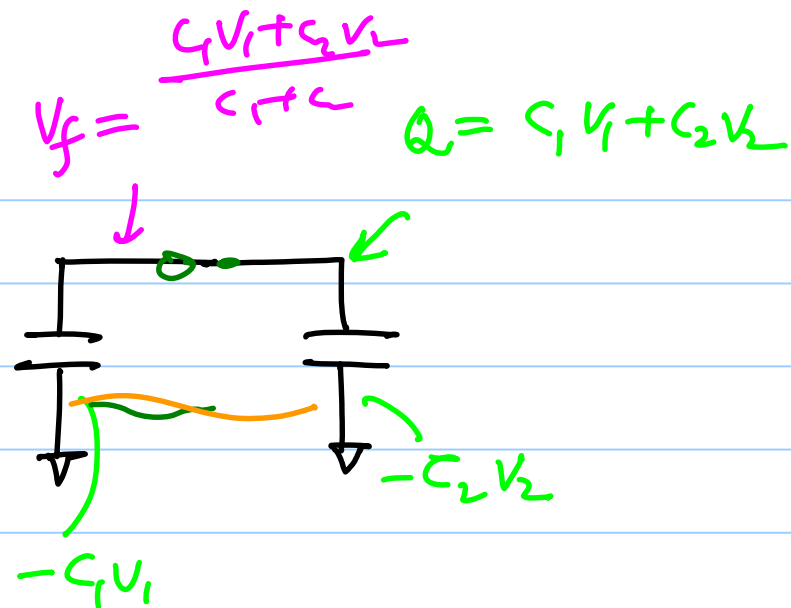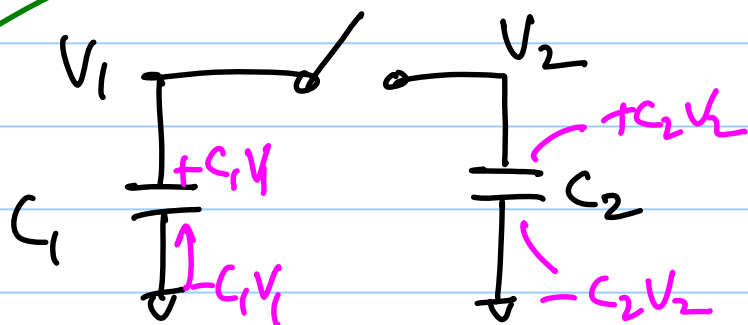


ϕ_1

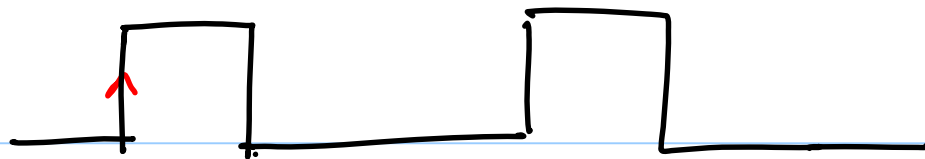


ϕ_2





V_{in}

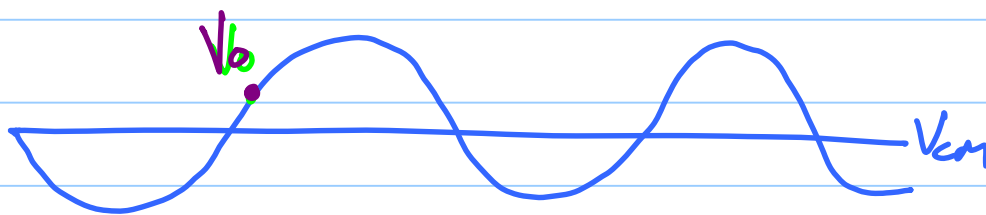

V_{out}

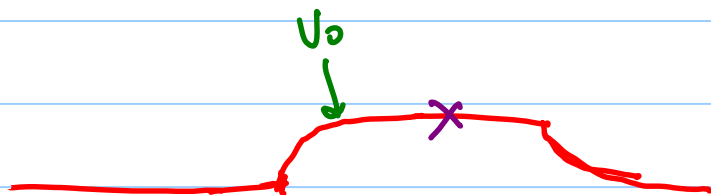

Slow-Mo Recap

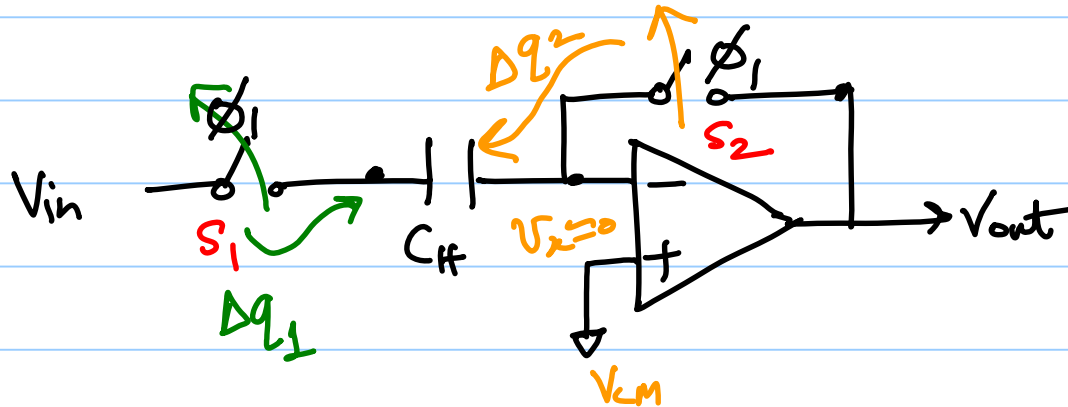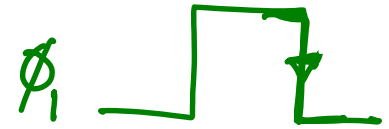


$$\Delta Q_1 = WLC_{ox} (V_{CLK} - \underbrace{V_{in}} - \underbrace{V_{THN}})$$

* Charge injection from S_1 to C_F is still a problem


$$\Delta Q_2 = WLC_{ox} (V_{CLK} - V_{THN})$$

↳ constant charge injected
↳ can be removed by differential operation

Trick: Delayed sampling clock

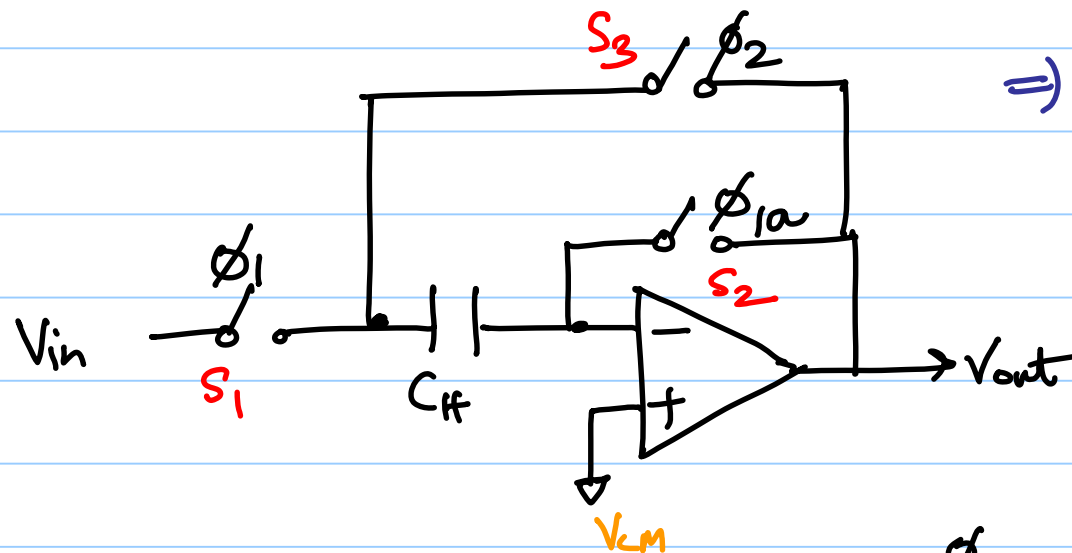


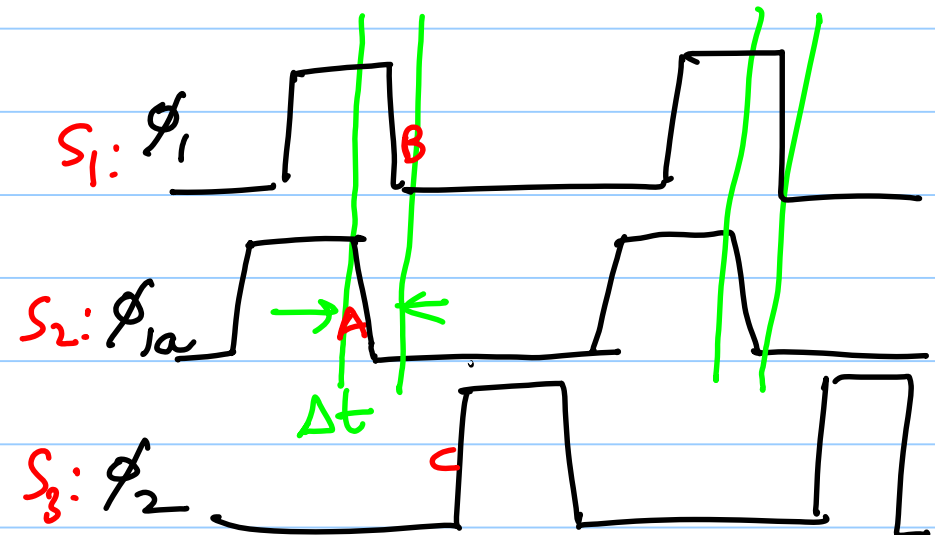ϕ_{1a} is advanced phase of ϕ_1
 $\Rightarrow$ Turn off S_2 earlier than S_1




ϕ_{1a} falls earlier than ϕ_1

①

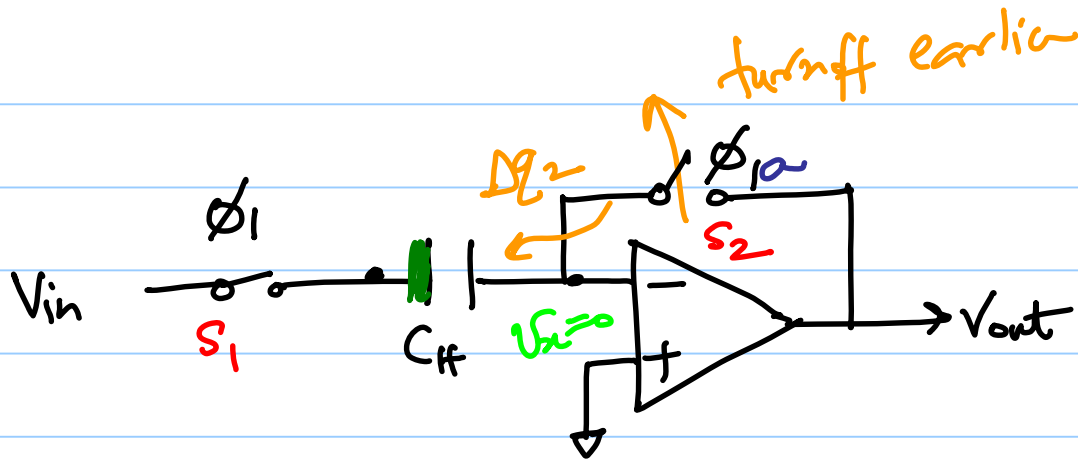

②

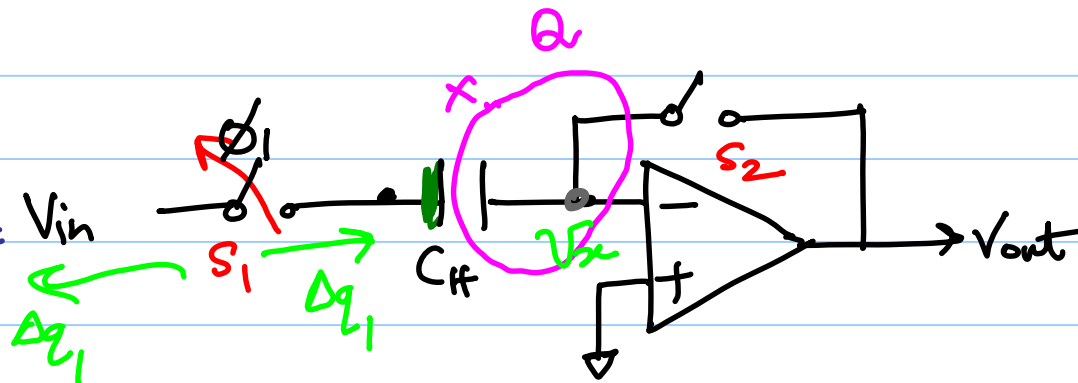

ΔQ_1 is injected from S_1 into one of the plates of C_H .

After $\phi_{1a} \downarrow$ i.e. S_2 turned off, total charge at X cannot change as no path exists for electrons to flow in or out of this node
 $\Rightarrow$ Conservation of charge at surface X

Simplify life

③ $S_3 \uparrow$

total charge on X is conservation

$$Q = -C_x V_x = -(V_{out} - V_x) C_H \rightarrow ①$$

when $V_0 = 0$,


$$V_x = -\frac{V_{out}}{A_v} \rightarrow ②$$

①②

$$-(C_x + C_H) \frac{V_{out}}{A_v} - V_{out} C_H = 0$$


$$\Rightarrow V_{out} = 0$$

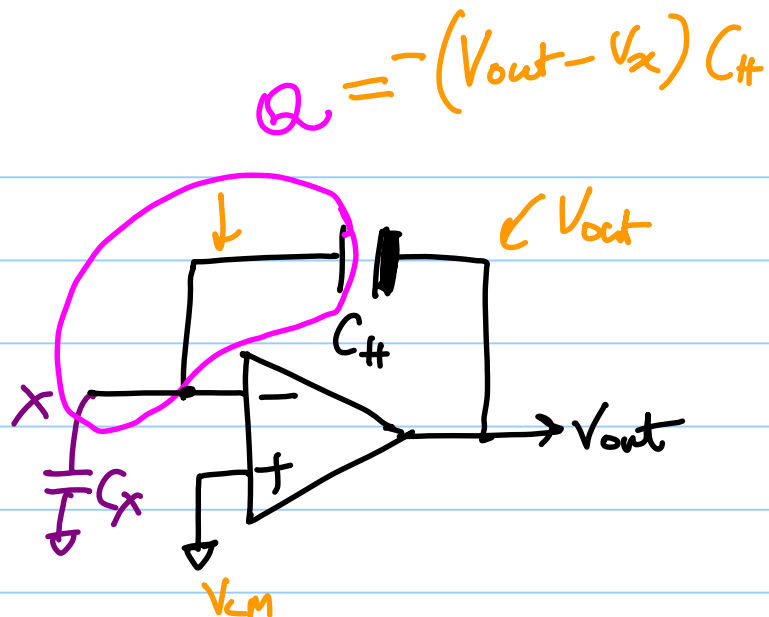→ result is independent of A_v ,
parasitic C_H value, A_v (opamp gain)




Do this for $V_{in} > 0$

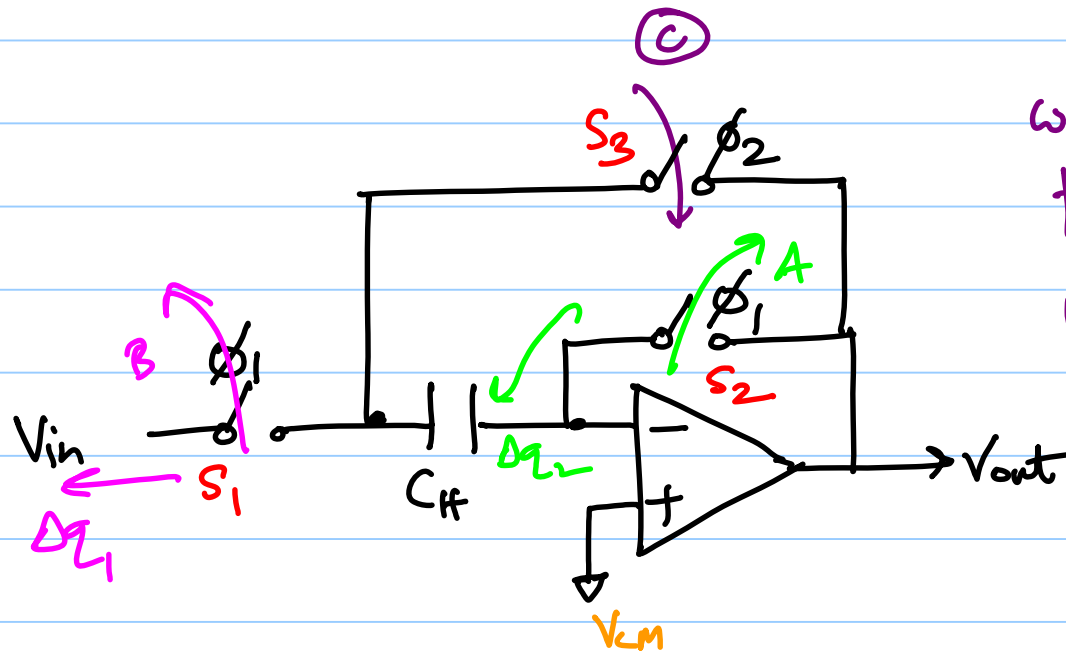Qualitatively, all the ΔQ_1 is absorbed into the source (V_{in})




when S_3 is turned on, the inversion layer charge is supplied by the opamp (not C_F)

①

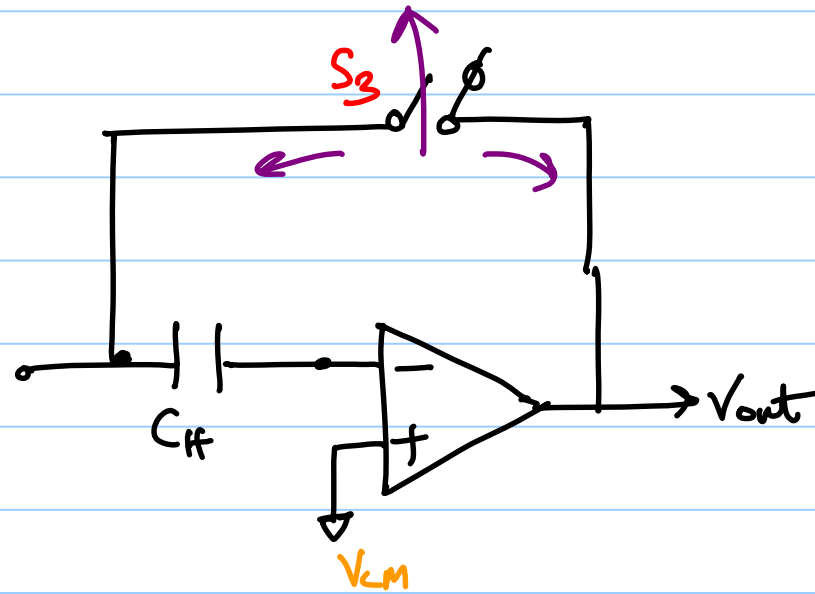

charge injected by S_3 is
unimportant

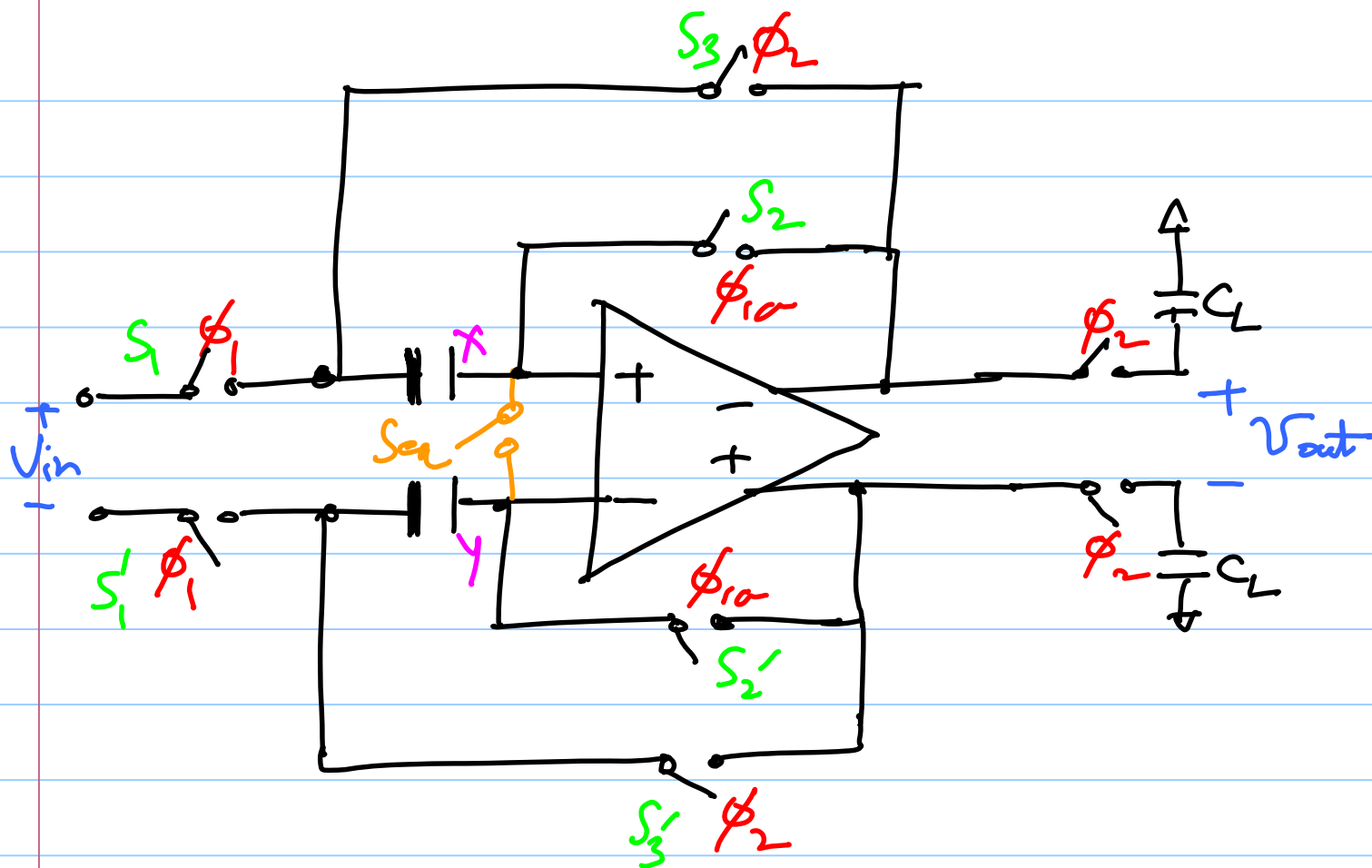

mismatch between S_2 & $S_2' \Rightarrow \Delta q_2 - \Delta q_2' \neq 0$

$S_2 \Rightarrow$ turns off slightly after S_2 & S_2' but before S_1 & $S_1' \Rightarrow$ equalizes the charge at nodes x & y