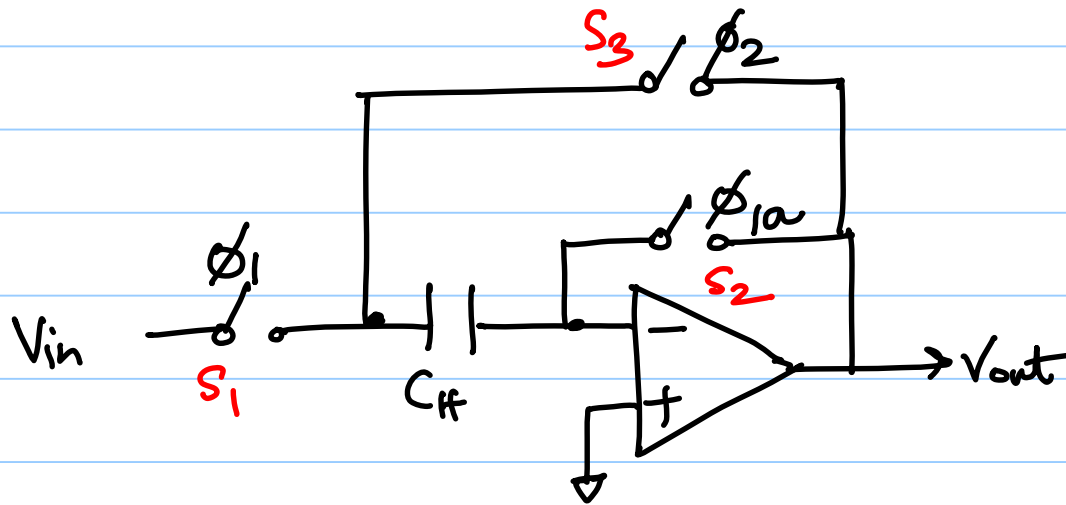


EECE 614 - Lecture 16

Note Title

10/16/2014



$\phi_{1,a} \Rightarrow$ sampling mode
 $\phi_2 \Rightarrow$ hold mode


A_v
"fun"

in S/C circuits

Single Stage Folded Cascode

Impact of finite $A_v \ll \infty$ DC gain

Sampling mode

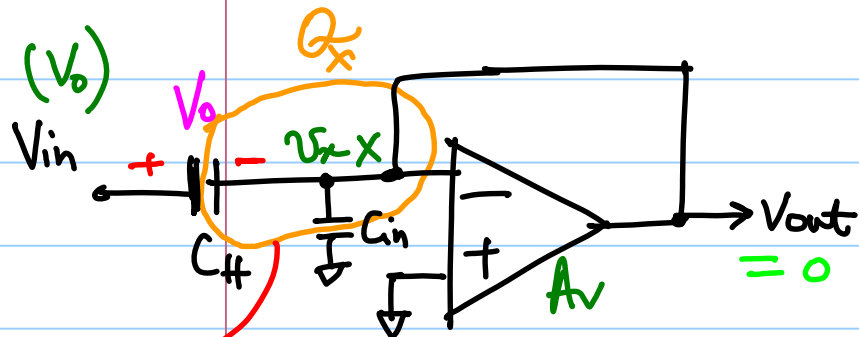

$$Q_x = -C_H V_0$$


$$V_{out} = A_v (0 - V_x)$$

$$V_x = -A_v V_x$$

$$V_x = 0$$

$$Q_x = -(V_{out} - V_x) C_H + C_{in} V_x$$

Hold mode

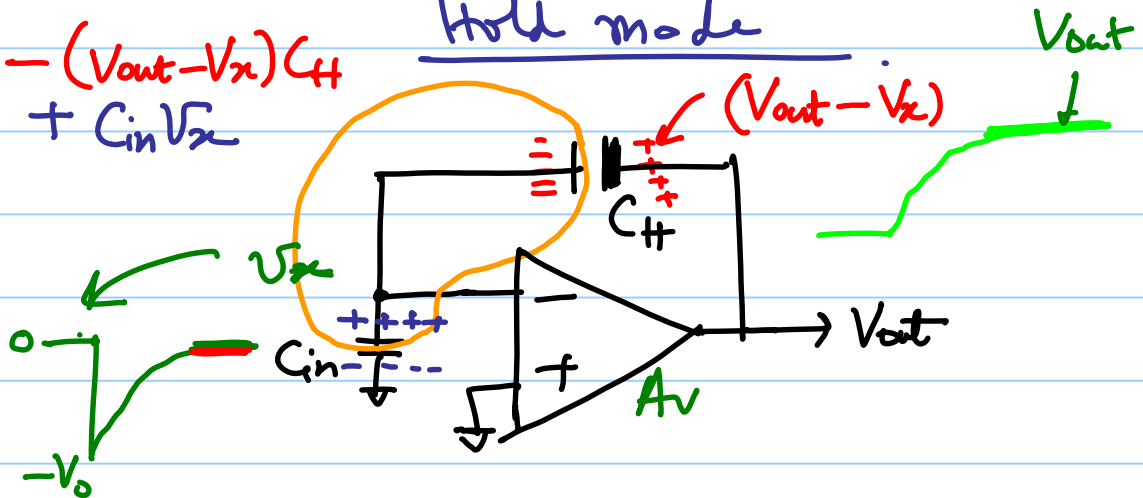

In steady-state, $V_x = ?$

$$V_{out} = A_v (0 - V_x)$$

$$\Rightarrow \underline{V_x = -\frac{V_{out}}{A_v}} \rightarrow \textcircled{1}$$

$$Q_x = -C_H V_0 = -(V_{out} - V_x) C_H + C_{in} V_x$$

$$\Rightarrow V_{out} = \frac{V_x (C_{in} + C_H) + V_0 C_H}{C_H}$$

$$\frac{1}{1+x} \approx 1-x$$

$$|x| \ll 1$$

$$V_{out} = V_o + \overbrace{V_x \left(1 + \frac{C_{in}}{C_H}\right)}^{\text{error}} \longrightarrow \textcircled{2}$$

$$\Rightarrow V_{out} = V_o - \frac{V_{out}}{A_v} \left(1 + \frac{C_{in}}{C_H}\right)$$

$$\Rightarrow V_{out} = \frac{V_o}{1 + \frac{1}{A_v} \left(1 + \frac{C_{in}}{C_H}\right)} = V_o \left[1 - \frac{1}{A_v} \left(1 + \frac{C_{in}}{C_H}\right)\right]$$

$$= V_o \left[1 - \frac{1}{A_v \beta}\right]$$

$$\beta = \frac{C_H}{C_H + C_{in}} \Leftarrow \text{feedback ratio}$$

$$A_v \beta \Rightarrow \text{loop-gain}$$

Steady-state error $\propto \frac{1}{\text{loop-gain}}$

for precision $\Rightarrow A_v \uparrow$ also $C_{in} \ll C_H$

$$V_{in} = V_o$$


$$V_{out} = V_o (1 - \varepsilon)$$

$$\varepsilon = \frac{1}{\beta \cdot A_v}$$


Ex. $C_{in} = 0.5 \text{ pF}$
 $C_H = 2 \text{ pF}$

A_v needed for $\varepsilon \Rightarrow 0.1\%$

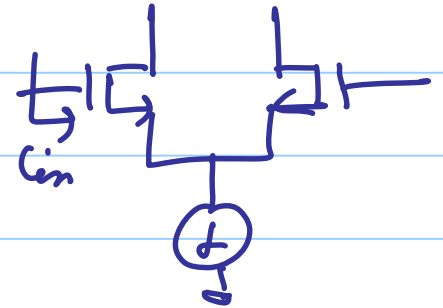$\Rightarrow 10^3 \Rightarrow \underline{\underline{60 \text{ dB}}}$



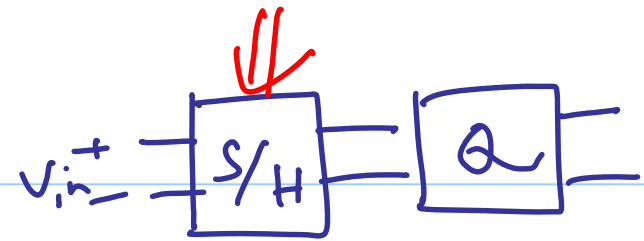$N=10\text{ bit ADC} \Rightarrow \text{S/H}$



$$V_{\text{LSB}} = \frac{V_{\text{ref}}}{2^N}$$


we want precision better than $\frac{1}{2} V_{\text{LSB}}$

$$\frac{1}{2} \text{LSB} \Rightarrow \frac{V_{\text{ref}}}{2^{N+1}}$$

We want S/H error $< \frac{V_{\text{ref}}}{2^{N+1}}$

$$\text{for } V_o = V_{\text{ref}}$$
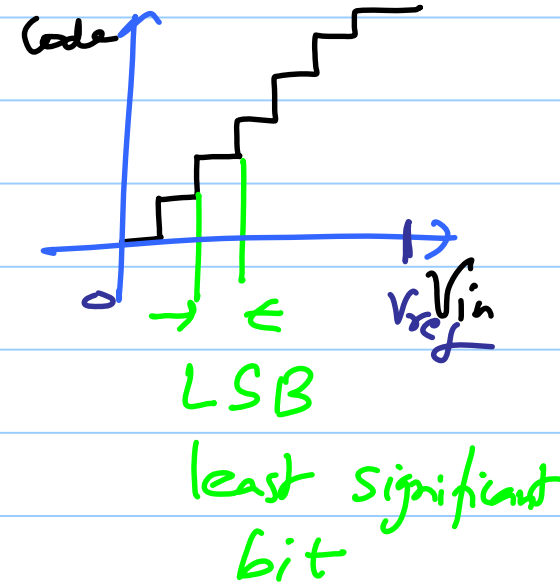
$$\frac{1}{A\beta} \varepsilon < \frac{1}{2^{N+1}} = \frac{1}{2^{11}}$$



$$A_{\beta} > 2^{11}$$

Let's say $\beta=1 \Rightarrow A > 2^{11} = 2000$
 $\Rightarrow 66 \text{ dB}$



$$\text{SNR} = 6.02 N_{\text{eff}} - 1.76 \quad \text{full-side line wave}$$

$\text{SNR} \approx 60 \text{ dB}$ for V_{LSB}
 66 dB for $\frac{1}{2} V_{\text{LSB}}$ resolution

Speed Considerations


$R_x = ?$

① Sampling mode:

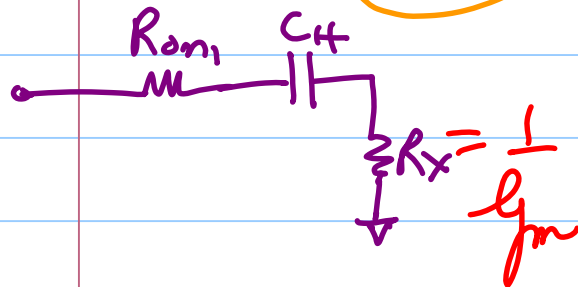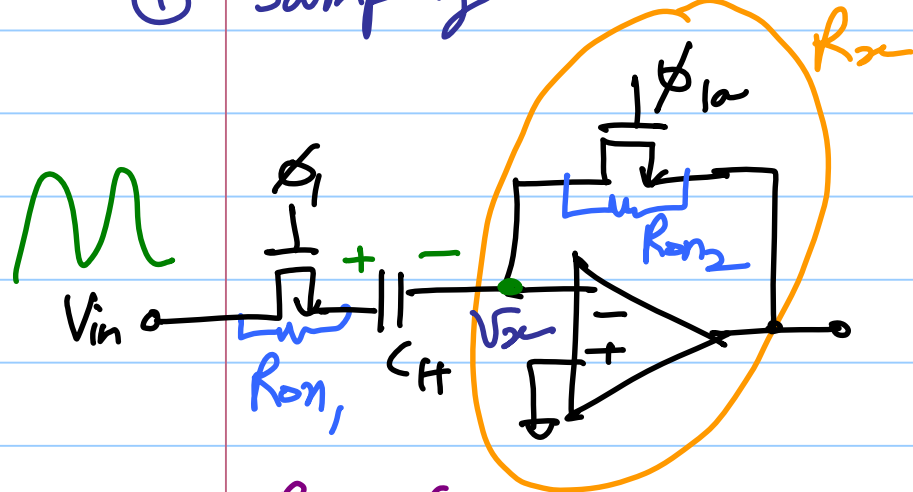

$$\tau_{\text{Sampling}} = \left(R_{on1} + \frac{1}{g_m} \right) C_H$$

$$4.7 \tau_{\text{Sampling}} < T_s / 2$$

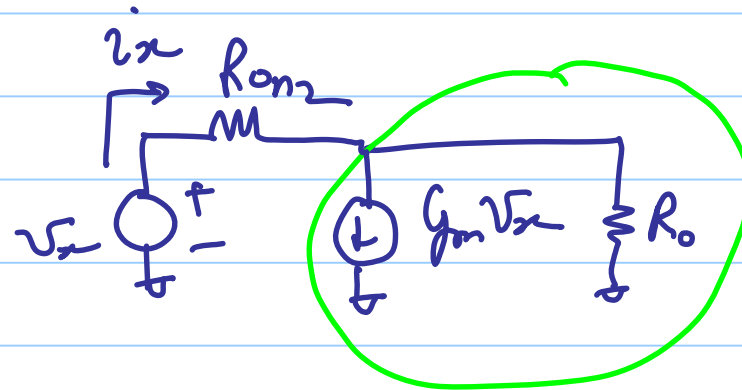

OTA

$$(i_x - g_m V_x) R_o + i_x R_{on2} = V_x$$



$$\Rightarrow R_x = \frac{V_x}{i_x} = \frac{R_o + R_{on2}}{1 + g_m R_o}$$

$$g_m R_o \gg 1$$


$$R_o \gg R_{on2}$$

$$\hookrightarrow \frac{R_o}{g_m R_o} \approx \frac{1}{g_m}$$

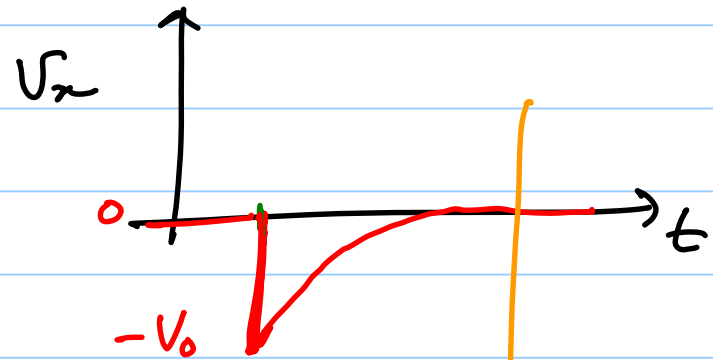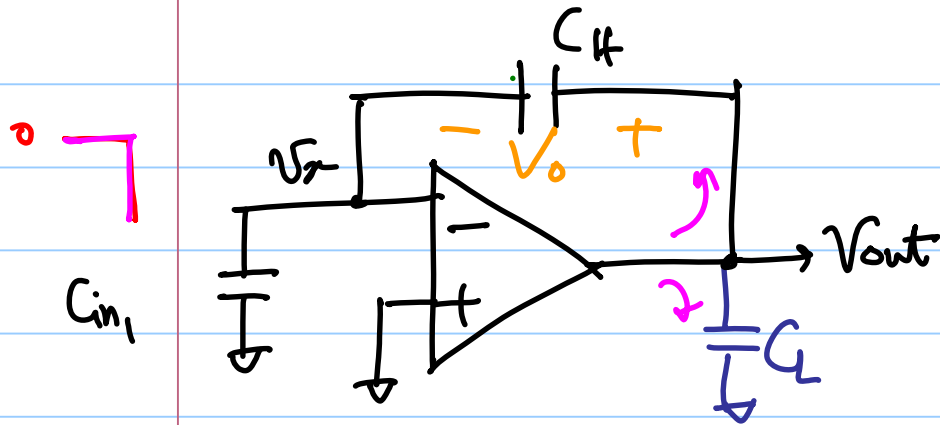Speed considerations in Hold/Amplification mode



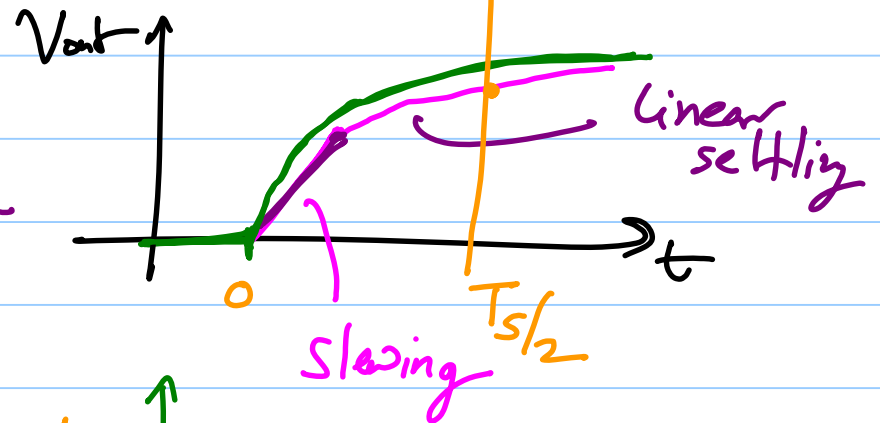
Slewing must be limited to at least $\frac{1}{4}$ of the settling time






$$T_{\text{slew}} < \frac{T_s}{8}$$

Single-stage $SR \approx \frac{I_{ss}}{C_{\text{load}}}$

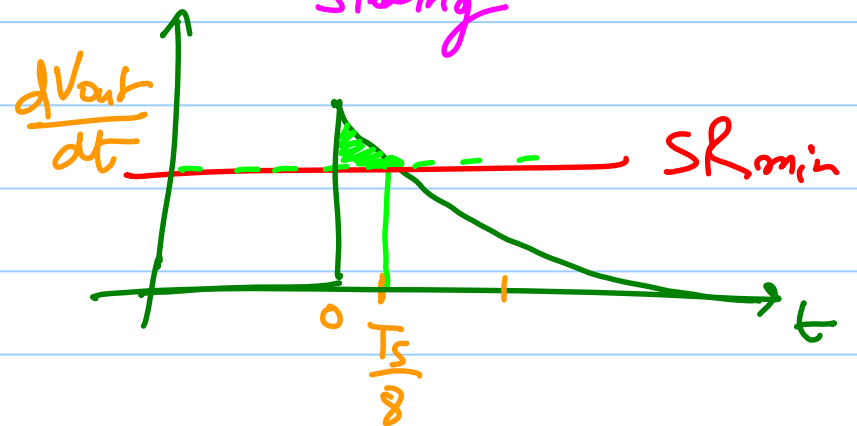Two-stage: $SR \approx \frac{I_{ss}}{C_c}$



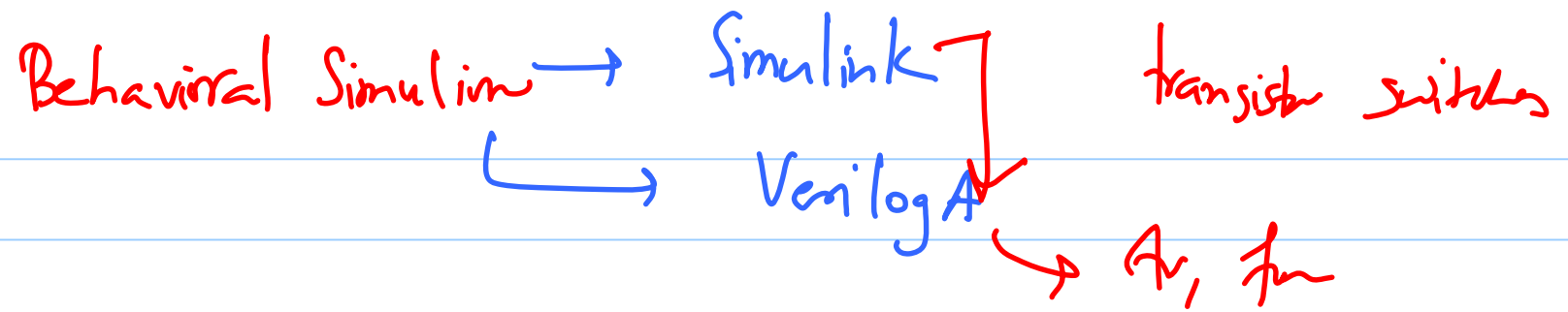

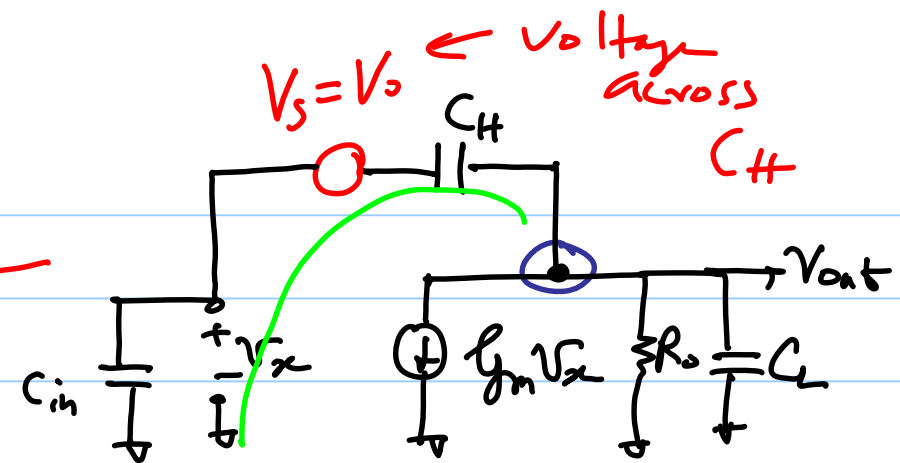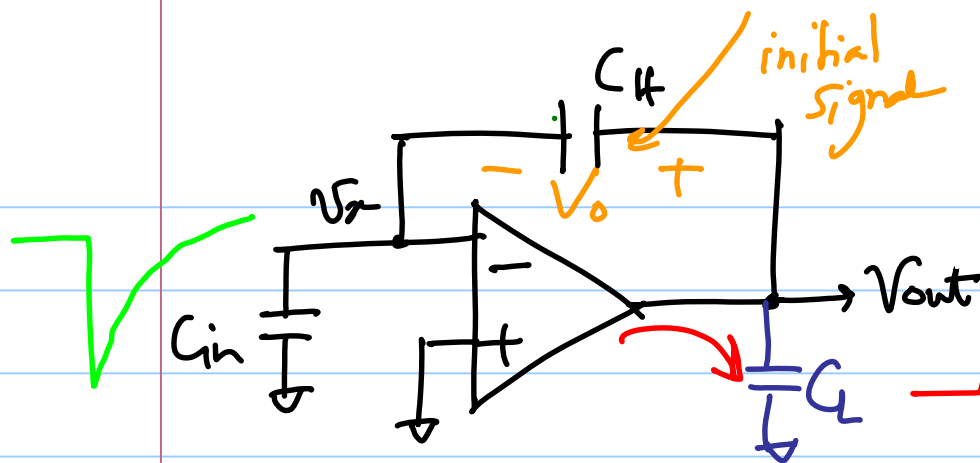

$$\frac{V_{out}(s)}{V_S}$$

$$\text{KCL: } V_{out} \left(\frac{1}{R_o} + sC_L \right) + g_m V_x = (V_S + V_x - V_{out}) sC_H \rightarrow (1)$$

$$\text{KVL: } V_x \frac{sC_{in}}{sC_H} + V_x + V_S = V_{out}$$

$V_x sC_{in}$ is the current through C_{in}

$$\frac{V_{out}}{V_s}(s) = \frac{(g_m + sC_{in})C_H}{(C_L C_{in} + C_{in} C_H + C_H C_L)s + g_m C_H}$$

$$\omega_{amp} = \frac{C_L C_{in} + C_{in} C_H + C_H C_L}{g_m C_H}$$

for $C_{in} \ll C_L, C_H \Rightarrow \beta \rightarrow 1$

$$\omega_{amp} \approx \frac{C_L}{g_m}$$



need sufficient
loop BW for
settling

$$\omega_{dom} = \frac{g_m}{C_L} \text{ for single stage OTA}$$

Depending upon the settling precision
0.1% $\Rightarrow 4.77$

$$4.7 \tau_{amp} \leq \frac{T_s}{2}$$

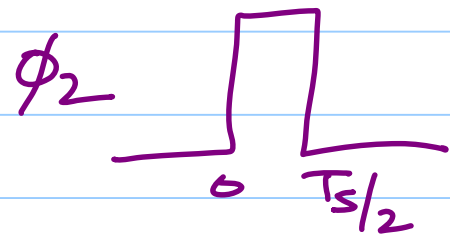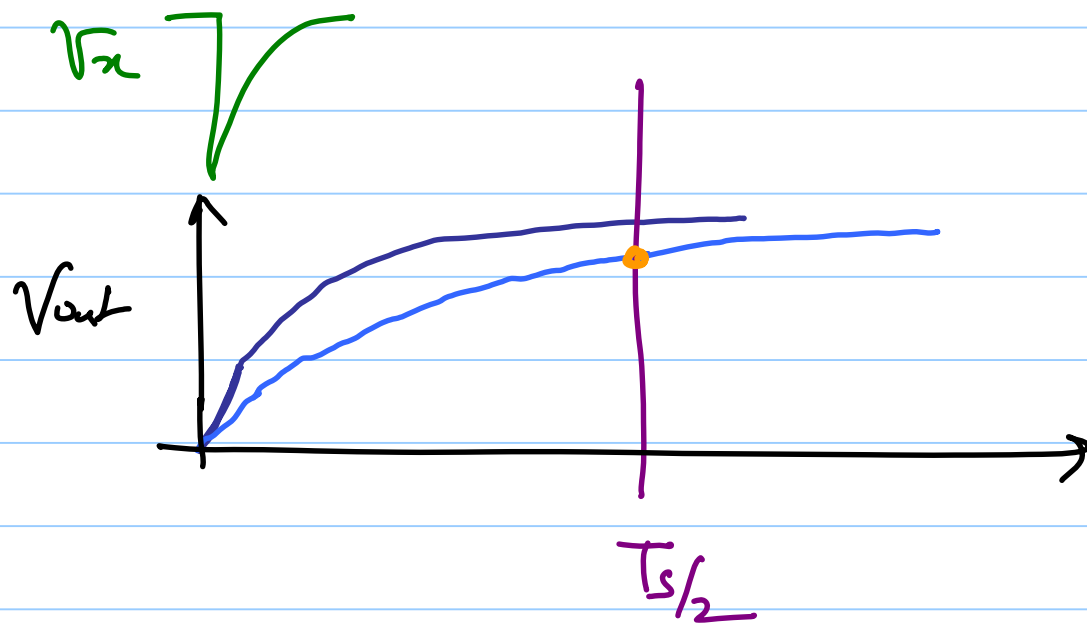$\rightarrow \Rightarrow$ ω_{um} for the opamp



Settling precision $\Rightarrow$ ω_{um}
 $SR = \frac{I_{ss}}{C}$