

ECE 614 - Lecture 17

Note Title

10/21/2014

S/H Buffer $\Rightarrow$ precision $\Rightarrow A_v \Rightarrow \beta A_v$
loop-gain

gain $\Rightarrow 1$

$\omega_{um} \Rightarrow$

"SR" $\Rightarrow$ should slow
for $< 25\%$ of
settling time

$$\beta = \frac{C_H}{C_{in} + C_H}$$

$$\sqrt{\frac{KT}{C}}$$

$$(1 - \frac{1}{A\beta}) \cdot V_o$$

ϵ

Inverting Amplifier




$p_{ss} \Rightarrow .op$

$p_{ac} \Rightarrow ac$

$p_{stb} \Rightarrow stb$

$p_{noise} \Rightarrow noise$

Inverting Amplifier

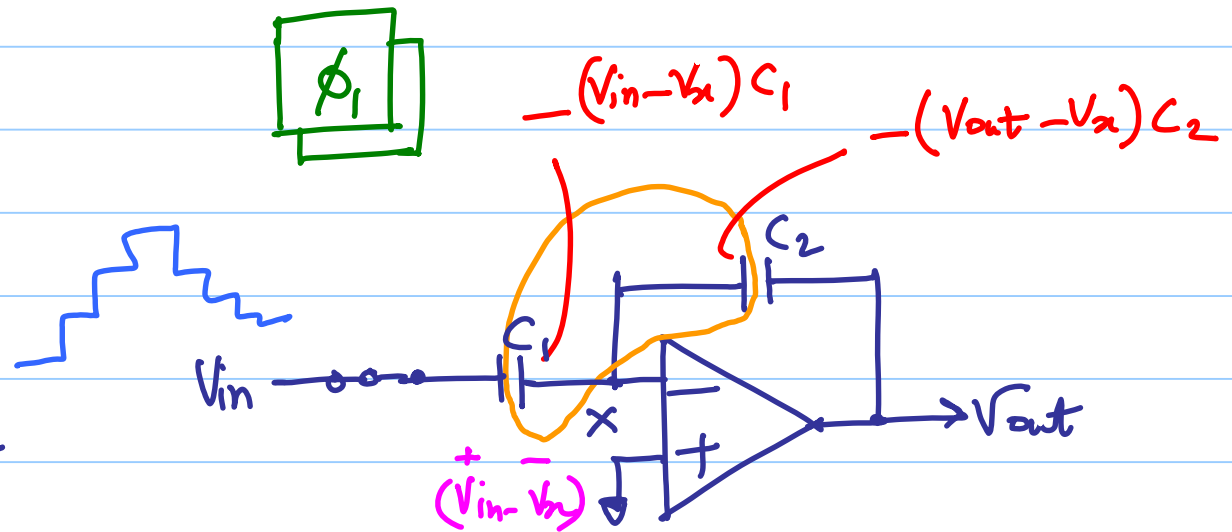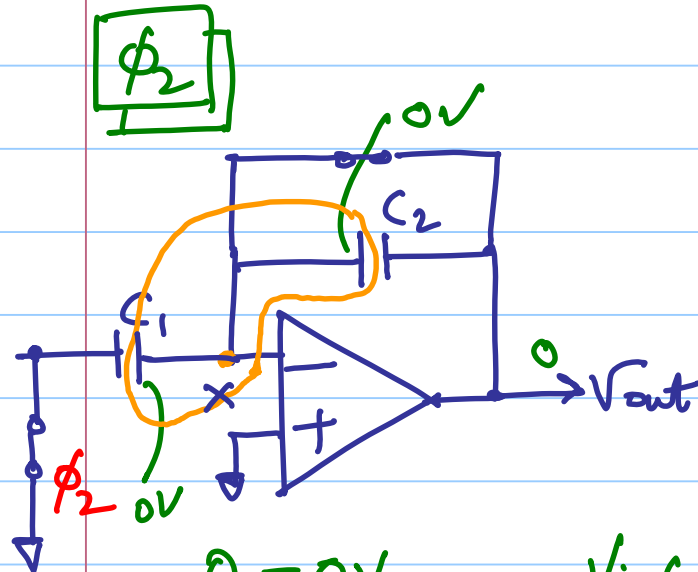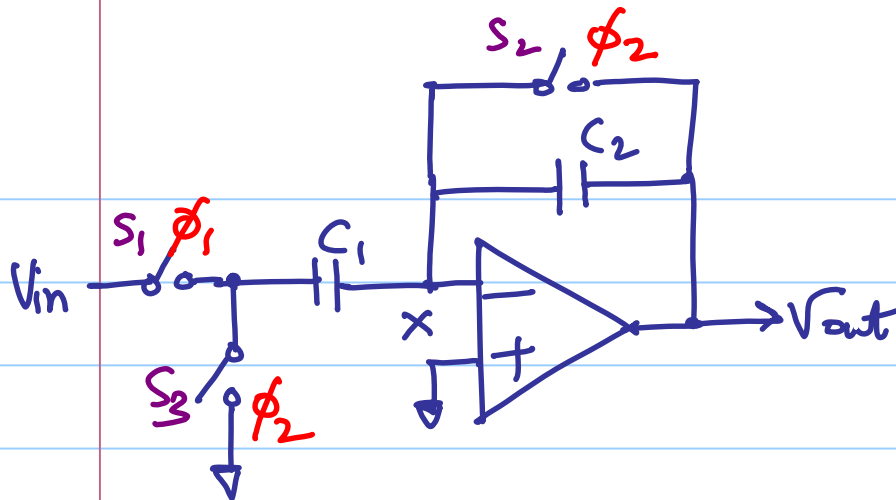

$$Q_x = 0V = -V_{in}C_1 + C_1V_x - V_{out}C_2 + C_2V_x = 0$$

$$V_{out} = A_v(0 - V_x) \Rightarrow V_x = \frac{V_{out}}{A_v}$$


for finite $V_{out} \Rightarrow V_x \rightarrow 0$ as $A_v \rightarrow \infty$

$$V_x = 0$$

$$\Rightarrow -V_{in}C_1 = V_{out}C_2$$


$$\Rightarrow \boxed{\frac{V_{out}}{V_{in}} = -\frac{C_1}{C_2}}$$

Inverting


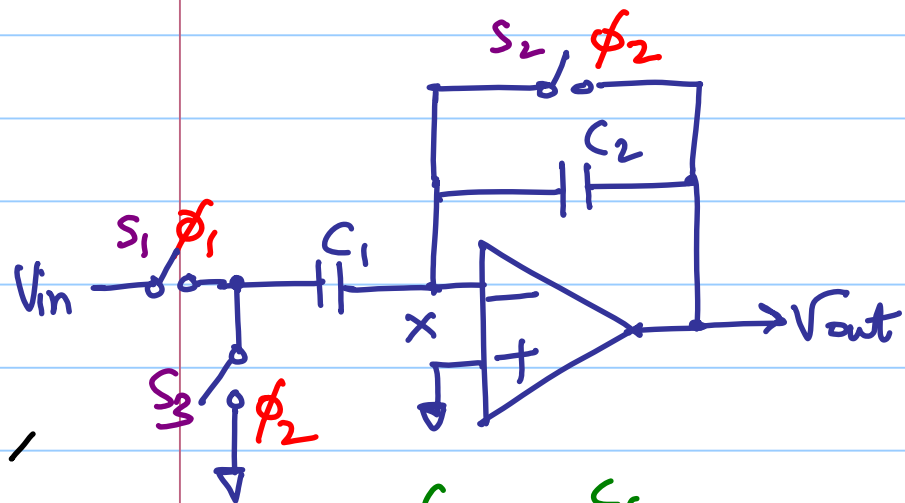


$$G = -\frac{C_1}{C_2}$$

Noninverting

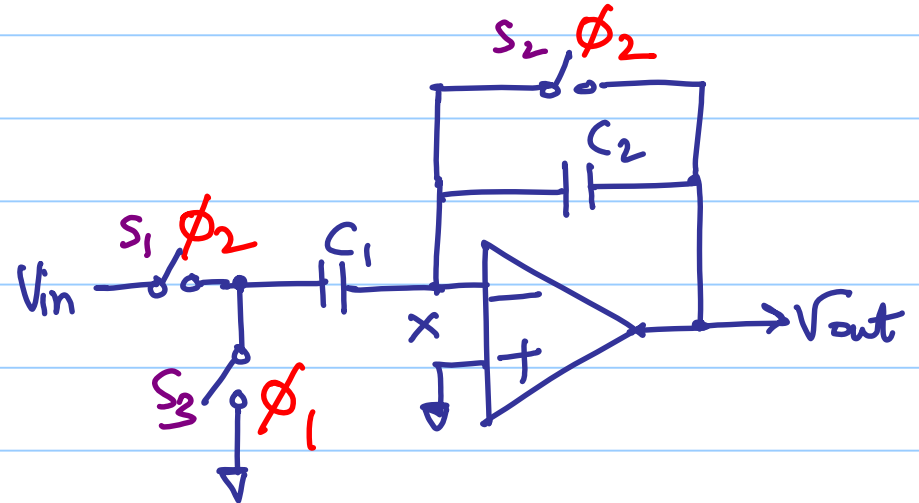

$$G = +\frac{C_1}{C_2}$$

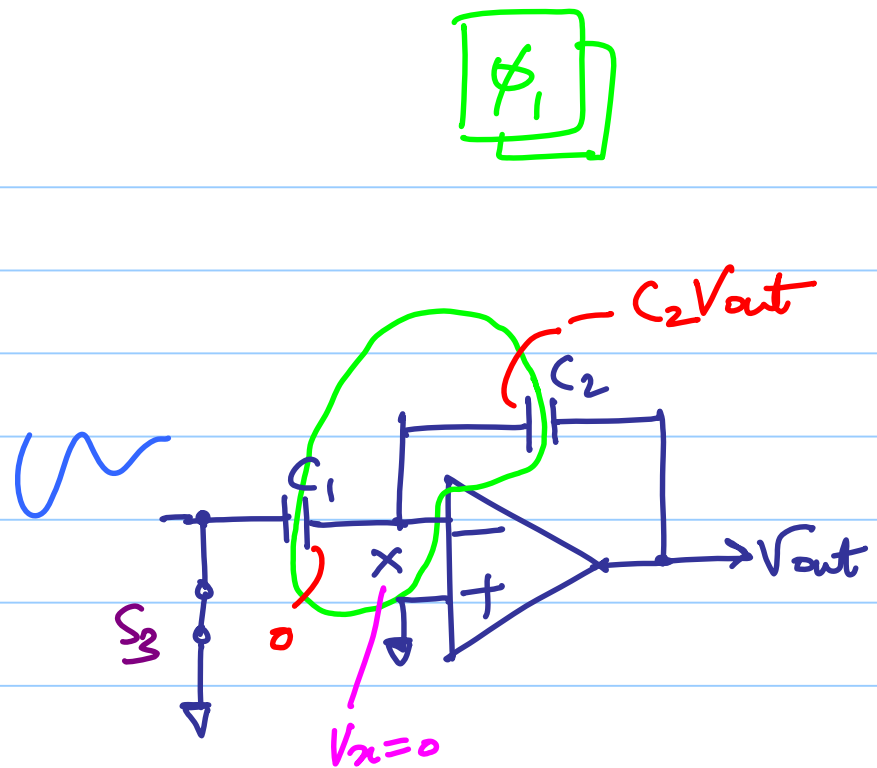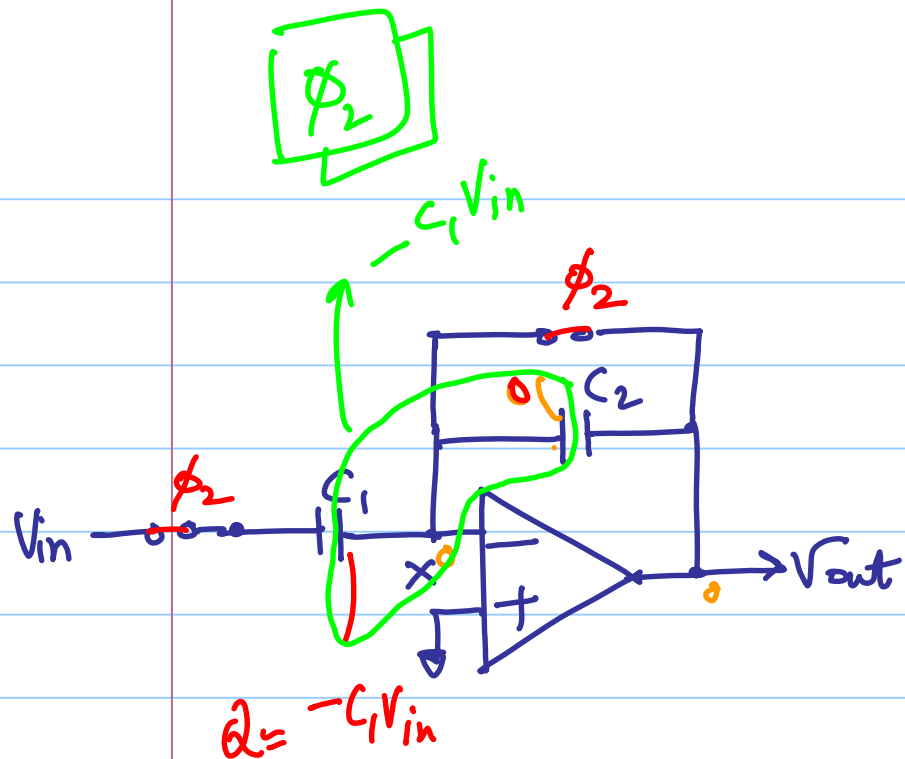

$$Q_x = -C_1 V_{in} = -C_2 V_{out}$$

$$\Rightarrow \frac{V_{out}}{V_{in}} = + \frac{C_1}{C_2}$$

S/H with amplification

* Same discussion for charge-injection techniques as in the S/H.

precision:

$$\left| \frac{V_{out}}{V_{in}} \right| \approx \frac{C_1}{C_2} \left[1 - \frac{1}{A\beta} \right]$$

$$\beta = \frac{C_2}{C_1 + C_2 + C_{in}} \stackrel{\Delta}{=} \frac{C_2}{C_1 + C_2}$$

Speed considerations :

$$C_{eq} = C_1 + C_{in}$$

$$\tau_{amp} = \frac{C_L C_{eq} + C_L C_2 + C_{eq} C_2}{g_m C_2}$$


Same as the S/H if C_{in} is replaced by $(C_{in} + C_1)$

C_2 & C_1

Precision Multiply X2 Circuit :

pipeline ADC


* previous circuit suffers from low β

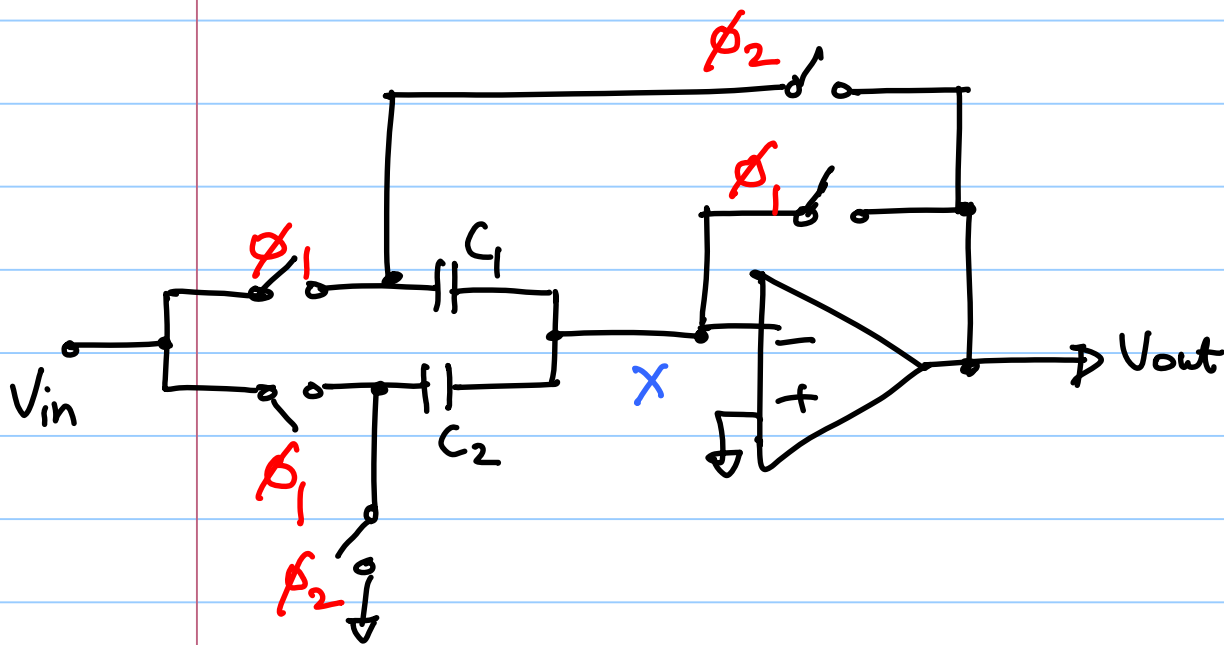

$$C_1 = C_2 = C$$

$$\frac{C_1}{C_2} = \frac{2C}{C}$$


Φ_1

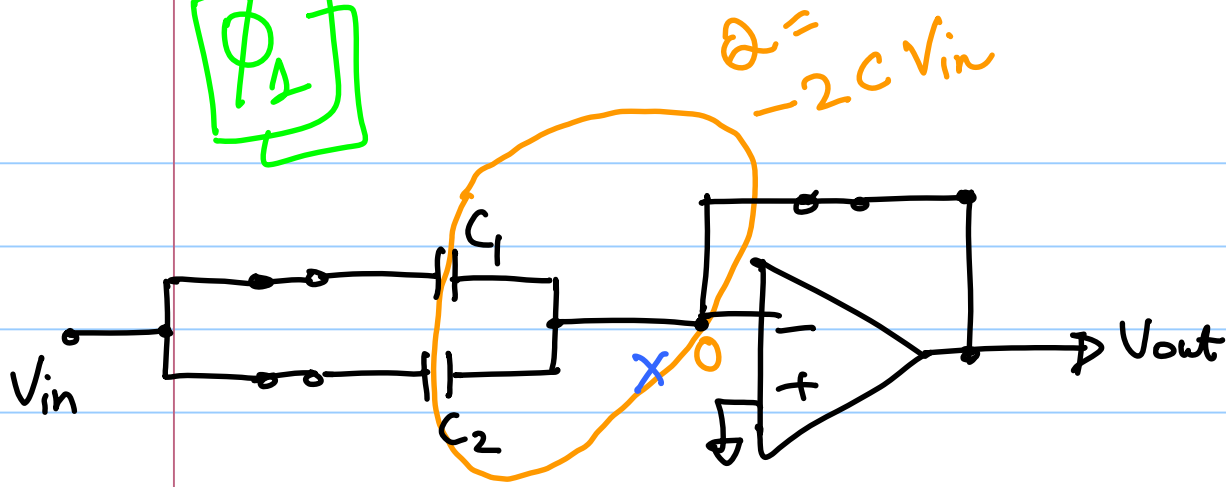

$$Q = -2C V_{in} = -C V_{out}$$

$$\Rightarrow \frac{V_{out}}{V_{in}} = 2$$

Φ_2

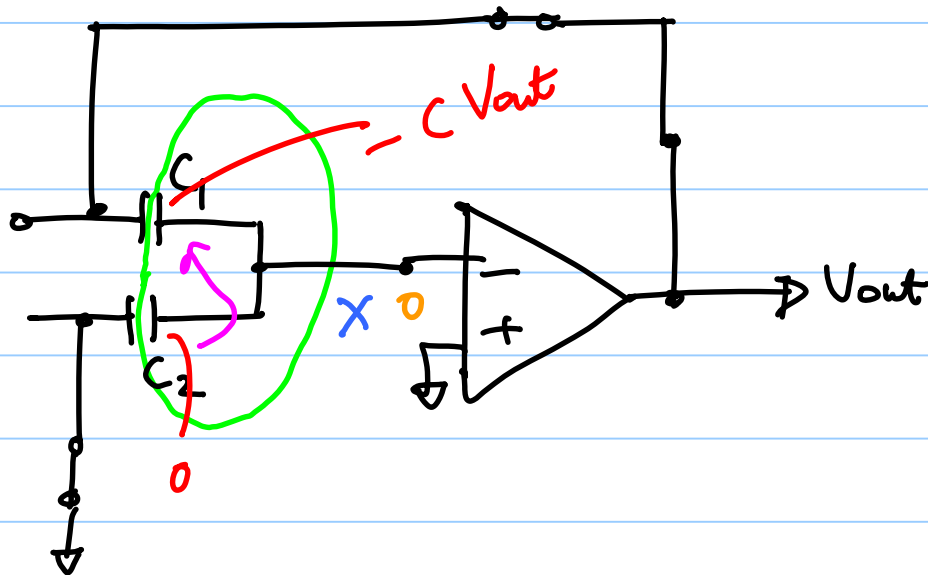

$$\beta = \frac{C_1}{C_1 + C_{in}}$$

