
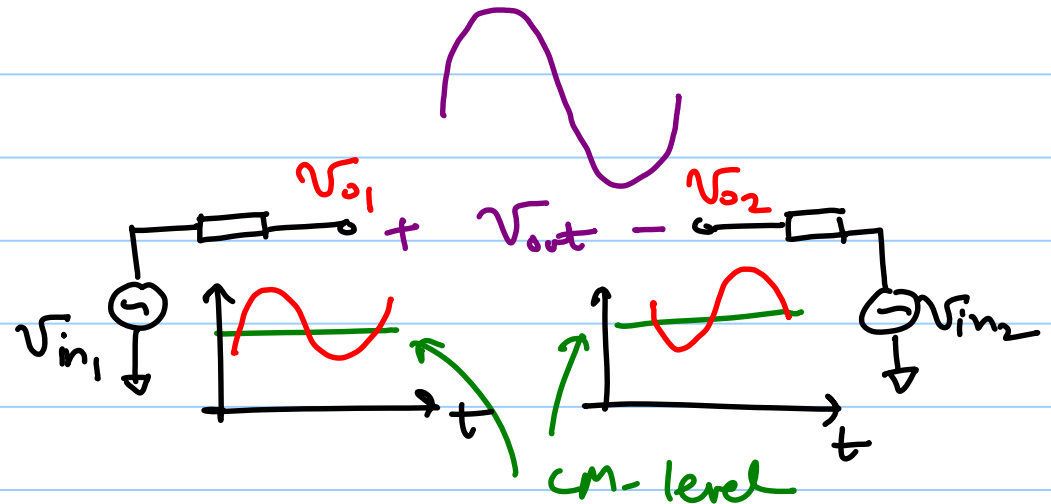


ECE 614 - Lecture 1

Note Title


8/26/2014

fully differential circuits:

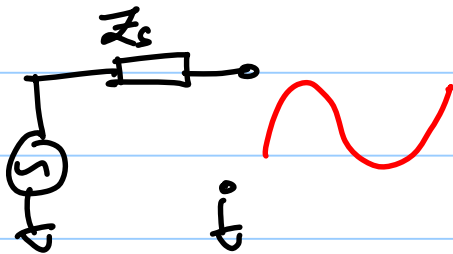

CM-level : $V_{cm} = \frac{V_{o1} + V_{o2}}{2} \leftarrow \text{Average}$

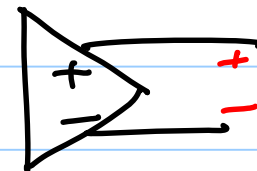differential signal: $V_d = V_{o1} - V_{o2} \leftarrow \text{Difference}$



(+) Rejects any CM disturbances

↳ V_{DD}/GND noise

↳ capacitively coupled noise

(+) $2\times$ signal swing


↳ 6 dB more signal power

only 3 dB increase in noise

$\Rightarrow$ 3 dB gain in SNR

(+)

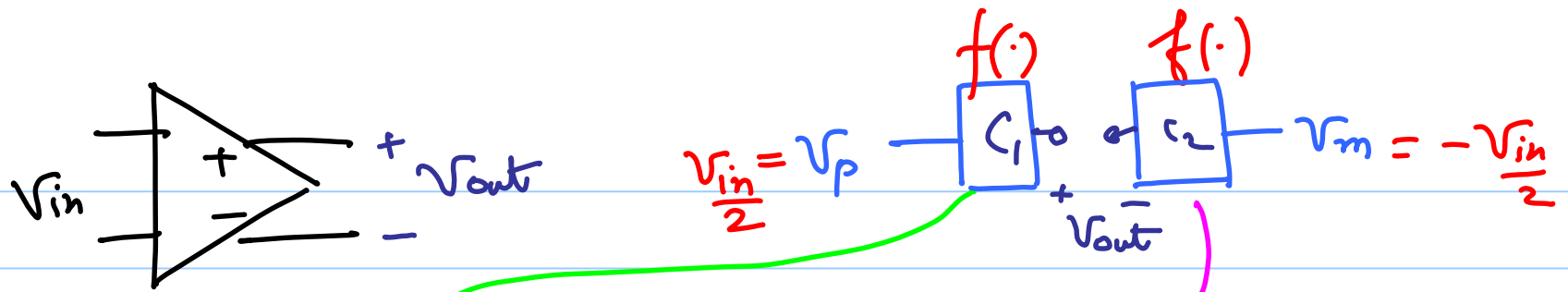get rid of even-order non-linearity.
rejects



Differential
circuit

$$V_{out} = f\left(\underbrace{\frac{V_{in}}{2}}_{V_{o1}}\right) - f\left(\underbrace{-\frac{V_{in}}{2}}_{V_{o2}}\right)$$


$$f_{odd}(x) = \frac{f(x) - f(-x)}{2} \leftarrow \text{odd } f^n \text{ doesn't have even order term}$$

$$= a_1 x + a_3 x^3 + a_5 x^5$$

$$f_{even}(x) = \frac{f(x) + f(-x)}{2} \Rightarrow \text{CM output level}$$

Half Circuit Analysis ← Razavi

$$V_L = V_{in1} - V_{in2}$$

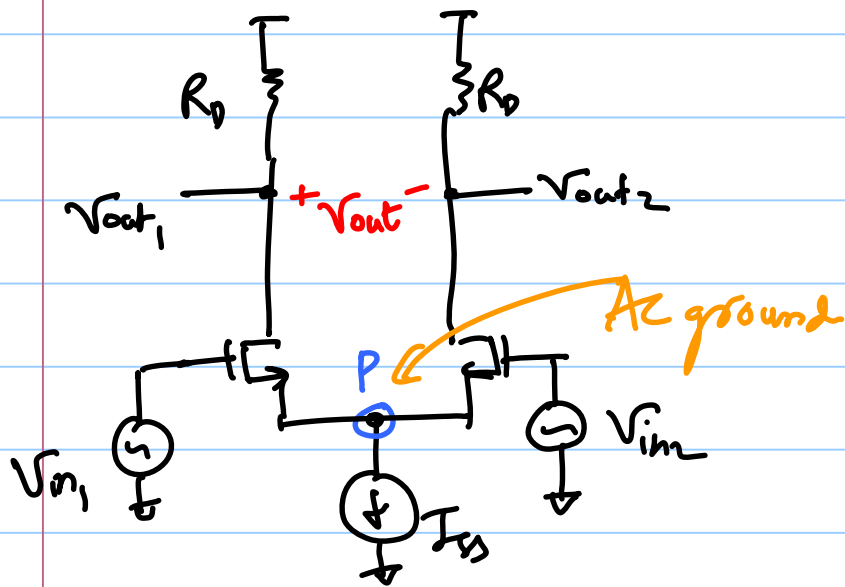


AC



Differential half-circuit

CM-Equiv. circuit



Differential half Circuits:

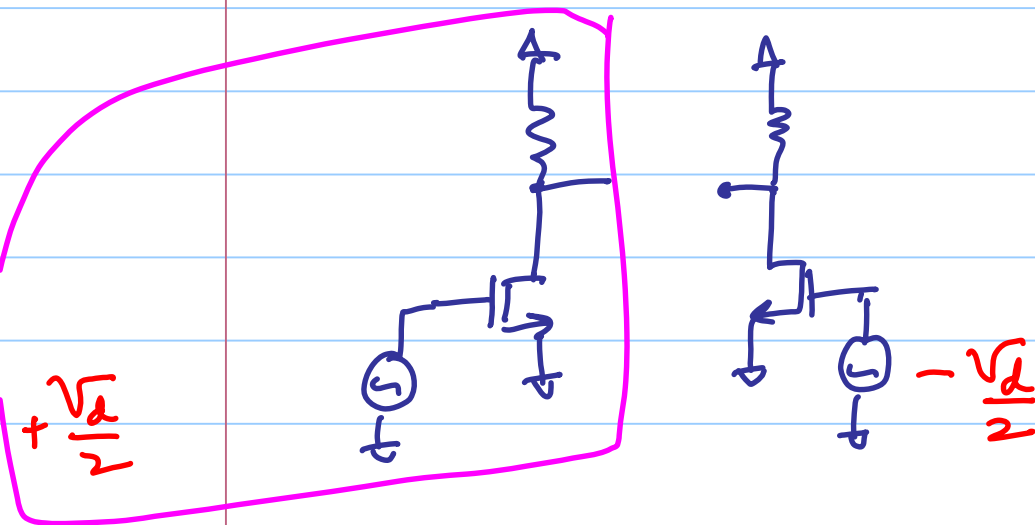



$$A_{DM} = -g_m(R_D || r_o)$$

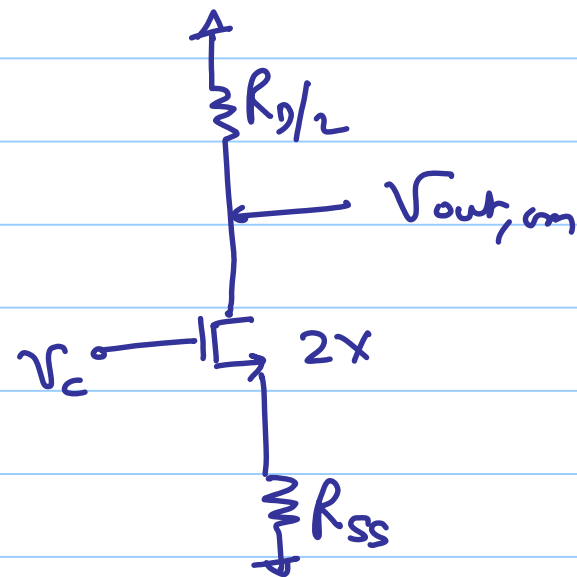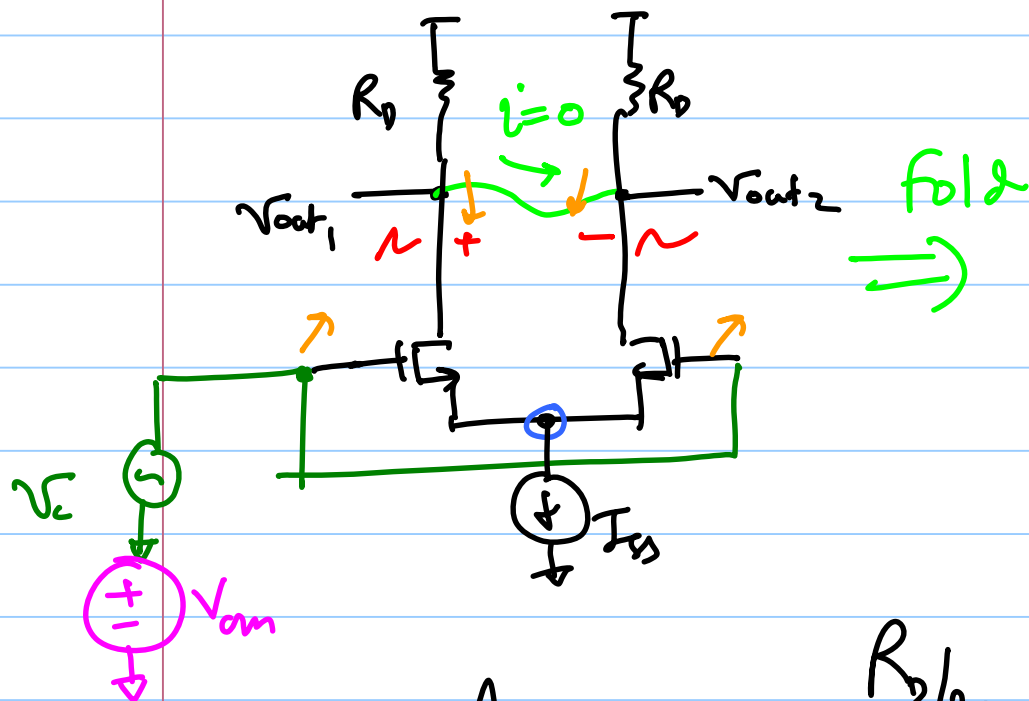

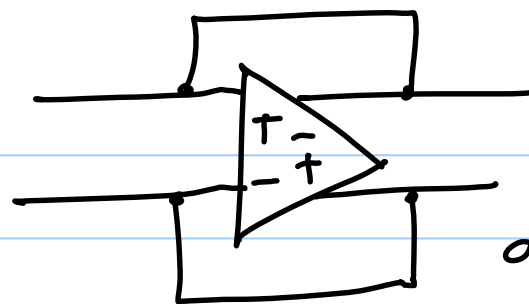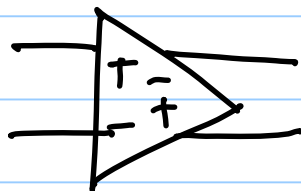
$$A_{v,cm} = - \frac{R_D/2}{\left(\frac{1}{2g_m} \right) + R_{SS}}$$




differential negative feedback

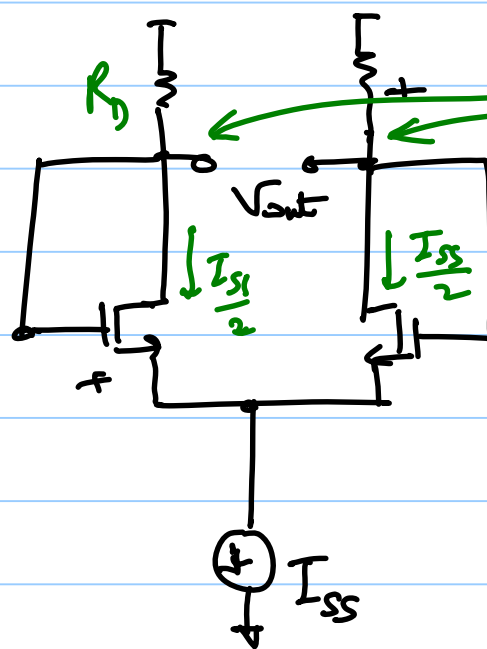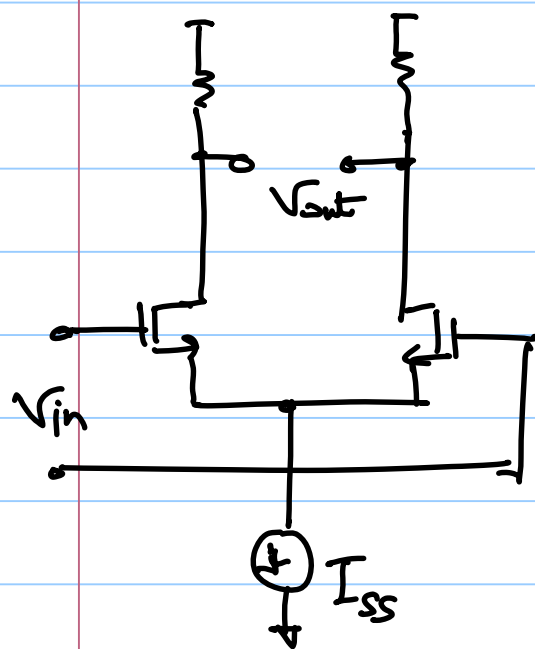

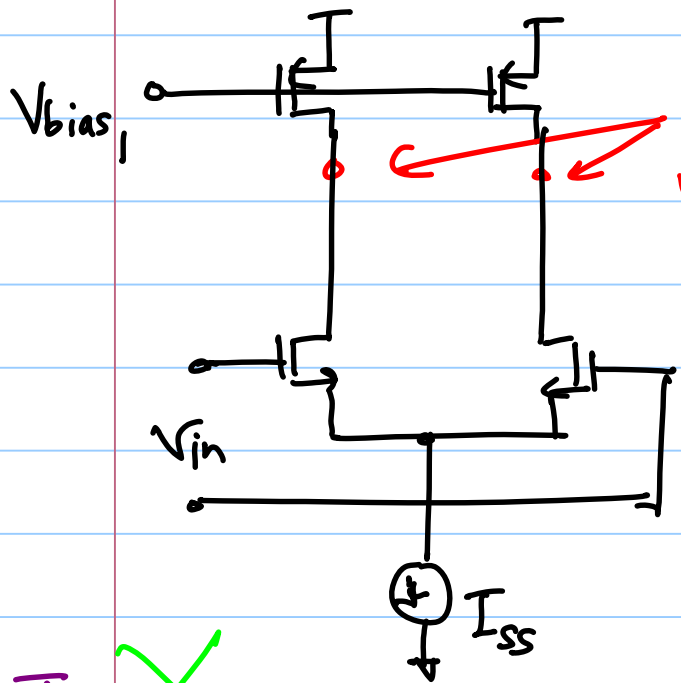cm - level
 $V_{DD} - \frac{I_{SS} R_D}{2}$




$V_{o,cm}$ is undefined

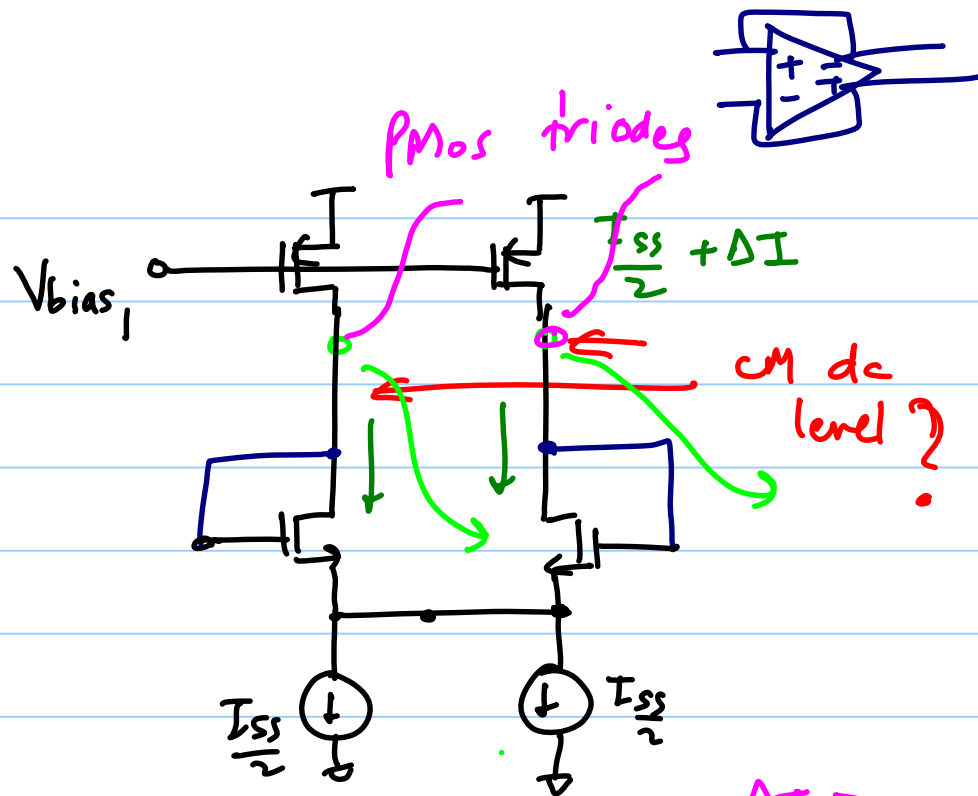


$\Delta I > 0$

$\Delta I < 0$

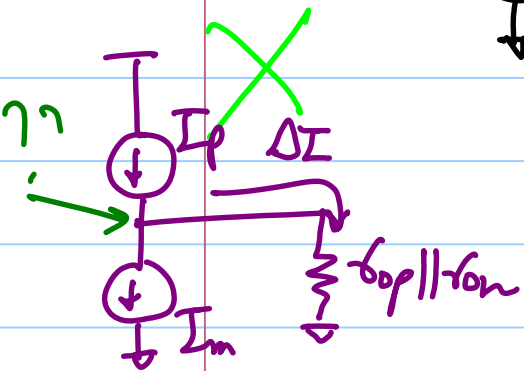Can never have two
"Independent" current sources fight to set
 a node voltage



CMFB loops

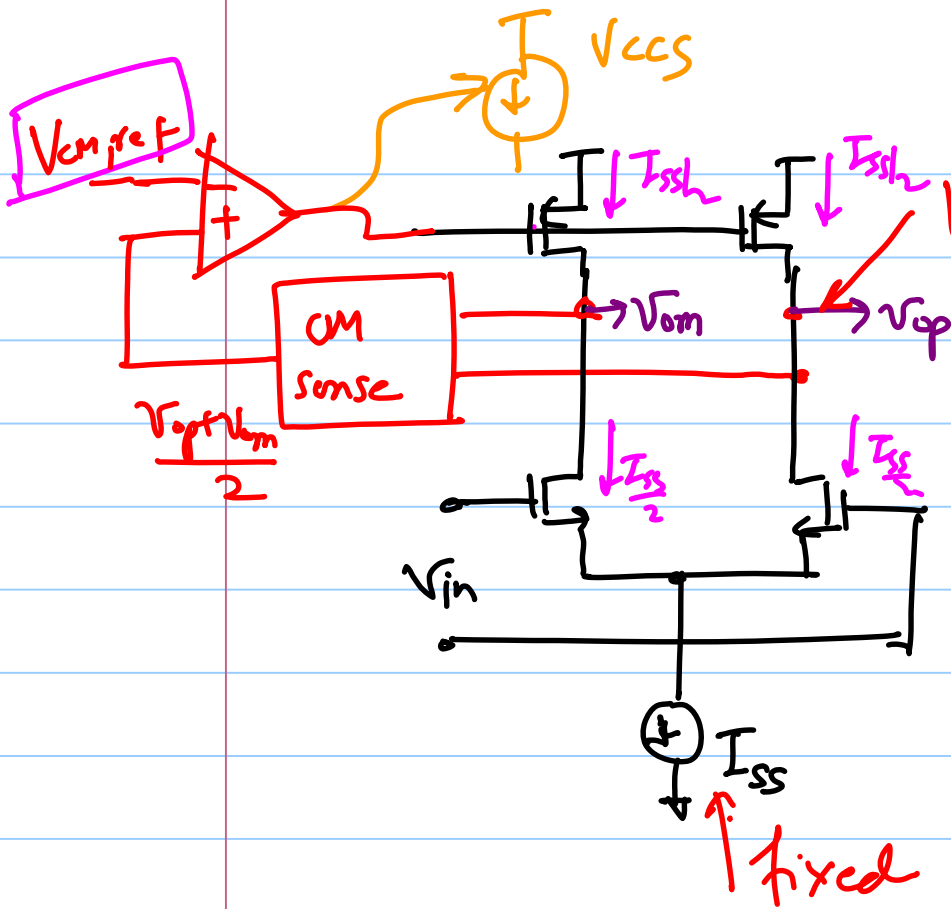

desired CM-level at the output


$\Delta I \rightarrow 0$ by the CMFB

Common-mode feedback loop

$\rightarrow V_{OCM} \rightarrow V_{CM,ref}$

& $I_{p,mos} = I_{n,mos}$

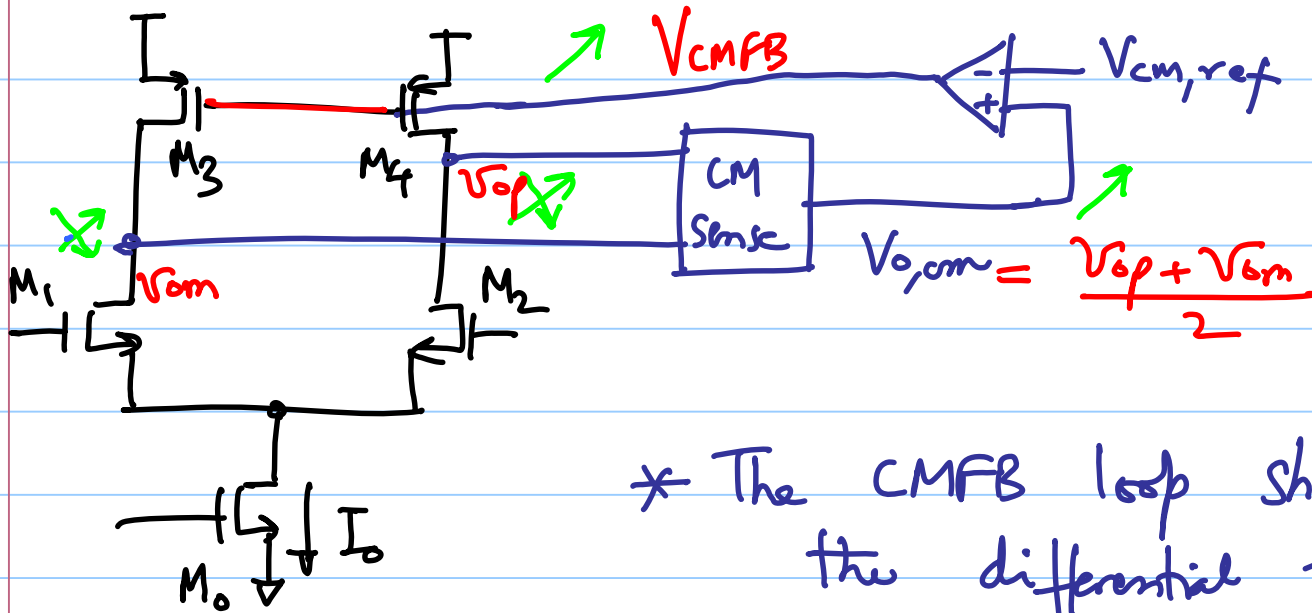-ve feedback loop to set the output CM-level.



- * The CMFB loop shouldn't disturb the differential picture

