
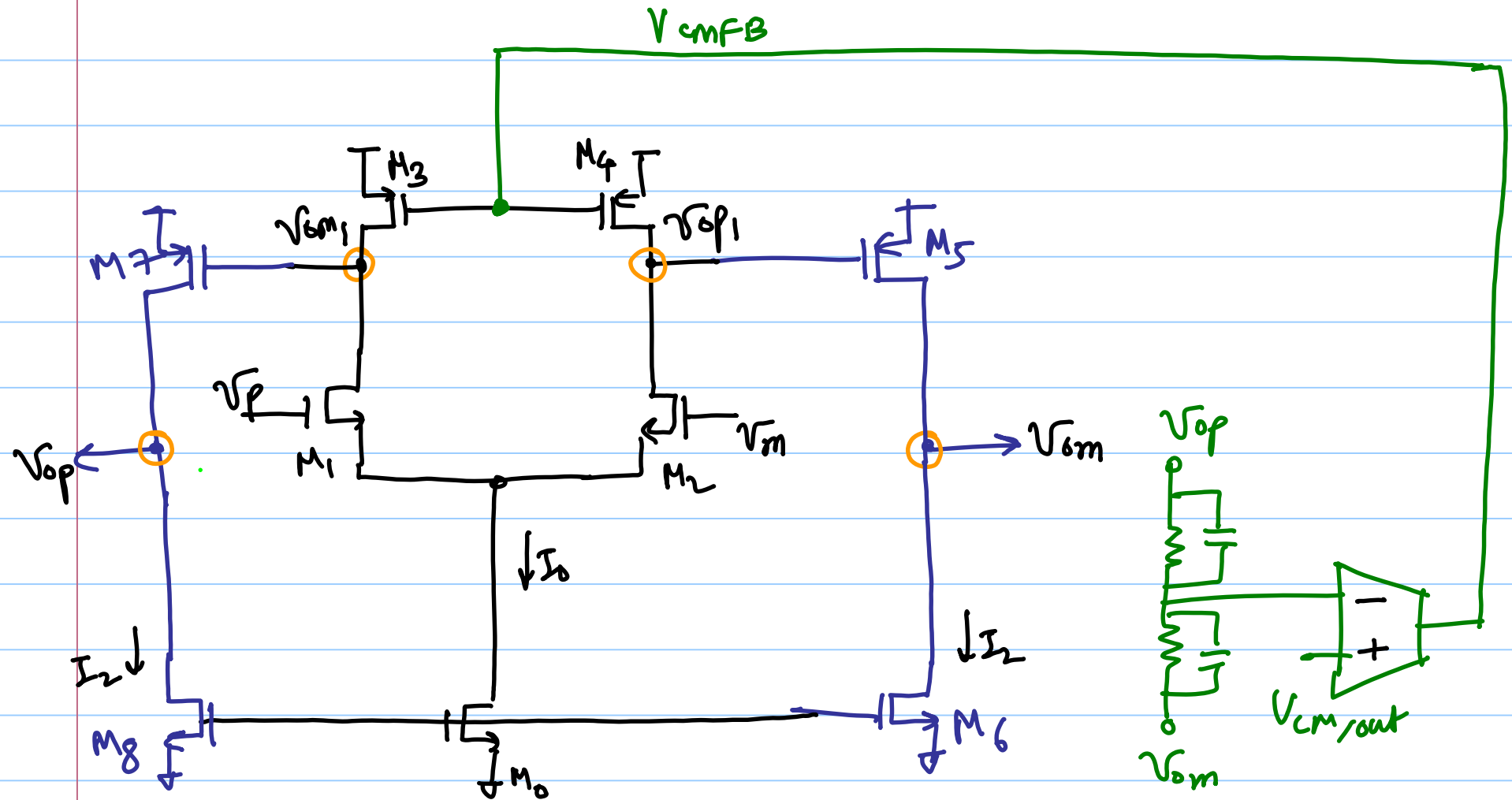


ECE 614 - Lecture 5


Note Title

9/9/2014

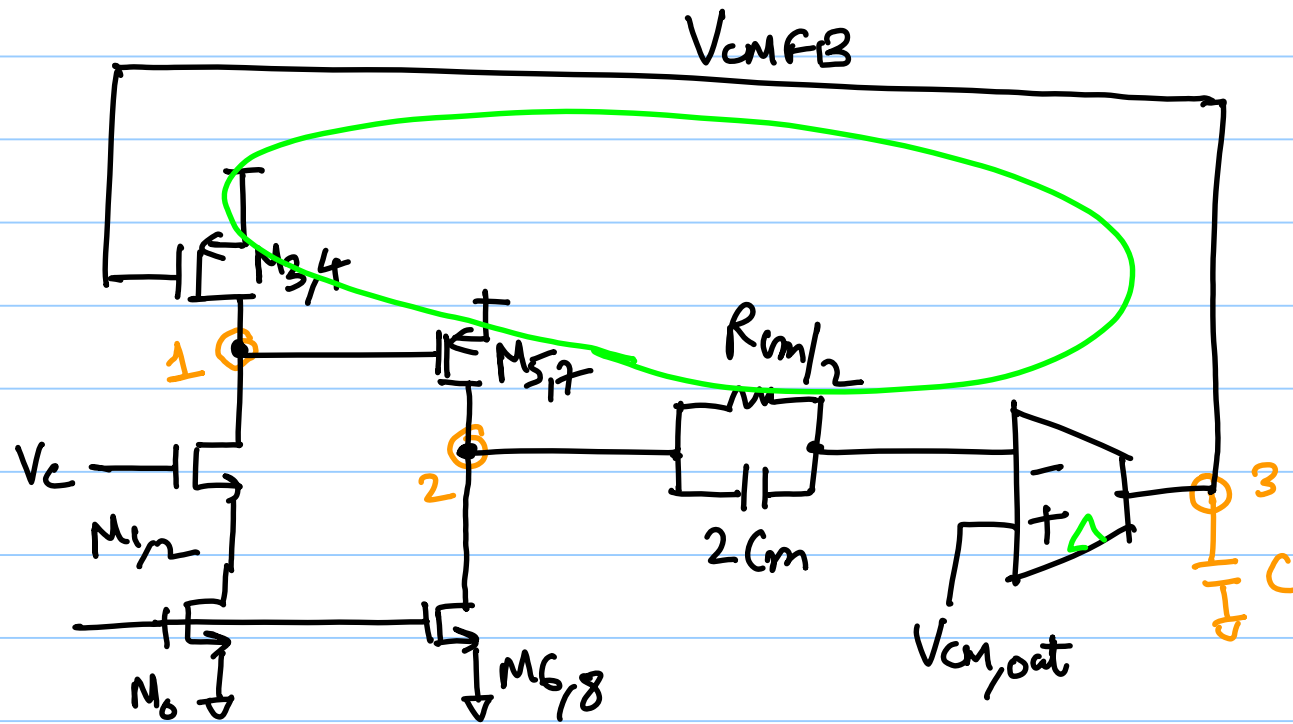



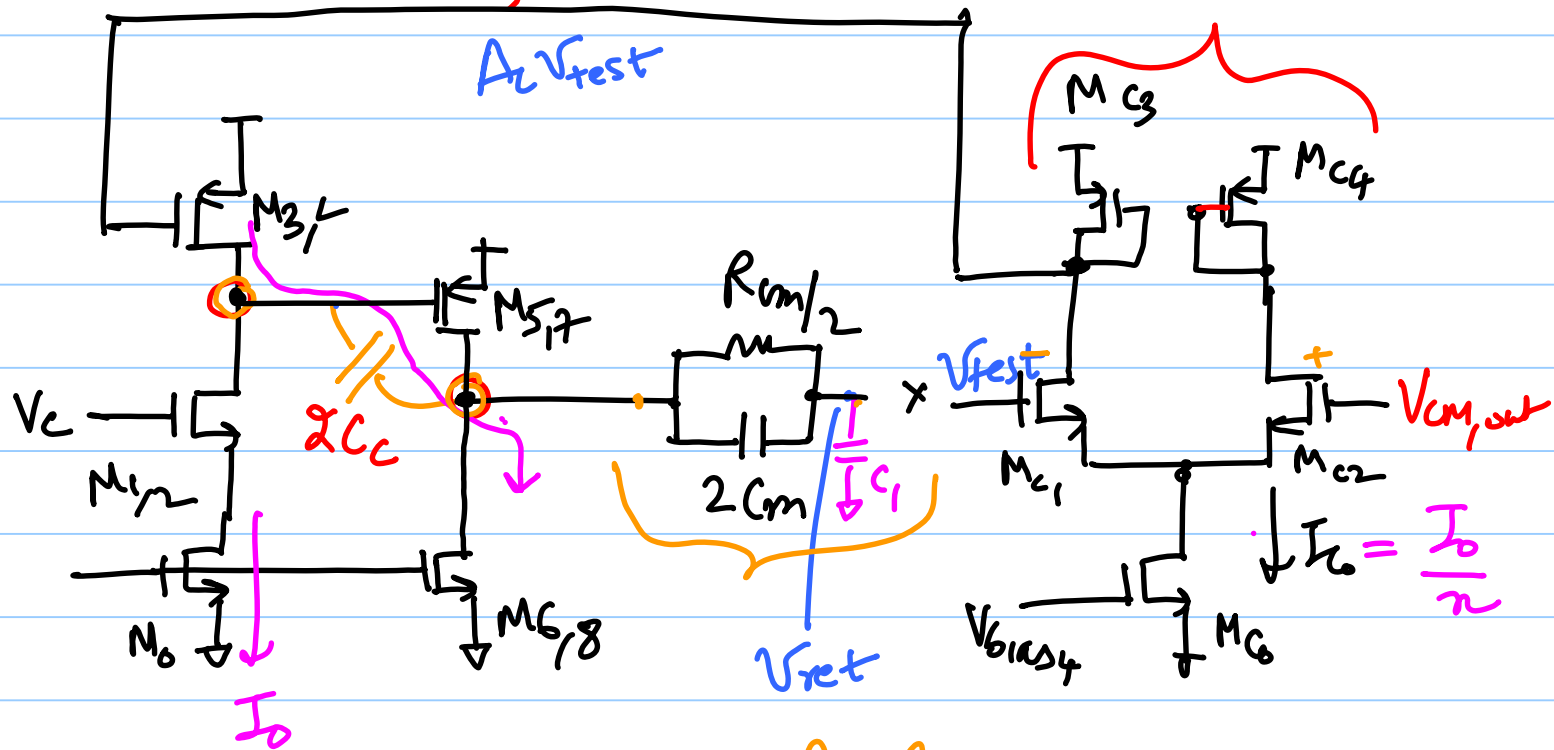Find open loop response gain $\Rightarrow A_v$
 $L(s)$



$$\frac{1 + s R_{cm} C_{cm}}{1 + s R_{cm} (C_{cm} + \frac{C_1}{2})} \approx 1$$

$$i = V_{test} A_v \cdot g_{m34} \leftarrow \text{this current flows through } 2C_c$$

$$V_{\text{refurn}} \simeq \frac{A_c g_{m3,4}}{s 2 C_c} \cdot V_{\text{test}}$$

$$L(s)_{\text{cm}} \simeq \frac{A_c g_{m3,4}}{2 s C_c}$$



$$\omega_{\text{cm}} = \frac{A_c g_{m3,4}}{2 C_c} = \frac{1}{2} \frac{g_{mc1}}{g_{mc3}} \times \frac{g_{m3,4}}{2 C_c}$$

$$= \frac{1}{2} \frac{g_{mc1}}{g_{mc3}} \times \frac{g_{m3}}{C_c}$$

$$= \frac{1}{2} \frac{g_{mc1}}{C_c} \left(\frac{g_{m3}}{g_{mc3}} \right) = \frac{1}{2} \frac{g_{mc1}}{C_c} \times n$$

$$= \frac{1}{2} \frac{g_{m1}}{C_c}$$

CM equivalent



$$g_{m3,4} = 2 g_{m3}$$


$$\frac{W_3}{W_{c3}} = n$$

→ W_{c3}

$$\omega_{u, \text{opamp}} = \frac{g_{m1}}{C_L} \quad \text{✗}$$

$$\omega_{u, \text{cm}} \leq \frac{1}{2} \cdot \frac{g_{m1}}{C_L}$$

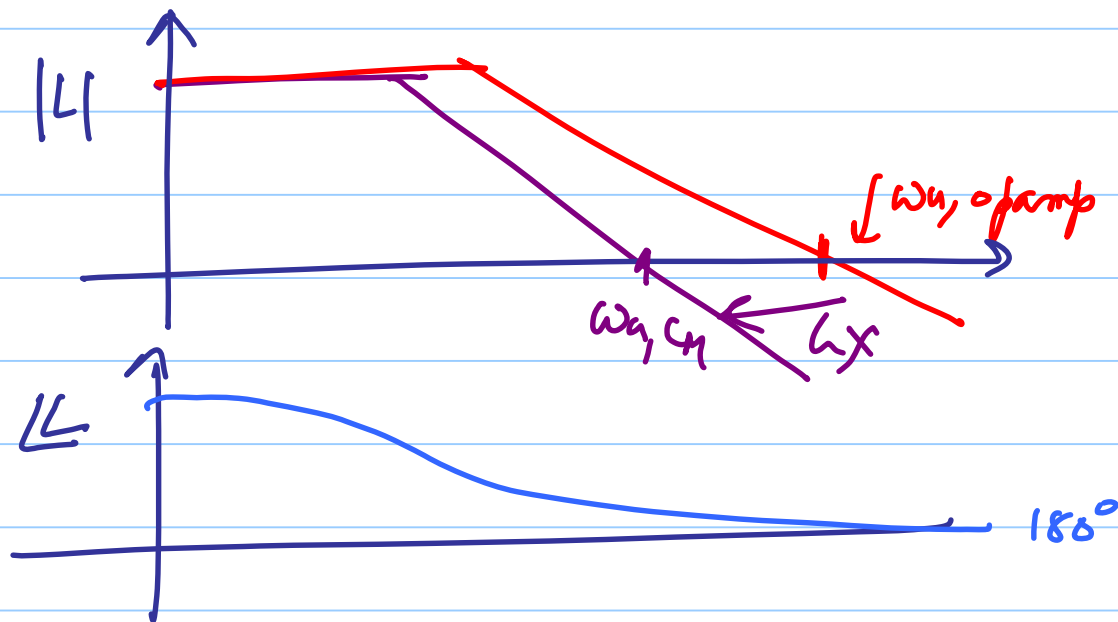
To ensure CMFB loop
stability
 $\omega_{u, \text{cm}} \leq \omega_{u, \text{opamp}}$



$$p_3 \approx \frac{g_{m_{c1,3}}}{C_x}$$


$$n = \frac{g_{m_{1,3}}}{g_{m_{c1,3}}}$$

$n \uparrow$
 $g_{m_{c1,3}} \downarrow$


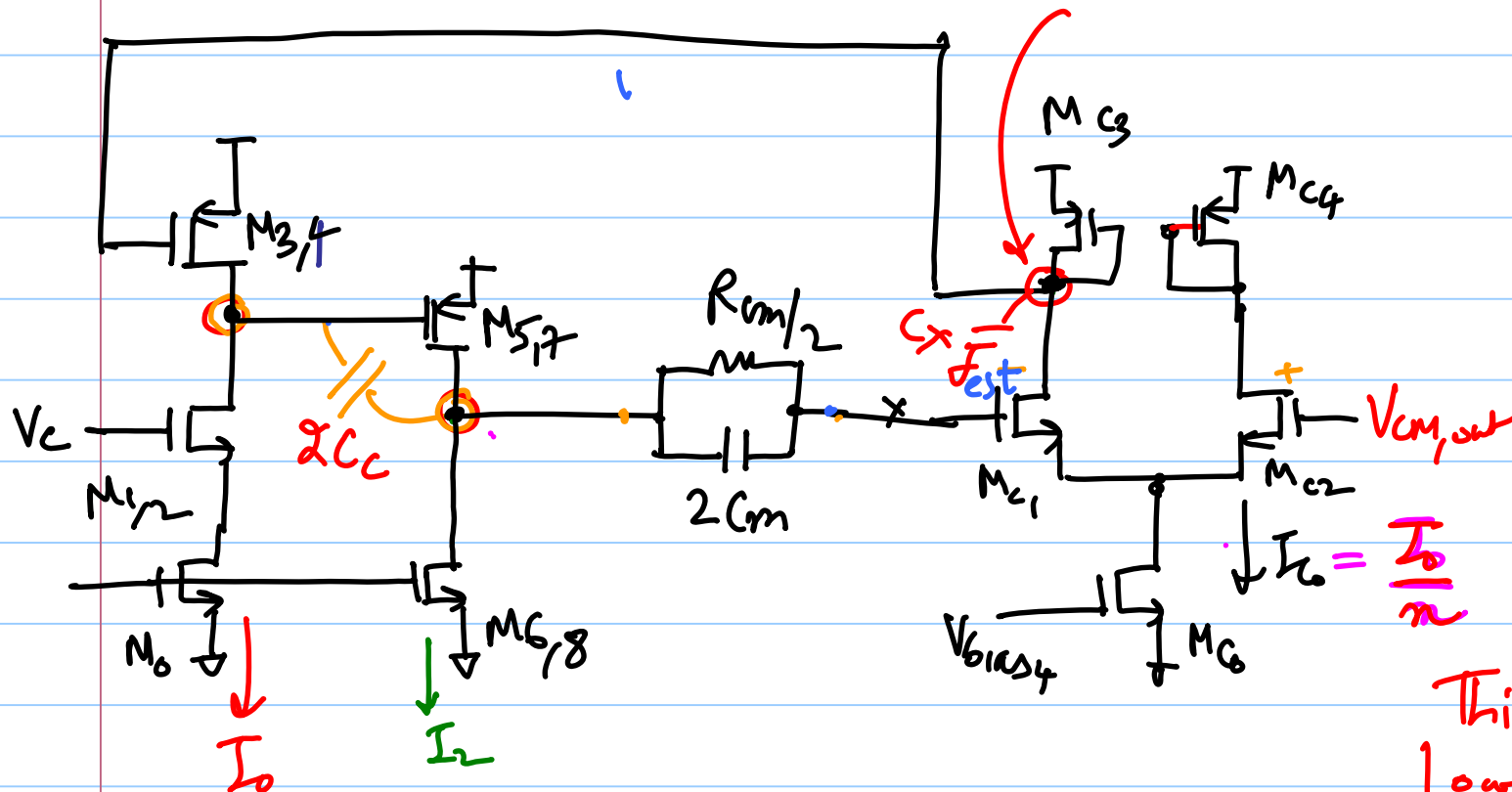


Third pole appears at lower frequency as $n \uparrow$
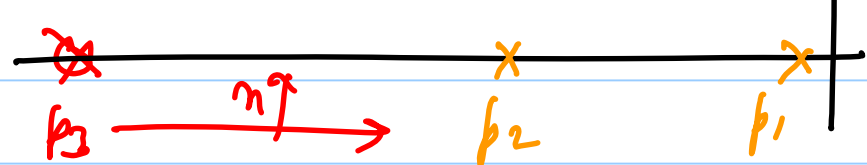
$$\frac{W_{3,4}}{I_0} = \frac{W_{5,7}}{I_2} = \frac{W_{3,4c}}{I_{0c}}$$



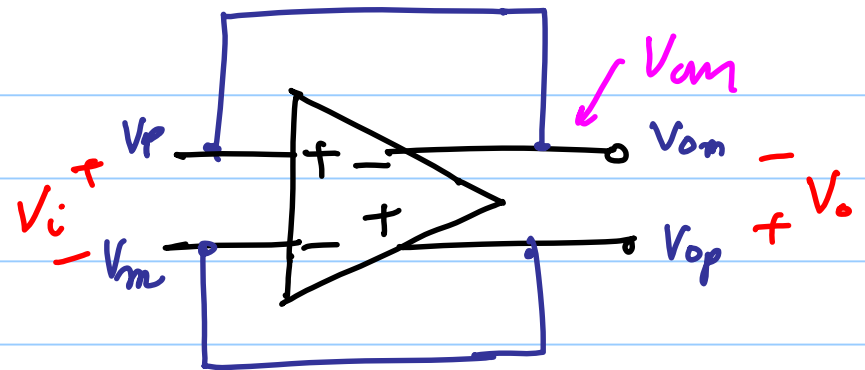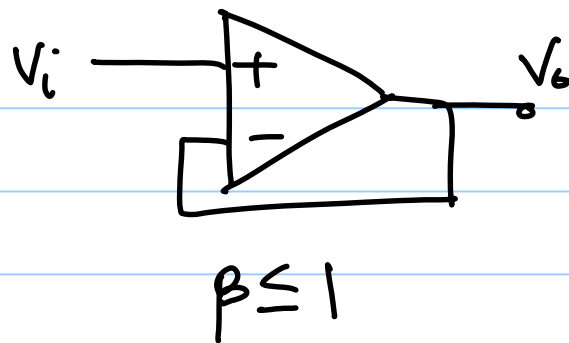Use same current density to avoid systematic offset.



$$(V_{op} - V_{om}) = A (V_p - V_m)$$


$$\forall \quad V_{op} = V_{om}$$

$$V_p = V_m$$


No unity gain configuration in
FD opamp

$\Rightarrow$ just shorts output and
inputs


Active-RC
filter

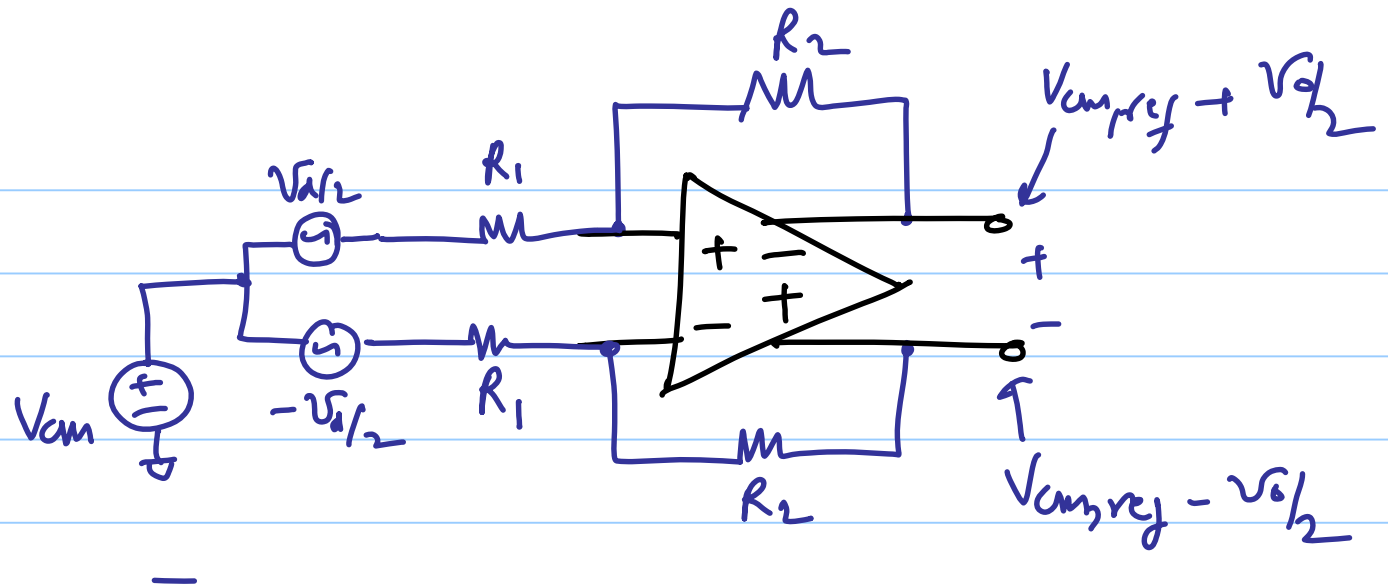


Integrator

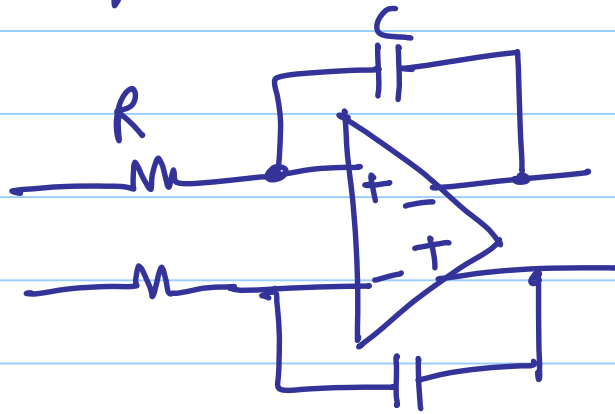
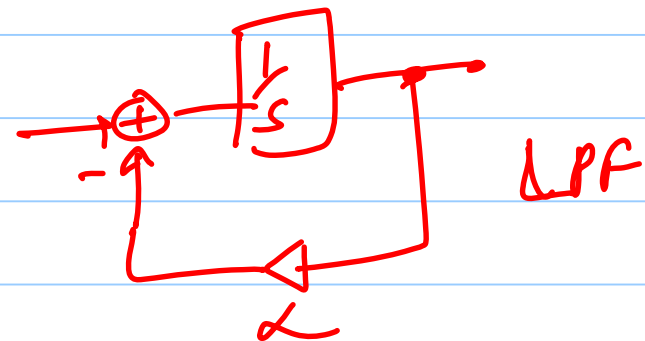
$$\beta \Rightarrow \frac{R_1}{R_1 + R_2}$$



CMFB using Triode Devices

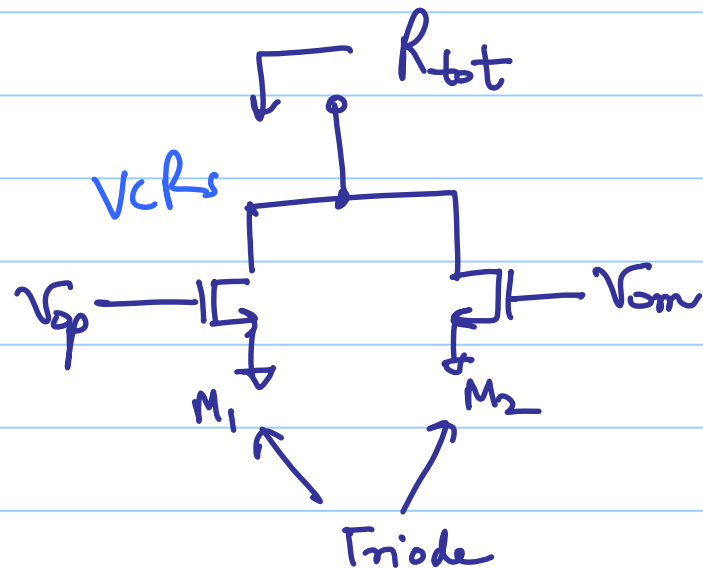


$$R_{tot} = R_{on1} \parallel R_{on2}$$




$$= \frac{1}{k_p n \frac{W}{L} (V_{op} - V_{THN})} \parallel \frac{1}{k_p n \frac{W}{L} (V_{om} - V_{THN})}$$

$$\approx \frac{1}{\underbrace{k_p n \frac{W}{L}}_{\beta_n} (V_{op} + V_{om} - 2V_{THN})}$$

$$G_{tot} = \frac{1}{R_{tot}} = g \beta_n \left(\underbrace{\frac{V_{op} + V_{om}}{2}}_{V_{cm, det}} - V_{THN} \right)$$

$$g_{tot} = f(V_{o, cm})$$

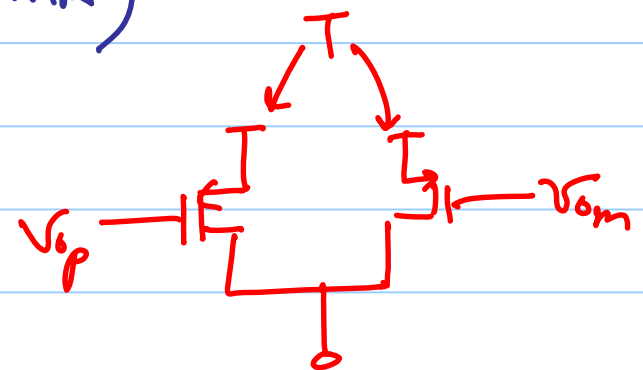

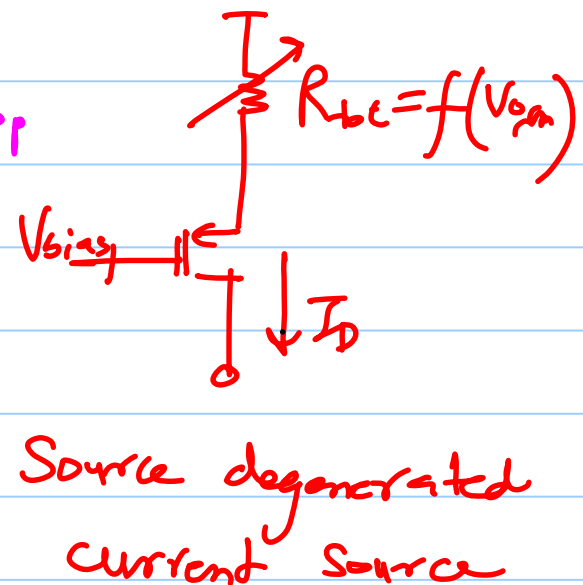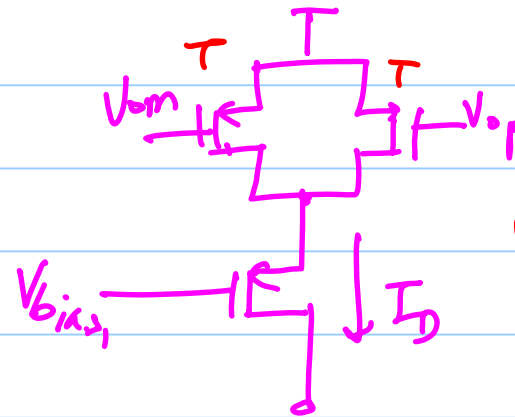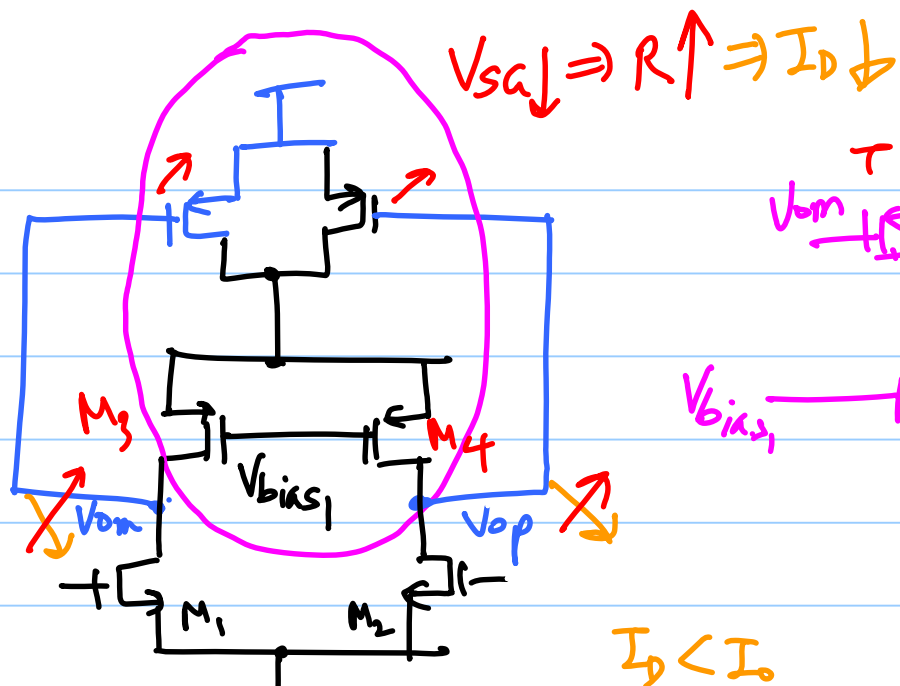

$$I_0 \leq \frac{V_{bias1} - V_{sa}}{R_{tot}}$$

(+) Not consuming additional current

(-) the output CM-level depends on the device parameters

$$V_{o,cm} = \left(\frac{V_{op} + V_{om}}{2} \right) = \frac{I_0}{k_{p,p} \left(\frac{W}{L} \right)_{3,4}} \cdot \frac{1}{(V_{DD} - V_{bias1} - V_{G3,4})} + \underline{V_{THP}}$$

See Razavi Section 9.6 for details.

Class AB Design :

push-pull state

